

EE210: Microelectronics-I


Lecture-27 :Common Collector Amplifier-3


Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur


Frequency Response

Frequency Response

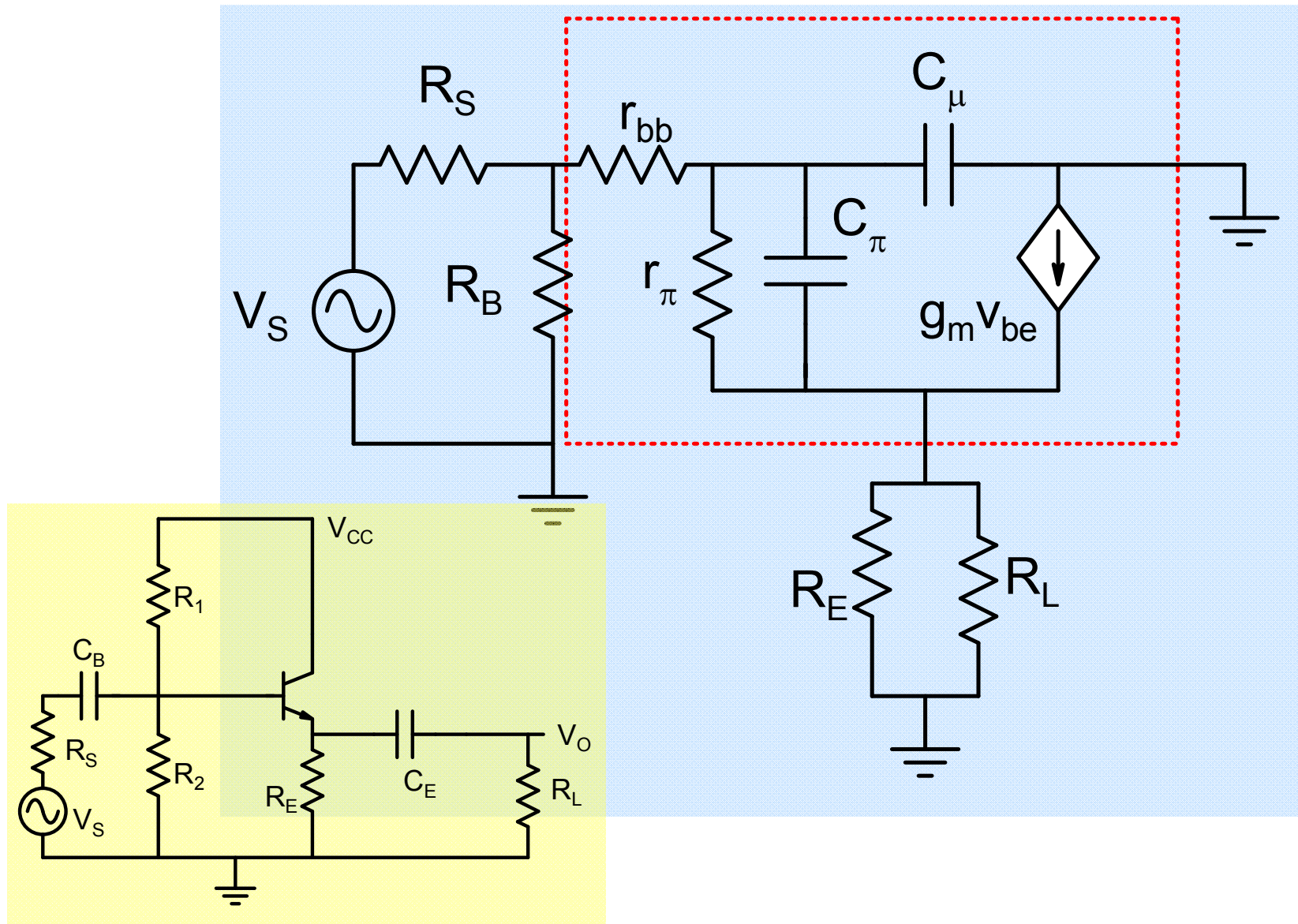

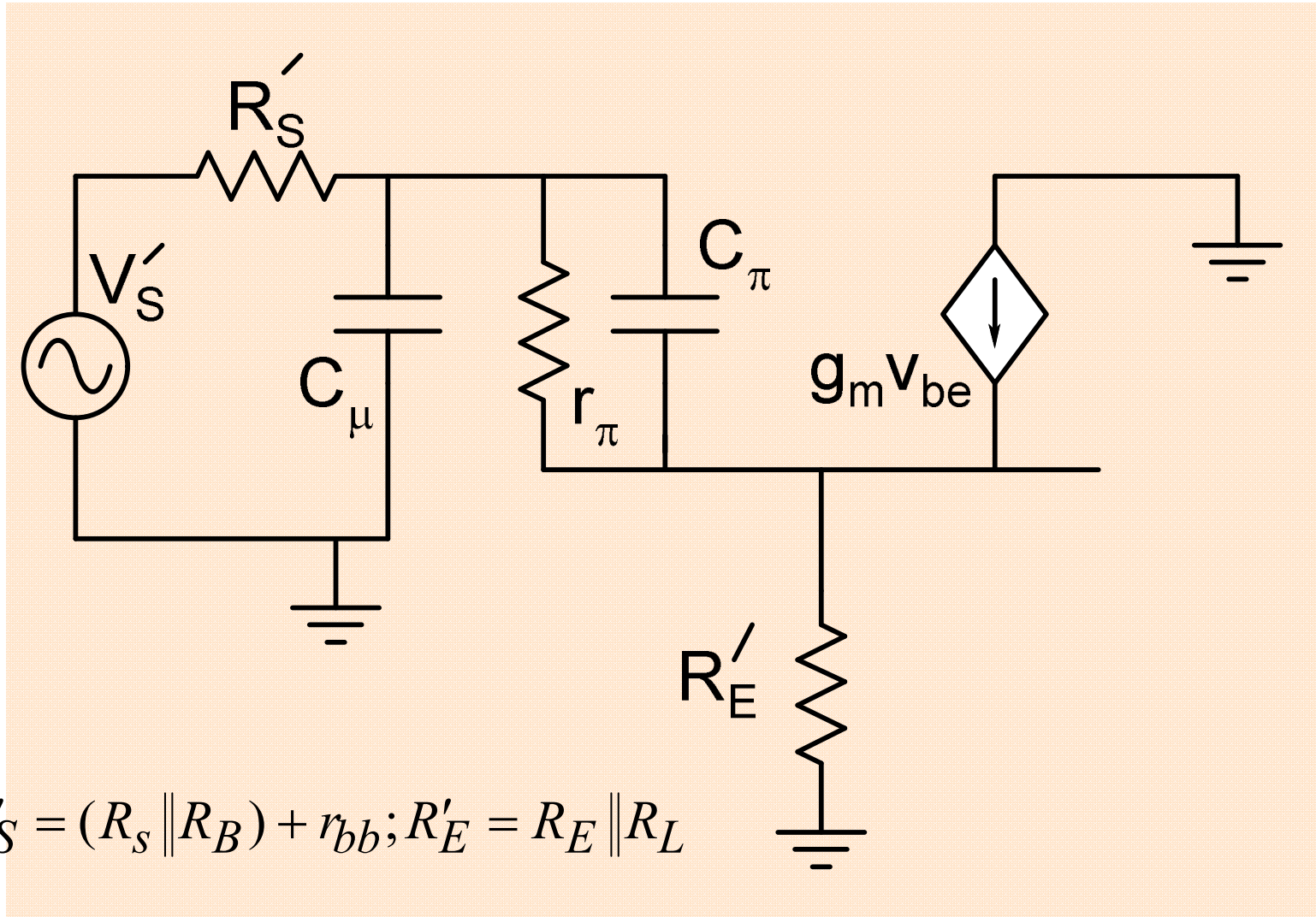

Open Circuit time constant approach

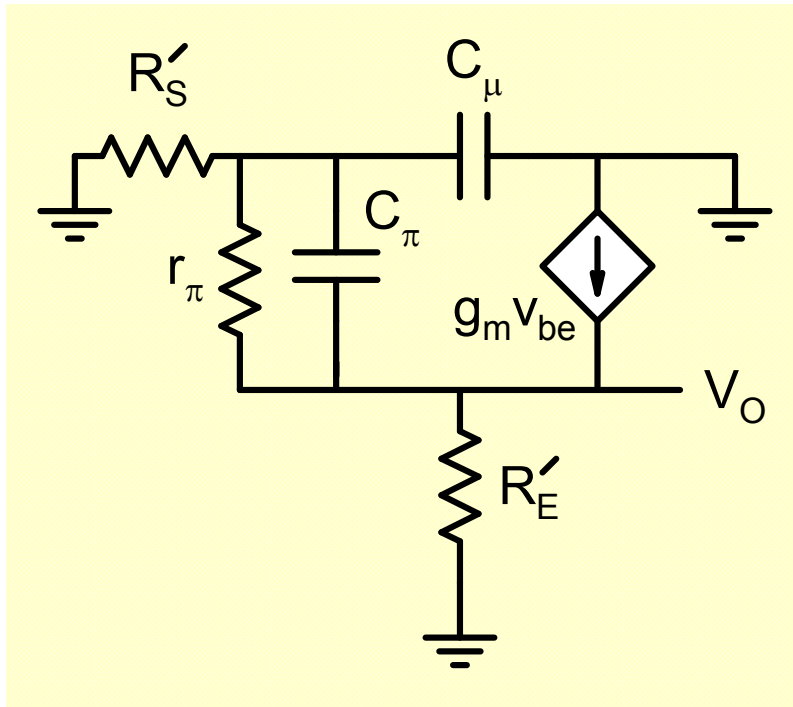


$$R_{\pi} = \frac{1 + \frac{R'_E}{R'_S}}{1 + \frac{g_m R'_E}{1 + \frac{R'_S}{r_{\pi}}}} \times (R'_S \parallel r_{\pi})$$

$$\cong \frac{1}{g_m} \text{ as } R'_E \rightarrow \infty$$

$$R_{\mu} = R'_s \left(1 - \frac{R'_S}{r_{\pi} + R'_S + (1 + \beta)R'_E} \right)$$

$$\cong R'_s \text{ as } R_E \rightarrow \infty$$
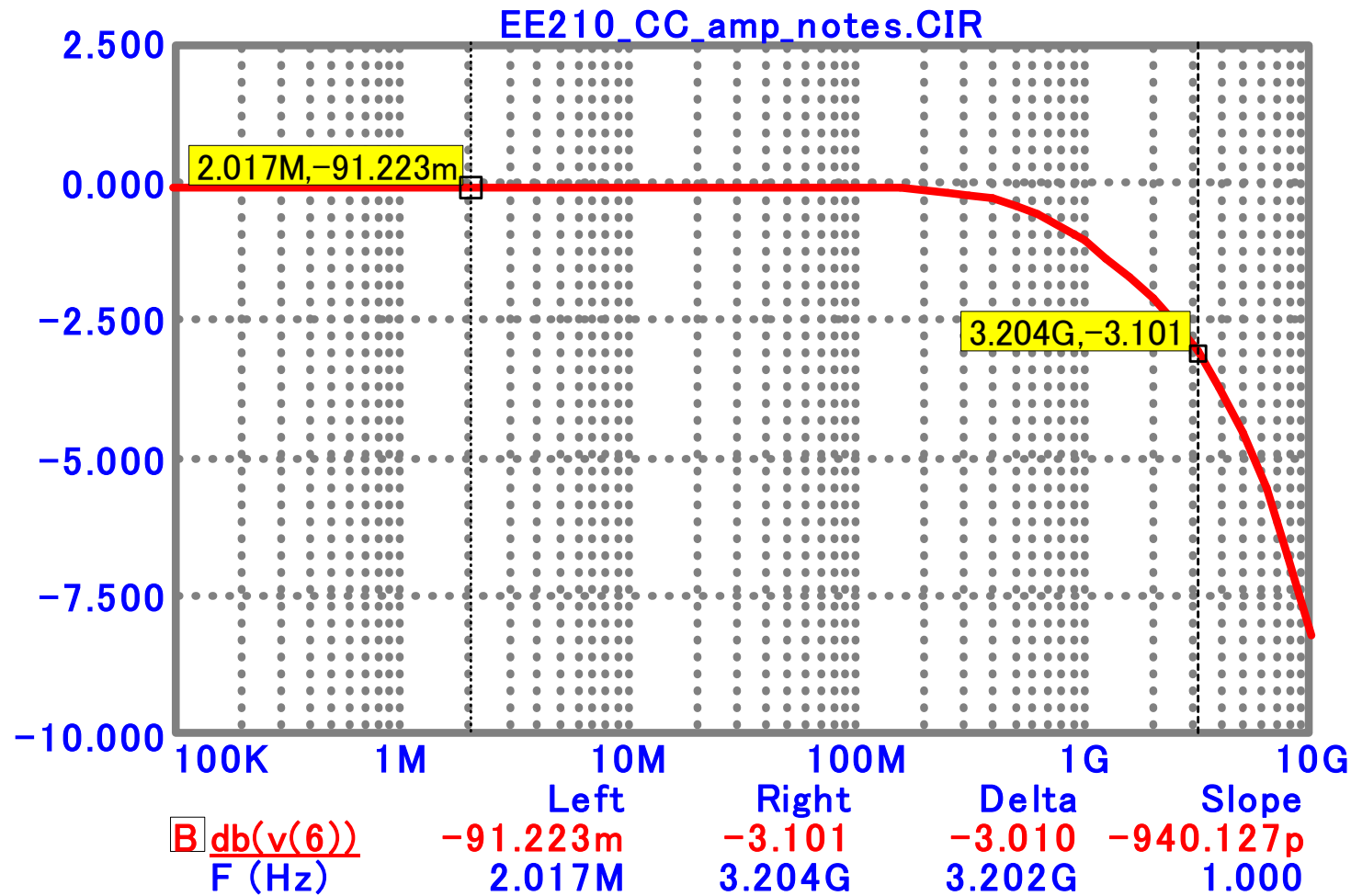
$$f_H \cong \frac{1}{2\pi \times \left(R'_S C_{\mu} + \frac{C_{\pi}}{g_m} \right)} ?$$



simulated is $\sim 3\text{GHz}$ while $f_H \cong \frac{1}{2\pi \times (r_{bb}C_\mu + \frac{C_\pi}{g_m})} = 126\text{MHz}$

Why is actual 3dB frequency so much higher?

$$H(s) \cong \frac{1 + \frac{C_{\pi}}{g_m} s}{1 + (R'_S C_{\mu} + \frac{C_{\pi}}{g_m})s + \frac{R'_S}{g_m} C_{\pi} C_{\mu} s^2}$$


$$f_H \cong \frac{1}{2\pi \times (R'_S C_{\mu} + \frac{C_{\pi}}{g_m})}$$

Besides the pole, there is a zero as well which is very close to the pole resulting in a cancellation effect !

$$f_Z \cong \frac{1}{2\pi \times \frac{C_{\pi}}{g_m}} = 156 \text{ MHz}$$


$$f_H \cong \frac{1}{2\pi \times R'_S C_{\mu}} = 4.5 \text{ GHz}$$

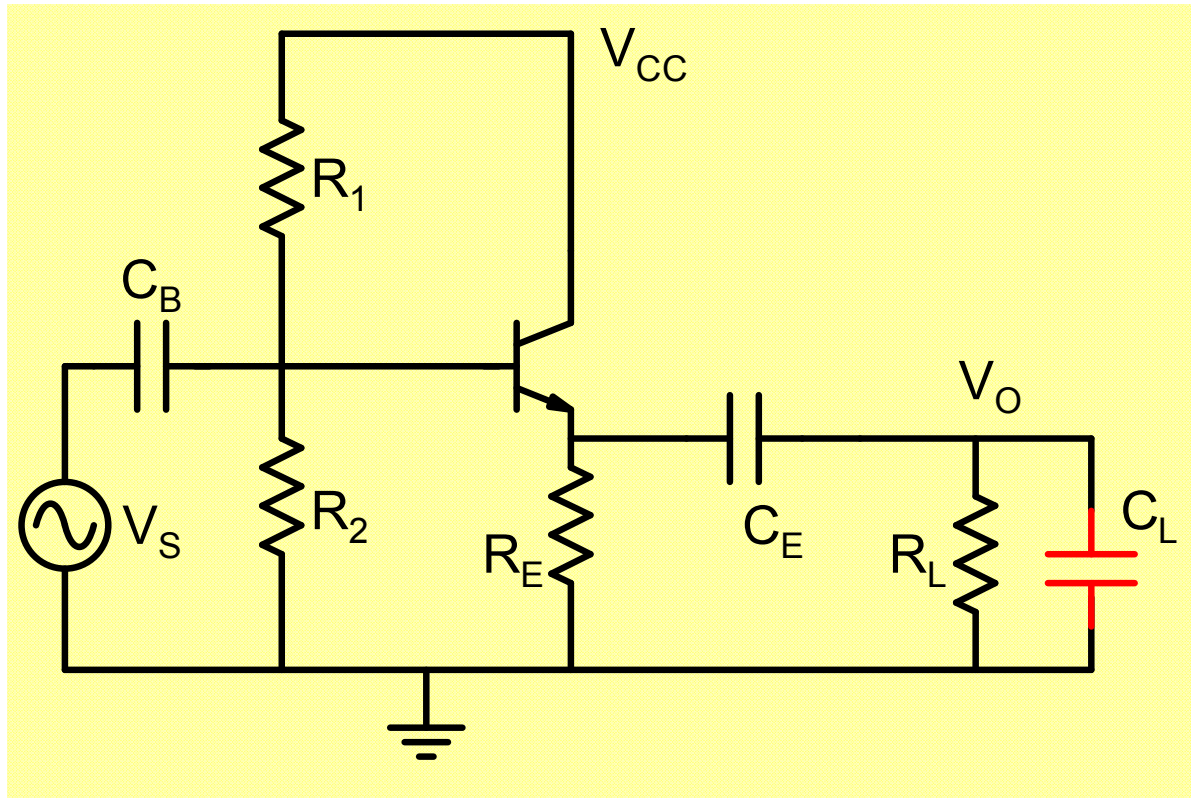Often the frequency response is dominated by the load capacitance




$$f_H \cong \frac{1}{2\pi \times (r_{bb}C_\mu + \frac{C_\pi}{g_m} + R_O \parallel R_L \times C_L)}$$


Output Resistance: Frequency response

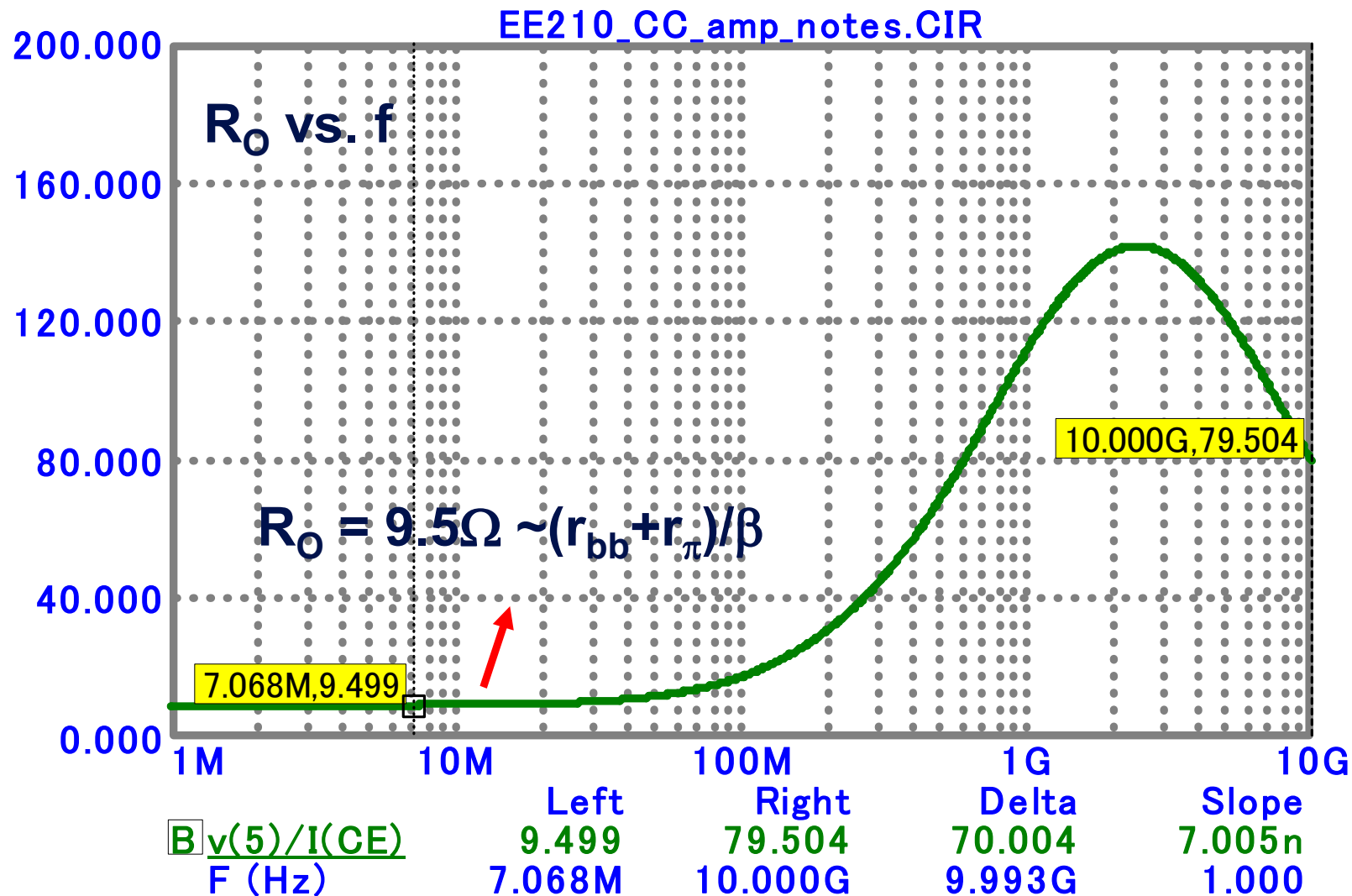

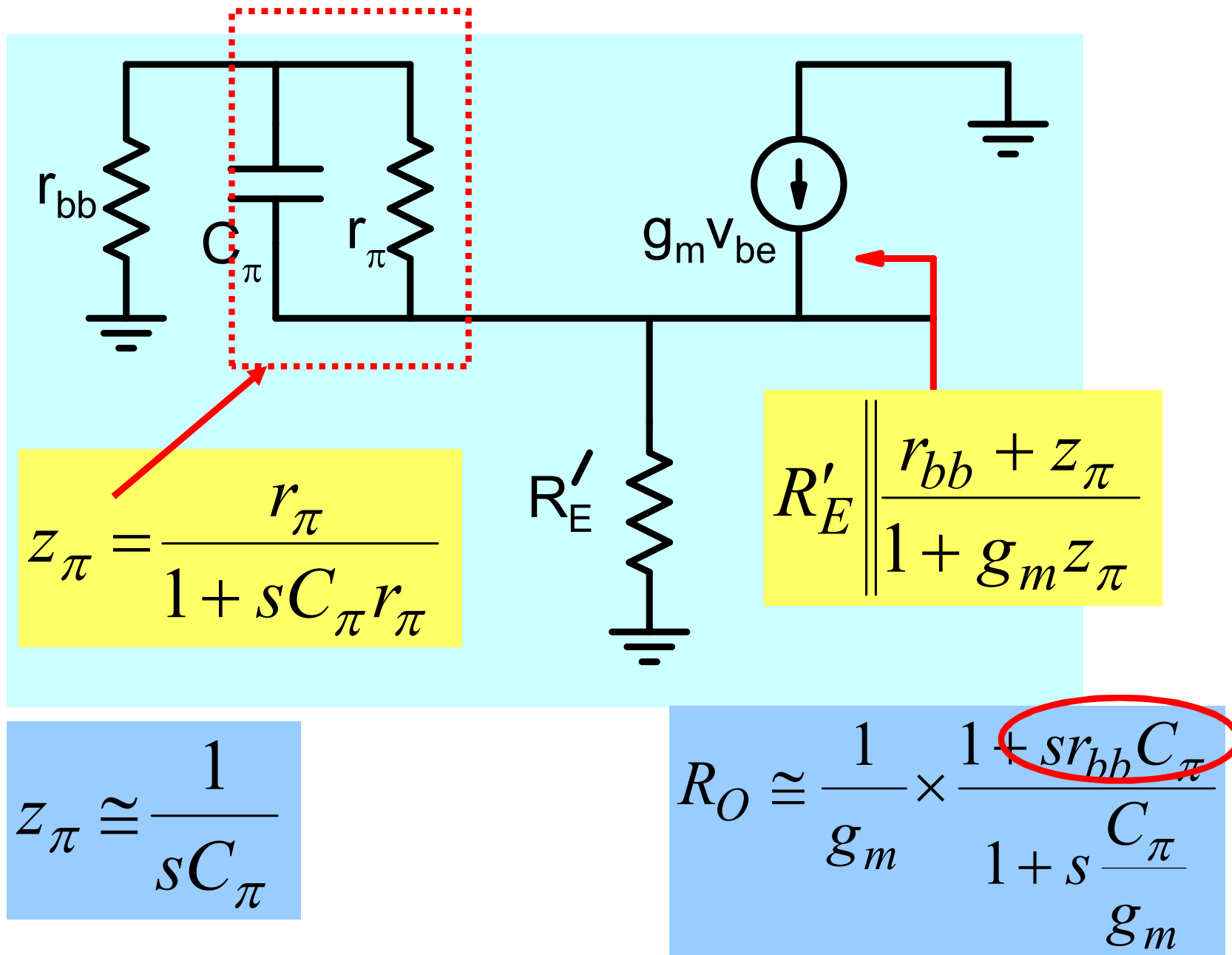
Behavior is inductive at higher frequencies



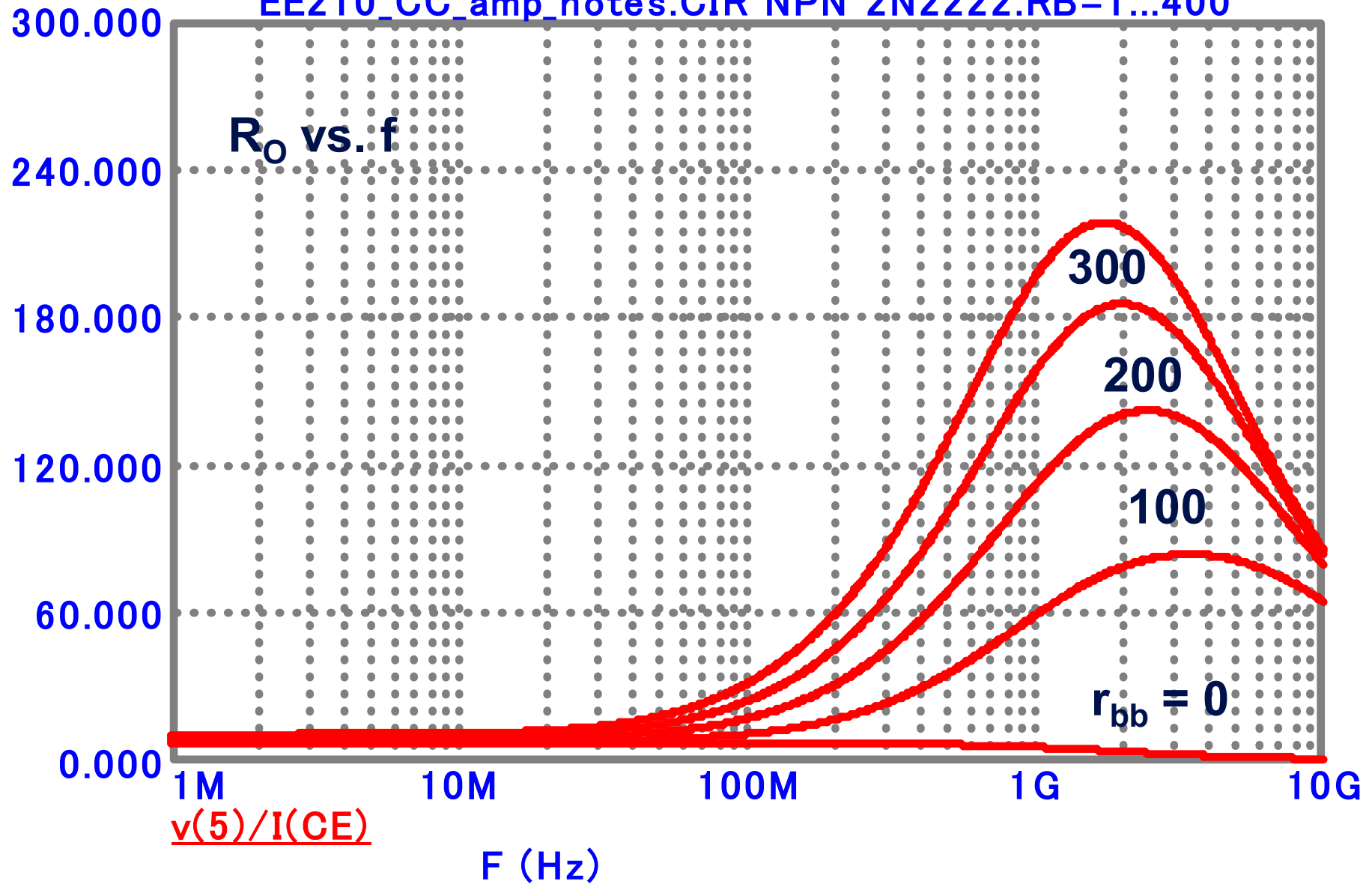EE210_CC_amp_notes.CIR NPN 2N2222.RB=1...400



Summary

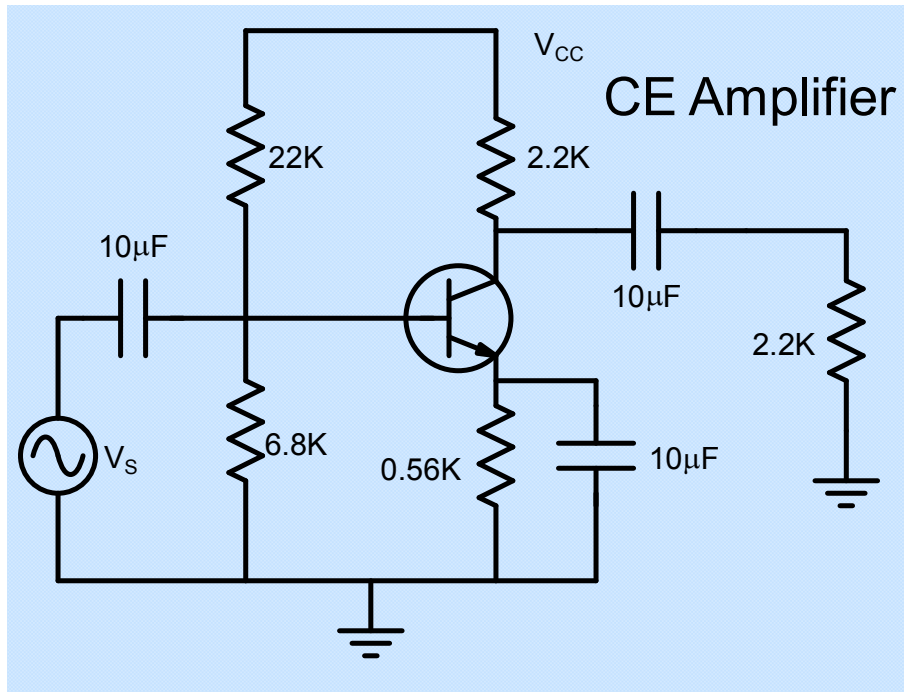


$$\beta = 100$$

$$I_{CQ} = 3.4mA; V_{CEQ} = 2.57V$$

$$A_V = 110.7; R_{in} = 0.82K; R_O = 2.2K$$

$$v_{om} = 0.39V @ THD = 1.9\%$$

$$f_L = 1.67kHz; f_H = 5.8MHz$$

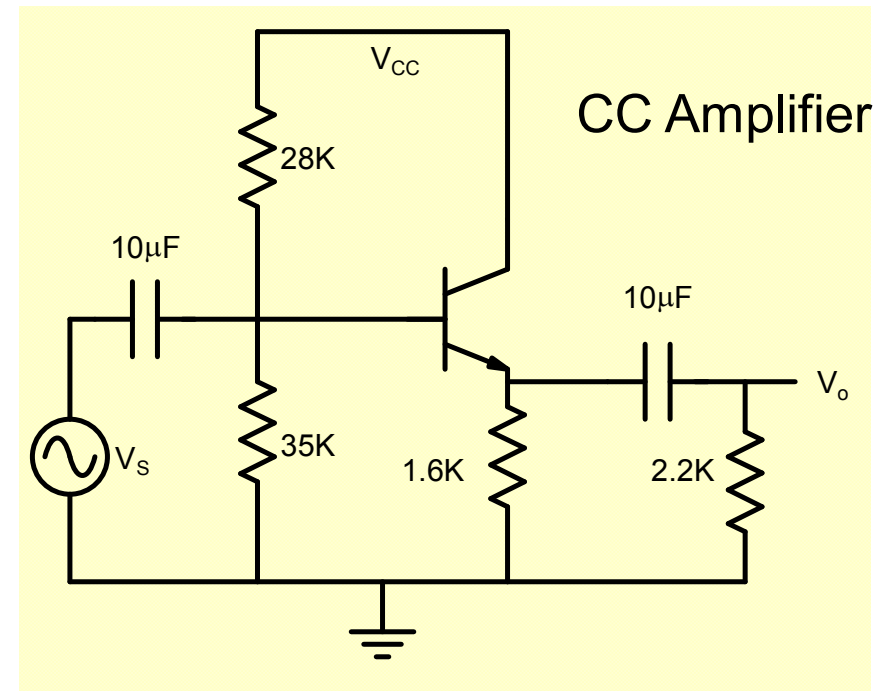

$$\beta = 100$$


$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V$$

$$A_V = 0.99; R_{in} = 13.4K (R_B = 16k); R_O = 9.5\Omega$$

$$v_{om} = 3V @ THD = 0.5\%$$

$$f_L = 7.6Hz; f_H = 3.1GHz$$


Summary

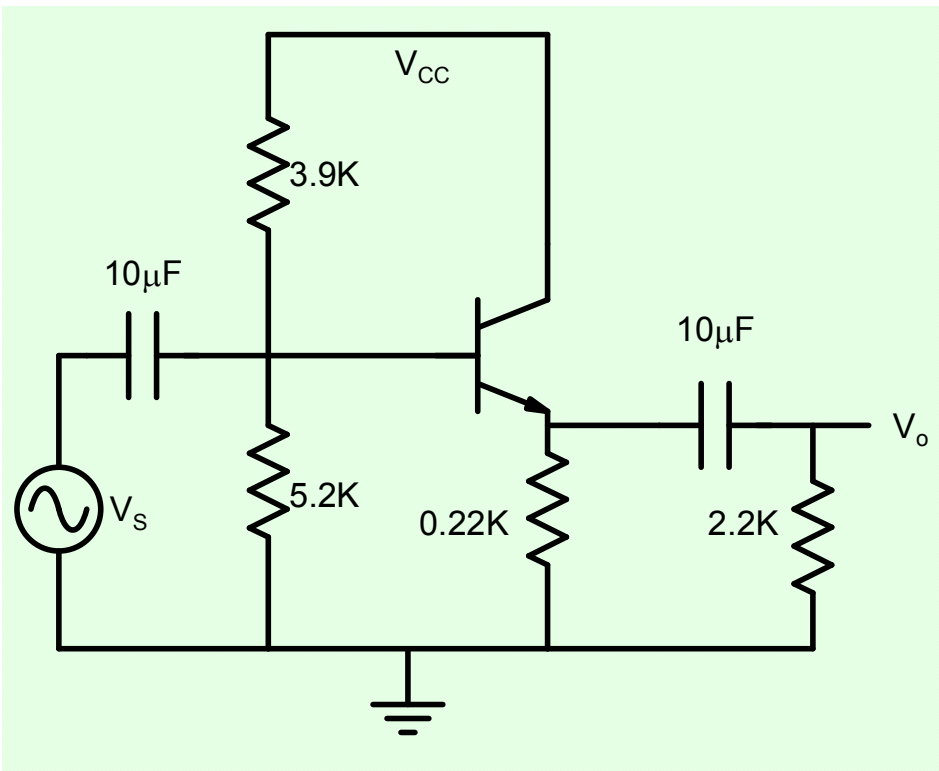

$$I_{CQ} = 25mA; V_{CEQ} = 6.5V$$

$$A_V = 0.98; R_{in} = 2K; R_O = 3\Omega$$

$$V_{om} = 6V$$

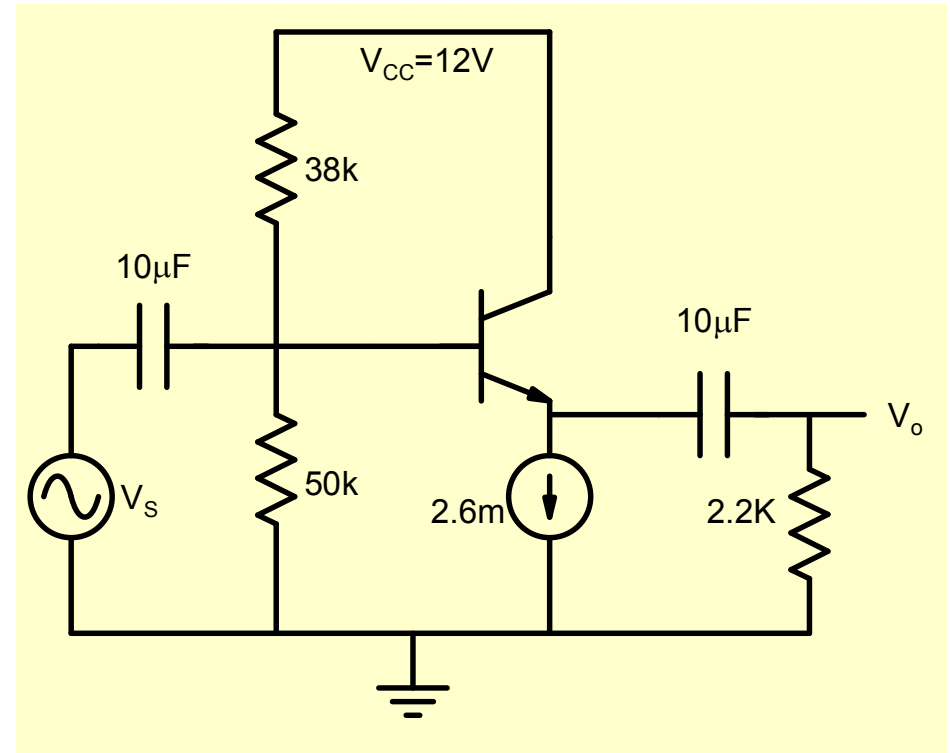


$$I_{CQ} = 2.6mA; V_{CEQ} = 6.5V$$

$$A_V = 0.99; R_{in} = 19.7K; R_O = 9.5\Omega$$

$$V_{om} = 6V$$

Power Gain

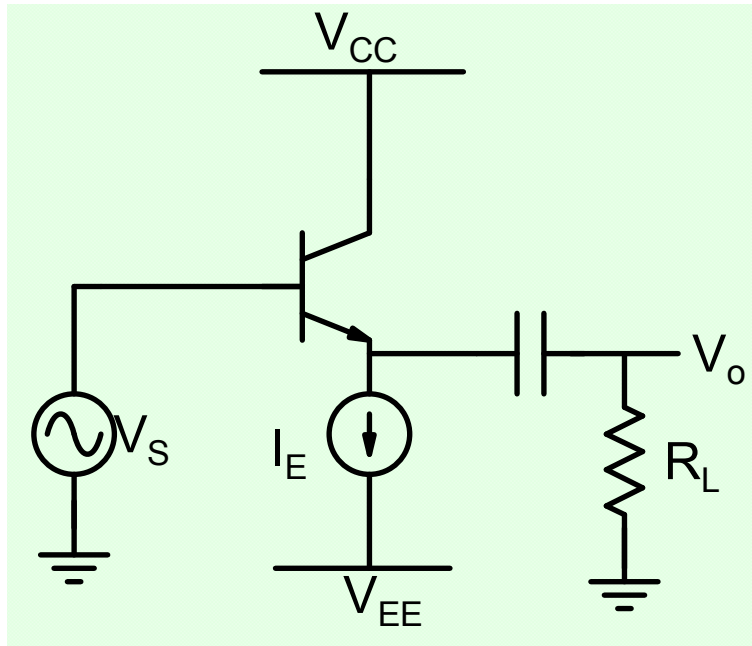

$$P_{in} = \frac{v_s^2}{2R_{in}}$$

$$P_o = \frac{v_o^2}{2R_L}$$

Noting that $v_o \sim v_s$


$$\frac{P_o}{P_{in}} \cong \frac{R_{in}}{R_L}$$

$$R_{in} = r_{\pi} + (\beta + 1) \times R_L$$
$$\cong \beta R_L$$

$$\frac{P_o}{P_{in}} \cong \beta$$

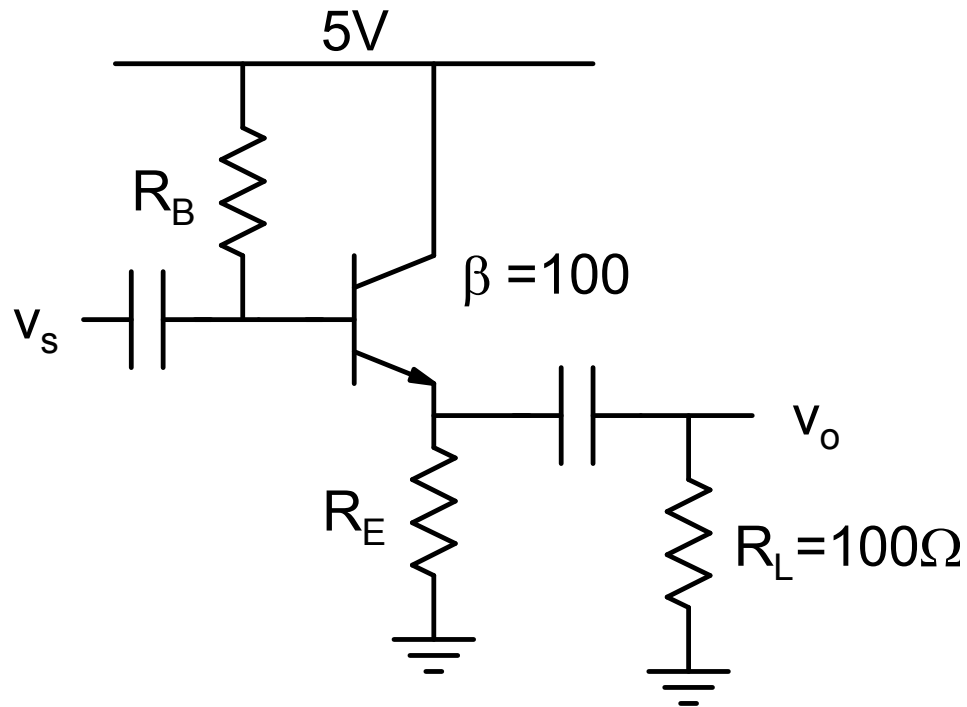Example-1

Determine the values of resistors R_B and R_E to obtain a maximum output voltage swing of 1V.



$$V_O \leq I_{CQ} R_E \parallel R_L$$

$$I_{CQ} \frac{R_E \times R_L}{R_E + R_L} \geq V_O$$


$$V_E \geq V_O \times (1 + R_E / R_L)$$

$$V_O \leq V_{CC} - V_{CEsat} - V_E$$

$$V_E \leq V_{CC} - V_{CEsat} - v_o$$

$$V_O \leq V_{CC} - V_{BE} - I_{CQ} R_E$$

$$V_E \leq V_{CC} - V_{BE} - V_O$$

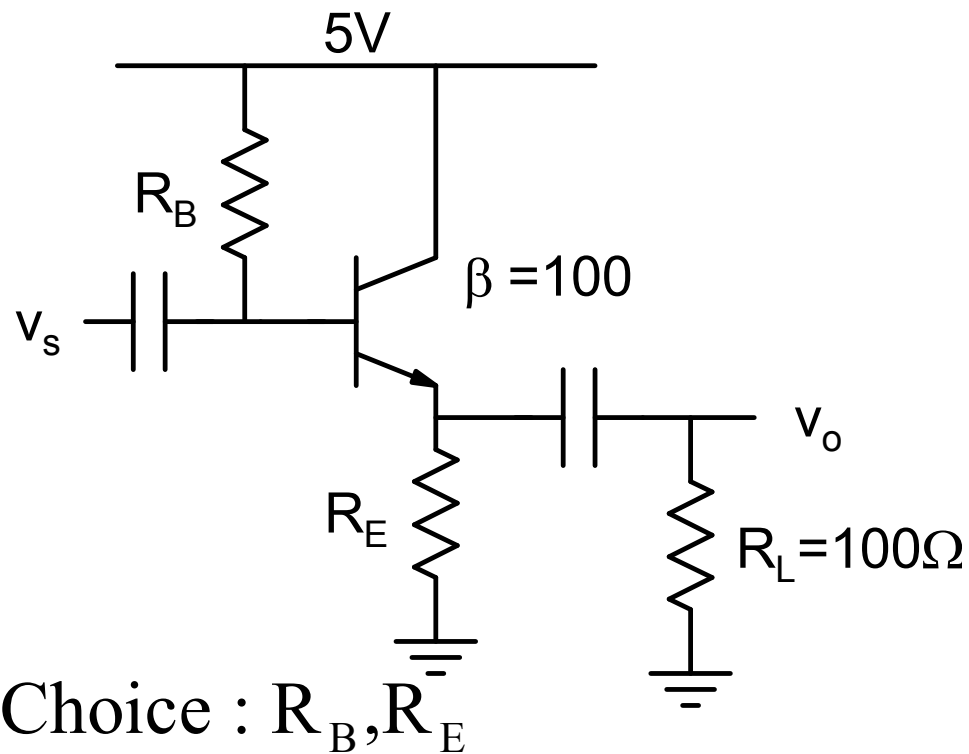

Choice : R_E, V_E

$$V_E \geq V_O \times (1 + R_E / R_L)$$


$$V_E \leq V_{CC} - V_{CEsat} - v_o$$

$$V_E \leq V_{CC} - V_{BE} - V_O$$

$$I_{CQ} = \frac{V_E}{R_E}$$

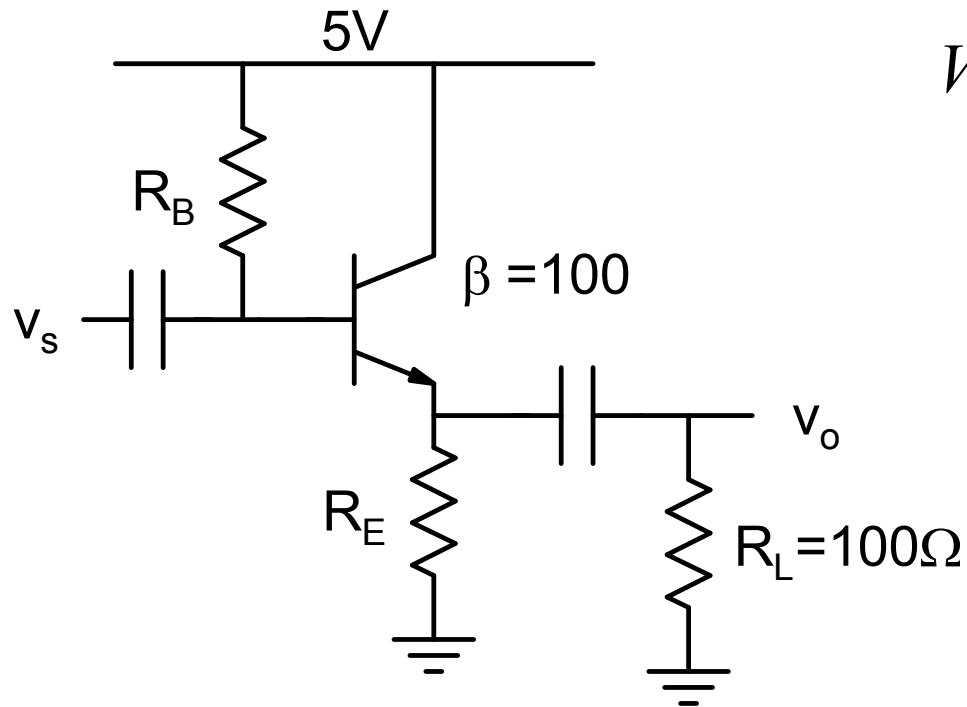Example-1

Determine the values of resistors R_B and R_E to obtain a maximum output voltage swing of 1V.



$$V_E \geq V_O \times (1 + R_E / R_L) = 1 + R_E / R_L$$

$$V_E \leq V_{CC} - V_{BE} - V_O = 3.3V$$

$$I_{CQ} = \frac{V_E}{R_E} \geq \frac{1}{R_E} + \frac{1}{R_L}$$


$$\text{Choose } R_E = 2R_L = 200\Omega$$

$$V_E = 3.1V \text{ and } I_{CQ} = 15.5\text{mA}$$

$$I_{CQ} = \frac{V_{CC} - 0.7 - V_E}{R_B} \times \beta \Rightarrow R_B = 7.7k\Omega$$

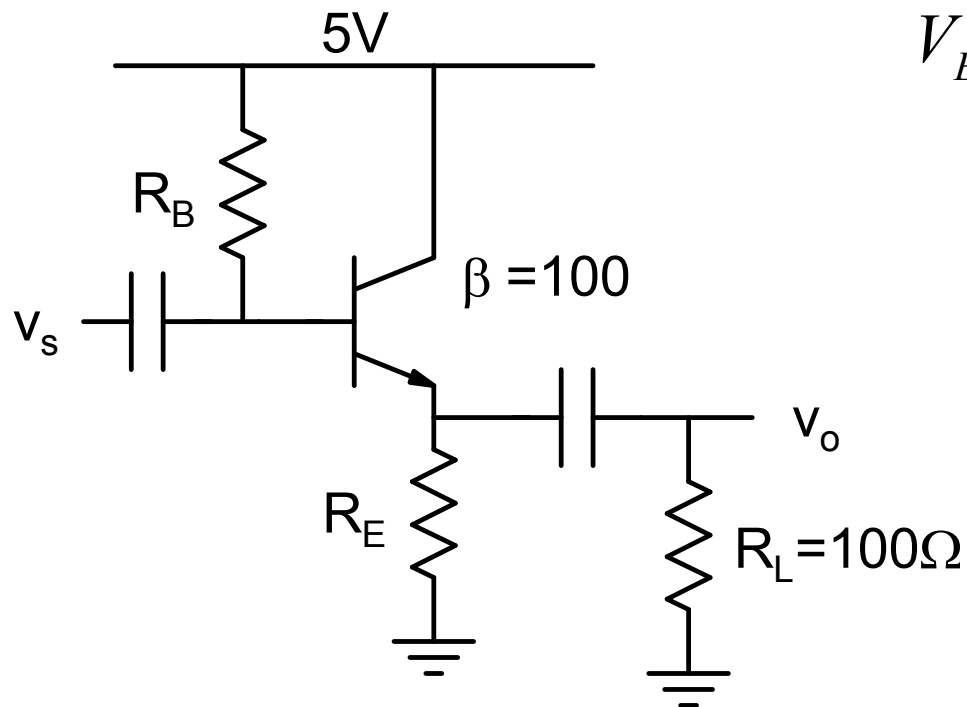Example-2

Determine the values of resistors R_B and R_E to obtain a maximum output voltage swing of 2V.



$$V_E \geq V_O \times (1 + R_E / R_L) = 2 + 2R_E / R_L$$


$$V_E \leq V_{CC} - V_{BE} - V_O = 2.3V$$

$$I_{CQ} = \frac{V_E}{R_E} \geq \frac{2}{R_E} + \frac{2}{R_L}$$


$$\text{Choose } R_E = 0.1R_L = 10\Omega$$

$$V_E = 2.25V \text{ and } I_{CQ} = 225\text{mA}$$
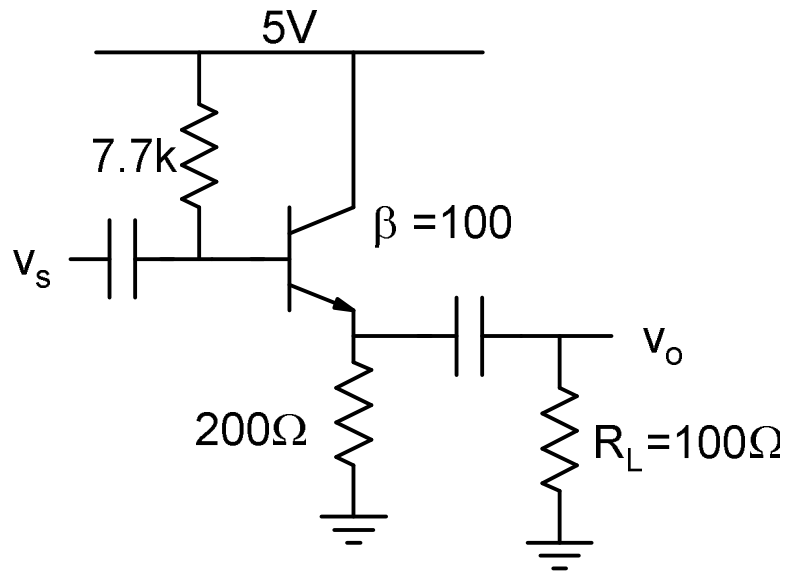
$$I_{CQ} = \frac{V_{CC} - 0.7 - V_E}{R_B} \times \beta \Rightarrow R_B = 0.9k\Omega$$



$$I_{CQ} = 15.5\text{mA}; V_O = 1V$$

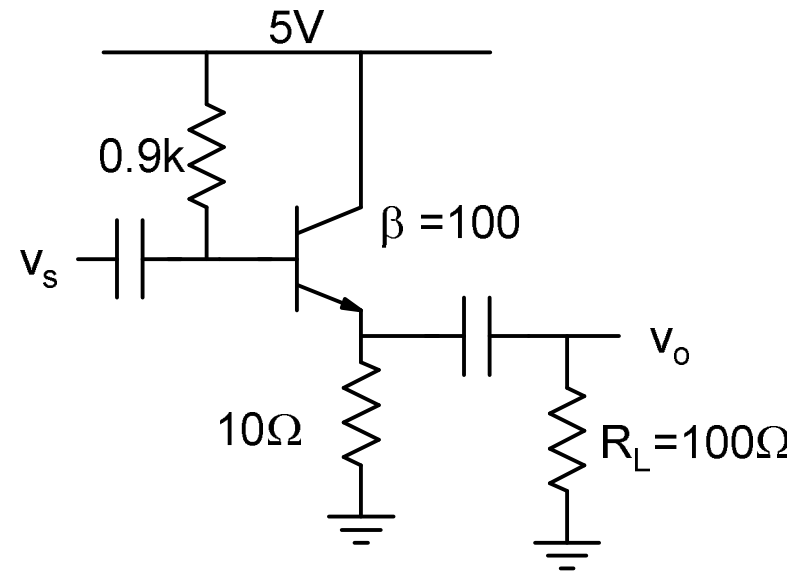


$$I_{CQ} = 225\text{mA}; V_O = 2V$$

$$V_O = 2V \Rightarrow P_L = 20\text{mW}$$

$$P_S = V_{CC} \times I_{CQ} = 1.1\text{W} \Rightarrow \eta = \frac{P_L}{P_S} = 1.8\%$$

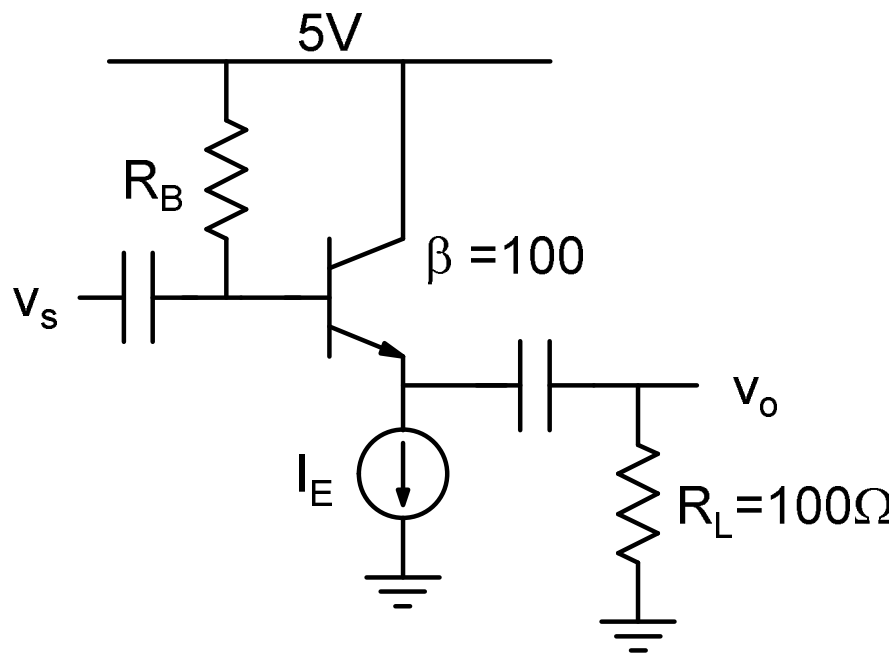Example-3

Determine the values of resistors R_B and R_E to obtain a maximum output voltage swing of 2V.



$$I_E \geq \frac{V_O}{R_L} = 20mA$$

$$V_E \leq V_{CC} - V_{BE} - V_O = 2.3V$$

$$V_E \geq V_O = 2.0V$$


$$\text{Choose } I_E = 22mA$$

$$V_E = 2.1V$$

$$I_{CQ} = \frac{V_{CC} - 0.7 - V_E}{R_B} \times \beta \Rightarrow R_B = 9.5k\Omega$$


$$V_O = 2V \Rightarrow P_L = 20mW$$
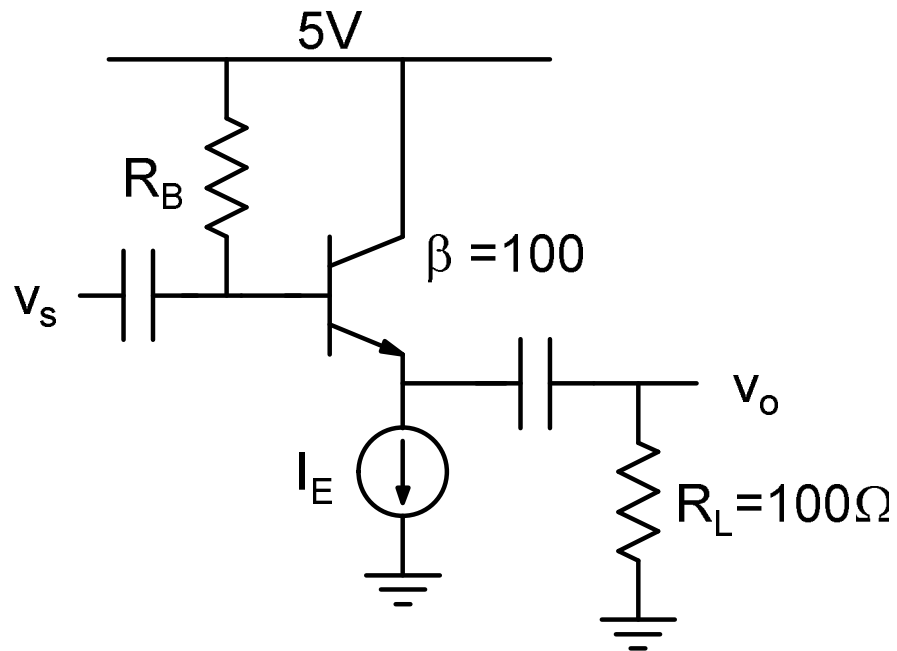
$$P_S = V_{CC} \times I_{EQ} = 110mW \Rightarrow \eta = \frac{P_L}{P_S} = 18\%$$



Choose $I_E = 22\text{mA}$

$V_E = 2.1\text{V}$

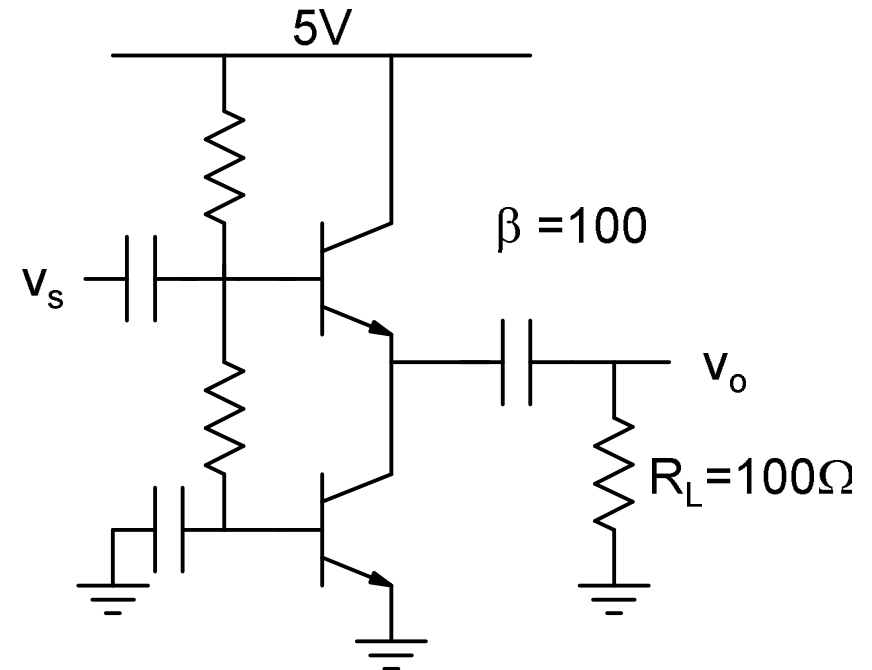

Choose $I_E = 22\text{mA}$

$V_E = 2.5\text{V}$