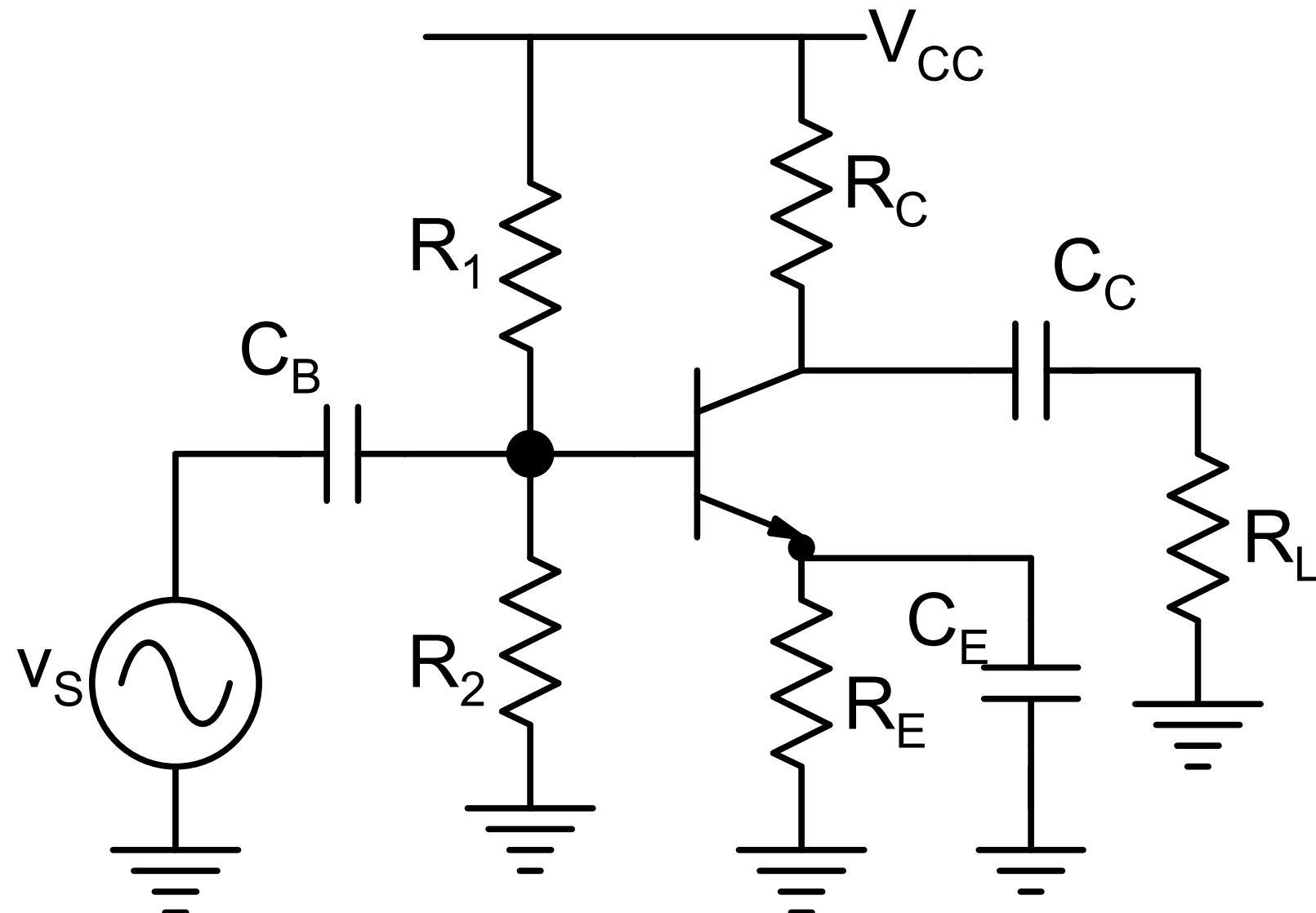


# **EE210: Microelectronics-I**

## **Lecture-17 : BJT Amplifier-part-6 Amplifier Analysis**

Instructor - Y. S. Chauhan

Slides from: B. Mazhari  
Dept. of EE, IIT Kanpur




**Is there a better way of remembering ?**

# A 10-step approach for drawing the CE amplifier


# **dc Analysis**

## Example-1

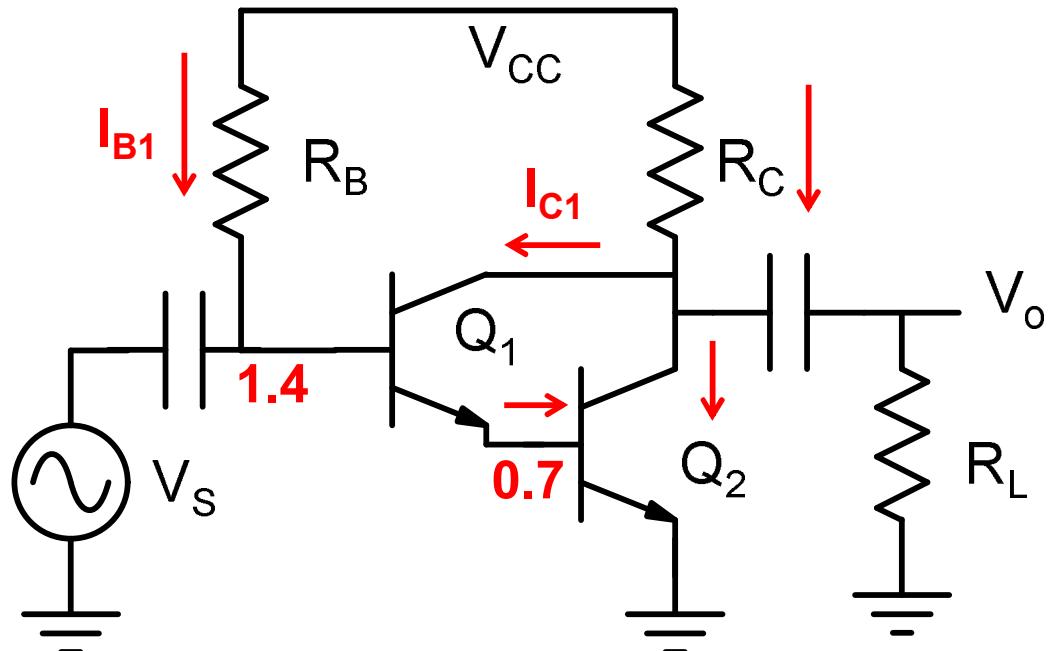


$$V_{BE} \sim 0.7V, I_C = \beta \times I_B$$


## Example-2

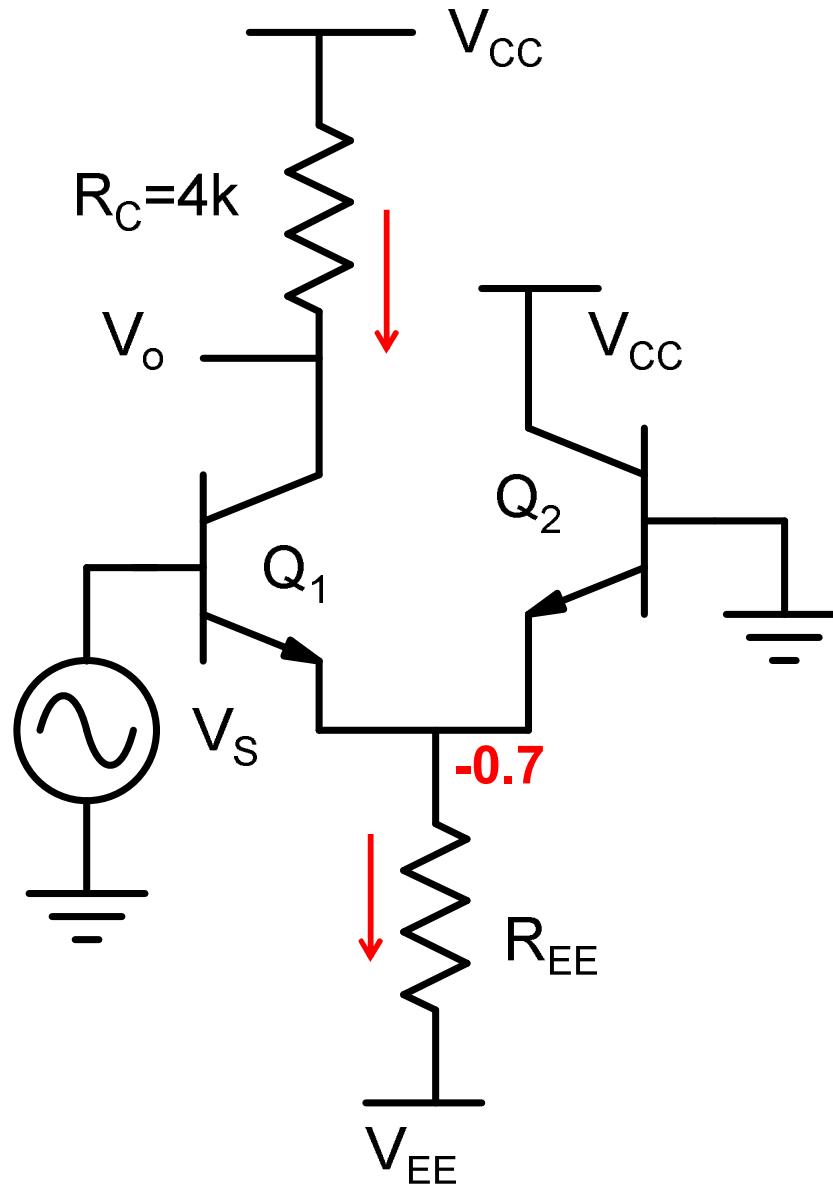

## Example-3

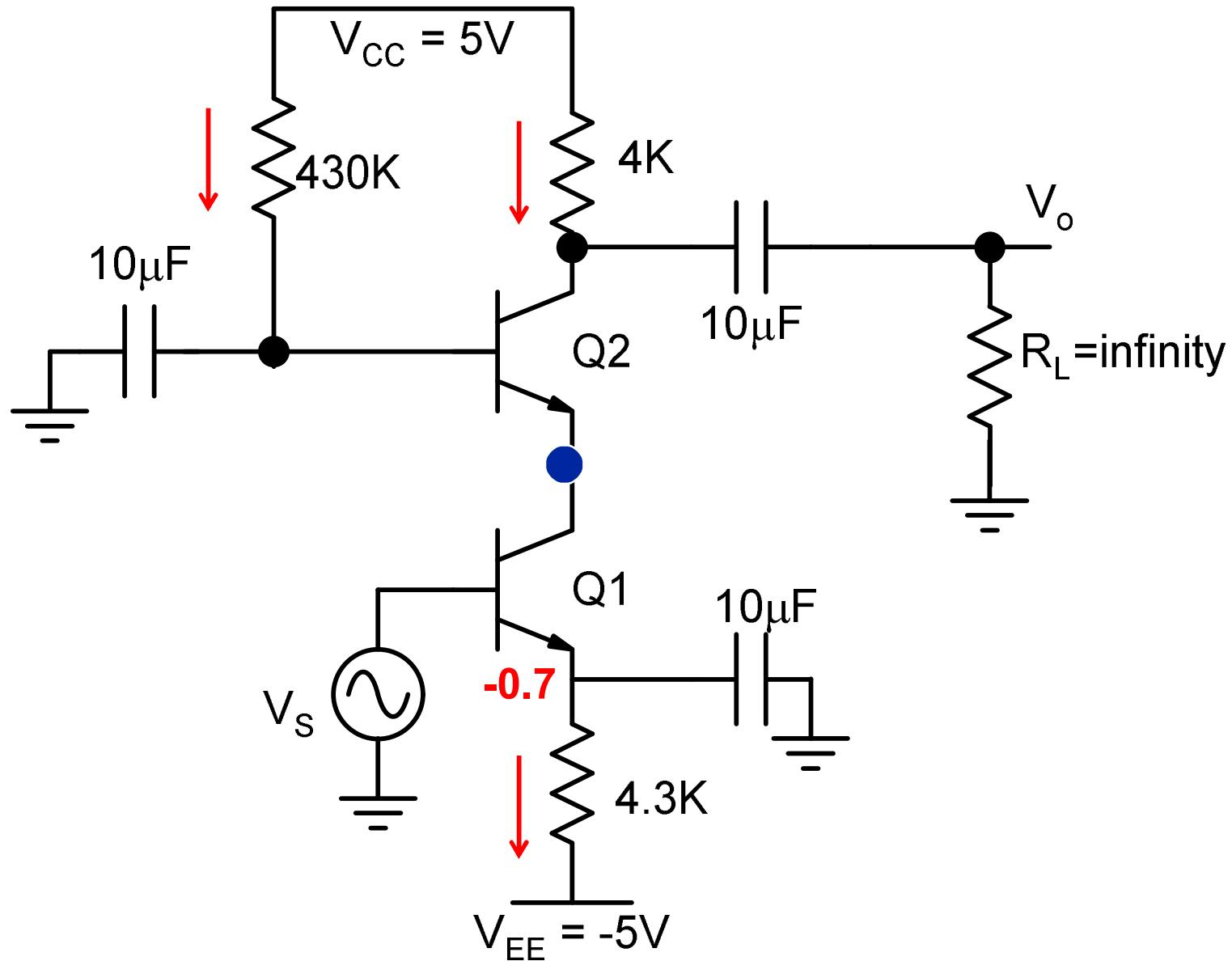


## Example-4

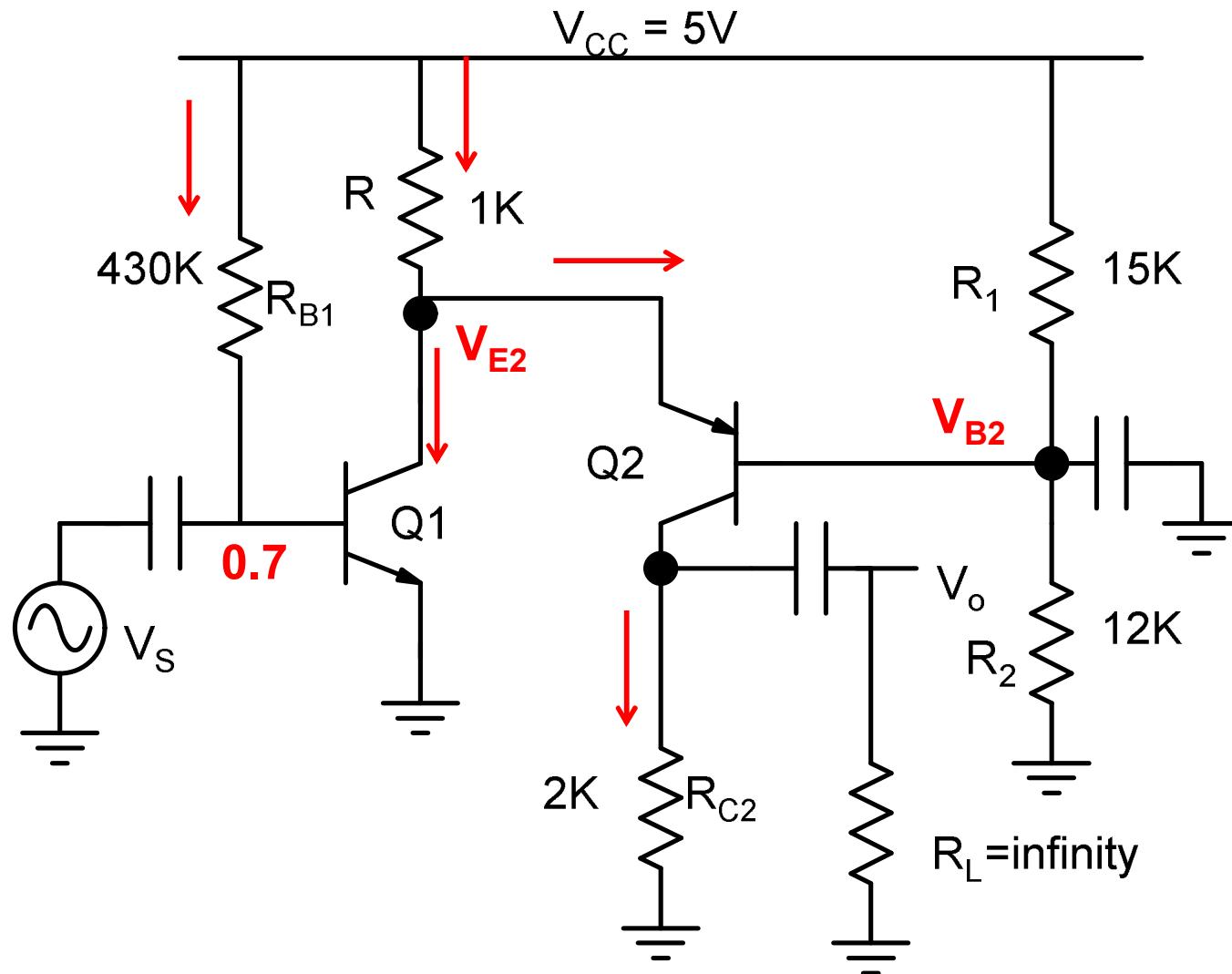


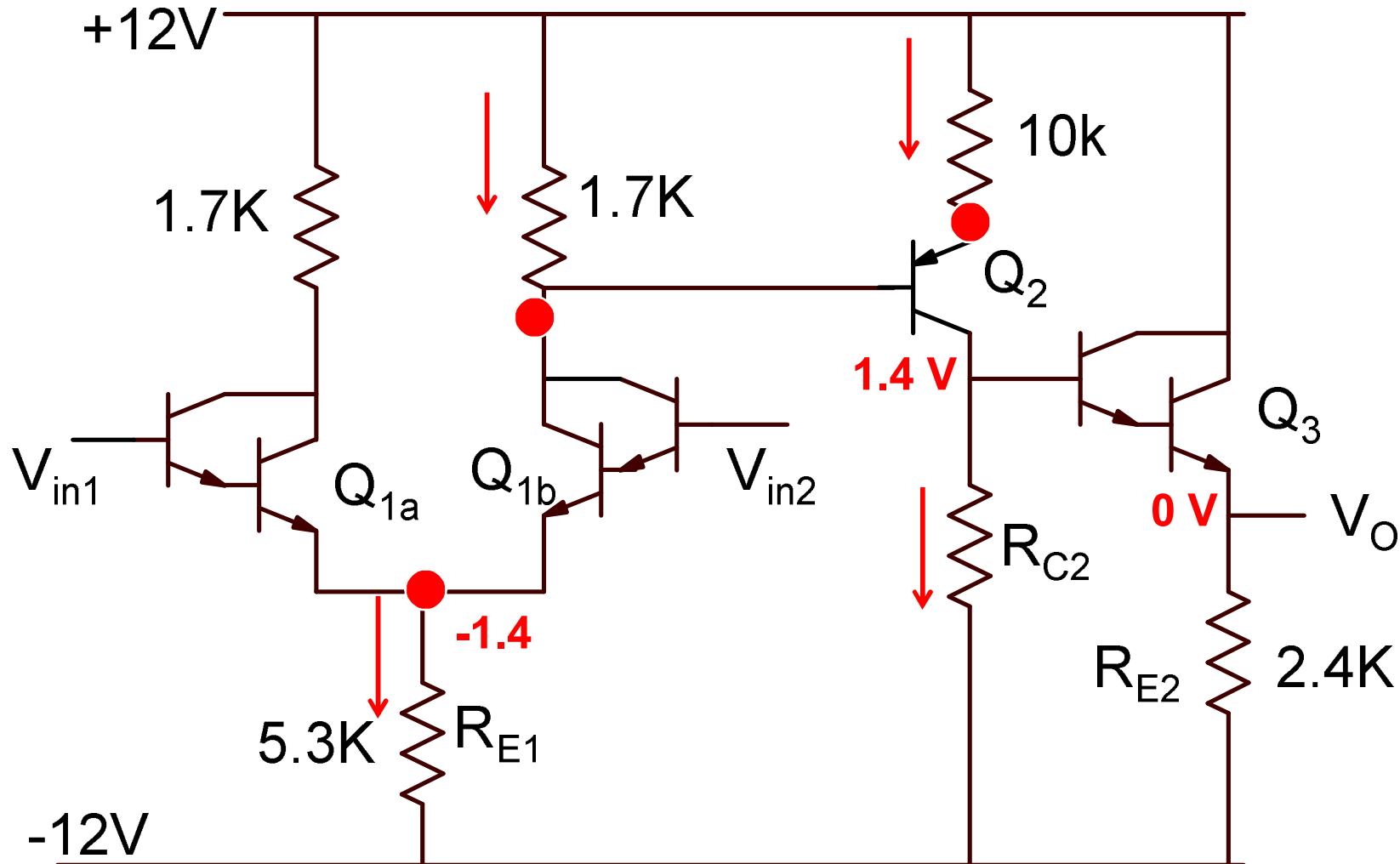
## Example-5

For what value of  $R_{C2}$ , is  $V_o = 0V$  ?



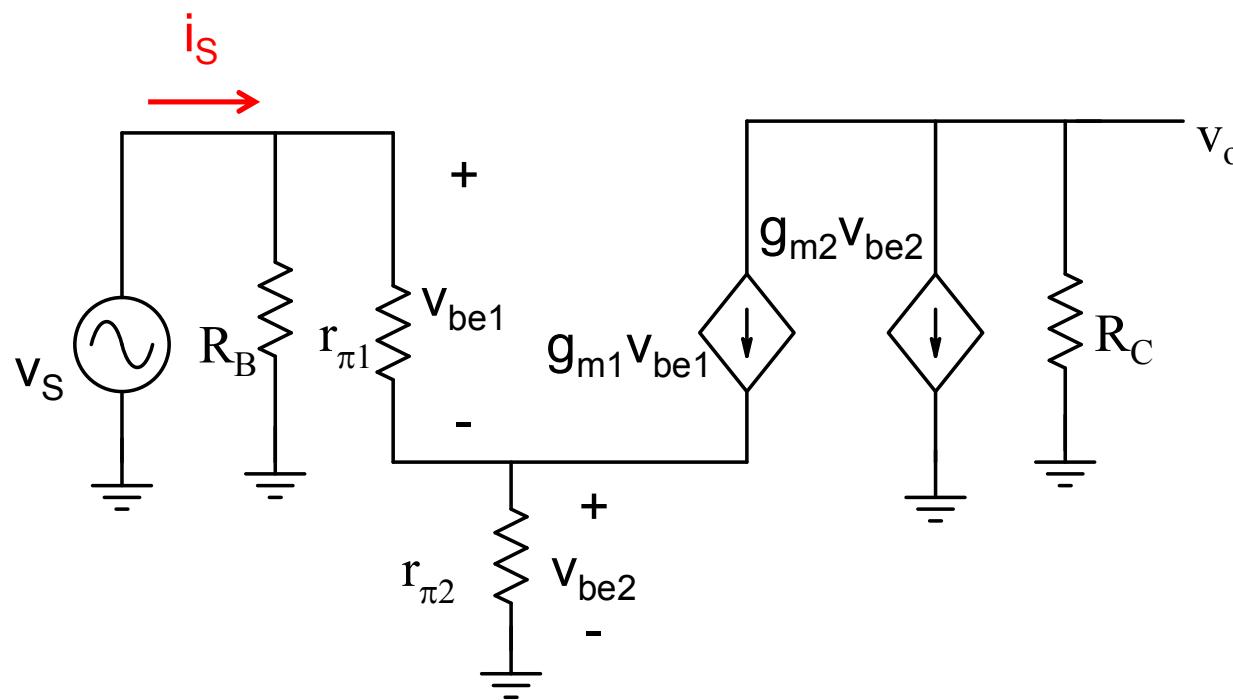
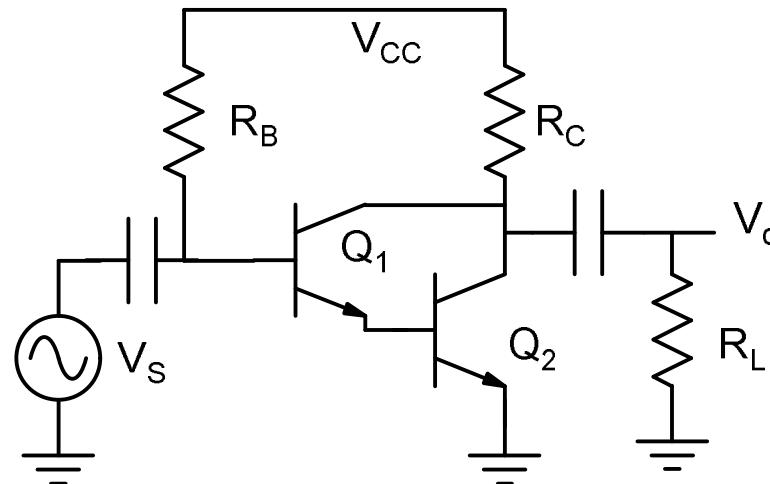
## Example-1

Determine input resistance of the amplifier shown below



$$R_{in} = \frac{v_s}{i_s}$$


## Example-2

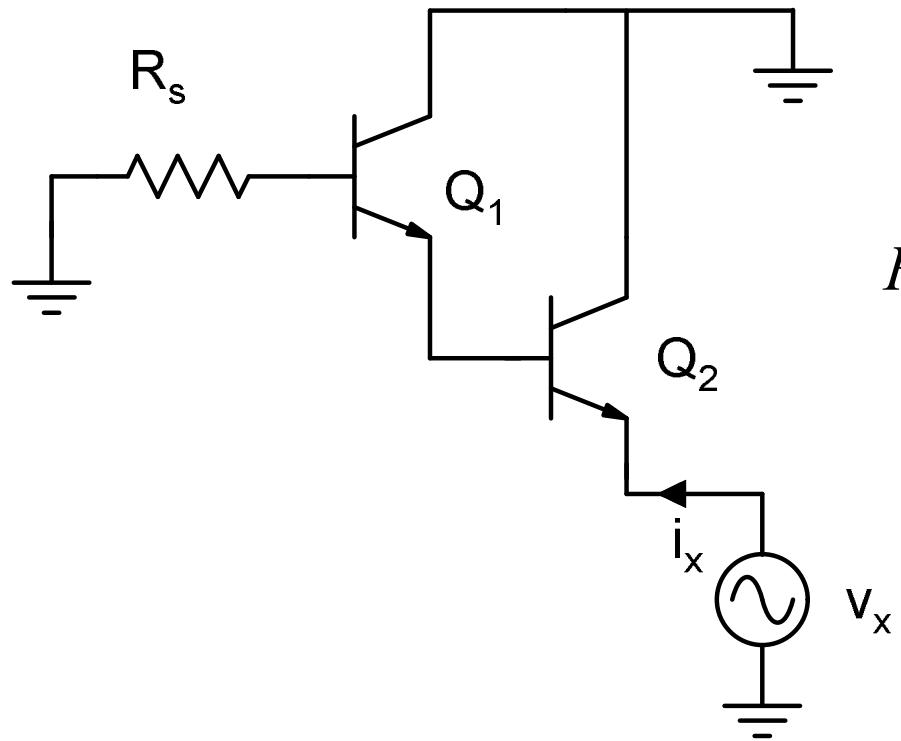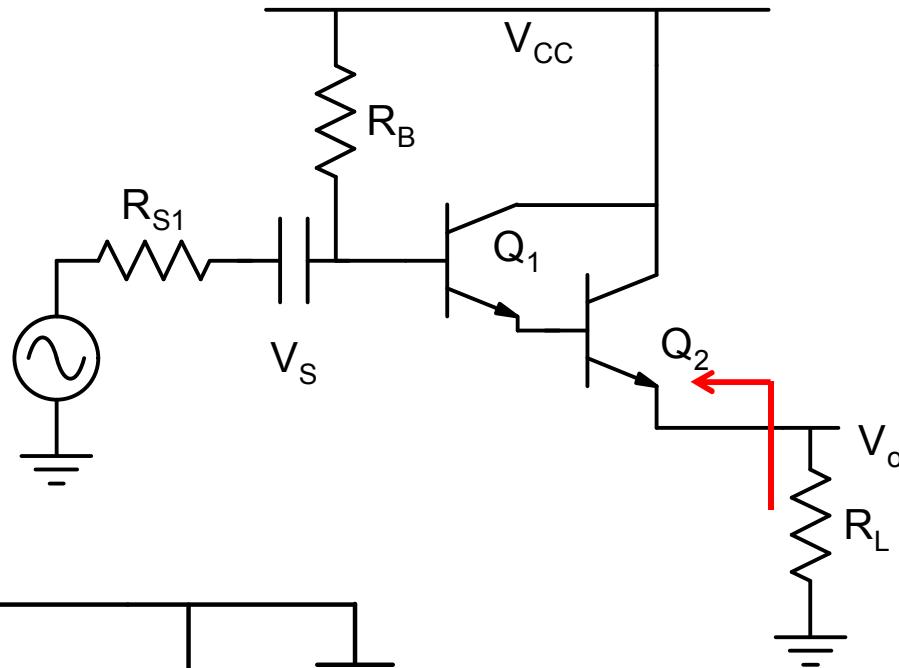

$$R_o = \frac{v_x}{i_x}$$


$$R_o = \frac{R_s}{\beta_1 \beta_2} + \frac{1}{g_m \beta_2} + \frac{1}{g_m}$$

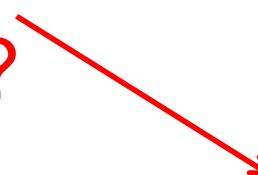Is there a “better” way of carrying out small signal analysis ?




Simpler




Less error prone

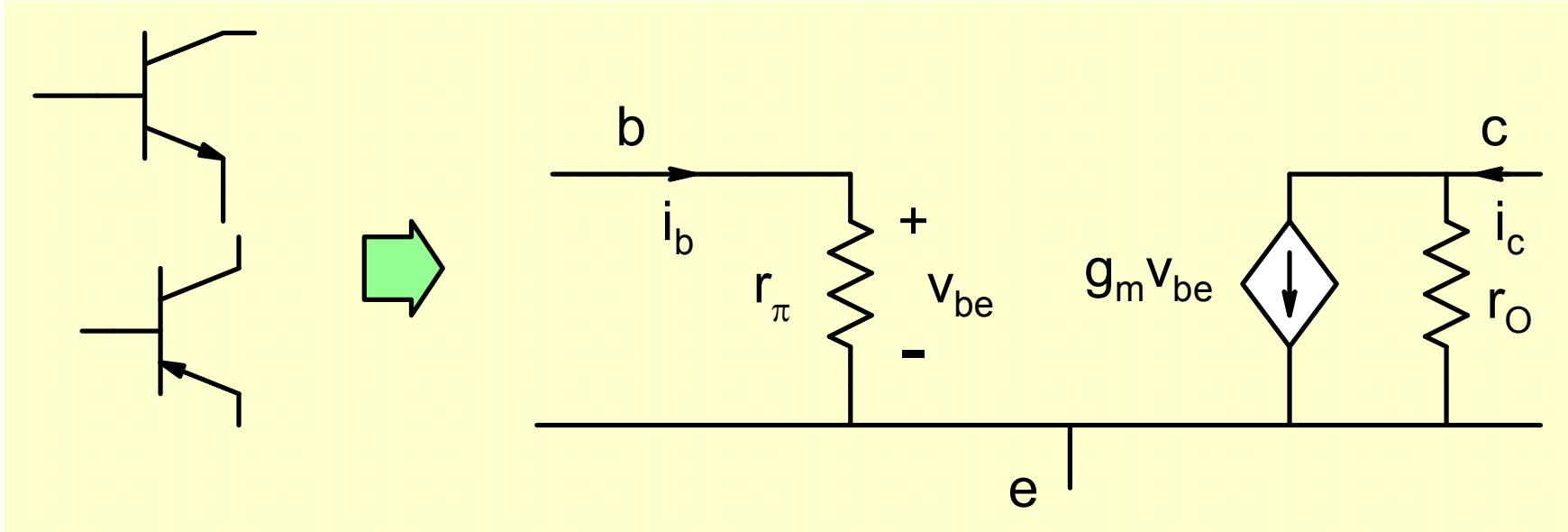



NPN and PNP models are identical

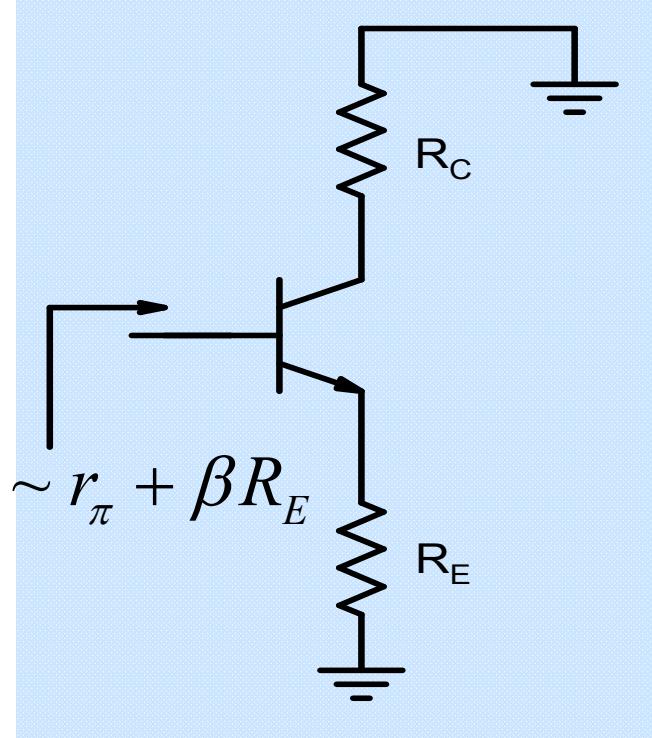


$$R_C, R_E, R_B \ll r_o$$

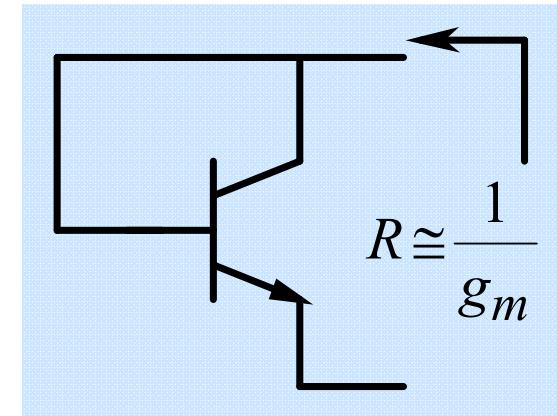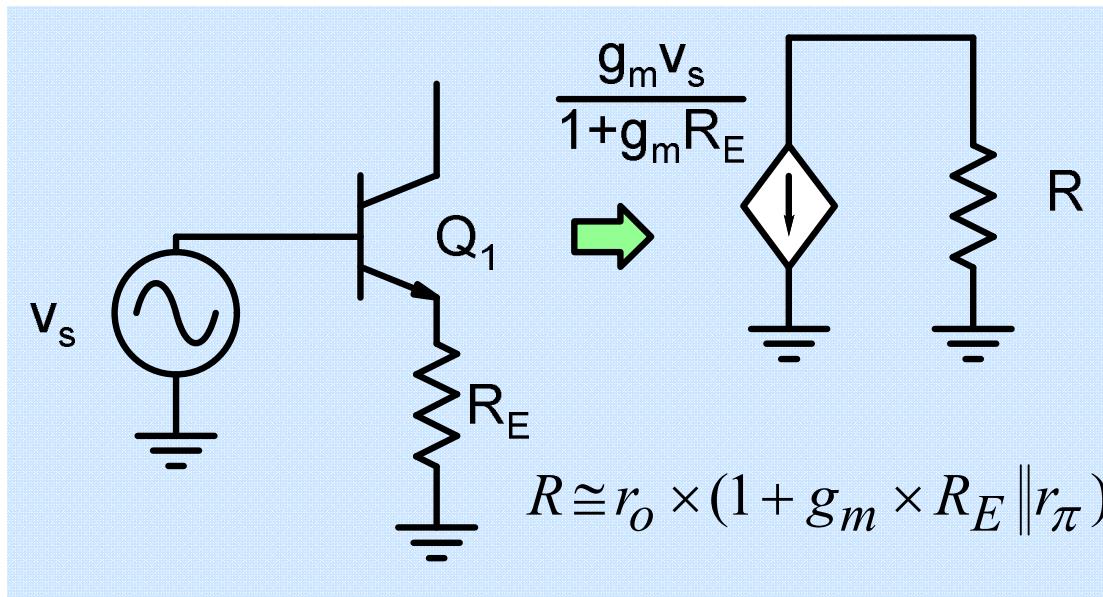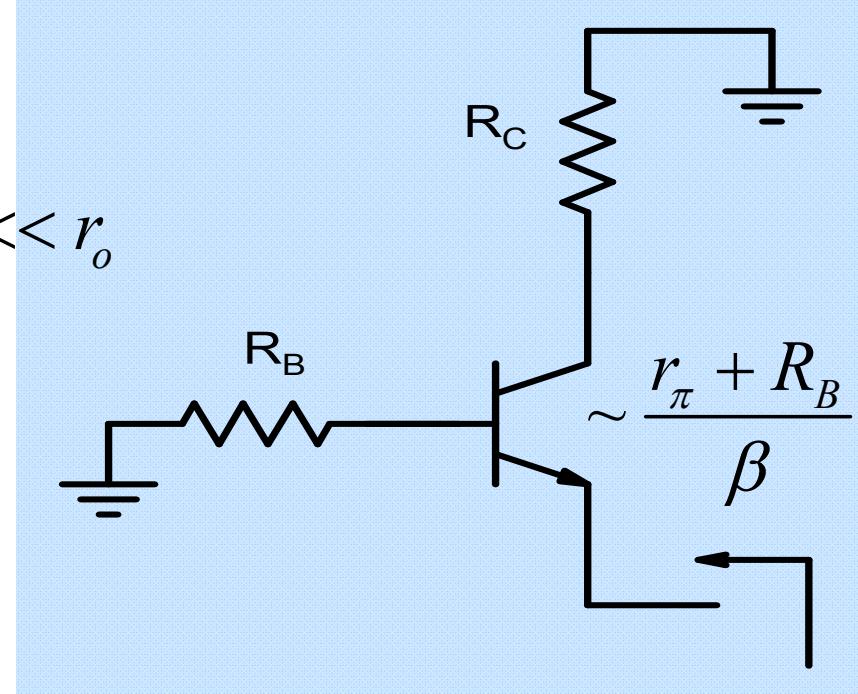



## Example-1


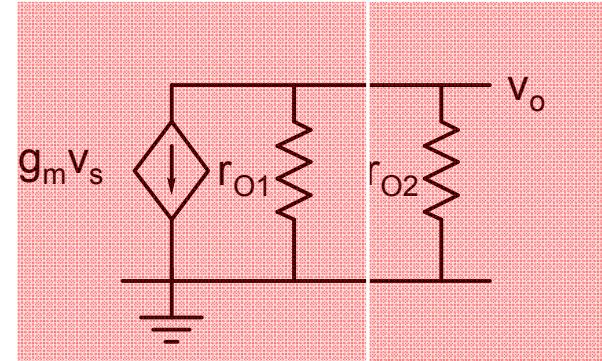
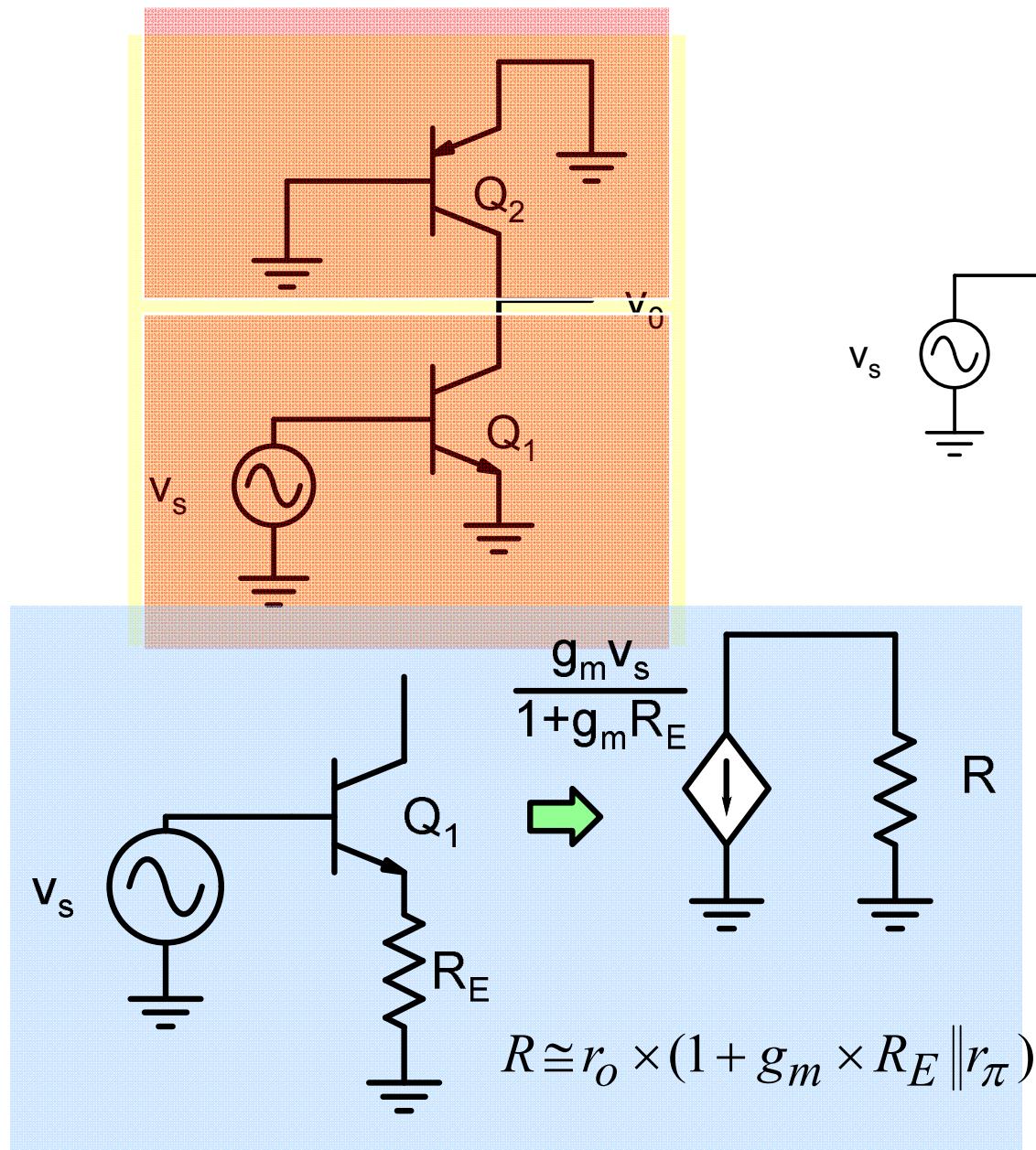


## Example-2

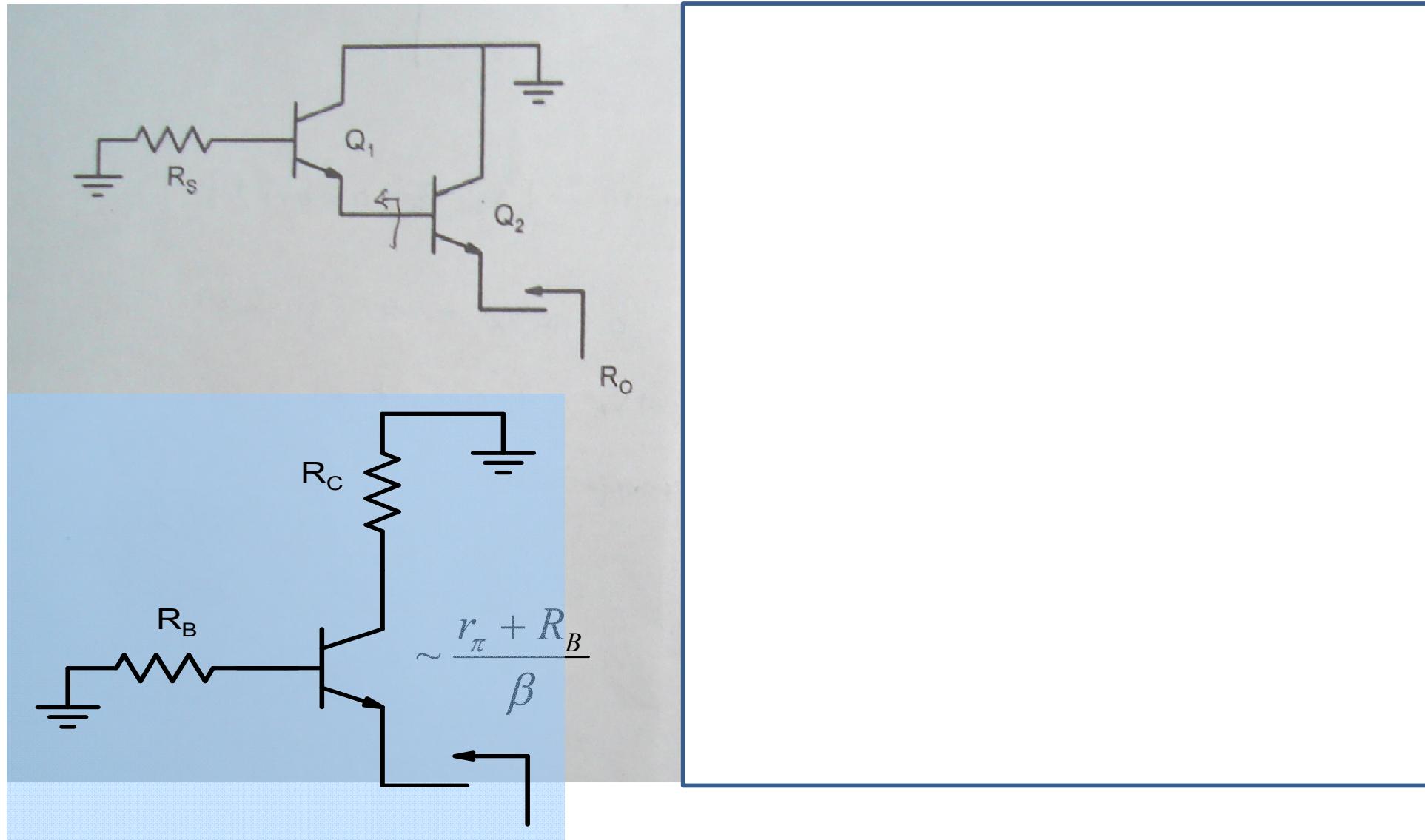






## Example-3

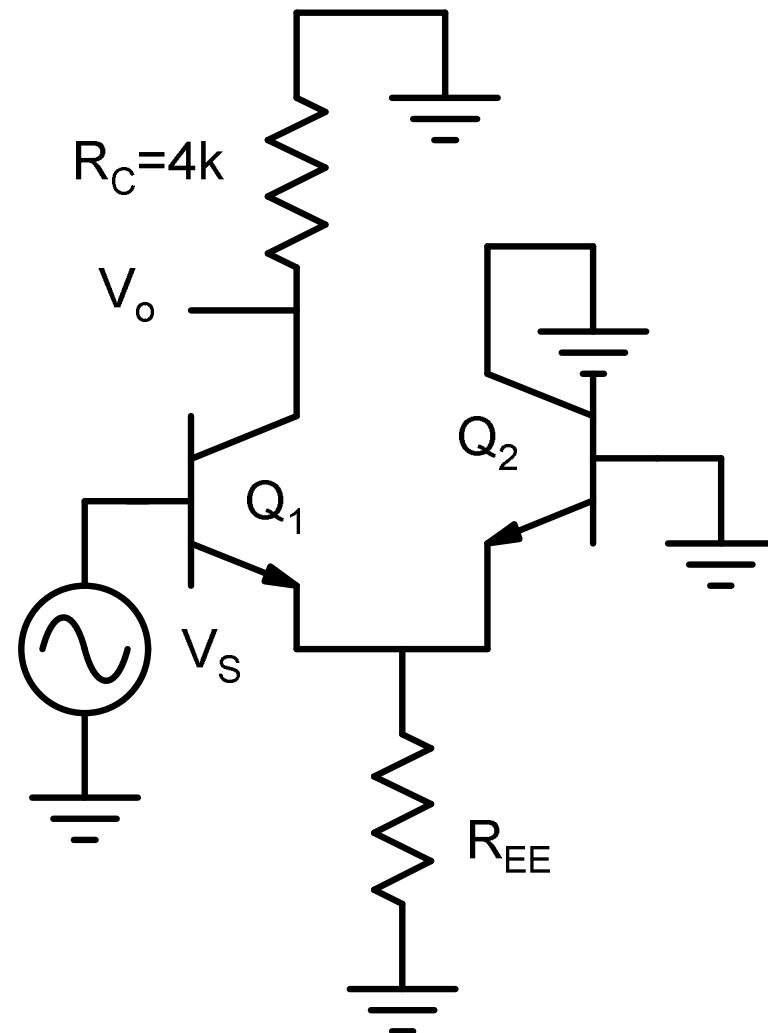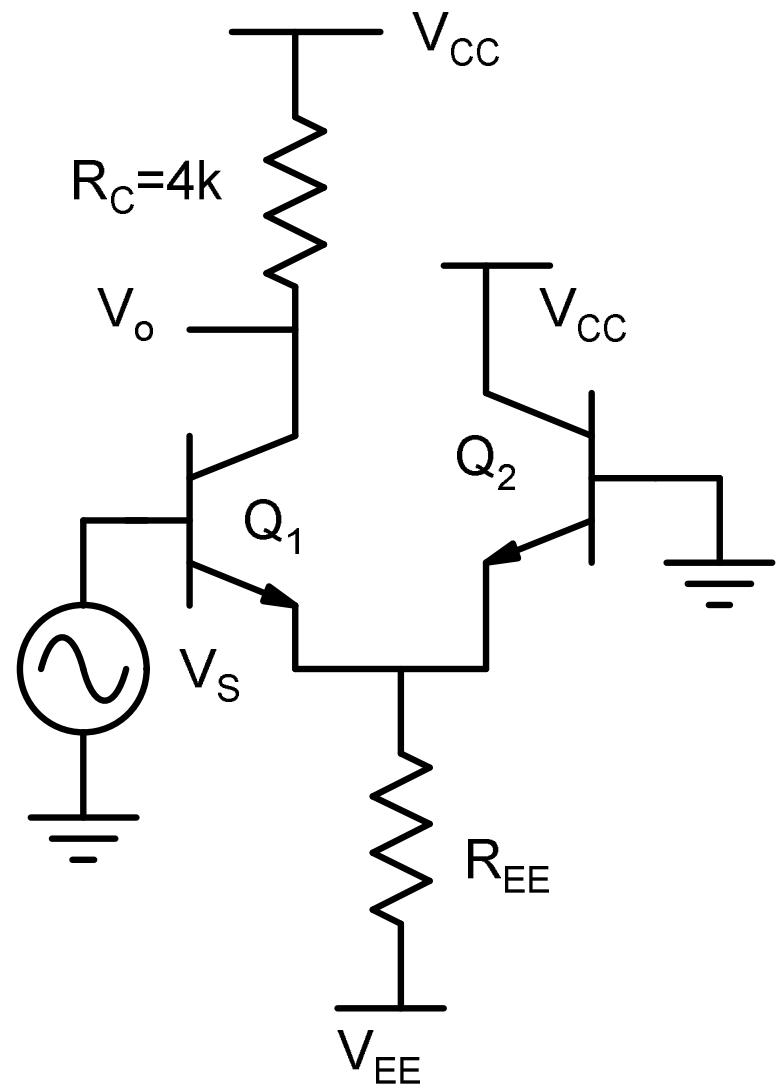

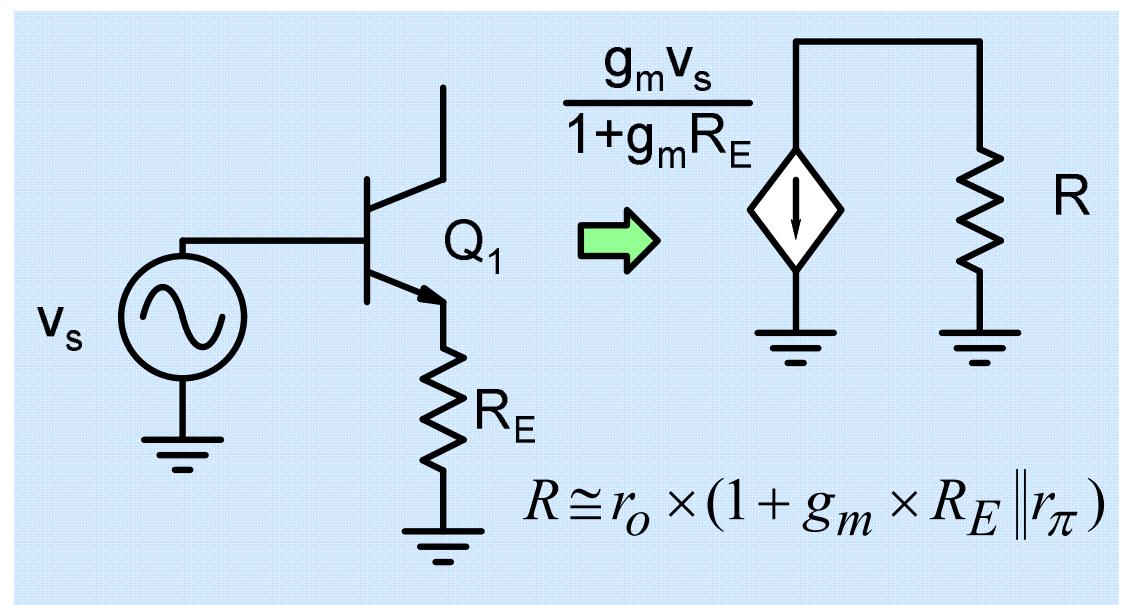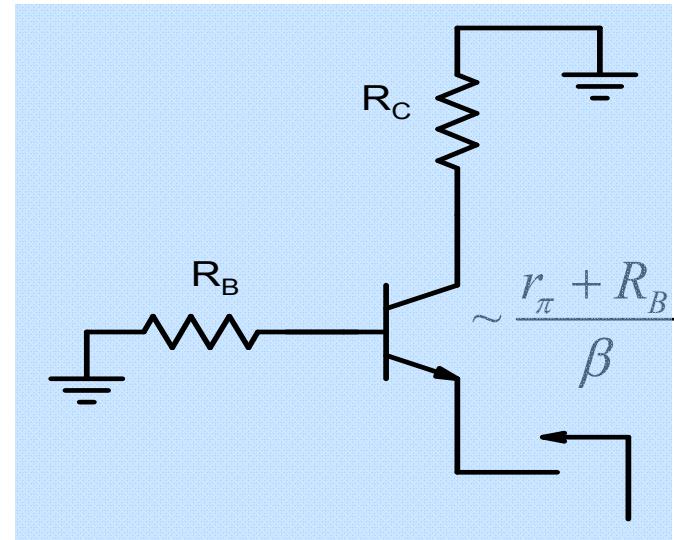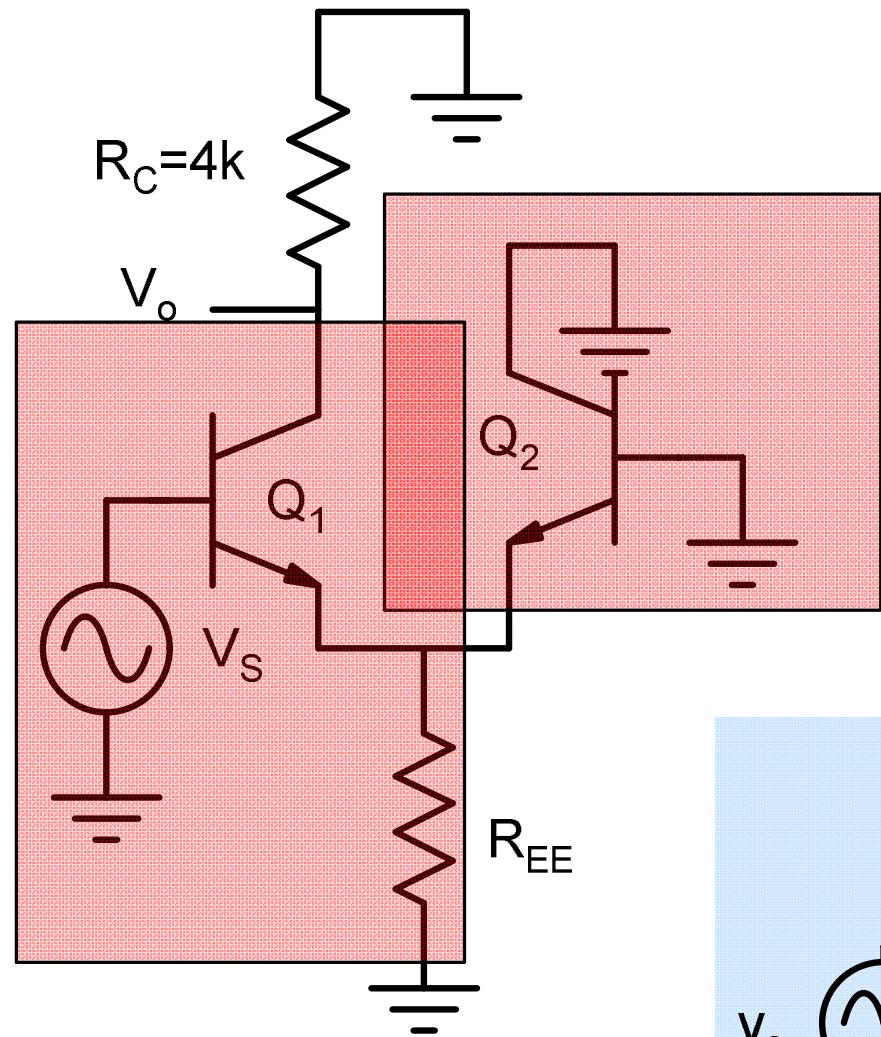






## Example-4

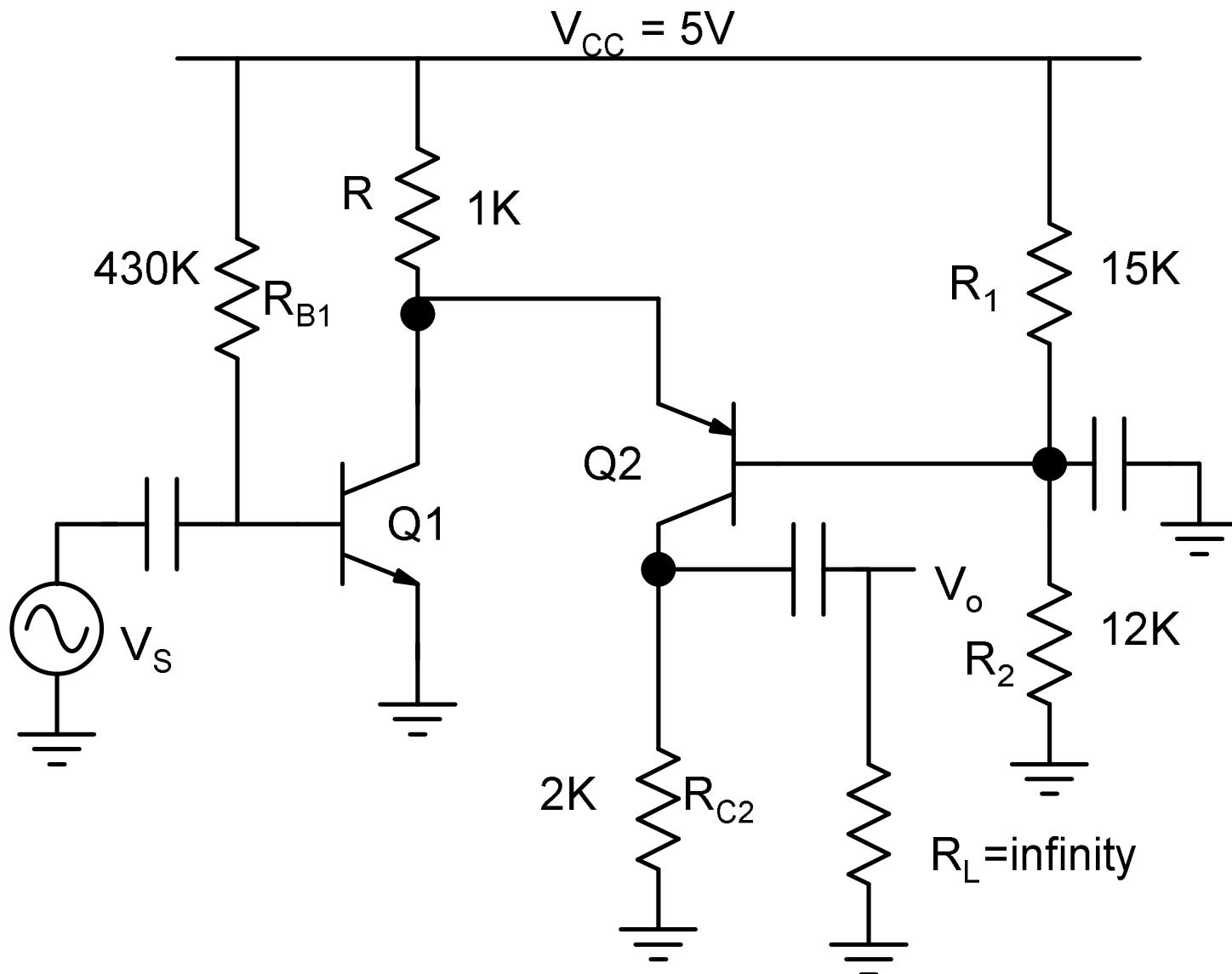

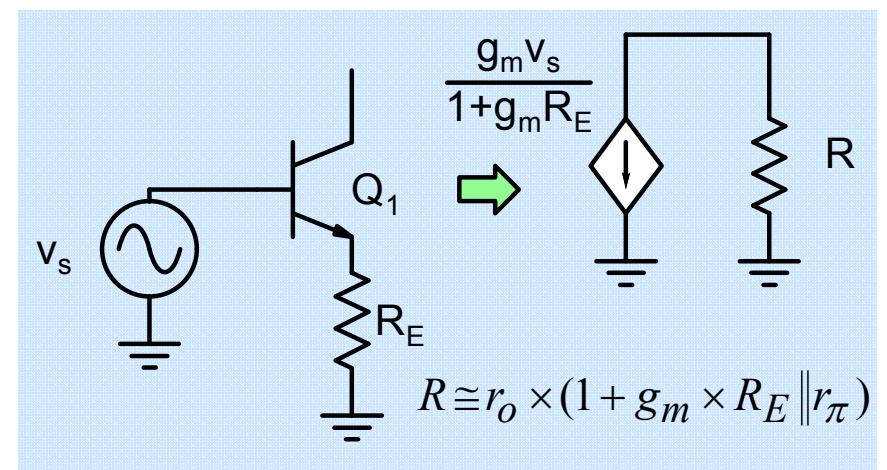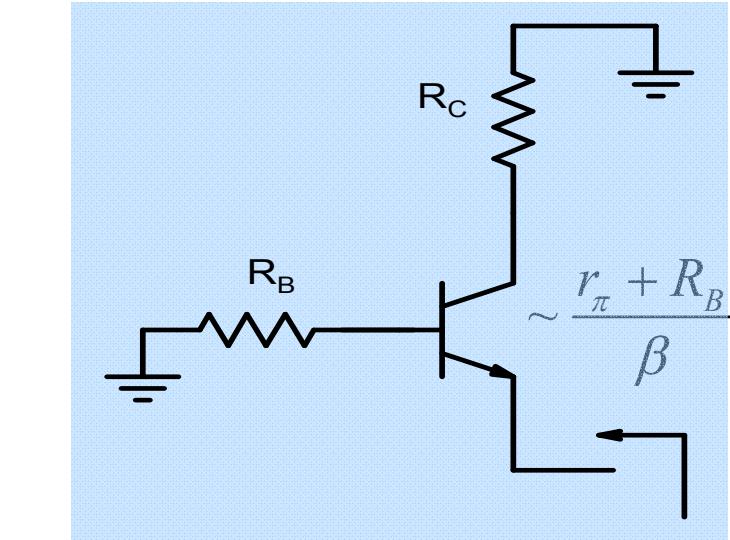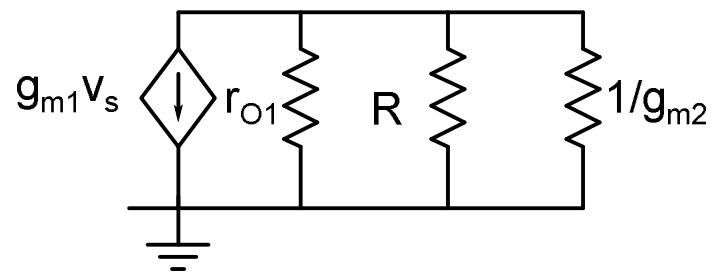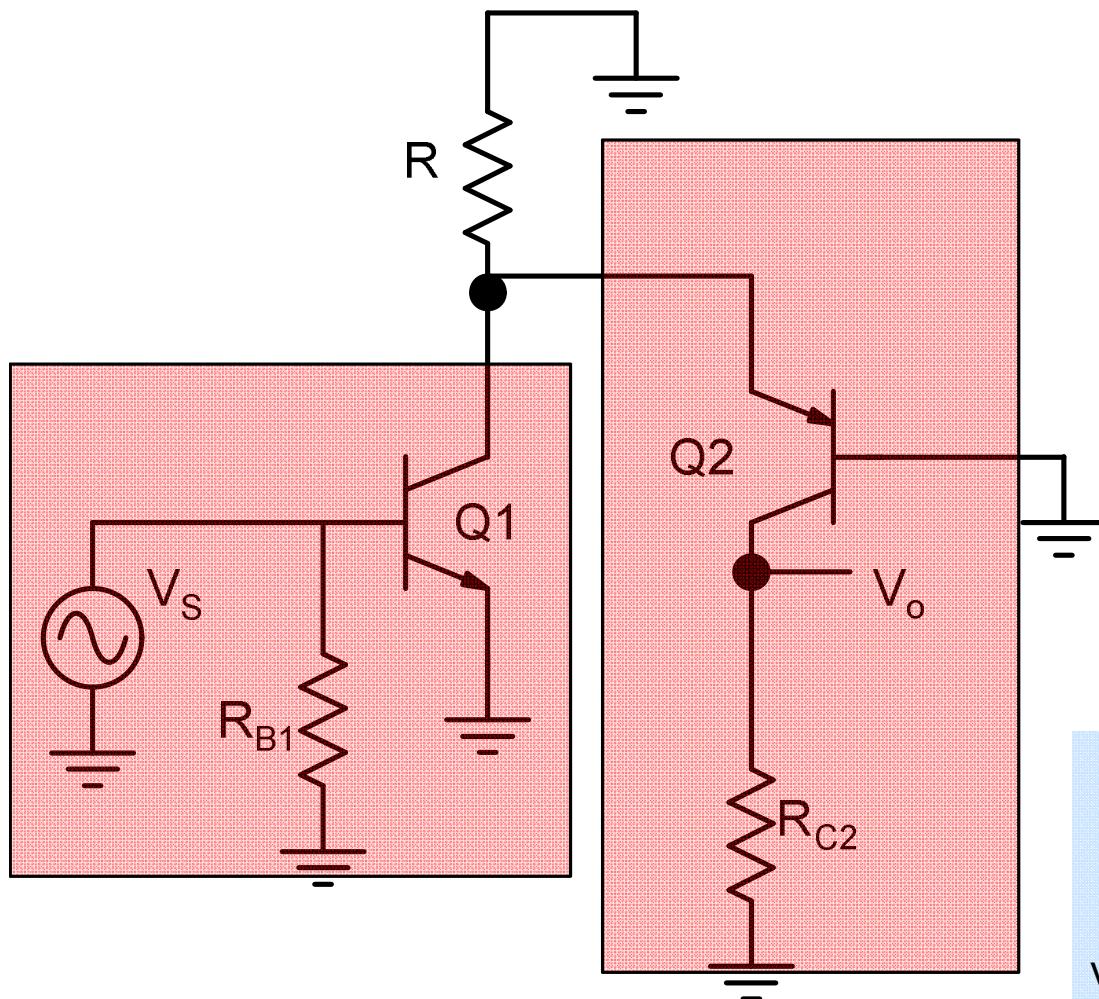


## Example-5


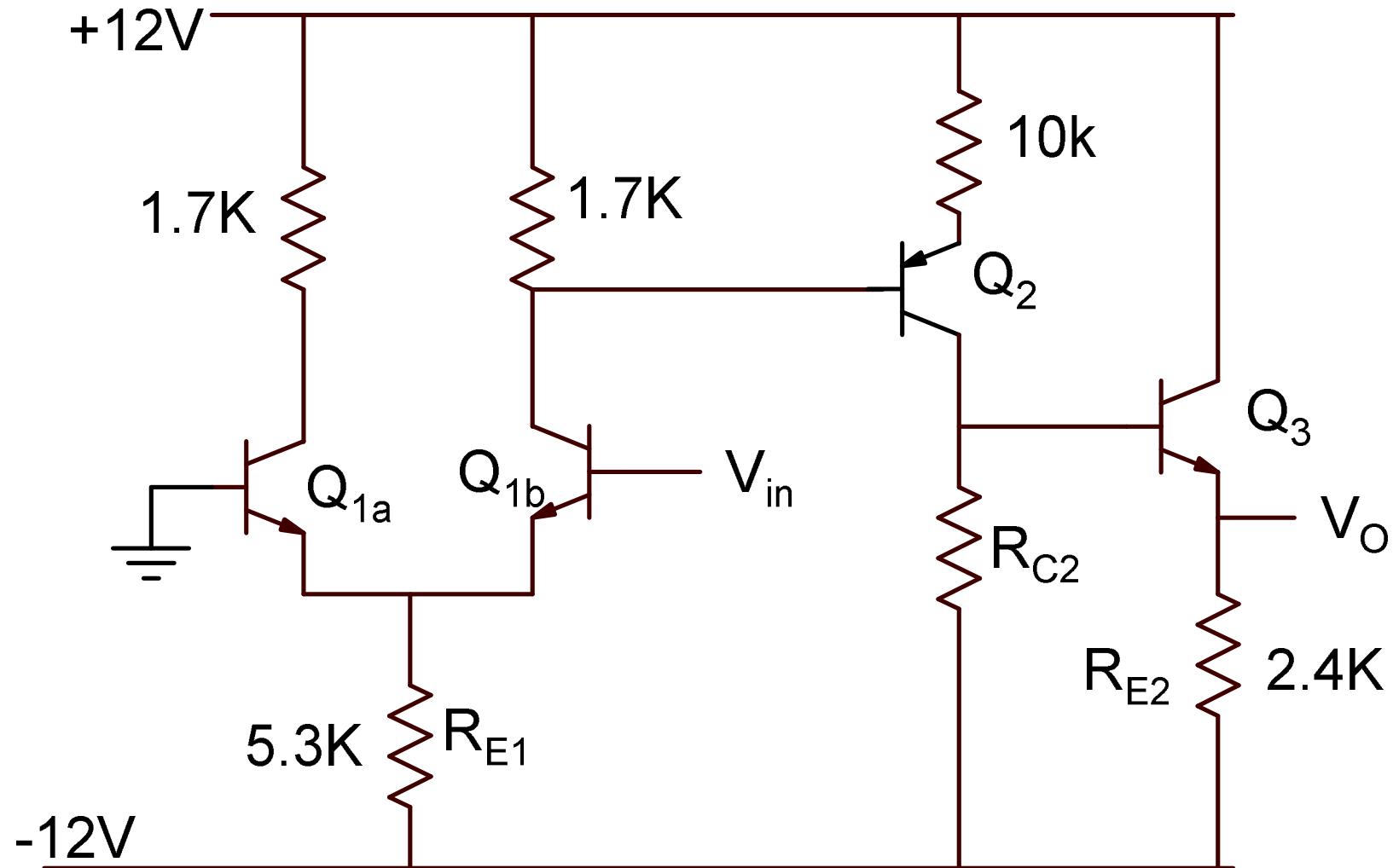


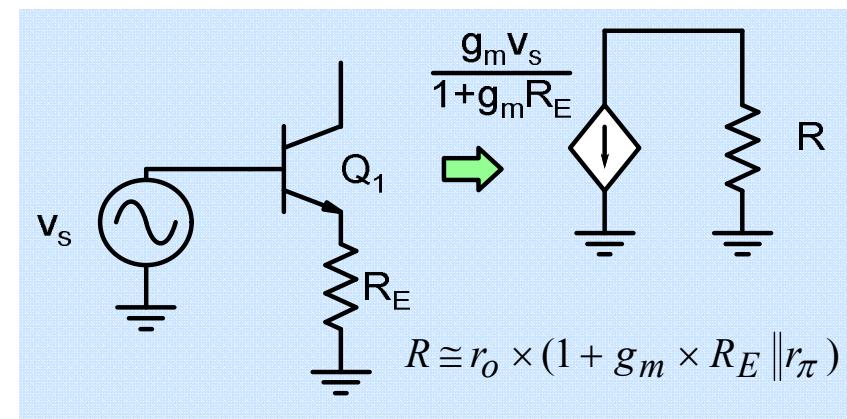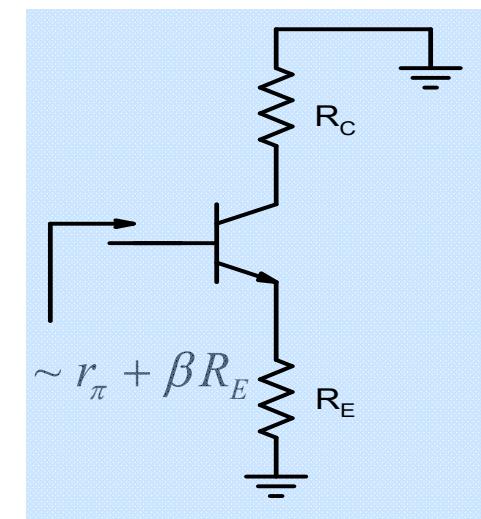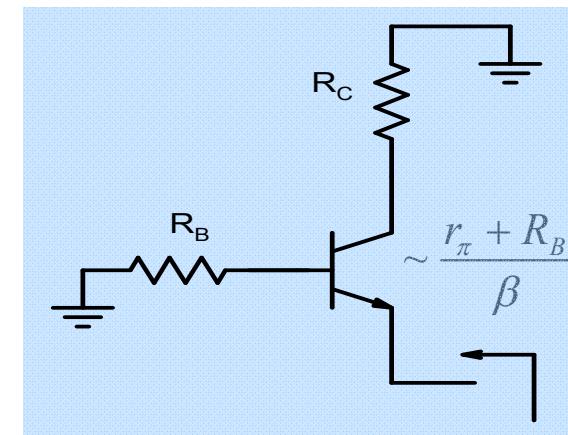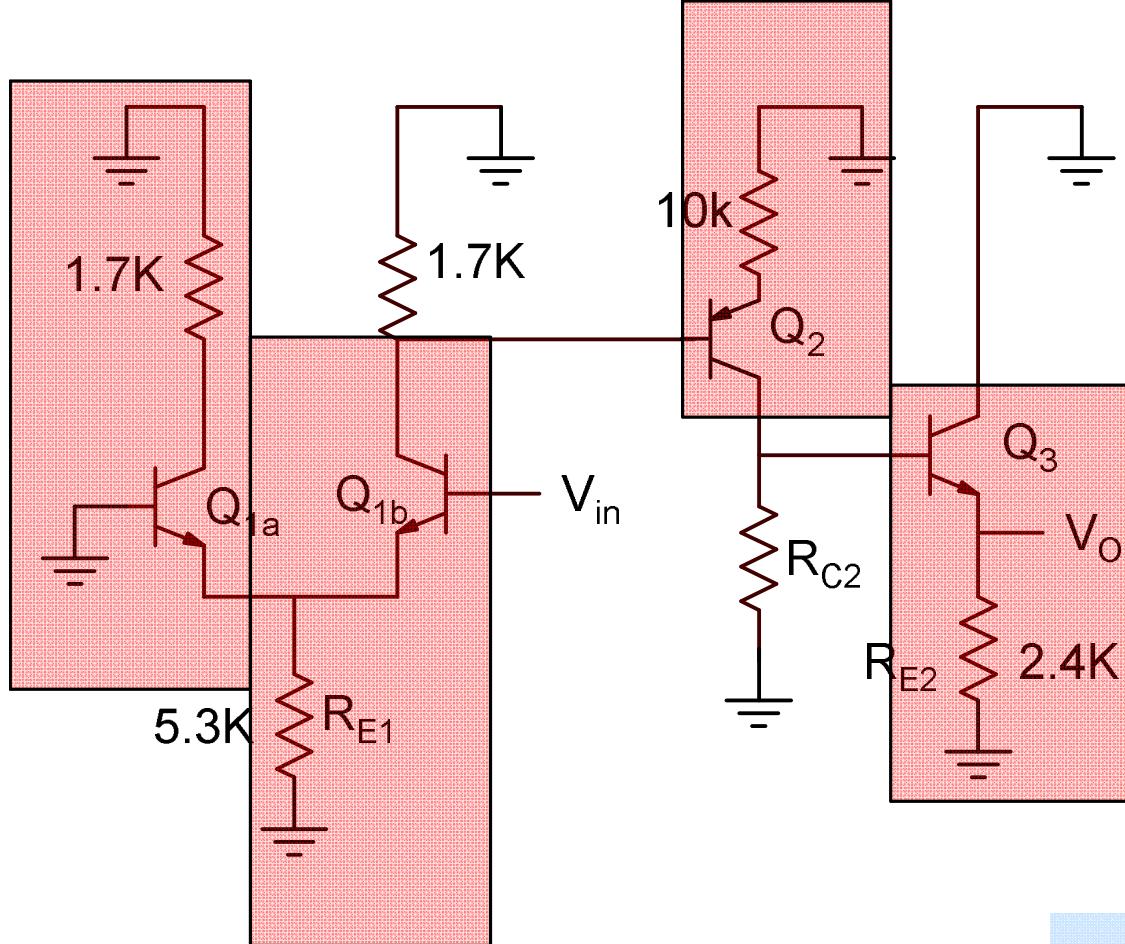


## Example-6

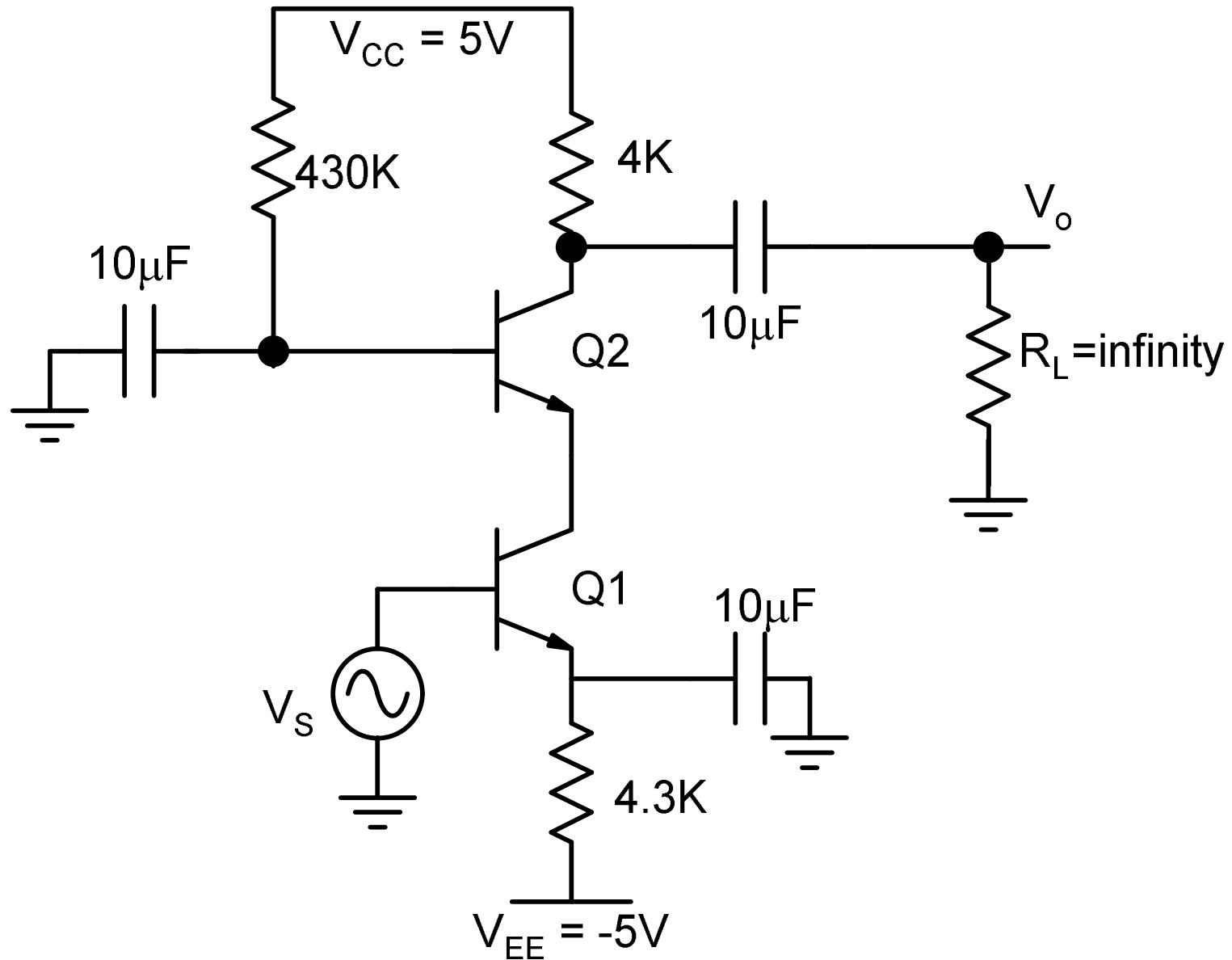


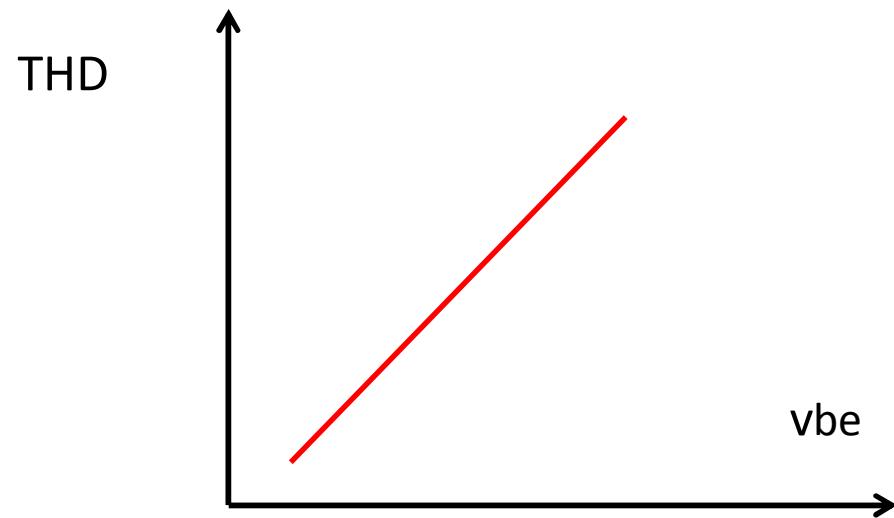
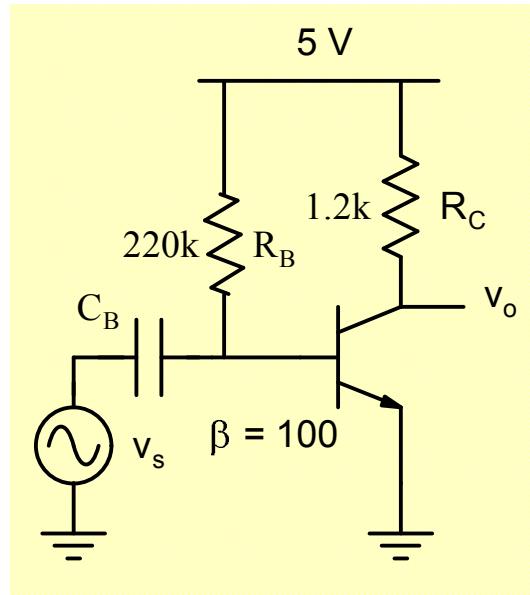
# COMMON Emitter AMPLIFIER WITH EMITTER DEGENERATION



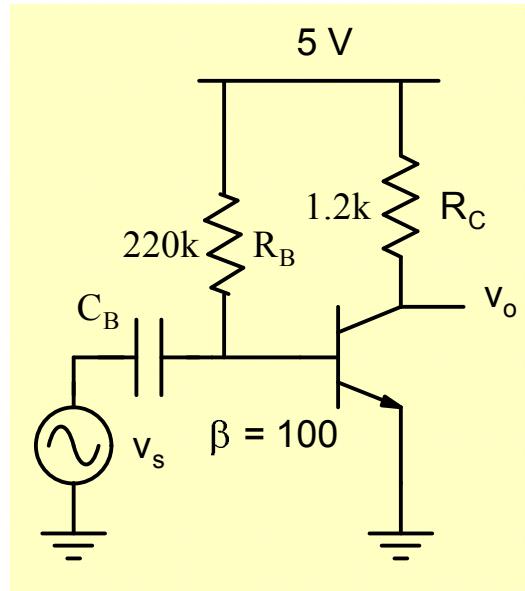


amplifier\_3\_voltage\_swing.CIR

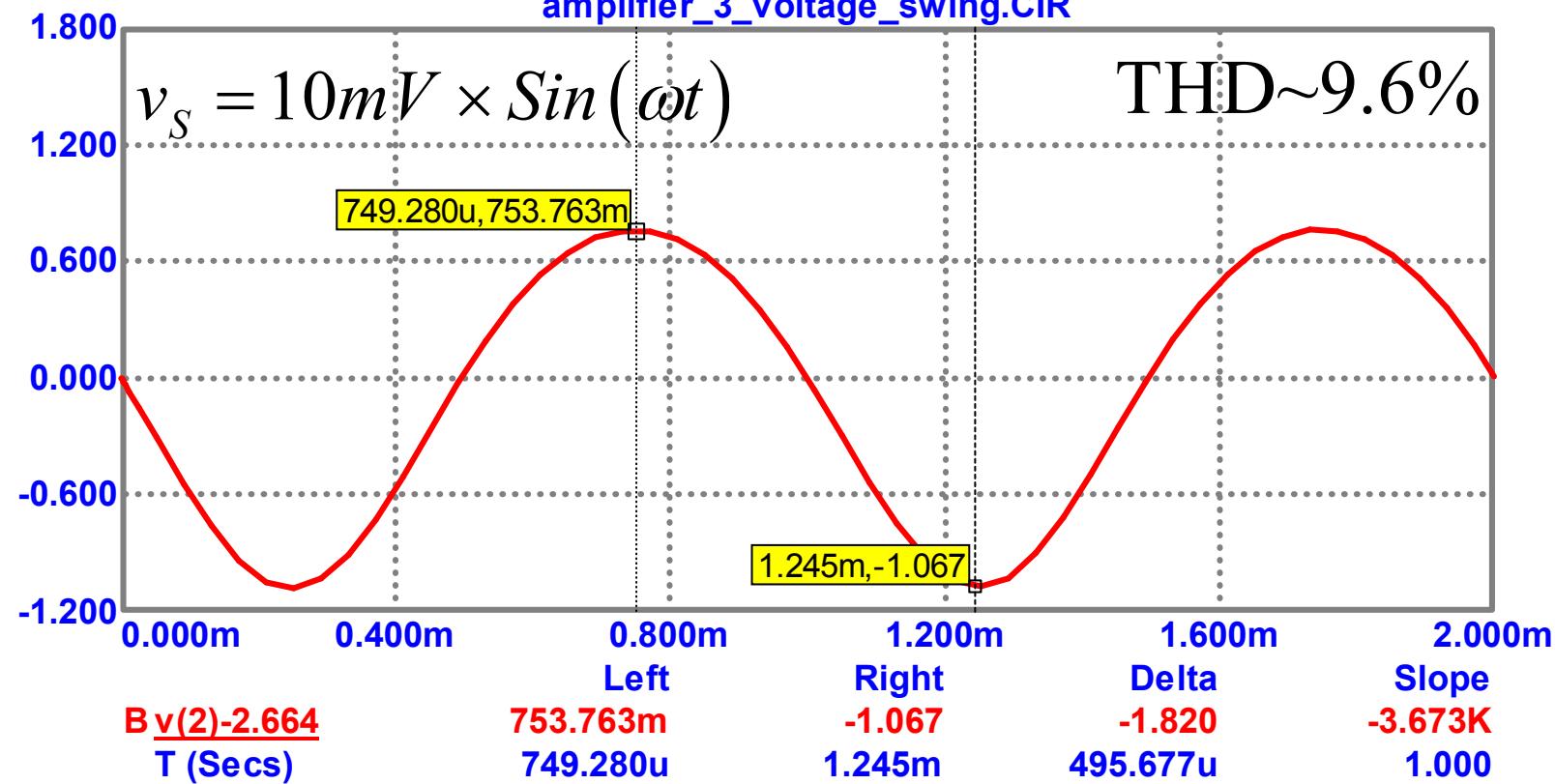

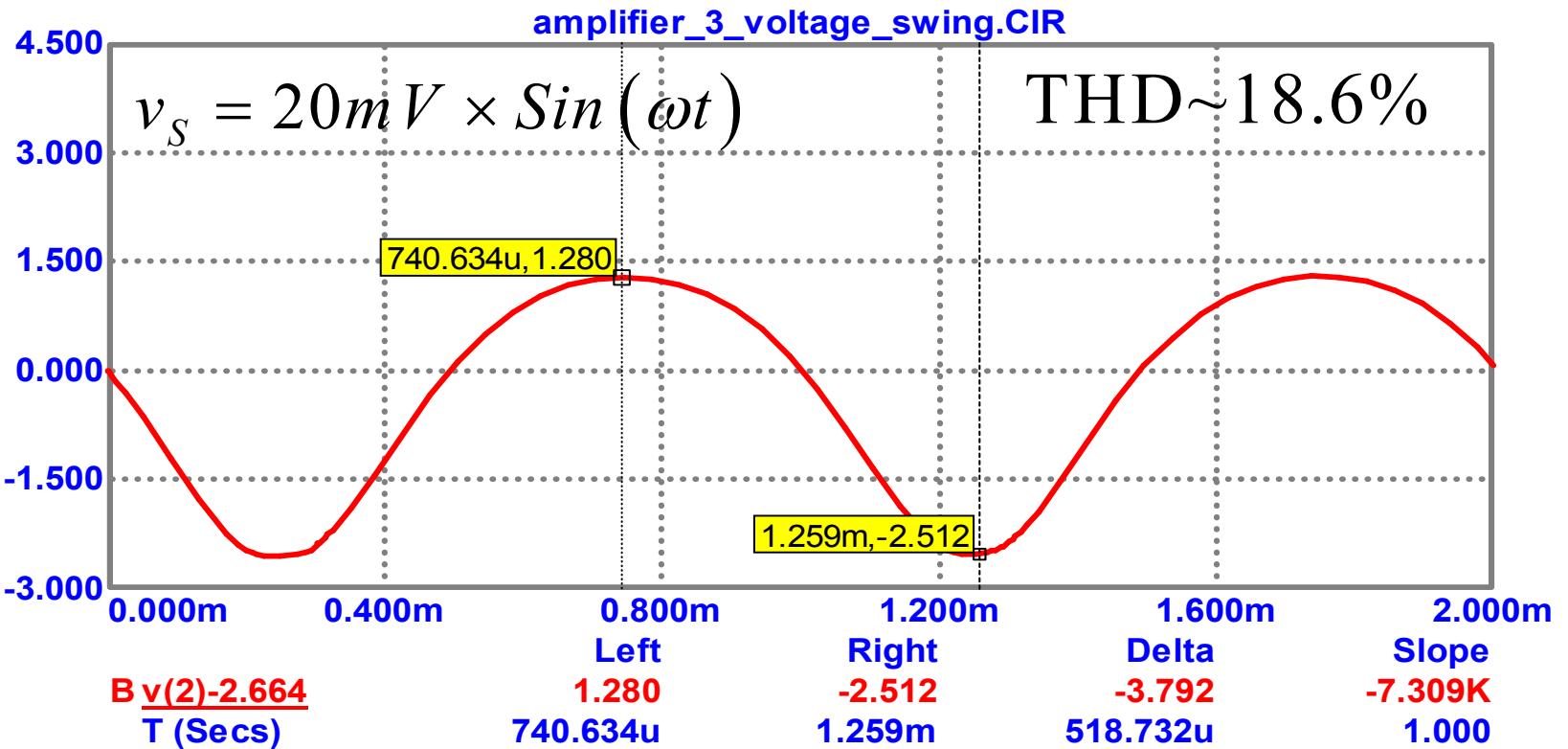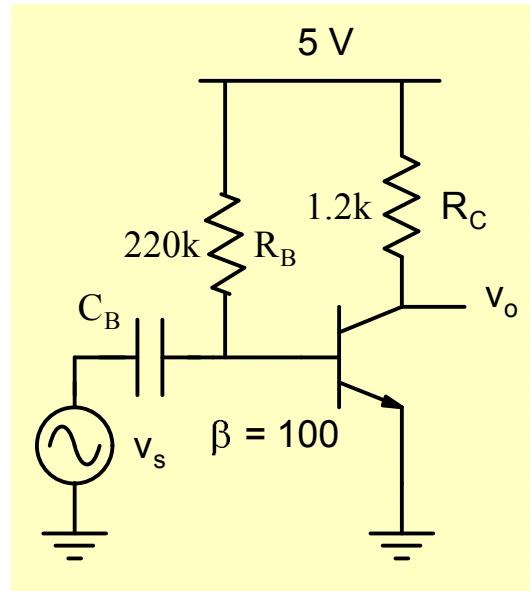


$$R_{in} \sim r_\pi(1 + g_m R_E)$$

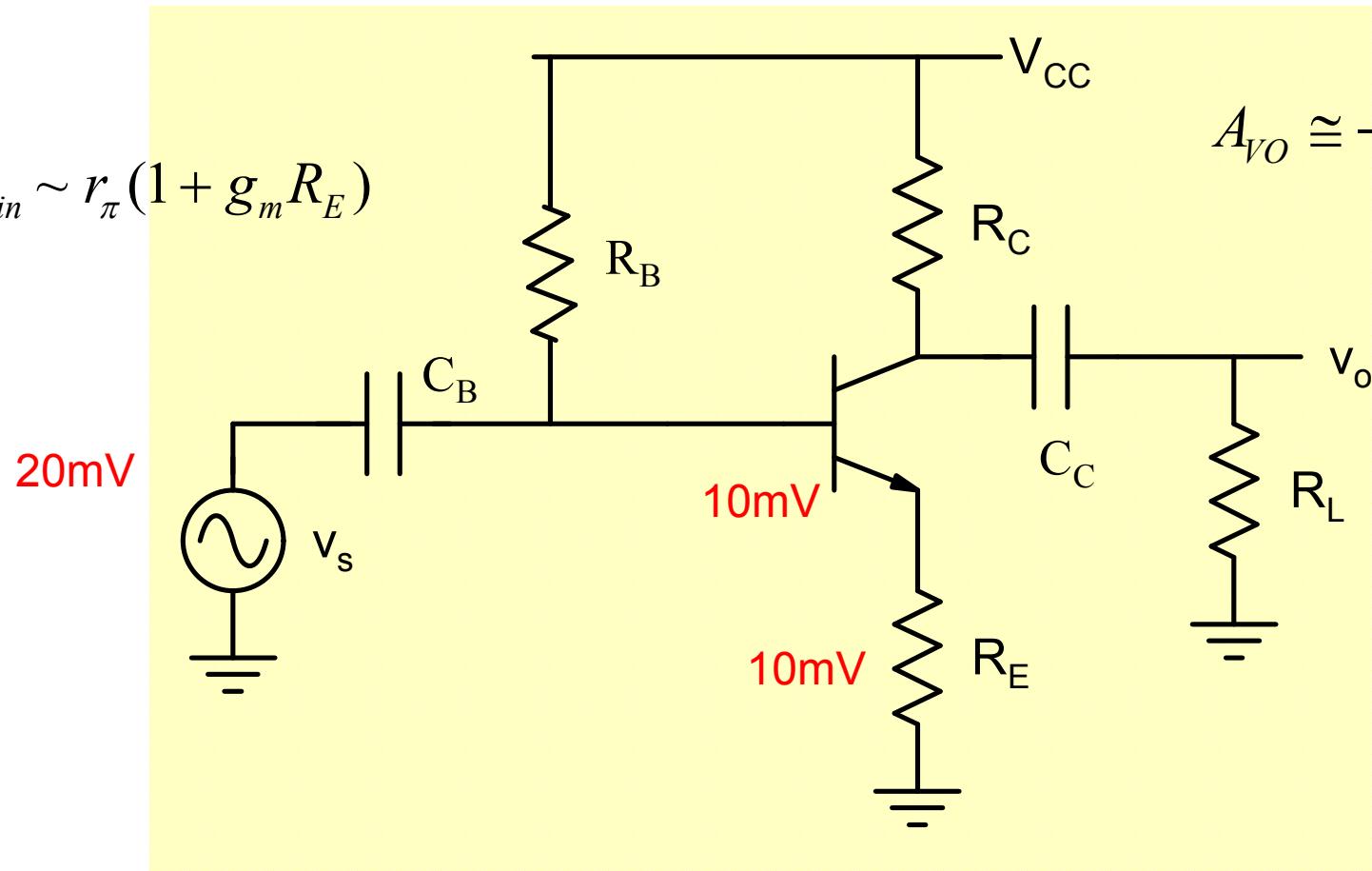

$$A_{VO} \cong -\frac{g_m R_C}{1 + g_m R_E}$$

$$v_{be} = \frac{v_S}{1 + g_m R_E}$$

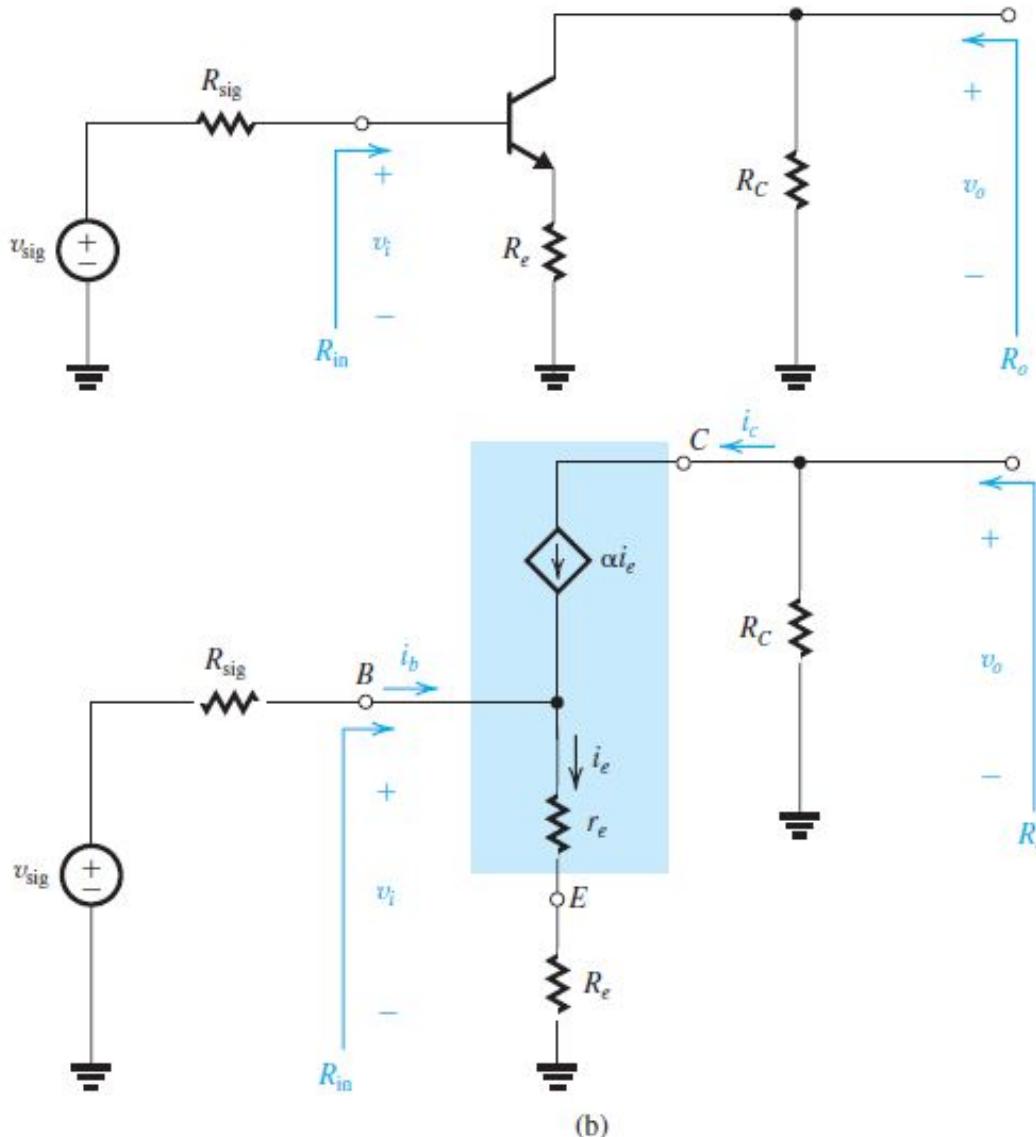

**Figure 6.52** The CE amplifier with an emitter resistance  $R_e$ ; (a) Circuit without bias details; (b) Equivalent circuit with the BJT replaced with its T model.

Another important consequence of including the resistance  $R_e$  in the emitter is that it enables the amplifier to handle larger input signals without incurring nonlinear distortion. This is because only a fraction of the input signal at the base,  $v_i$ , appears between the base and the emitter. Specifically, from the circuit in Fig. 6.52(b), we see that





$$\frac{v_\pi}{v_i} = \frac{r_e}{r_e + R_e} \simeq \frac{1}{1 + g_m R_e} \quad (6.89)$$


Thus, for the same  $v_\pi$ , the signal at the input terminal of the amplifier,  $v_i$ , can be greater than for the CE amplifier by the factor  $(1 + g_m R_e)$ .

To summarize, including a resistance  $R_e$  in the emitter of the CE amplifier results in the following characteristics:

1. The input resistance  $R_{in}$  is increased by the factor  $(1 + g_m R_e)$ .
2. The voltage gain from base to collector,  $A_v$ , is reduced by the factor  $(1 + g_m R_e)$ .
3. For the same nonlinear distortion, the input signal  $v_i$  can be increased by the factor  $(1 + g_m R_e)$ .
4. The overall voltage gain is less dependent on the value of  $\beta$ .
5. The high-frequency response is significantly improved (as we shall see in Chapter 9).



Sedra and Smith

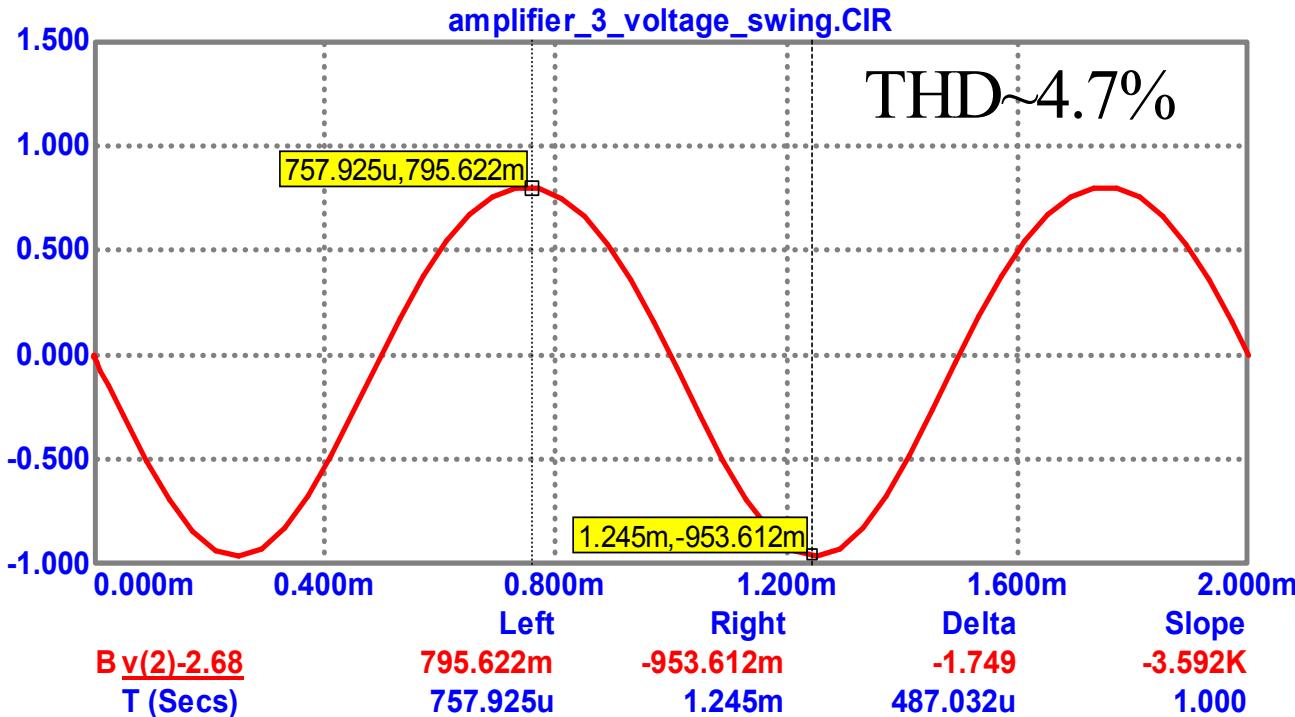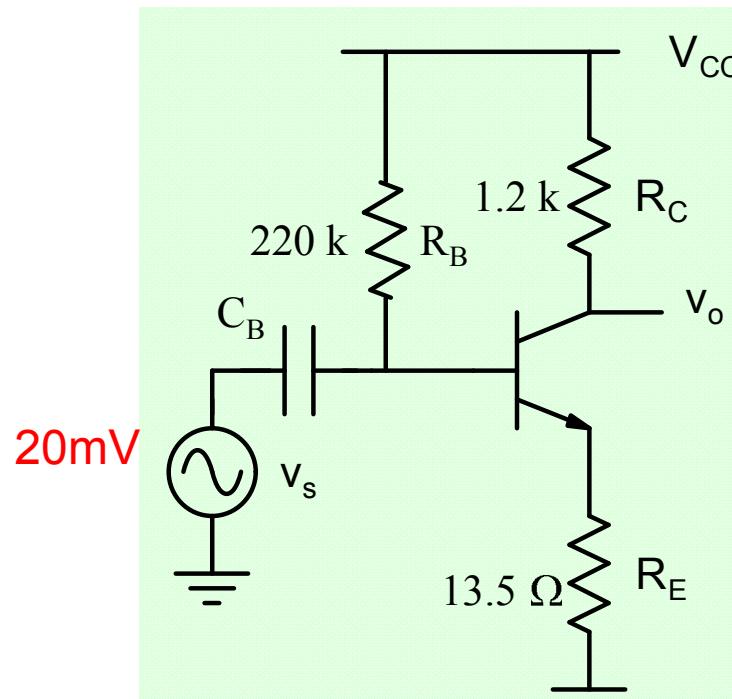

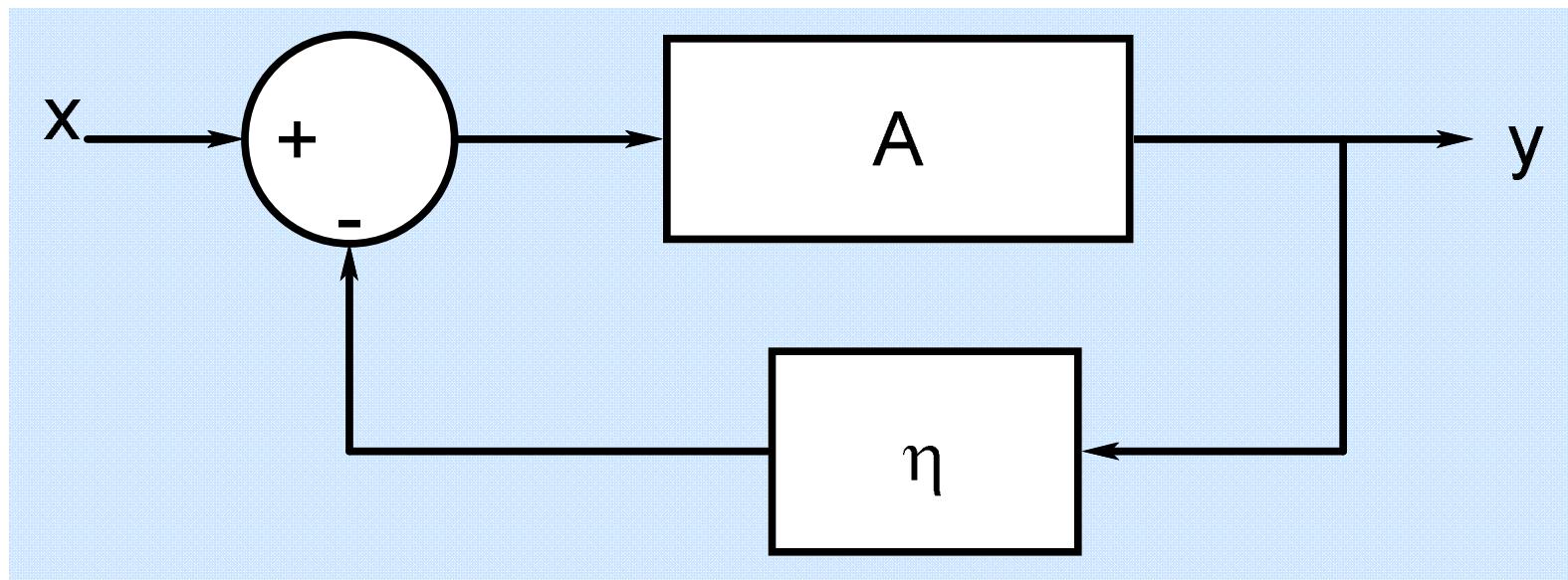


$$\frac{y}{x} = \frac{A}{1 + \eta A}$$

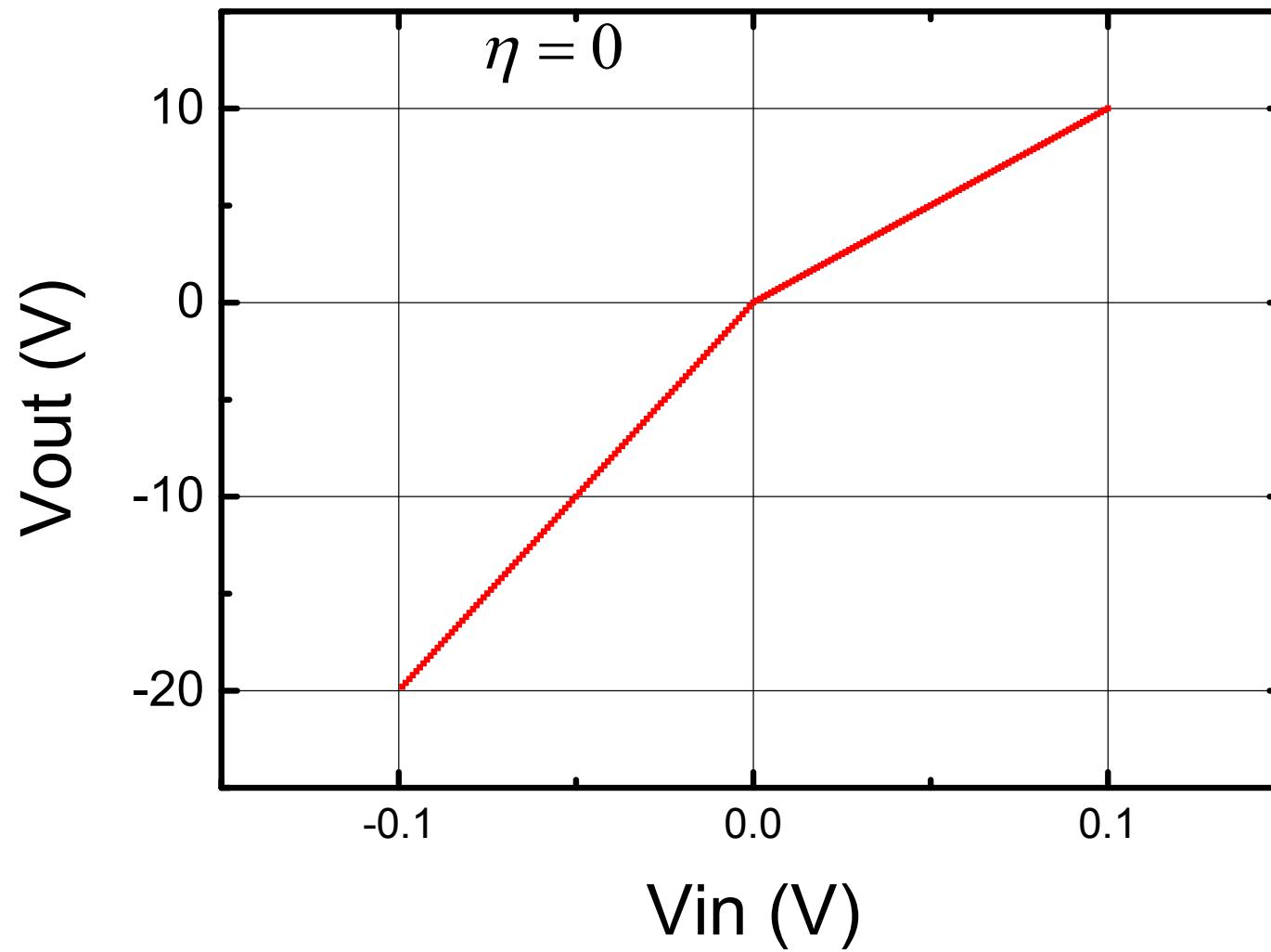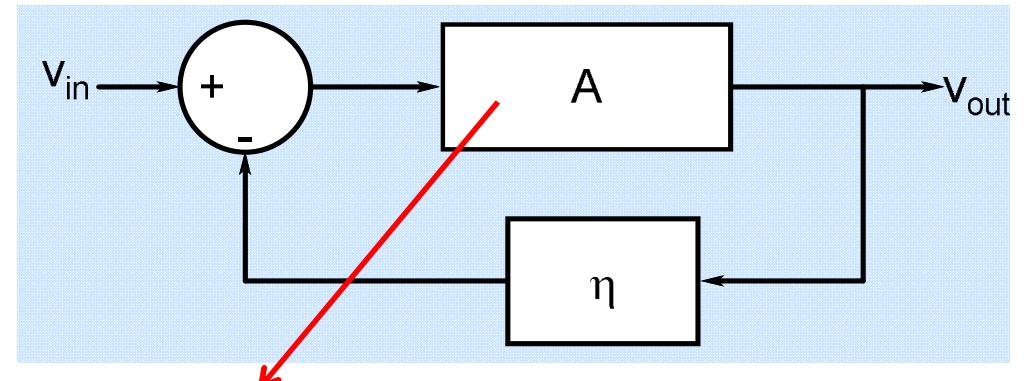
Harmonic distortion occurs due to nonlinearity. Negative feedback helps in reducing non-linearity



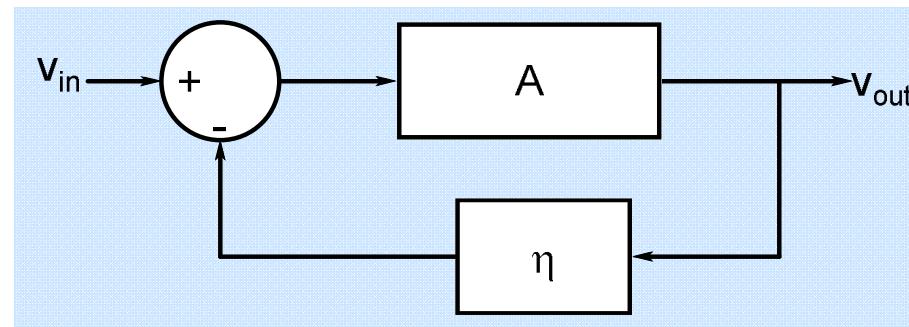
$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + \eta A}$$


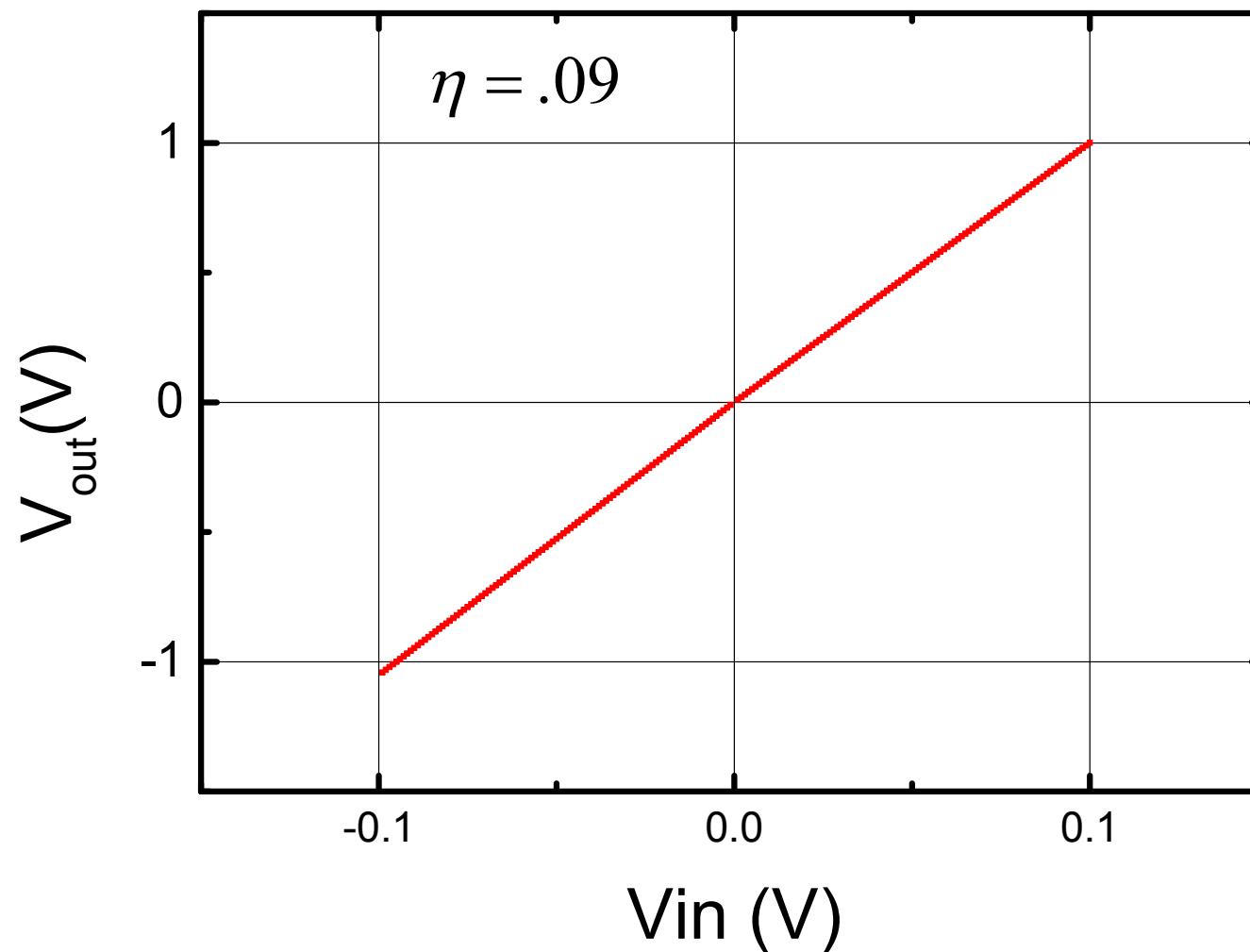
$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + \eta A}$$



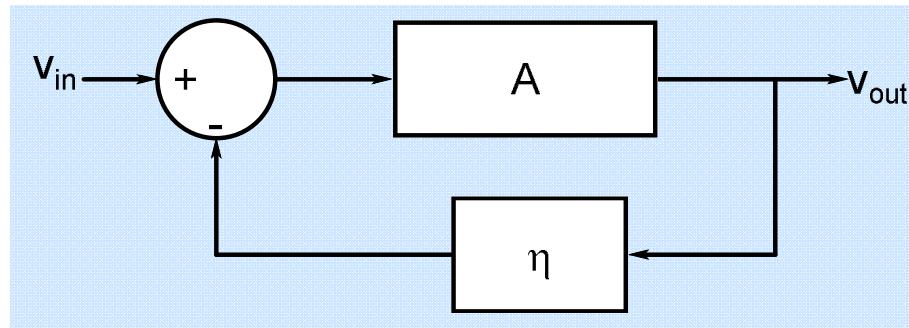

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + \eta A}$$

