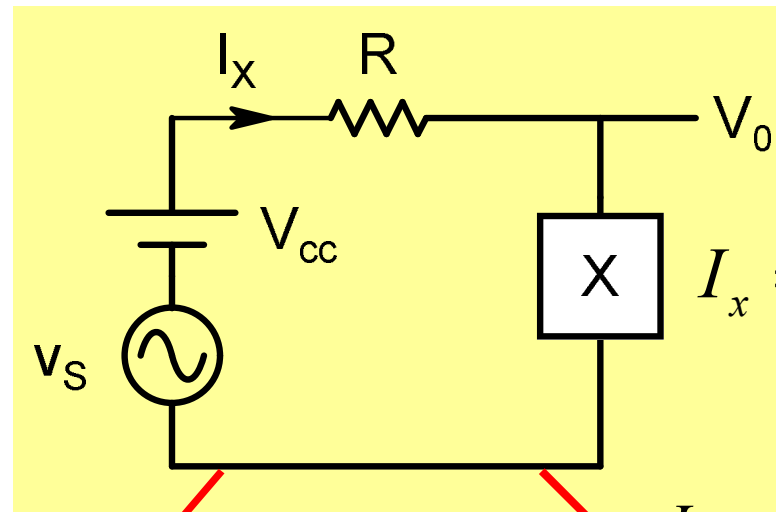


EE210: Microelectronics-I

Lecture-4 Small Signal Device Model-2


Instructor - Y. S. Chauhan

Slides from: B. Mazhari
Dept. of EE, IIT Kanpur




$$I_x = k \times \exp\left(\frac{V_x}{.026}\right)$$

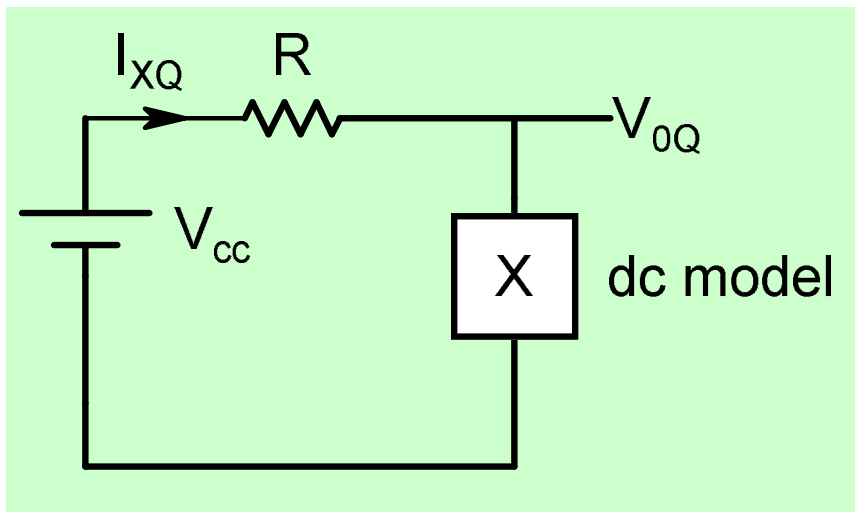
$$I_{xQ} + i_x = k \times \exp\left(\frac{V_{xQ} + v_x}{.026}\right)$$


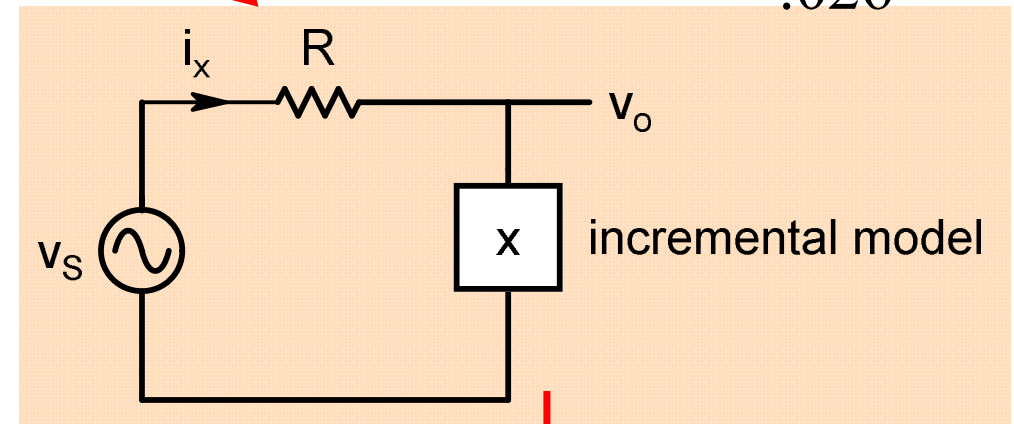
$$I_{xQ} = k \times \exp\left(\frac{V_{xQ}}{.026}\right)$$



incremental model

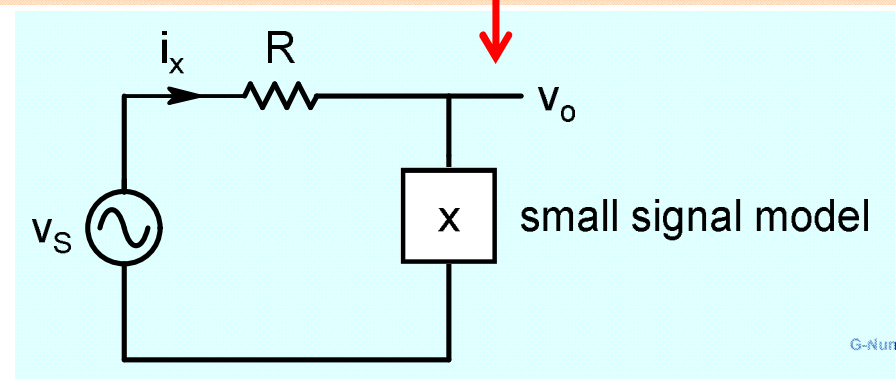

small signal model

$$I_x = k \times \exp\left(\frac{V_x}{.026}\right)$$


$$I_{XQ} + i_x = k \times \exp\left(\frac{V_{XQ} + v_x}{.026}\right)$$


$$i_x = k \times \exp\left(\frac{V_{XQ}}{.026}\right) \times \left\{ \exp\left(\frac{v_x}{.026}\right) - 1 \right\}$$

$$i_x \cong I_{XQ} \times \left(\frac{v_x}{.026}\right)$$


$$r_x \cong \frac{0.026}{I_{XQ}}$$

v_x (mV)	Error (%)
0.53	1
2.6	4.9
5.4	10
10	18
26	41.8

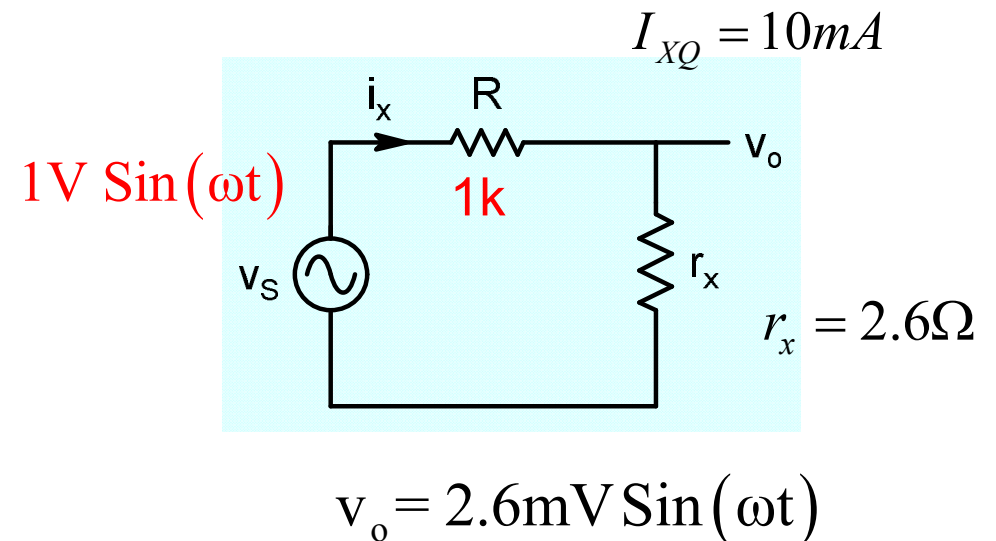


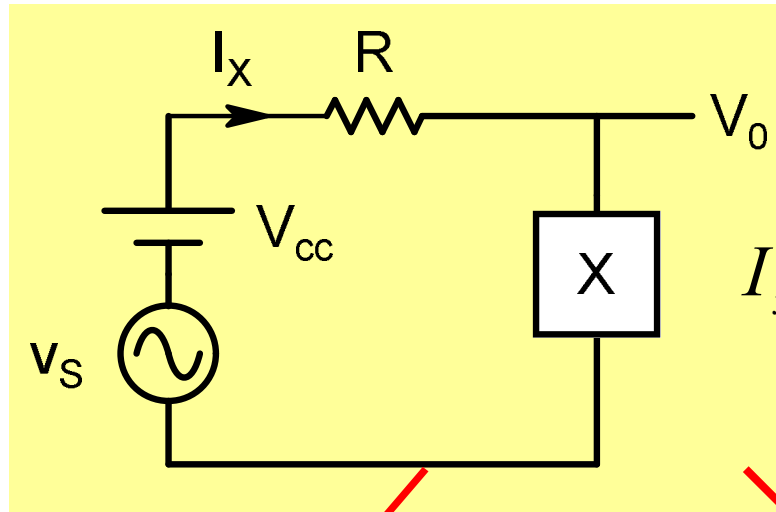
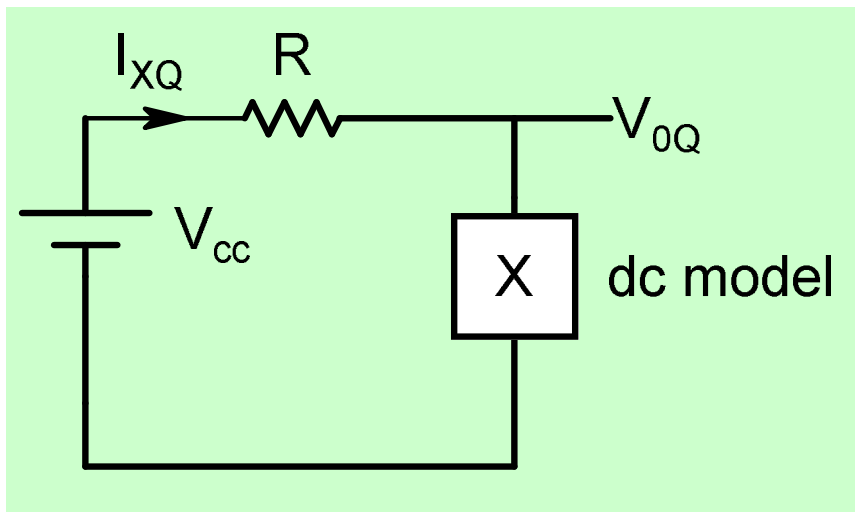
$$I_x = k \times \exp\left(\frac{V_x}{.026}\right) + C_x \frac{\partial V_x}{\partial t}$$


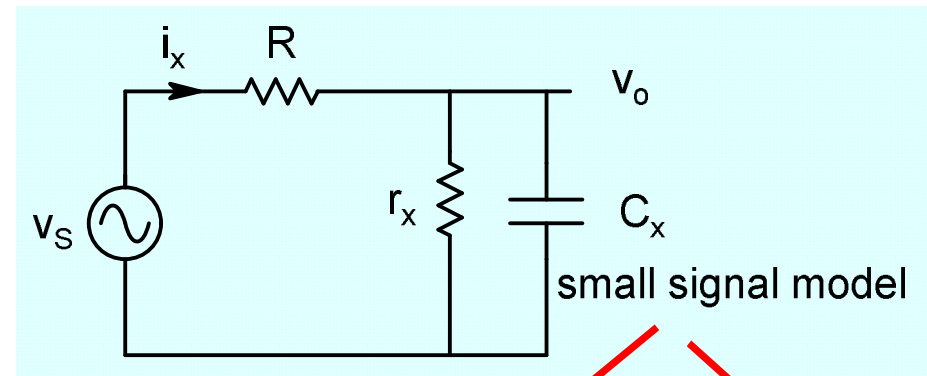
$$I_{xQ} = k \times \exp\left(\frac{V_{xQ}}{.026}\right)$$



Low frequency

High frequency



General approach for obtaining **small signal model** for a 2-terminal device (not containing capacitor/inductors)

$$I_x = f(V_x)$$


$$\begin{aligned} I_X + i_x &= f(V_X + v_x) \\ &= f(V_X) + v_x \left(\frac{df}{dV_x} \right) \Big|_{V_X} + \dots \end{aligned}$$

$$i_x = v_x / r_x \quad r_x = \frac{1}{\left. \frac{df}{dV_x} \right|_{V_X}}$$

Small signal model is a resistor

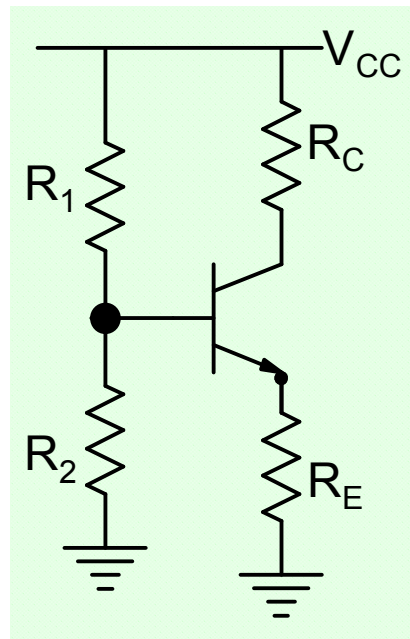
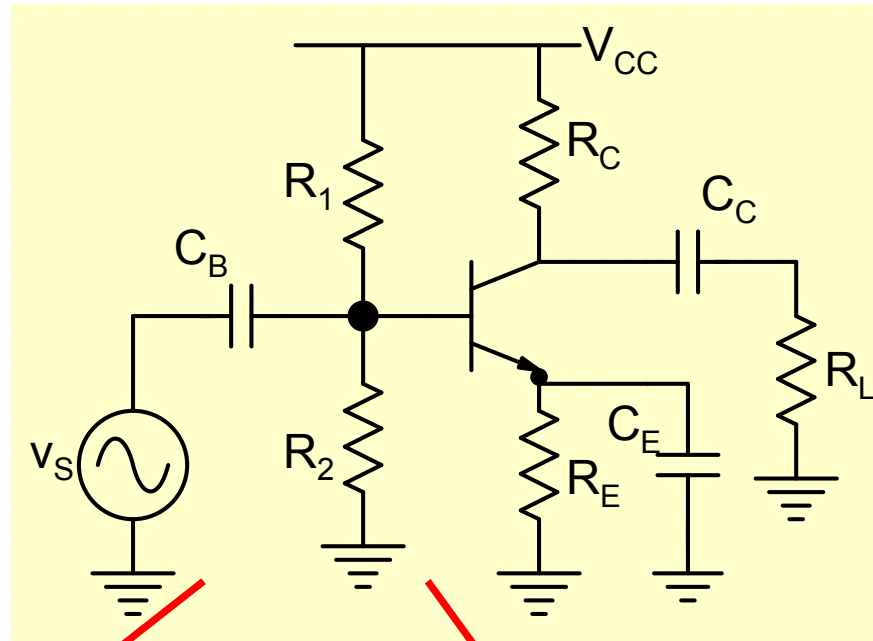


dc model

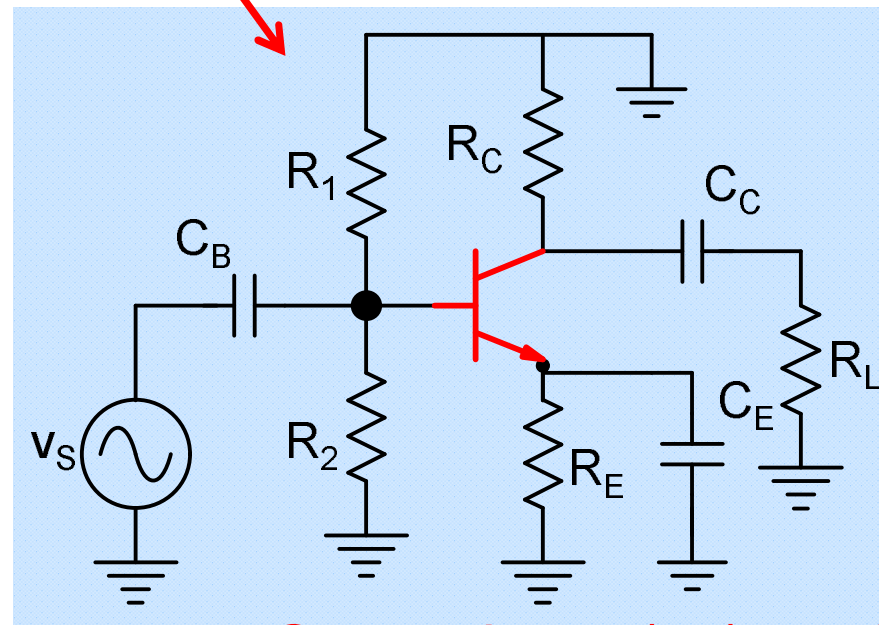


Small signal (ac) model

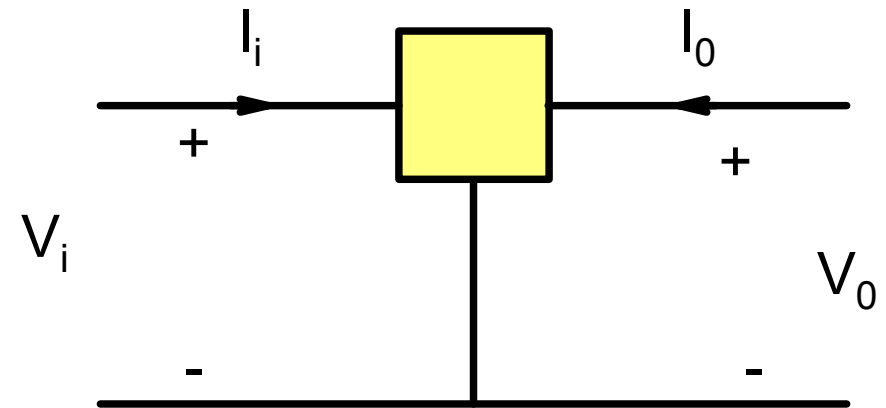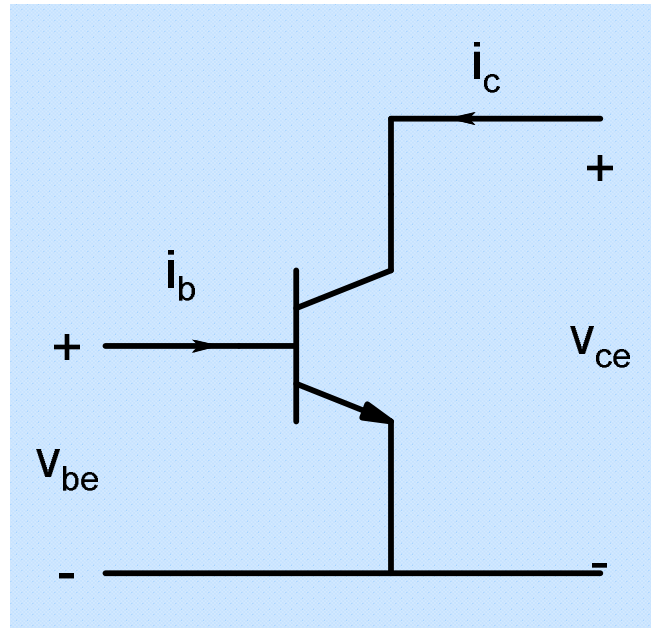Small signal model of a three terminal device



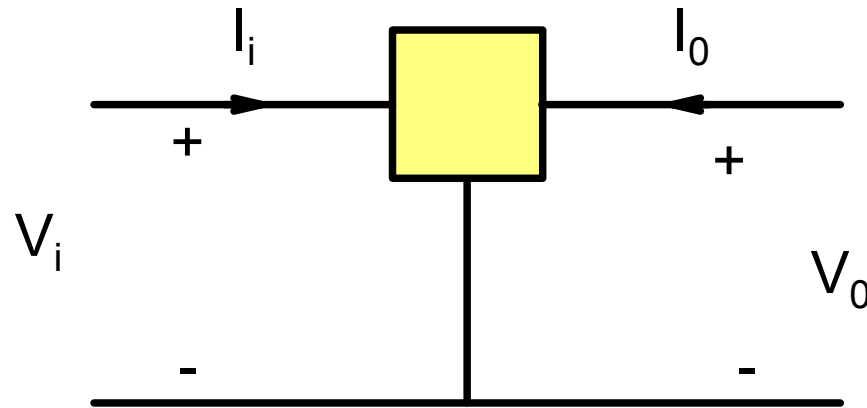General approach for obtaining small **signal model** for a 3-terminal unilateral device



Unilateral:

(Output does not affect the input)

$$I_o = f_o(V_i, V_o)$$

$$I_i = f_i(V_i)$$


$$I_i = f_i(V_i)$$

$$I_i + i_i = f_i(V_i + v_i)$$

$$\Rightarrow i_i = v_i \left. \frac{\delta f_i}{\delta V_i} \right|_{V_i} = \frac{v_i}{r_i}$$

$$r_i = \frac{1}{\left. \frac{\delta f_i}{\delta V_i} \right|_{V_i}}$$

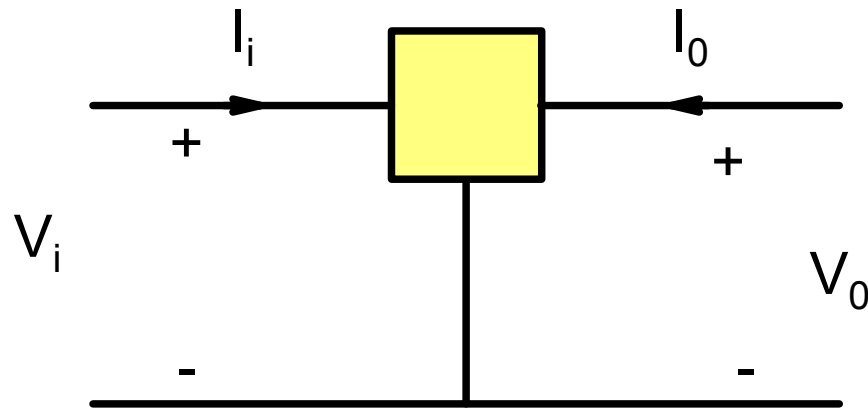From the input port, the device appears as a resistance



Output port:

$$I_O = f_O(V_i, V_O)$$


$$I_O + i_o = f_O(V_i + v_i, V_O + v_o)$$

$$I_O + i_o = f_O(V_i, V_o) + v_i \frac{\partial f_O}{\partial V_i} \bigg|_{V_o} + v_o \frac{\partial f_O}{\partial V_O} \bigg|_{V_i} + \dots$$



$$i_o \cong v_i \frac{\partial f_O}{\partial V_i} \bigg|_{V_o} + v_o \frac{\partial f_O}{\partial V_O} \bigg|_{V_i}$$

$$i_o = g_m v_i + \frac{v_o}{r_o}$$

$$g_m = \frac{\partial f_O}{\partial V_i} \bigg|_{V_o} \quad r_o = \frac{1}{\frac{\partial f_O}{\partial V_O} \bigg|_{V_i}}$$


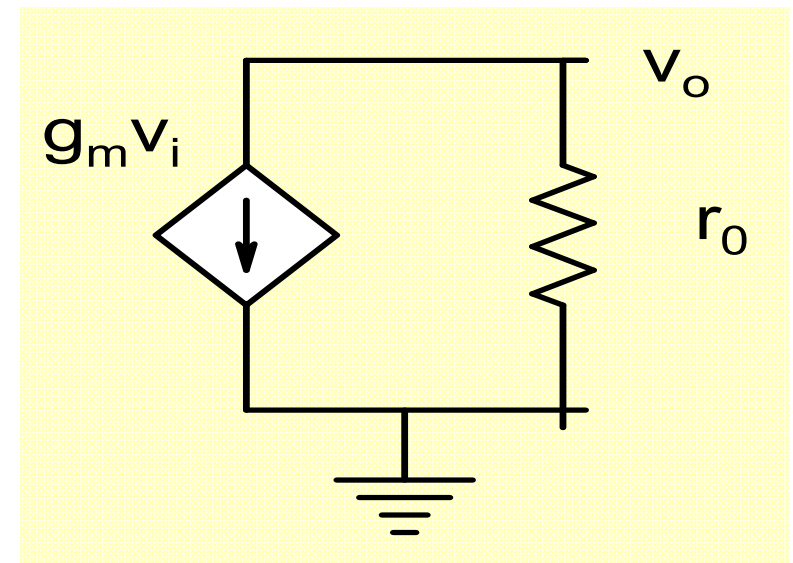


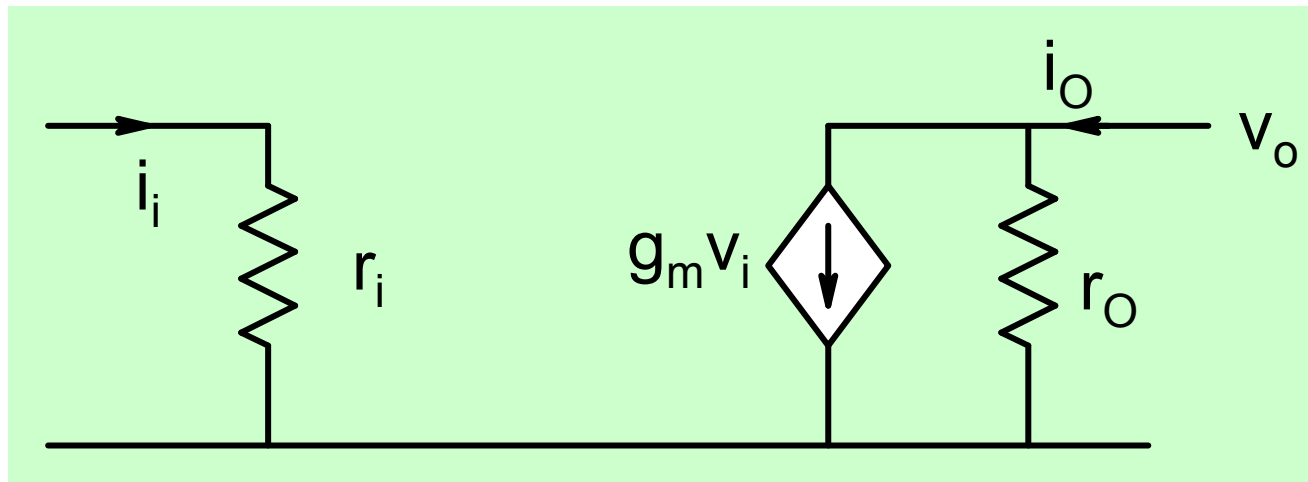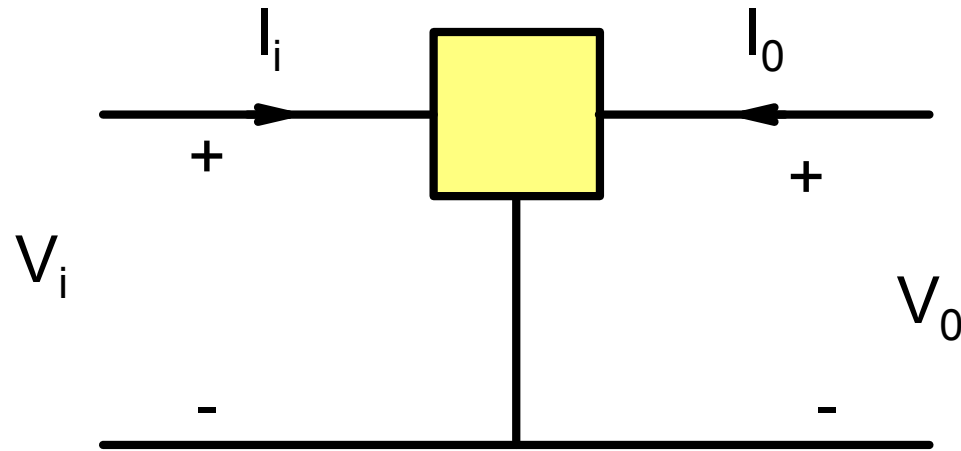Complete **small signal model** (dc) for a 3-terminal unilateral device.




Example Build a small signal model around the bias point

$$V_{ab} = 1V; V_{cb} = 2V$$

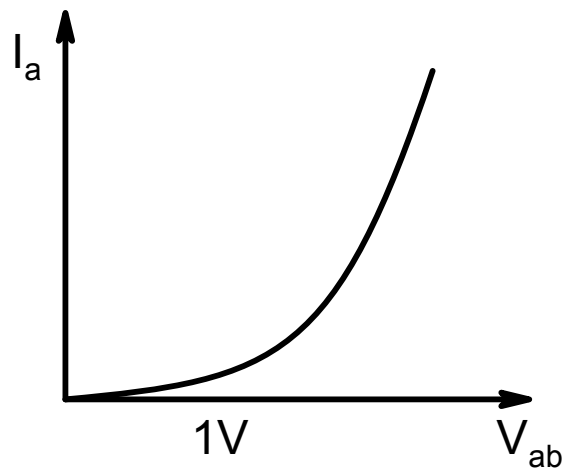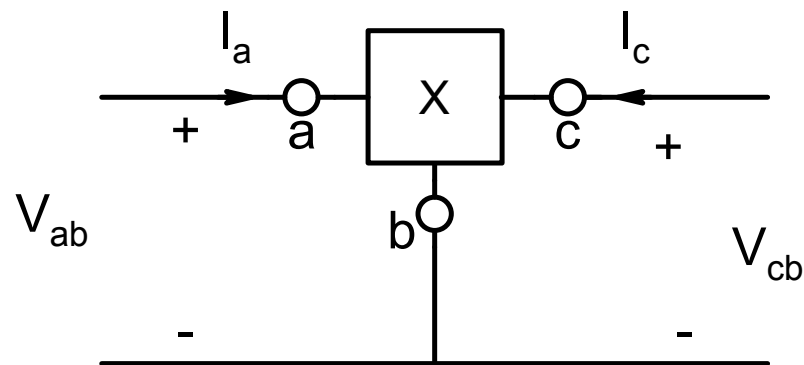


$$I_a = 10^{-5} \times V_{ab}^2$$

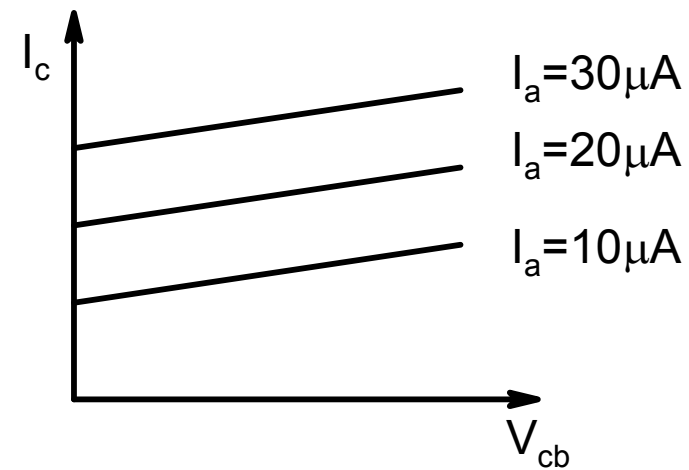

$$I_c = 100 \times I_a + 10^{-5} \times V_{cb}$$

Bias point: $V_{ab} = 1V$; $V_{cb} = 2V$

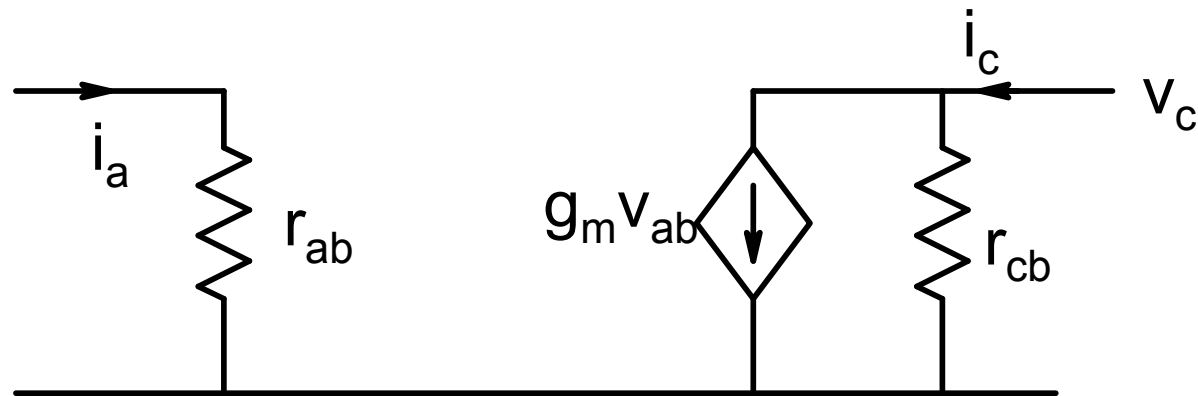

$$I_a = 10^{-5} \times V_{ab}^2$$

$$I_a = 100 \times I_a + 10^{-5} \times V_{cb}$$

$$I_i = f_i(V_i)$$

$$I_o = f_o(V_i, V_o)$$

$$r_i = \frac{1}{\left. \frac{\delta f_i}{\delta V_i} \right|_{V_i}}$$

$$r_{ab} = \left. \frac{1}{\frac{\partial I_a}{\partial V_{ab}}} \right|_{V_{ab}=1V}$$

$$g_m = \left. \frac{\delta f_0}{\delta V_i} \right|_{V_o}$$

$$r_o = \left. \frac{1}{\frac{\delta f_0}{\delta V_o}} \right|_{V_i}$$