


EE210: Microelectronics-I

Lecture-19 :CE Amplifier Lower Cutoff Frequency

Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur

Example

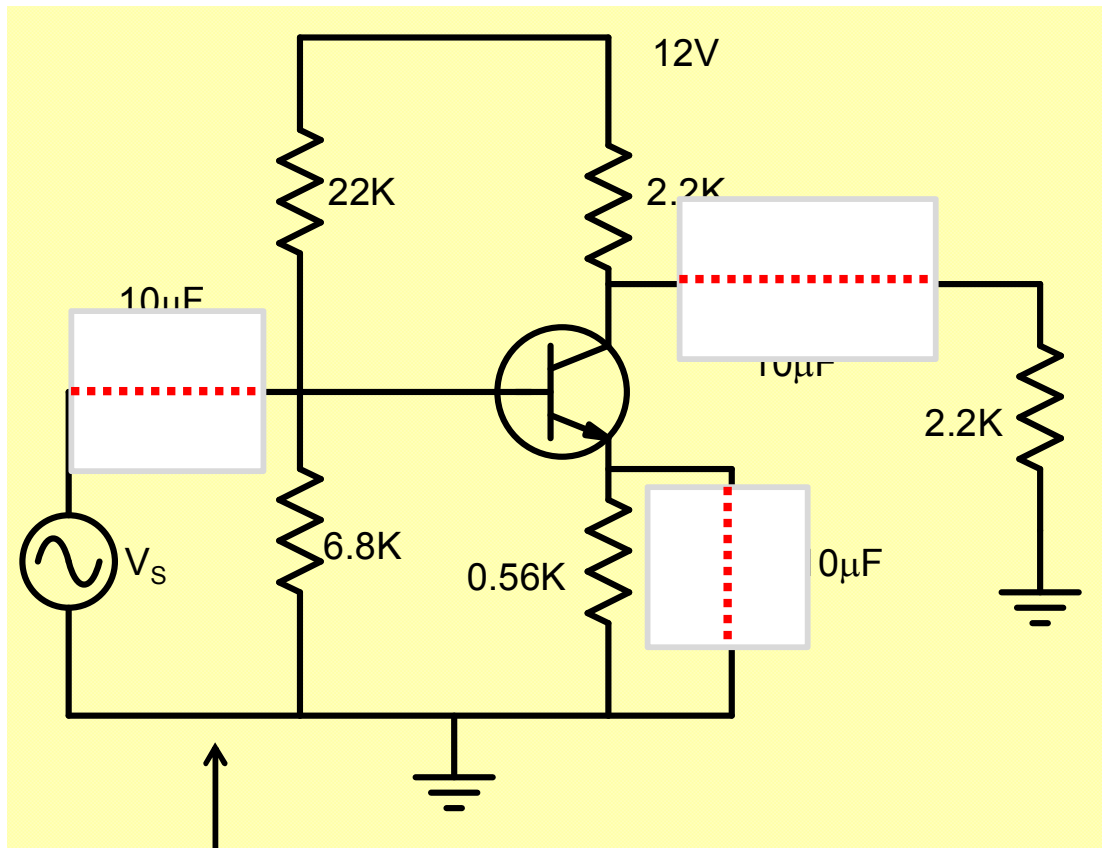

$$I_{CQ} = 3.48mA$$

$$r_{\pi} = 0.74K; g_m = 0.13\Omega^{-1}$$


$$A_V = -147.5$$

$$f_B = 24.4Hz$$

$$f_C = 3.6Hz$$


$$f_E = 2.18KHz$$

$$f_L \cong 2.18KHz$$

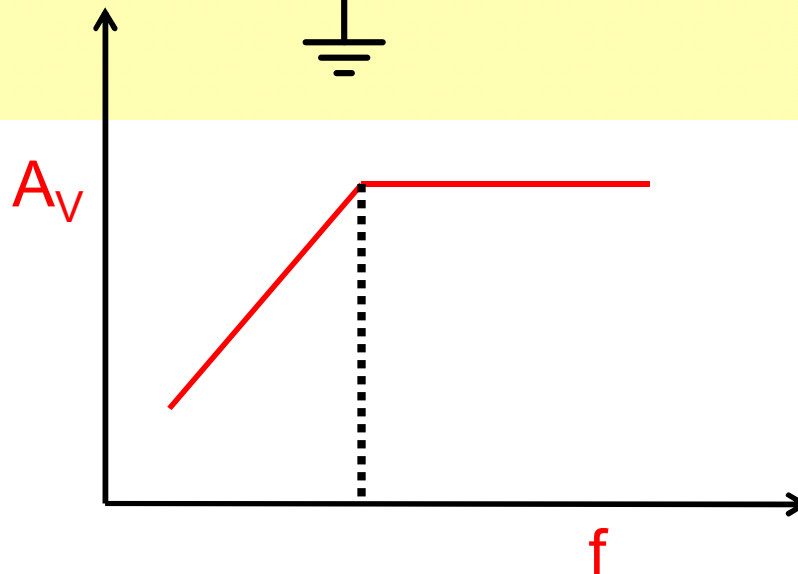

Q.1 Determine the lower cutoff frequency for the amplifier shown below. The transistor is biased at 2.6mA.

$$\beta_F = 100; V_T = 26mV$$

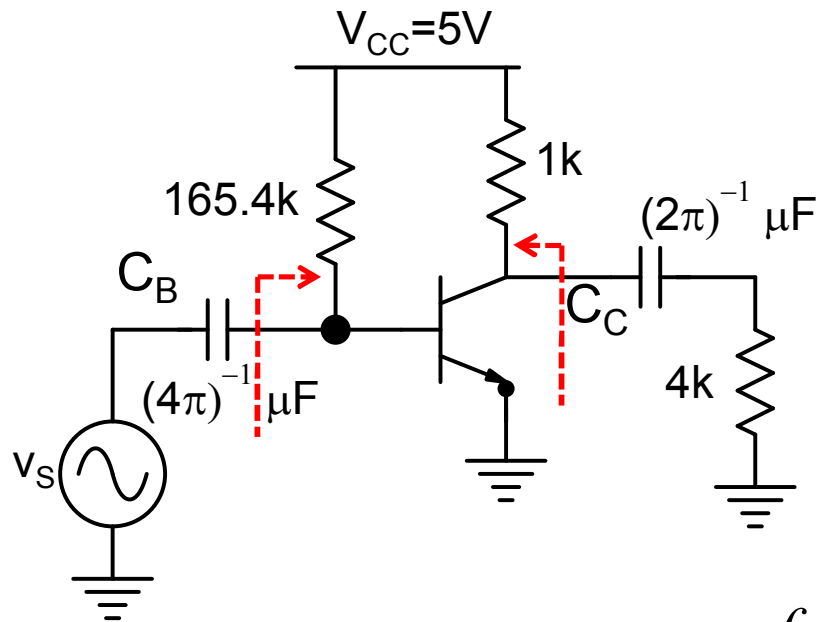

$$r_\pi = \frac{V_T}{I_{CQ}} \beta = 1k \quad f_b = \frac{1}{2\pi C_B R_{in}} = 2kHz$$


$$R_{in} = R_B \parallel r_\pi \sim 1k$$

$$f_c = \frac{1}{2\pi C_C \times (R_C + R_L)} = 200Hz$$


$$f_L \cong f_b = 2kHz$$

In the amplifier shown below, is it possible to obtain the following values for open circuit voltage gain, lower cutoff frequency and output resistance :

$|A_{vo}| \geq 150$; $f_L \leq 100\text{Hz}$; $R_o \leq 1\text{k}\Omega$ simultaneously? Justify your answer

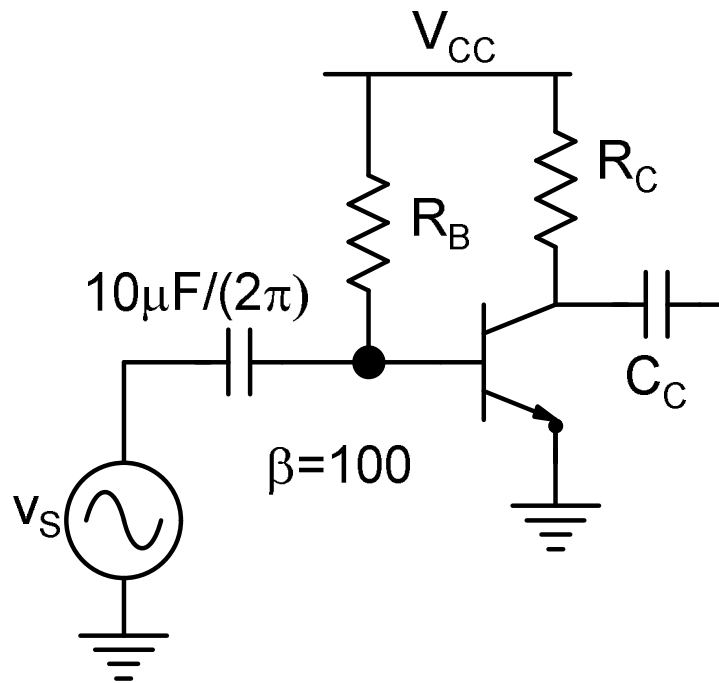


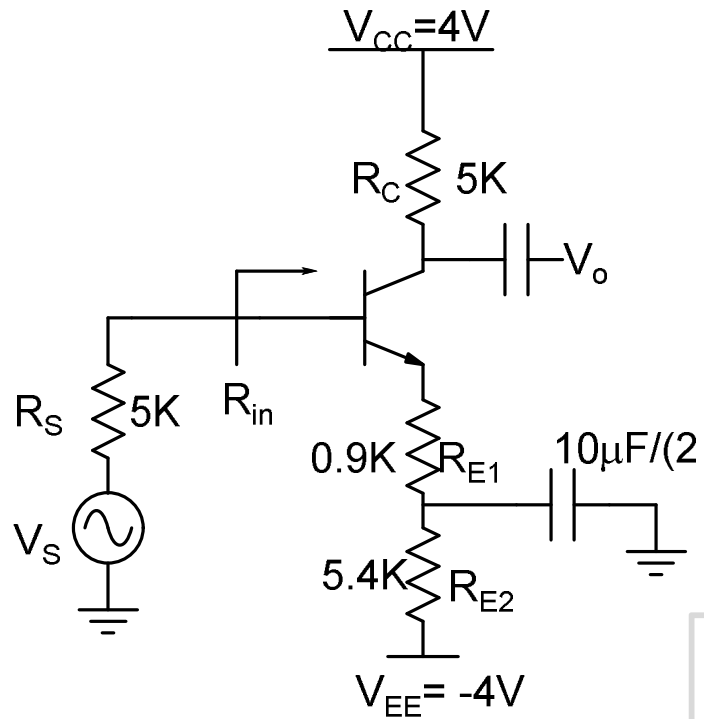Q.3 Determine lower cutoff frequency of the amplifier shown below




2


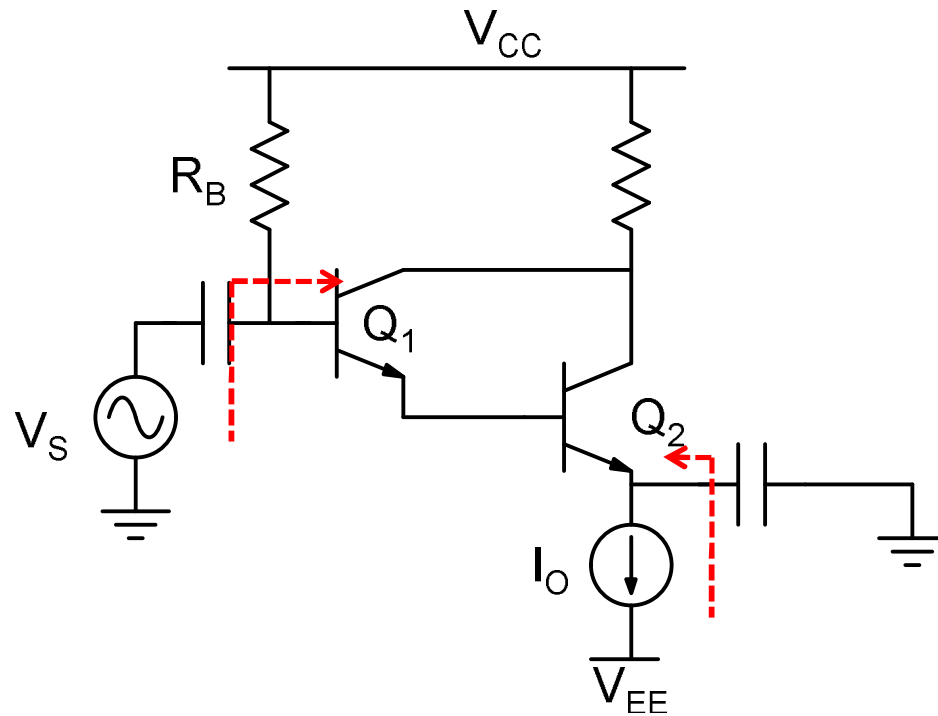
Q.4 Determine lower cutoff frequency of the amplifier shown below




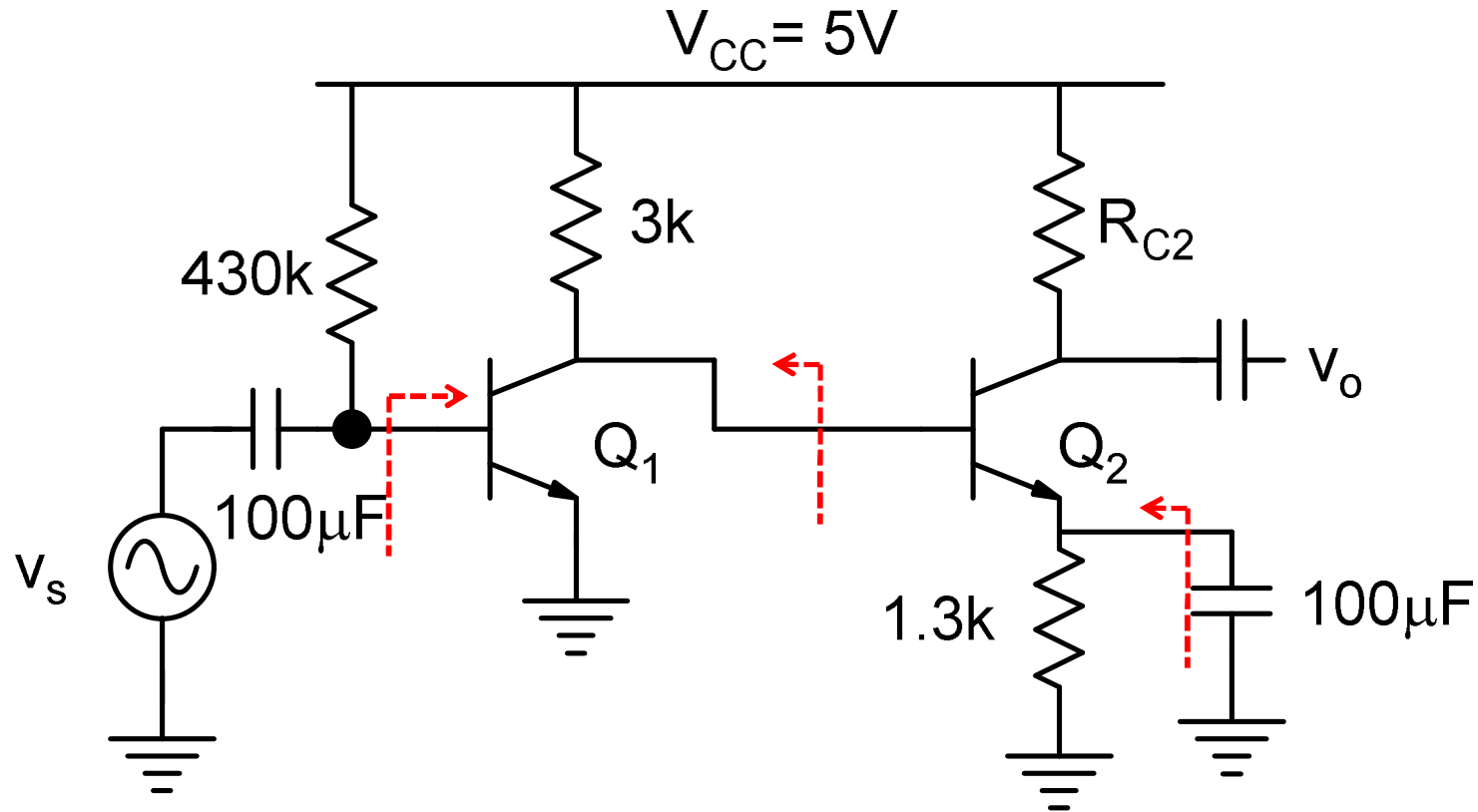Q.5 Determine lower cutoff frequency of the amplifier shown below



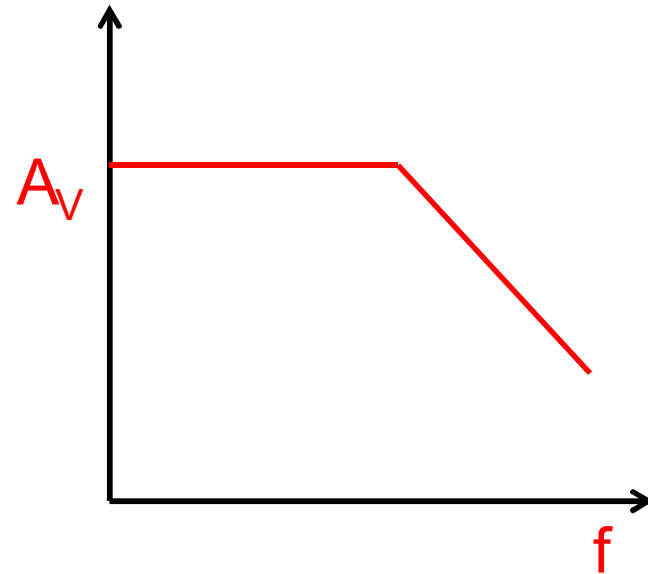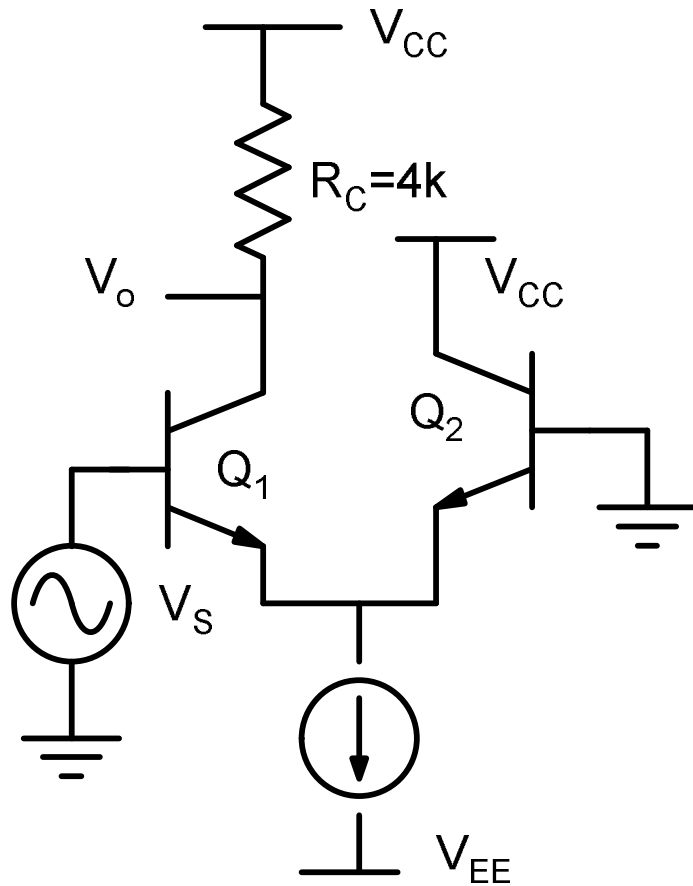Q.6 Determine lower cutoff frequency of the amplifier shown below



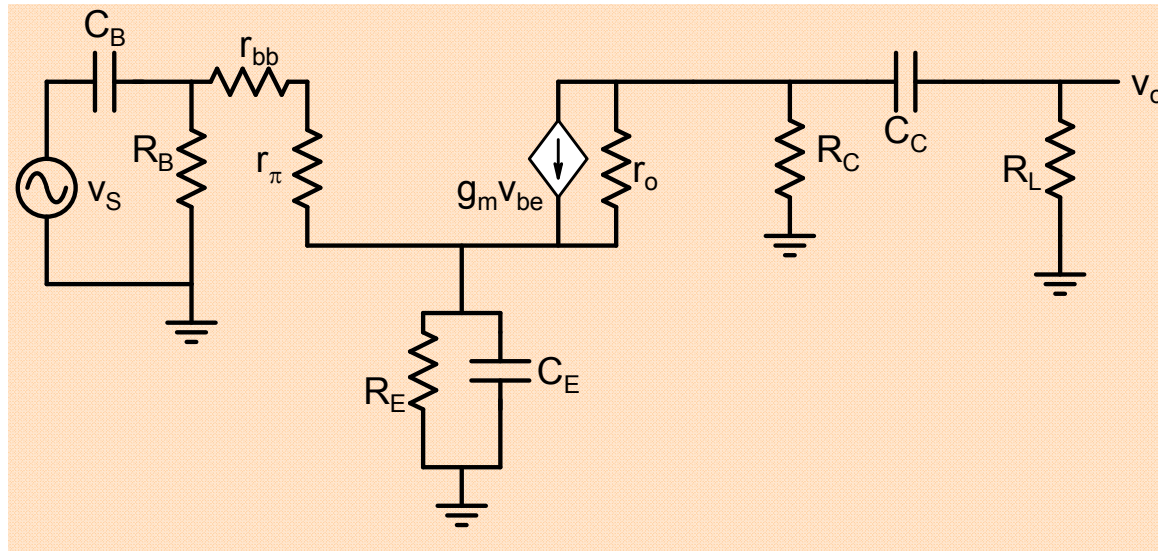

$$H(j\omega) = \frac{v_o}{v_s}$$

$$(-H_{gm_q1} C_c C_B R_B R_C R_L) s^2$$

$$(-H_{gm_q1} C_c C_E C_B R_B R_C R_E R_L) s^3$$

$$(+G_{be_q1} R_E + G_{be_q1} R_B + H_{gm_q1} R_E + 1)$$

$$(+G_{be_q1} C_B R_E R_S + G_{be_q1} C_B R_B R_S + G_{be_q1} C_B R_B R_E + H_{gm_q1} C_B R_E R_S + H_{gm_q1} C_B R_B R_E + C_B R_S + C_B R_B + G_{be_q1} C_E R_B R_E + C_E R_E + G_{be_q1} C_c R_E R_L + G_{be_q1} C_c R_C R_E + G_{be_q1} C_c R_B R_L + G_{be_q1} C_c R_B R_C + H_{gm_q1} C_c R_E R_L + H_{gm_q1} C_c R_C R_E + C_c R_L + C_c R_C) s$$

$$(+G_{be_q1} C_E C_B R_B R_E R_S + C_E C_B R_E R_S + C_E C_B R_B R_E + G_{be_q1} C_c C_B R_E R_L R_S + G_{be_q1} C_c C_B R_C R_E R_S + G_{be_q1} C_c C_B R_B R_L R_S + G_{be_q1} C_c C_B R_B R_E R_L + G_{be_q1} C_c C_B R_B R_C R_S + G_{be_q1} C_c C_B R_B R_C R_E + H_{gm_q1} C_c C_B R_E R_L R_S + H_{gm_q1} C_c C_B R_C R_E R_S + H_{gm_q1} C_c C_B R_B R_E R_L + H_{gm_q1} C_c C_B R_B R_C R_E + C_c C_B R_L R_S + C_c C_B R_C R_S + C_c C_B R_B R_L + C_c C_B R_B R_C + G_{be_q1} C_c C_E R_B R_E R_L + G_{be_q1} C_c C_E R_B R_C R_E + C_c C_E R_E R_L + C_c C_E R_C R_E) s^2$$

$$(+G_{be_q1} C_c C_E C_B R_B R_E R_L R_S + G_{be_q1} C_c C_E C_B R_B R_C R_E R_S + C_c C_E C_B R_E R_L R_S + C_c C_E C_B R_C R_E R_S + C_c C_E C_B R_B R_E R_L + C_c C_E C_B R_B R_C R_E) s^3$$

$$(-H_{gm_q1} C_c C_B R_C R_L) s^2$$

$$(-H_{gm_q1} C_c C_E C_B R_C R_E R_L) s^3$$

$$(+G_{be_q1})$$

$$(+G_{be_q1} C_B R_E + H_{gm_q1} C_B R_E + C_B + G_{be_q1} C_E R_E + G_{be_q1} C_c R_L + G_{be_q1} C_c R_C) s$$

$$(+C_E C_B R_E + G_{be_q1} C_c C_B R_E R_L + G_{be_q1} C_c C_B R_C R_E + H_{gm_q1} C_c C_B R_E R_L + H_{gm_q1} C_c C_B R_C R_E + C_c C_B R_L + C_c C_B R_C + G_{be_q1} C_c C_E R_E R_L + G_{be_q1} C_c C_E R_C R_E) s^2$$

$$(+C_c C_E C_B R_E R_L + C_c C_E C_B R_C R_E) s^3$$

Among important elements of engineering analysis & design are:

- ❑ Judicious use of approximations (~)
- ❑ Iterative approach
- ❑ divide and conquer
- ❑ Reuse
- ❑ division of labor
- ❑