

EE210: Microelectronics-I

Lecture-23 :Common Base Amplifier-1

Instructor - Y. S. Chauhan


Slides - B. Mazhari
Dept. of EE, IIT Kanpur

Outline

- ☐ Voltage Gain, Input and Output Resistance, current gain
- ☐ Comparison with CE amplifier
- ☐ Frequency response
- ☐ Cascode amplifier


Common Base Amplifier

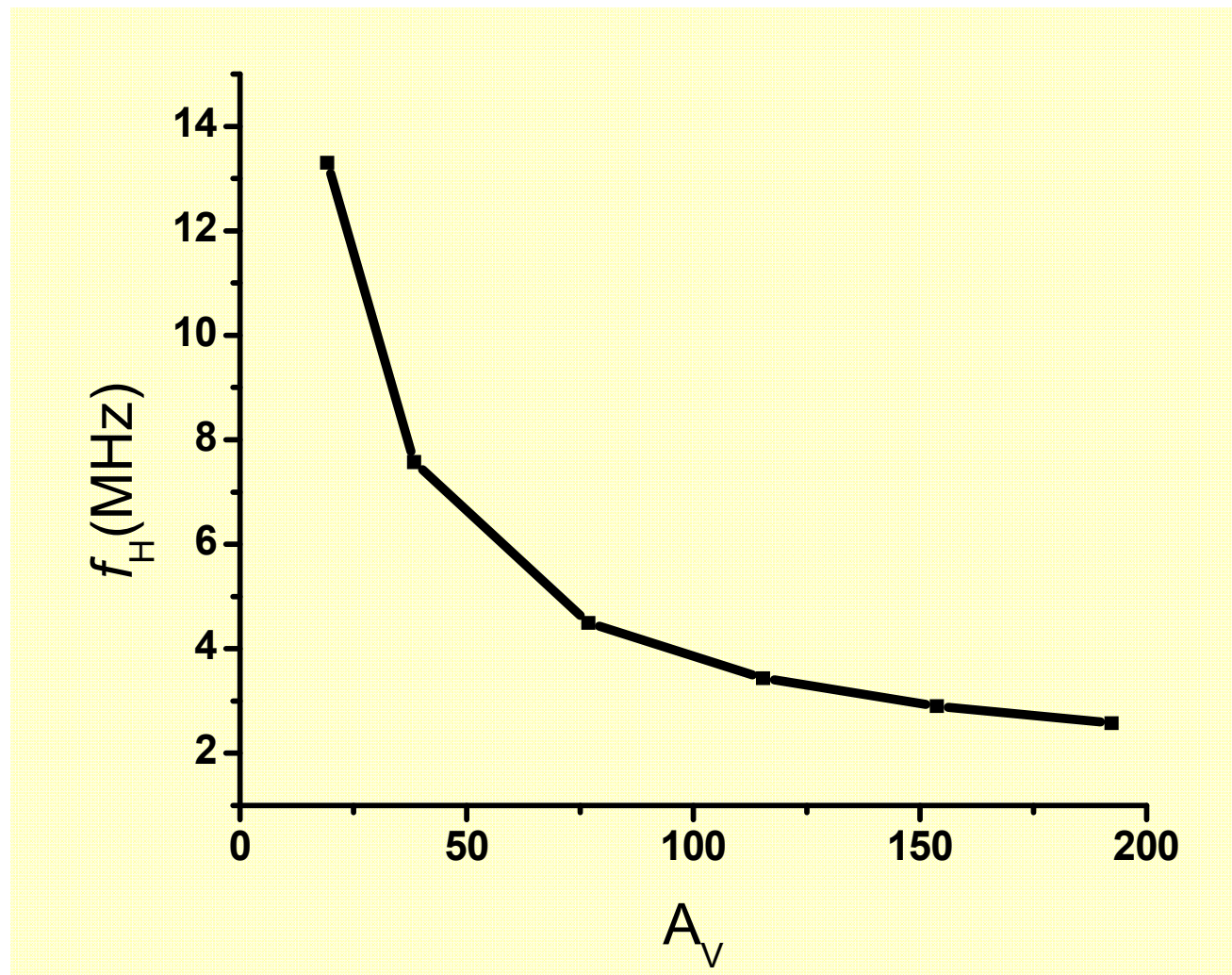Why do we need another amplifier when we have a CE amplifier?




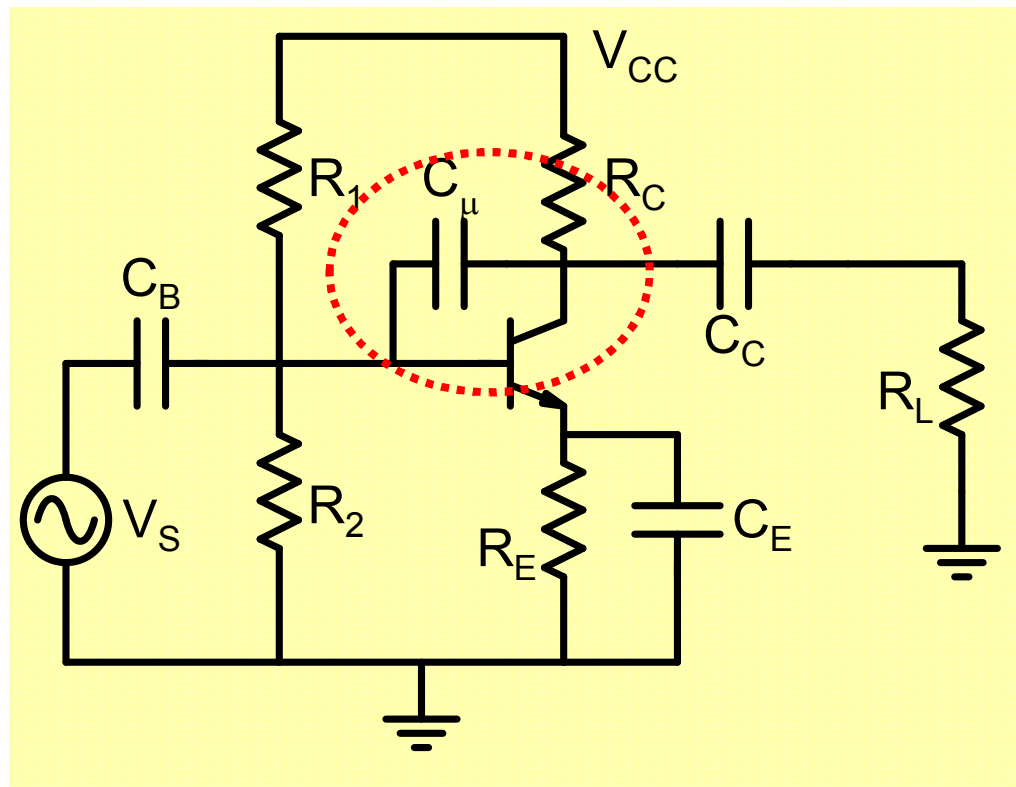Problem: Miller's capacitance reduces bandwidth at high gain

$$\omega_H \cong \frac{1}{(R'_S \parallel r_\pi) \{C_\pi + C_\mu(1 + g_m R'_C)\} + R'_C C_\mu}$$




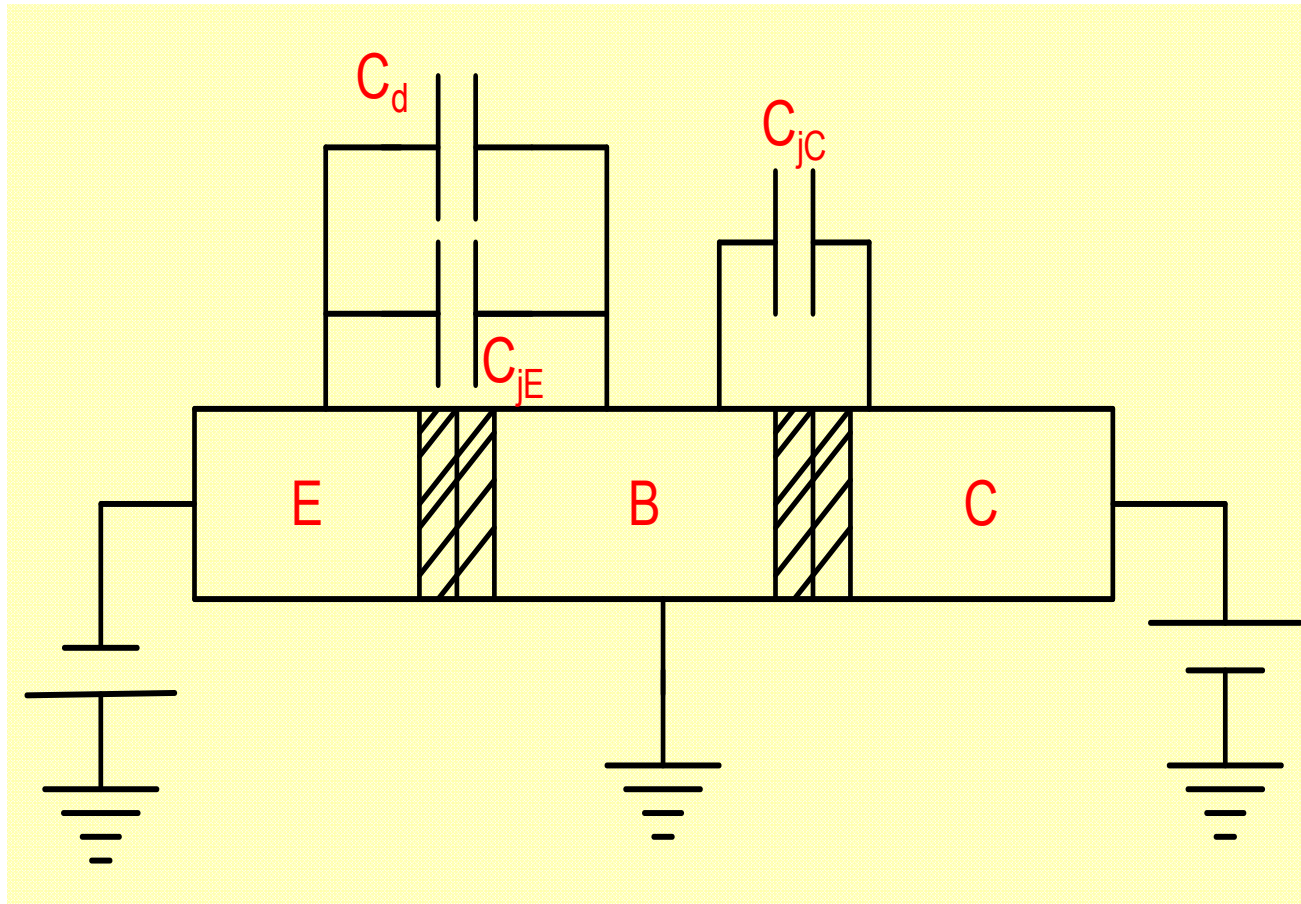Look for an amplifier circuit in which there is no capacitance between input and output ports




Note that there is no capacitance between emitter and collector

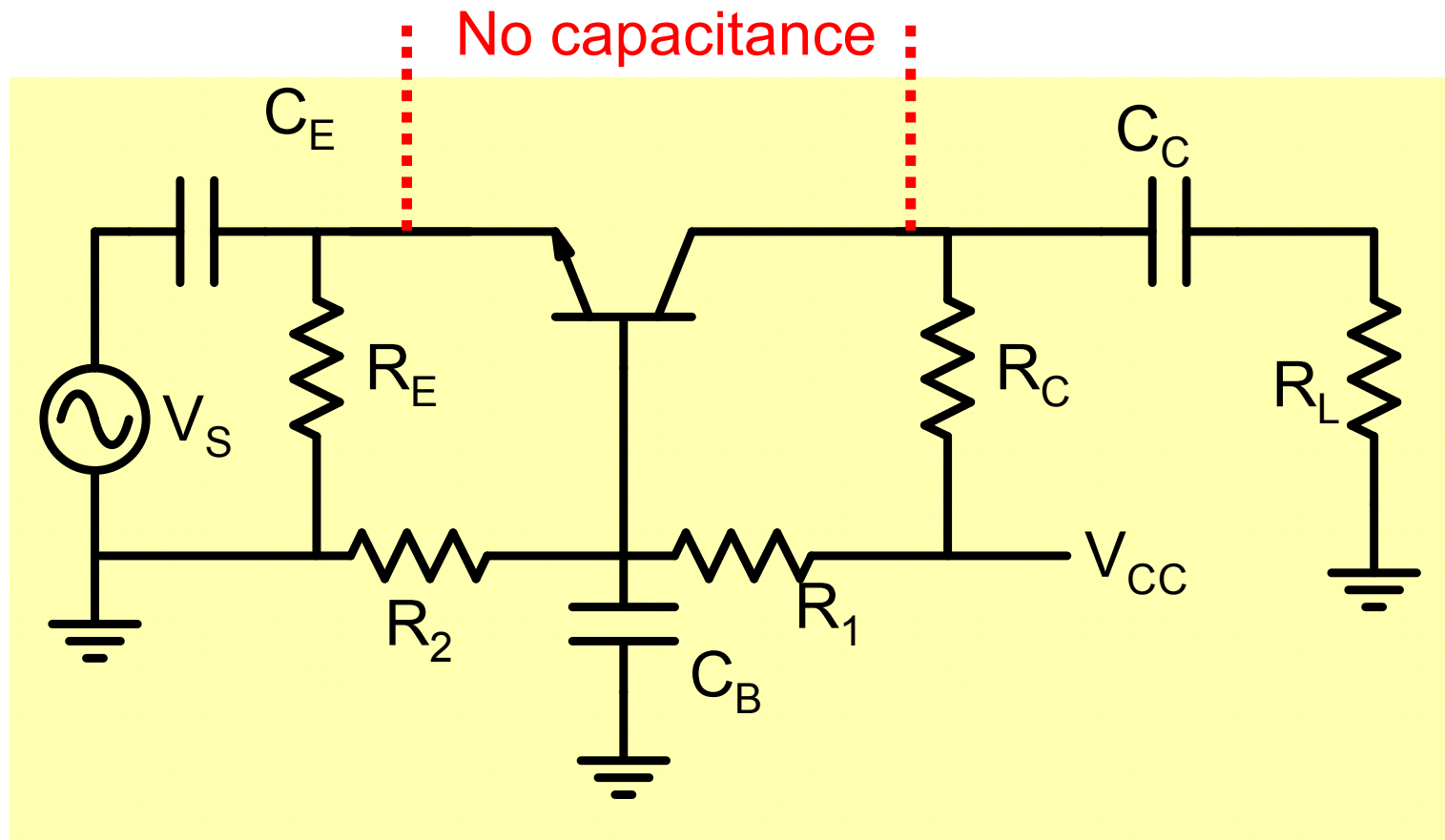Natural solution is a Common Base (CB) Amplifier



dc Analysis


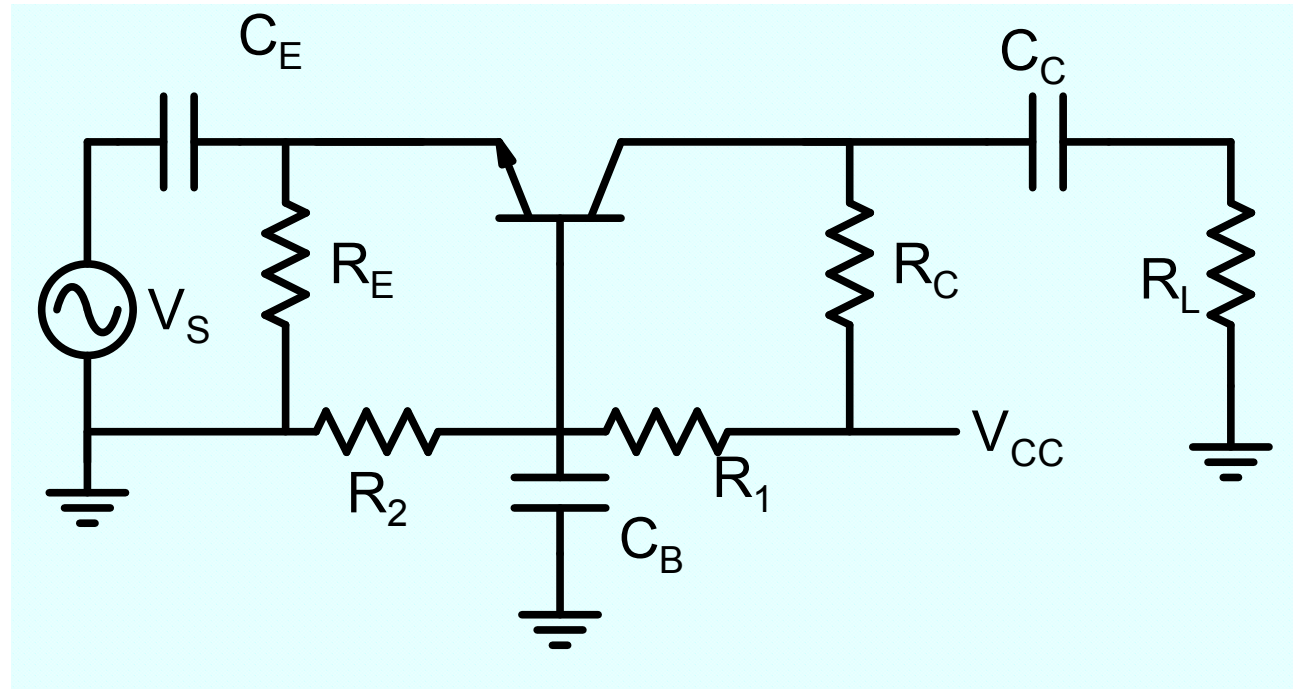


$$I_{CQ} = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE(on)}}{\frac{R_B}{\beta} + R_E}$$

$$V_{CC} = V_{CEQ} + I_{CQ}(R_C + R_E)$$


$$S = \frac{\Delta I_{CQ} / I_{CQ}}{\Delta \beta / \beta} = \frac{1}{1 + \frac{\beta R_E}{R_B}}$$

Mid-frequency small signal analysis

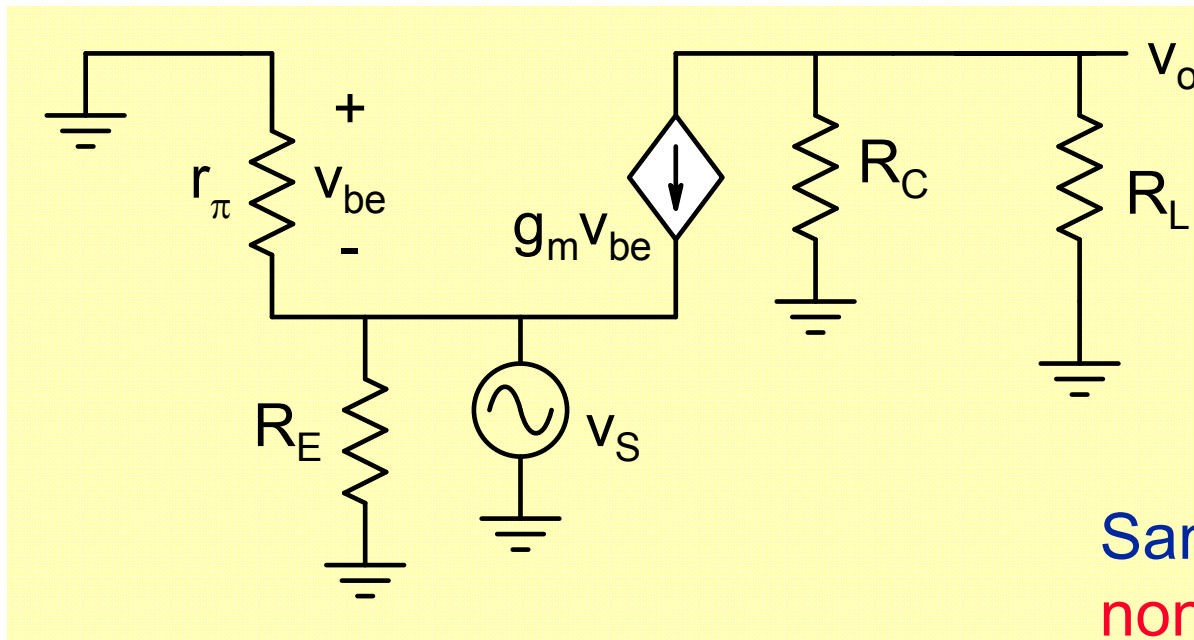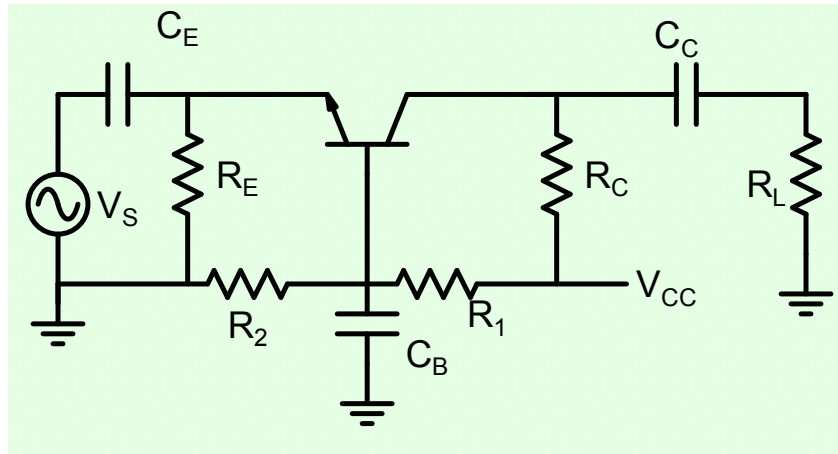

$$A_V = + \frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$


Same as CE amplifier but
non-inverting

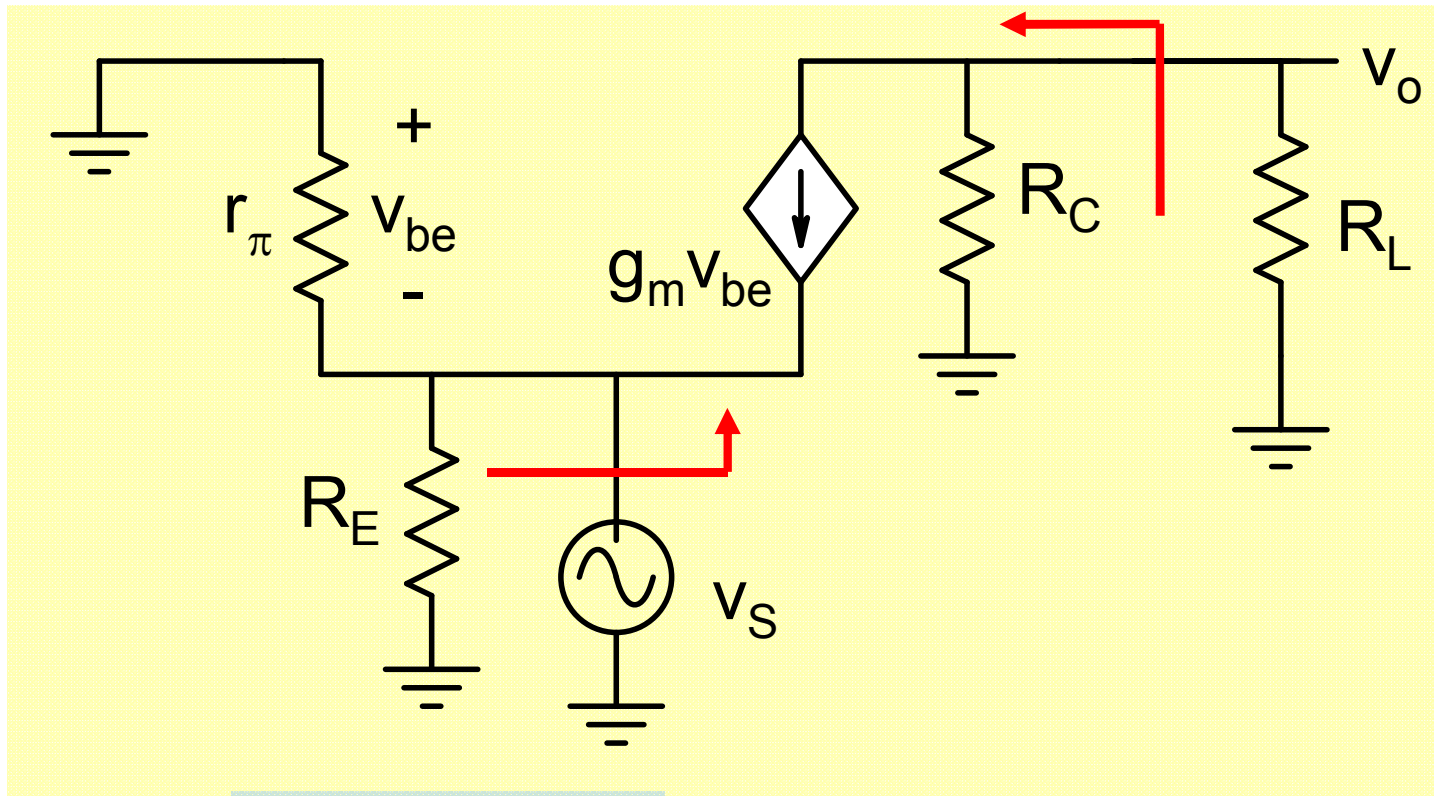

$$R_{in} \cong \frac{r_\pi}{\beta} \parallel R_E$$


$$R_o = R_C$$

Voltage swing is same as CE amplifier

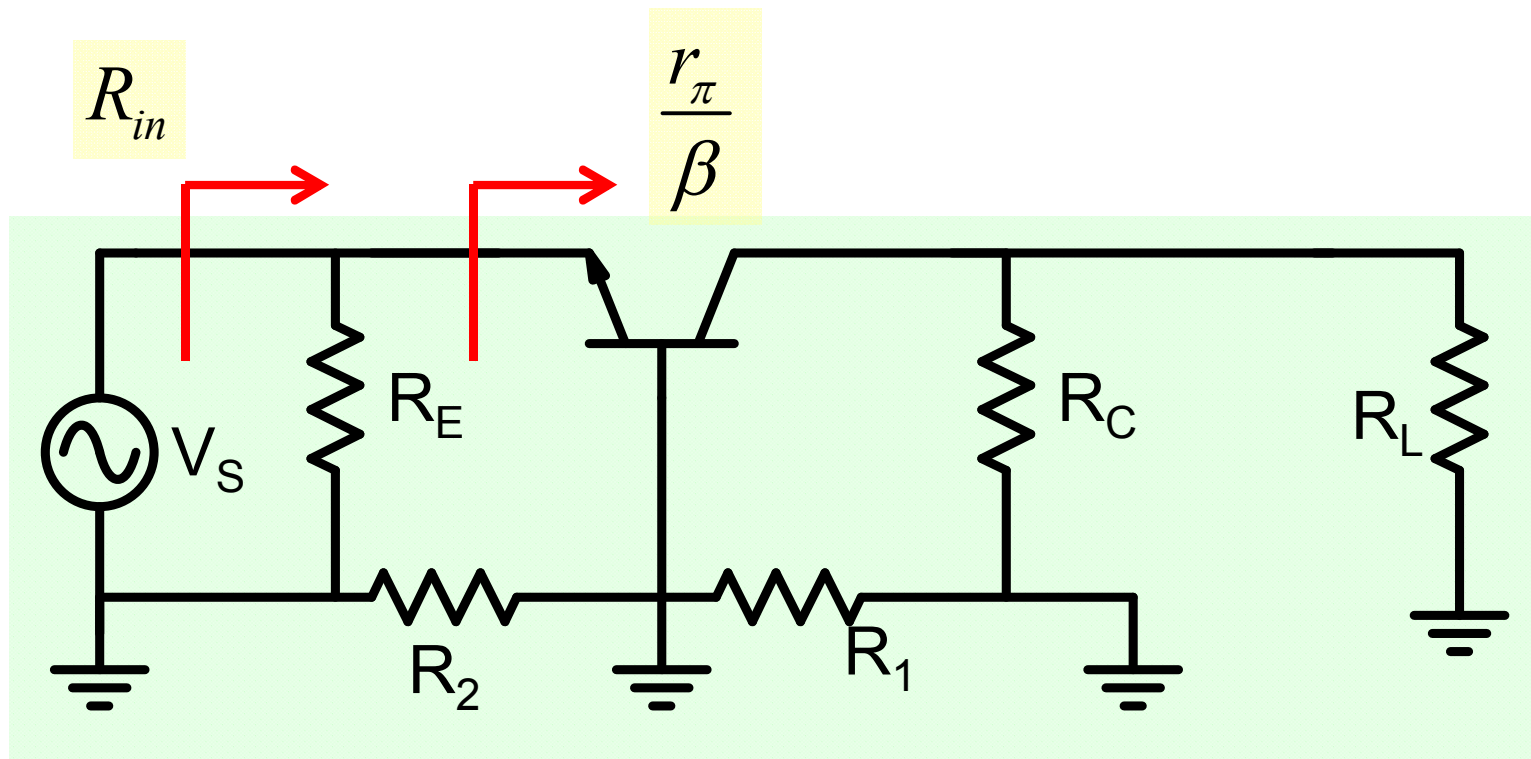

$$R_{in} \cong \frac{r_\pi}{\beta} \parallel R_E$$

Short Circuit Current Gain

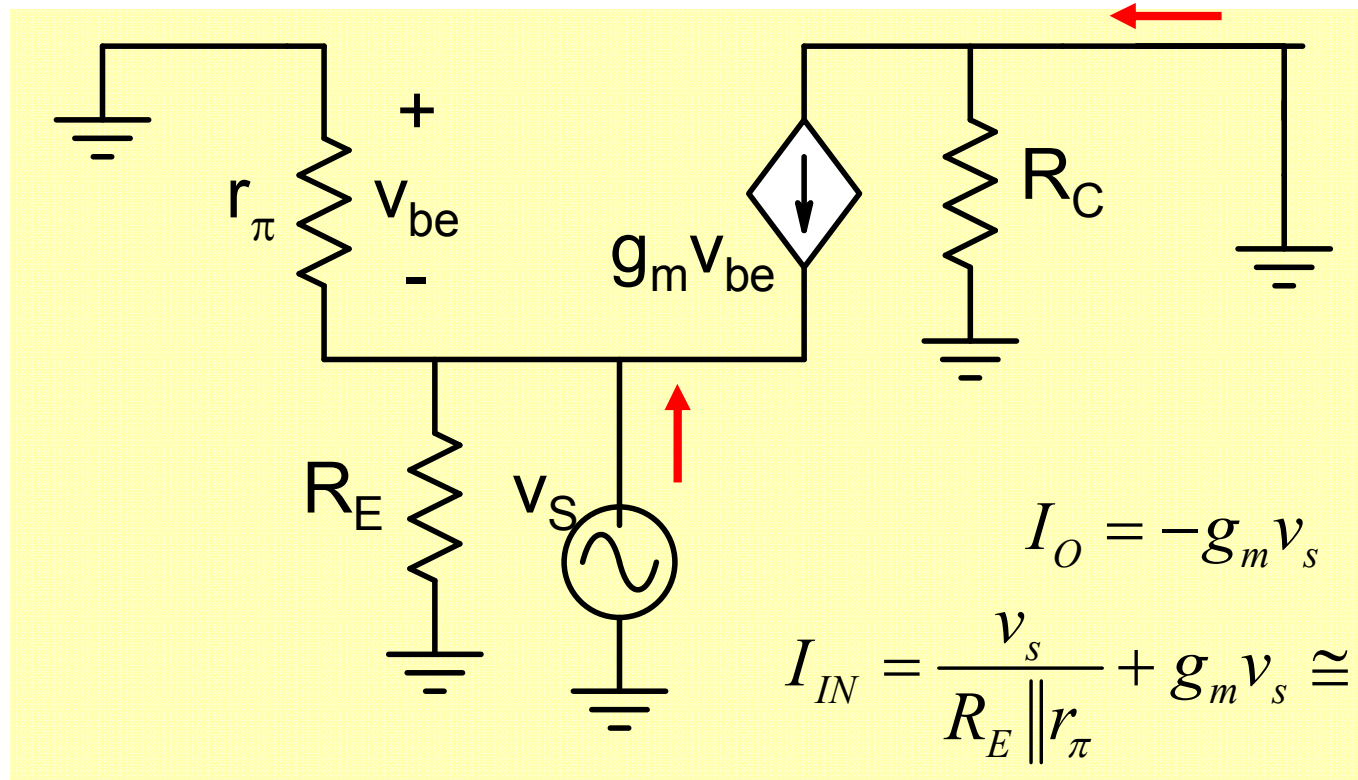

$$A_{IS} = \frac{I_O}{I_{IN}} \cong -\frac{\beta}{\beta + 1}$$

$$A_V = \frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$R_{in} \cong \frac{r_\pi}{\beta} \parallel R_E$$

$$R_o = R_C$$

$$A_V < \frac{I_{CQ}}{V_T} \times R_C$$

$$R_{in} < \frac{r_\pi}{\beta} = \frac{V_T}{I_{CQ}}$$

$$\frac{A_V \times R_{in}}{R_O} \leq 1$$

Tradeoff between voltage gain, input and output resistances

$$\frac{A_V \times R_{in}}{R_O} \leq 1$$

100

.01K

1K

Parameter	Voltage Gain	Input Resistance	Output Resistance
Value	High	Low	Medium

Amplifier	Voltage Gain	Input Resistance	Output Resistance
CE	High	Medium	Medium
CB	High	Low	Medium

$$\frac{A_V \times R_{in}}{R_O} \leq \beta$$

$$\frac{A_V \times R_{in}}{R_O} \leq 1$$

A better Comparison with CE amplifier

$$\frac{A_V(CB) \times R_{in}(CB)}{R_O(CB)} \sim 1$$

$$\frac{A_V(CE) \times R_{in}(CE)}{R_O(CE)} \sim \beta$$


$$\frac{A_V(CE)}{A_V(CB)} \times \frac{R_{in}(CE)}{R_{in}(CB)} \times \frac{R_O(CB)}{R_O(CE)} \sim \beta$$

$$1 \times 10^2$$

$$1 \times 10^2$$



$$1 \times 10^2$$

Frequency Response



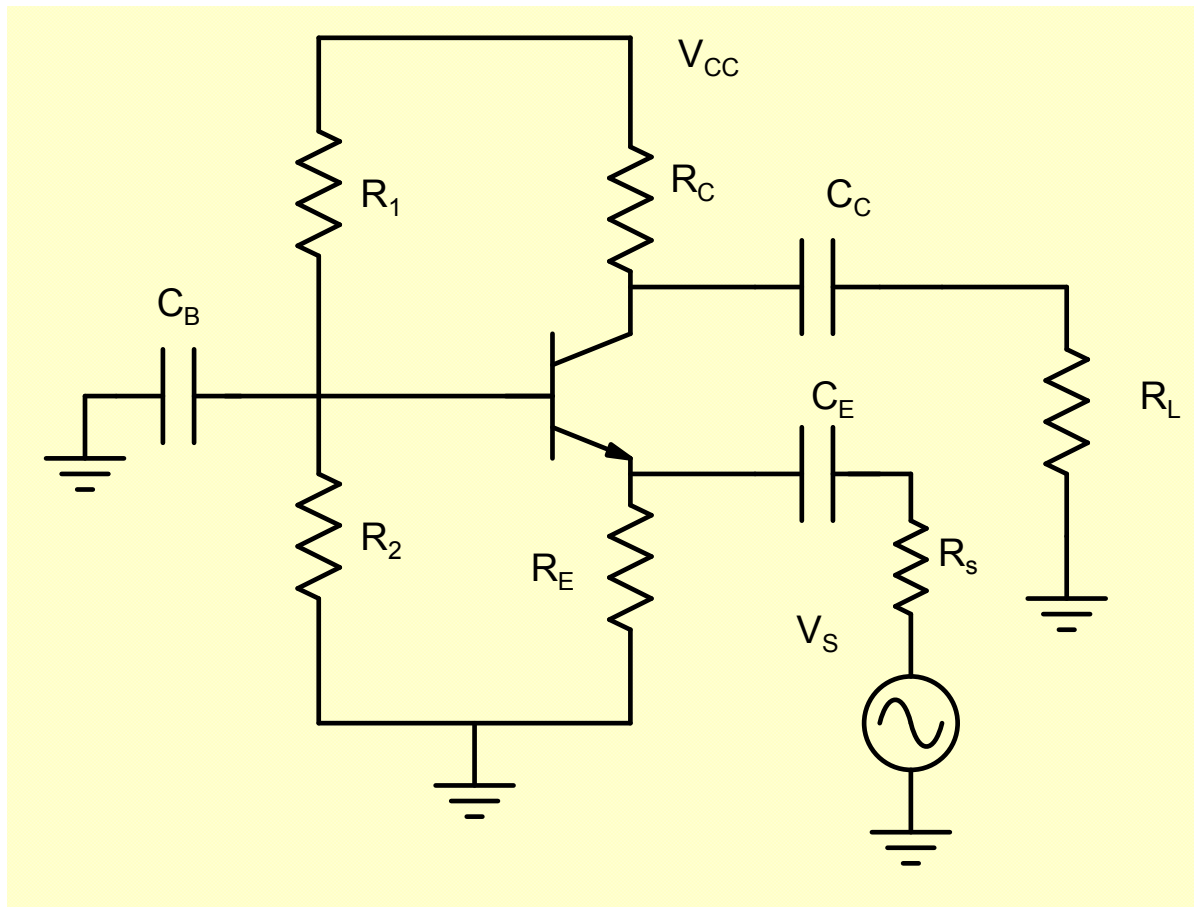


Lower Cutoff frequency is similar to CE amplifier

Upper Cutoff Frequency

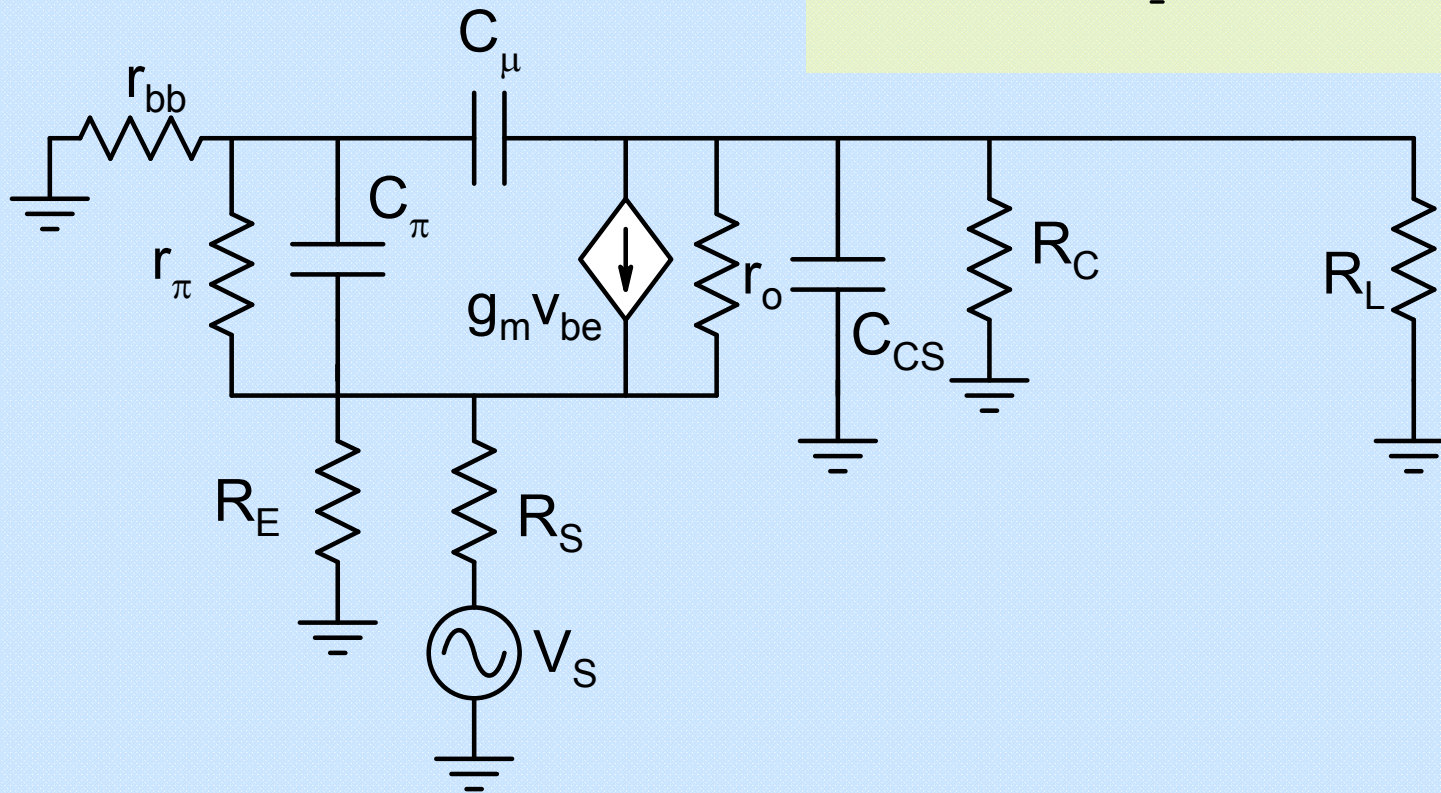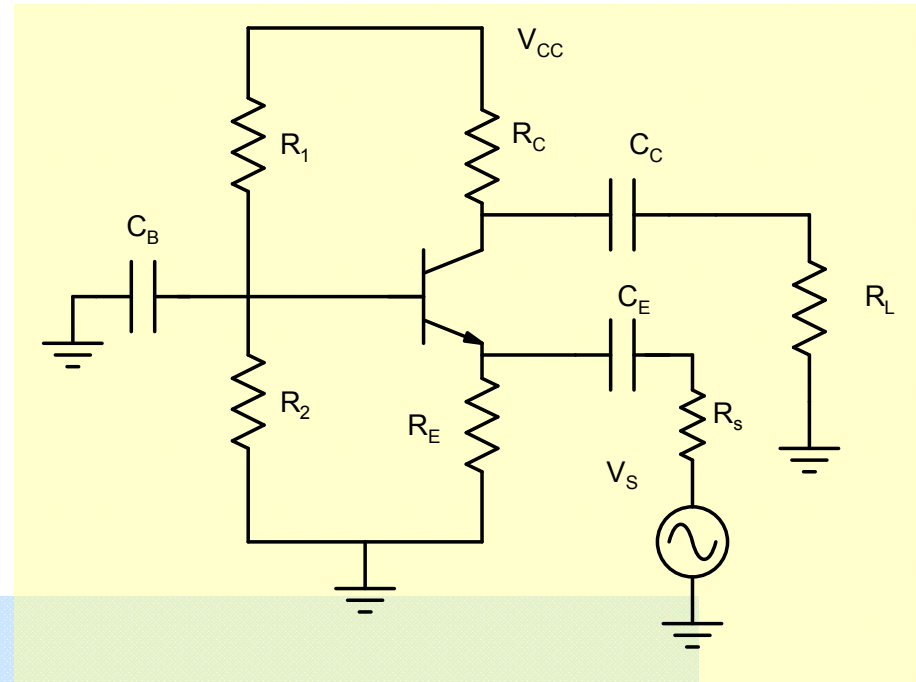


Negligible R_s

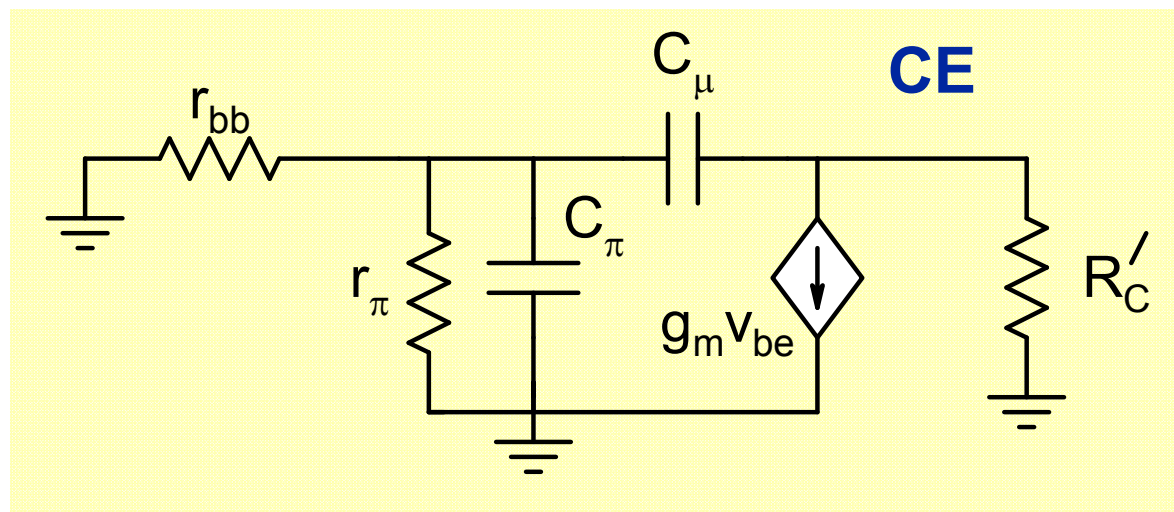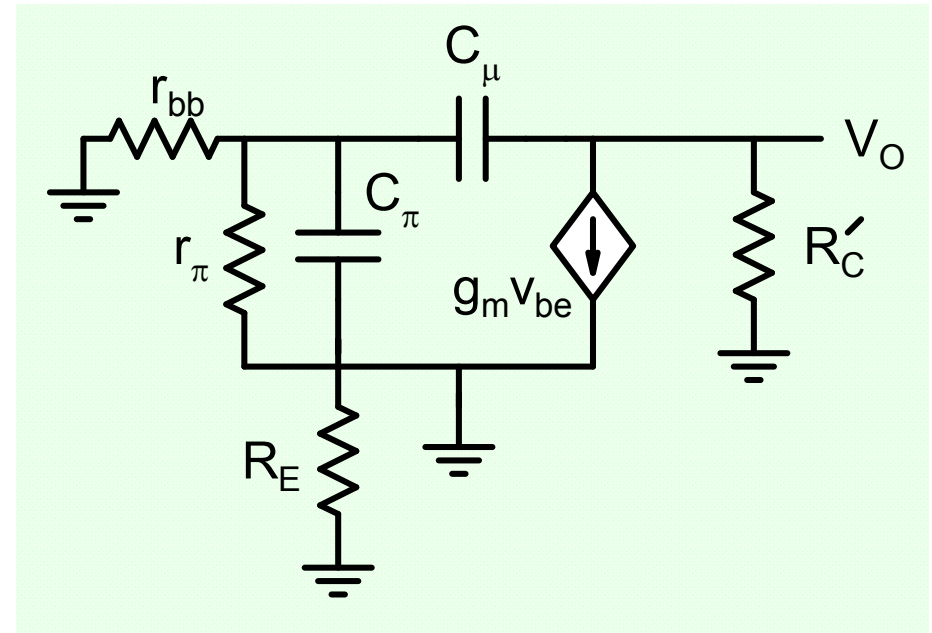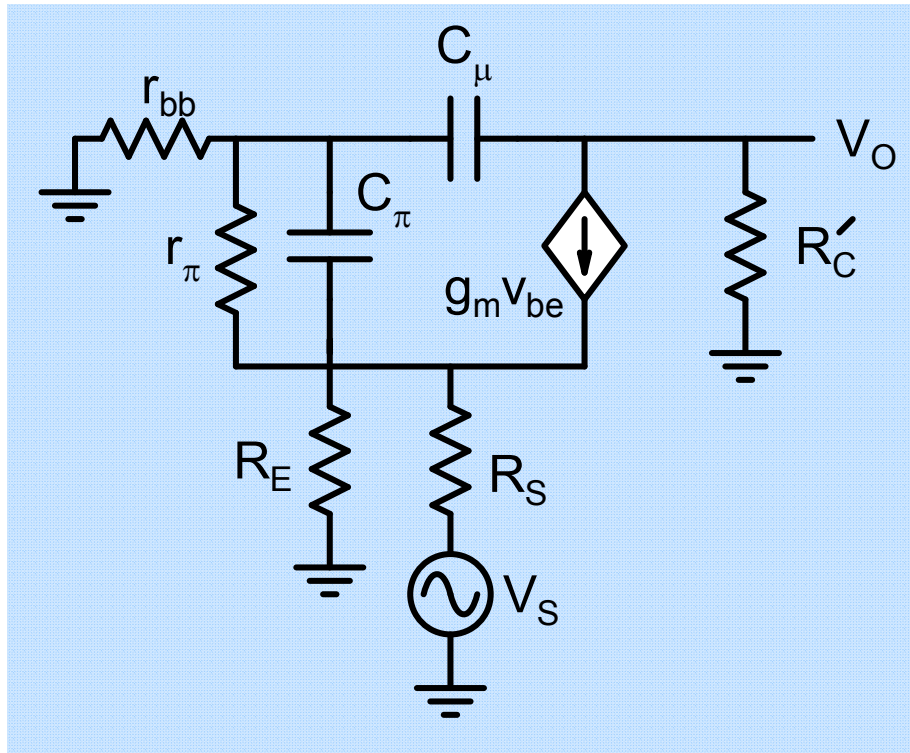

CB has same upper cutoff frequency as CE !

Example

Simulation Results

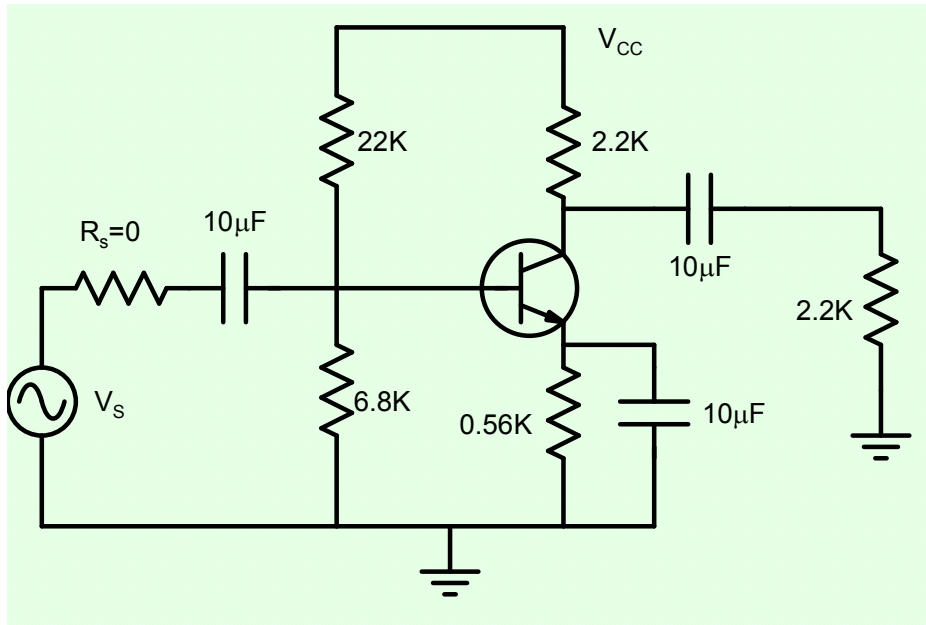


$$A_v = -110.7$$

$$R_{in} = 0.82\text{k}\Omega; R_o = 2.2\text{k}\Omega$$

$$\frac{A_v \times R_{in}}{R_o} = 41 < \beta$$

$$f_H = 5.8\text{MHz}$$

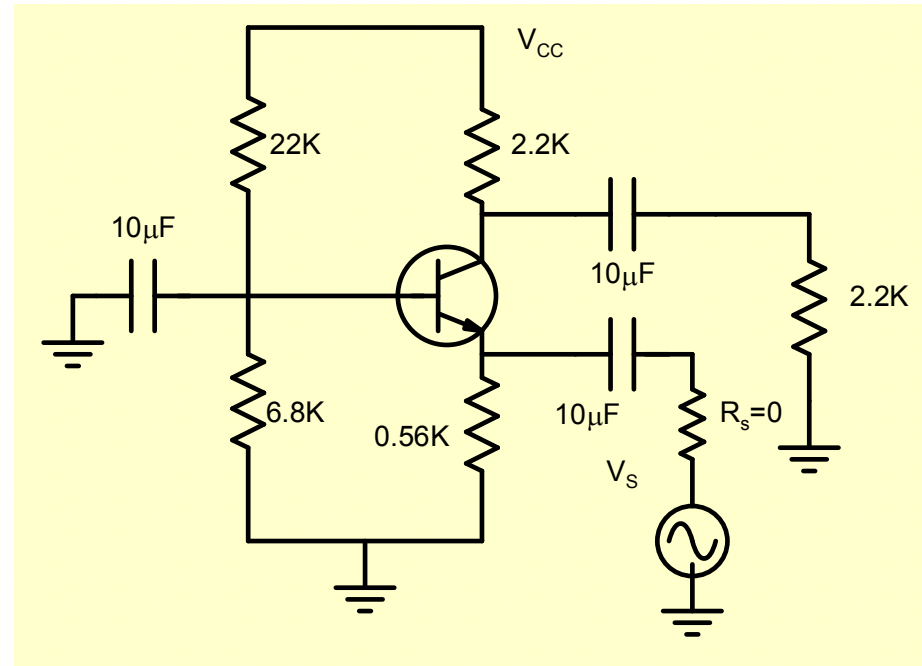

$$A_v = 110.7$$


$$R_{in} = 9.66\Omega; R_o = 2.2\text{k}\Omega$$

$$\frac{A_v \times R_{in}}{R_o} = 0.48$$


$$f_H = 5.8\text{MHz}$$

Simulation results

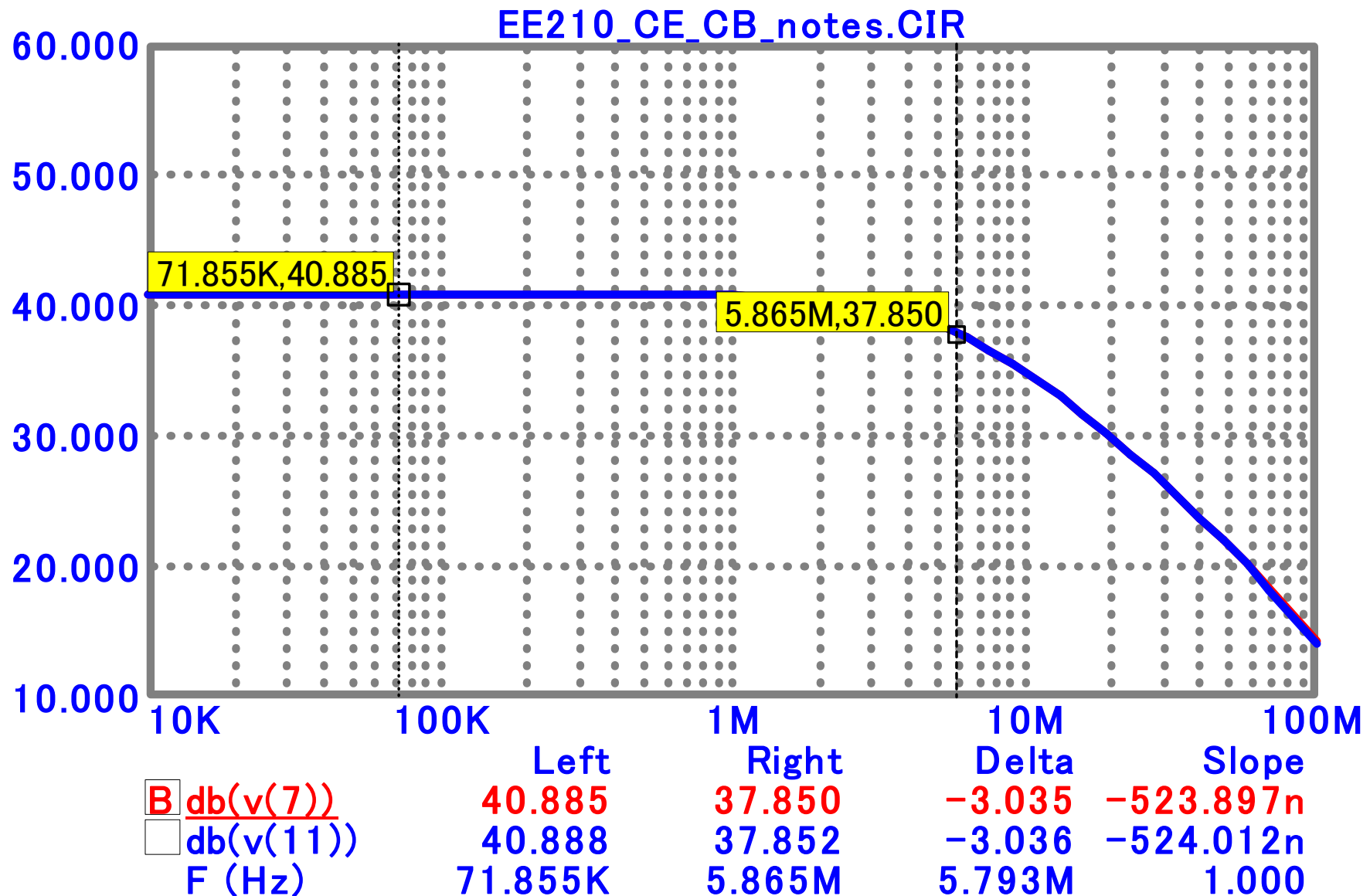
Both amplifiers have same response for RS=0




$$R_S = 2.2k$$

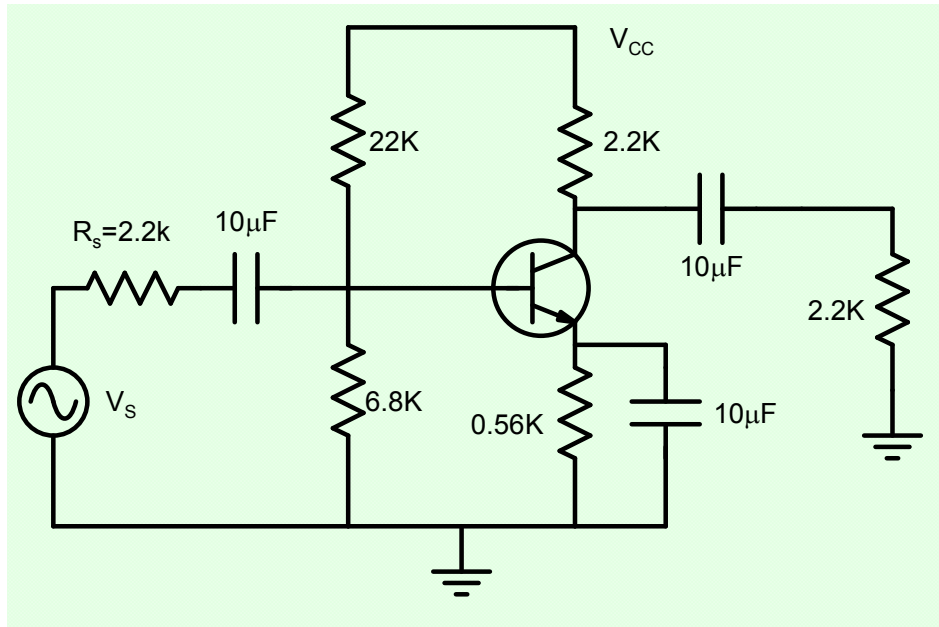


$$CE: A_V = -30; f_H = 1.76MHz$$

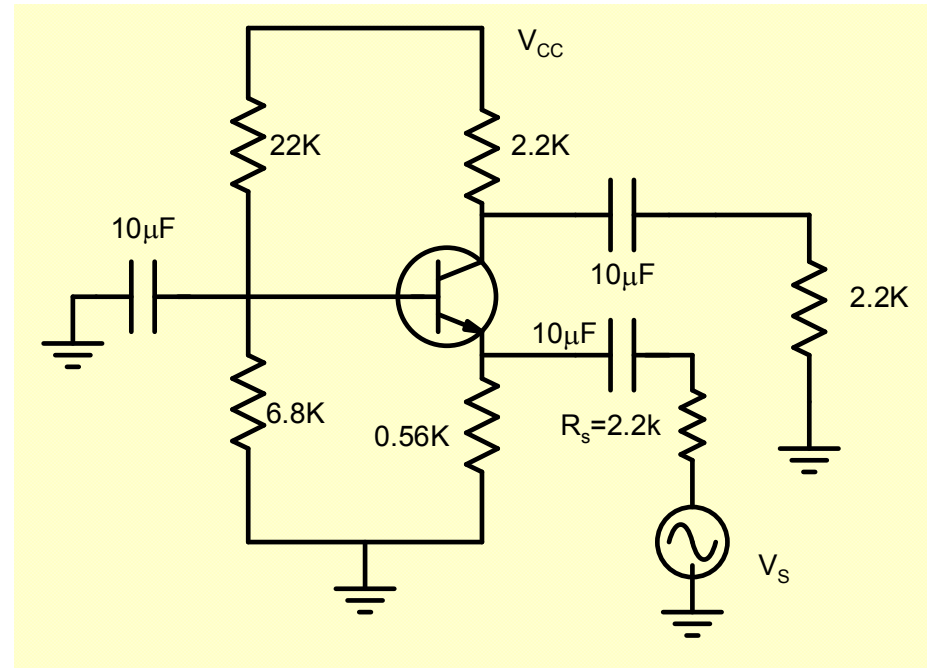

$$CB: A_V = 0.48; f_H = 61MHz$$

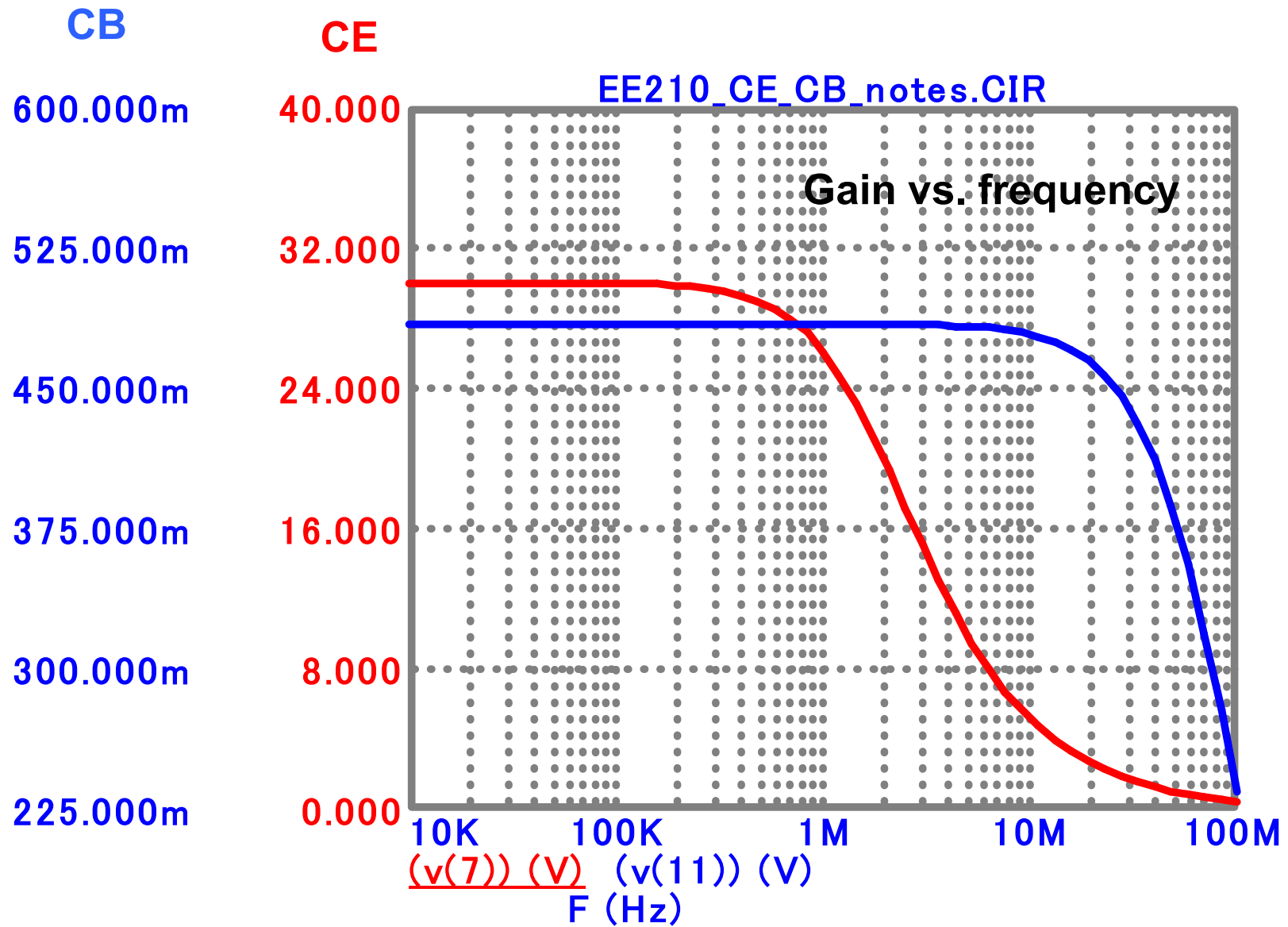

Effect of emitter (source) resistance

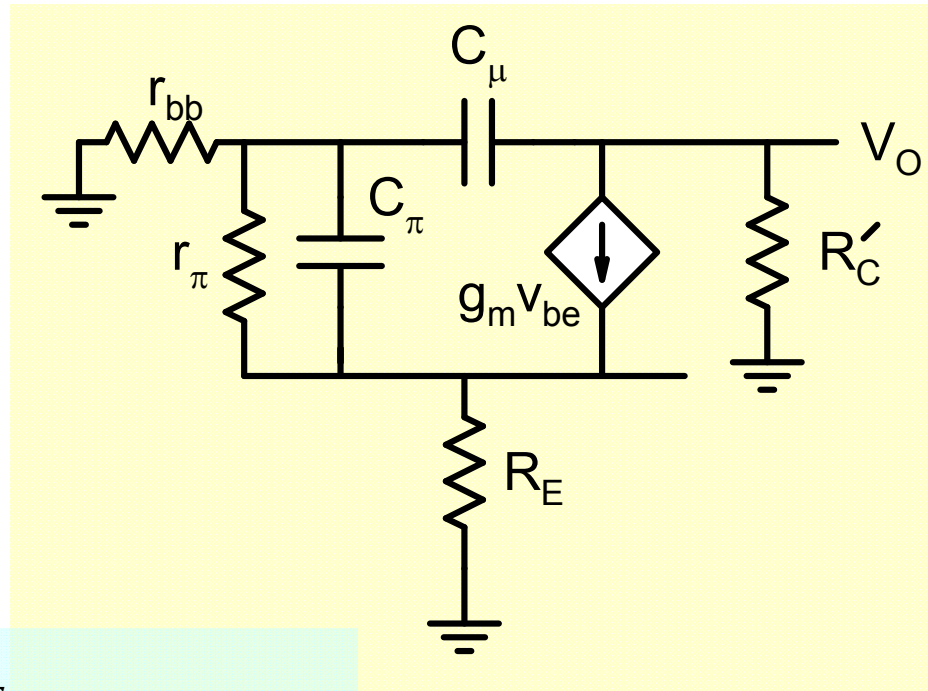


$$R_{\pi} = \frac{1 + \frac{R_E}{r_{bb}}}{1 + \frac{g_m R_E}{1 + \frac{r_{bb}}{r_{\pi}}}} \times (r_{bb} \parallel r_{\pi})$$


$$\cong \frac{1}{g_m} \text{ as } R_E \rightarrow \infty$$

$$R_{\mu} = r_{bb} + R_C + \frac{(\beta R_C - r_{bb}) \times r_{bb}}{r_{\pi} + r_{bb} + (1 + \beta) R_E}$$

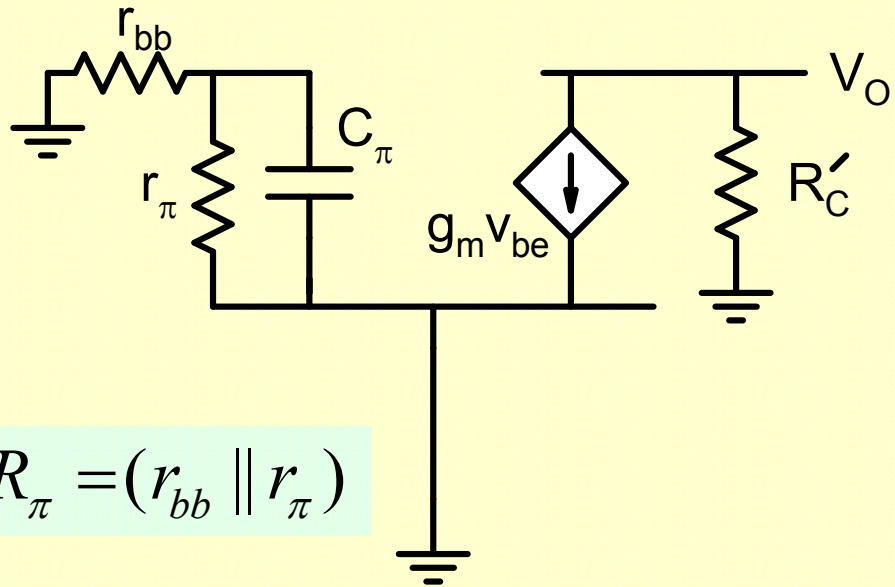
$$\cong r_{bb} + R_C \text{ as } R_E \rightarrow \infty$$




$$R_{\pi} = (r_{bb} \parallel r_{\pi})$$

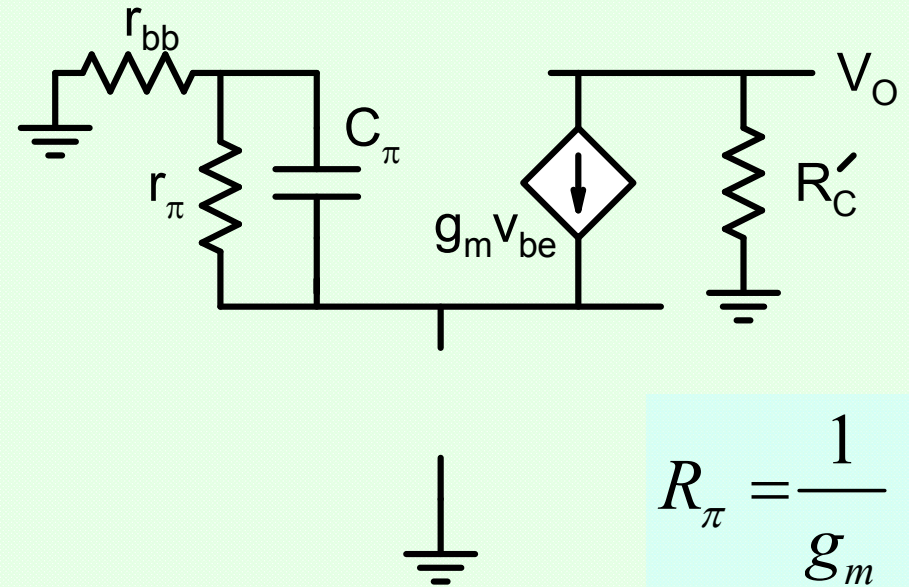

$$R_{\pi} = \frac{1}{g_m}$$

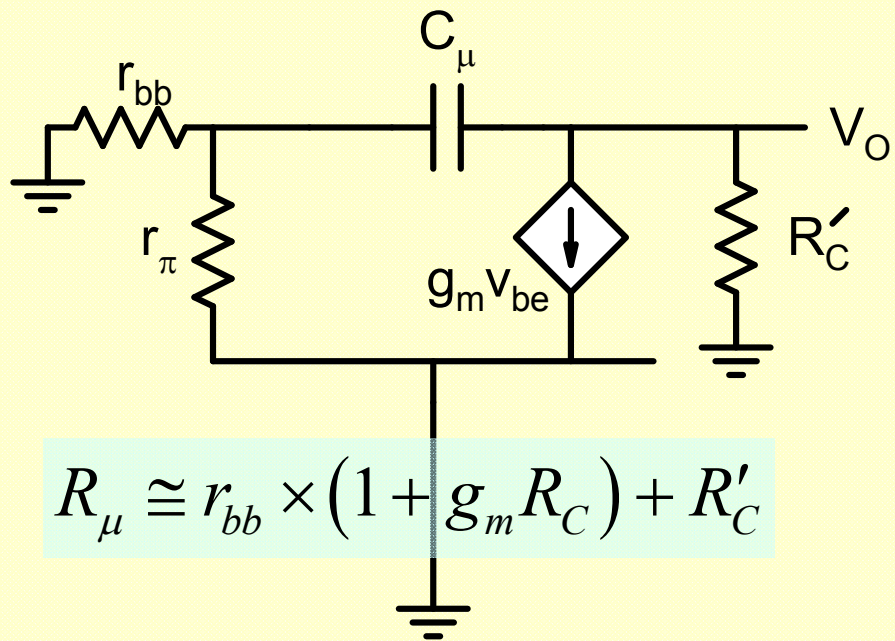

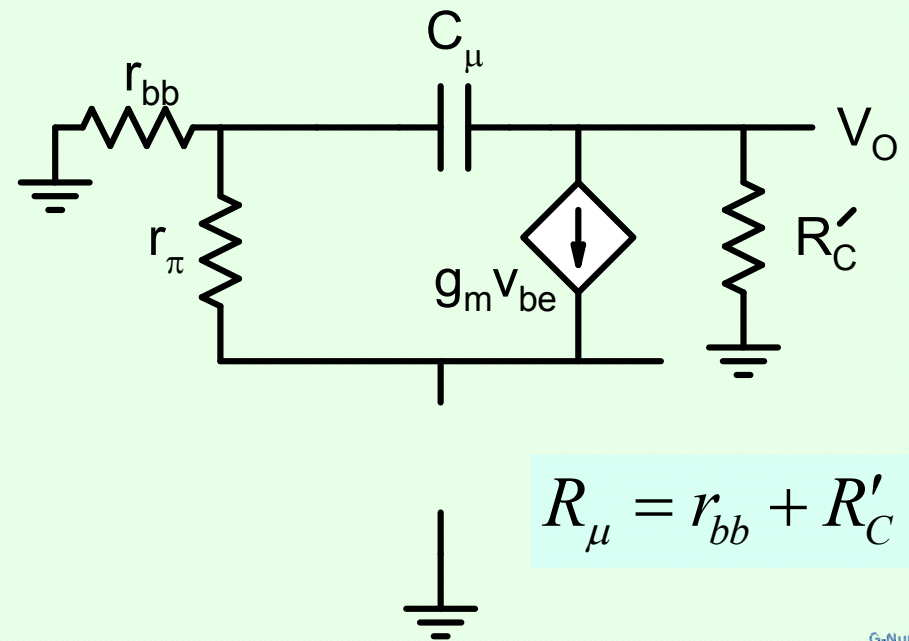
$$R_{\mu} \cong r_{bb} \times (1 + g_m R_C) + R'_C$$





$$R_{\mu} = r_{bb} + R'_C$$

Large source and emitter resistance

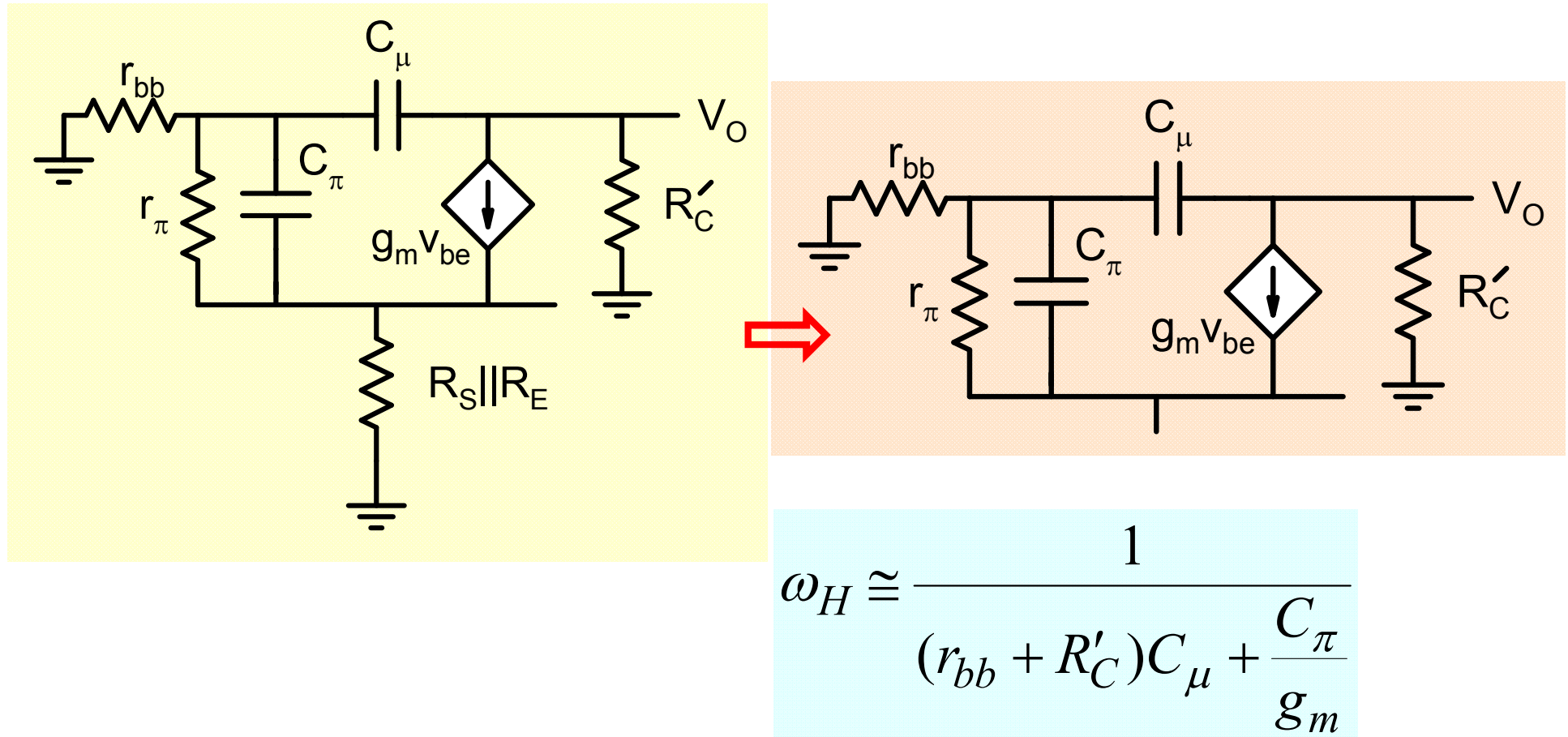


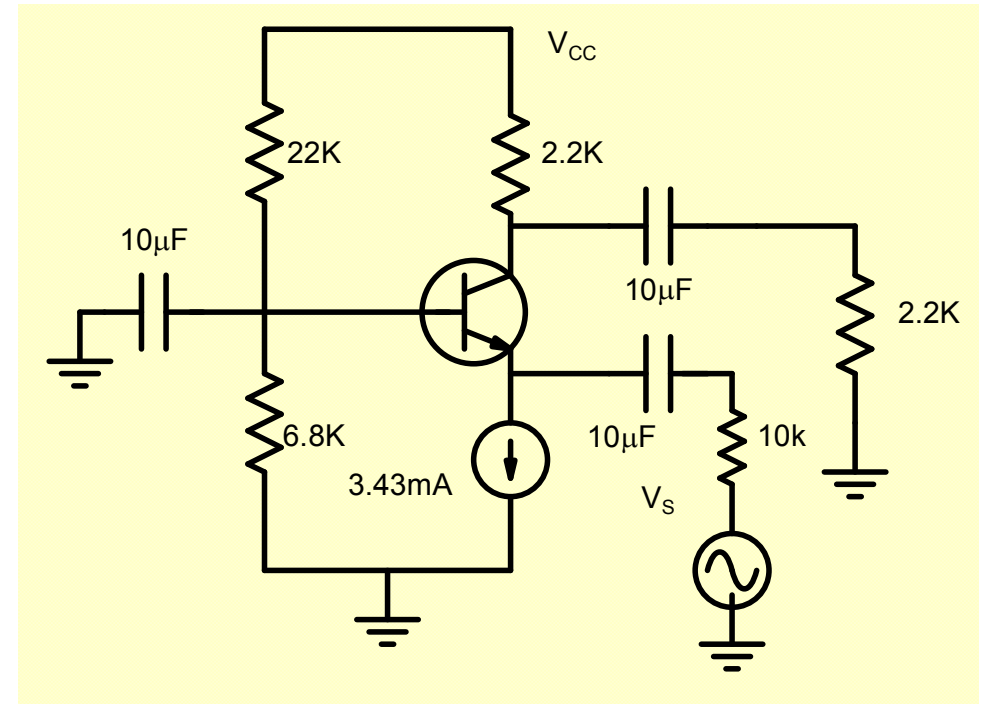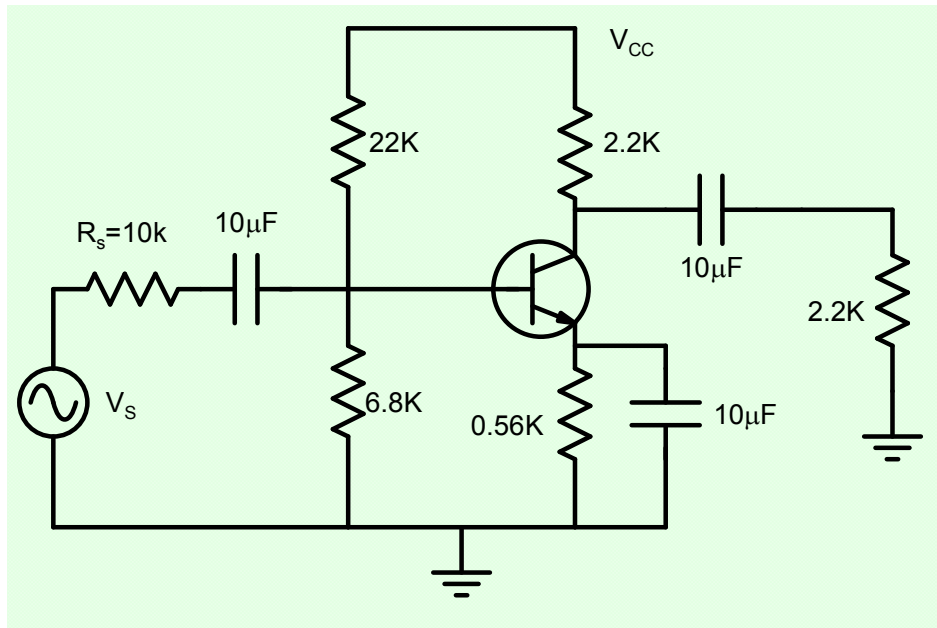
No Miller's effect and effect of C_π is reduced as well



CE: $A_V = -8.3$; $f_H = 1.45\text{MHz}$


CB: $A_V = 0.1$; $f_H = 73.5\text{MHz}$

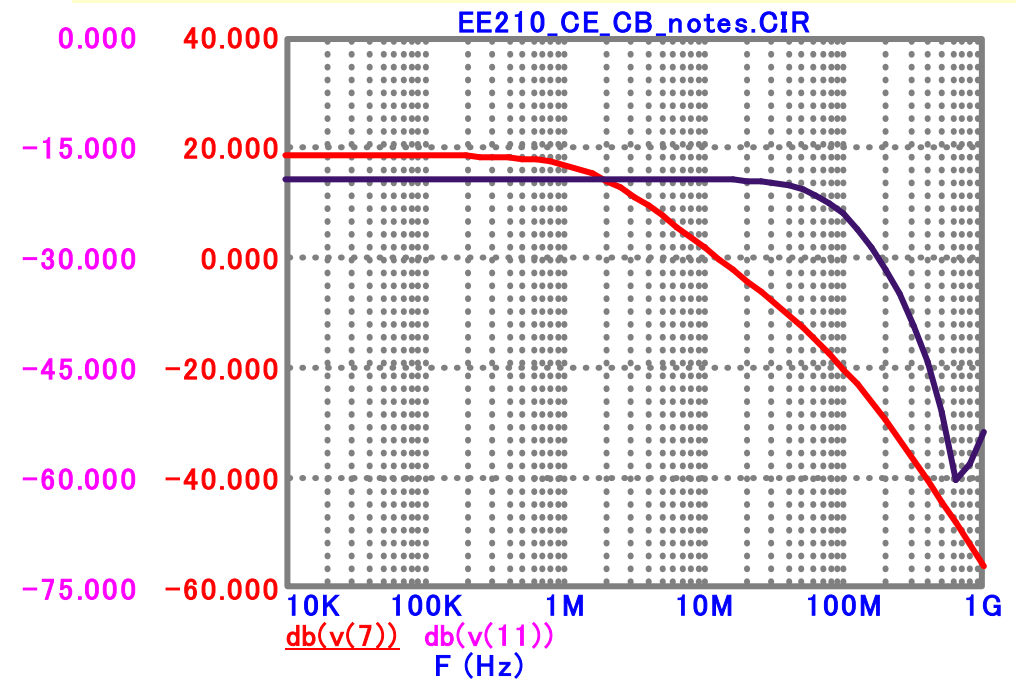

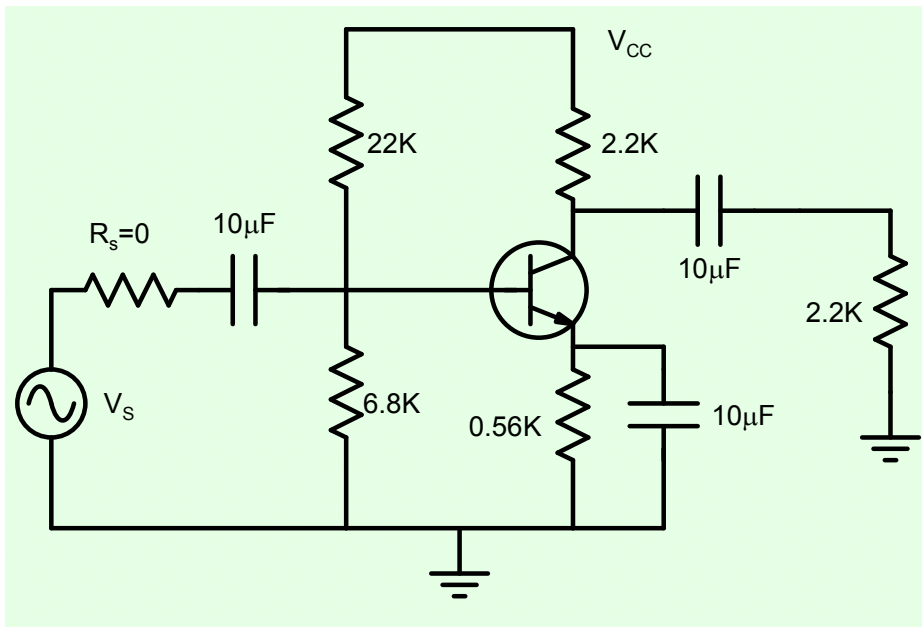


$$A_v = -110.7; R_{in} = 0.82 k\Omega; R_o = 2.2 k\Omega$$

$$f_H = 5.8 MHz$$

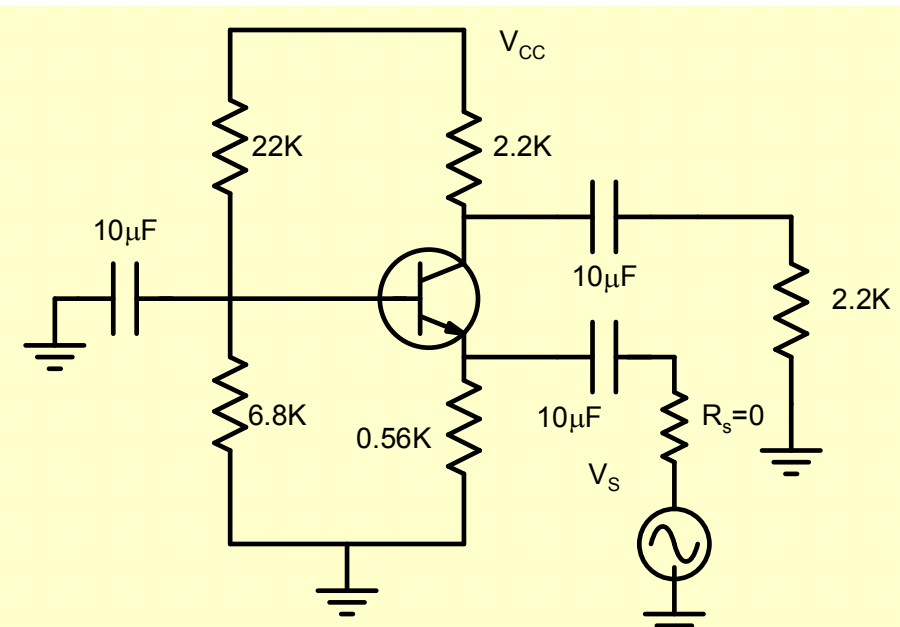


$$A_v = 110.7; R_{in} = 9.66 \Omega; R_o = 2.2 k\Omega$$



$$f_H = 5.8 MHz$$

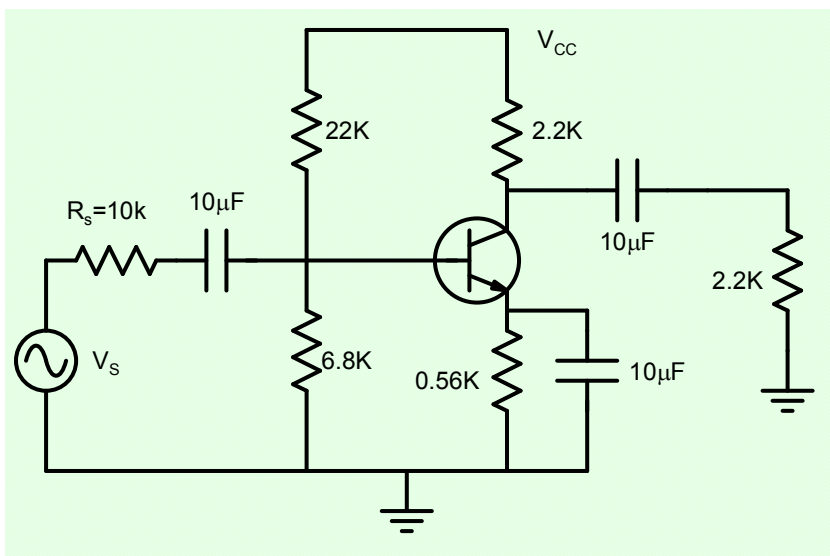



$$CE: A_v = -8.3; f_H = 1.45 MHz$$

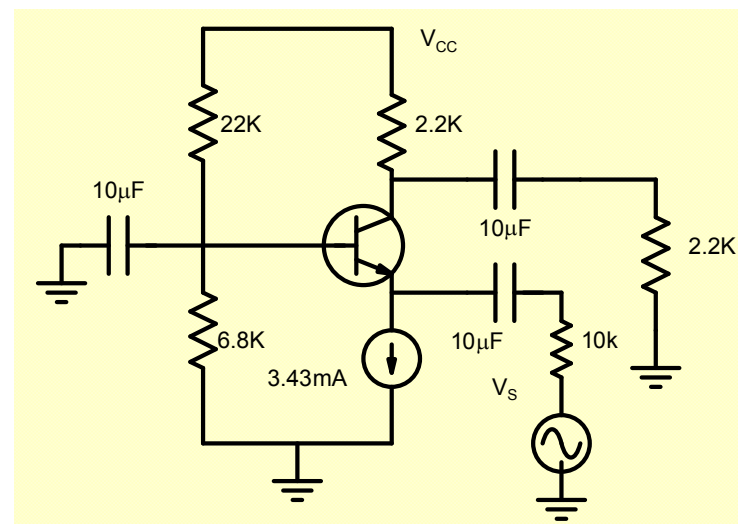

$$CB: A_v = 0.1; f_H = 73.5 MHz$$

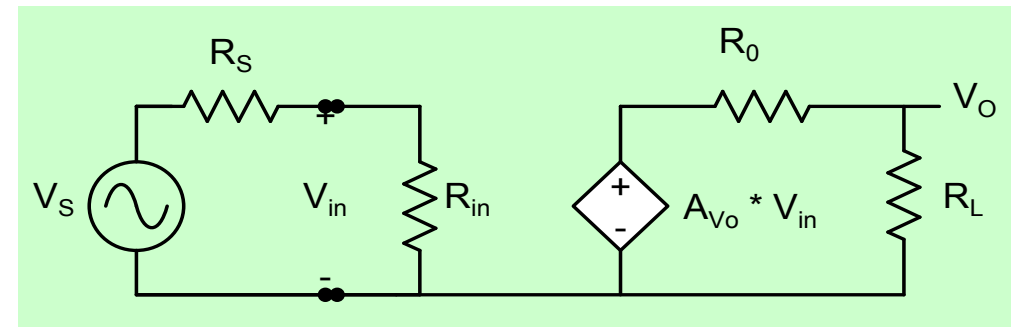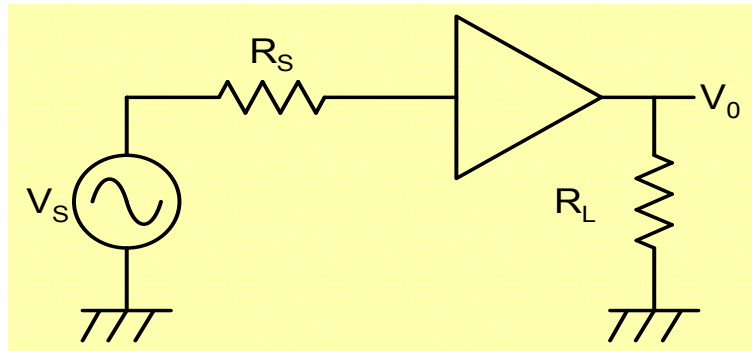

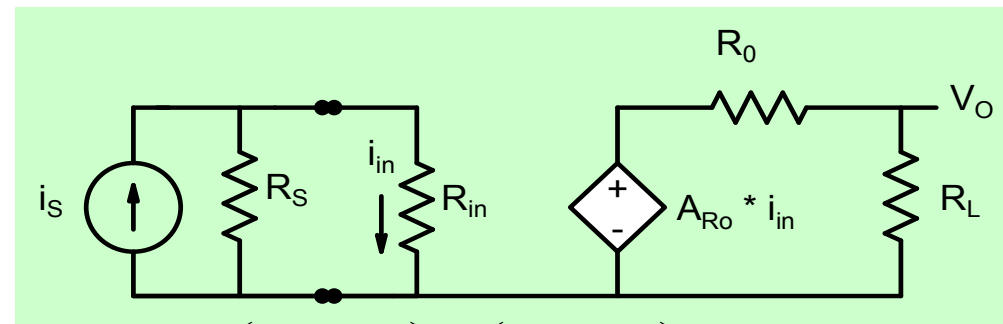
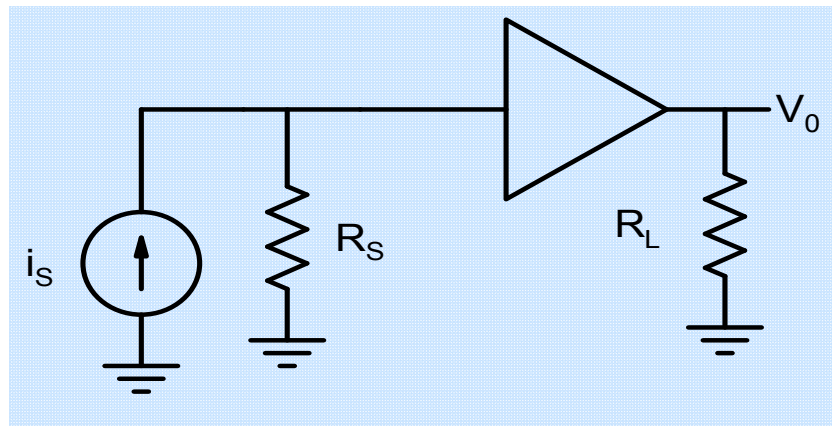
$$\frac{v_o}{v_s} = \left(\frac{1}{1 + \frac{R_S}{R_{in}}} \right) \times \left(\frac{1}{1 + \frac{R_O}{R_L}} \right) \times A_{VO}$$





$$\frac{v_o}{i_s} = \left(\frac{1}{1 + \frac{R_{in}}{R_S}} \right) \times \left(\frac{1}{1 + \frac{R_O}{R_L}} \right) \times A_{RO}$$

Low input resistance is desirable for current input: **trans-resistance** amplifier

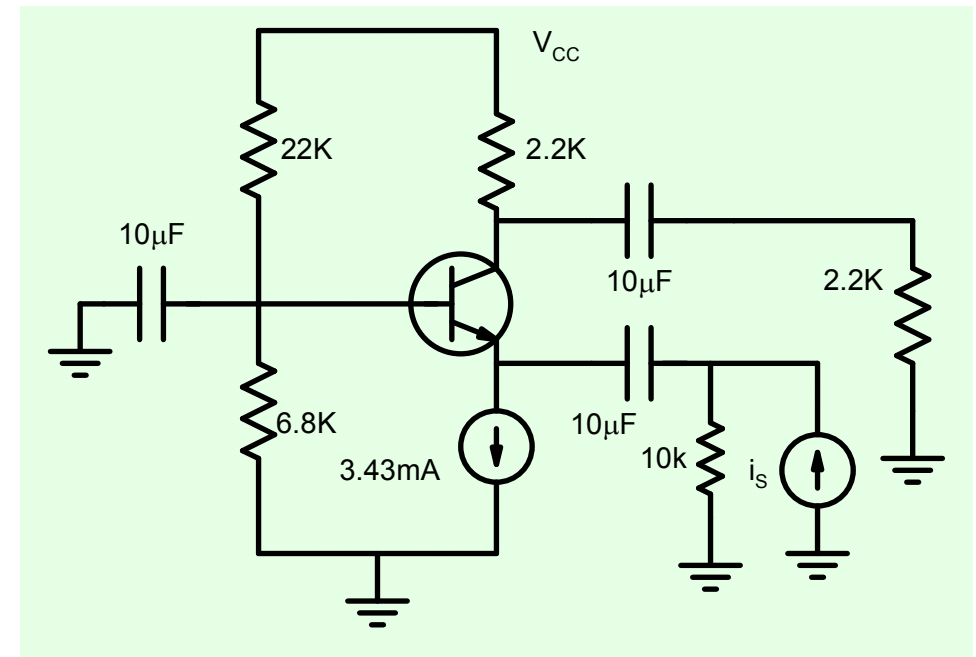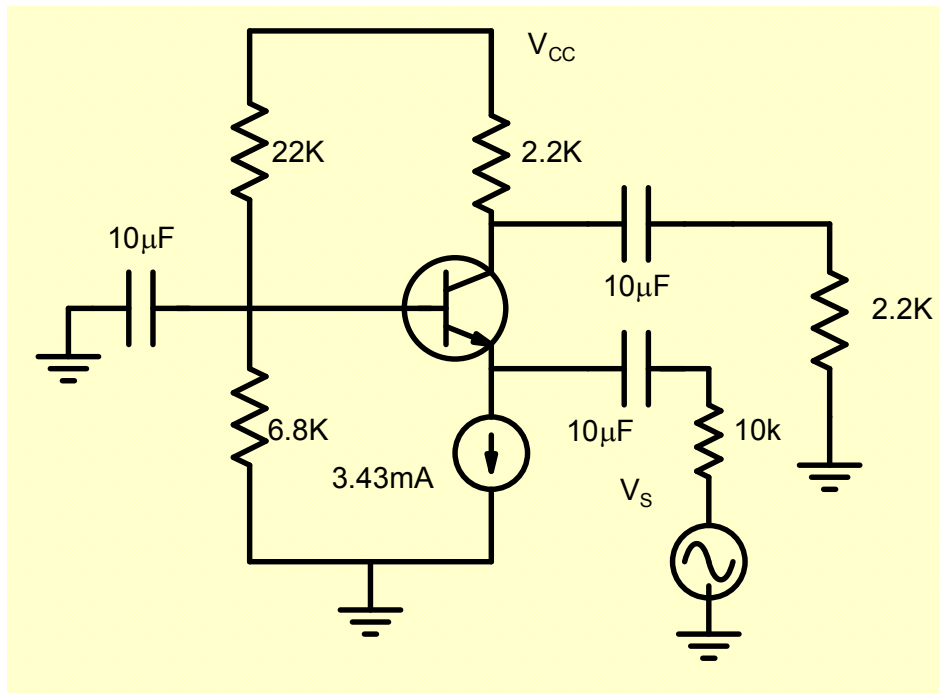Low input resistance in CB amplifier makes it well suited for current input



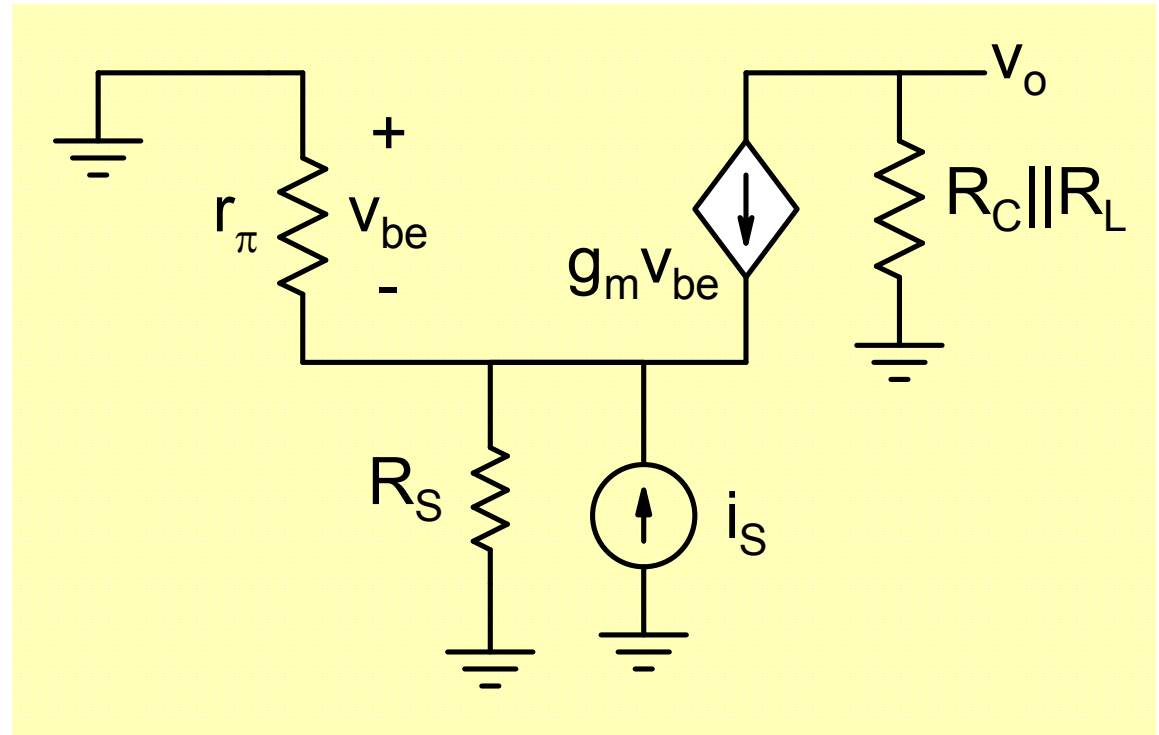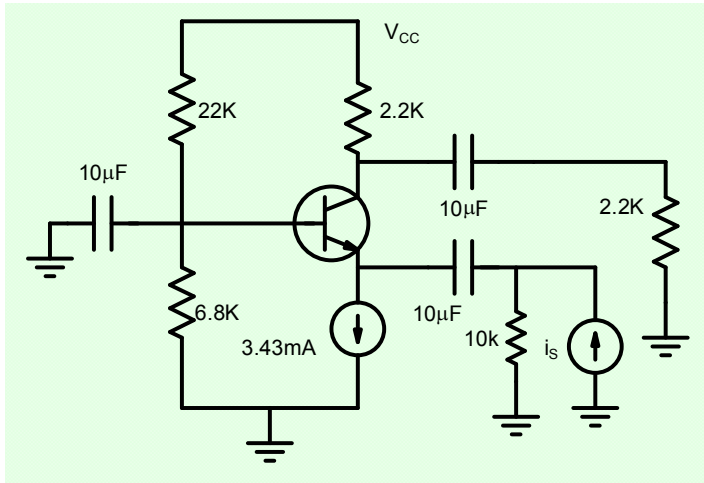

$$v_o \cong i_s \times R_C \parallel R_L$$

How do we utilize an amplifier with current input and high bandwidth?