
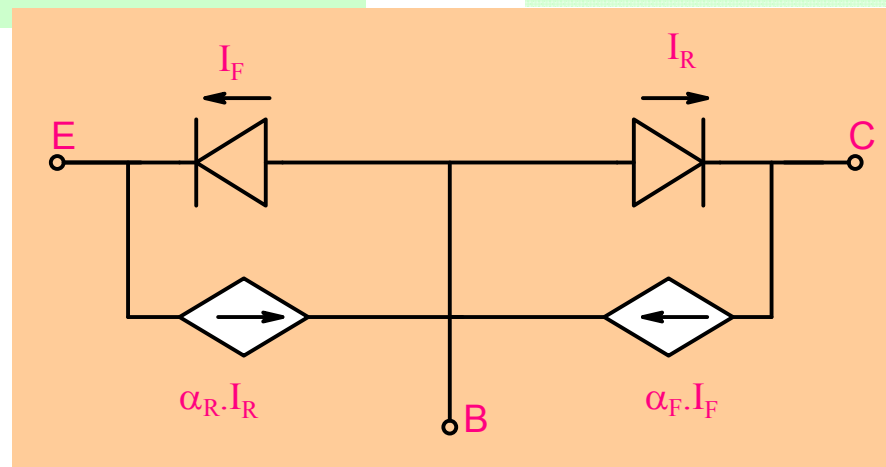
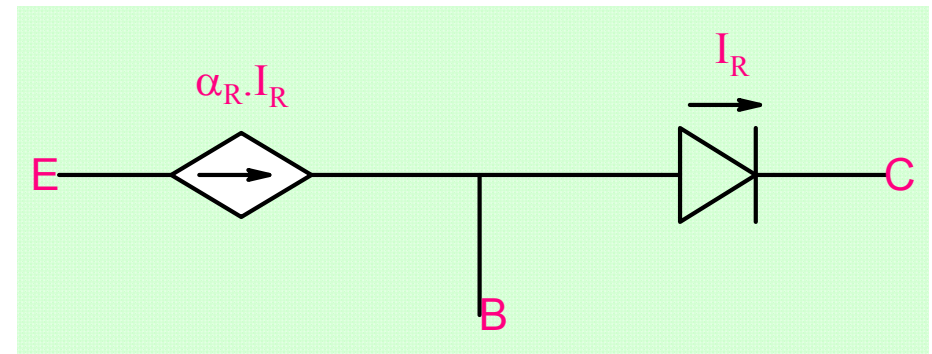
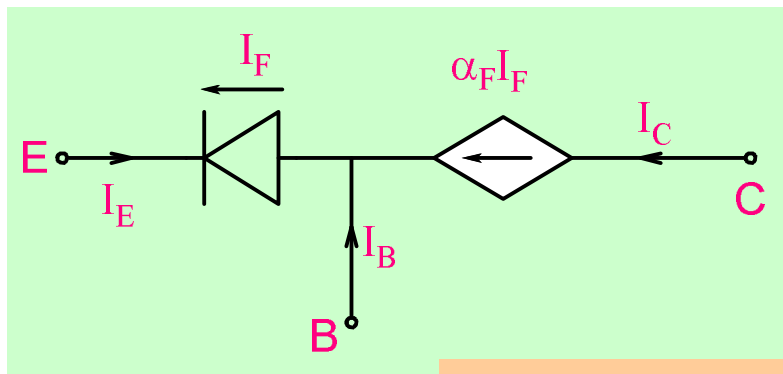
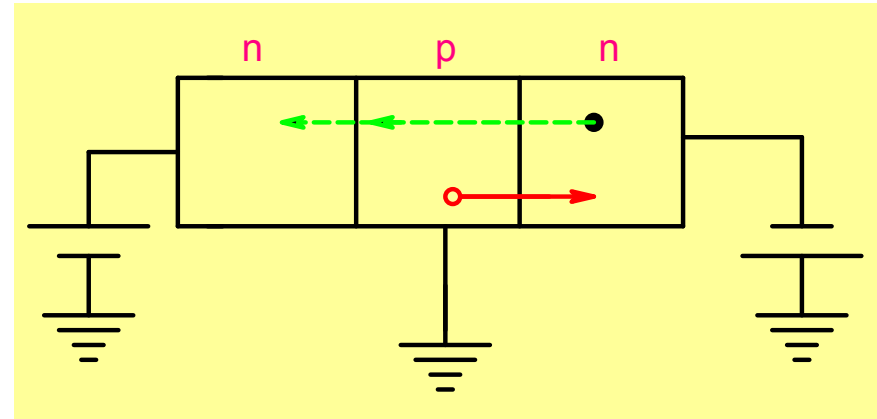


EE210: Microelectronics-I




Lecture-10 : Bipolar Junction Transistor-3



Instructor: Y. S. Chauhan

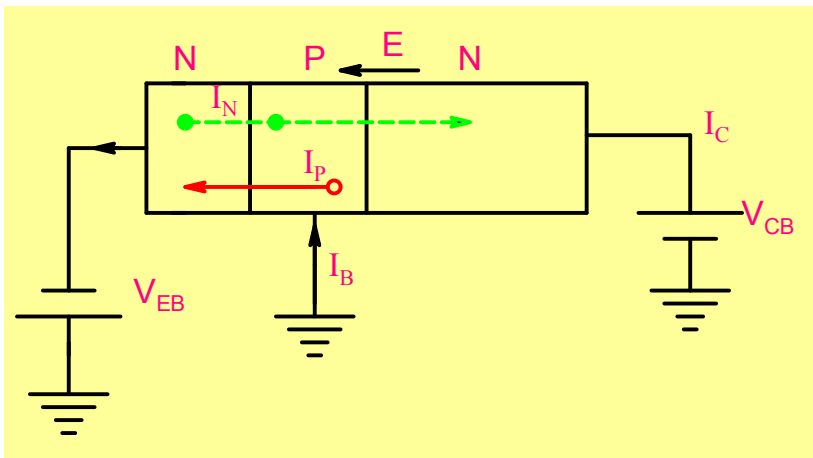Slides from: B. Mazhari
Dept. of EE, IIT Kanpur




Ebers Moll Model

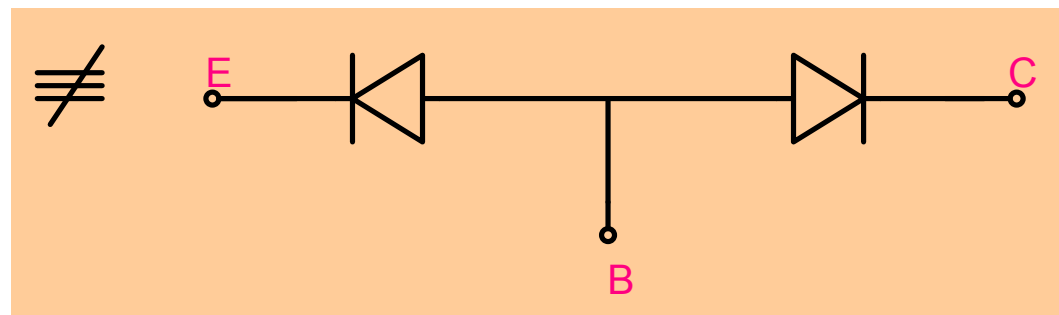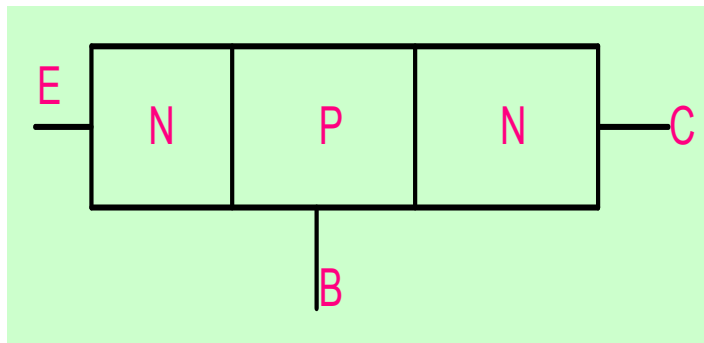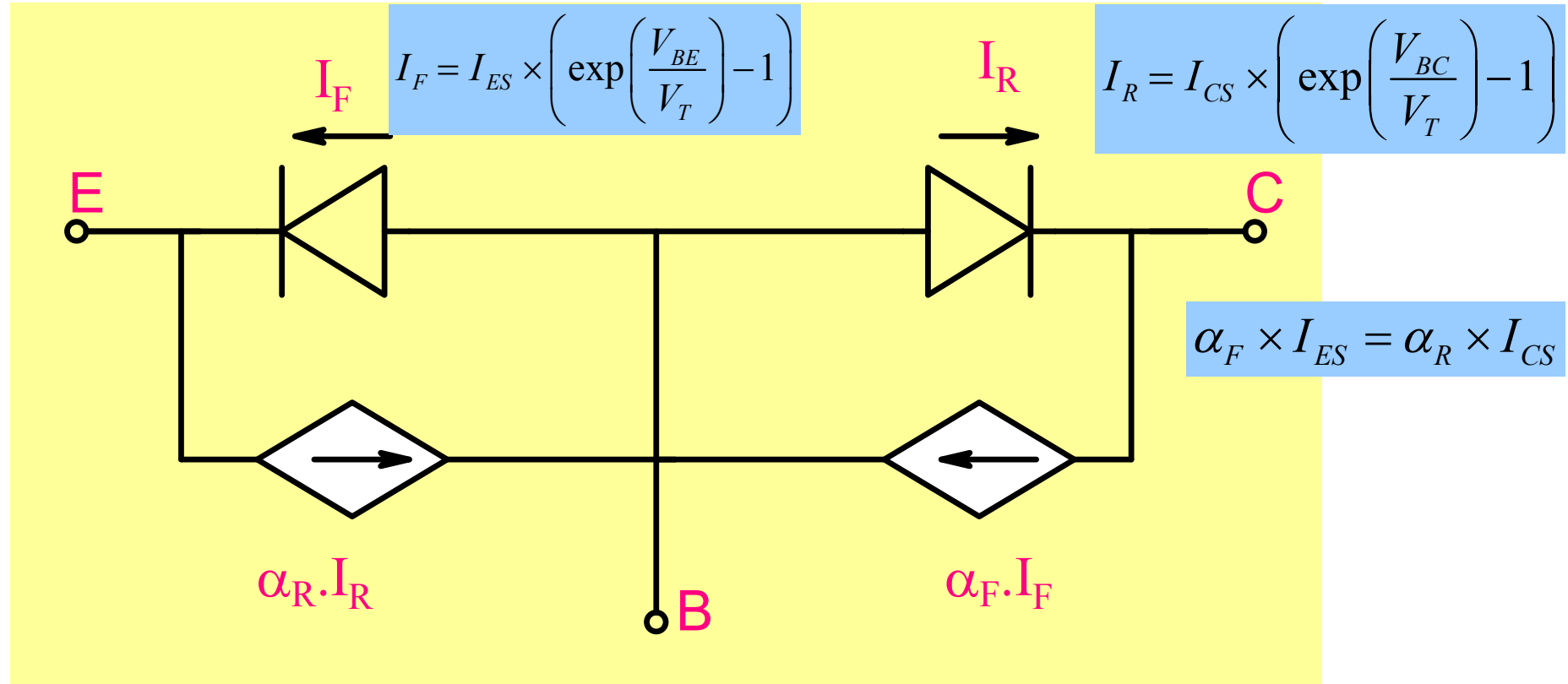


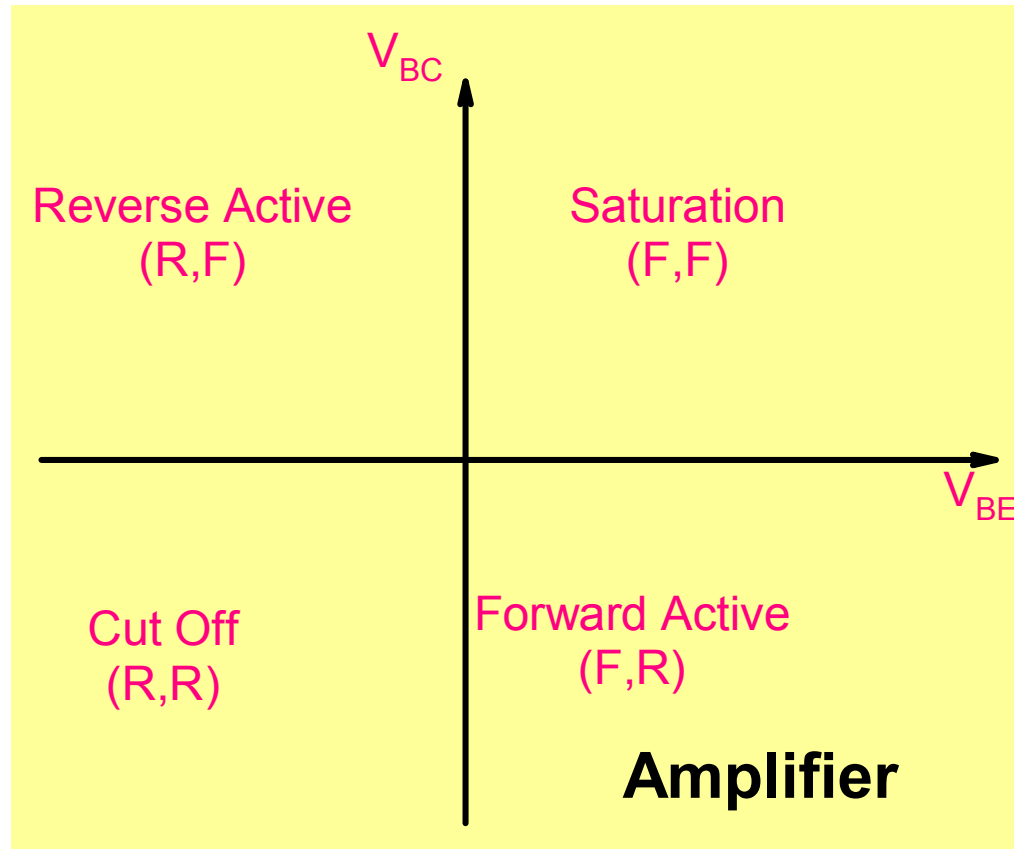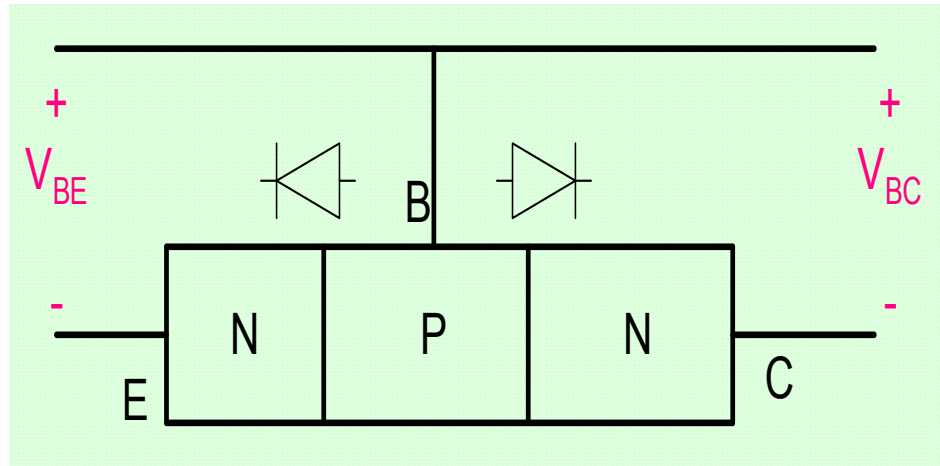

Forward Active Mode: Early Voltage

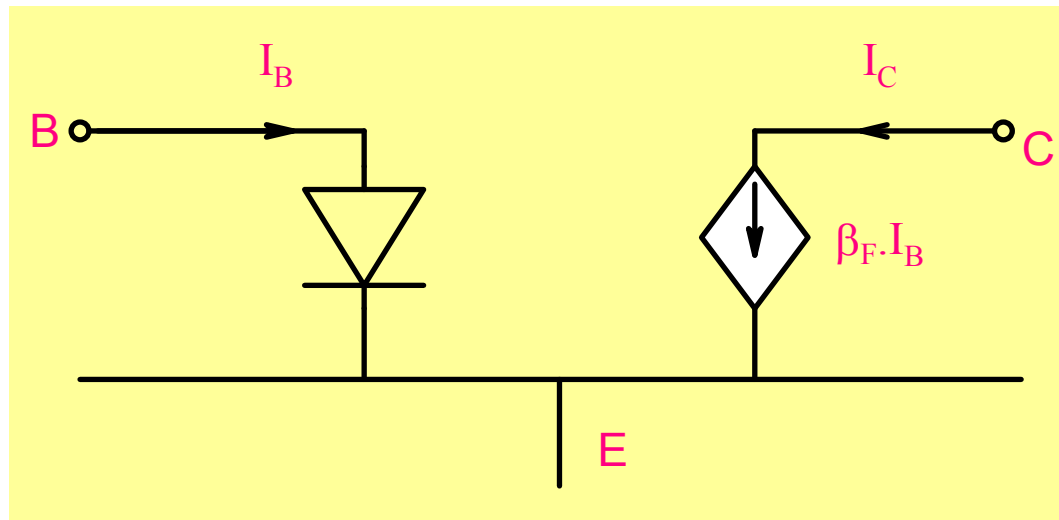

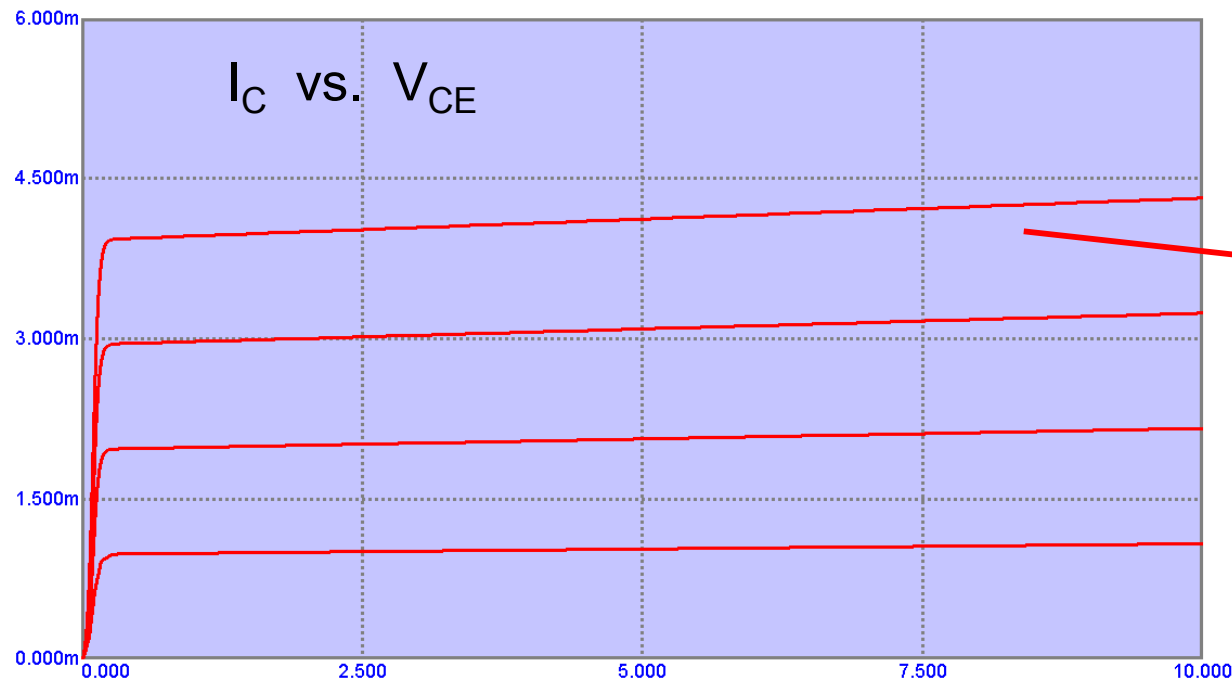
$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta_F}$$



Current does increase with collector voltage through the increase is usually small

Early Voltage

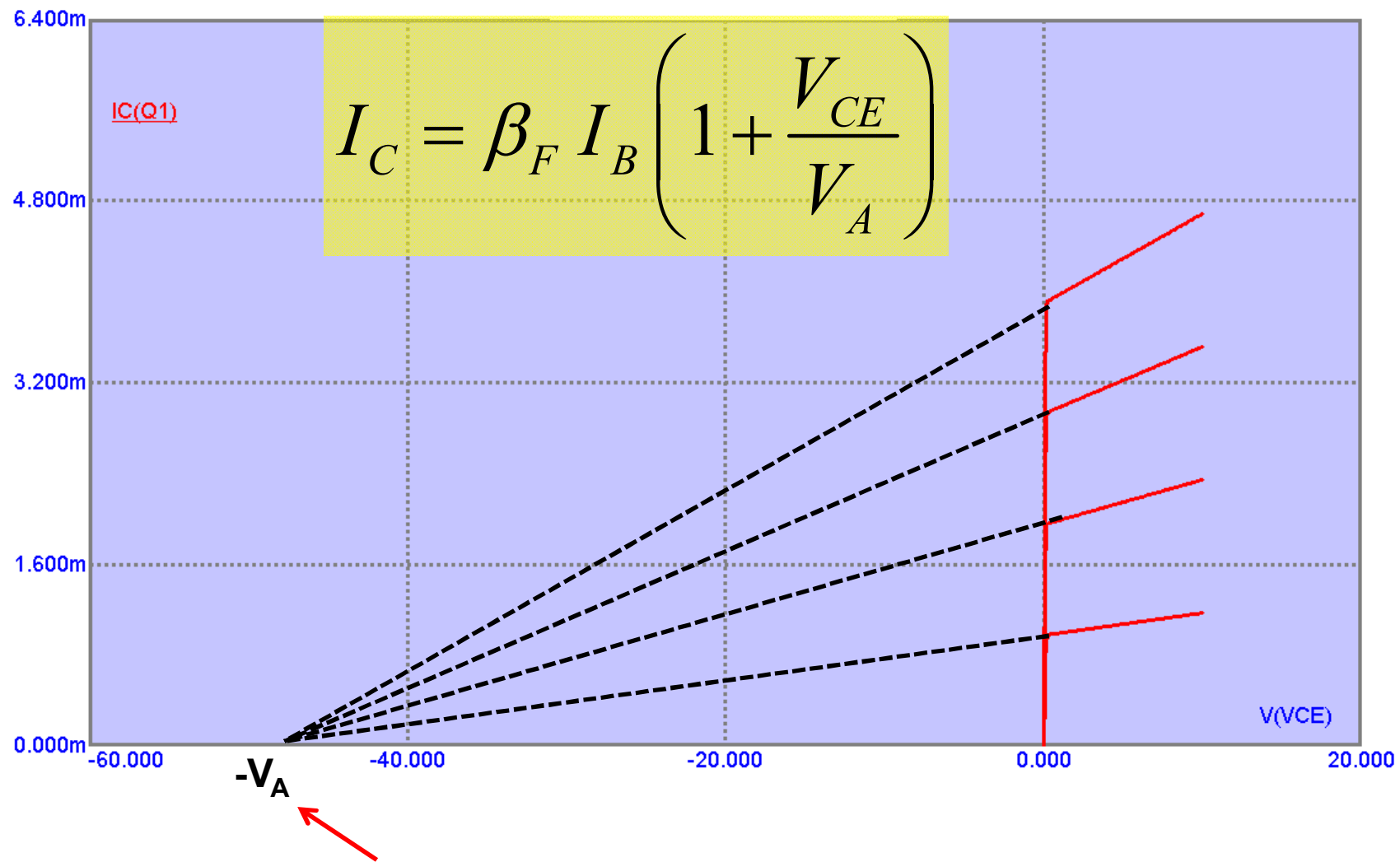


$$I_C = \beta_F I_B \left(1 + \frac{V_{CE}}{V_A} \right)$$

Early Voltage

Base Width Modulation
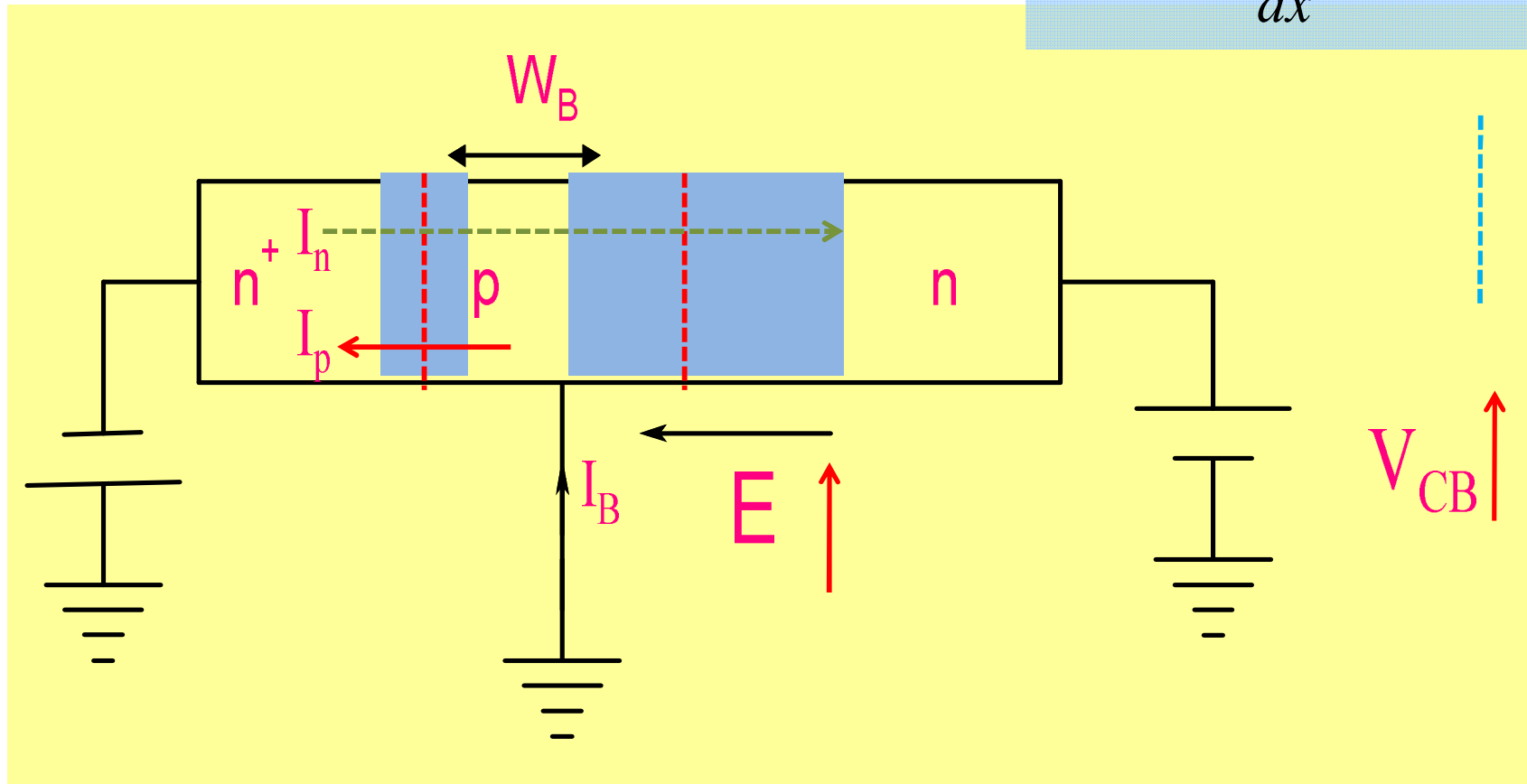
$$I_N = qD_n \frac{dn}{dx} \cong qD_n \times \frac{n(0)}{W_B}$$





Decrease in effective base width causes an increase in collector current !

$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$


$$I_B = \frac{I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)}{\beta_F}$$

$$I_C = \beta_F I_B \left(1 + \frac{V_{CE}}{V_A} \right)$$

Variation of current gain with Current

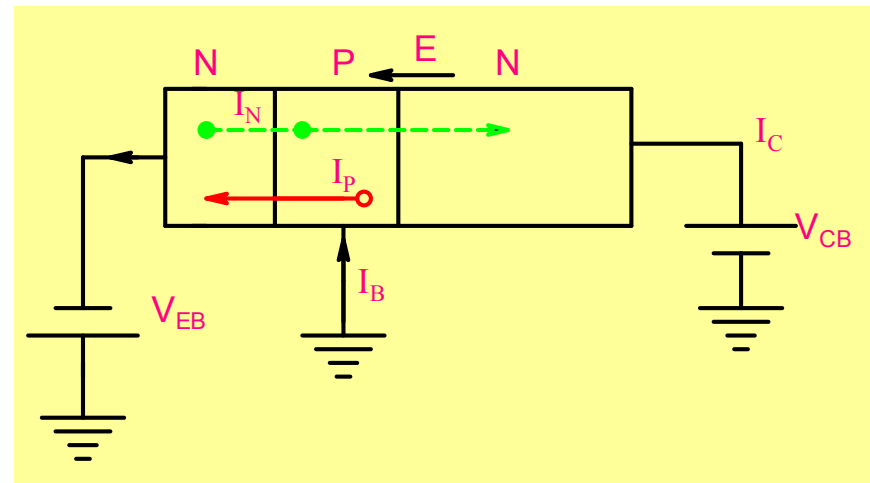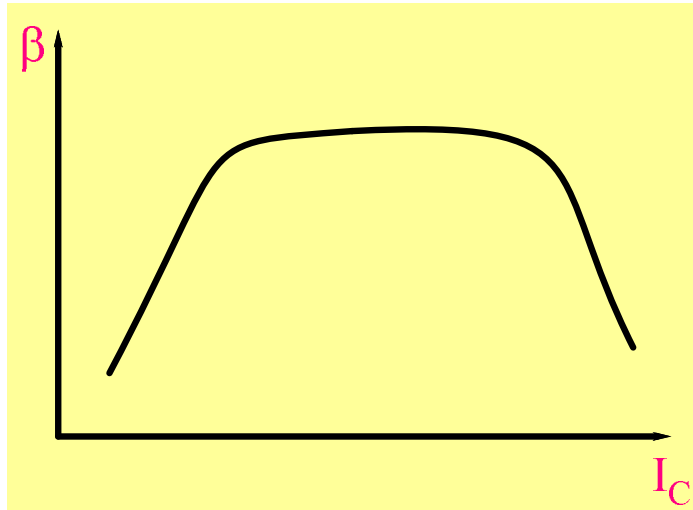


NPN Transistor: P2N2222

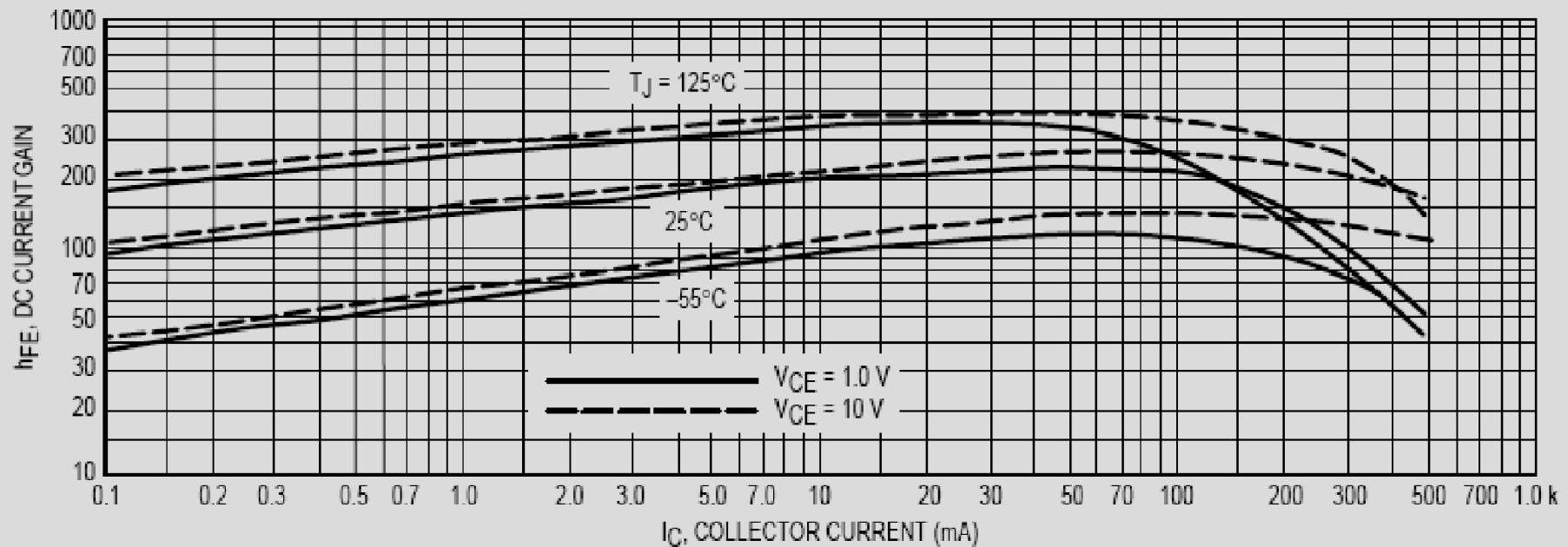


Breakdown

Collector-Base junction Breakdown

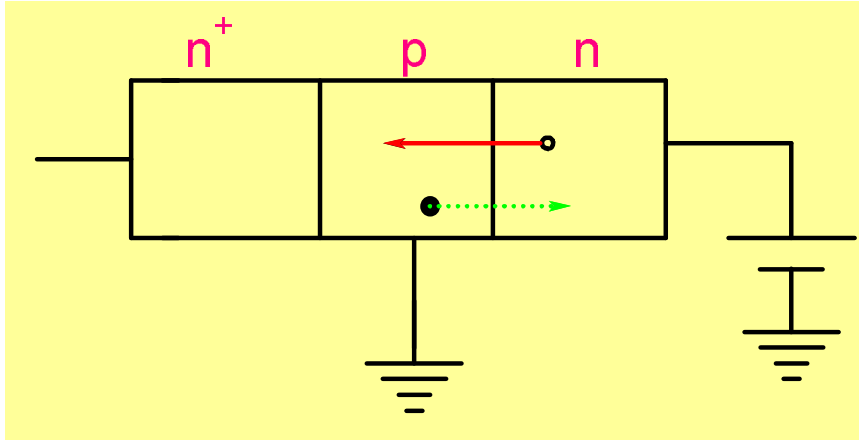

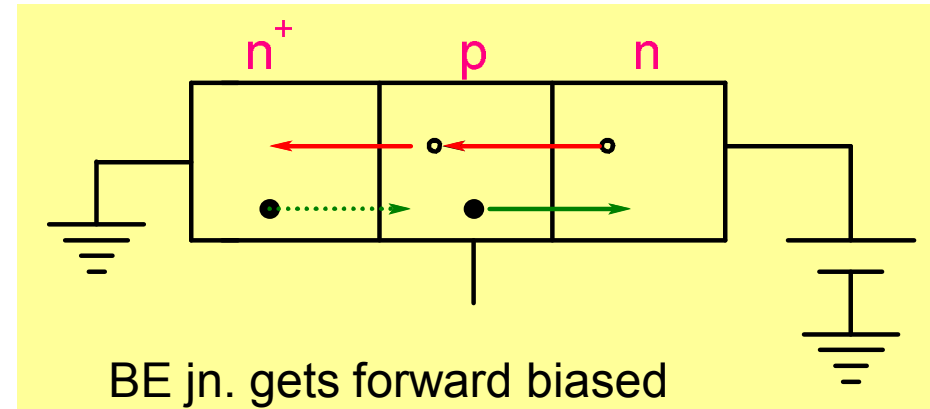BV_{CBO} : Breakdown voltage with emitter open




BV_{CEO} : Breakdown voltage with base Open.

Example: P2N2222: $BV_{CBO} \sim 75V$ while $BV_{CEO} \sim 40V$

Breakdown


Emitter-Base junction Breakdown

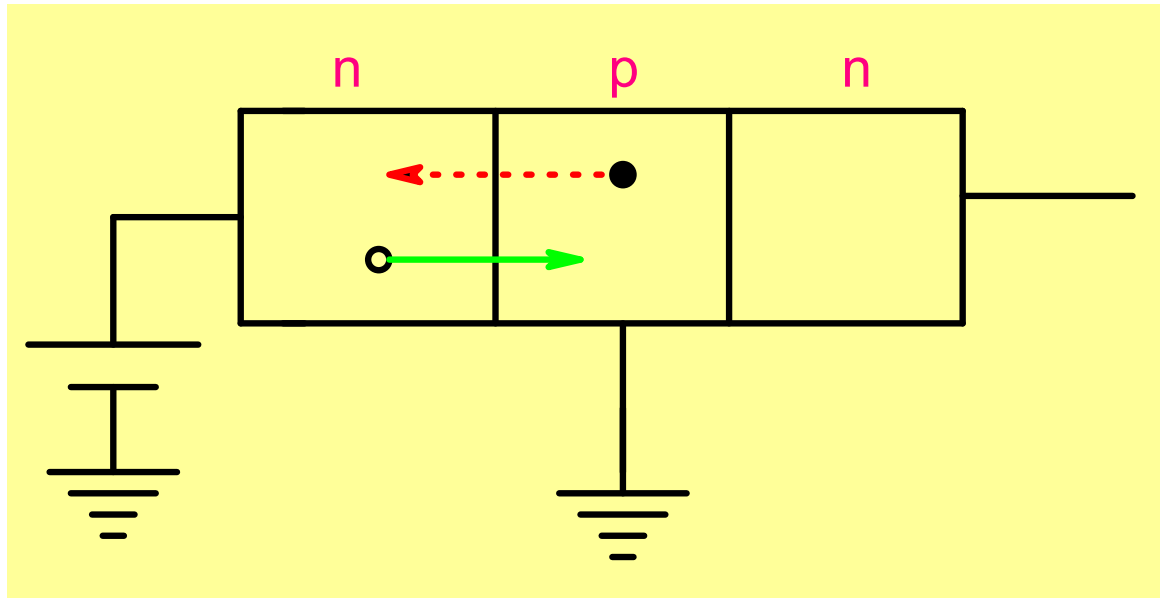



BV_{EBO} : Breakdown voltage with collector open

Example: P2N2222: $BV_{EBO} \sim 6V$ (much smaller due to heavy doping)



BJT : Small Signal Model

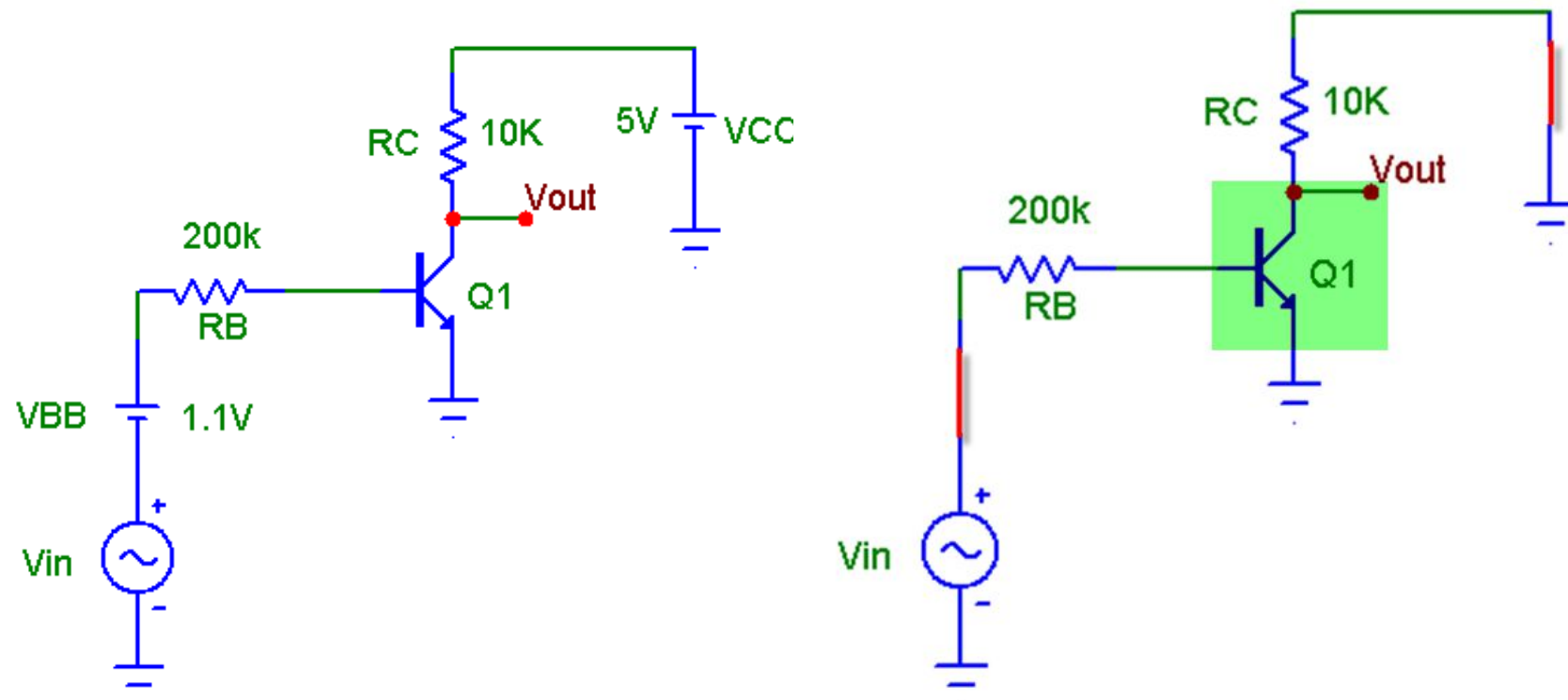

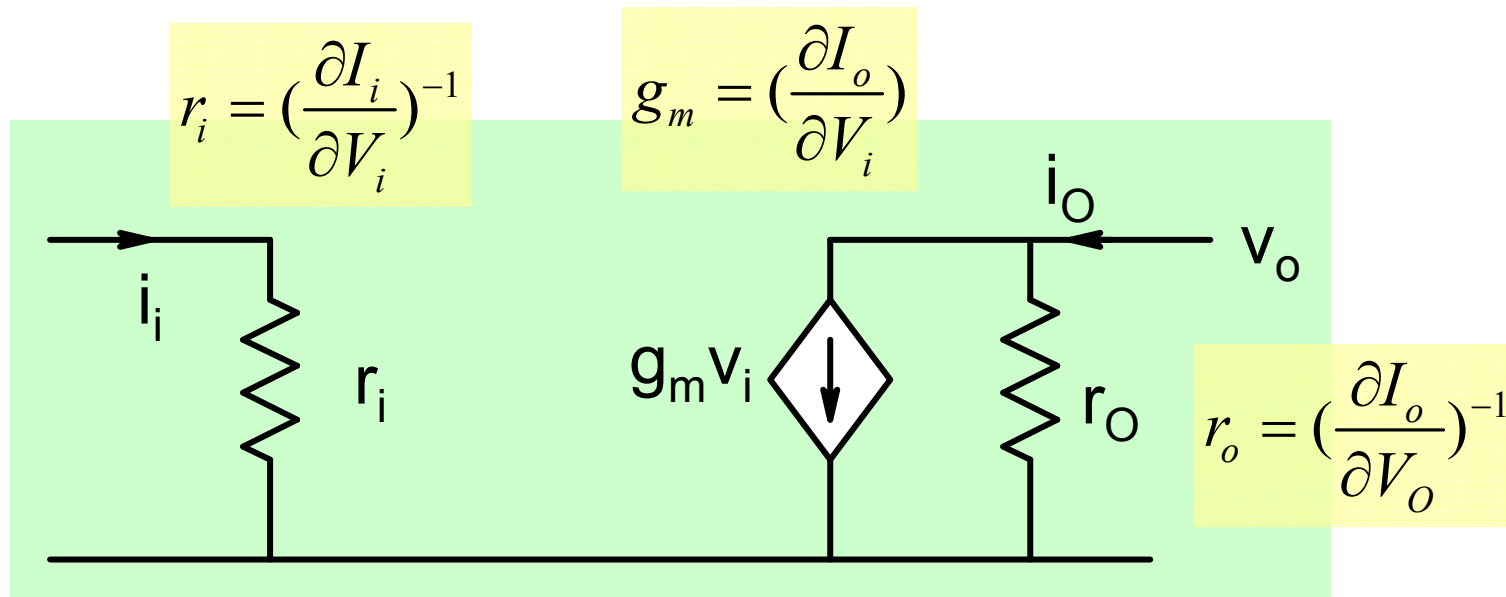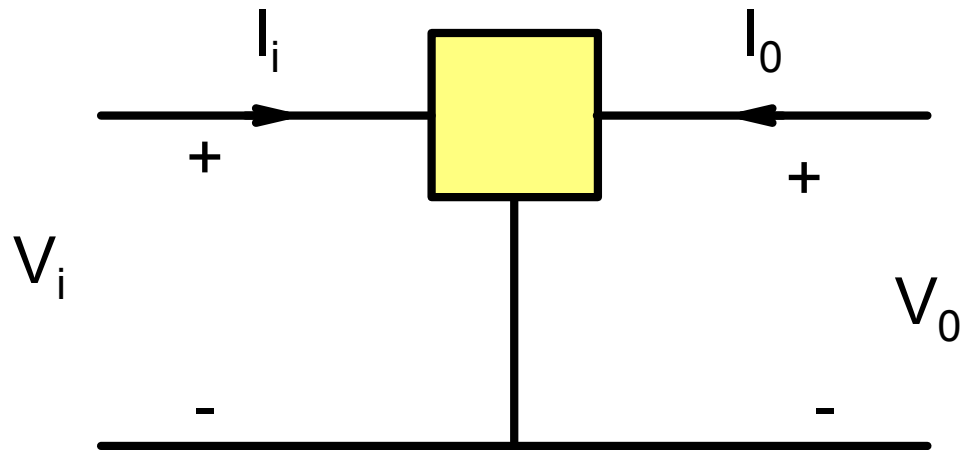Complete **small signal model** (dc) for a 3-terminal **unilateral** device.



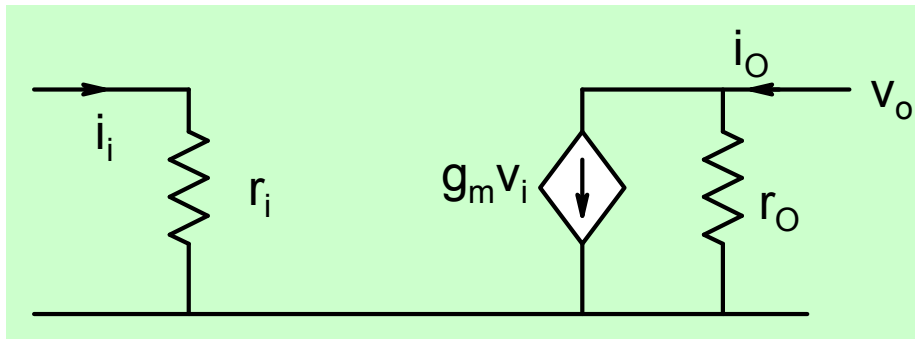
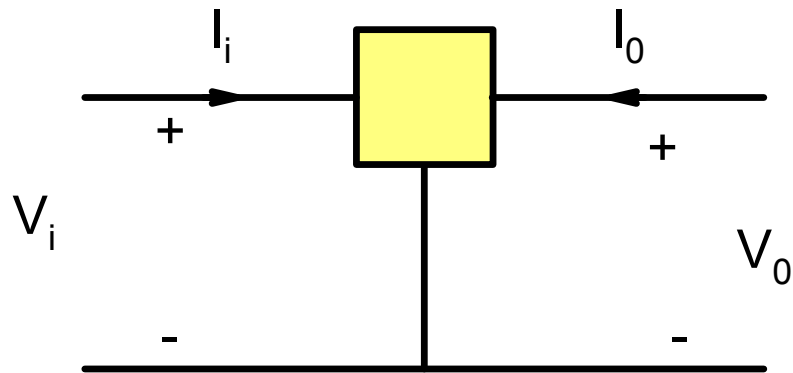
Complete **small signal model**
(dc) for a 3-terminal unilateral
device.



$$r_i = \left(\frac{\partial I_i}{\partial V_i} \right)^{-1}$$

$$g_m = \left(\frac{\partial I_o}{\partial V_i} \right)$$

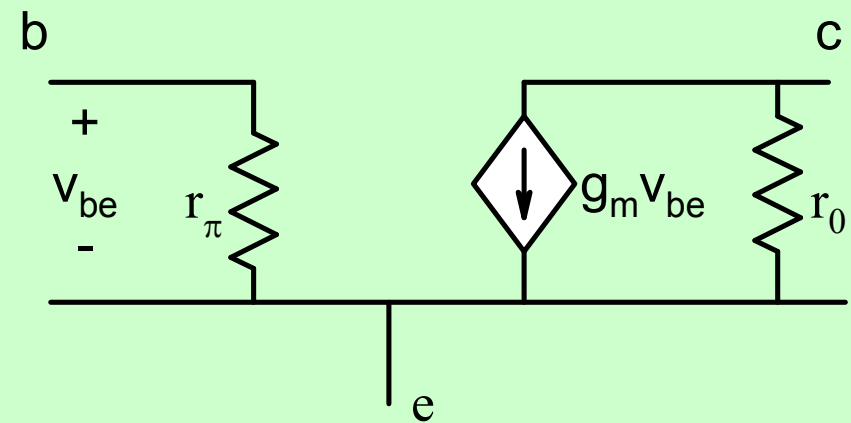
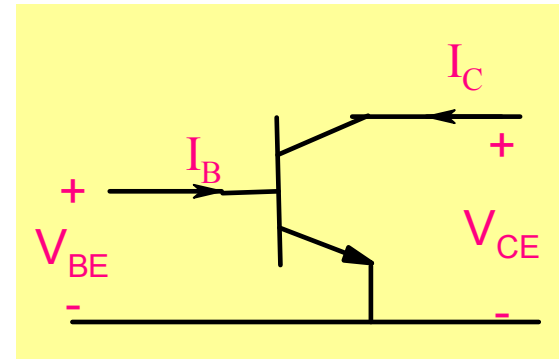
$$r_o = \left(\frac{\partial I_o}{\partial V_o} \right)^{-1}$$



$$I_b = \frac{I_S}{\beta_F} \left(\exp\left(\frac{V_{be}}{V_T}\right) - 1 \right)$$

$$r_\pi^{-1} = \left. \frac{\partial I_b}{\partial V_{be}} \right|_{I_B} \cong \frac{I_B}{V_T}$$
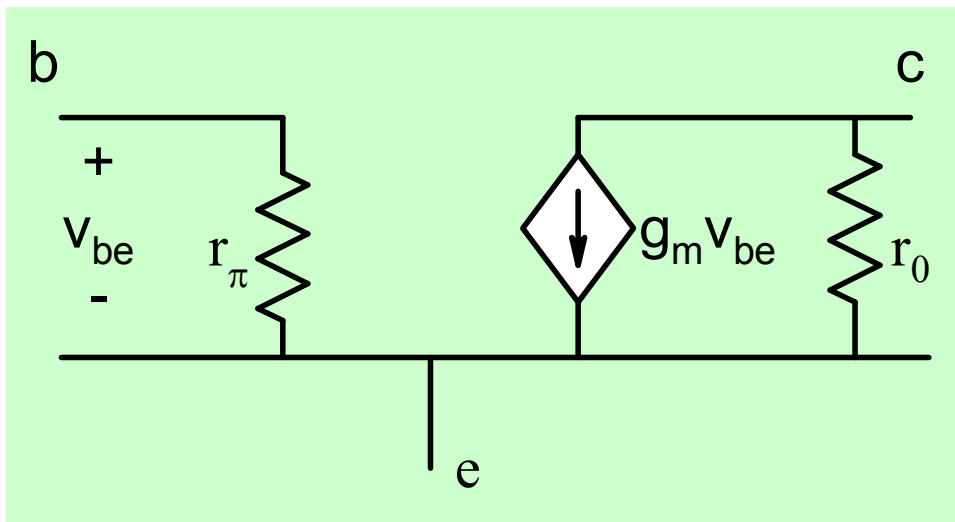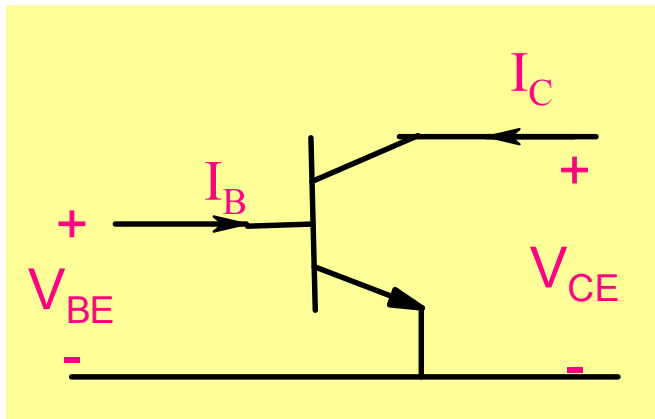
$$r_\pi = \frac{V_T}{I_B} = \frac{V_T}{I_C} \cdot \beta ; \quad r_\pi = r_E \cdot \beta$$




$$I_c = I_S \left(\exp\left(\frac{V_{be}}{V_T}\right) - 1 \right) \left(1 + \frac{V_{ce}}{V_A} \right)$$

$$g_m = \left. \frac{\partial I_c}{\partial V_{be}} \right|_{V_{CE}} \cong \frac{I_C}{V_T}$$

$$r_o^{-1} = \left. \frac{\partial I_c}{\partial V_{ce}} \right|_{V_{BE}} = \frac{I_C}{V_{CE} + V_A} \approx \frac{I_C}{V_A}$$

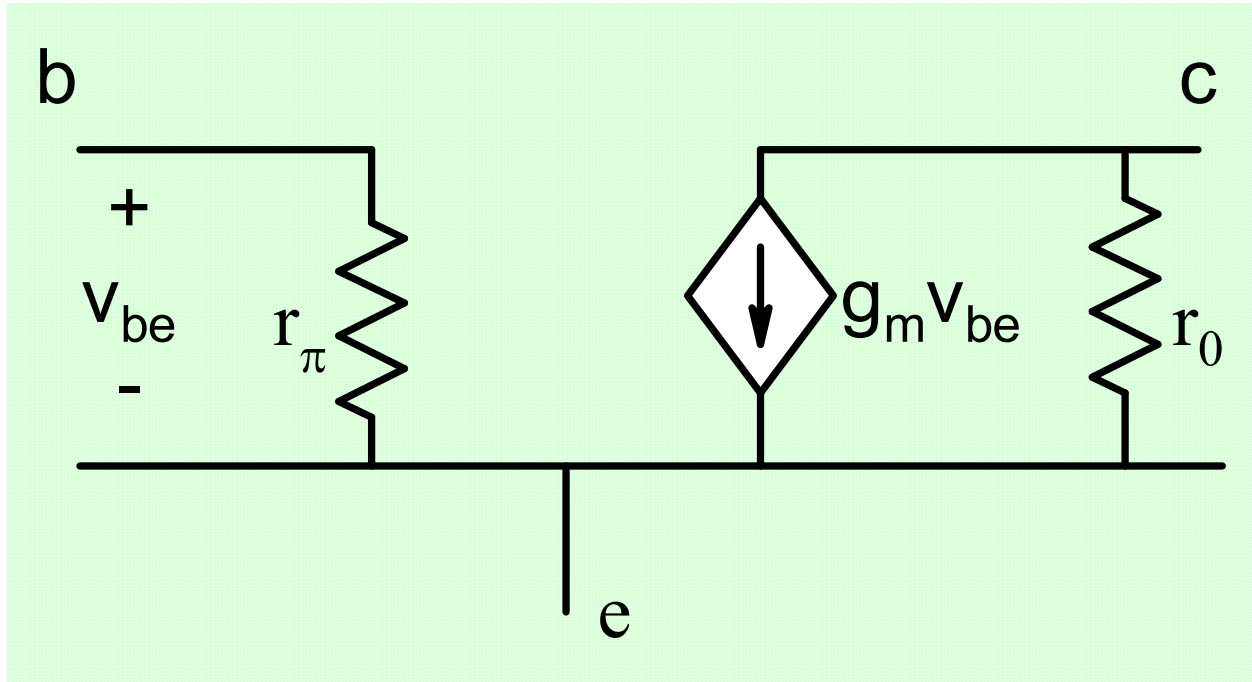Hybrid-pi Small Signal Model : low frequency



$$r_\pi = \frac{V_T}{I_B} = \frac{V_T}{I_C} \cdot \beta$$

$$g_m = \frac{I_C}{V_T} ; r_o = \frac{V_A}{I_C}$$

$$I_b = \frac{I_S}{\beta_F} \left(\exp\left(\frac{V_{be}}{V_T}\right) - 1 \right) \quad I_c = I_S \left(\exp\left(\frac{V_{be}}{V_T}\right) - 1 \right) \left(1 + \frac{V_{ce}}{V_A} \right)$$

Validity : $v_{be} \ll V_T$