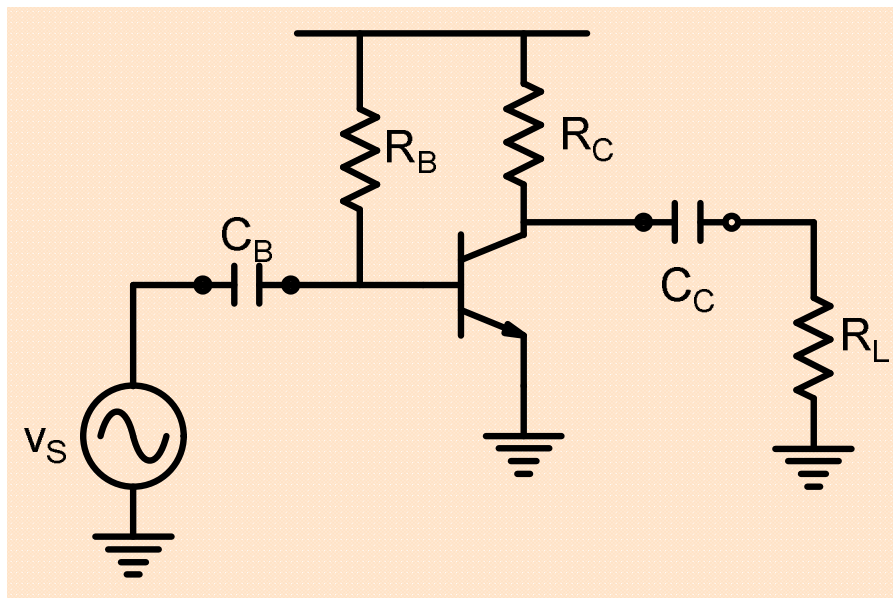


EE210: Microelectronics-I


Lecture-32: Differential Amplifiers_4

Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur







$$A_V < \frac{I_{CQ} R_C}{V_T}$$

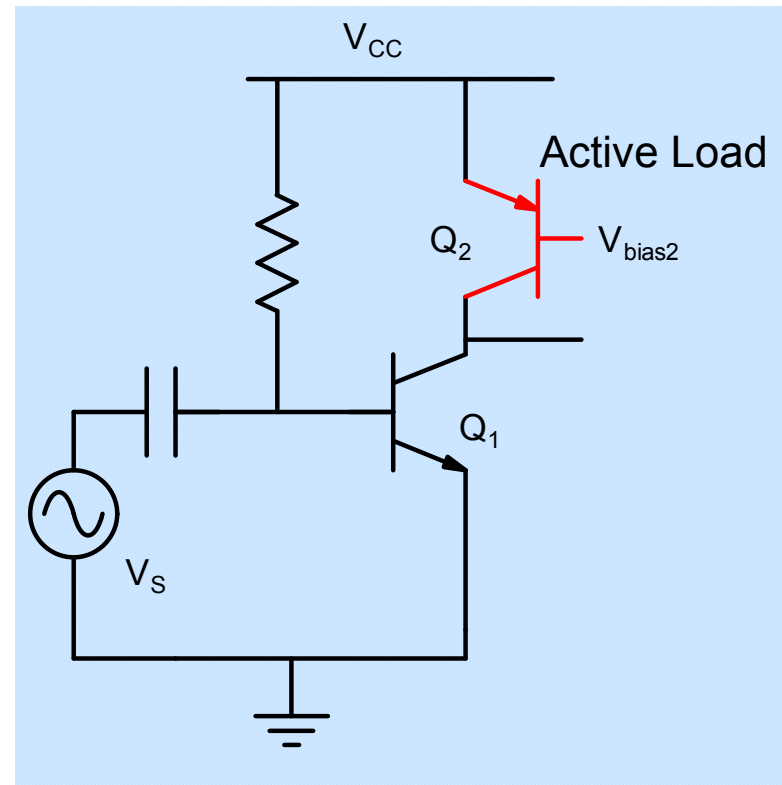



$$|A_V| = \frac{1}{V_T} \times \frac{V_{AN} \times V_{AP}}{V_{AN} + V_{AP}}$$

Differential Amplifier with Active Load

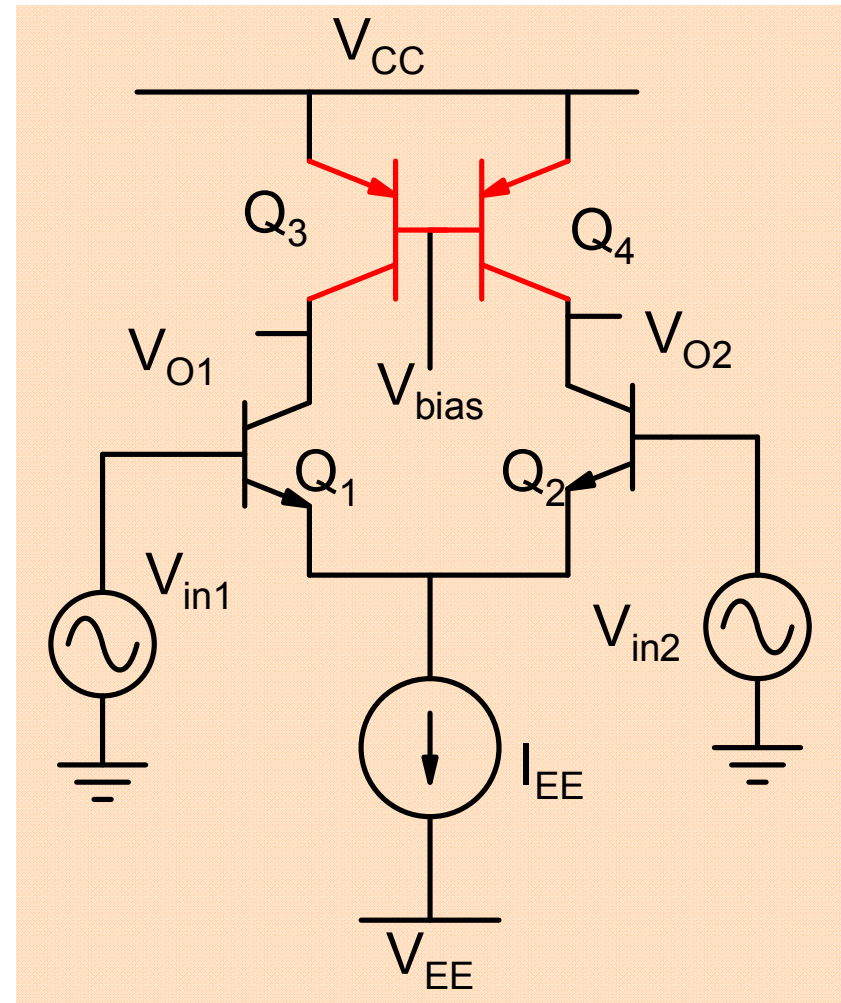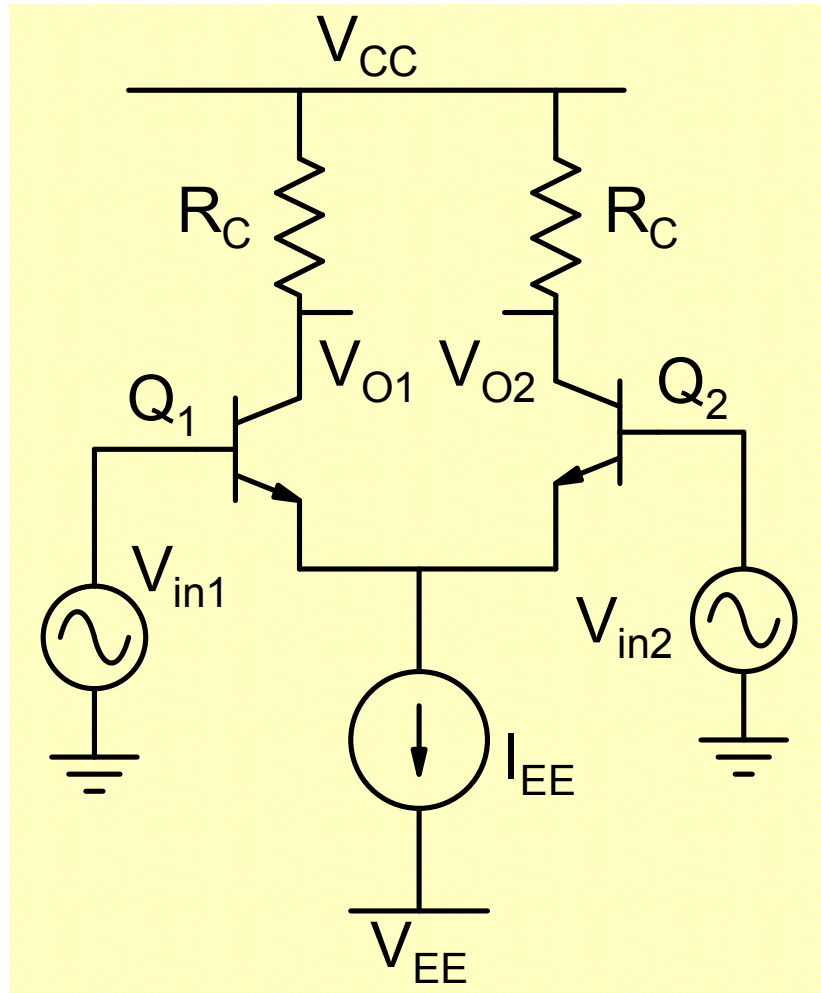

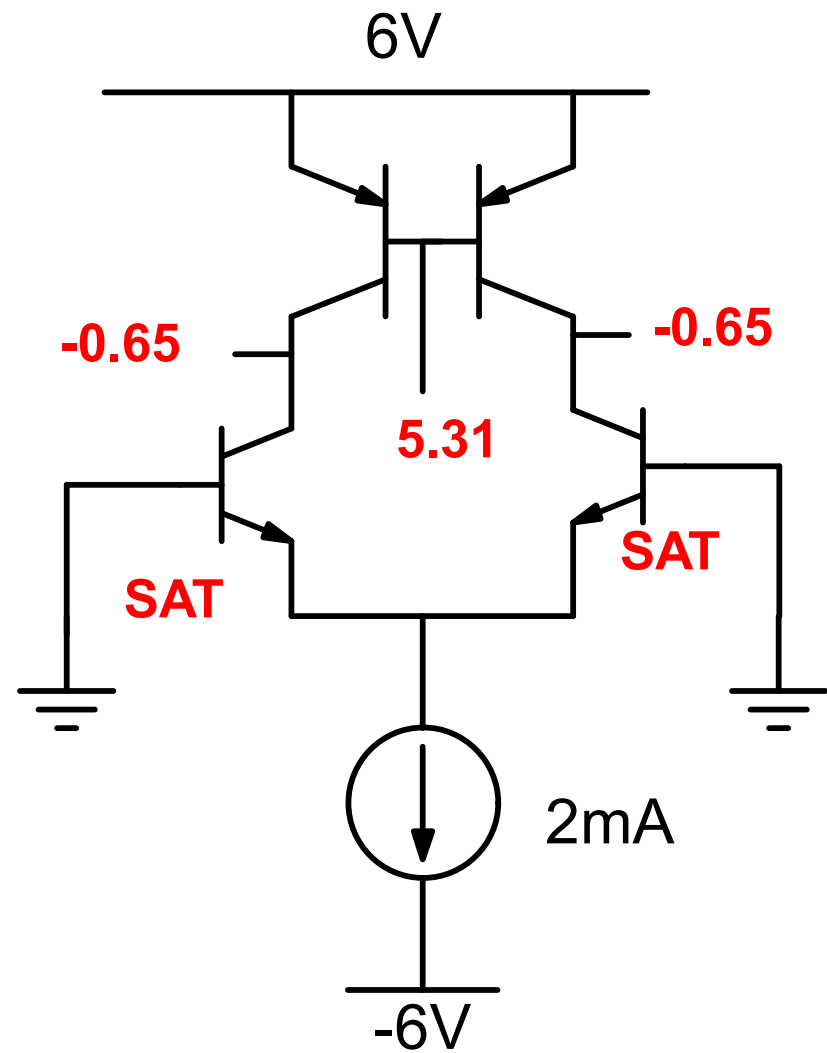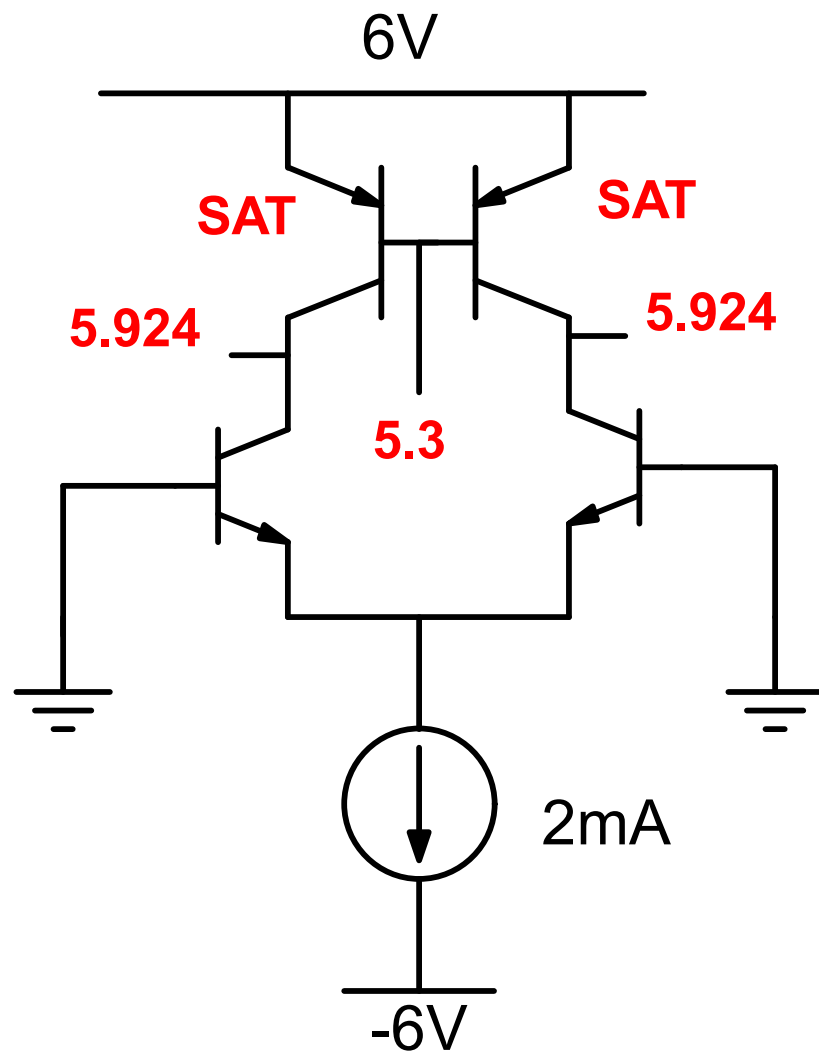

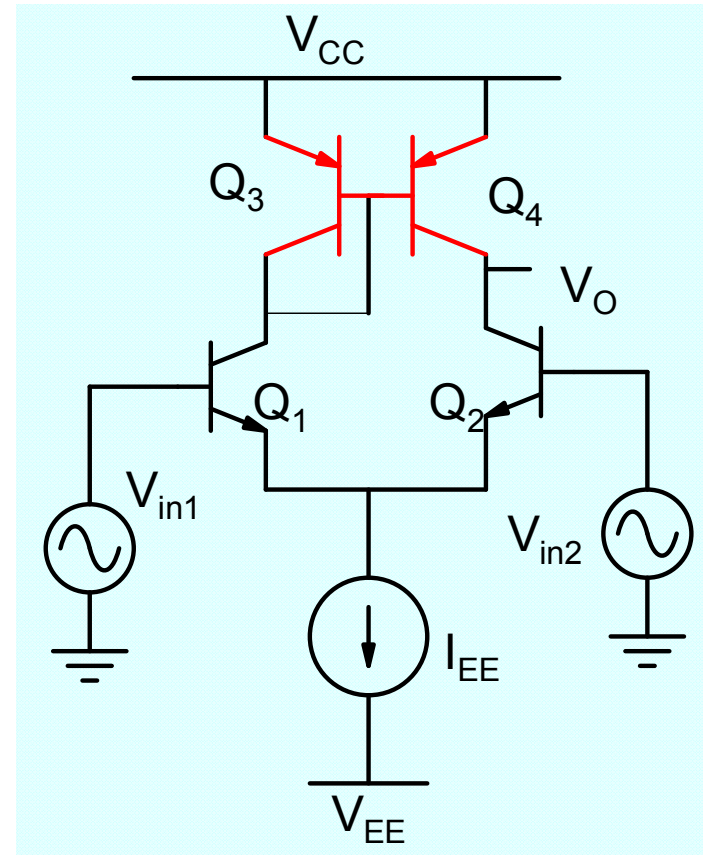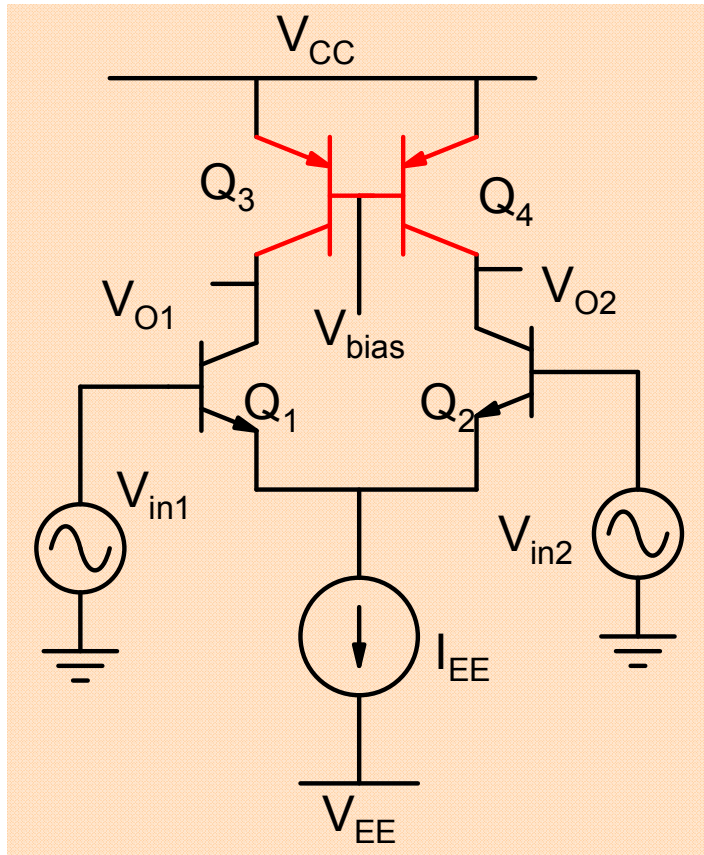Differential amplifier with current mirror load





Bias point is stable, high differential gain and low common mode gain are obtained in this circuit

Note that Q_1 & Q_2 are matched and Q_3 & Q_4 are matched

Example




$$\beta_n = \beta_p = 100$$

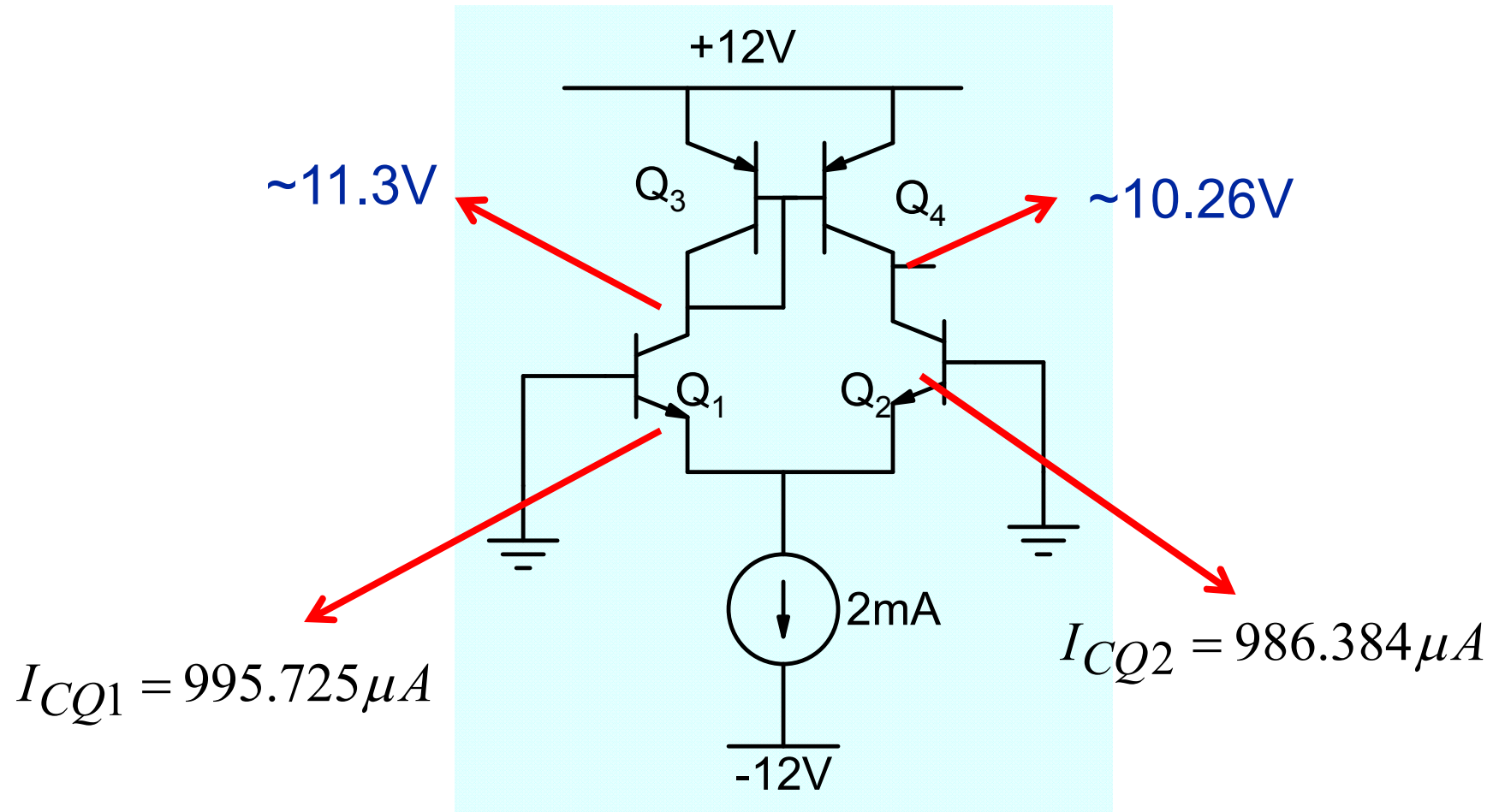

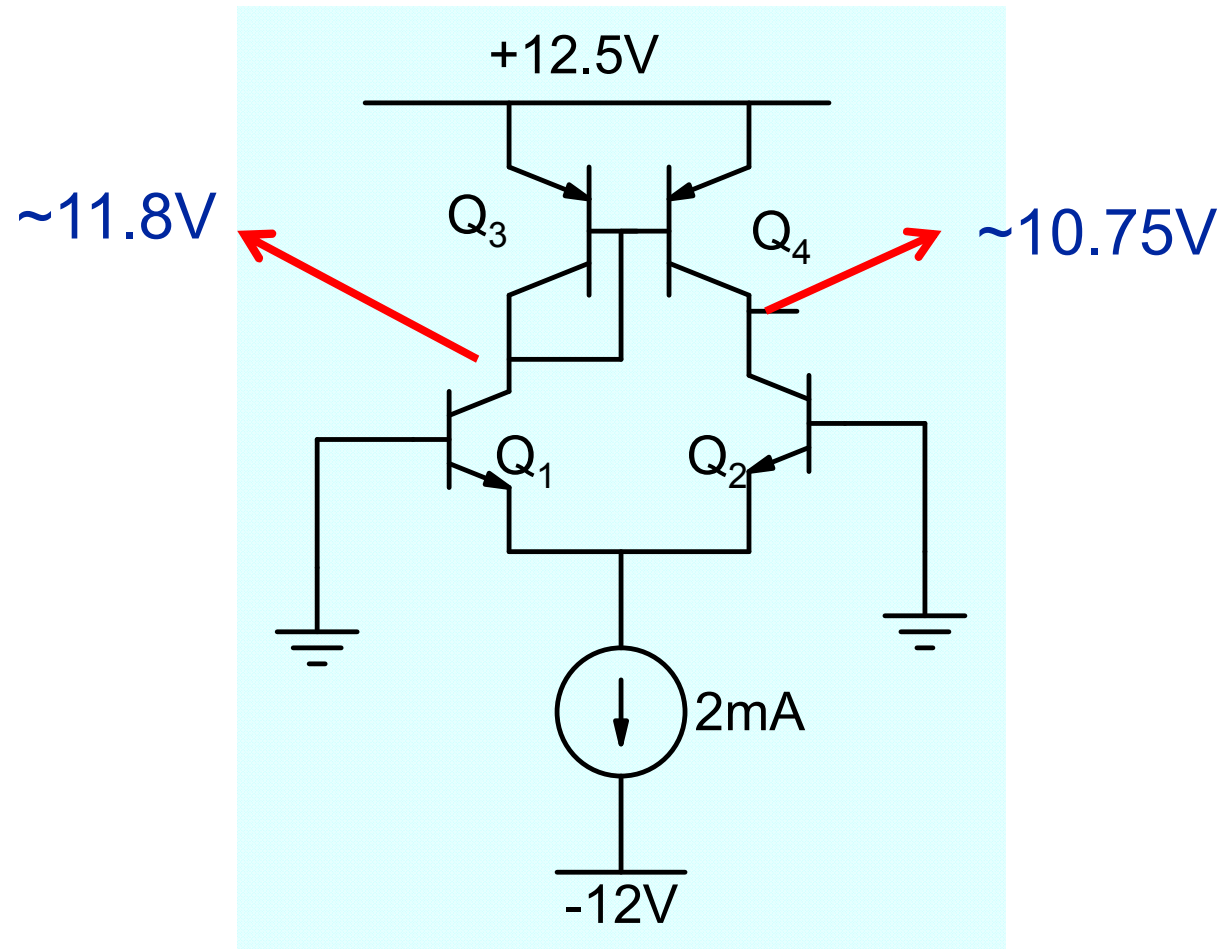





Bias point is much less sensitive !


Differential Mode Analysis

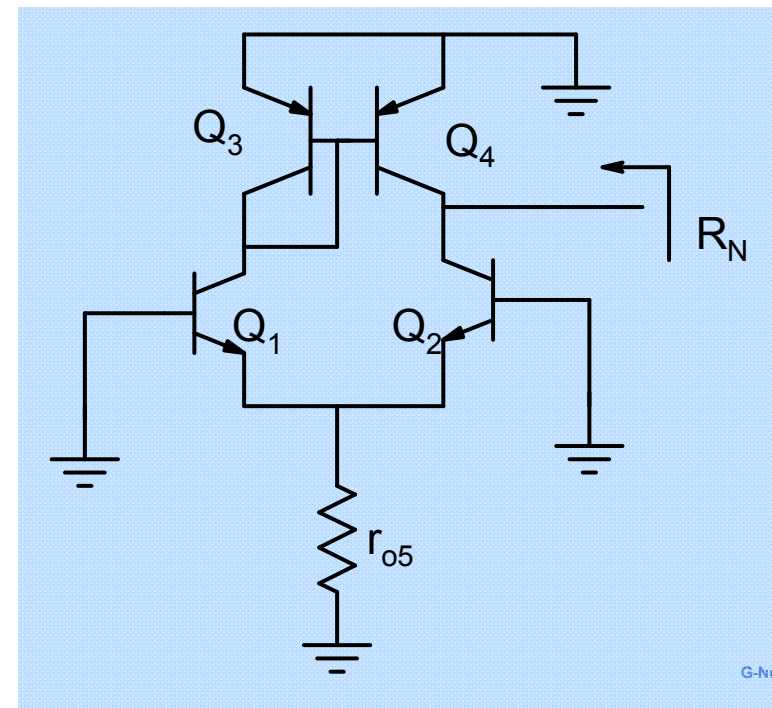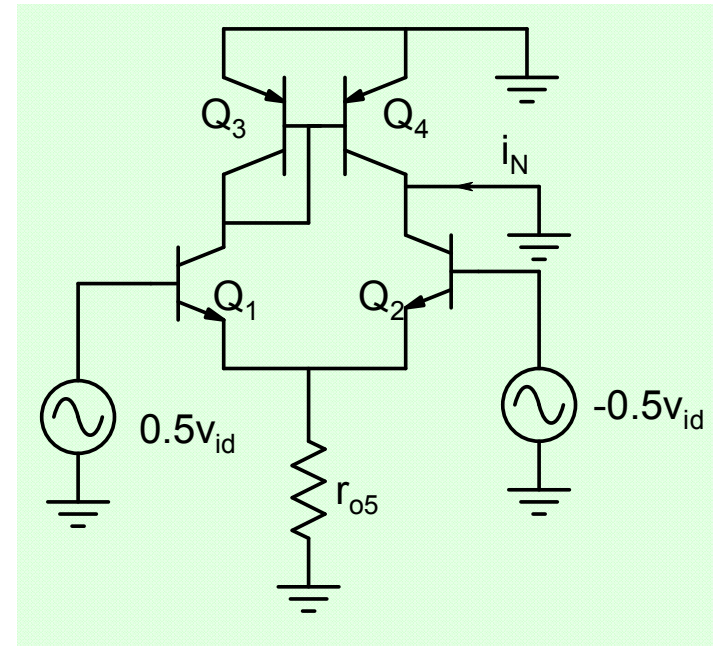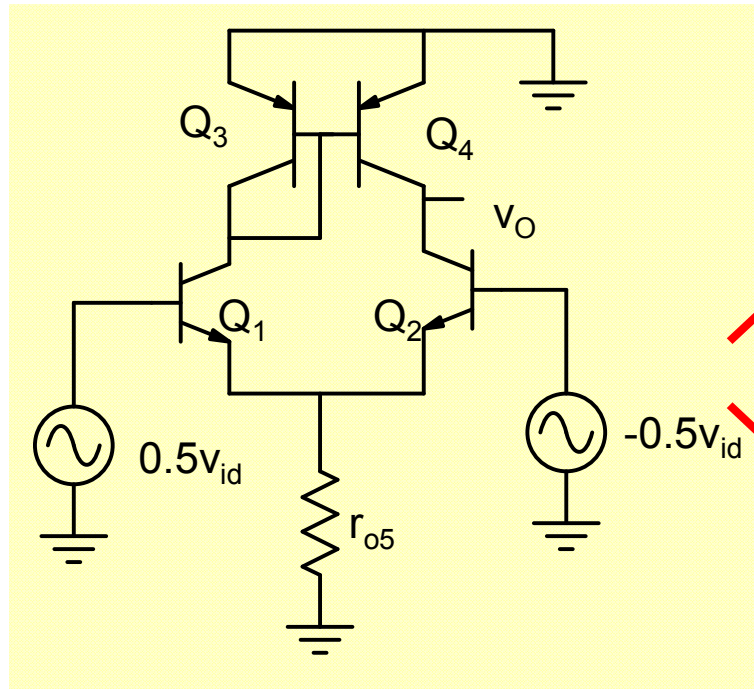

Norton's Current


small

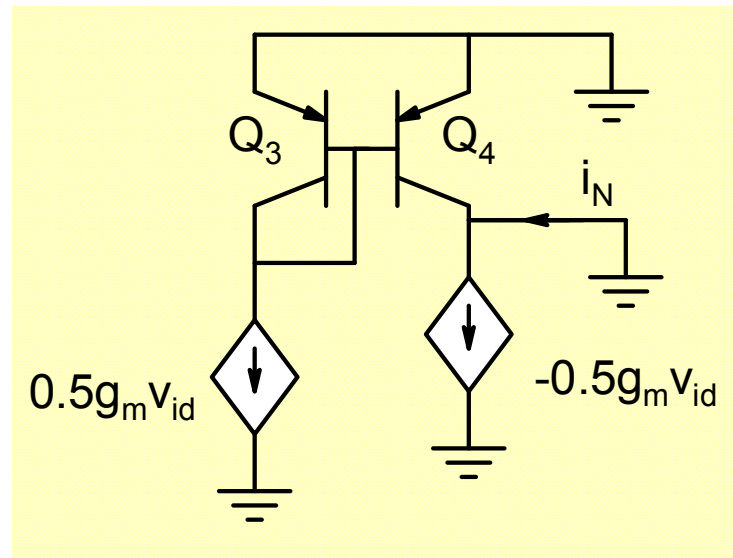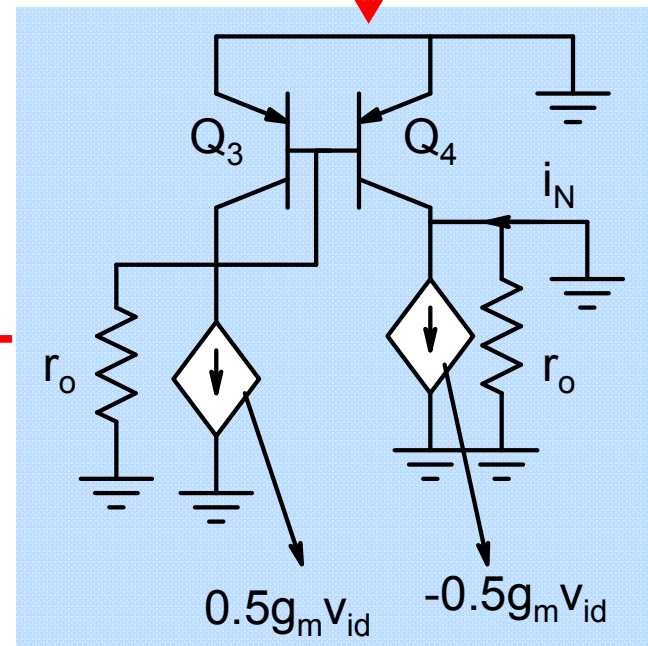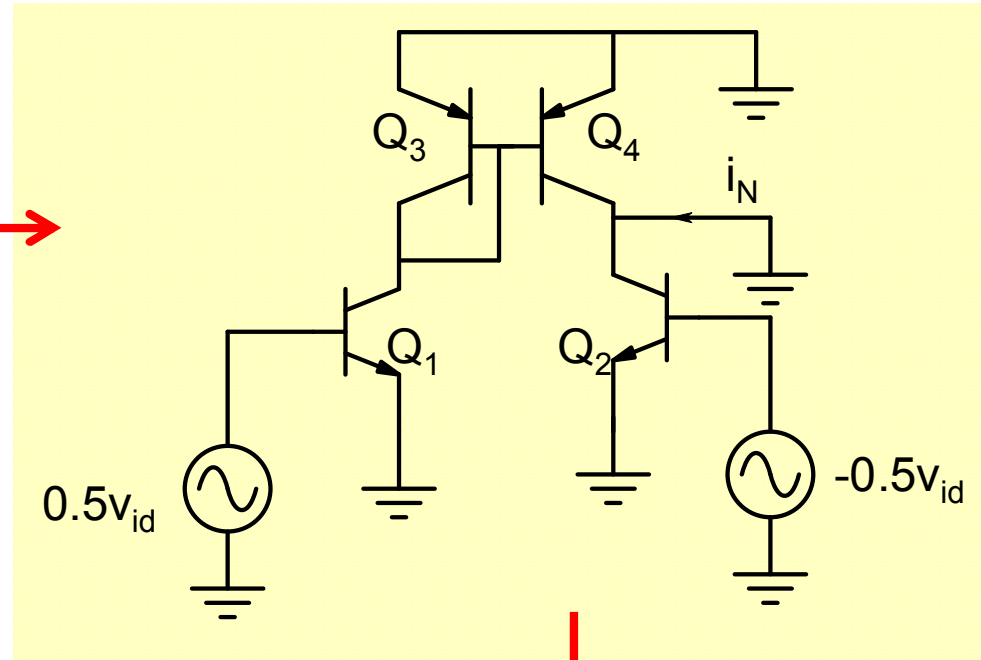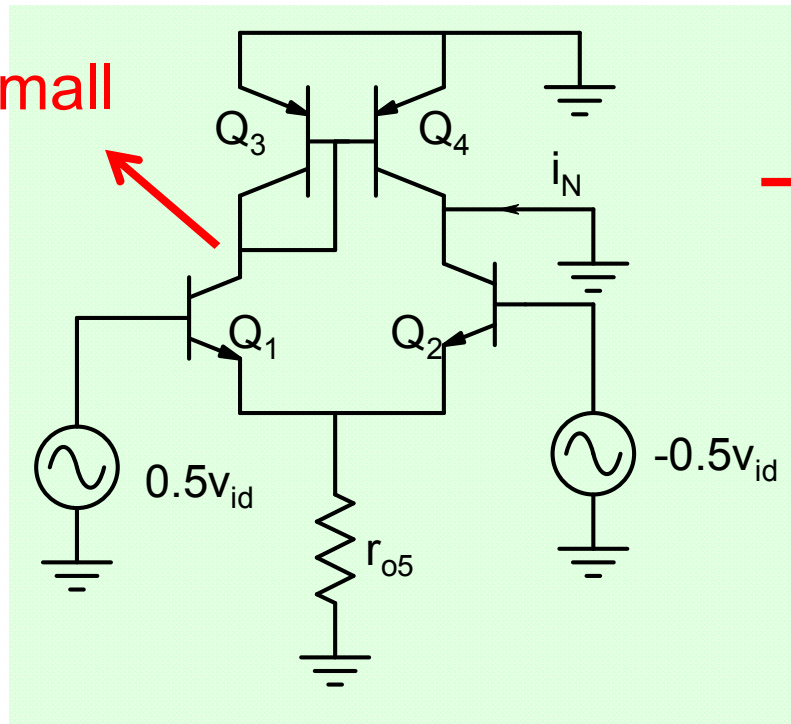

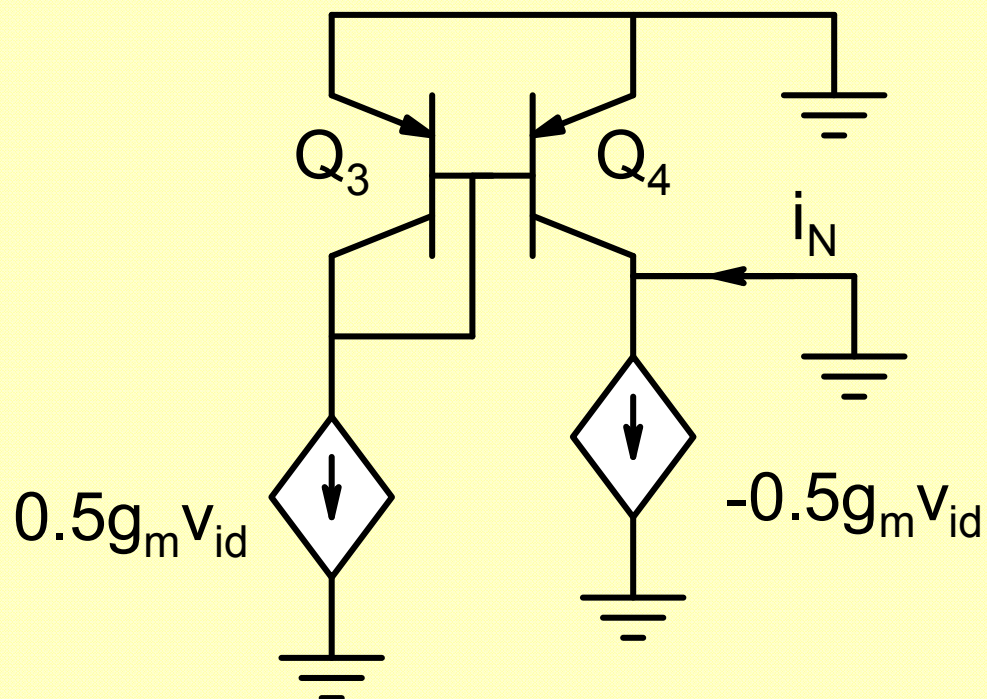


$$i_N = -0.5g_m v_{id} - -0.5g_m v_{id}$$


$$= -g_m v_{id}$$

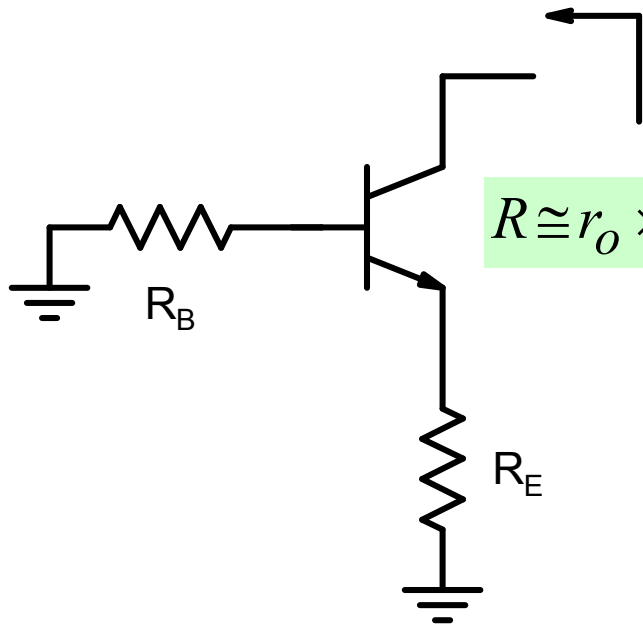

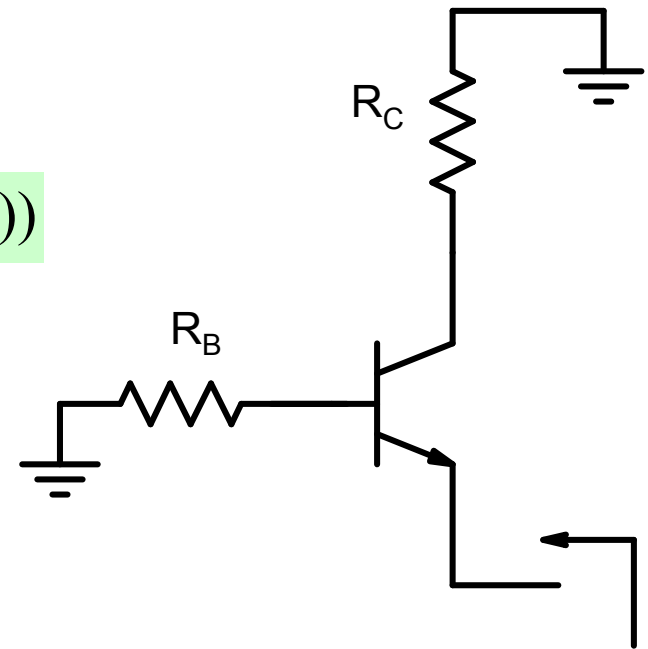
$$R \cong r_o \times (1 + g_m \times R_E \parallel (R_B + r_\pi))$$


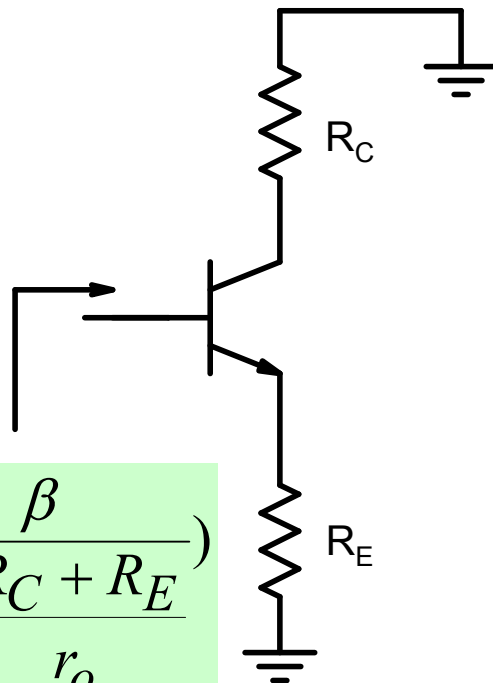
$$R \cong \frac{(R_C + r_o)(R_B + r_\pi)}{R_B + r_\pi + R_C + r_o + \beta r_o}$$



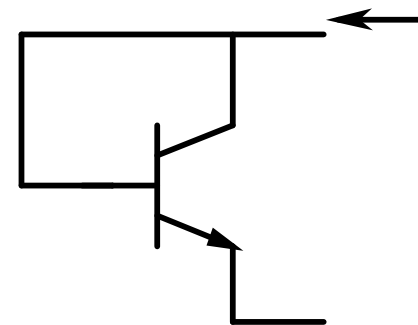
$$R \cong r_\pi + R_E \left(1 + \frac{\beta}{1 + \frac{R_C + R_E}{r_o}}\right)$$




$$R \cong \frac{1}{g_m}$$



Norton's Resistance

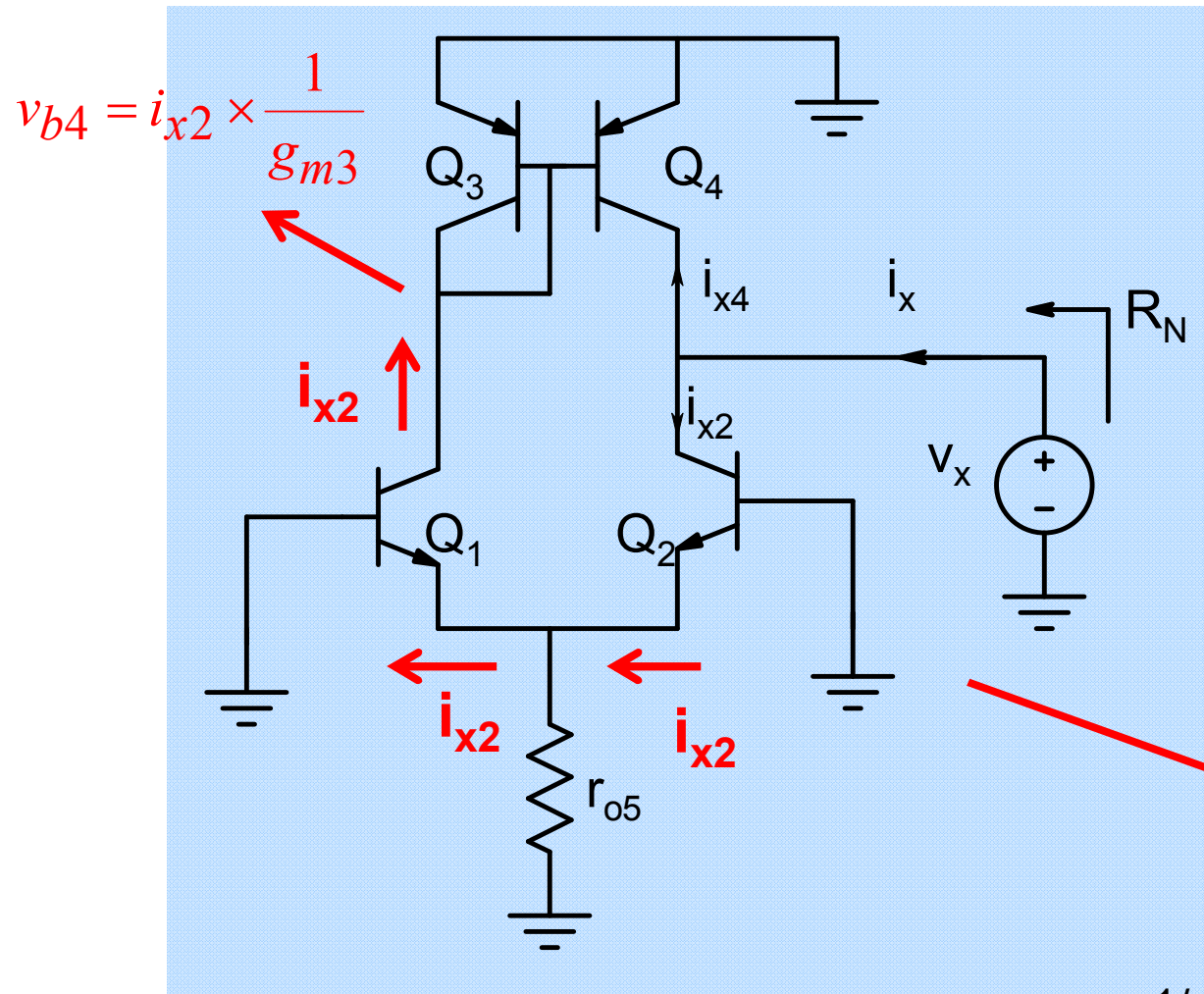

$$\frac{1}{R_N} = \frac{i_x}{v_x} = \frac{i_{x2}}{v_x} + \frac{i_{x4}}{v_x}$$

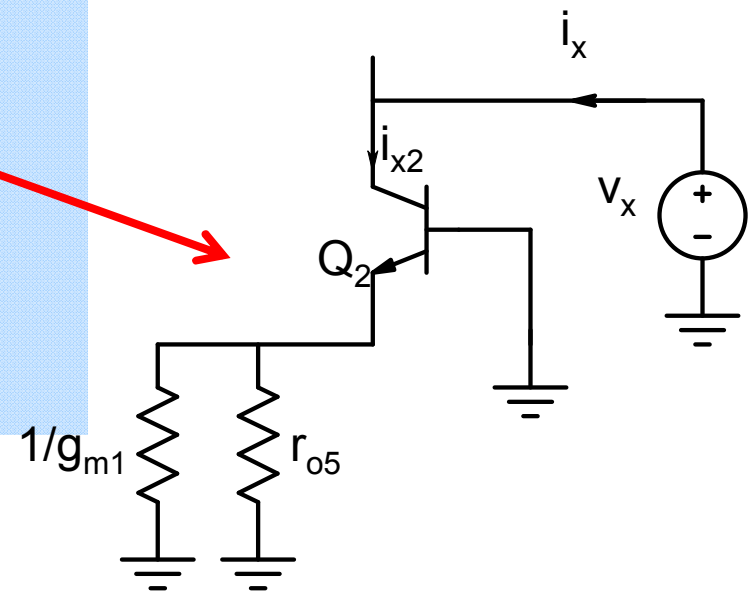
$$i_{x2} = \frac{v_x}{r_{o2} \times \left(1 + g_m \times \frac{1}{g_m}\right)} = \frac{v_x}{2r_{o2}}$$



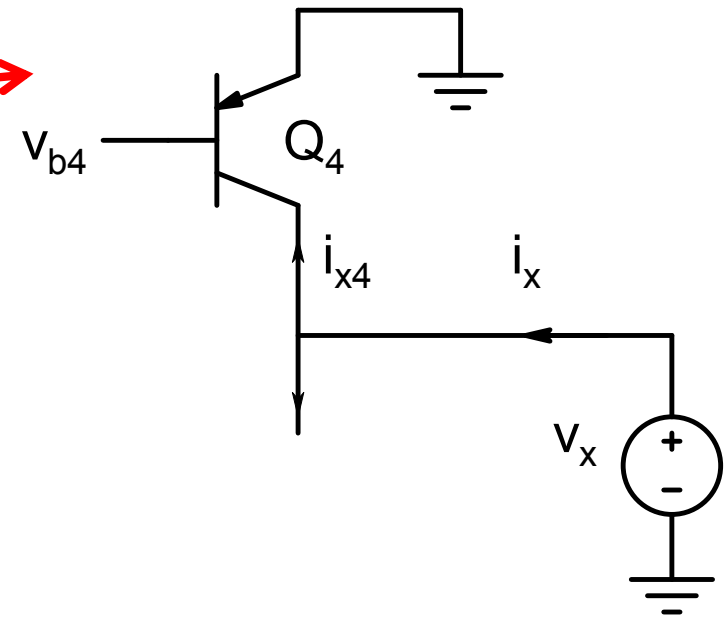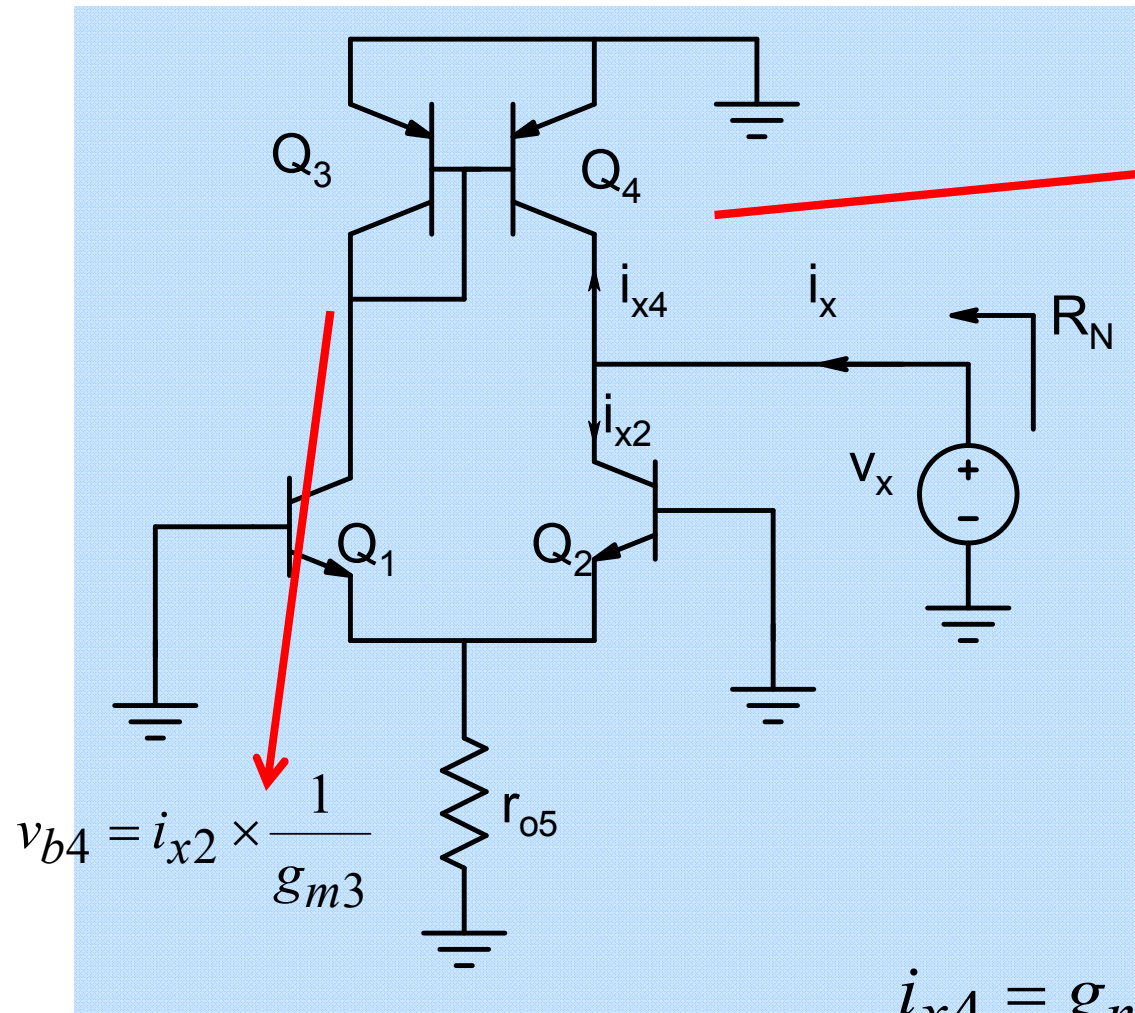

$$i_{x4} = g_{m4} \times v_{b4} + \frac{v_x}{r_{o4}}$$
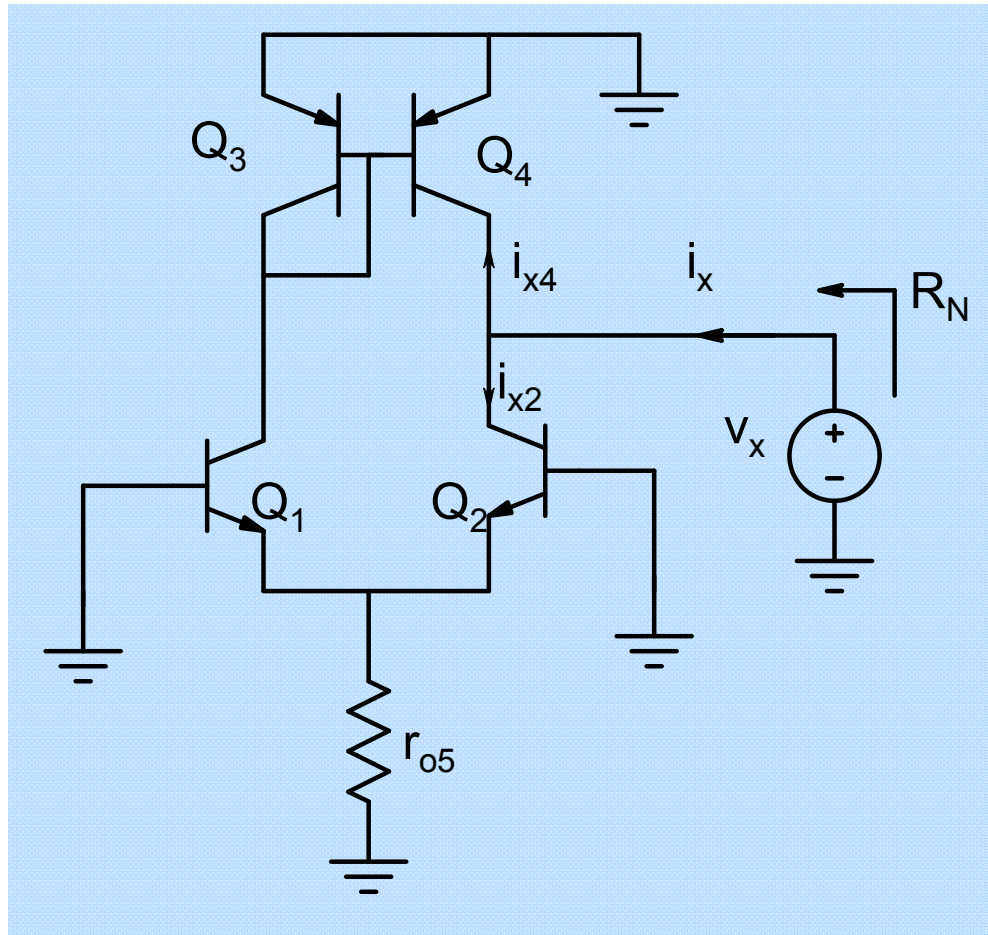
$$= g_{m4} \times i_{x2} \times \frac{1}{g_{m3}} + \frac{v_x}{r_{o4}} = i_{x2} + \frac{v_x}{r_{o4}}$$




$$i_{x2} = \frac{v_x}{2r_{o2}}$$

$$i_{x4} = i_{x2} + \frac{v_x}{r_{o4}}$$

$$\frac{1}{R_N} = \frac{i_x}{v_x} = \frac{i_{x2}}{v_x} + \frac{i_{x4}}{v_x} = \frac{1}{r_{o2}} + \frac{1}{r_{o4}}$$

Differential Mode Analysis


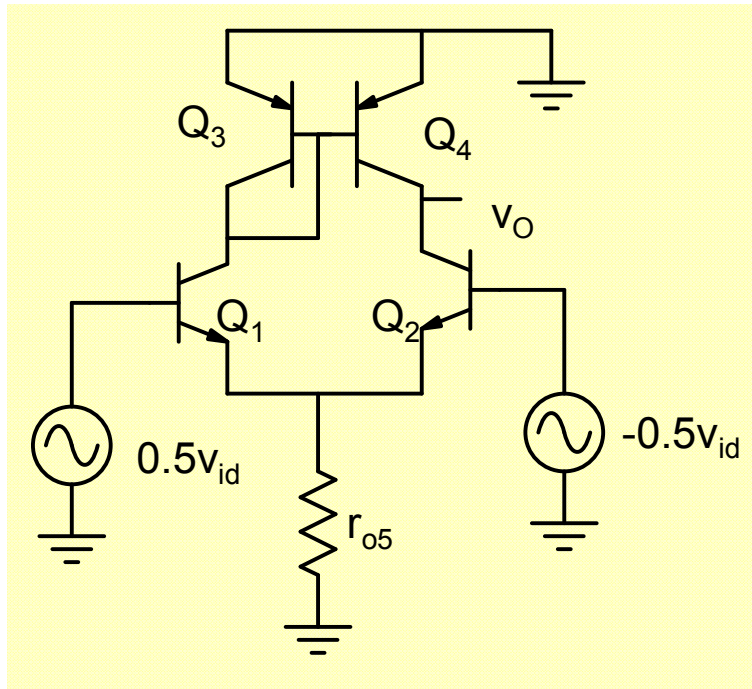


$$i_N = -g_m v_{id}$$

$$R_N = r_{o2} \parallel r_{o4}$$



$$A_{dm} = \frac{v_o}{v_{id}} = -\frac{i_N \times R_N}{v_{id}} = g_{m1} \times r_{o2} \parallel r_{o4}$$



$$R_O = r_{o2} \parallel r_{o4}$$

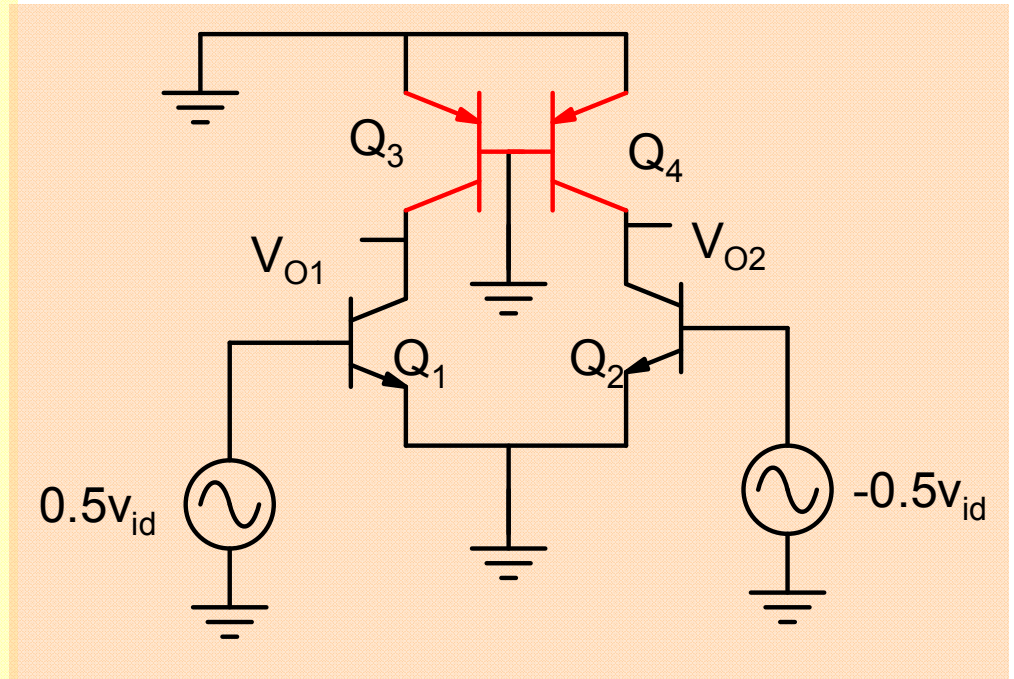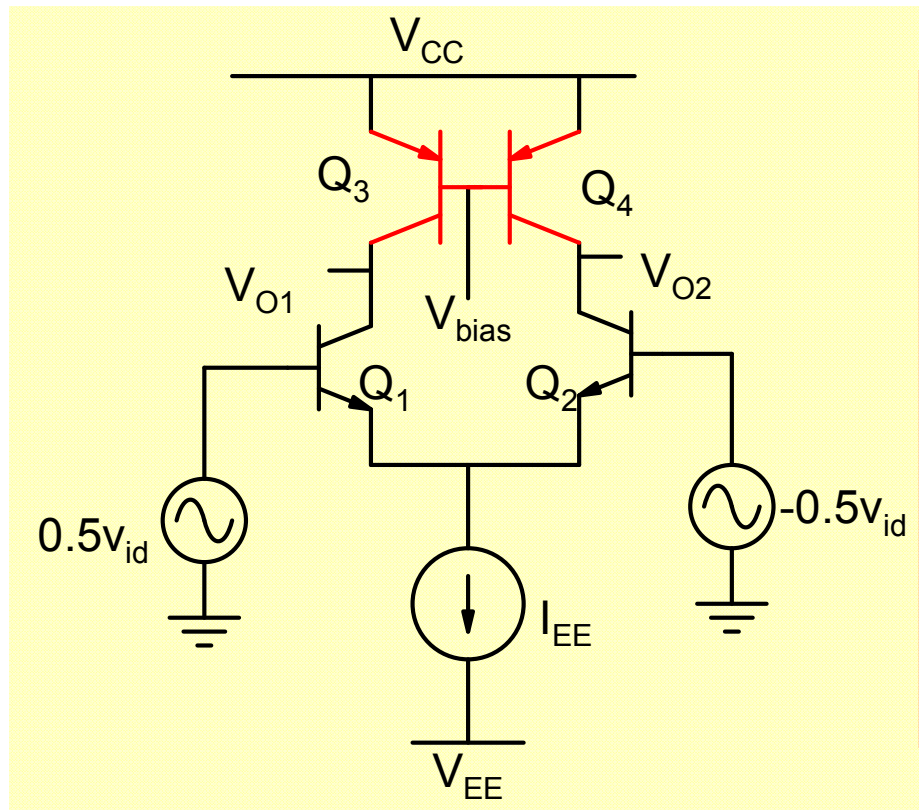

$$A_{dm} = \frac{v_{o2}}{v_{id}} = 0.5g_m \times r_{o2} \parallel r_{o4}$$


Common Mode Analysis

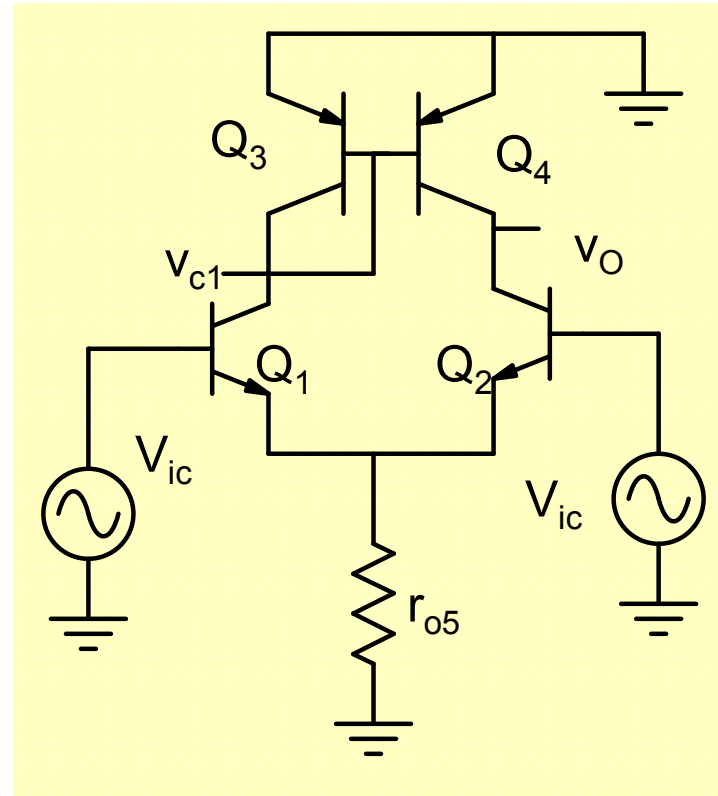
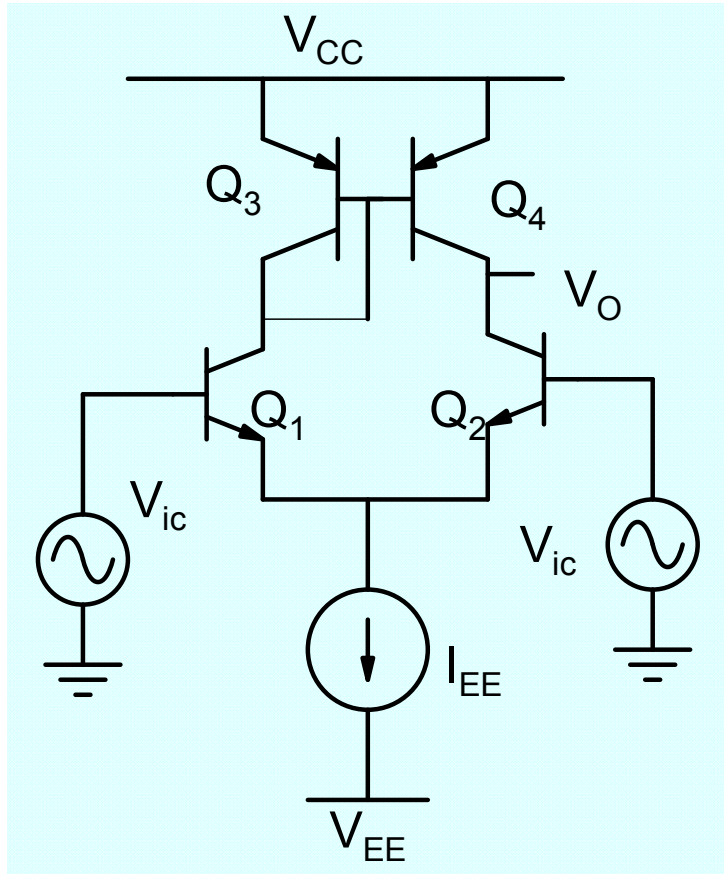


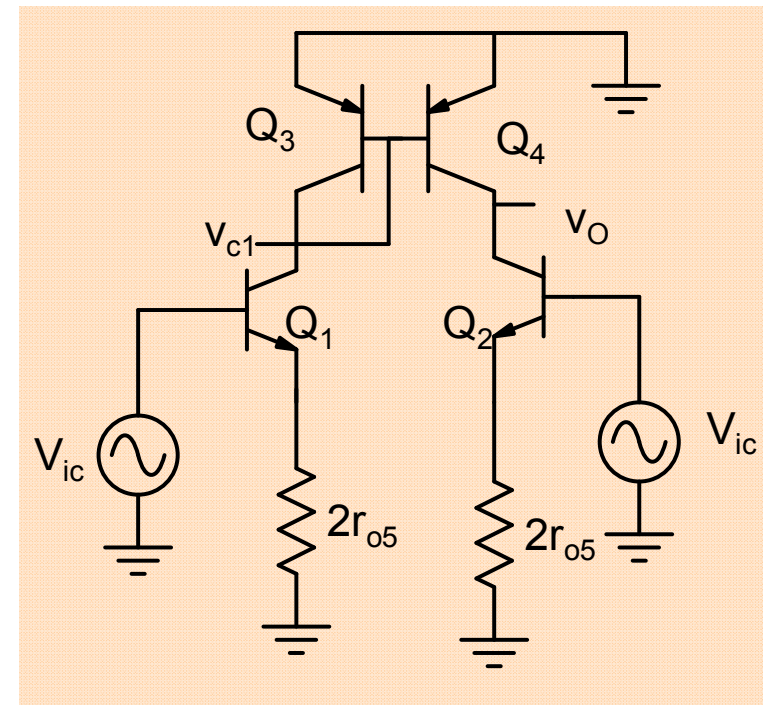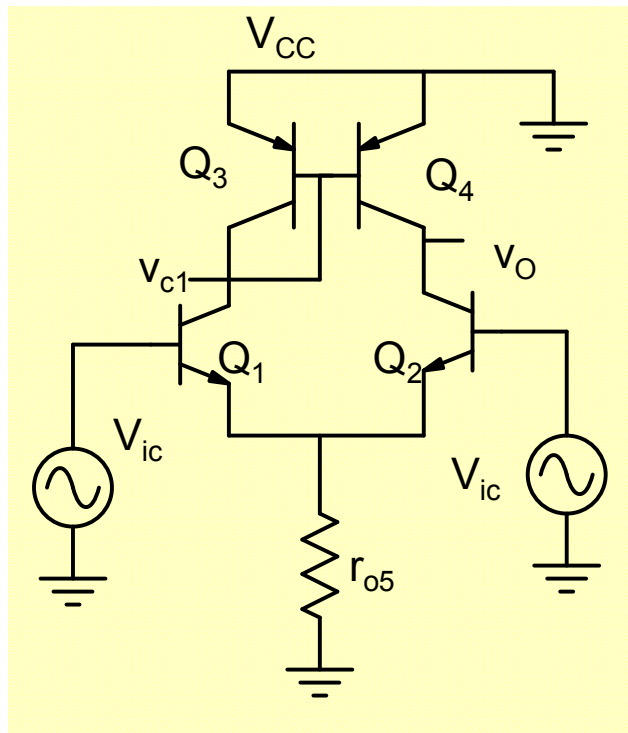


$$\frac{v_{c1}}{v_{ic}} = - \frac{g_{m1} \times \frac{1}{g_{m3}}}{1 + 2g_{m1}r_{o5}}$$

$$\cong - \frac{1}{2g_{m1}r_{o5}}$$

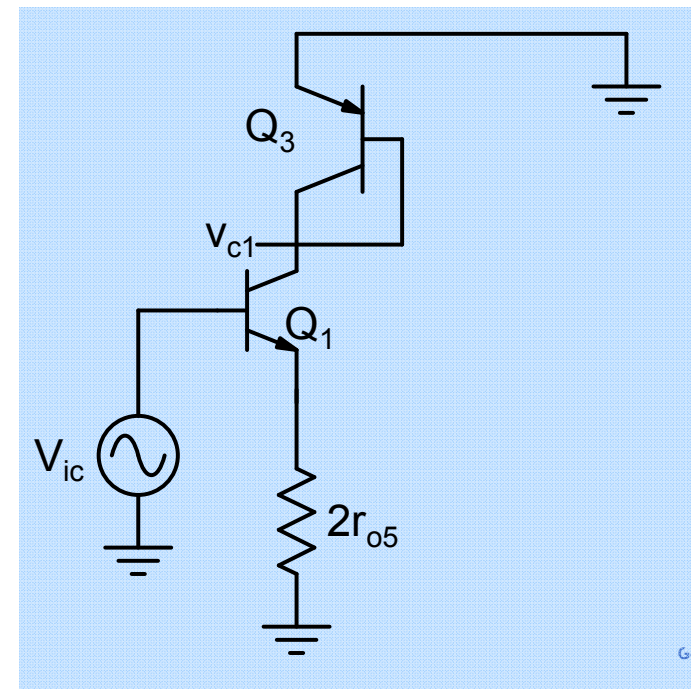


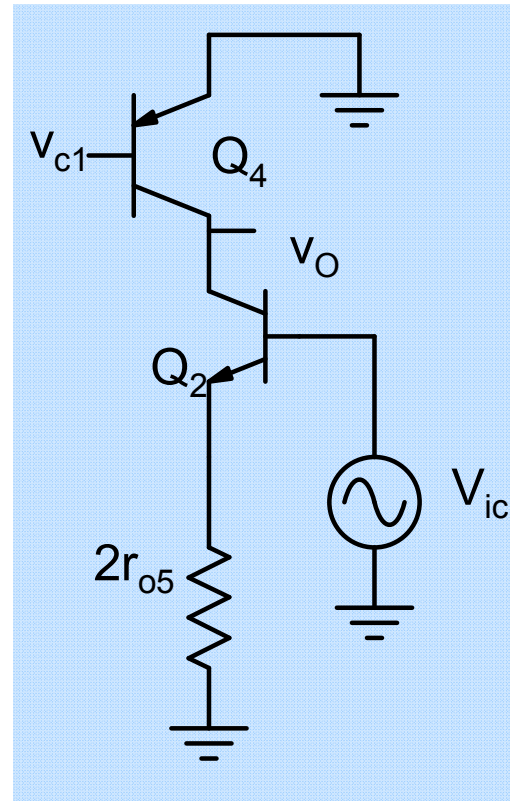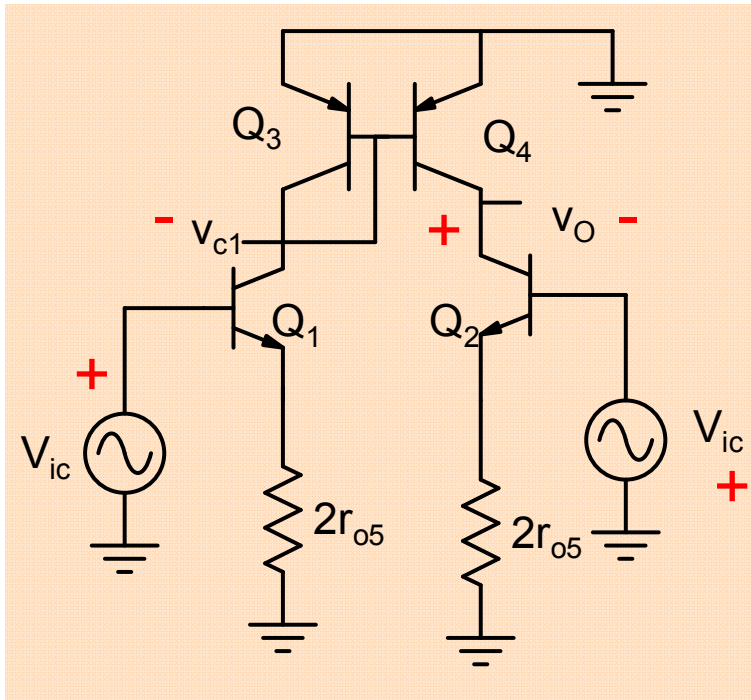

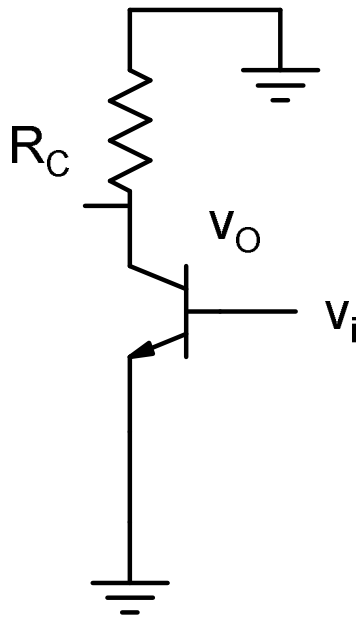
$$v_{c1} \cong -\frac{v_{ic}}{2g_{m1}r_{O5}}$$





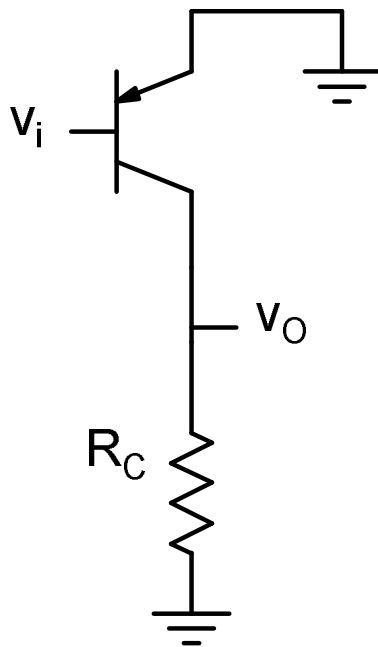
$$\frac{v_o}{v_i} = -g_m \times R_C \parallel r_o$$


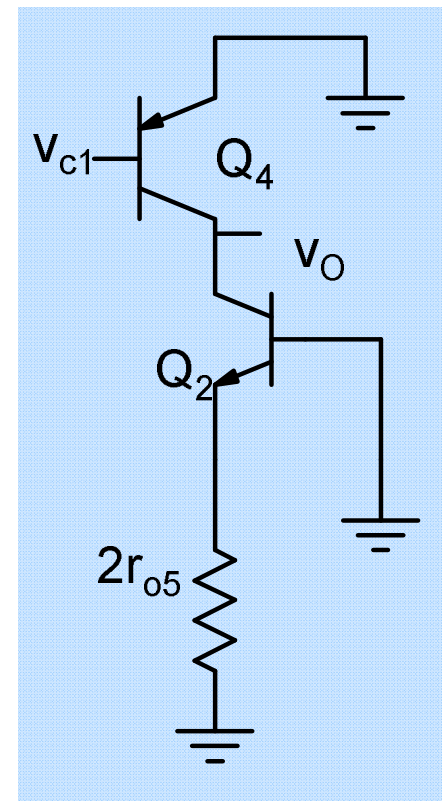
$$\frac{v_o}{v_i} = -g_m \times R_C \parallel r_o$$


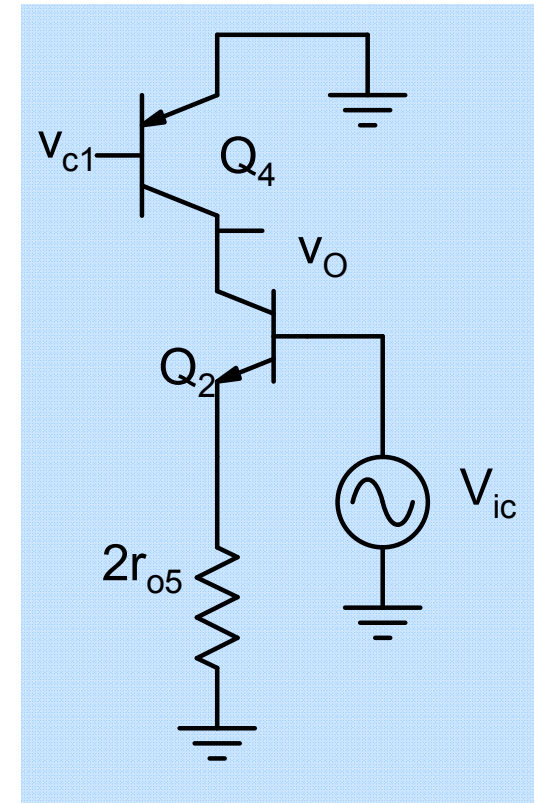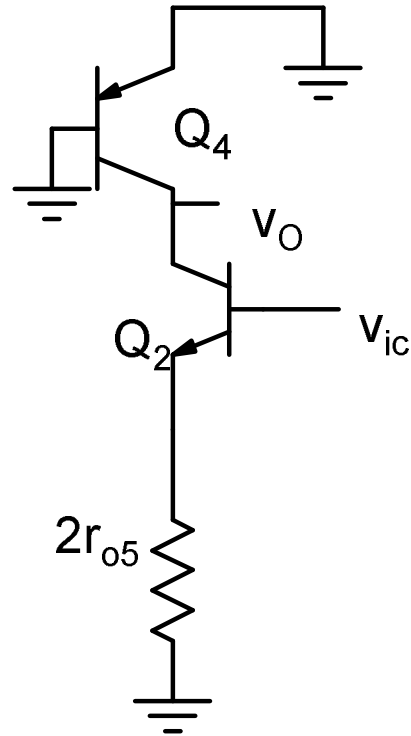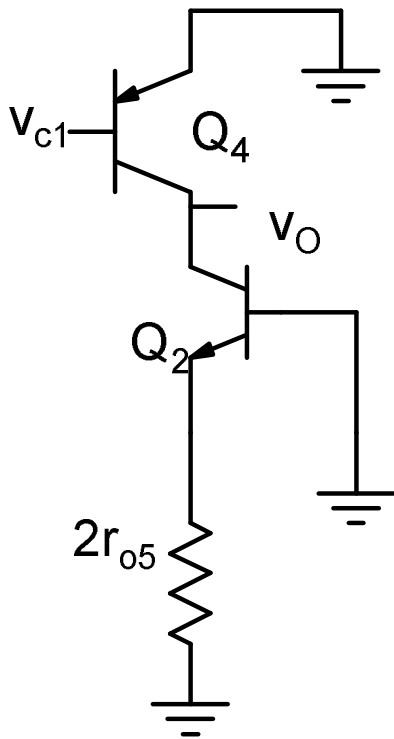
$$\begin{aligned} \frac{v_o}{v_{c1}} &= -g_{m4} \times r_{o4} \parallel r_{down} \\ &\cong -g_{m4} \times r_{o4} \end{aligned}$$





$$\frac{v_o}{v_{c1}} = -g_{m4} \times r_{o4} \parallel r_{down}$$

$$\cong -g_{m4} \times r_{o4}$$

$$\frac{v_o}{v_{ic}} = -\frac{g_{m2}}{1 + g_{m2} \times 2r_{o5}} \times r_{o4} \parallel r_{down}$$

$$\cong -\frac{r_{o4}}{2r_{o5}}$$

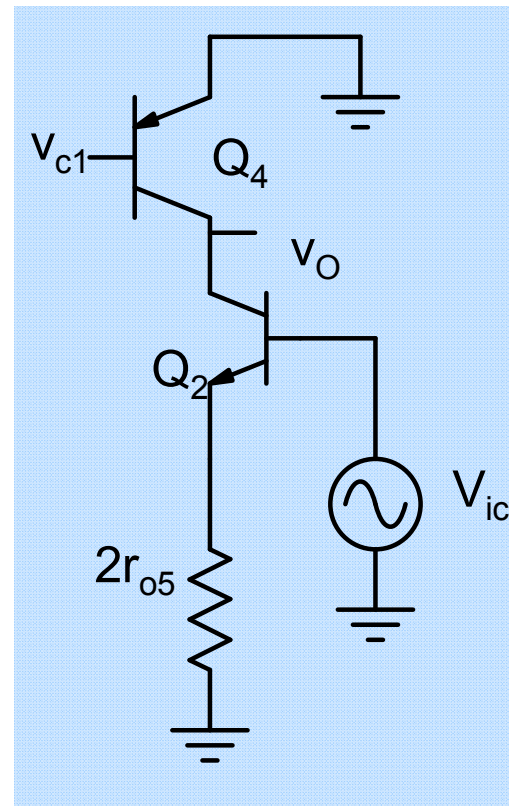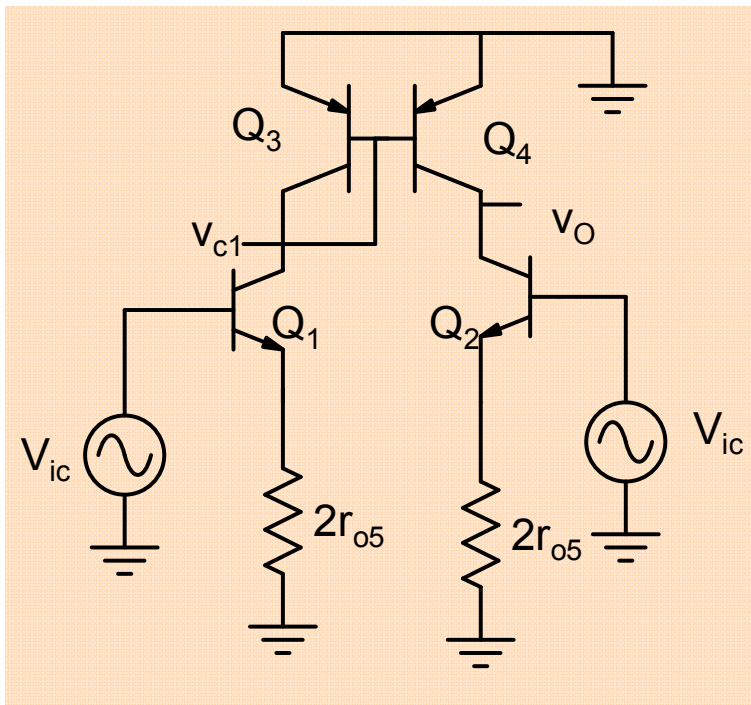


$$v_{c1} \cong -\frac{v_{ic}}{2g_{m1}r_{O5}}$$

$$v_o \cong -v_{ic} \times \frac{r_{o4}}{2r_{o5}} - v_{c1} \times g_{m4} \times r_{o4}$$

$$\cong -v_{ic} \times \frac{r_{o4}}{2r_{o5}} + v_{c1} \times g_{m4} \times \frac{r_{o4}}{2r_{o5}} = 0$$

More accurate calculations are needed but common mode gain is expected to be quite small


Example

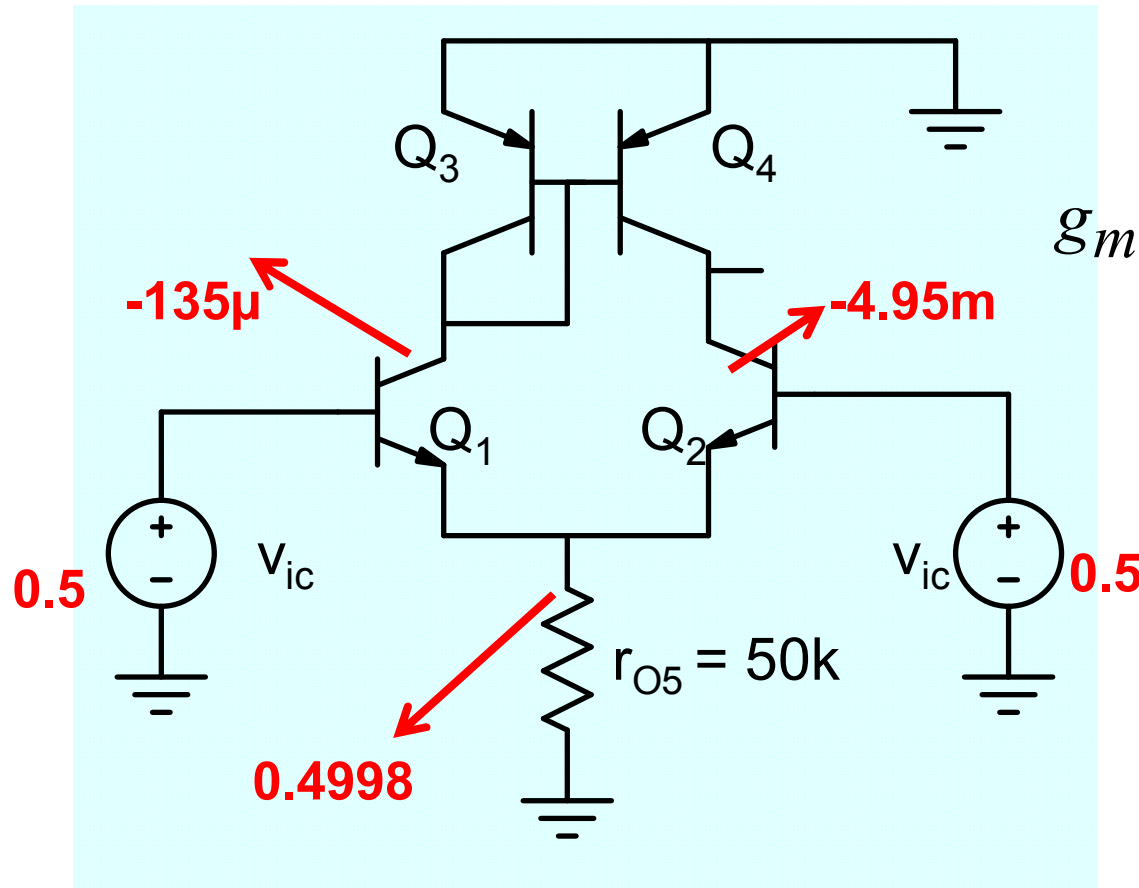


$$g_m = 38.5m\Omega^{-1}; r_o = 100k\Omega$$

$$A_{cm} = .01$$
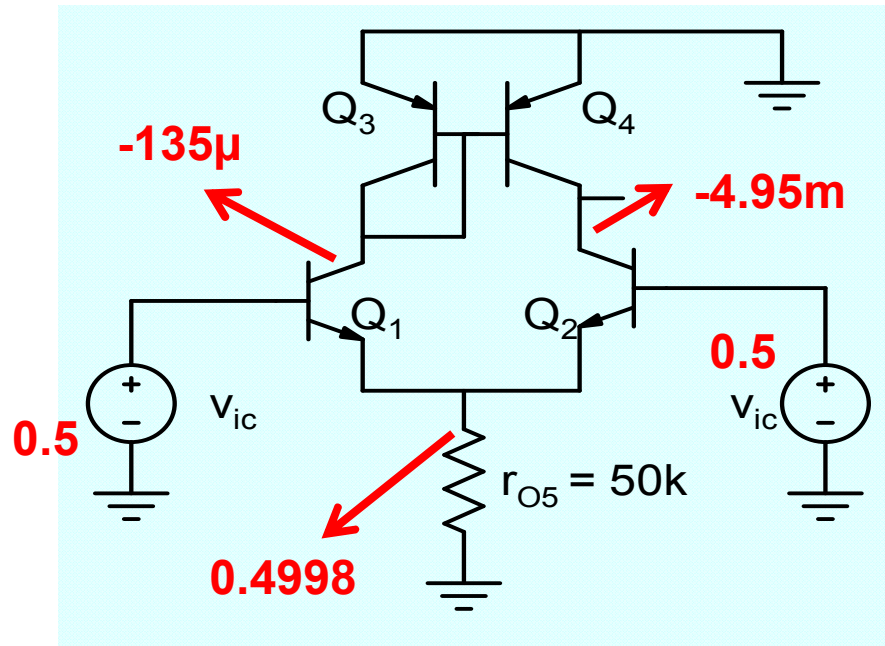
$$v_{c1} \cong -\frac{v_{ic}}{2g_{m1}r_{O5}} = -0.13mV$$




$$A_{cm} = .01$$

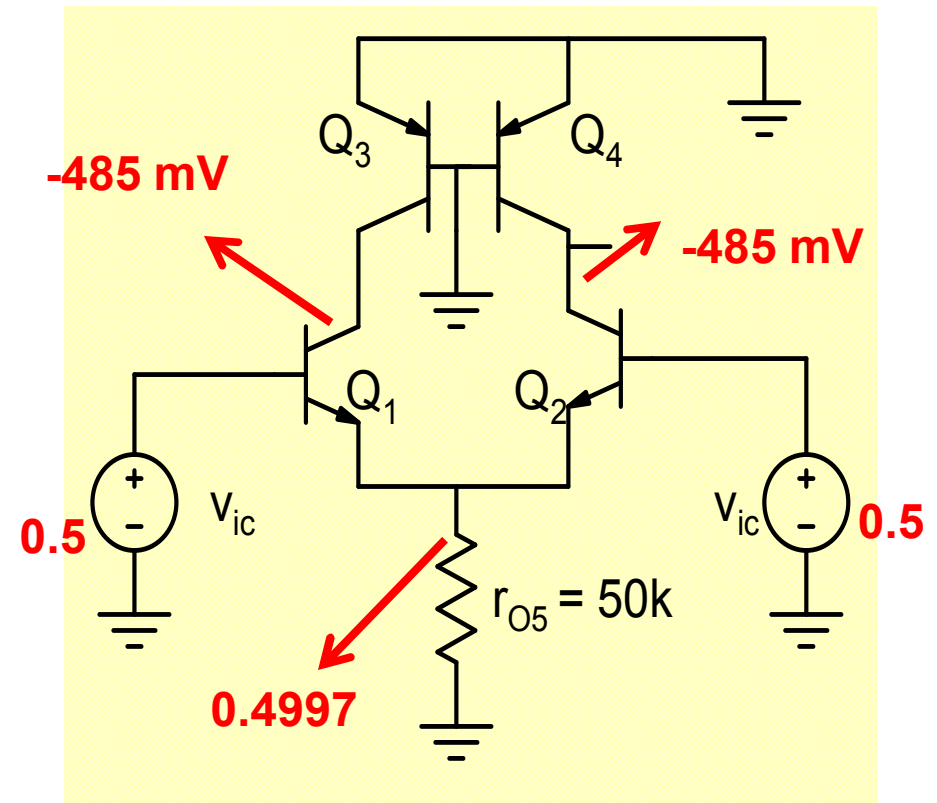

$$A_{cm} \sim 1$$

Common Mode gain is much higher !

Summary

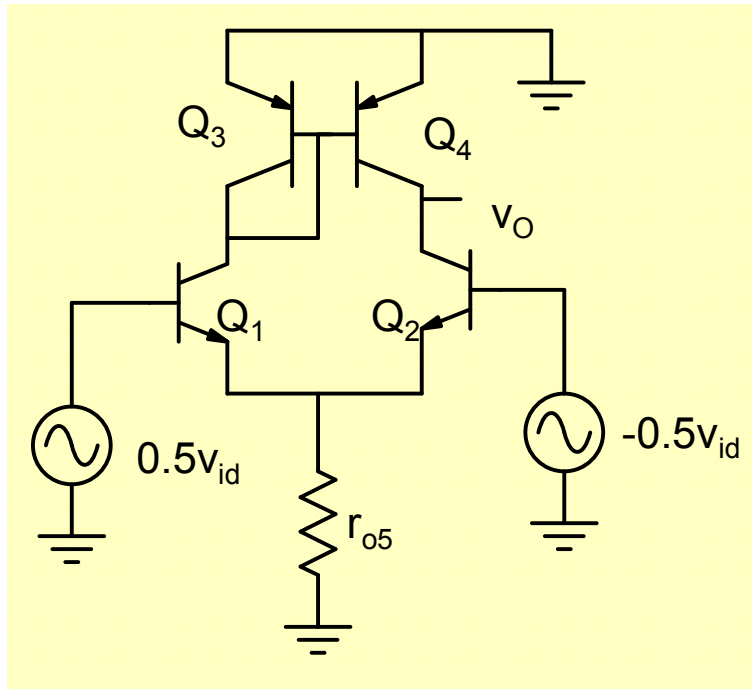

$$i_N = -g_m v_{id}$$

$$R_N = r_{o2} \parallel r_{o4}$$


$$A_{dm} = \frac{v_o}{v_{id}} = -i_N \times R_N = g_{m1} \times r_{o2} \parallel r_{o4}$$

$$R_O = r_{o2} \parallel r_{o4}$$

$$A_{cm} =$$

$$cmrr =$$

Example

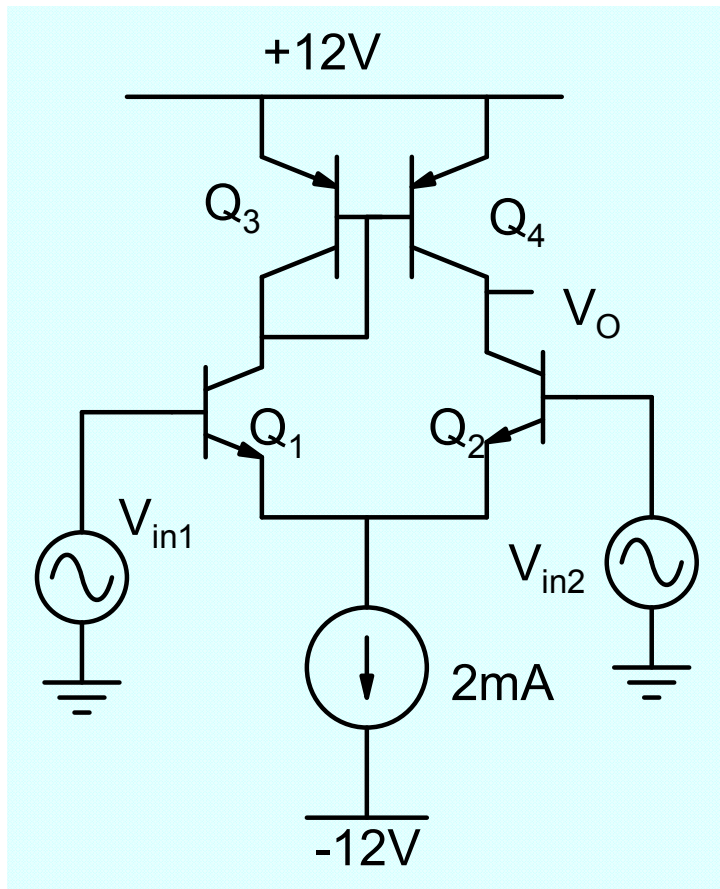

Bias Point

$$I_{EE} = 2mA$$

$$I_{CQ1} = I_{CQ2} = 1mA$$

$$g_{m1} = 38.46mS ; r_{o2} = 100k\Omega$$

$$r_{o5} = 50k\Omega$$


$$A_{dm} = -1.9 \times 10^3 ; R_{id} = 5.2K\Omega$$

$$A_{cm} = -10^{-2} ; R_{ic} = 1.14M\Omega$$

$$CMRR = 1.9 \times 10^5 = 105.5dB$$

From simulation


The difference a single wire can make !

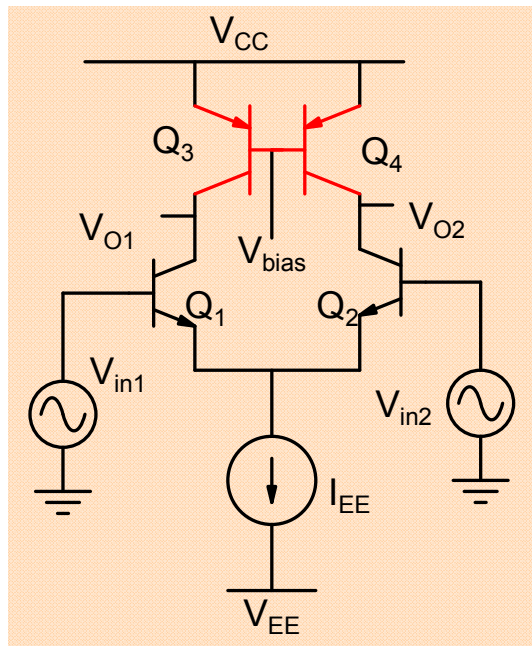

Additional bias source and sensitive Q-point

$$A_{dm} = 0.5g_{m1} \times r_{o2} \parallel r_{o4}$$

$$A_{cm} \cong -\frac{r_{o3}}{2r_{O5}}$$

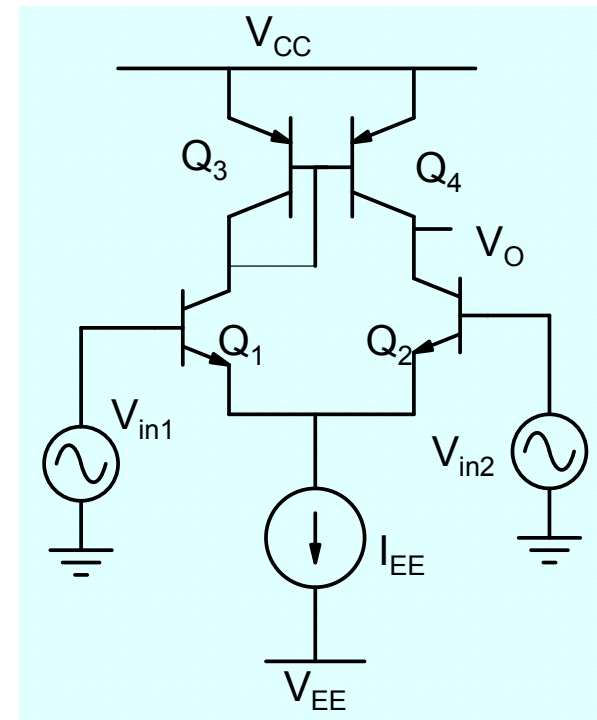


Stable bias point

$$A_{dm} = g_{m1} \times r_{o2} \parallel r_{o4}$$

$$A_{cm} \cong \text{much smaller}$$

General Large Signal Analysis

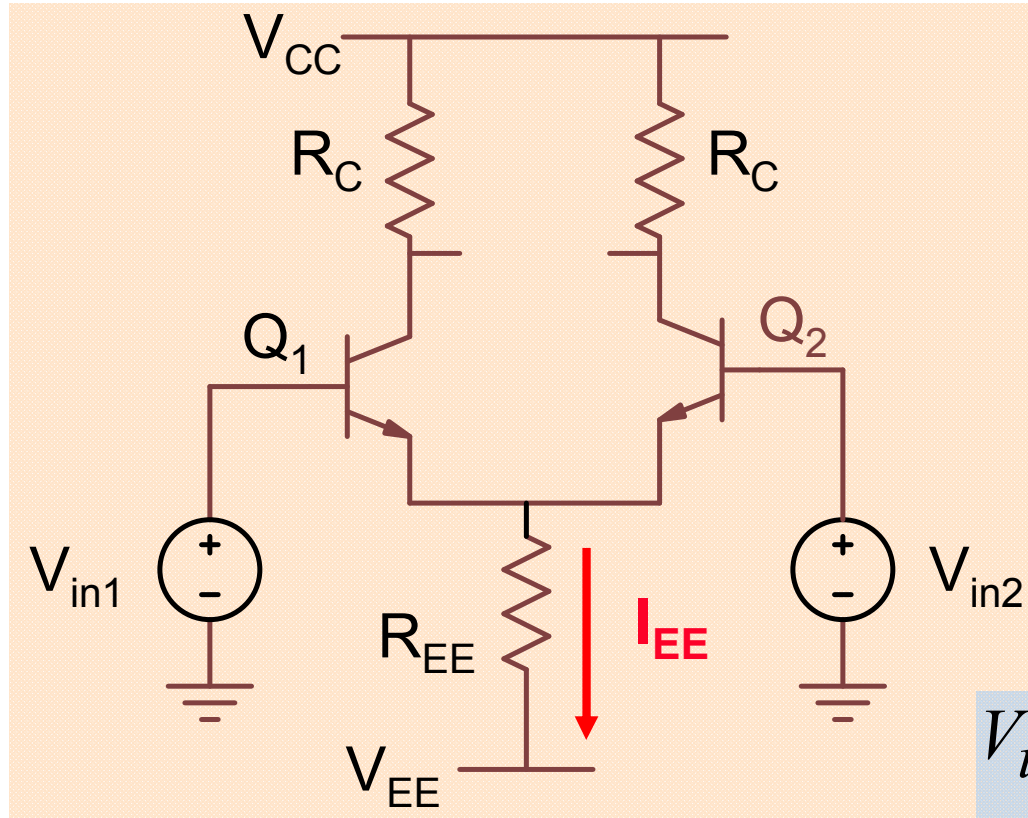

$$I_{EE} \cong I_{C1} + I_{C2}$$


$$I_{C1} = A \times J_S \times \exp\left(\frac{V_{BE1}}{V_T}\right)$$

$$I_{C2} = A \times J_S \times \exp\left(\frac{V_{BE2}}{V_T}\right)$$

$$V_{in1} - V_{BE1} - V_{EB2} - V_{in2} = 0$$


$$V_{BE1} - V_{BE2} = V_{in1} - V_{in2}$$
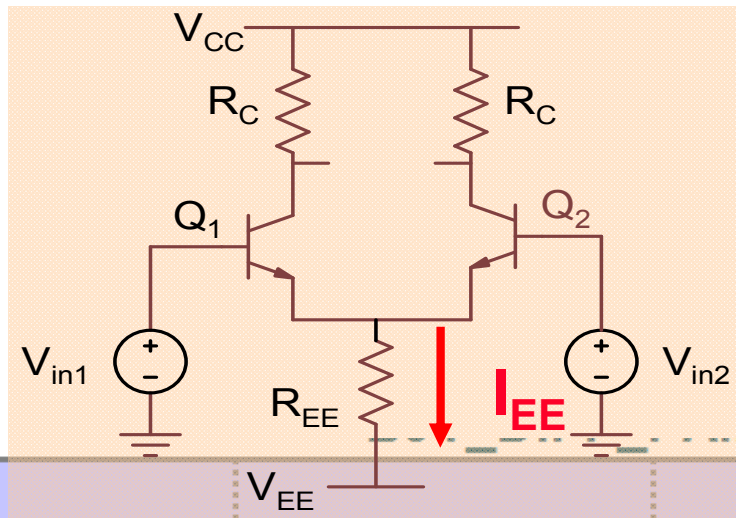
$$I_{C1} = I_{EE} \times \frac{\exp(V_{id}/V_T)}{1 + \exp(V_{id}/V_T)} ; I_{C2} = I_{EE} \times \frac{1}{1 + \exp(V_{id}/V_T)}$$




$$I_{C1} = I_{EE} \times \frac{\exp(V_{id}/V_T)}{1 + \exp(V_{id}/V_T)}$$

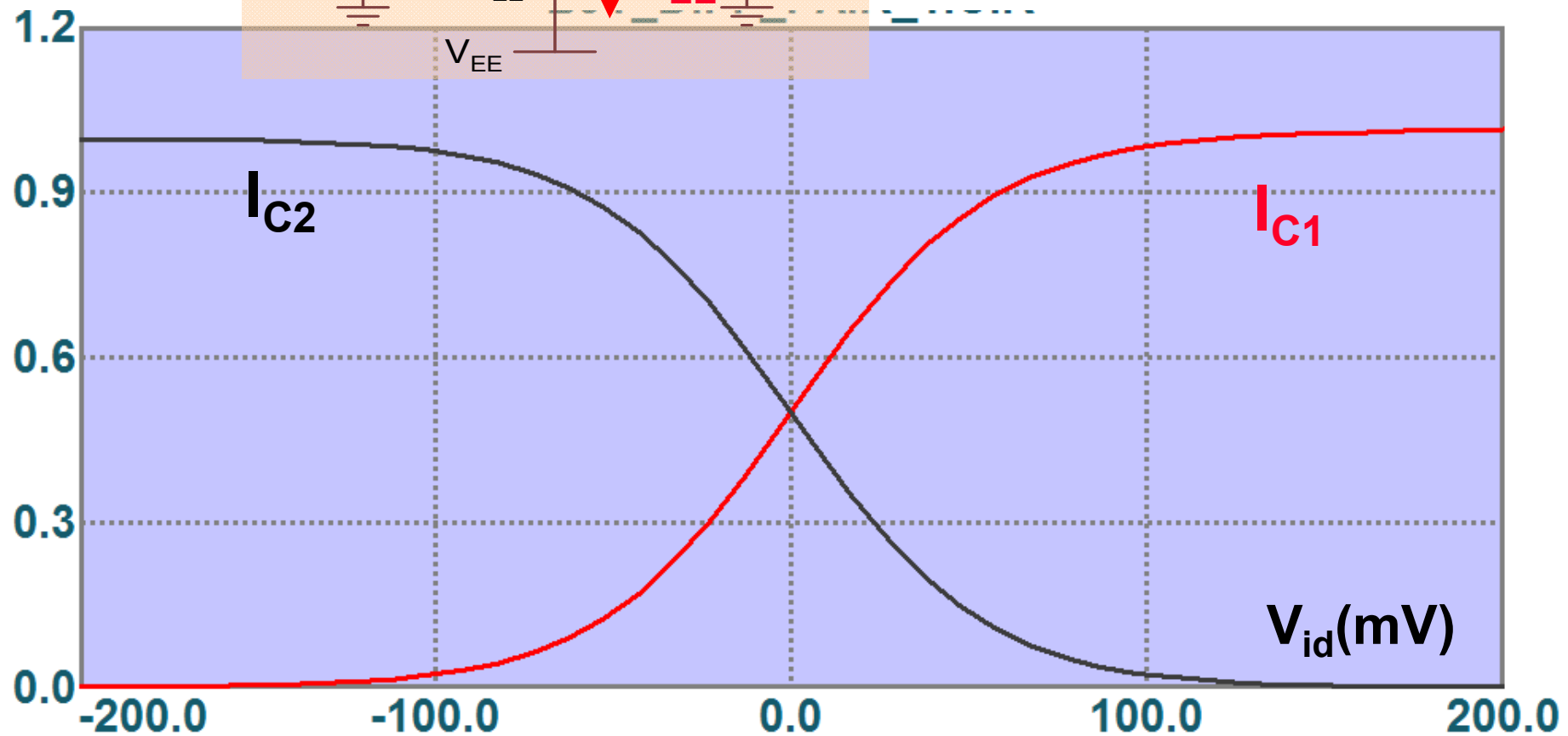
$$I_{C2} = I_{EE} \times \frac{1}{1 + \exp(V_{id}/V_T)}$$




Current I_{EE} switches between the two transistors


Current Switching

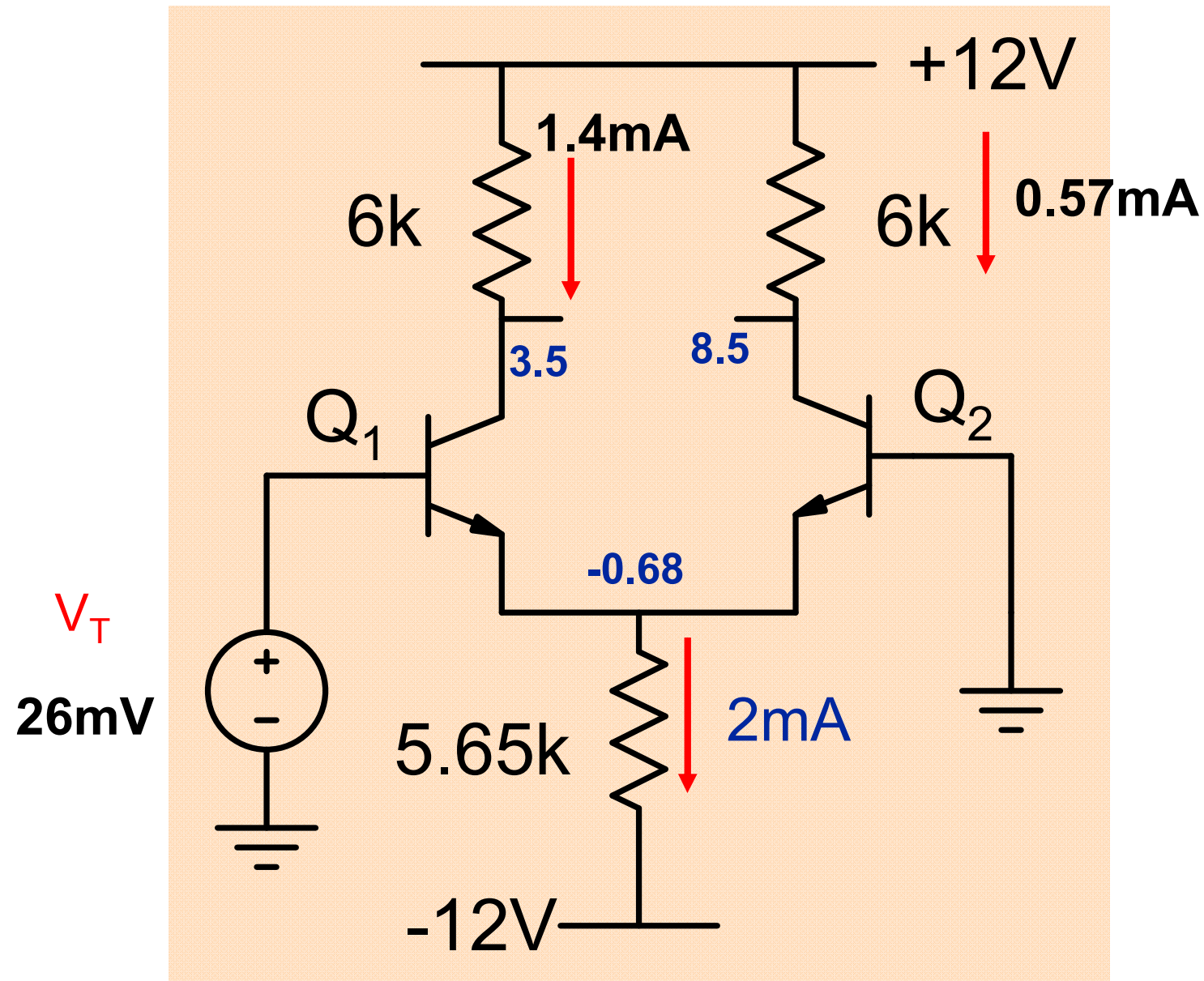


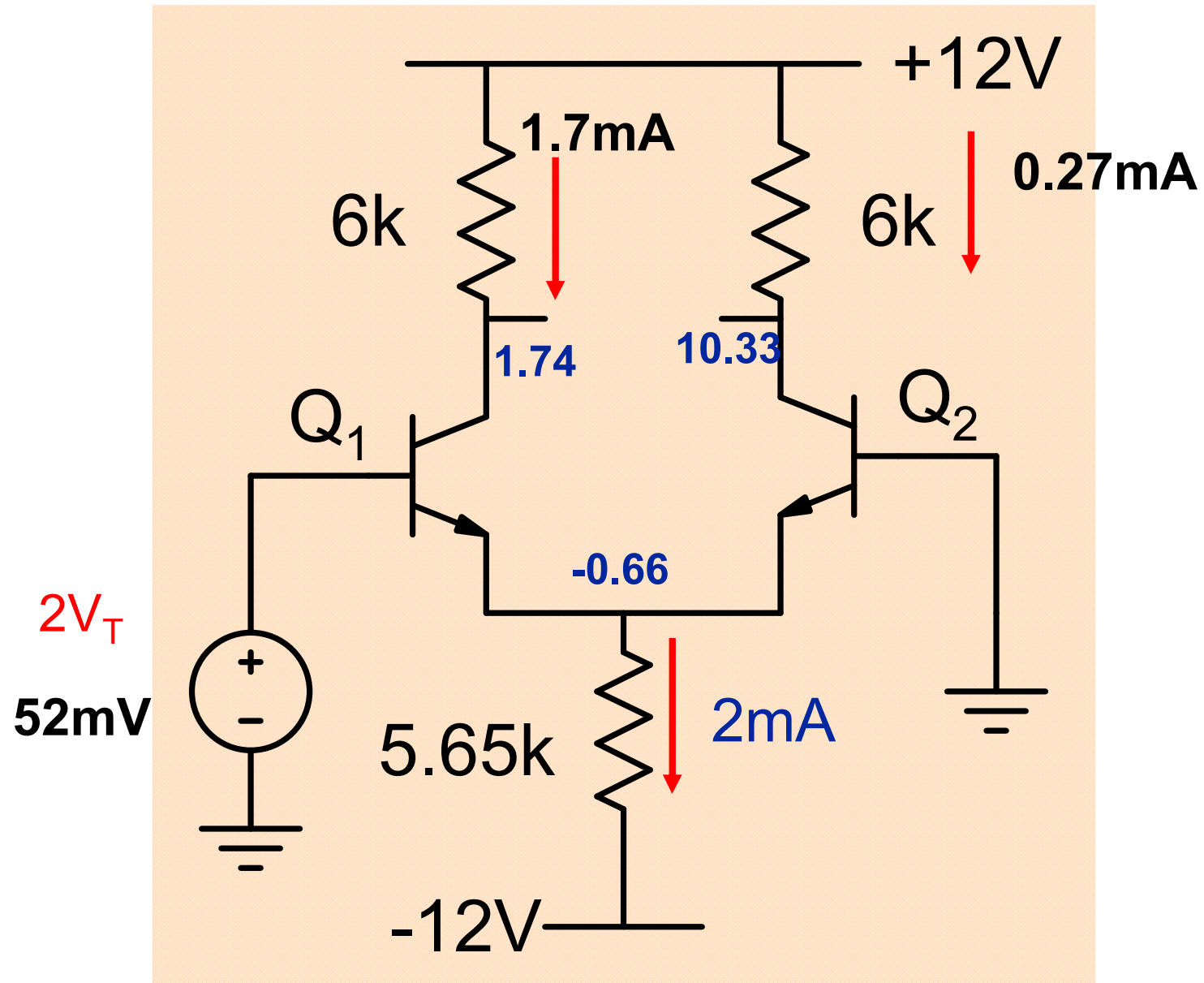

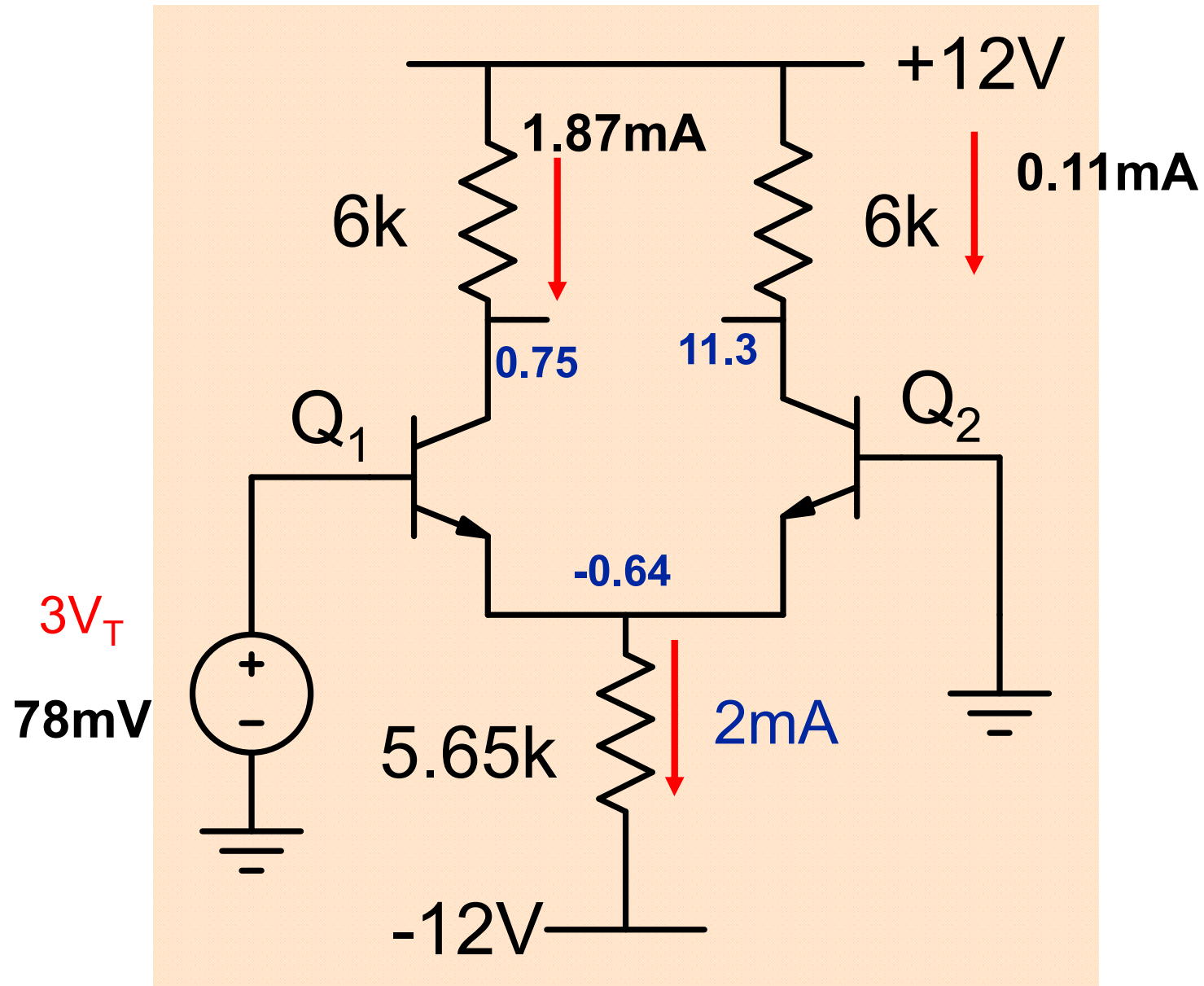


How low can the output go?

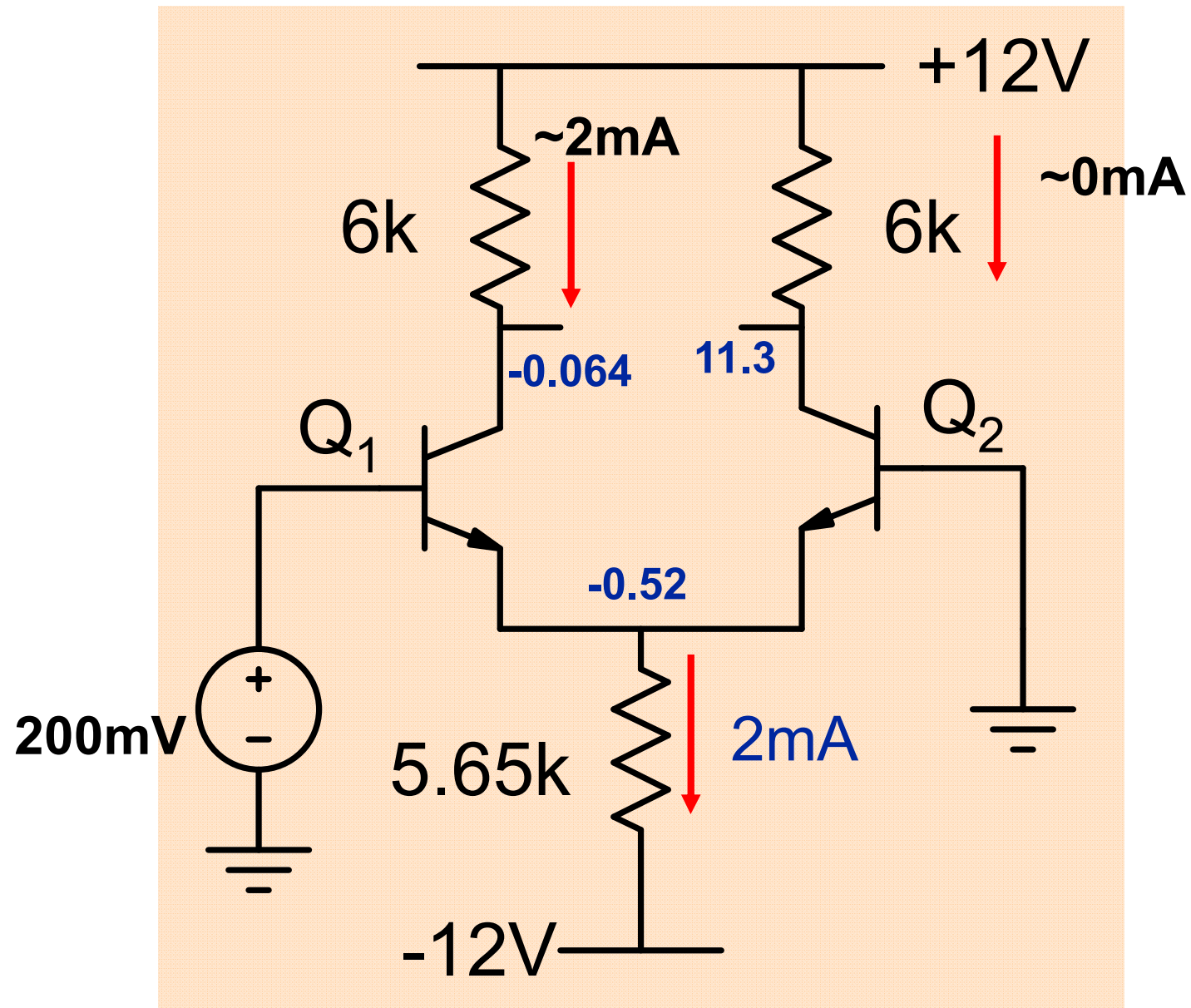

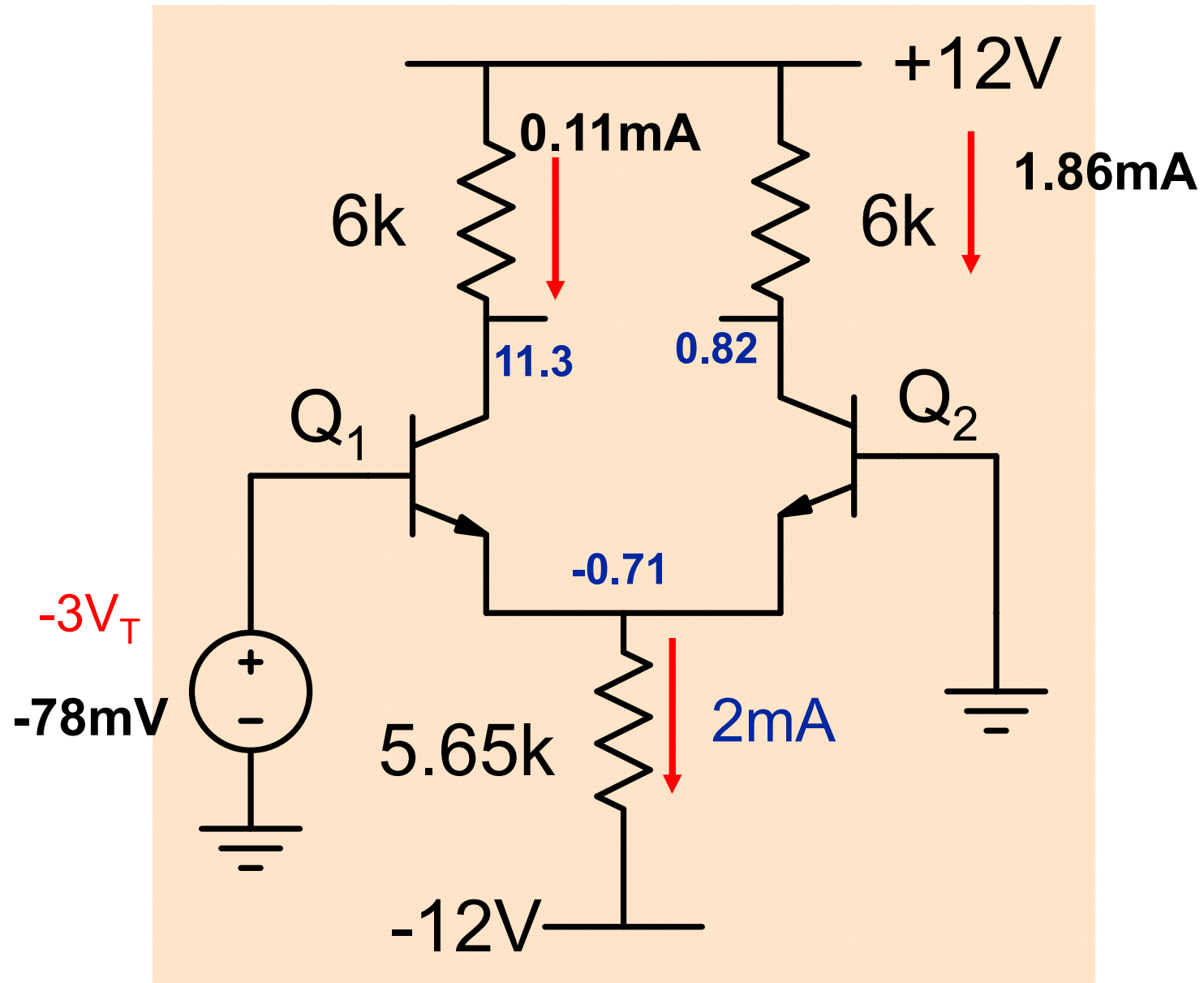


Single ended Output Voltage

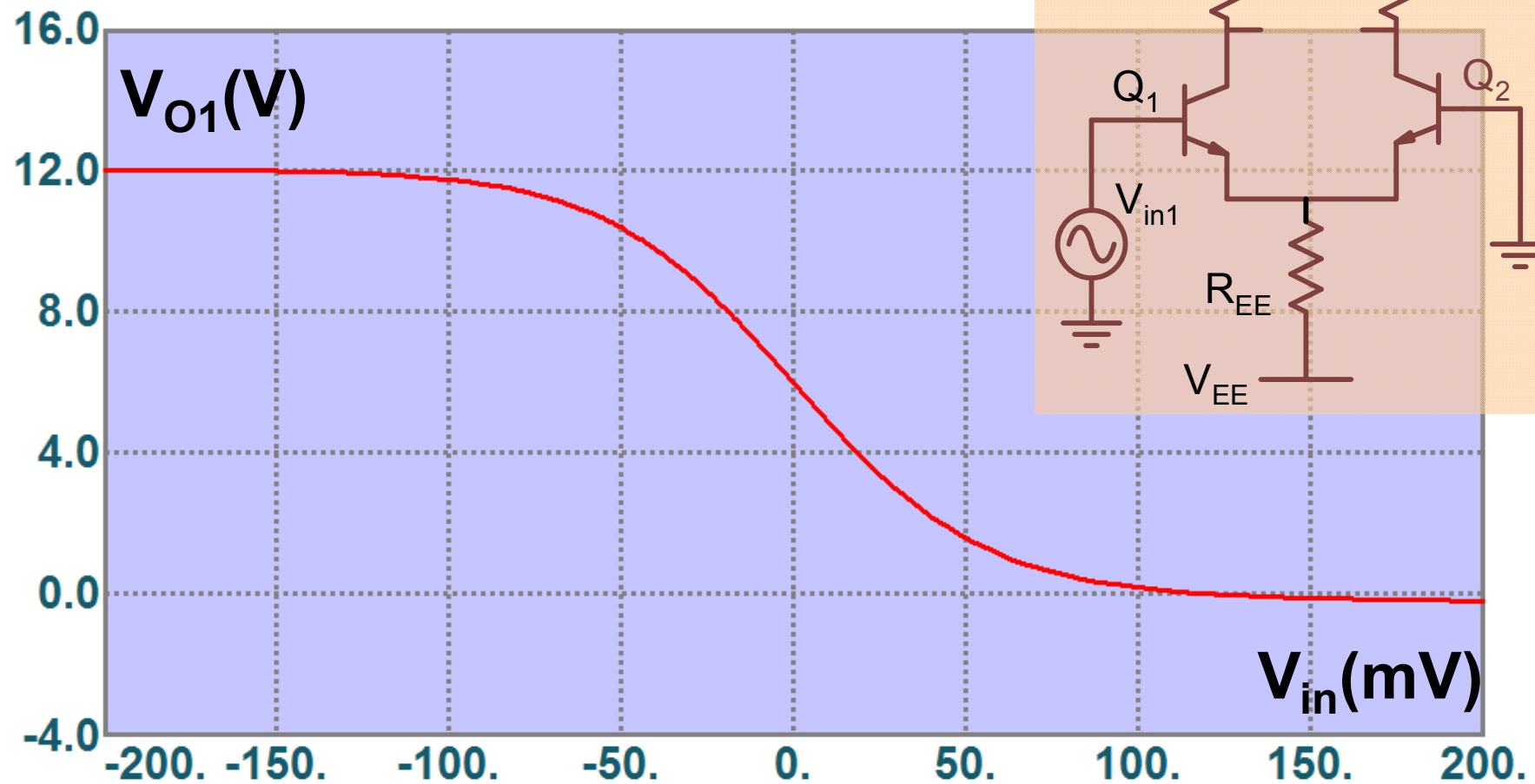


Poor Negative Swing

Negative Swing

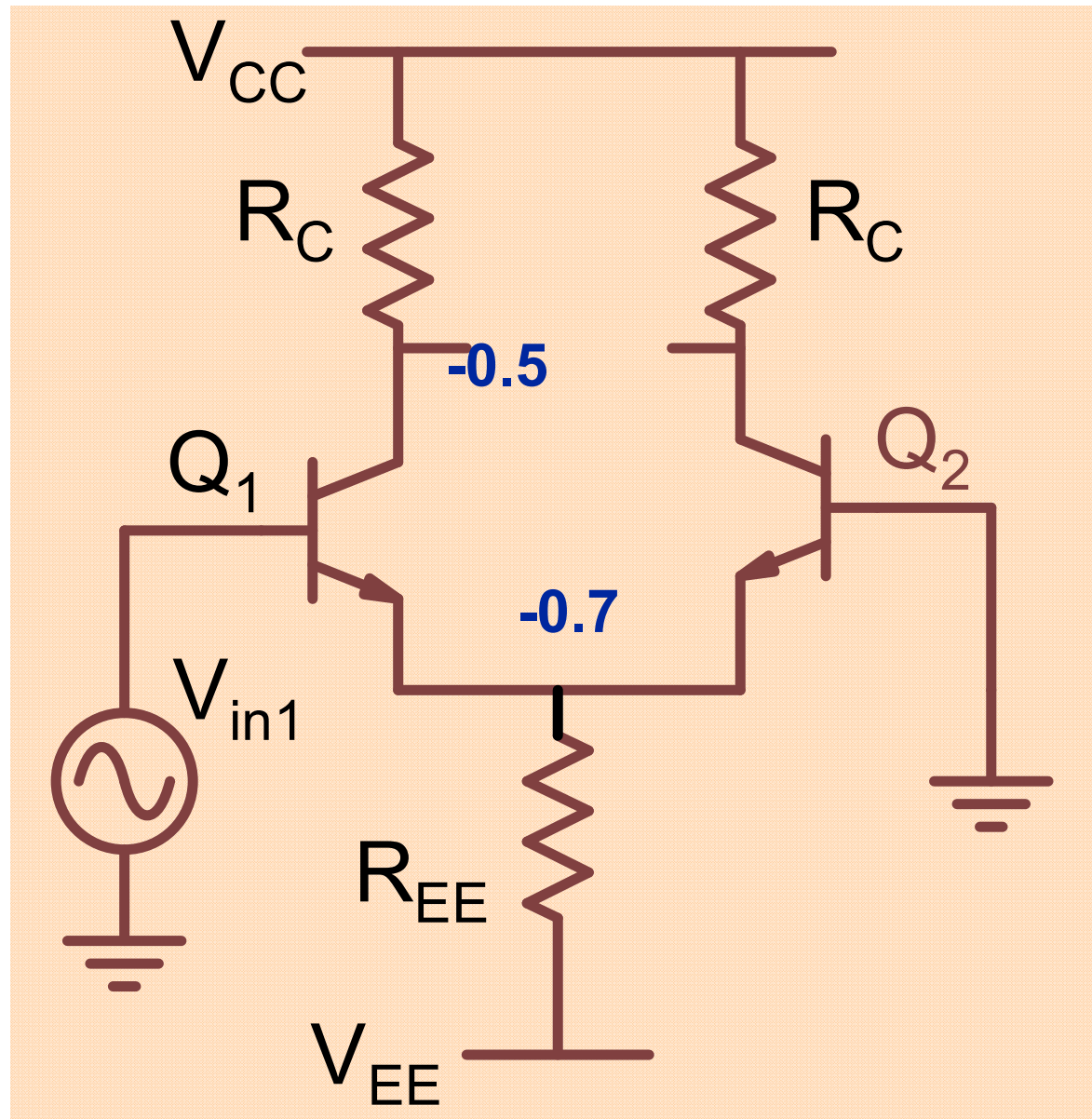

Differential Output Voltage

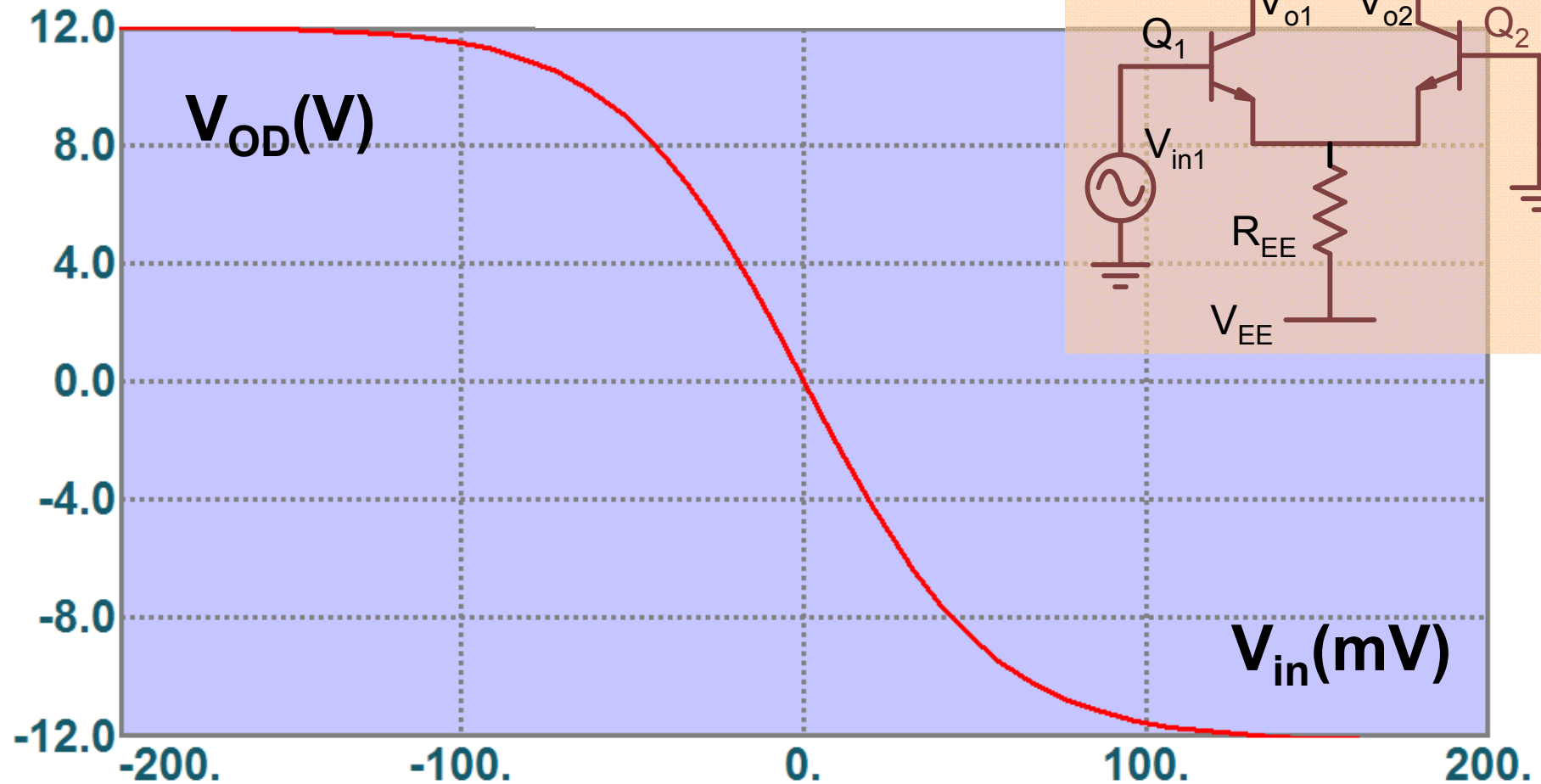

Swing is perfect !

