




EE210: Microelectronics-I

Lecture-25 :Common Collector Amplifier-1

Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur


Example

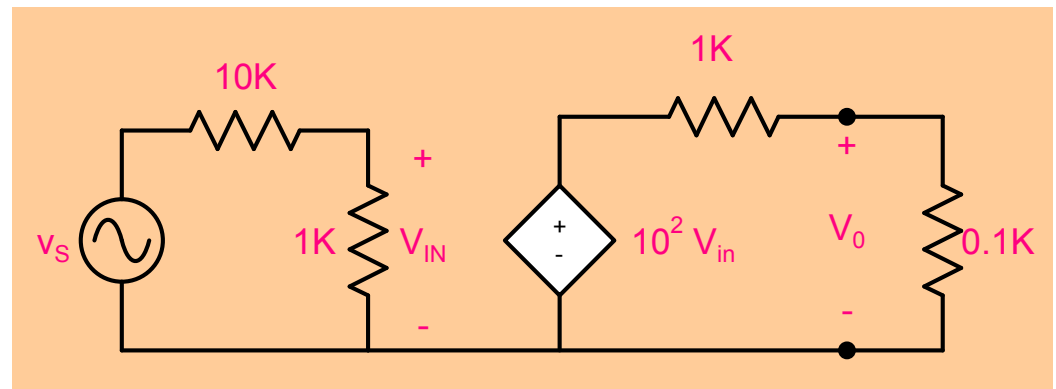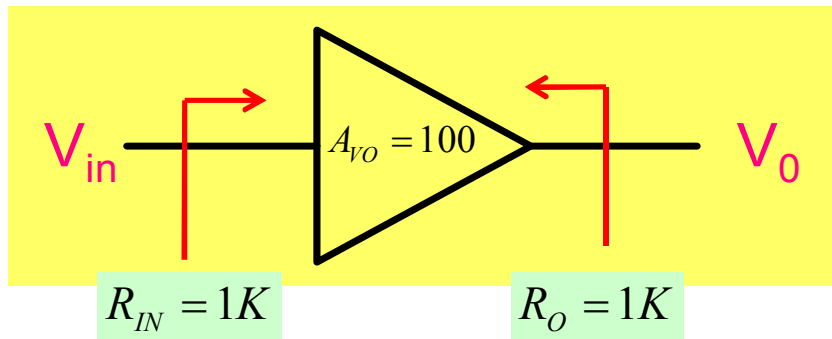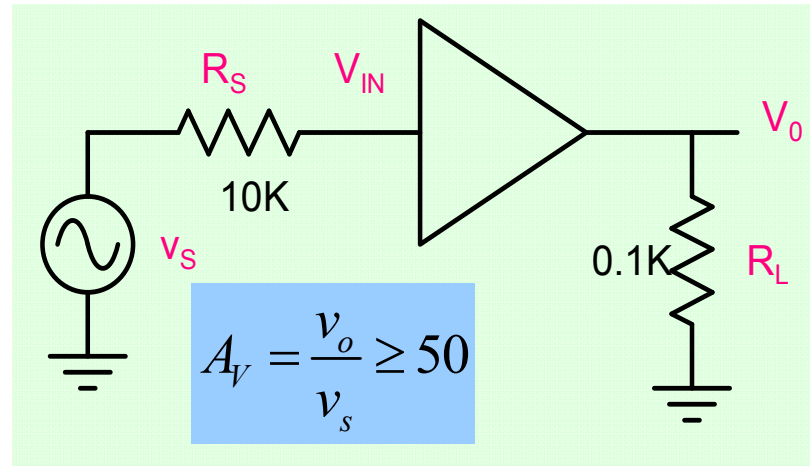

$$A_V = \frac{v_o}{v_s} = \left(\frac{R_{in}}{R_S + R_{in}} \right) \times A_{VO} \times \left(\frac{R_L}{R_O + R_L} \right) = 0.826$$


A CE amplifier by itself may not be sufficient for all applications

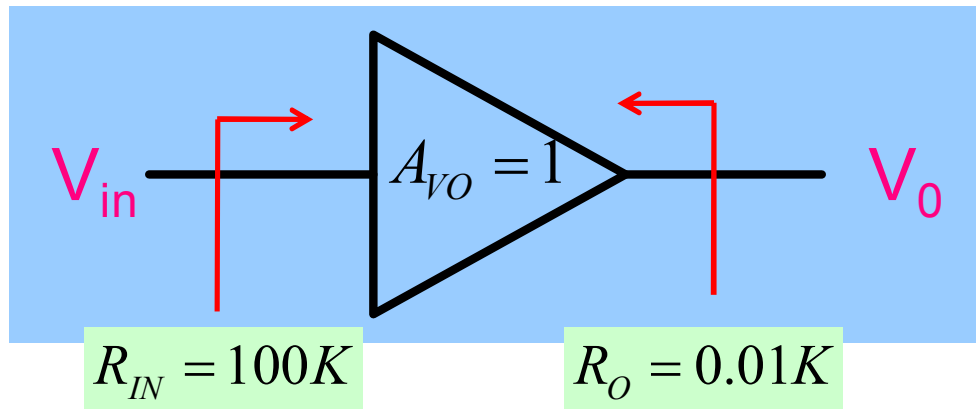Suppose we have a new amplifier stage with the following characteristics





High bandwidth
High swing & linearity



$$\frac{R_{in}}{R_O} = 10^4$$

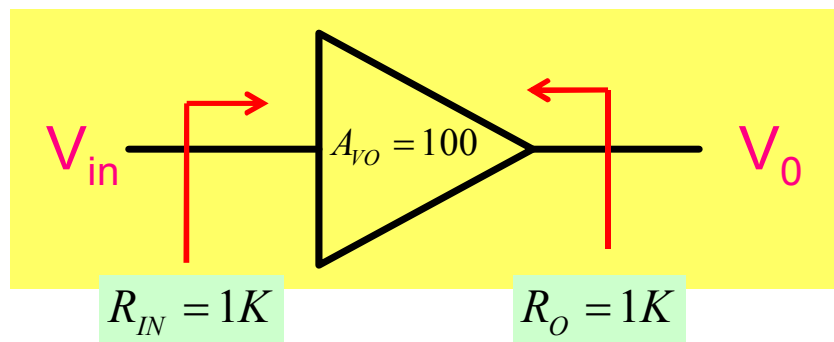

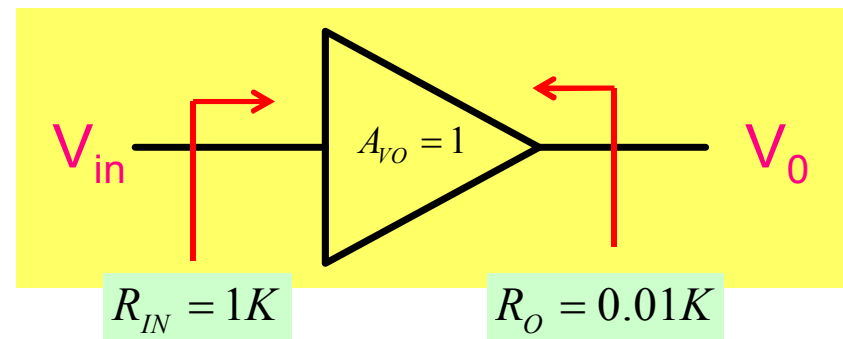
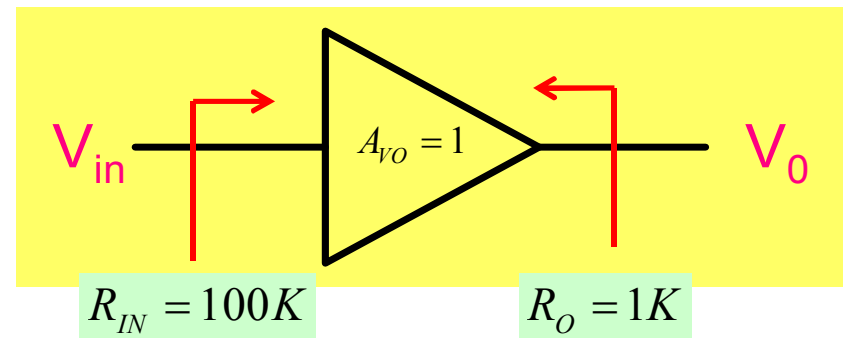
$$\frac{A_{vo} \times R_{in}}{R_O} = \beta = 100$$



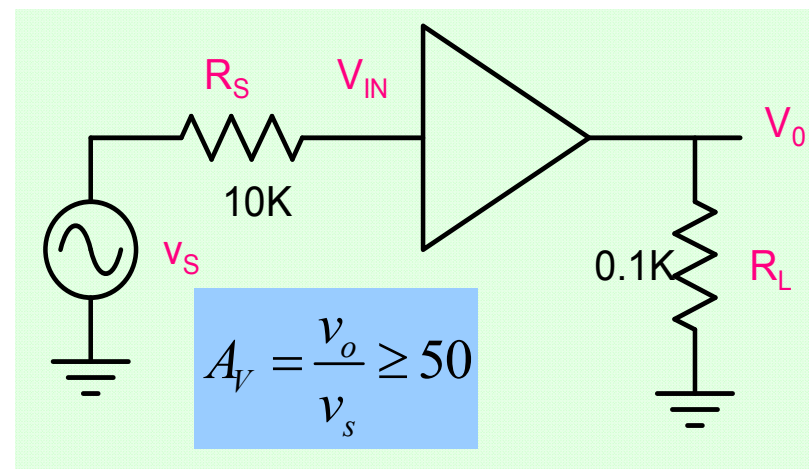
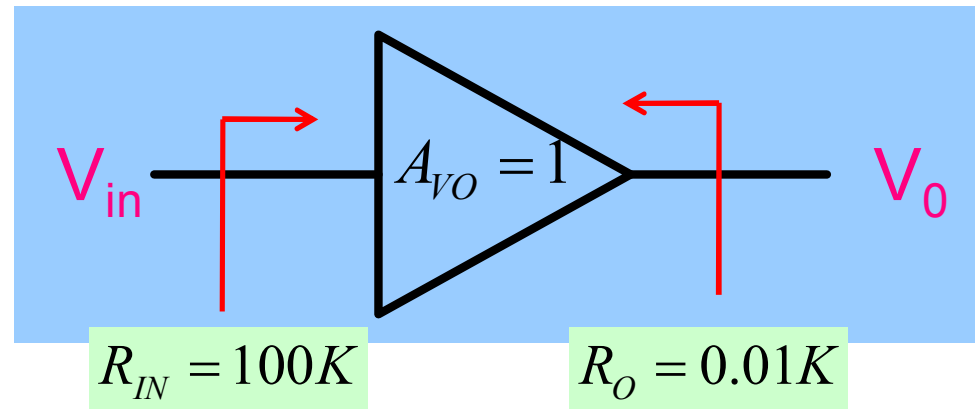
Can we use this amplifier for our application?



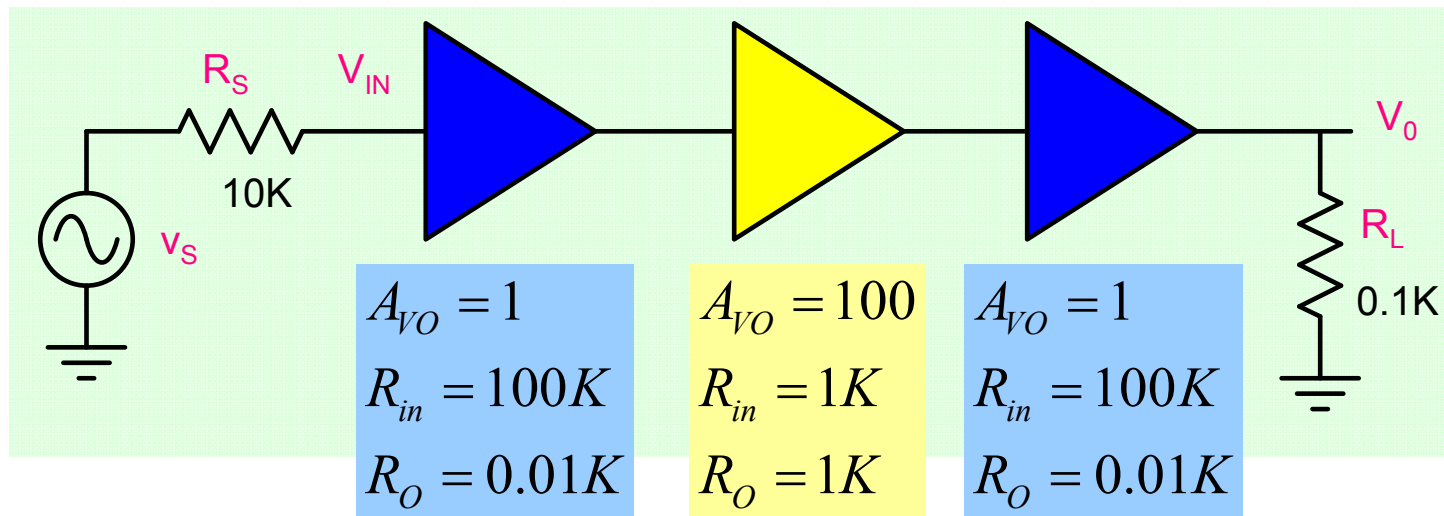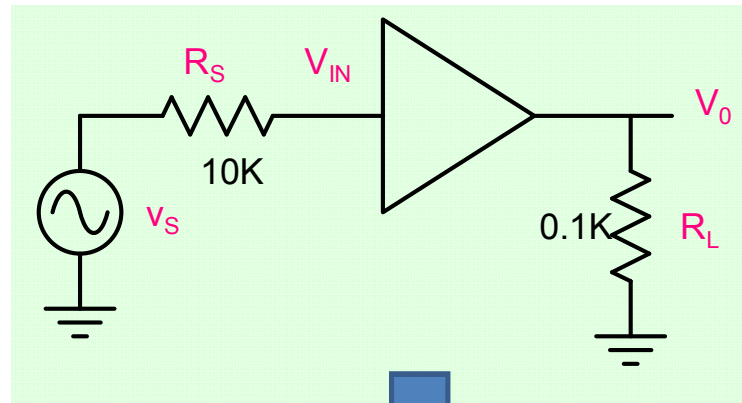
Not directly but in combination with the first amplifier


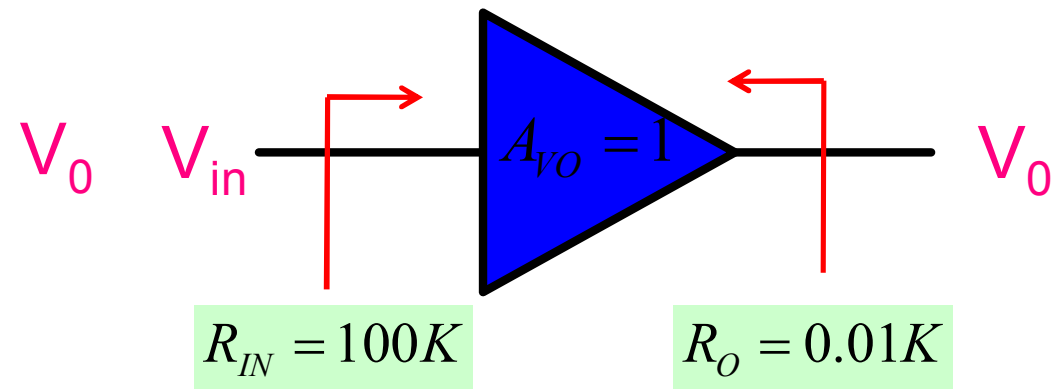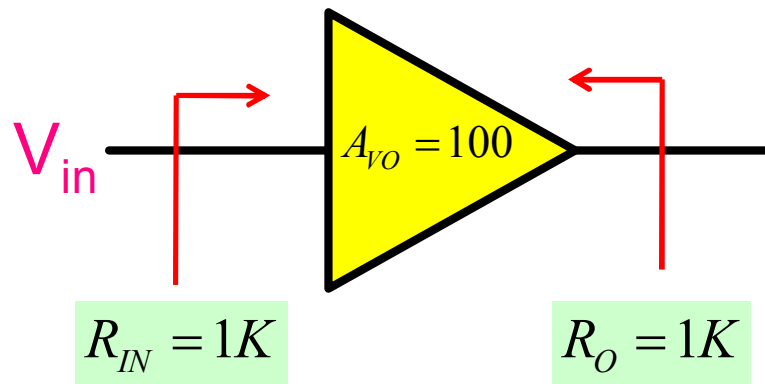
$$A_V = \frac{v_o}{v_s} = A_{VO} \times \frac{R_{in}}{R_S + R_{in}} \times \frac{R_L}{R_O + R_L} = 81$$




Increased input resistance

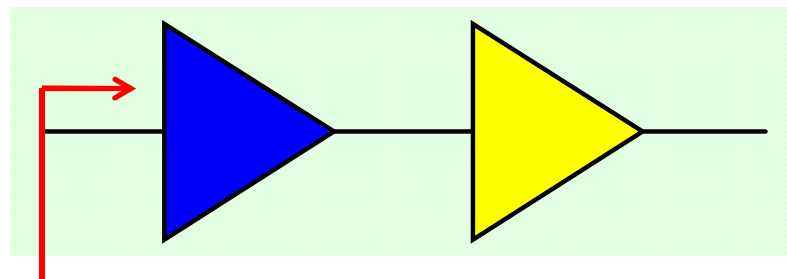


$$R_{IN} = 100K$$

Lower output resistance

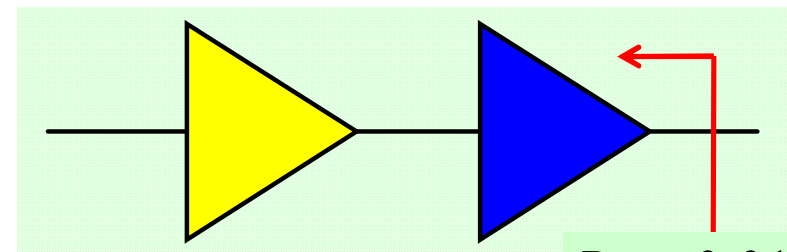

$$R_O = 0.01K$$

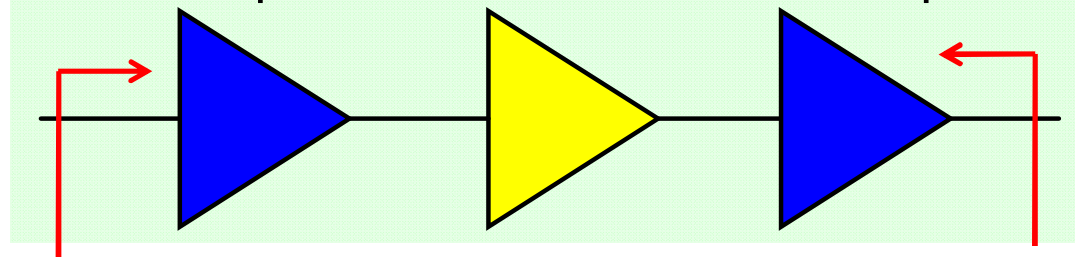
Increased input resistance and lower output resistance



$$R_{IN} = 100K$$

$$R_O = 0.01K$$


What are we looking for?

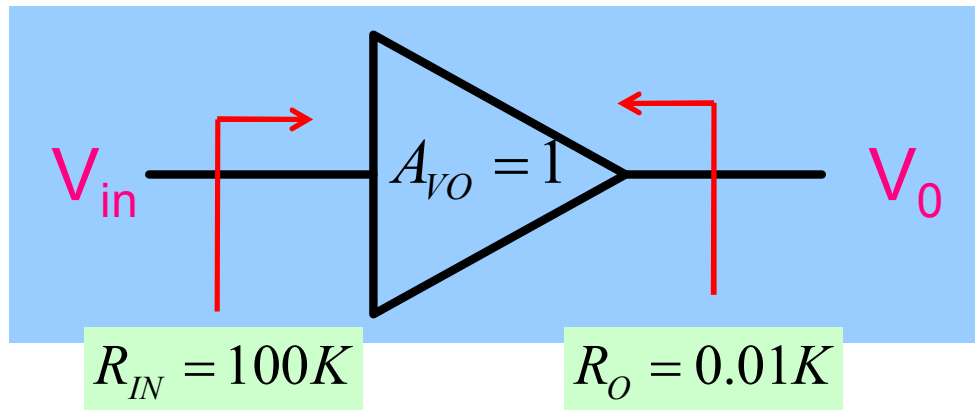

High bandwidth
High swing & linearity

- ❑ Low output resistance and high input resistance
- ❑ Large voltage swing with good linearity
- ❑ High bandwidth


Low output resistance

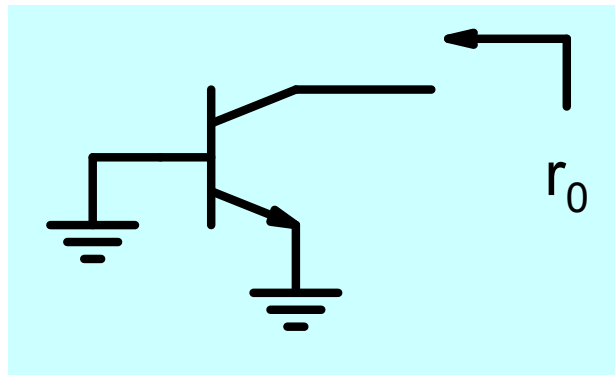


$$I_c = 2.6mA, \beta = 100, V_A = 104V$$

$$1/g_m = 10, r_\pi = 1000, r_o = 4 \times 10^4$$
$$1/g_m \ll r_\pi \ll r_o$$

Common Collector Amplifier

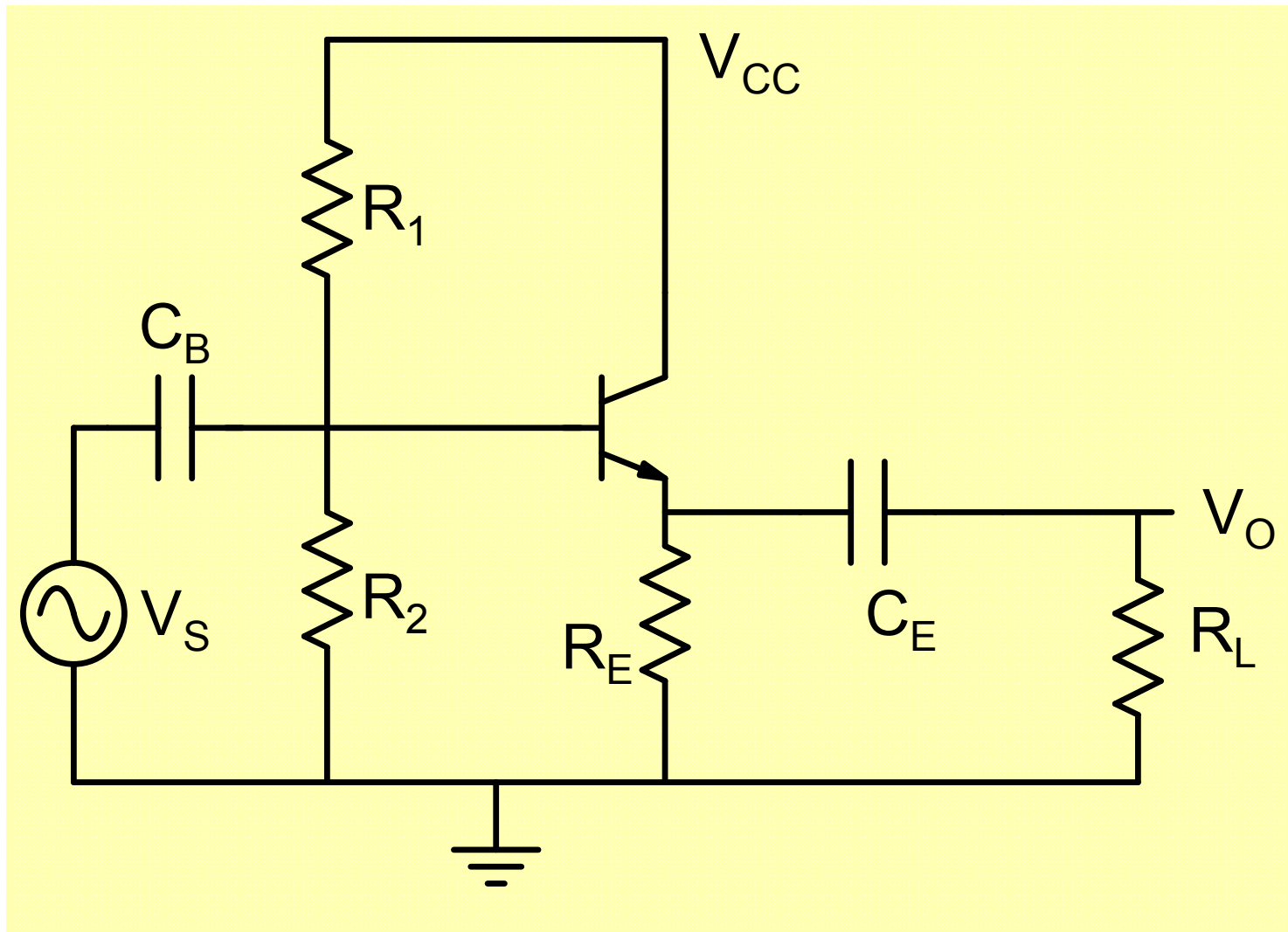


Small Signal Analysis

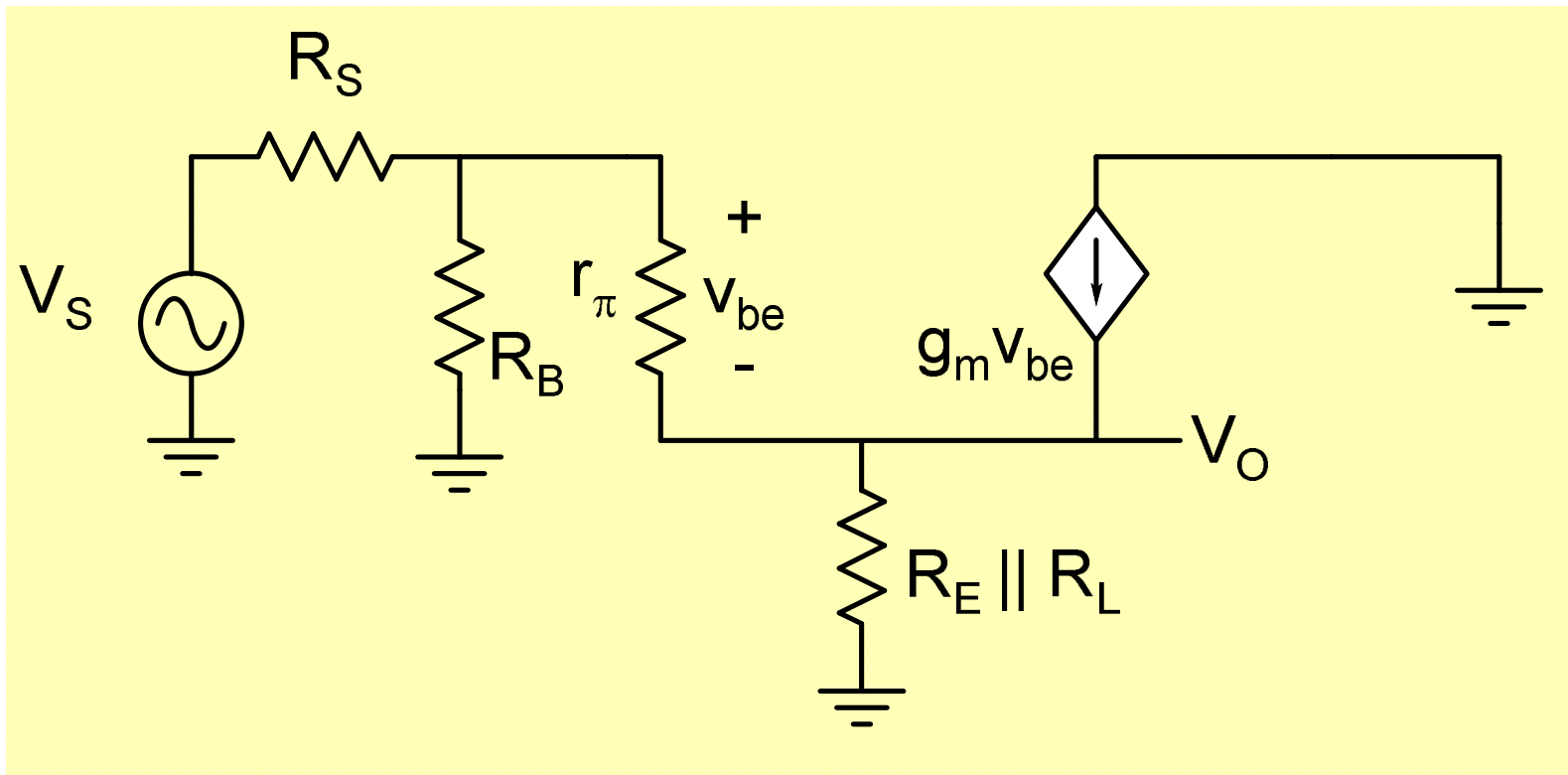

$$A_V = \left(\frac{1}{1 + R_S / R_B} \right) \times \frac{(\beta + 1) \times R_E \parallel R_L}{R_S \parallel R_B + r_\pi + (\beta + 1) \times R_E \parallel R_L}$$



Less than unity but almost ~ 1

Emitter Follower

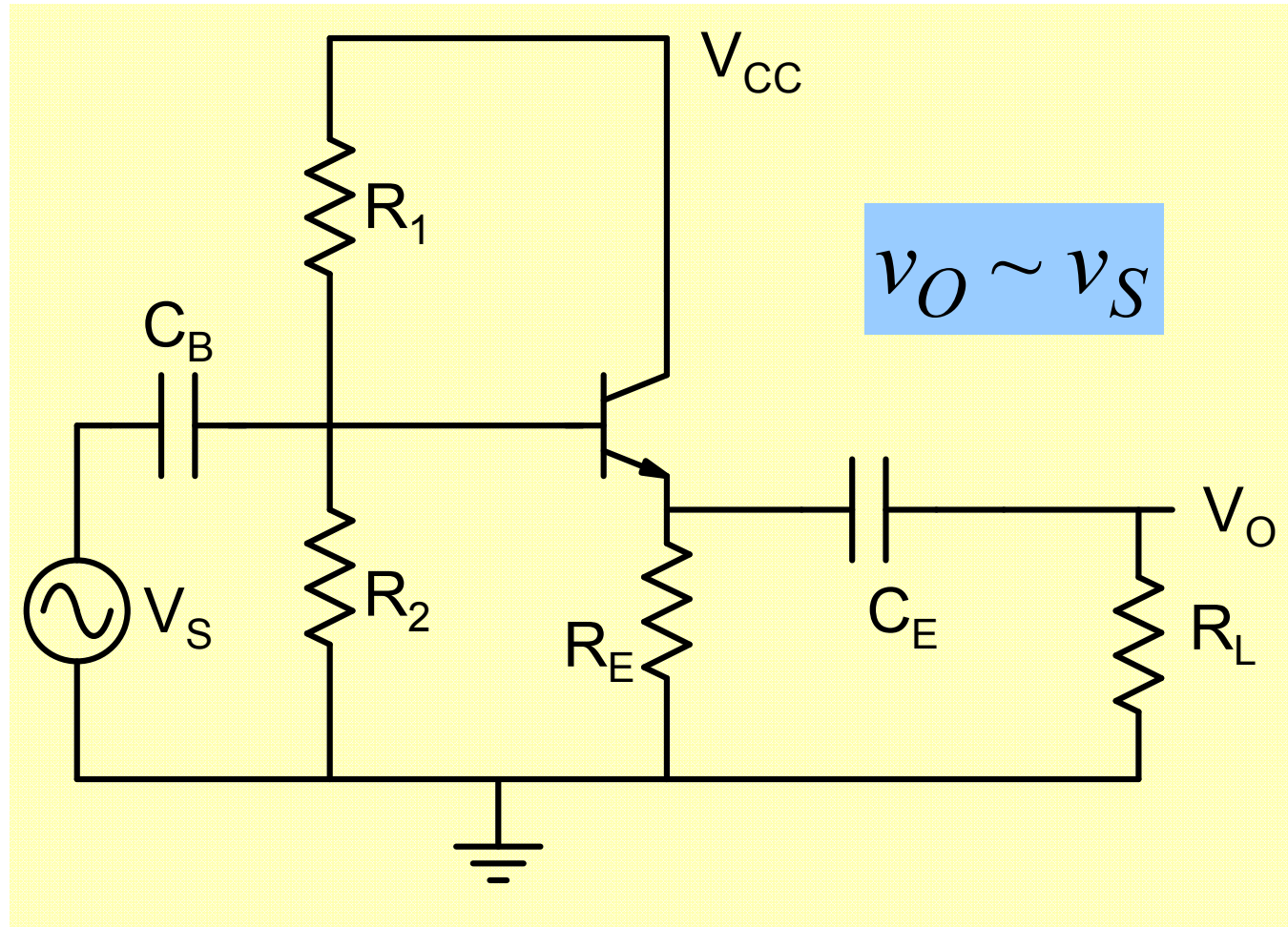



Why is emitter follower called an amplifier when its voltage gain is less than unity?

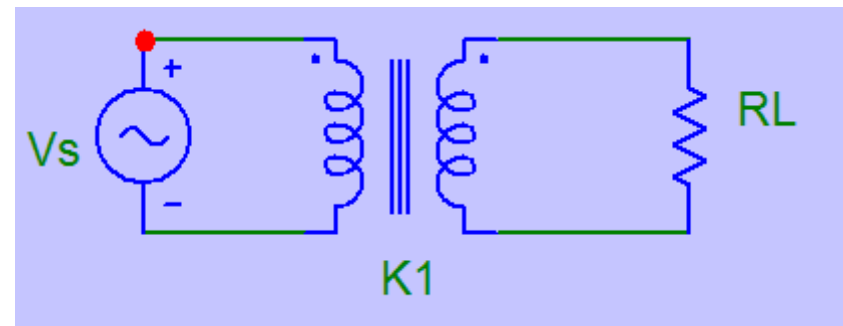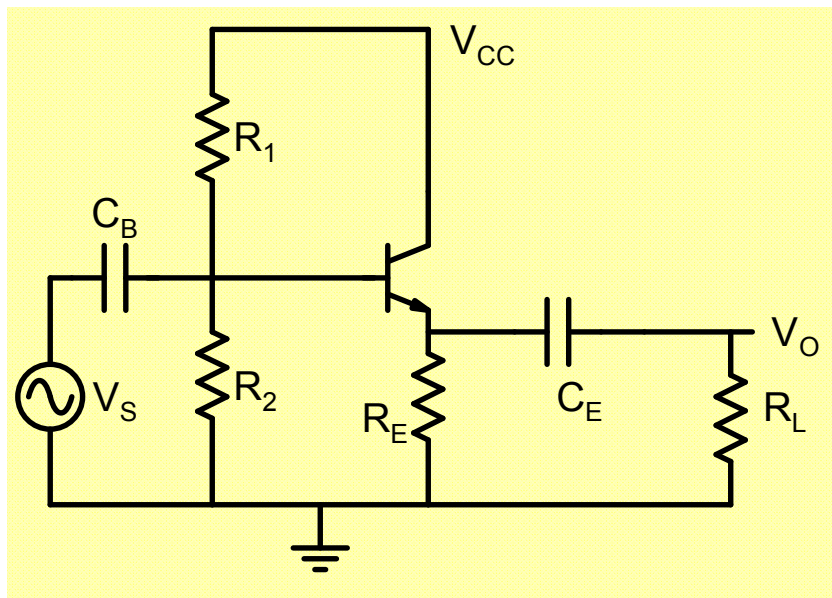Why don't we call a step-up transformer an amplifier?





A necessary condition is **Power Gain**

Input Resistance

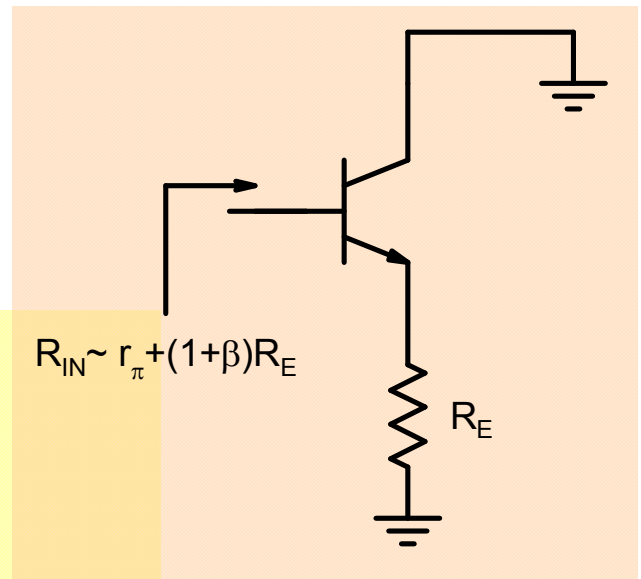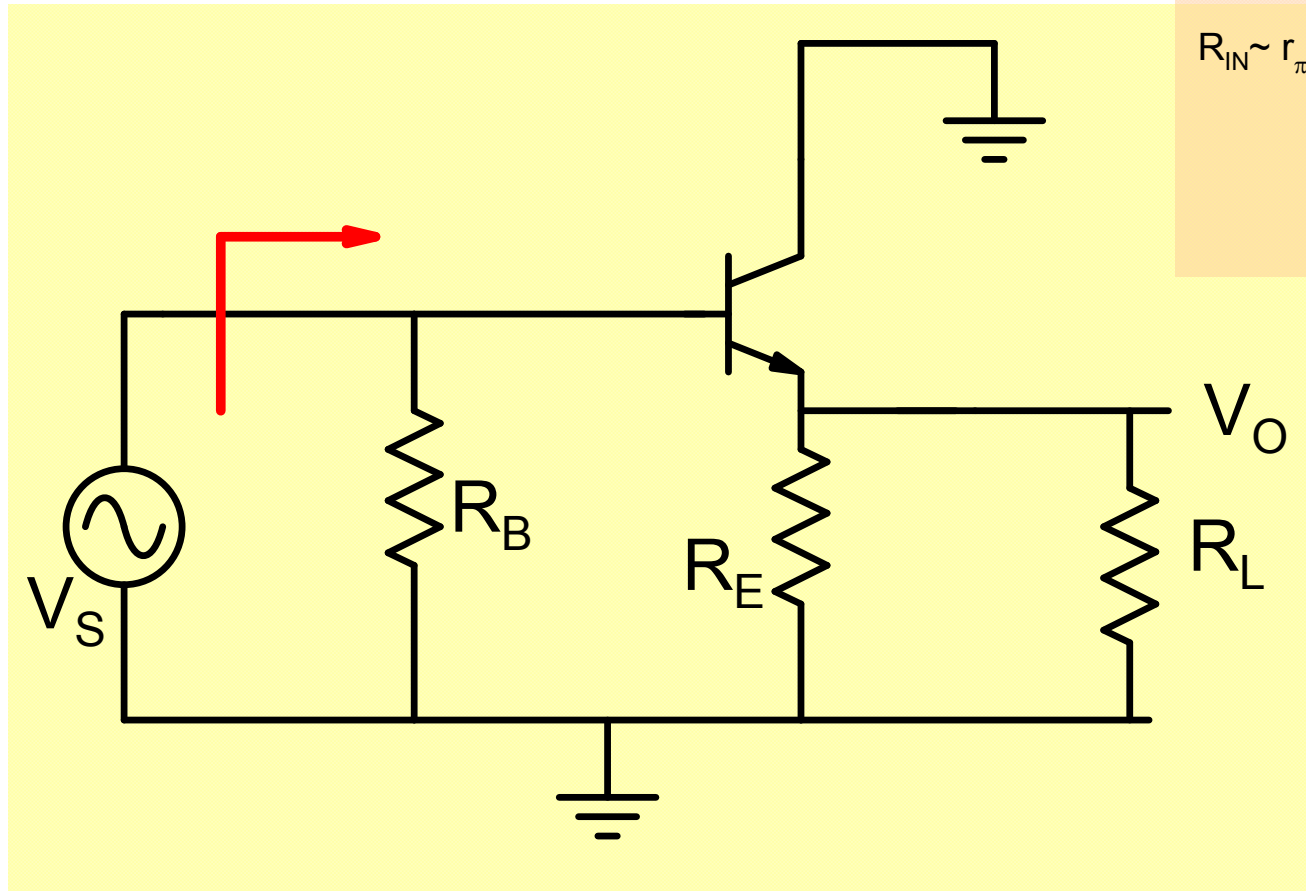

$$R_{in} = (r_\pi + (\beta + 1) \times R_E \parallel R_L) \parallel R_B$$

Output Resistance

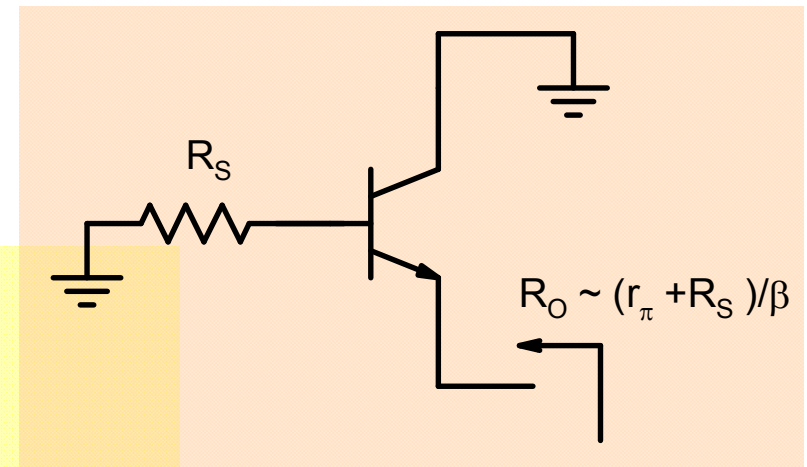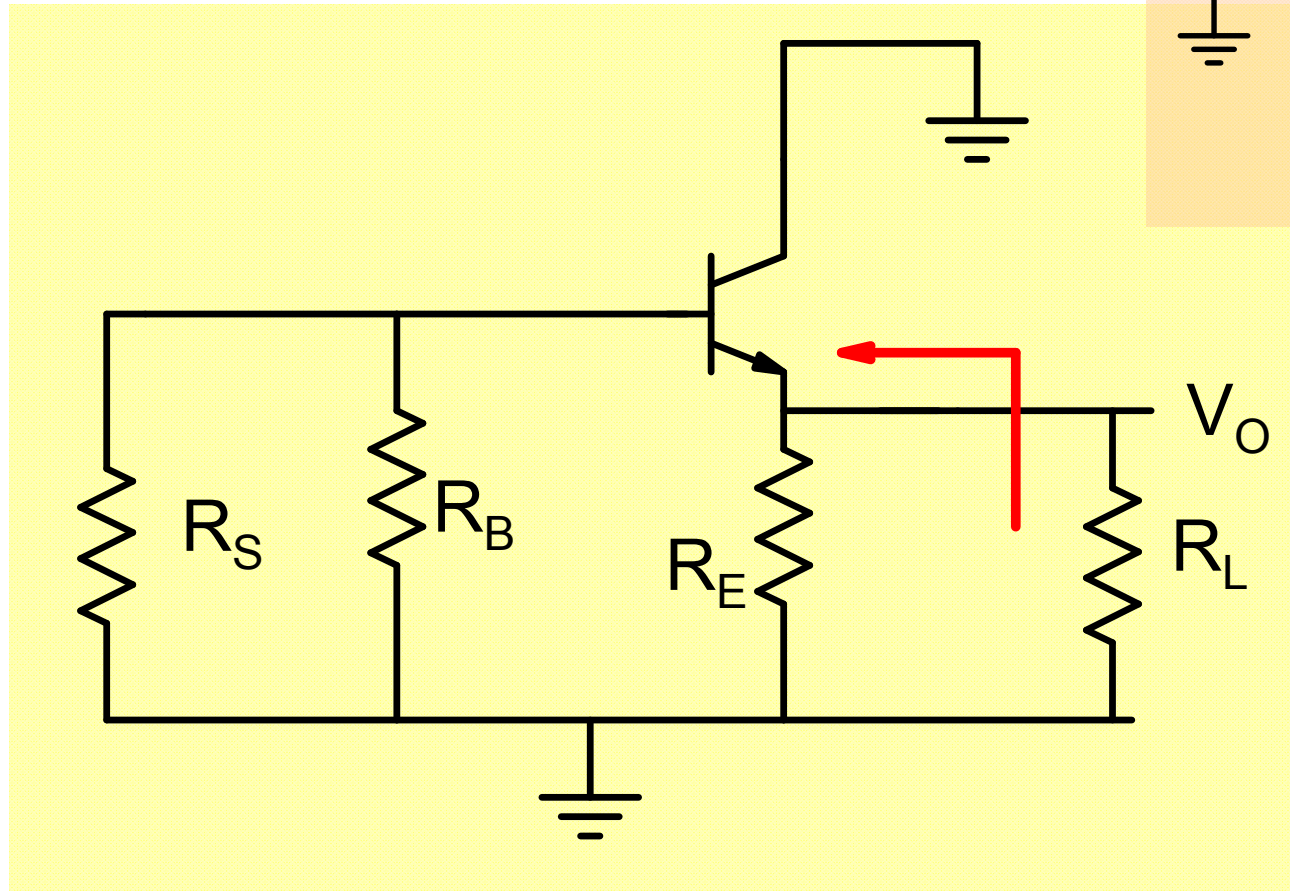

$$R_O = \frac{(r_\pi + R_B \parallel R_S)}{\beta + 1} \parallel R_E$$

Relationship between gain, input & output resistances

$$A_V = \frac{R'_S}{R_S} \times \frac{(\beta + 1) \times R'_E}{R'_S + r_\pi + (\beta + 1) \times R'_E}$$

$$A_V \sim 1$$

$$R'_S = R_S \parallel R_B; R'_E = R_E \parallel R_L$$

$$R_O = \frac{(r_\pi + R'_S)}{\beta + 1} \parallel R_E$$

$$R_O \cong \frac{(r_\pi + R'_S)}{\beta + 1}$$


$$R_{in} = \{r_\pi + (\beta + 1) \times R'_E\} \parallel R_B$$

$$R_{in} \cong (\beta + 1) \times R'_E$$

$$\frac{R_{in}}{R_O} \cong \beta \times \frac{I_{CQ} R_E}{V_T} \frac{1}{1 + R'_S / r_\pi} \times \frac{1}{1 + R_E / R_L}$$

To obtain high swing

$$I_{CQ}R_E \sim \frac{V_{CC}}{2}$$

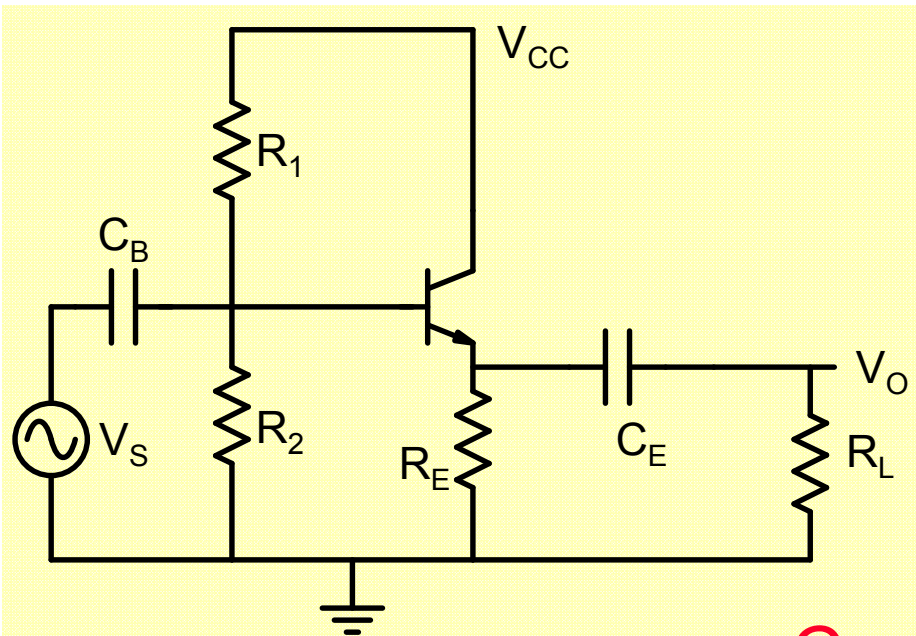

$$\frac{R_{in}}{R_O} \cong \beta \times \frac{V_{CC}}{2V_T} \frac{1}{1 + R'_S/r_\pi} \times \frac{1}{1 + R_E/R_L}$$

Comparison with CE amplifier


$$\frac{A_V \times R_{in}}{R_O} \cong \beta$$

Even with a gain of unity

$$\frac{R_{in}}{R_O} \cong \beta$$

Clearly, a common collector amplifier can deliver much lower output resistance and higher input resistance as compared to CE amplifier. Further it has higher swing and low distortion !

Example

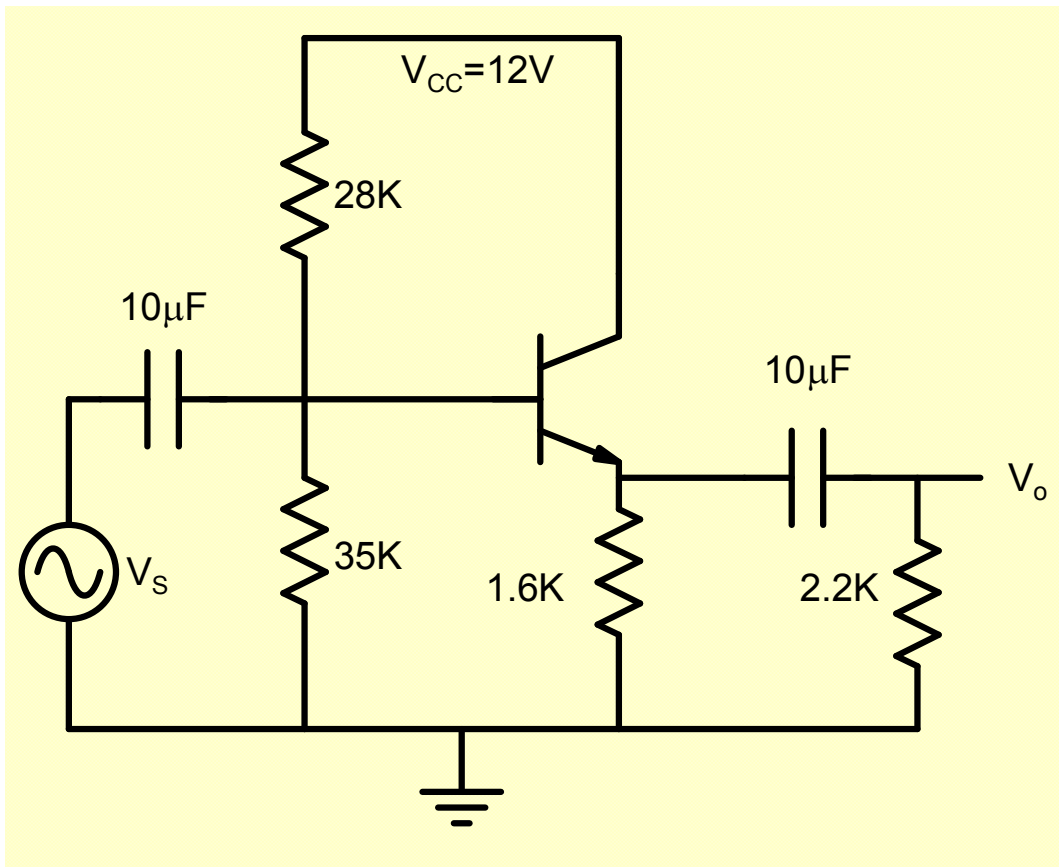

$$\beta = 100$$



$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V$$

$$A_V = 0.99;$$

$$R_{in} = 13.4K (R_B = 16k)$$

$$R_O = 9.5\Omega$$
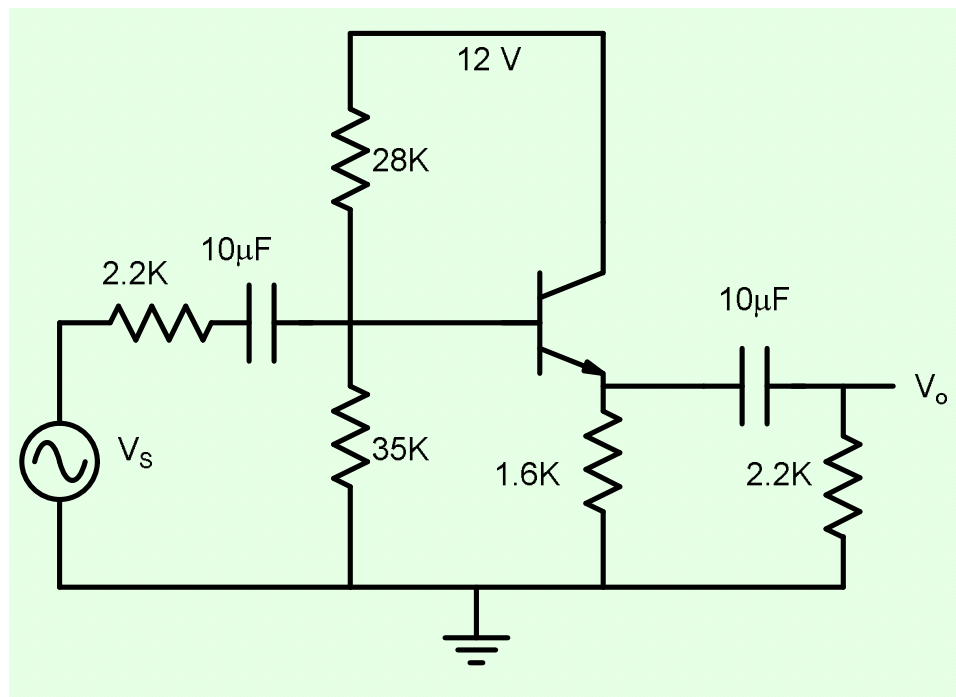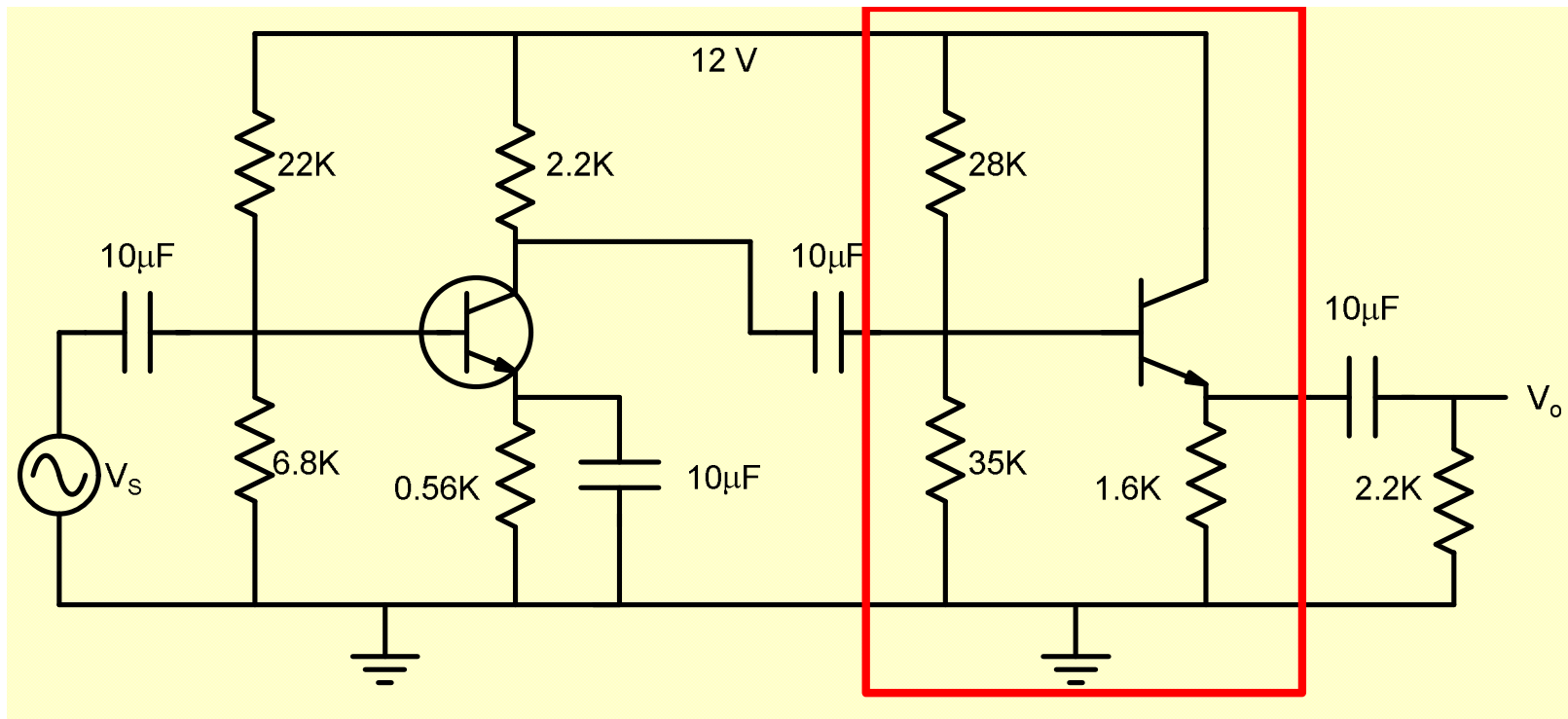
$$\frac{R_{in}}{R_O} = 1.4 \times 10^3 \cong \beta \times 14$$



$$\beta = 100$$

$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V$$


$$A_v = 0.85;$$

$$R_{in} = 13.4K (R_B = 16k)$$

$$R_O = 27\Omega$$

$$\frac{A_v R_{in}}{R_O} = 422 \cong \beta \times 4.2$$

Example

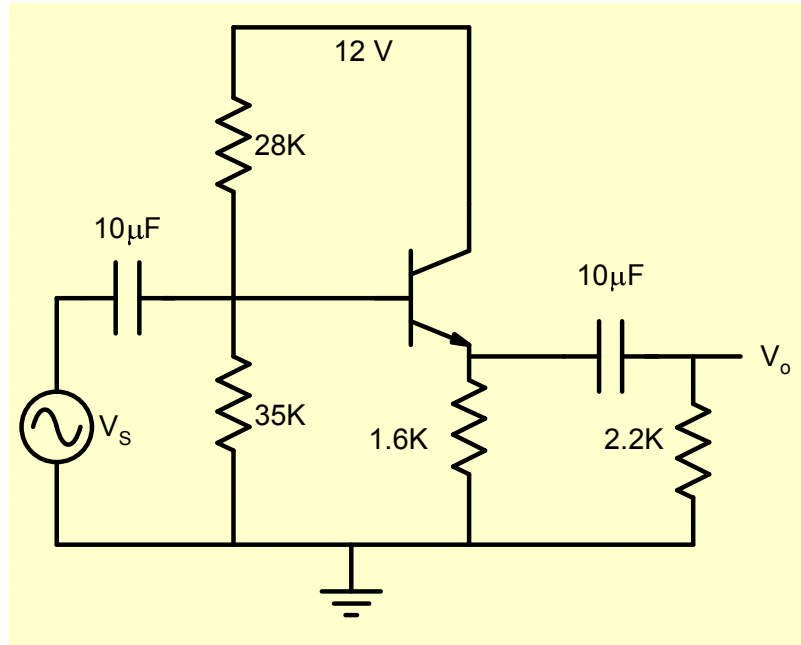

$$\beta = 100$$


$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V$$

$$A_V = 0.99;$$

$$R_{in} = 13.4K (R_B = 16k)$$

$$R_O = 9.5\Omega$$

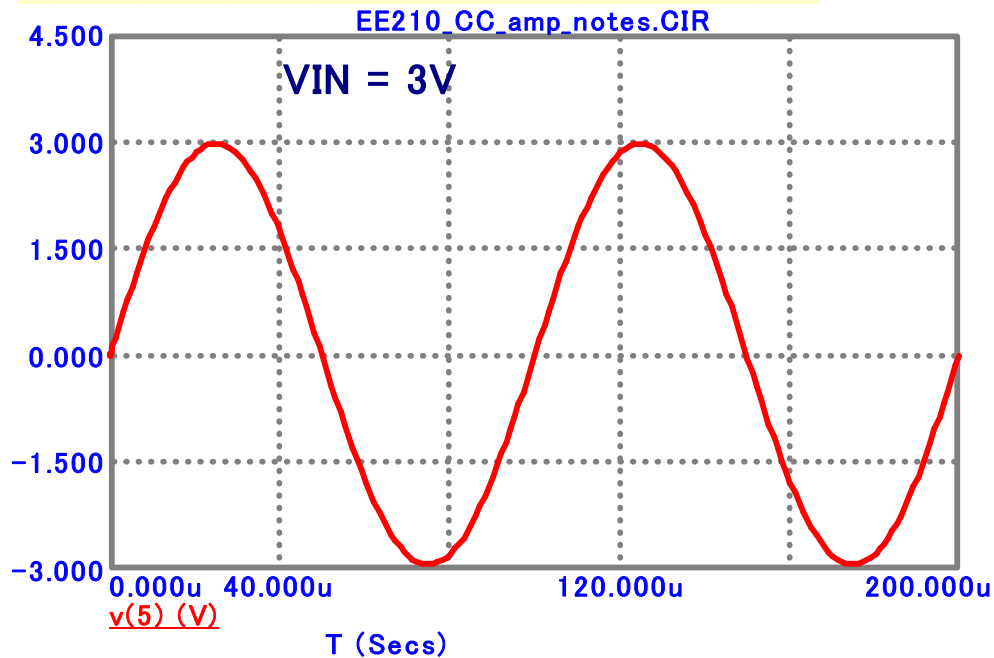
$$\frac{R_{in}}{R_O} \cong \beta \times 14$$



$$V_{OM} \sim 6V \text{ p-p}$$

$$THD \sim 0.5\%$$

Comparison-1

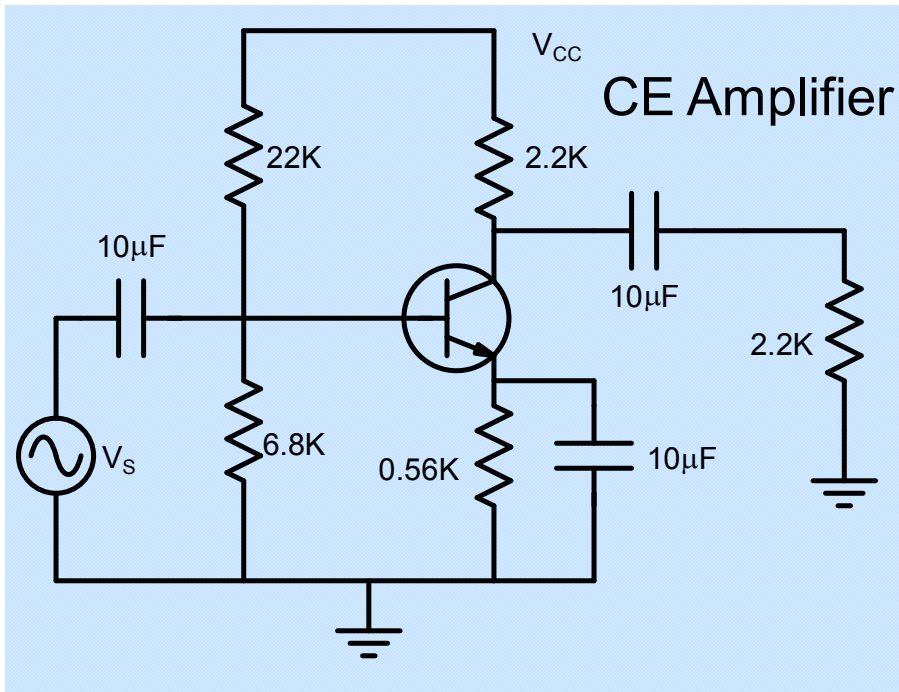


$$\beta = 100$$

$$I_{CQ} = 3.4mA; V_{CEQ} = 2.57V$$

$$A_V = 110.7; R_{in} = 0.82K; R_O = 2.2K$$

$$v_{om} = 0.39V @ THD = 1.9\%$$

$$f_L = 1.67kHz; f_H = 5.8MHz$$

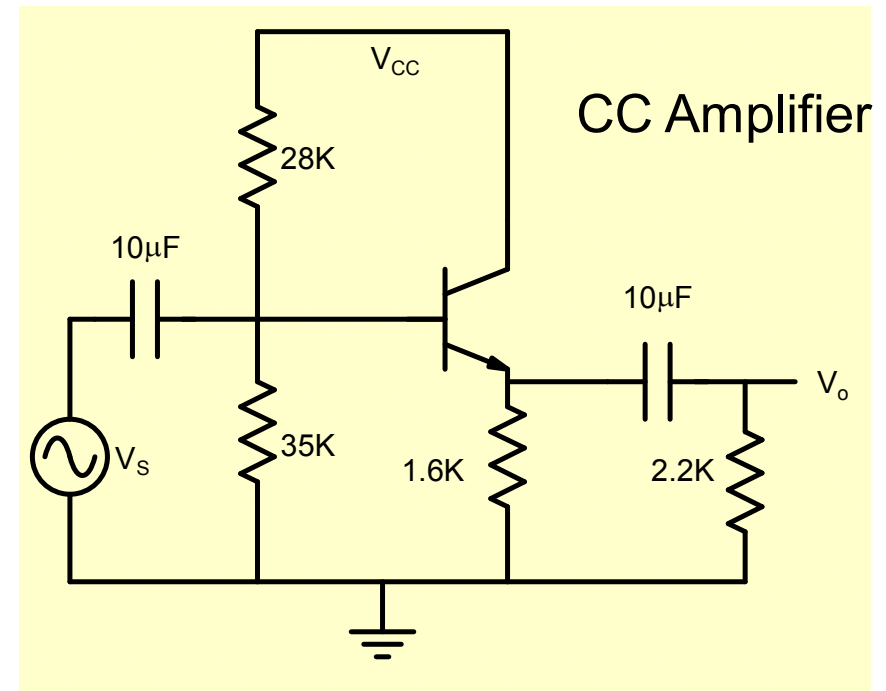

$$\beta = 100$$


$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V$$

$$A_V = 0.99; R_{in} = 13.4K (R_B = 16k); R_O = 9.5\Omega$$

$$v_{om} = 3V @ THD = 0.5\%$$

$$f_L = 7.6Hz; f_H = 3.1GHz$$

Comparison-2

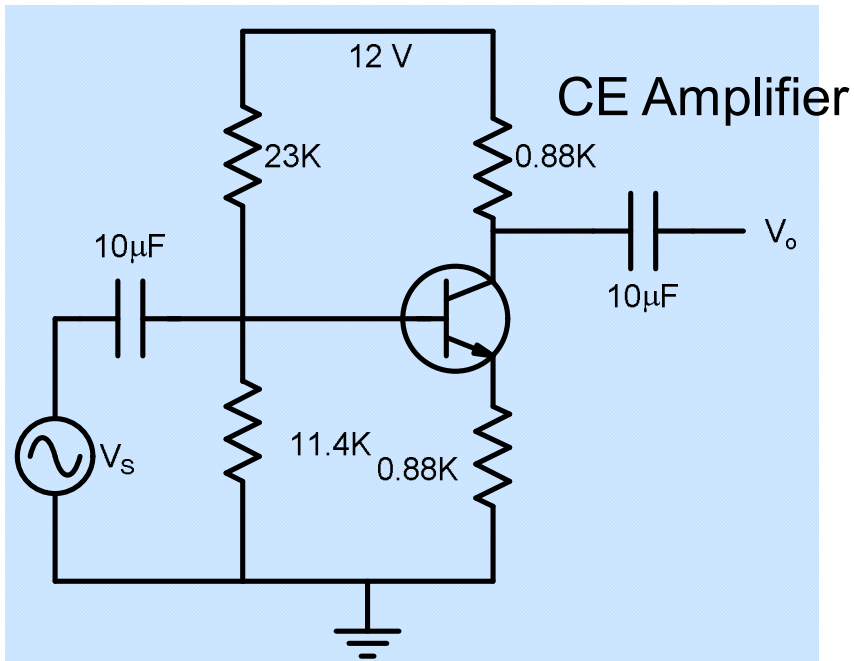

$$\beta = 100$$


$$I_{CQ} = 3.4mA; V_{CEQ} = 6V; R_B / \beta R_E = 0.09$$

$$A_{Vo} = 0.98; R_{in} = 7K; R_O = 0.88K$$

$$\frac{A_{Vo} \times R_{in}}{R_O} = 7.8$$

$$v_{om} = 3V @ THD = 0.5\%$$

$$f_L = 2.3Hz; f_H = 50MHz$$

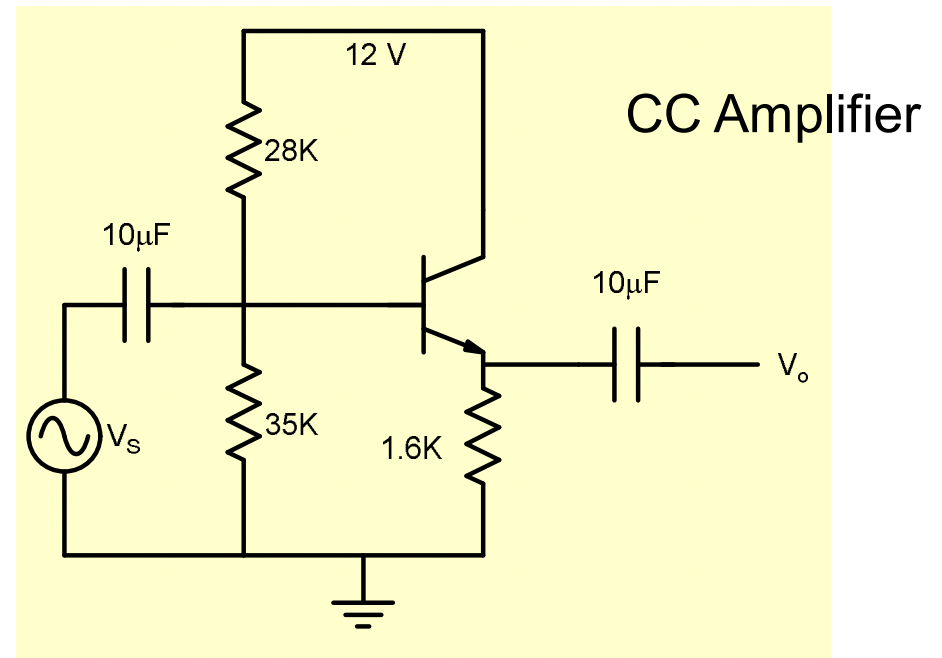

$$\beta = 100$$

$$I_{CQ} = 3.4mA; V_{CEQ} = 6.5V; R_B / \beta R_E = 0.1$$

$$A_V = 0.99; R_{in} = 14.2K; R_O = 9.5\Omega$$

$$\frac{A_{Vo} \times R_{in}}{R_O} = 1.5 \times 10^3 \quad \times 192$$

$$v_{om} = 3V @ THD = 0.5\%$$

$$f_L = 1.1Hz; f_H = 3.8GHz \quad \times 76$$