



EE210: Microelectronics-I

Lecture-28 :Output Stage-2

Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur


Class A Amplifier

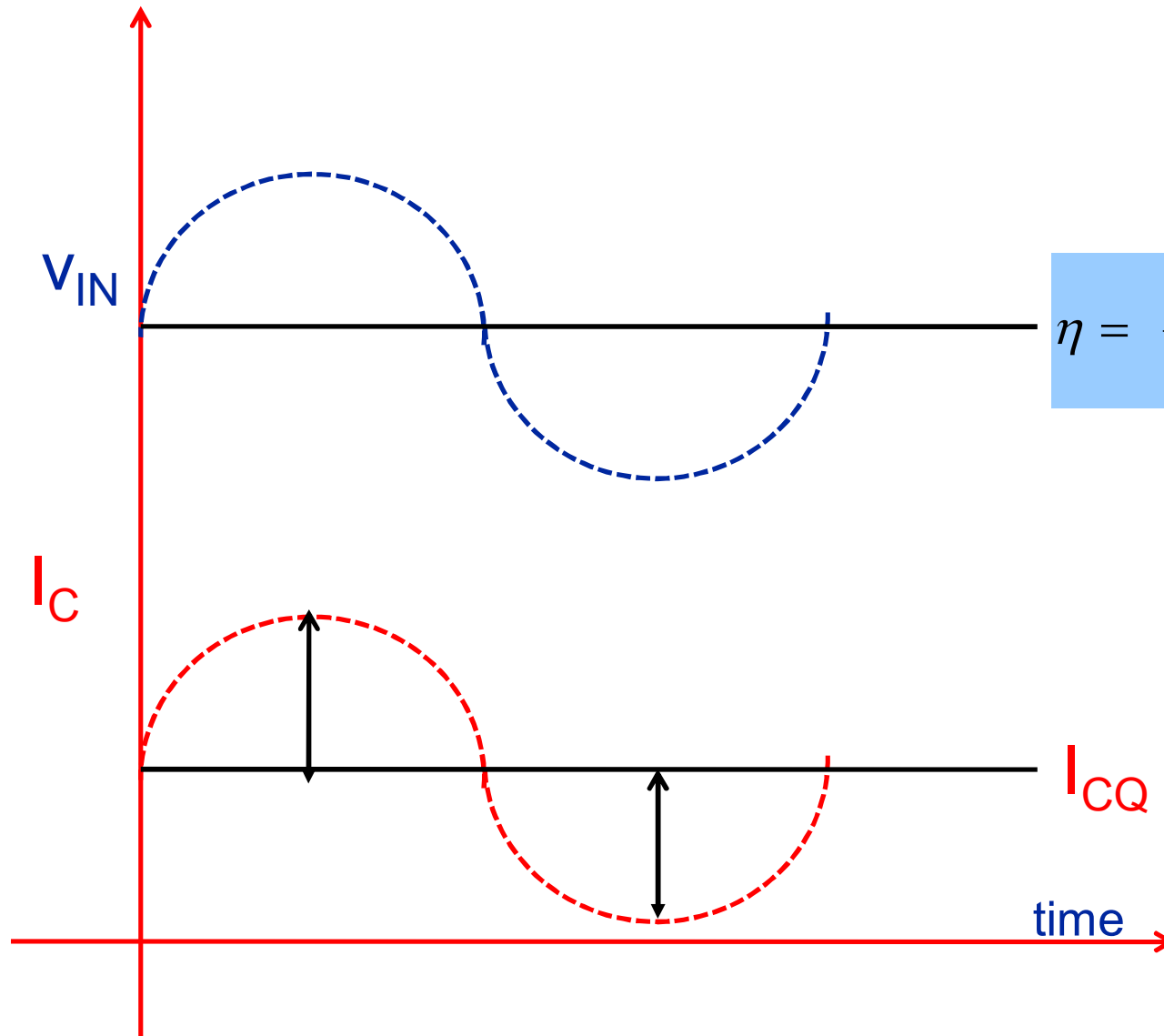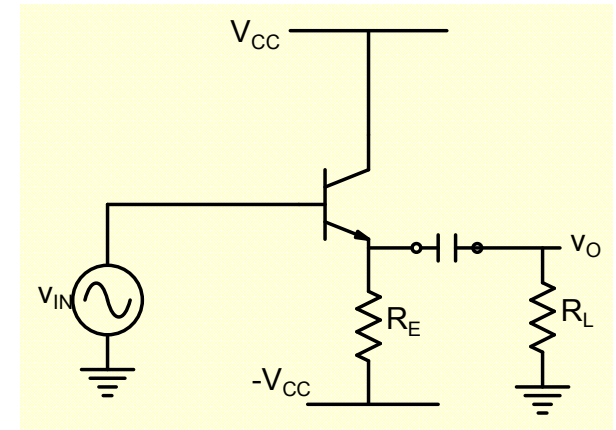


$$\eta = \frac{1}{4} \times \left(\frac{v_{op}}{V_{CC}} \right) \left(\frac{v_{op}}{I_E \times R_L} \right) < 25\%$$

An efficient amplifier should take power from the supply only when power is to be delivered to the load !

Class B Amplifier

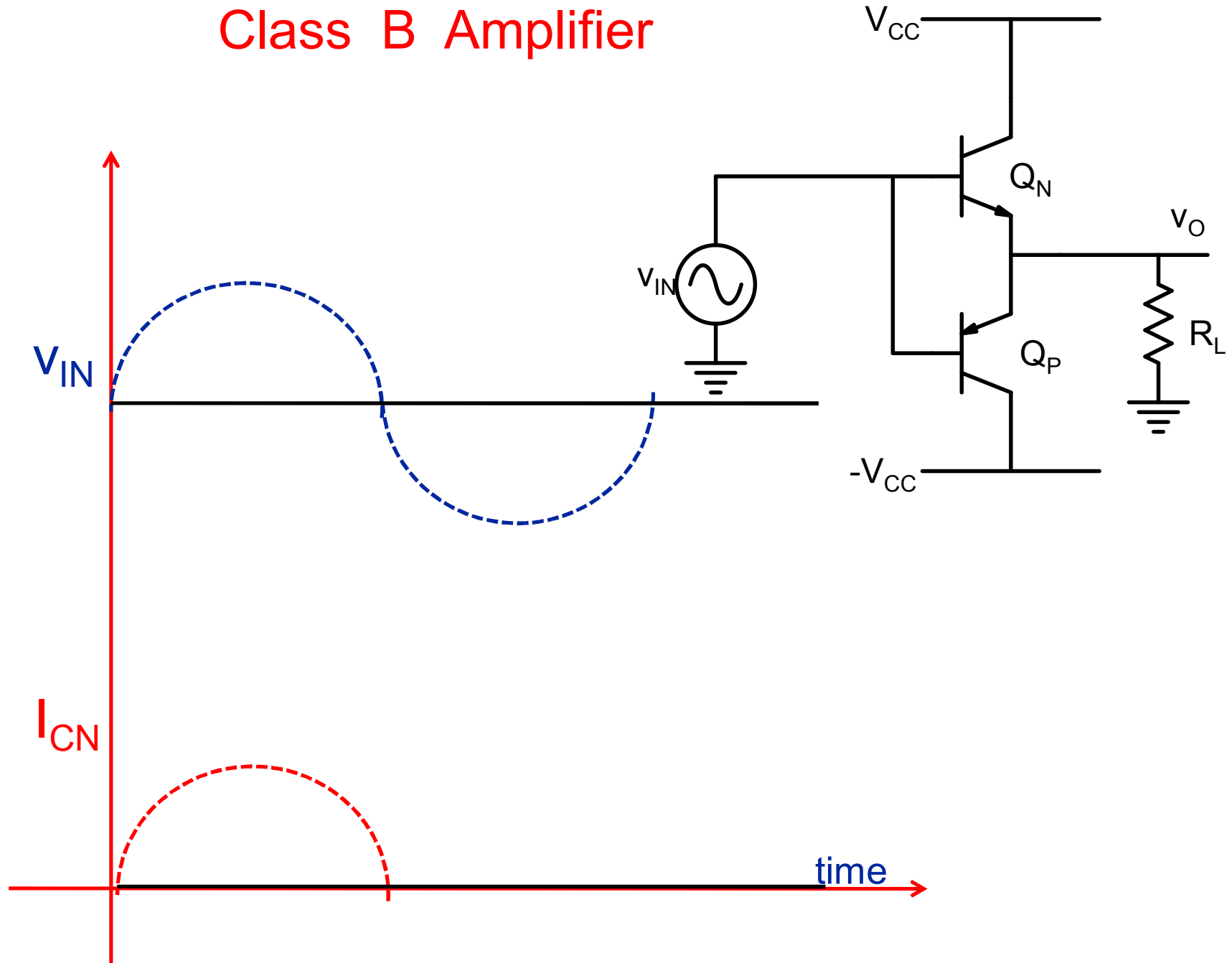

Maximum Efficiency

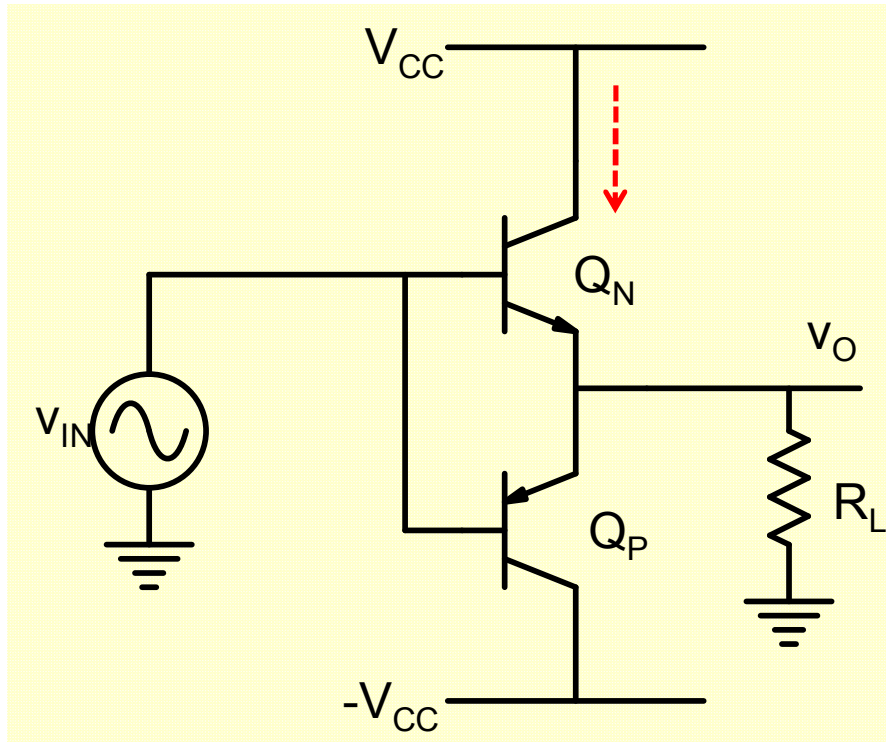

$$P_L = \frac{v_{op}^2}{2R_L}$$

$$i_{CN} = \frac{v_{op} \sin(\omega t)}{R_L} \text{ for } 0 \leq t \leq T/2$$

$$= 0 \text{ for } T/2 \leq t \leq T$$

$$P_S = 2 \frac{1}{T} \int_0^T V_{CC} \times i_{CN} dt$$

For two supplies

$$P_S = 2 \frac{V_{CC} \times v_{op}}{\pi R_L}$$

$$\eta = \frac{\pi}{4} \times \frac{v_{op}}{V_{CC}} \times 100$$

$$v_{CE} > V_{CEsat}$$




$$V_{CC} - v_{op} \sin(\omega t) > V_{CEsat}$$


$$v_{op} \leq V_{CC} - V_{CEsat}$$

$$\eta_{max} \cong 78.5\%$$

$$v_{op} \leq V_{CC} - V_{BE}$$




Cross-over Distortion

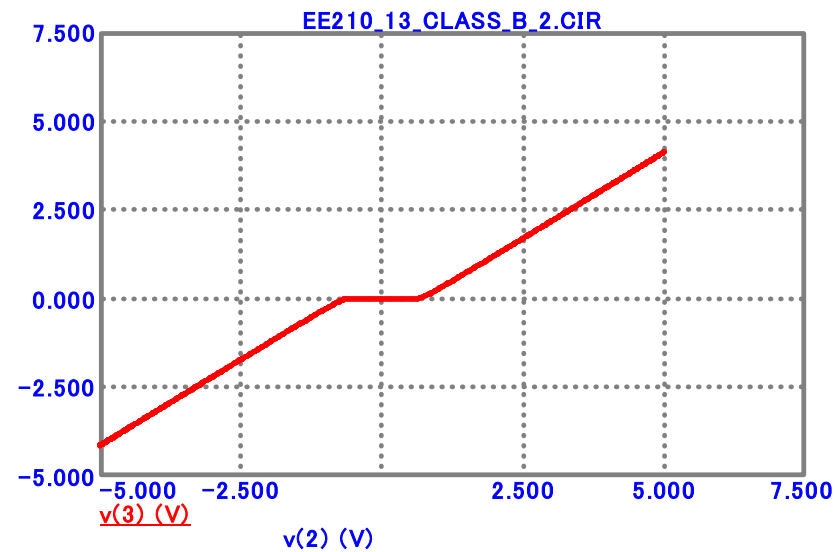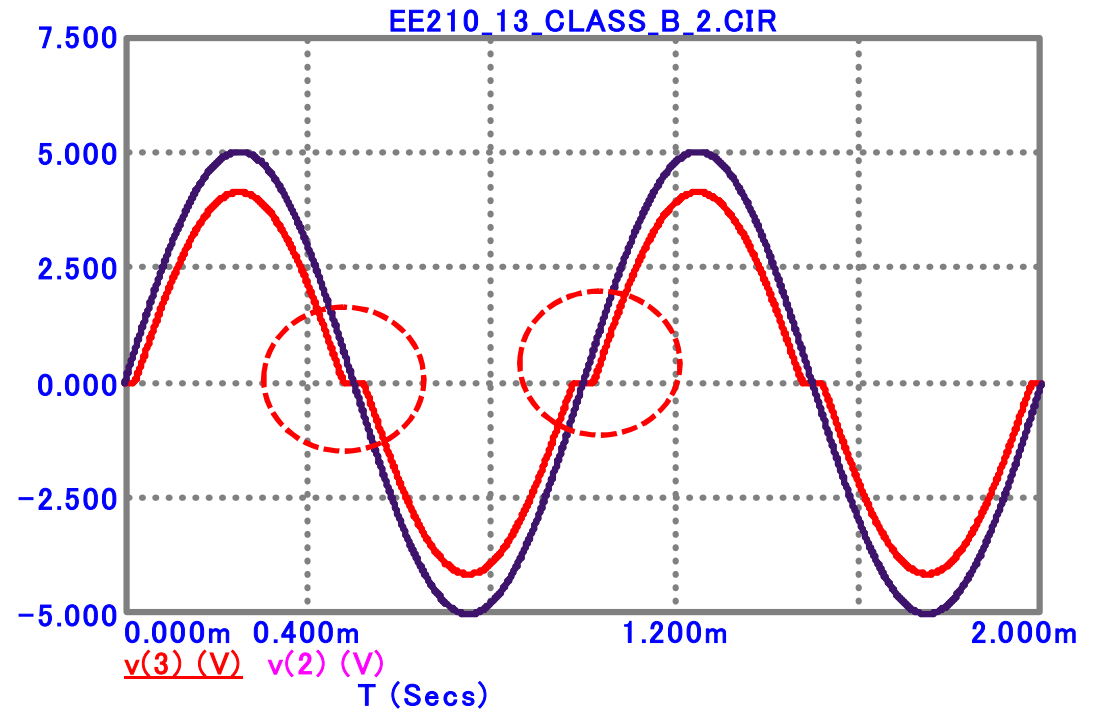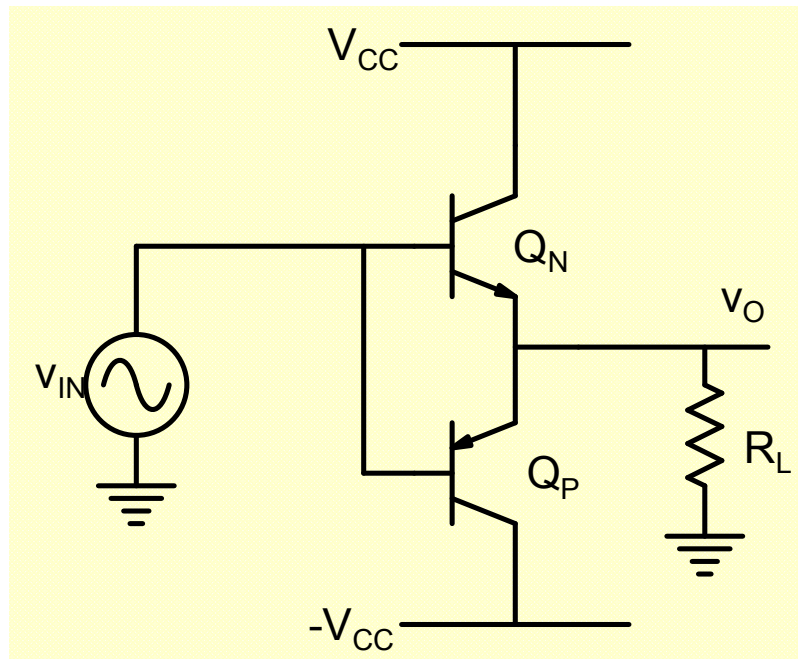

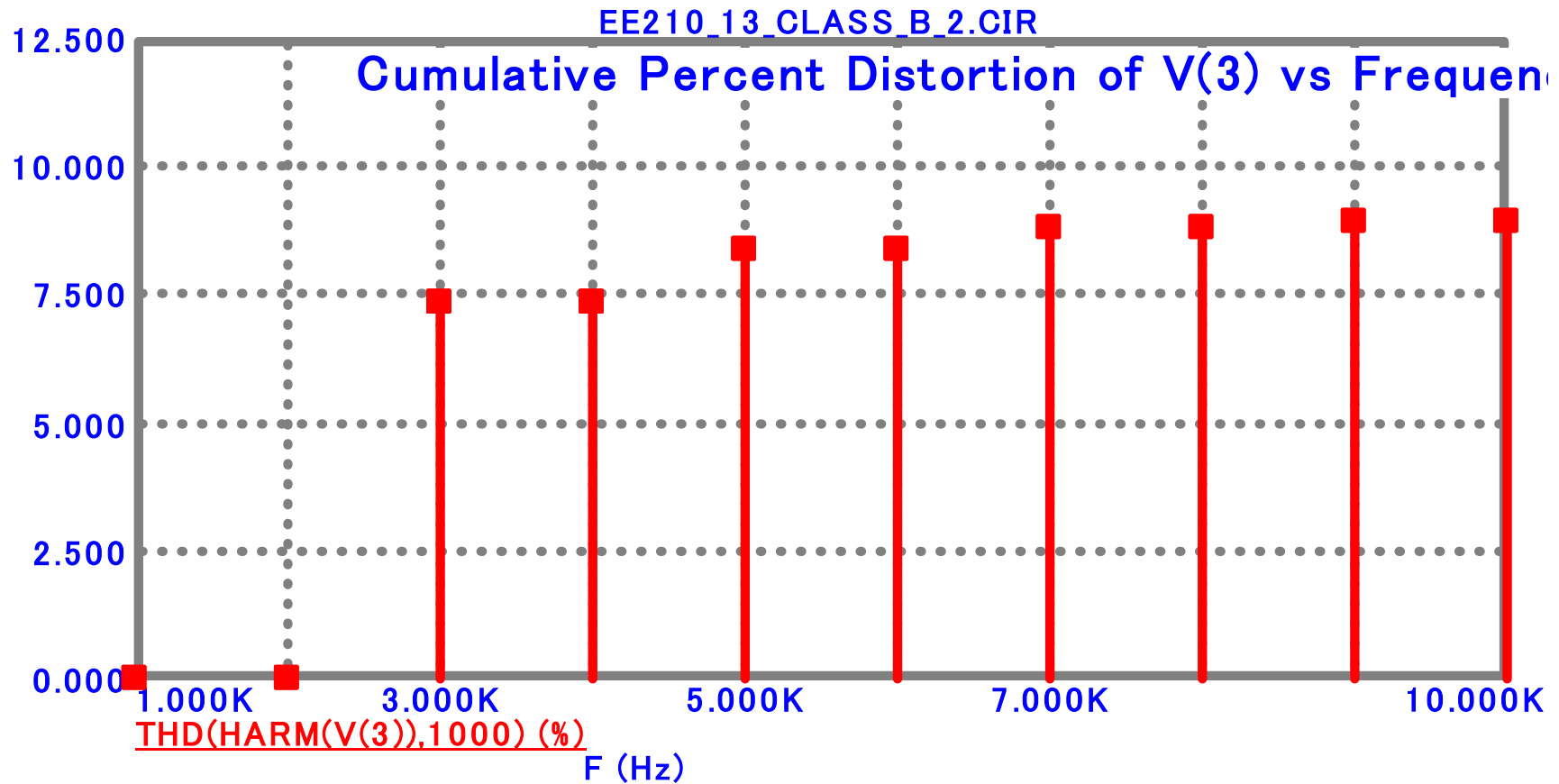

$$V_{CC} = 5V; V_{in} = 5V$$





Solution

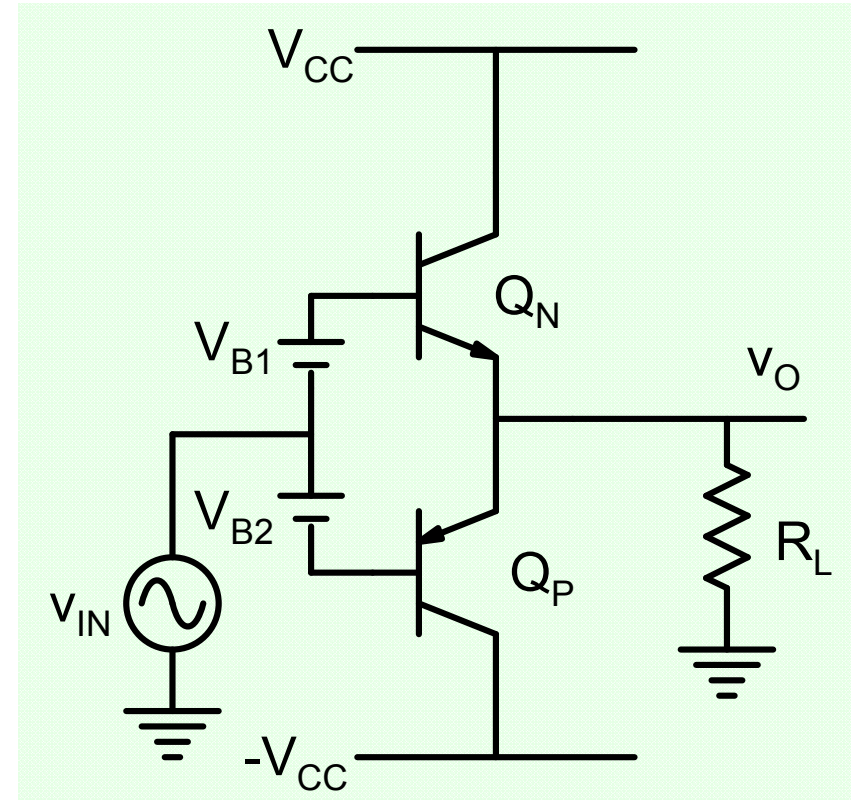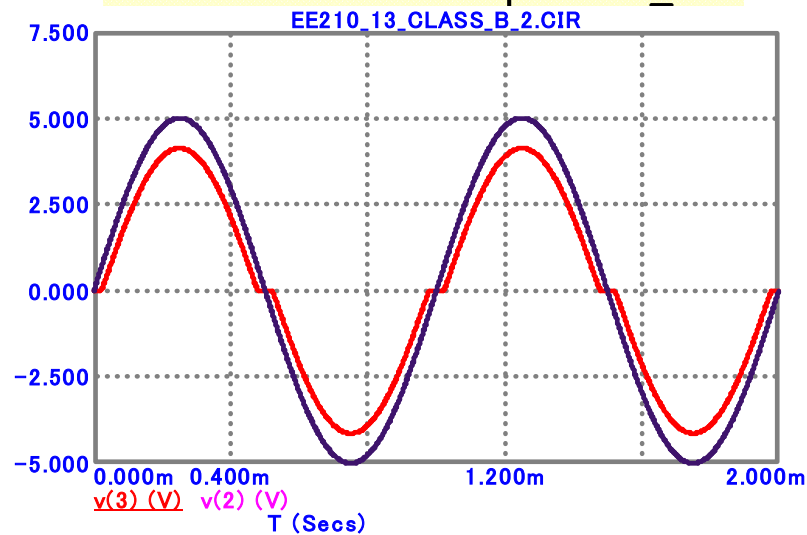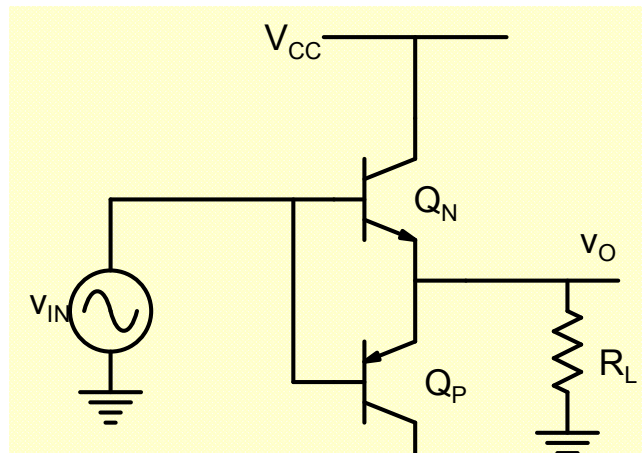


Voltages V_{B1} and V_{B2} are chosen such that both transistors are ON but conducting small current.

The amplifier now works from $V_{IN} = 0$ onwards

$$V_B = 0.65V$$

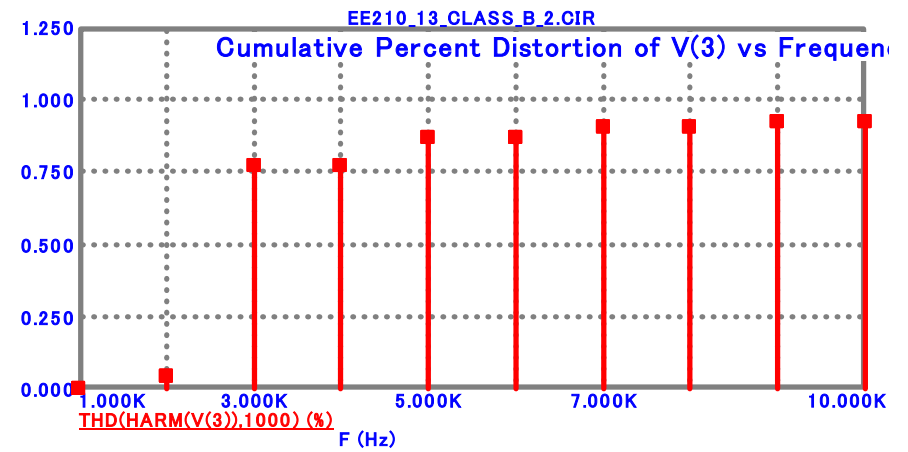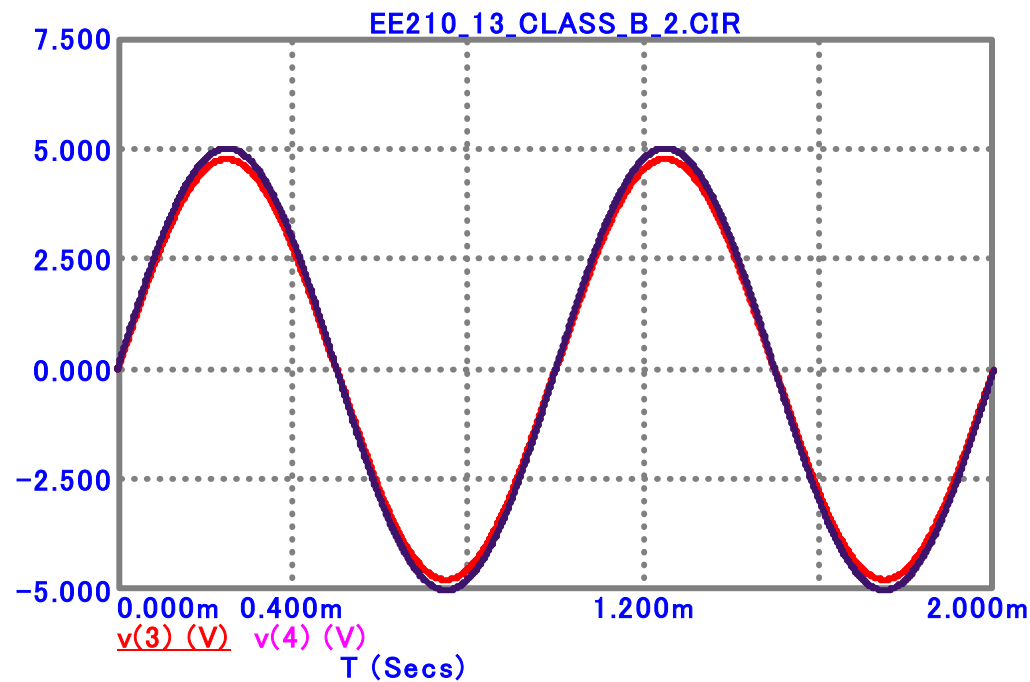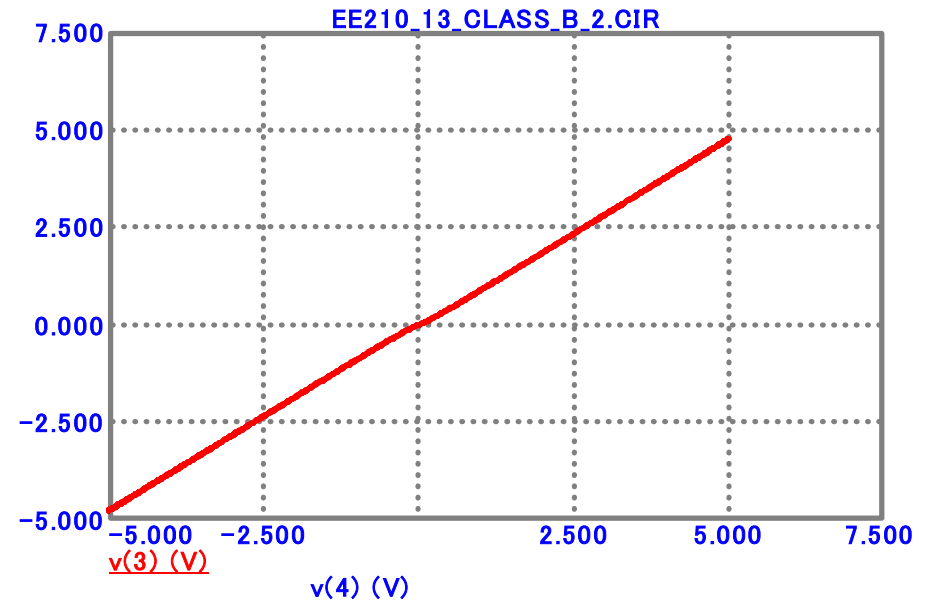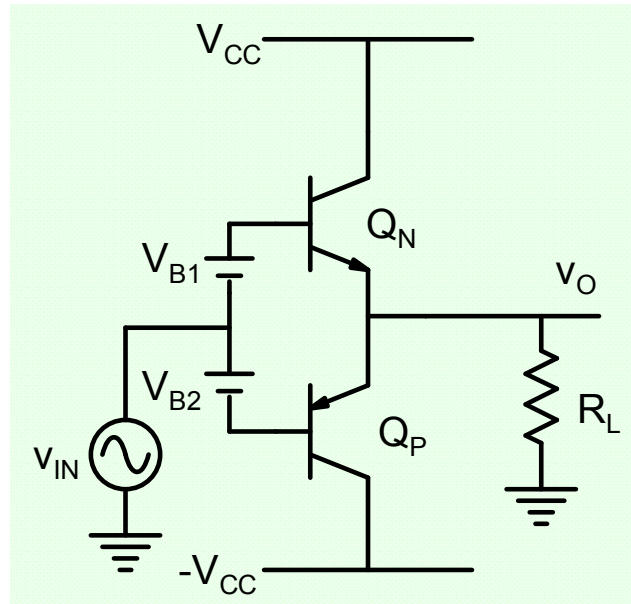


Class AB Amplifier

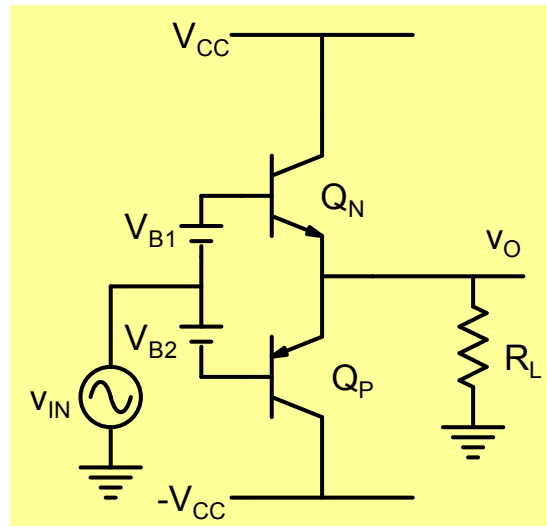

$$V_{CC} = 5V; V_{in} = 1V; V_B = 0.7V$$


Current sourced by each transistor

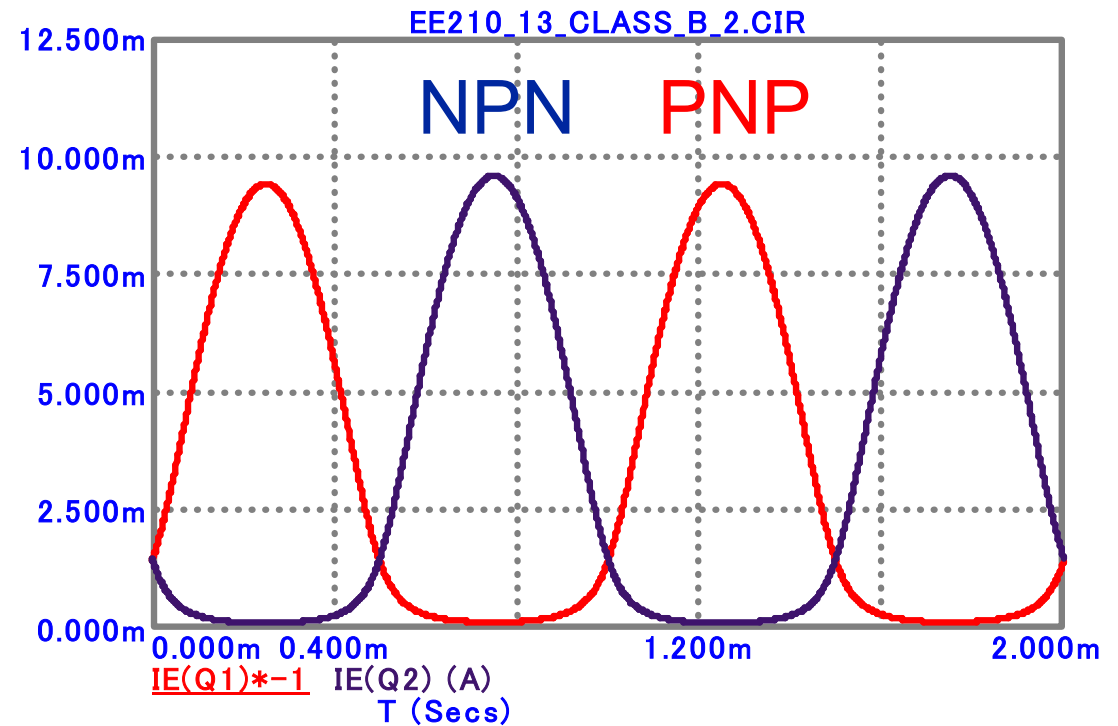

Each transistor conducts for more than half the cycle

There is some standby power dissipation and efficiency is a little lower.

How do we realize the battery?

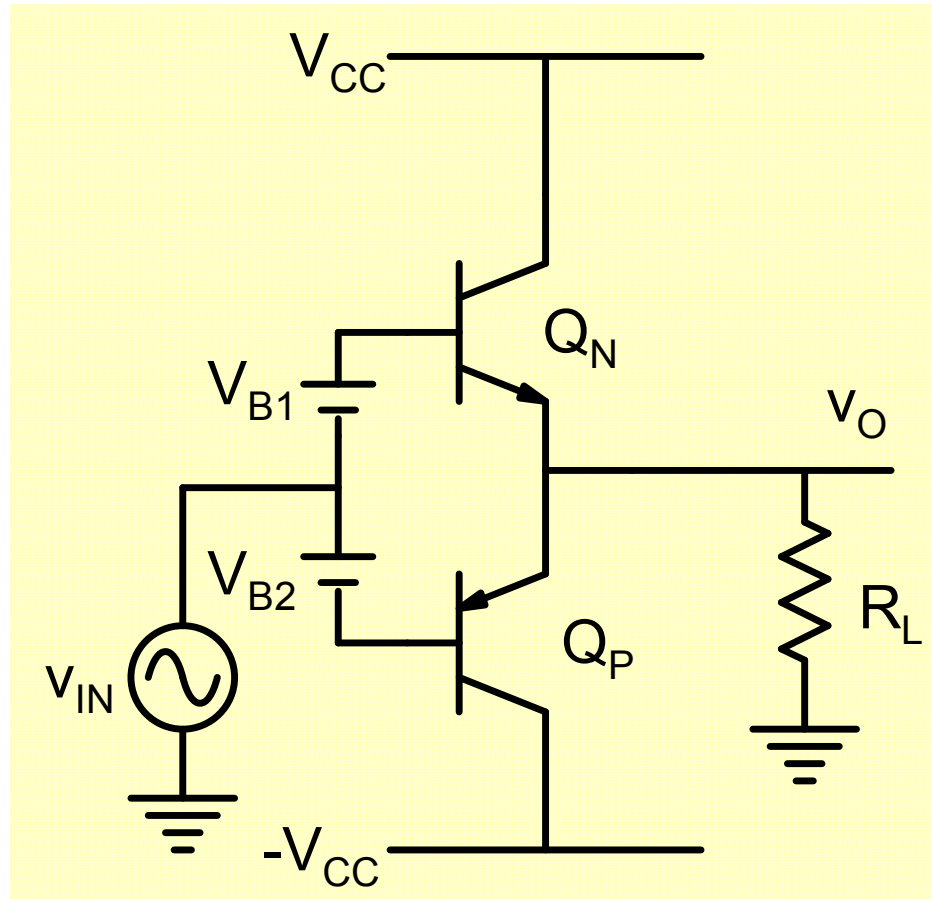


We need to bias the transistors at about ~0.7 Volts.


A slight increase in voltage would significantly increase standby power dissipation

A lower value of bias voltage may result in some crossover distortion

Solution


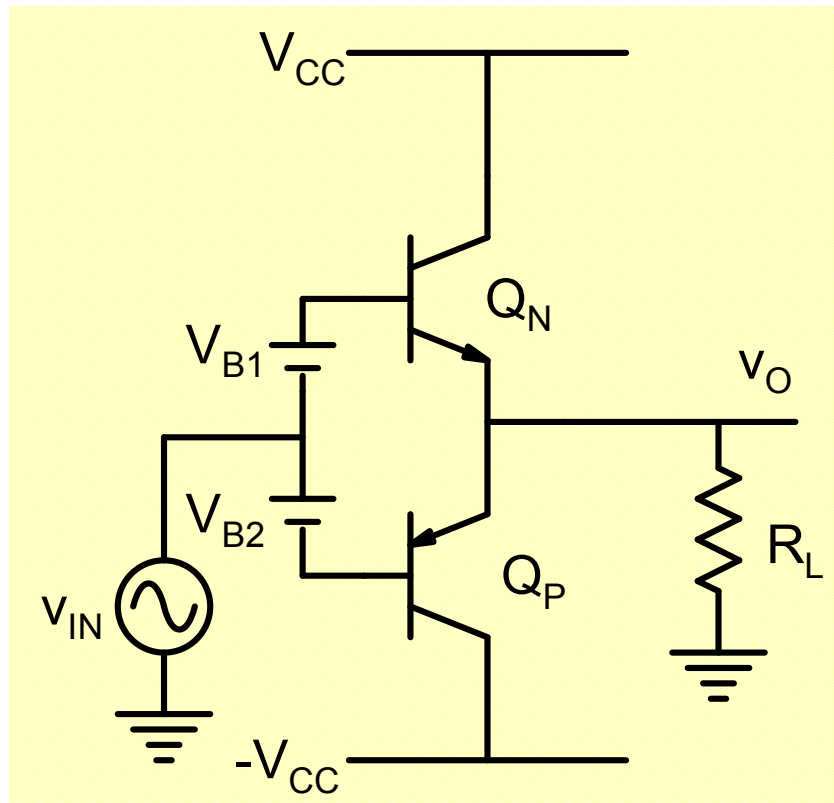

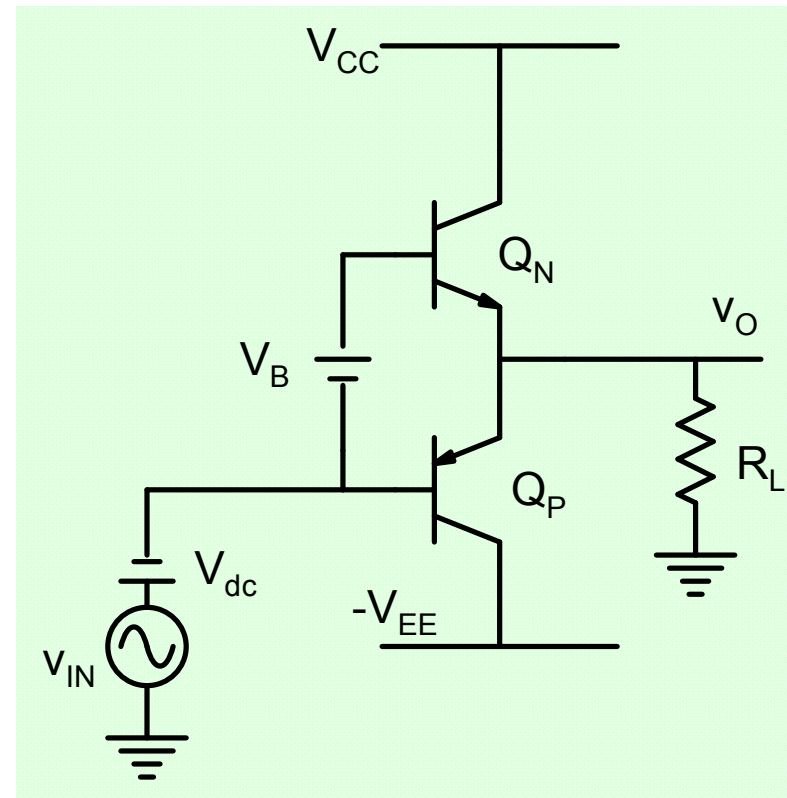
$$V_{BN} - V_{BP} \cong 0.65 + 0.65 = 1.3V$$







$$V_{dc} \sim 0.65V; V_B \sim 1.3V$$

Solution

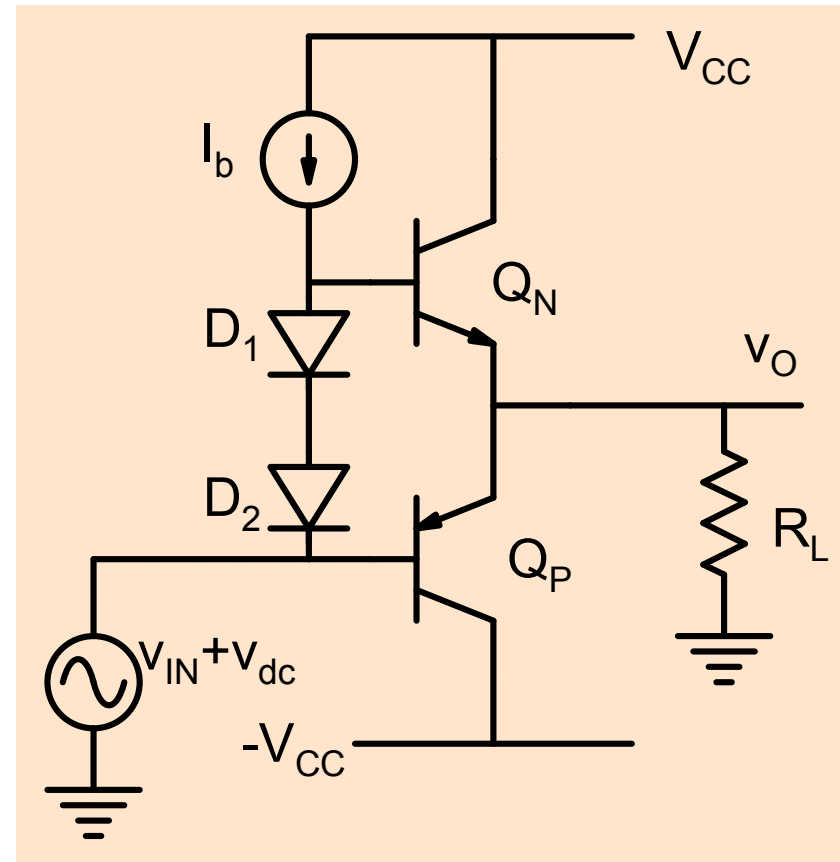
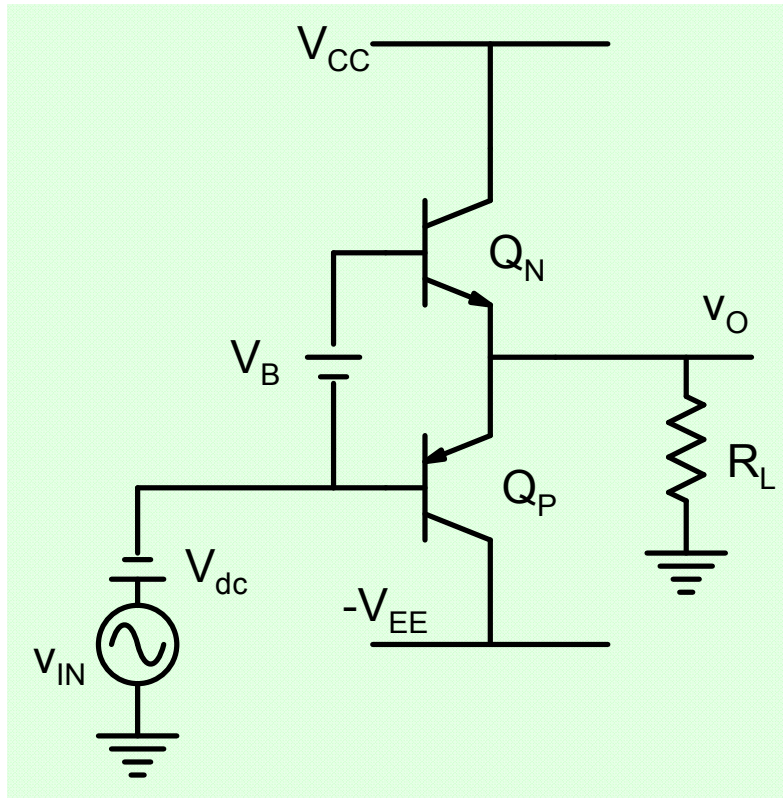

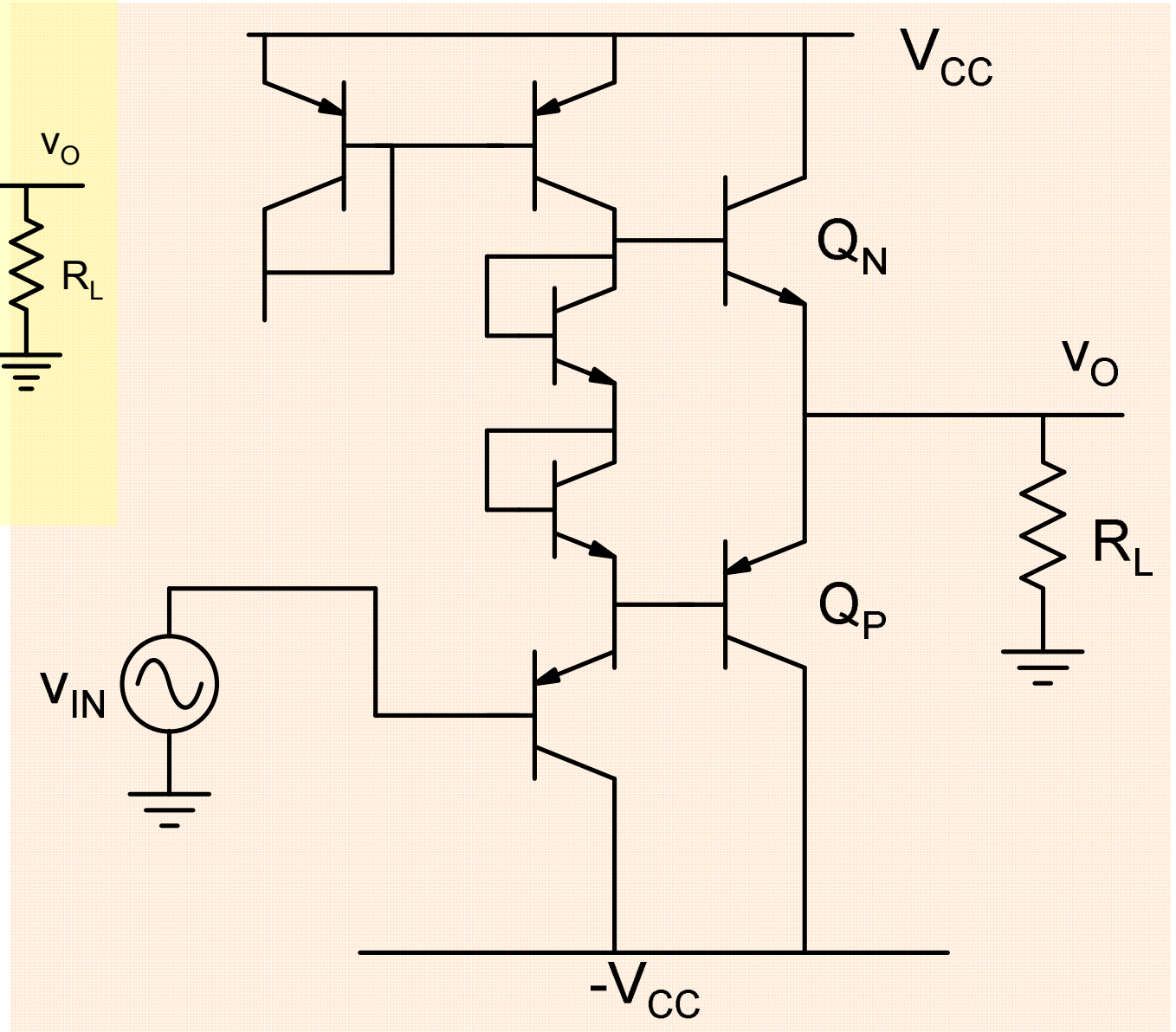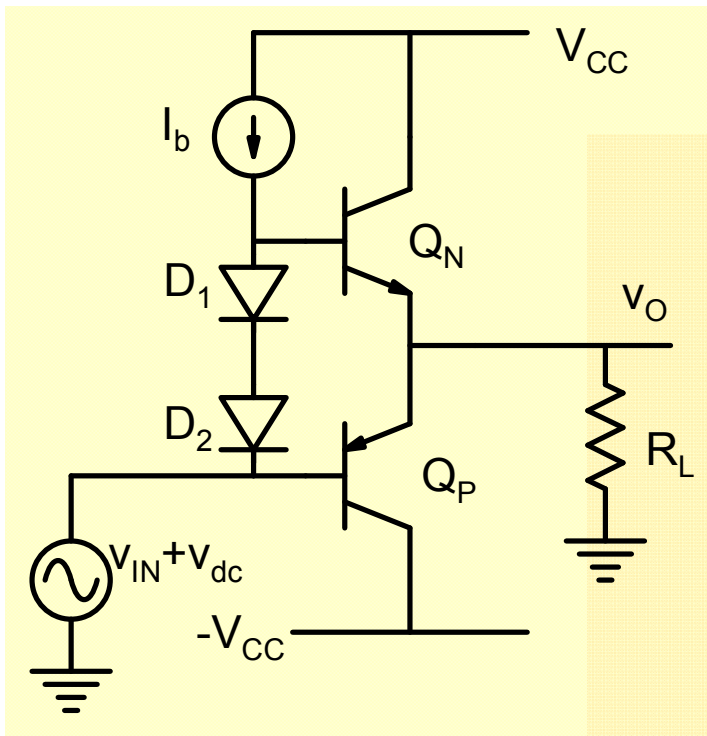
$$V_{BN} - V_{BP} \cong 0.65 + 0.65 = 1.3V$$



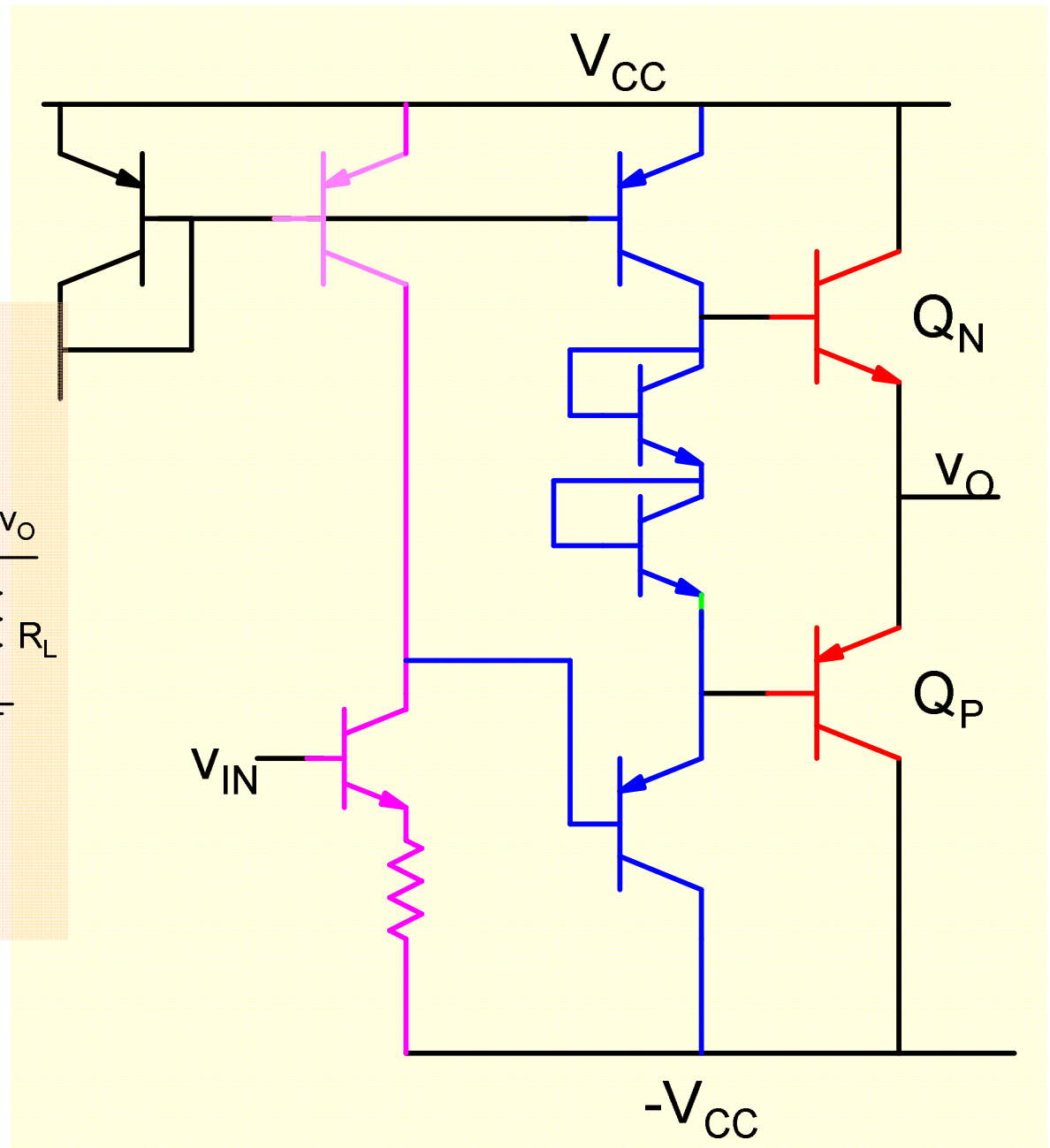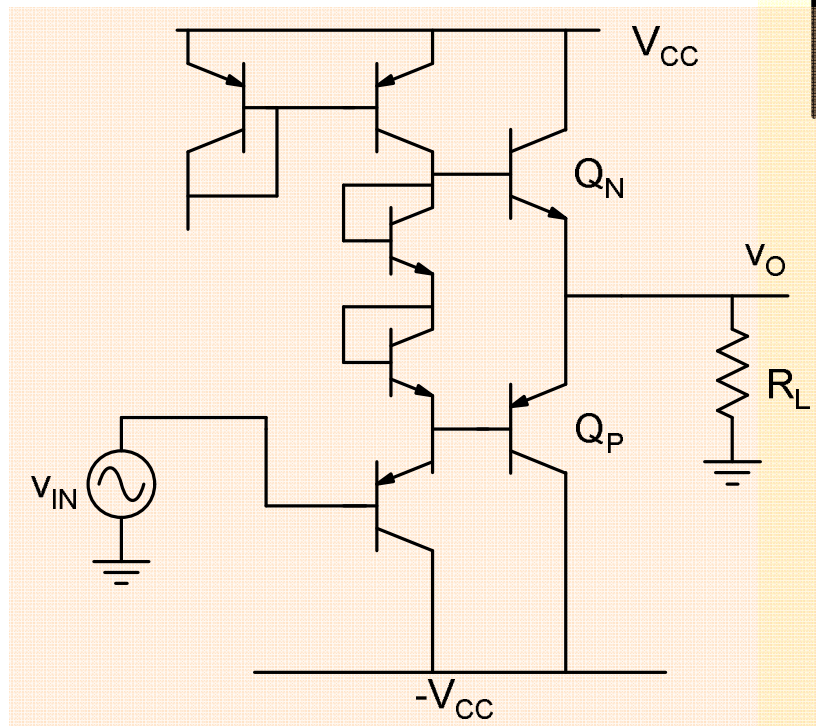

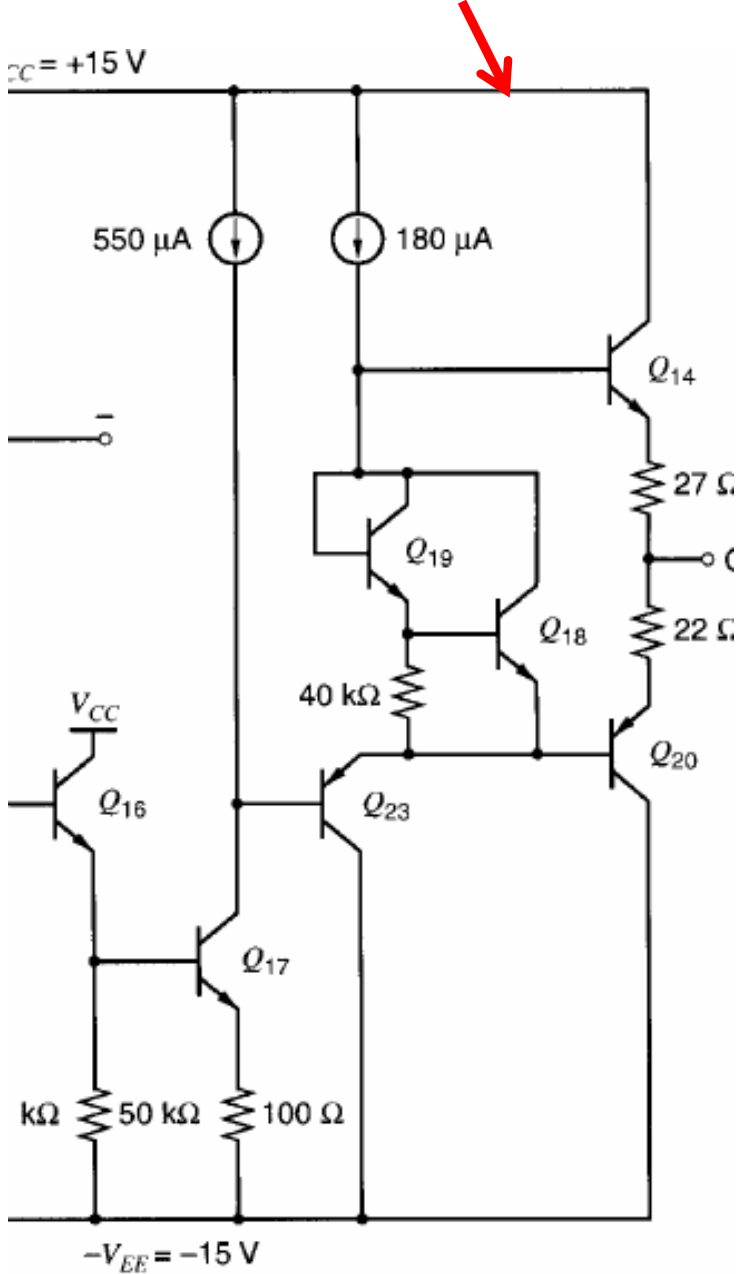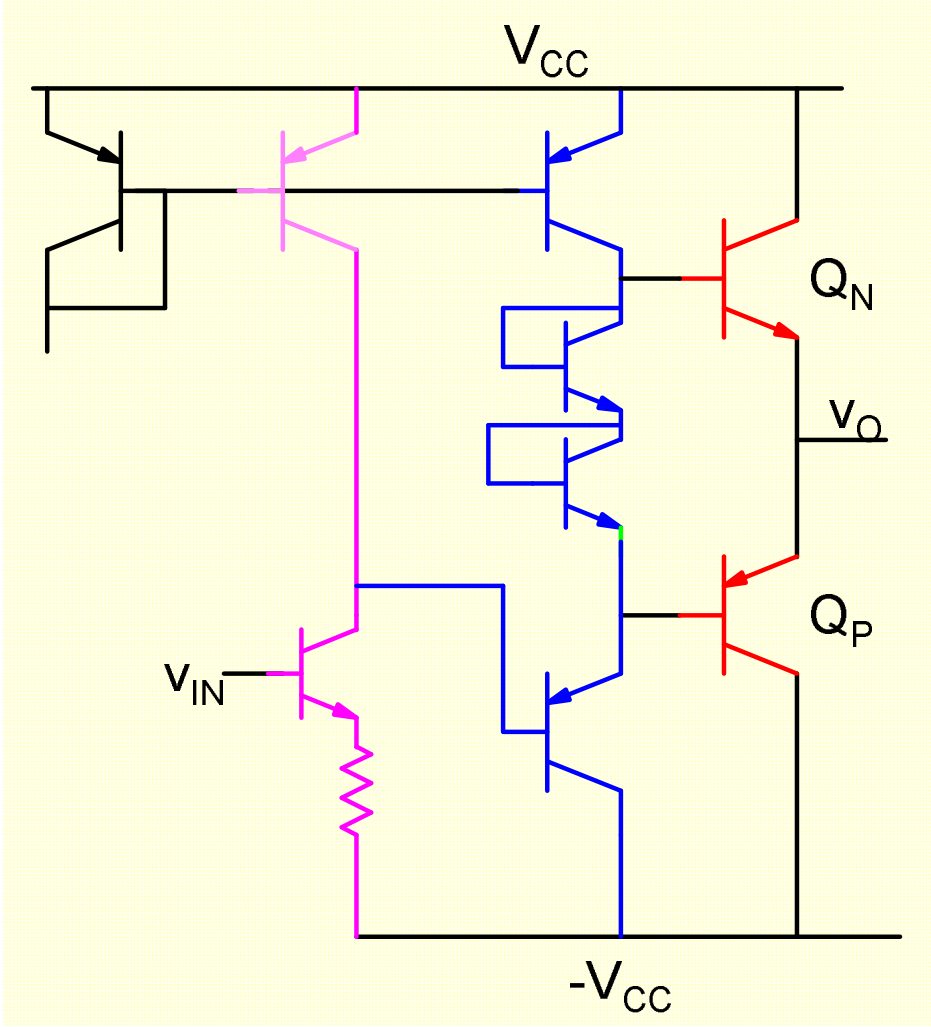Simplified 741 opamp schematic from Gray & Meyer



Simplified 741 opamp schematic from Gray & Meyer

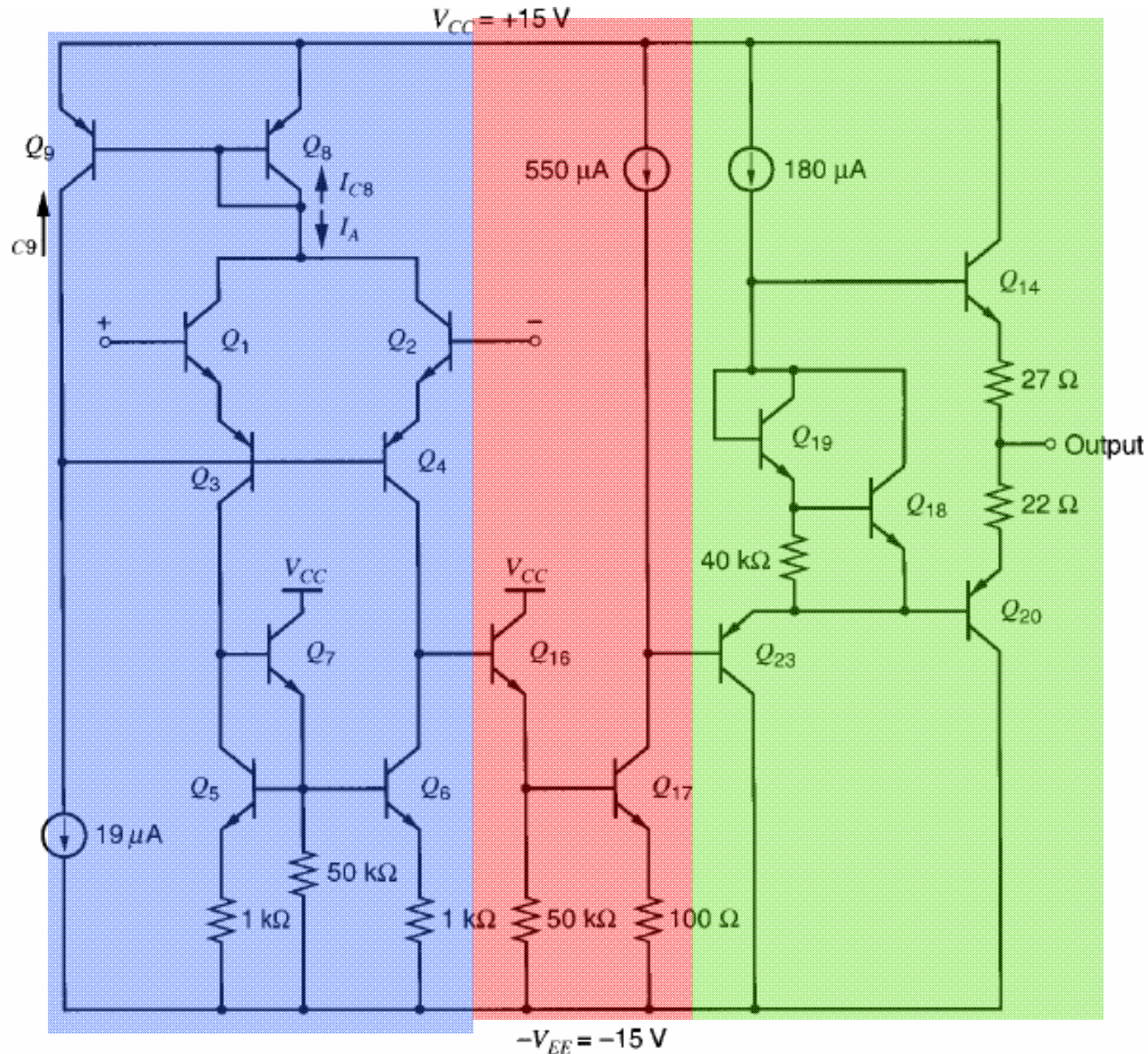


Figure 6.35 Simplified schematic of the 741 with idealized biasing current sources.

Summary

