

EE210: Microelectronics-I

Lecture-33: Operational Amplifiers_1

<https://youtu.be/ehekdOHOIZ0>

B. Mazhari
Dept. of EE, IIT Kanpur

BJT Operational Amplifier

- ❑ Simple BJT Opamp
- ❑ Compensation
- ❑ Buffer and Non-inverting amplifier


Specifications:

$$A_V \sim 10^3 ; R_{in} \sim 100K\Omega ; R_O = 100\Omega$$

Supply : $\pm 12V$


In the simple opamp, no active load would be used

General architecture:

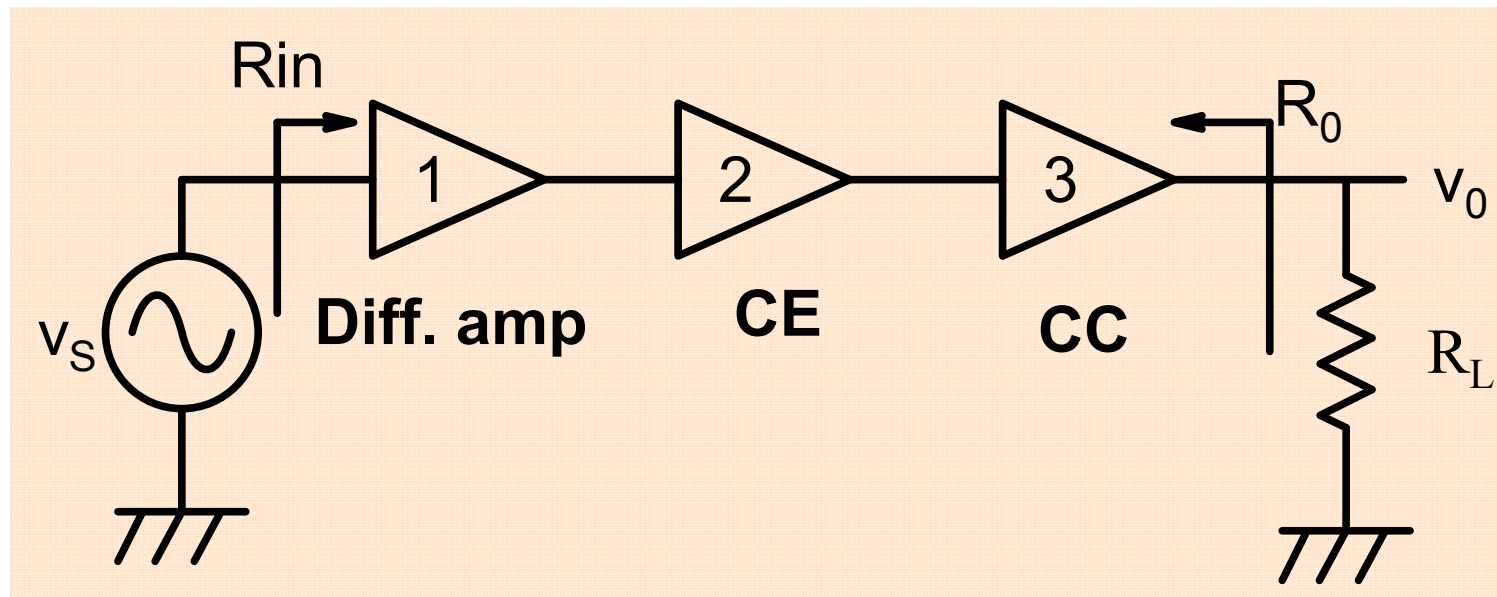

Input Stage
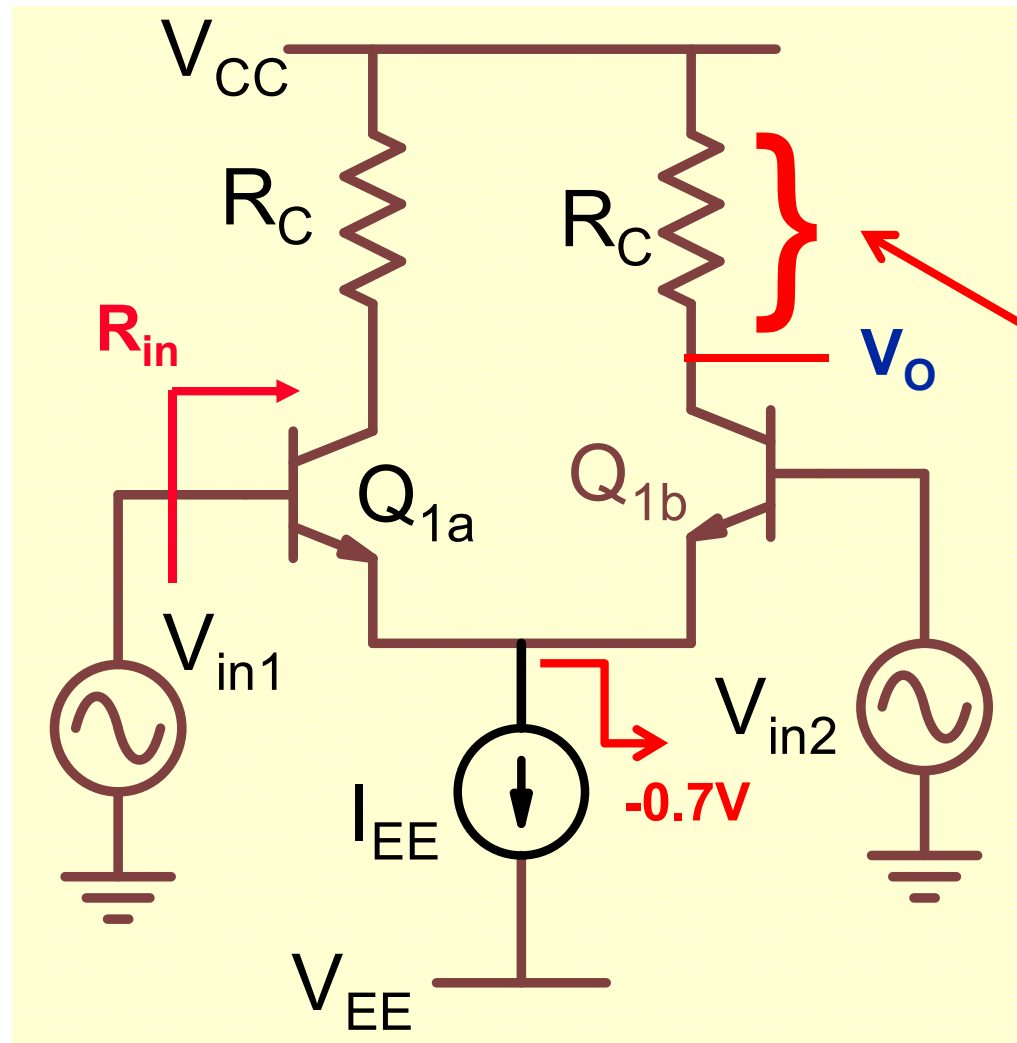
$$A_V \sim 10^3 ; R_{in} \sim 100K\Omega ; R_O = 100\Omega$$




$$R_{in} = 2r_{\pi} = 2 \frac{V_T}{I_{CQ1}} \beta = 10^5 \Omega$$

$$I_{EE} = 2I_{CQ1} = 0.1mA$$

$$R_C = ?$$
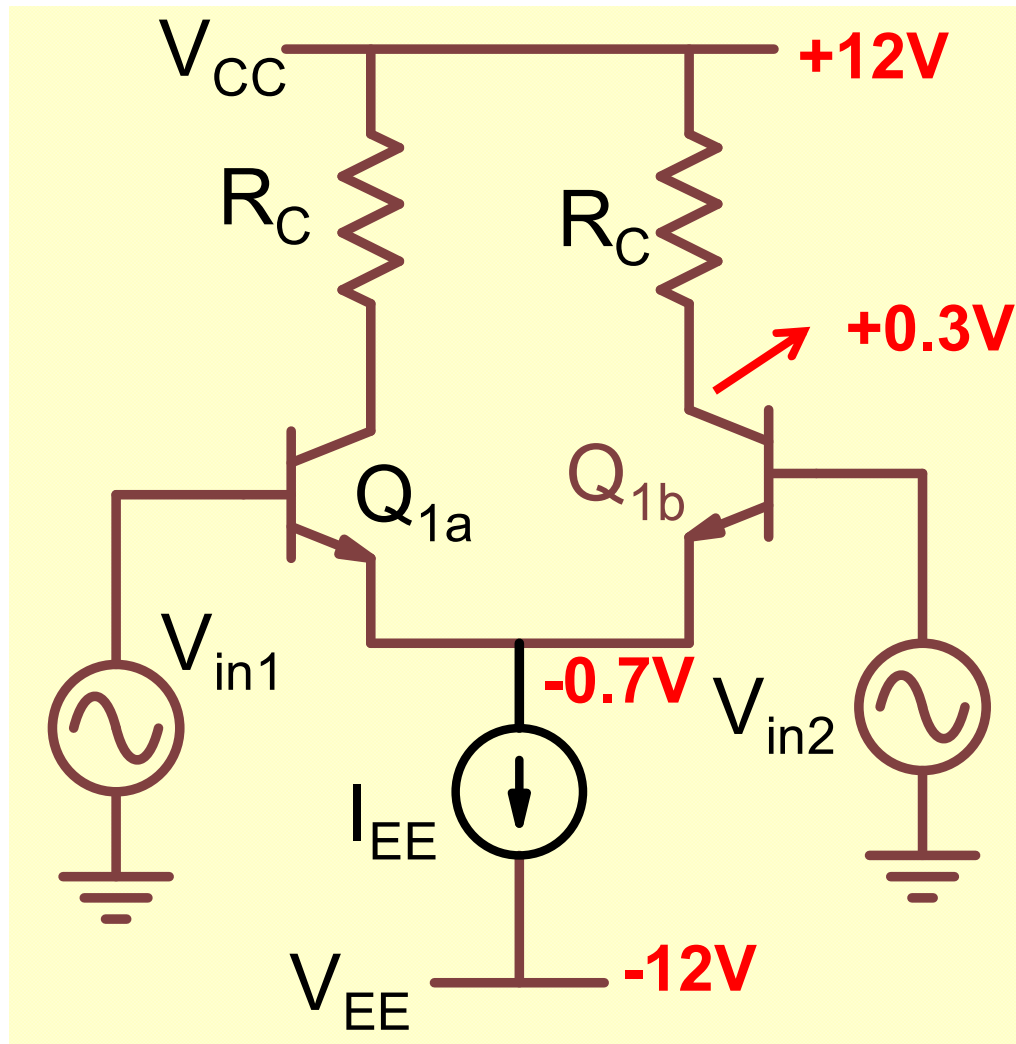
$$A_{dm} = 0.5g_m R_C = 0.5 \frac{I_{CQ1} R_C}{V_T}$$



$$I_{EE} = 2I_{CQ1} = 0.1mA$$


$$A_{V1} = 0.5 \frac{I_{CQ1} R_C}{V_T}$$

$$\text{Say } V_{CE1} = 1V$$


$$A_{V1} = 227$$

$$R_C = \frac{V_{CC} - V_{C1b}}{I_{CQ1}} = 227K$$


Differential Amplifier

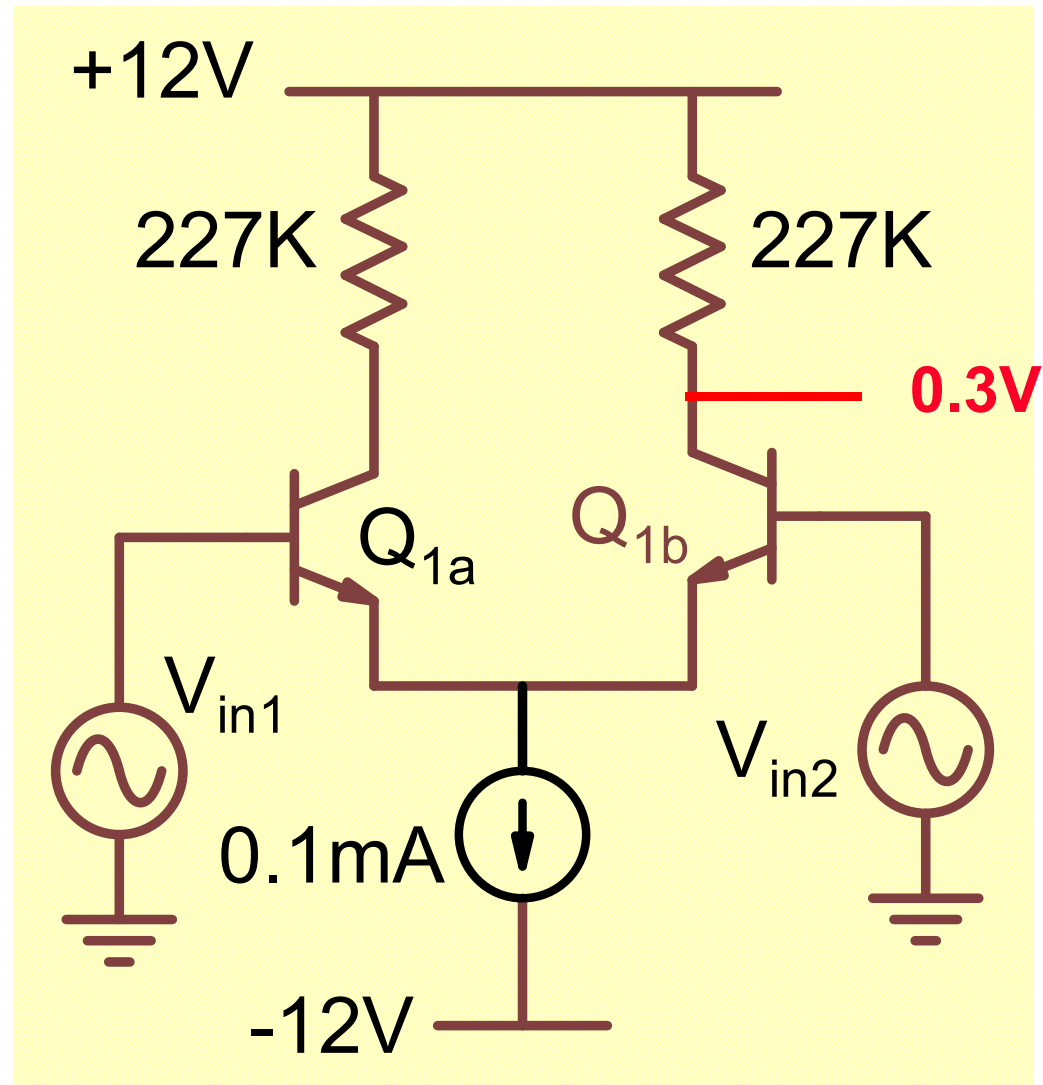


CE Gain Stage

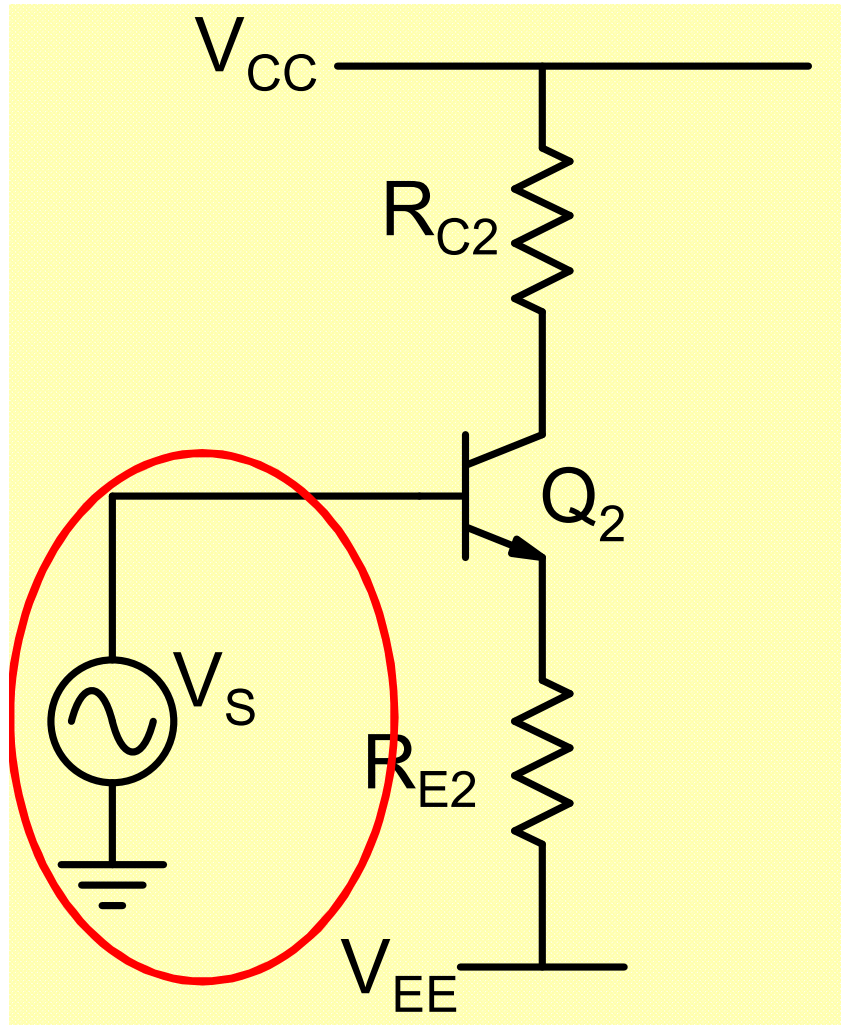

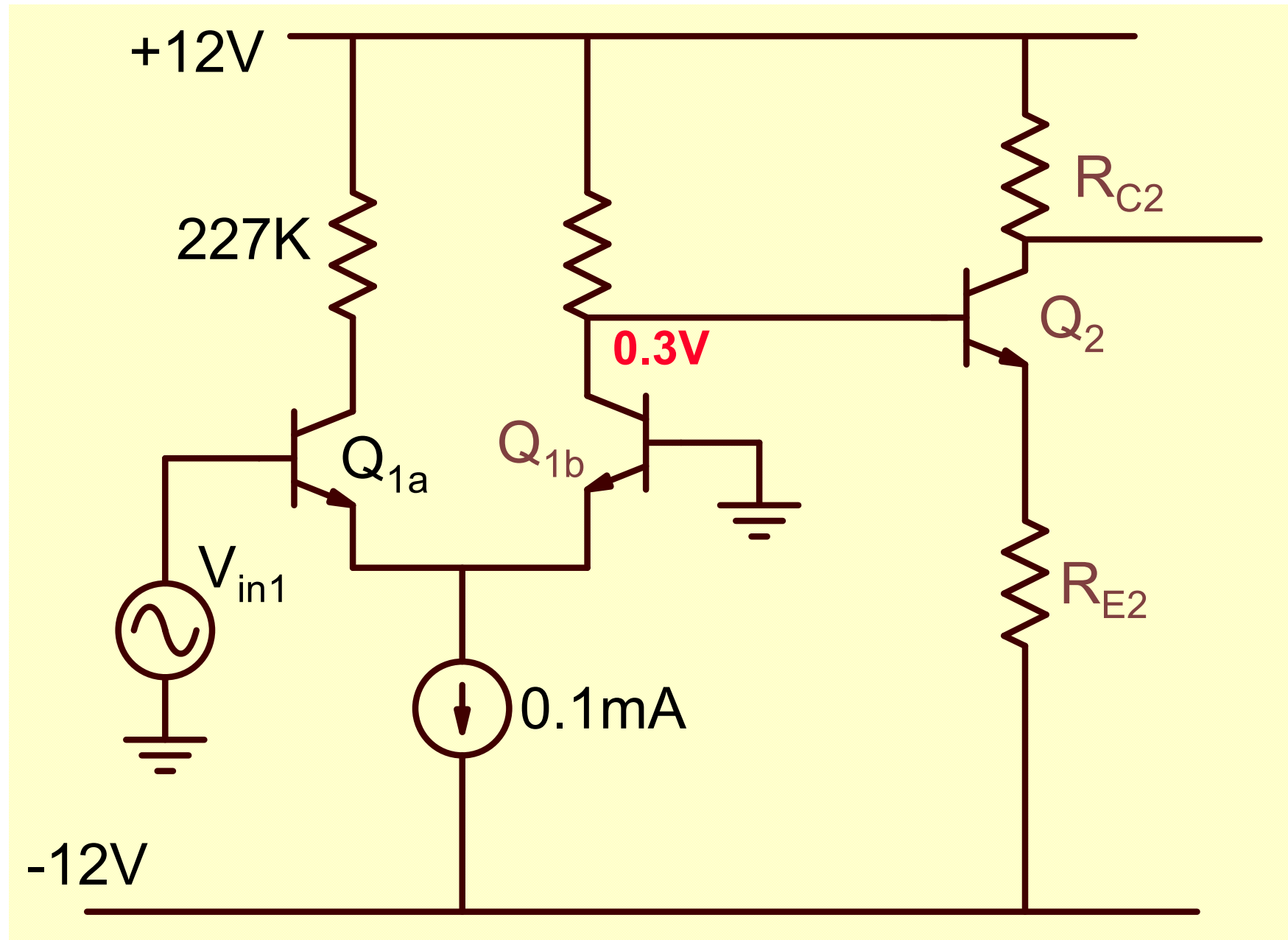We have to see how to interface it to previous stage



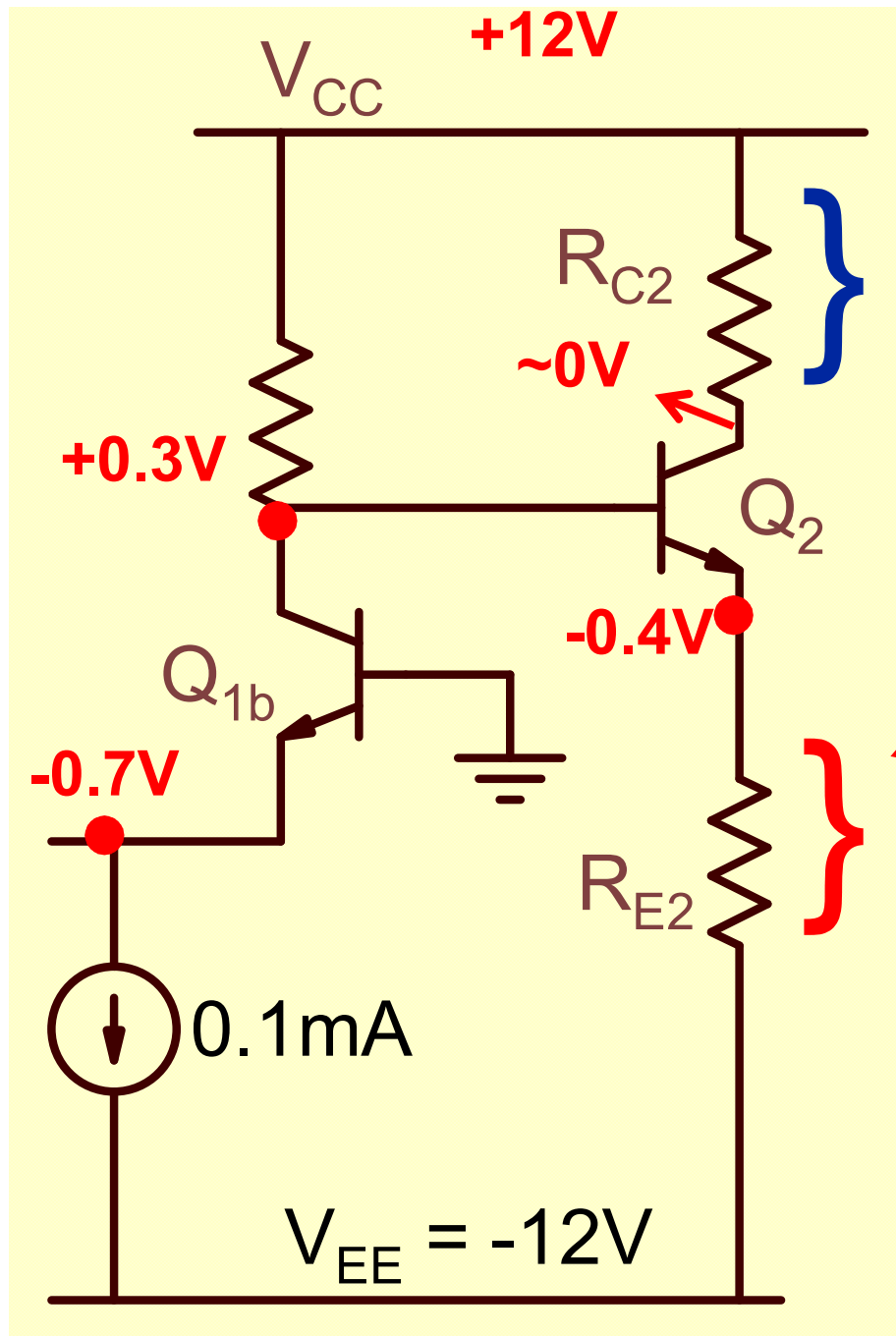


$$A_{V2} = \frac{g_{m2} \times R_{C2}}{1 + g_{m2} \times R_{E2}} \cong \frac{R_{C2}}{R_{E2}}$$


$$A_{V2} \cong \frac{I_{CQ2} \times R_{C2}}{I_{CQ2} \times R_{E2}} = \frac{\Delta V_C}{\Delta V_E}$$


$$A_{V2} \sim \frac{12}{11.6}$$


Negligible Gain !

PNP Gain Stage:

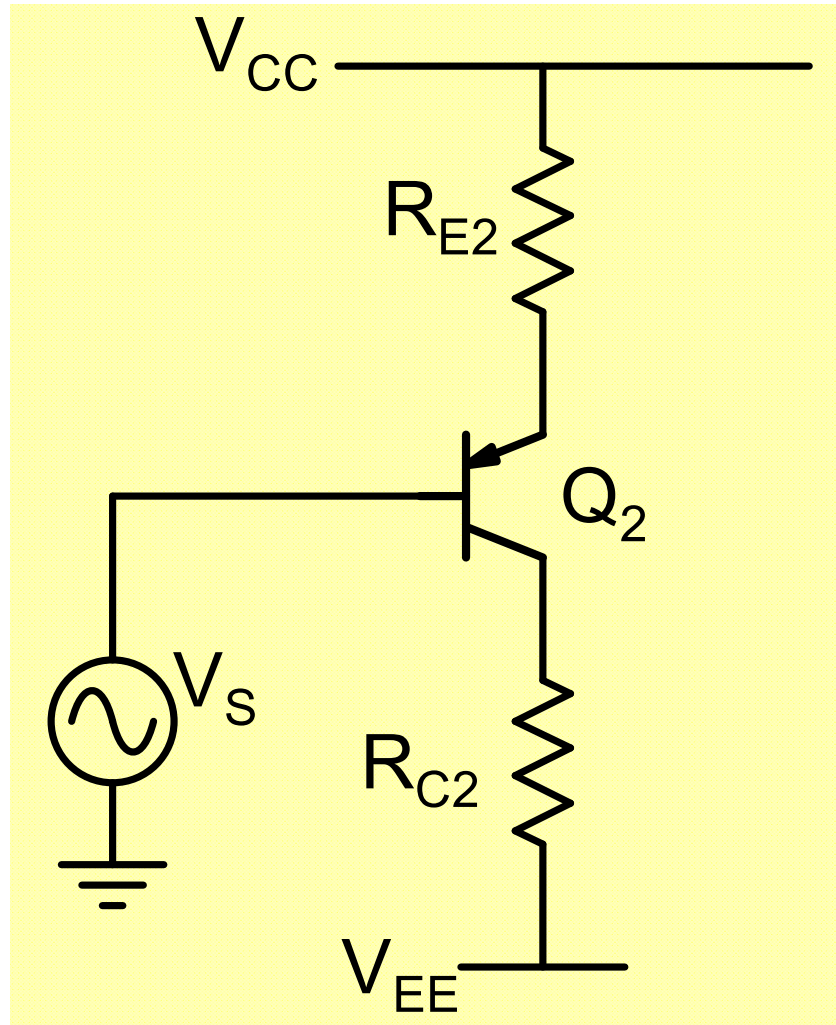

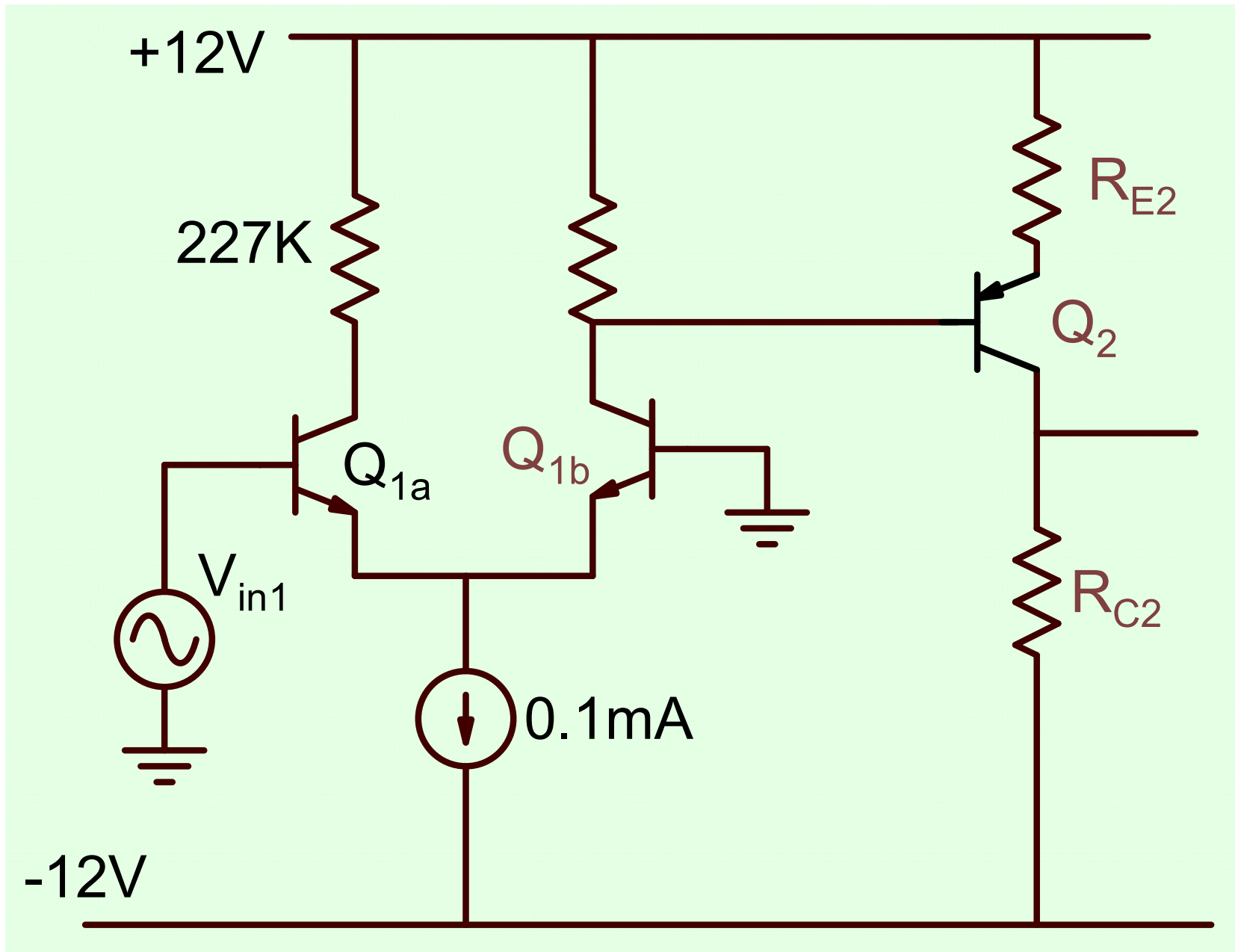

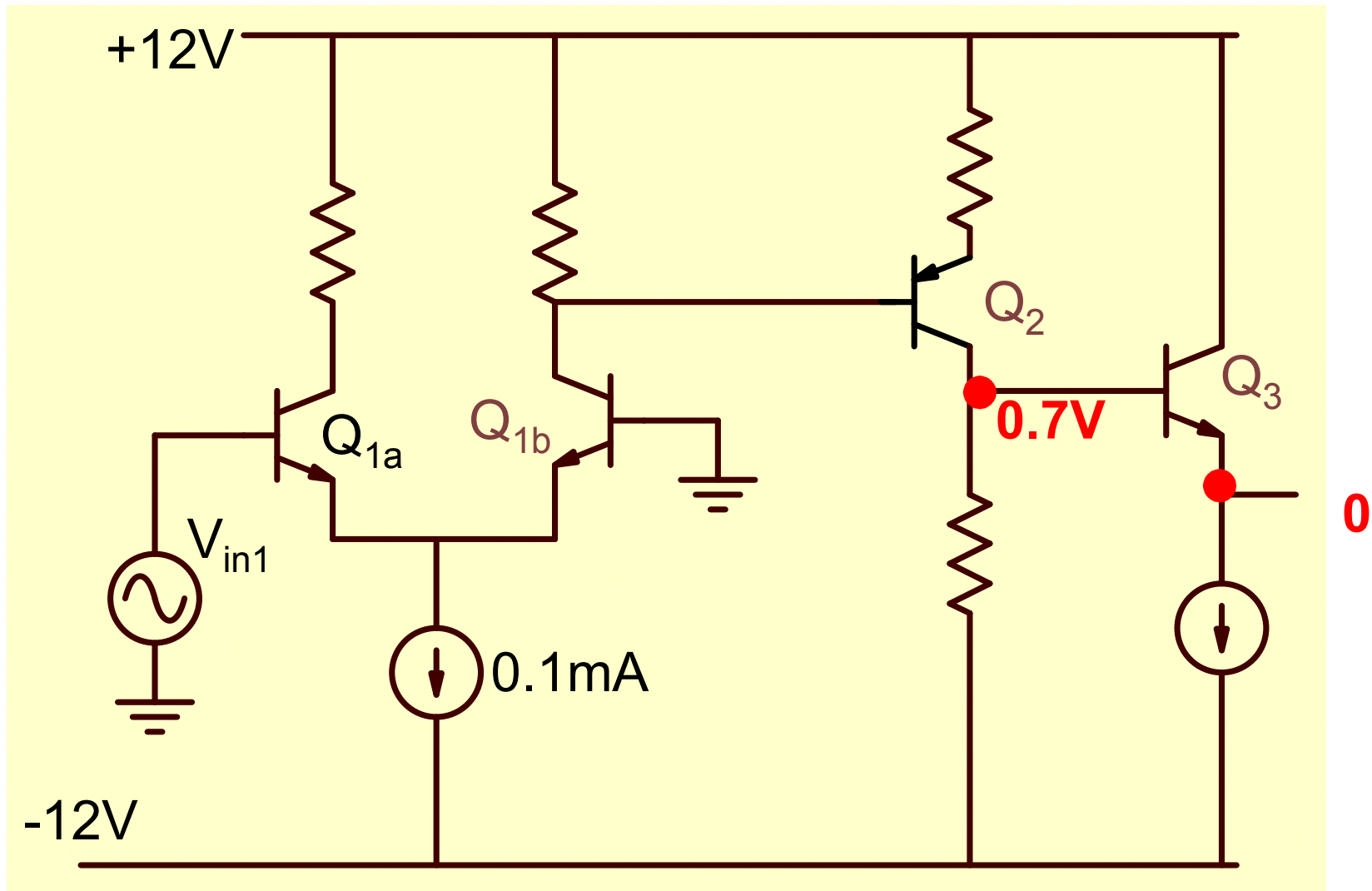

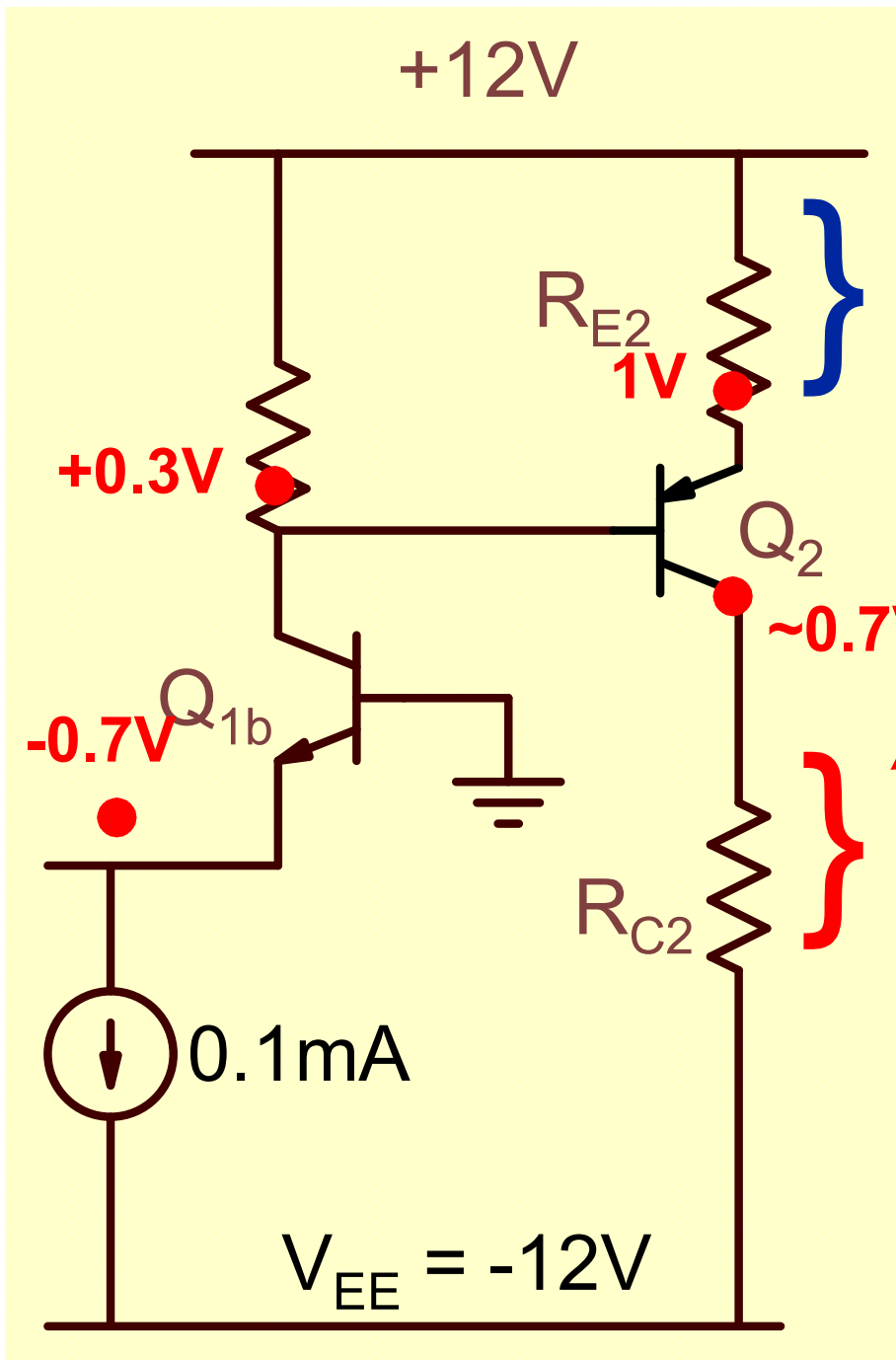


$$A_{V2} \cong \frac{R_{C2}}{R_{E2}} = \frac{I_{CQ2} \times R_{C2}}{I_{CQ2} \times R_{E2}}$$

~~$$A_{V2} \cong \frac{\Delta V_C}{\Delta V_E}$$~~

$$A_{V2} \sim \frac{12.7}{11}$$


Gain negligible again

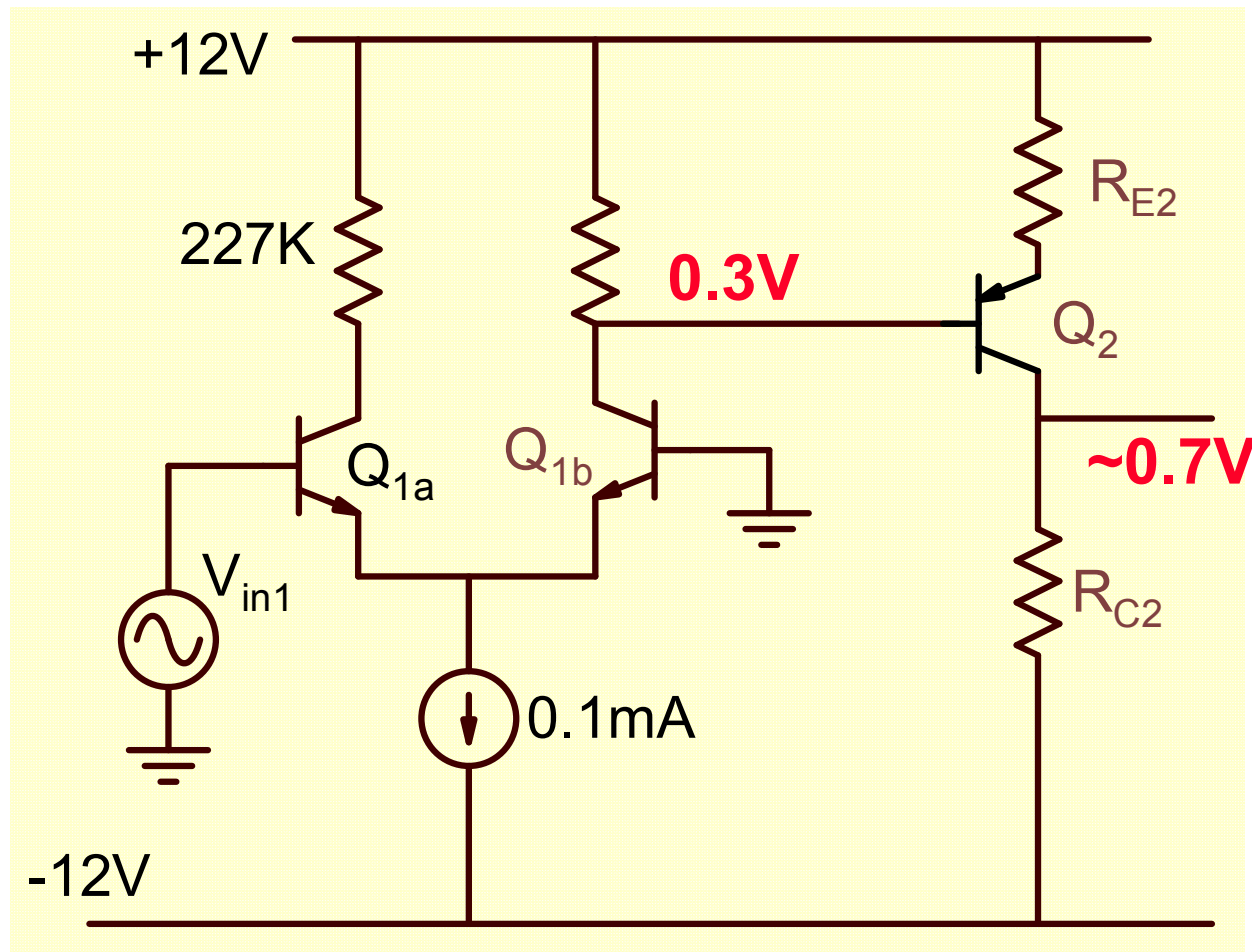With present first stage design, gain of second stage is still negligible



$$A_{V2} = \frac{R_{C2}}{R_{E2}} = \sim 1$$

Re-look at design of first stage

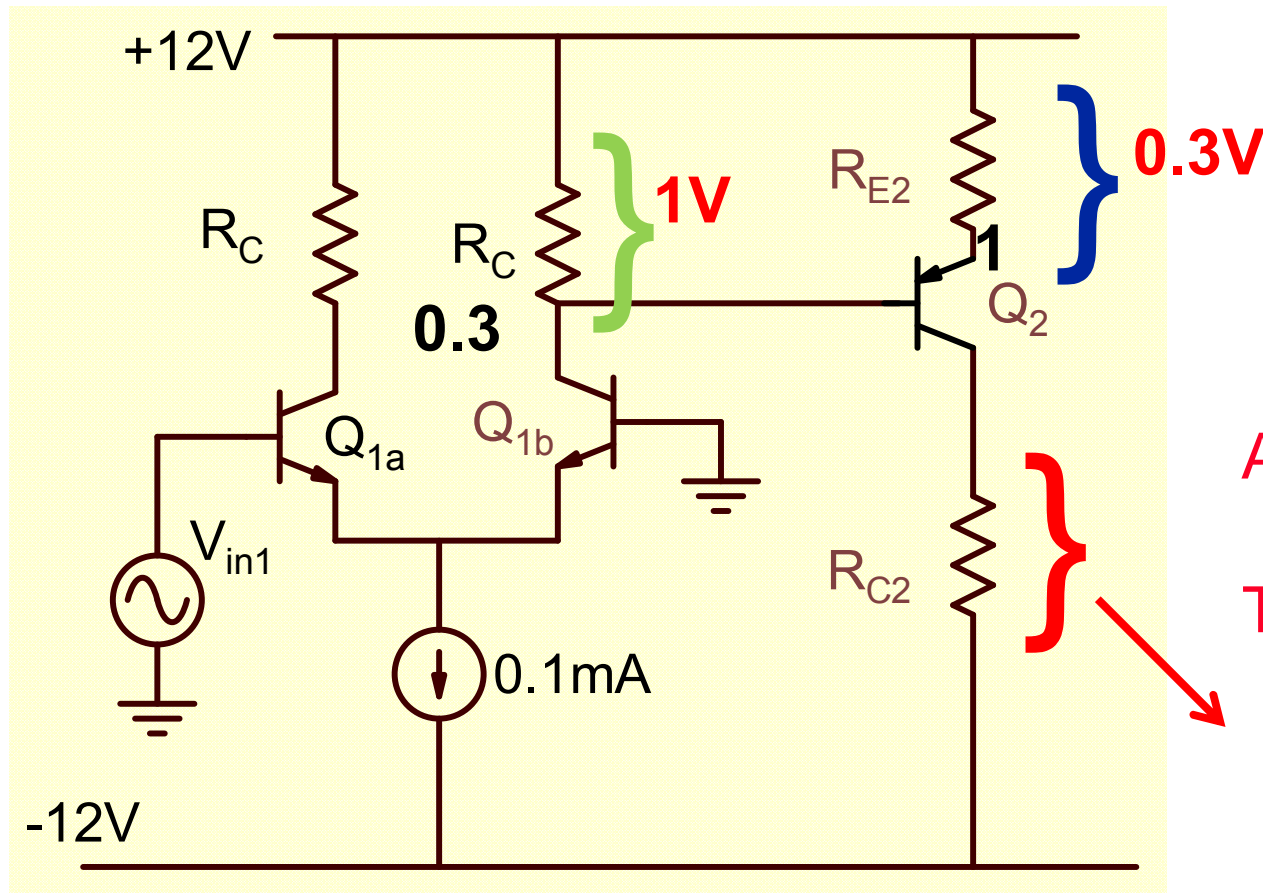

$$A_{V1} = 0.5 \frac{\Delta V_{C1}}{V_T}$$

$$A_{V2} = \frac{R_{C2}}{R_{E2}} = \frac{\Delta V_{C2}}{\Delta V_{E2}}$$

Assuming no loading :

Total gain: $A_{V1} \times A_{V2}$

Constant $\sim 12.7V$


$$\text{Earlier } A_V = \left(0.5 \frac{11.7}{V_T} \right) \times \left(\frac{12.7}{11} \right)$$

$$\sim 225 \times 1.15 = 260$$

$$\text{Now } A_V = \left(0.5 \frac{1}{V_T} \right) \times \left(\frac{12.7}{0.3} \right)$$

$$\sim 19.2 \times 42.3 = 814$$

For $V_{C1b} = 11V$ choice:

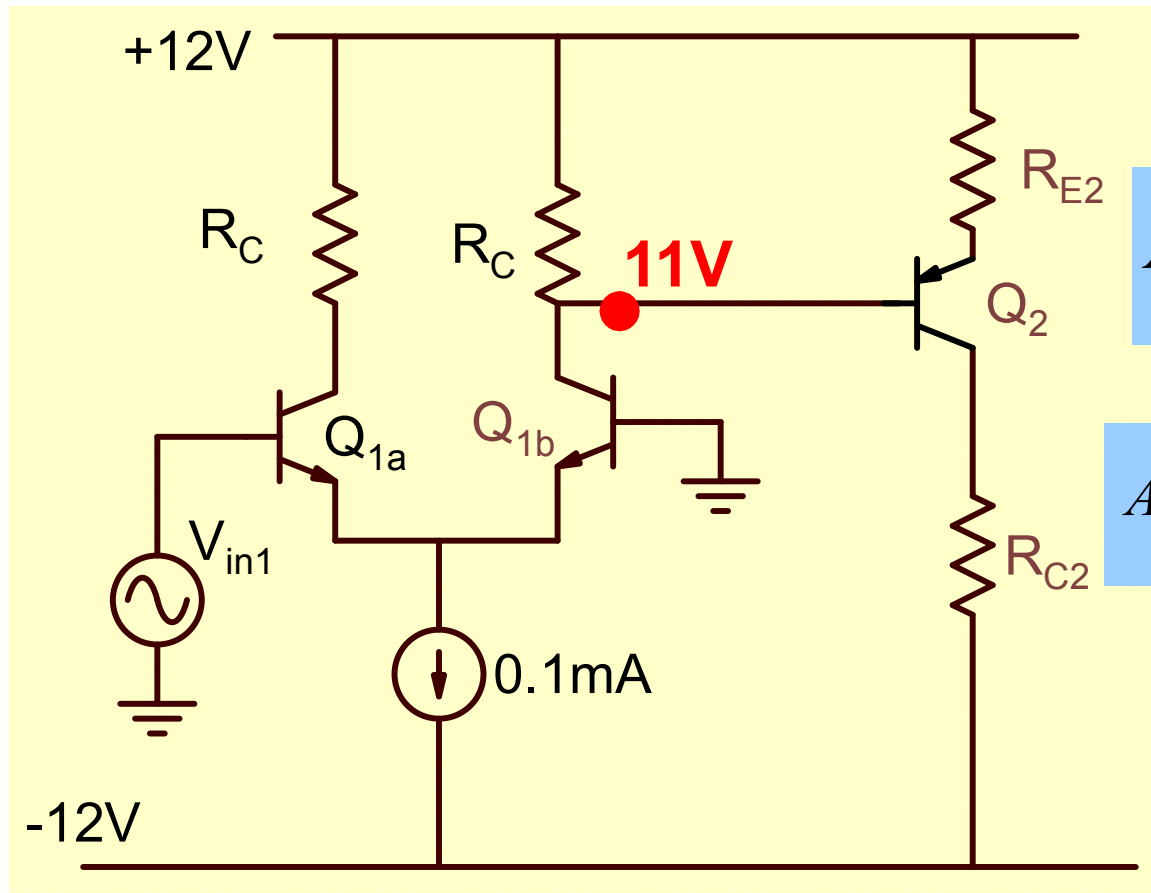


$$A_{V1} = 0.5 \frac{V_{CC} - V_{C1b}}{V_T} = 19.2$$

$$A_{V2} = \frac{R_{C2}}{R_{E2}} = \frac{12.7}{11.3 - V_{C1b}} = 42.33$$

$$R_C = \frac{V_{CC} - V_{C1b}}{I_{CQ1}} = 20K\Omega$$

R_{E2} and R_{C2} ?

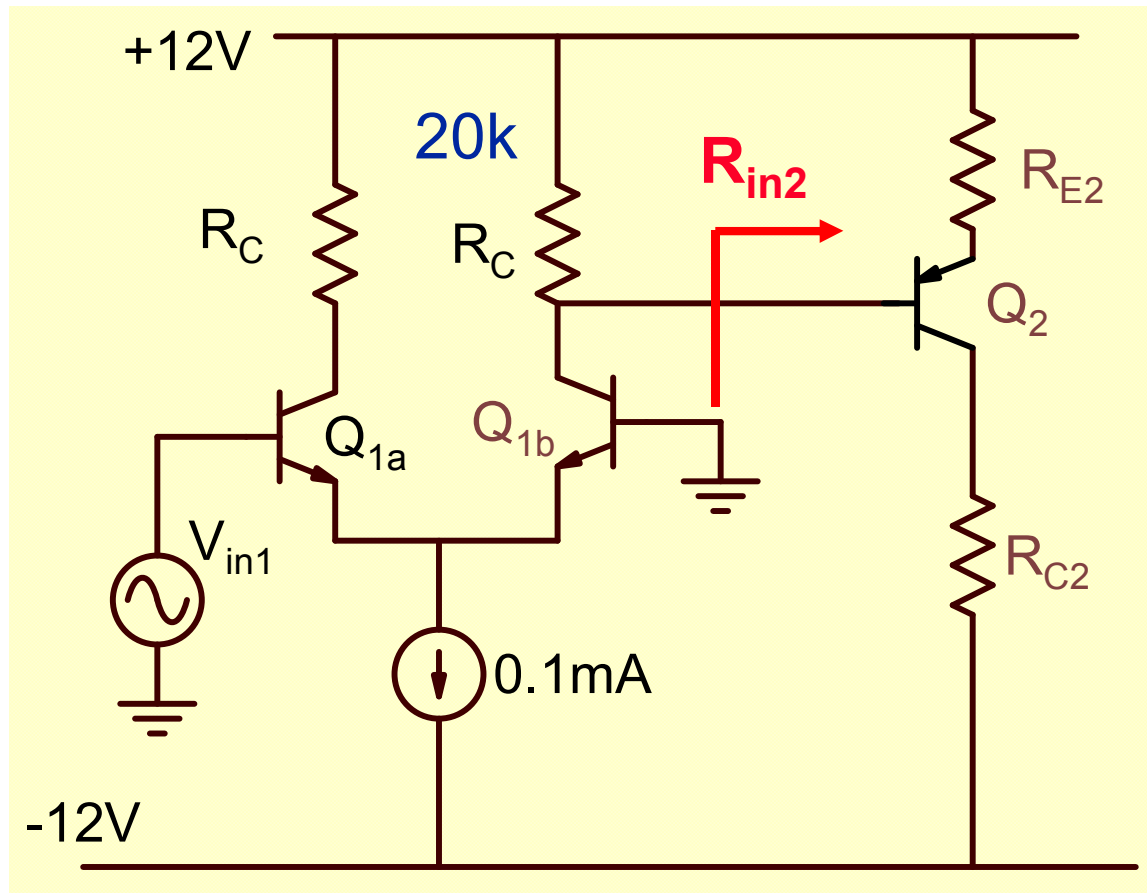

$$A_{V2} = \frac{R_{C2}}{R_{E2}} = \frac{12.7}{11.3 - V_{C1b}} = 42.33$$

$$R_{E2} = ?$$

$$R_{in2} \gg R_C$$

$$R_{in2} \cong \beta R_{E2} \gg R_C = 20K$$


$$R_{E2} \gg 200\Omega$$

$$\text{Choose } R_{E2} = 2K$$

$$\Rightarrow R_{C2} = 84.7K$$

Simulation Results
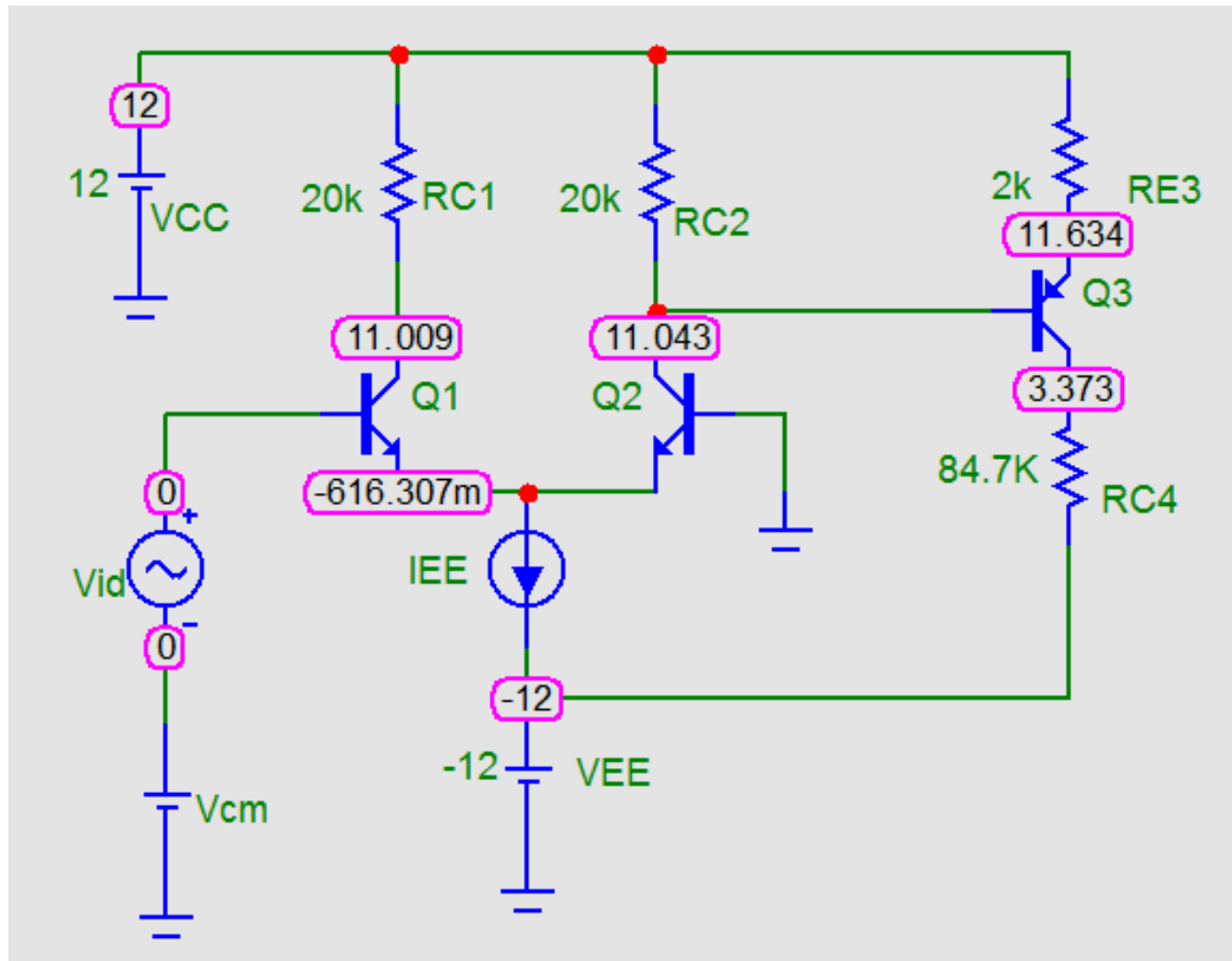
$$A_V \sim 10^3 ; R_{in} \sim 100K\Omega ; R_O = 100\Omega$$



$$A_V = 671$$


$$= 17.3 \times 38.8$$

$$R_{in1} = 116K\Omega$$

$$R_O = 82.9K\Omega$$

Expected Gain $\sim 19.2 \times 42.3 = 814$

Output Stage: CC Amplifier

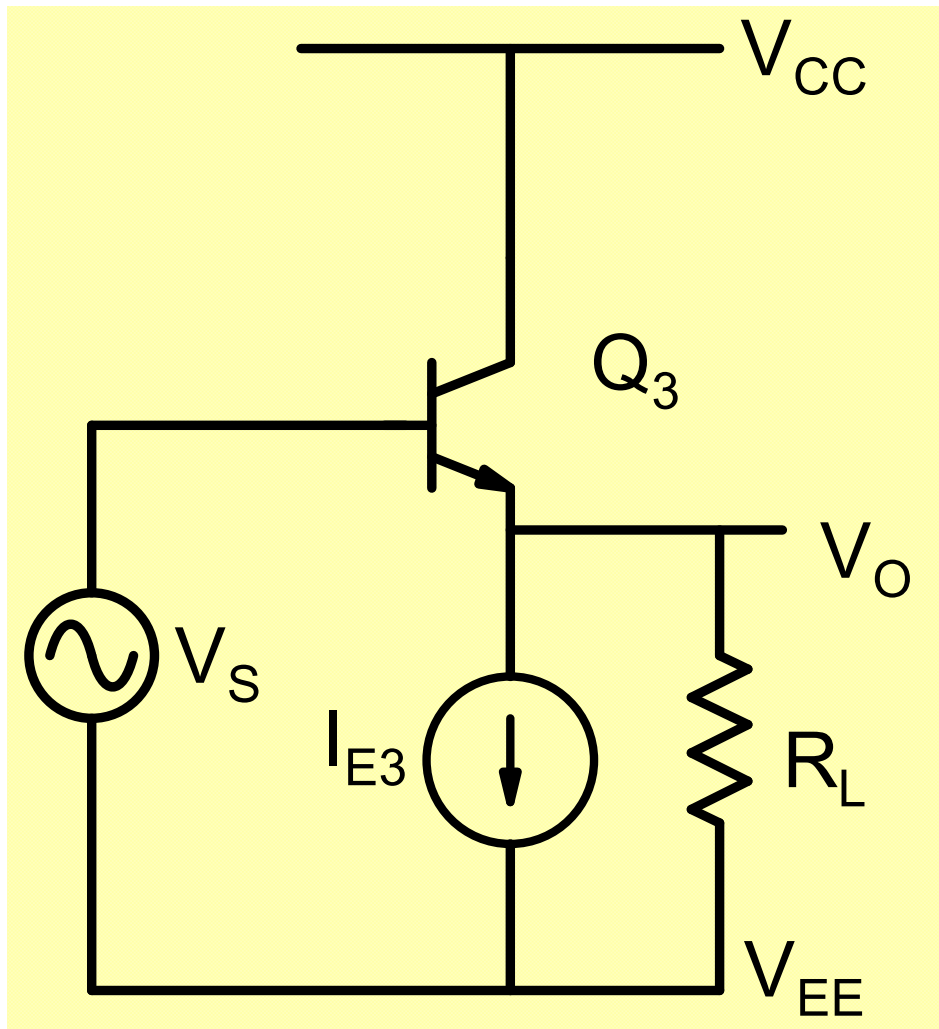

V_O is directly coupled so
 $V_O(\text{dc}) = 0\text{V}$


Current source bias gives better swing for a given bias current

Suppose $R_L \geq 1\text{K}\Omega$

For a $\pm 10\text{V}$ Swing $I_{E3} \geq 10\text{mA}$


Choose 10mA

Complete Amplifier

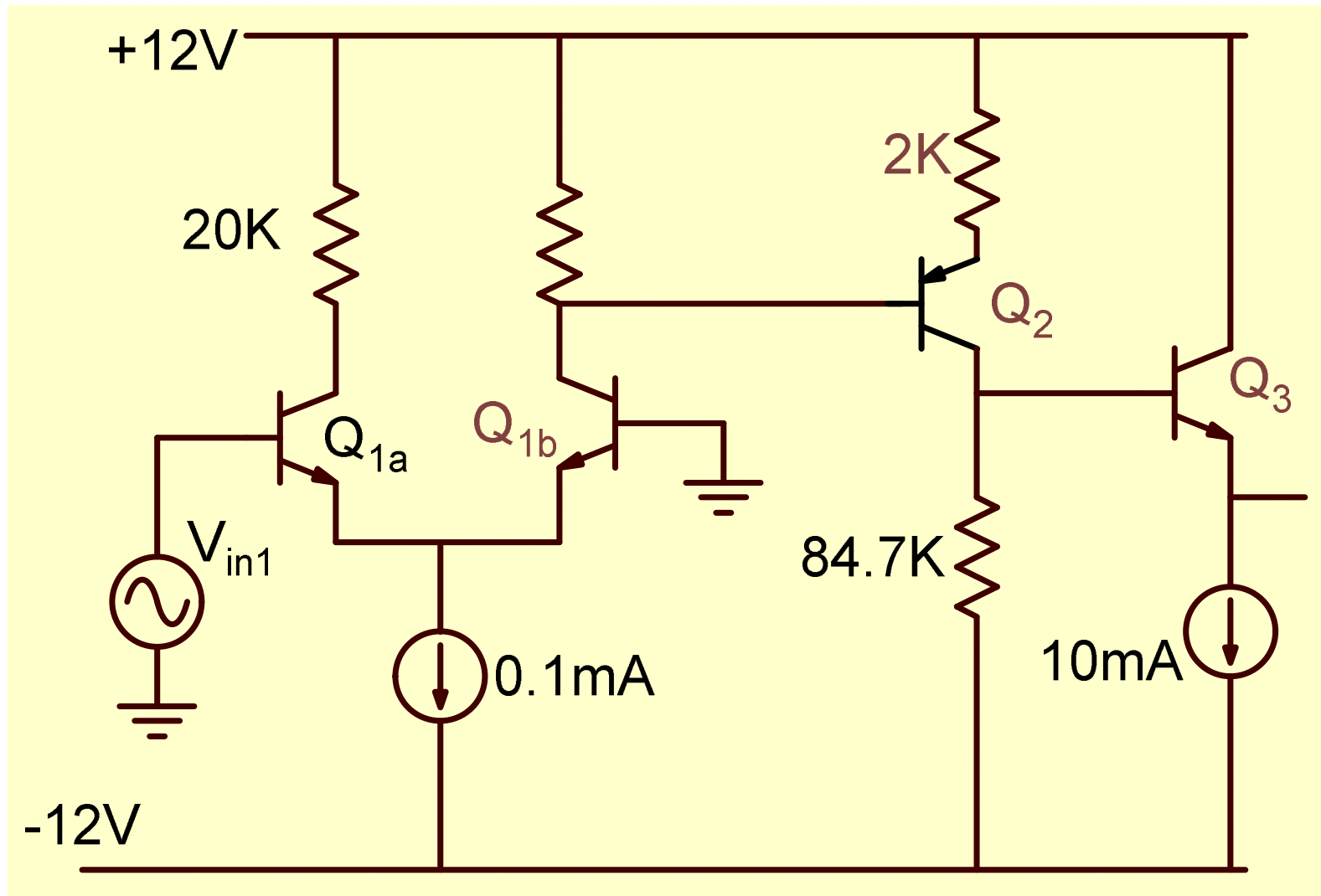

Simulation Results

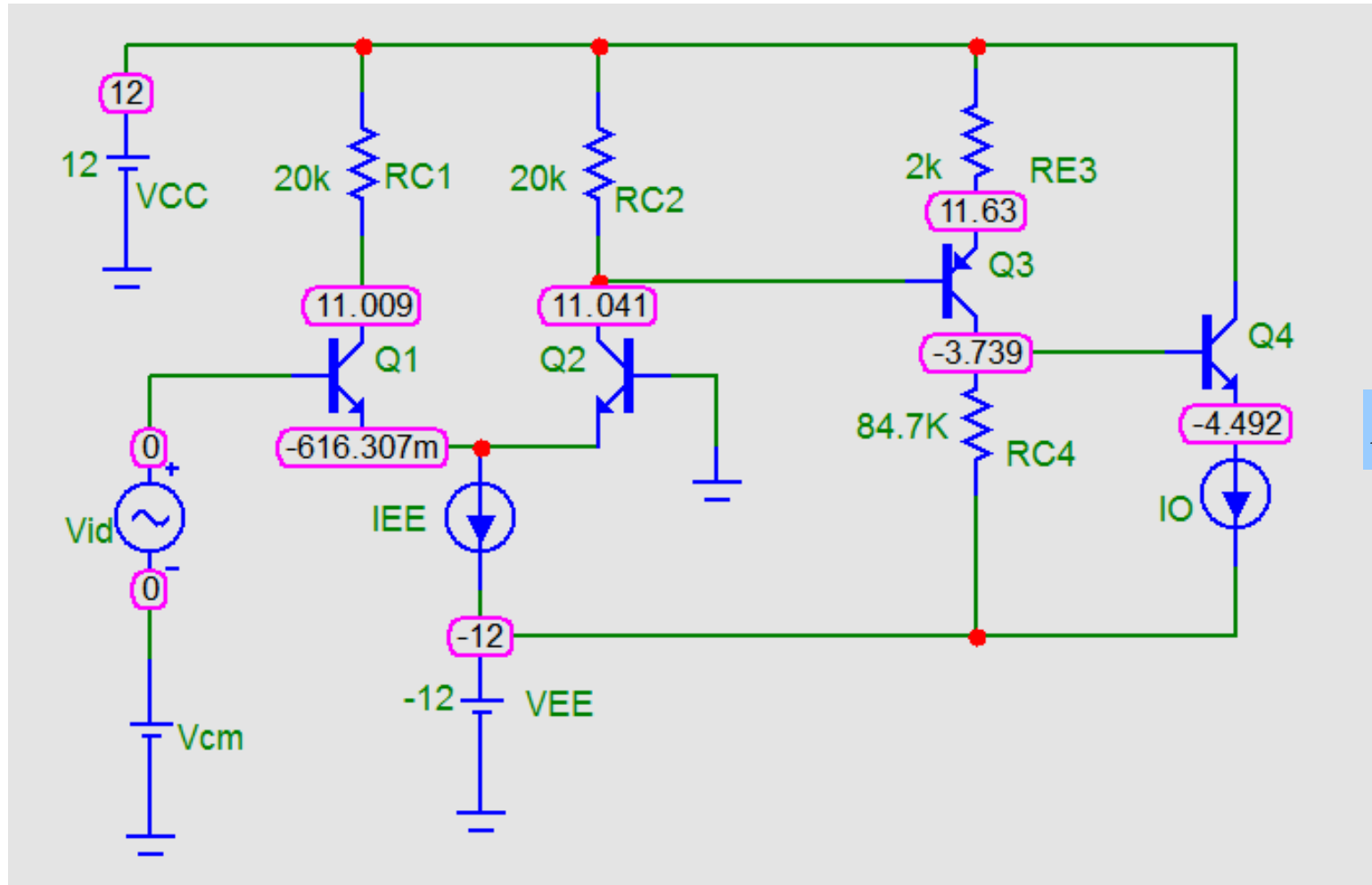
$$A_V \sim 10^3 ; R_{in} \sim 100K\Omega ; R_O = 100\Omega$$



$$A_V = 637$$

$$R_O = 673\Omega$$

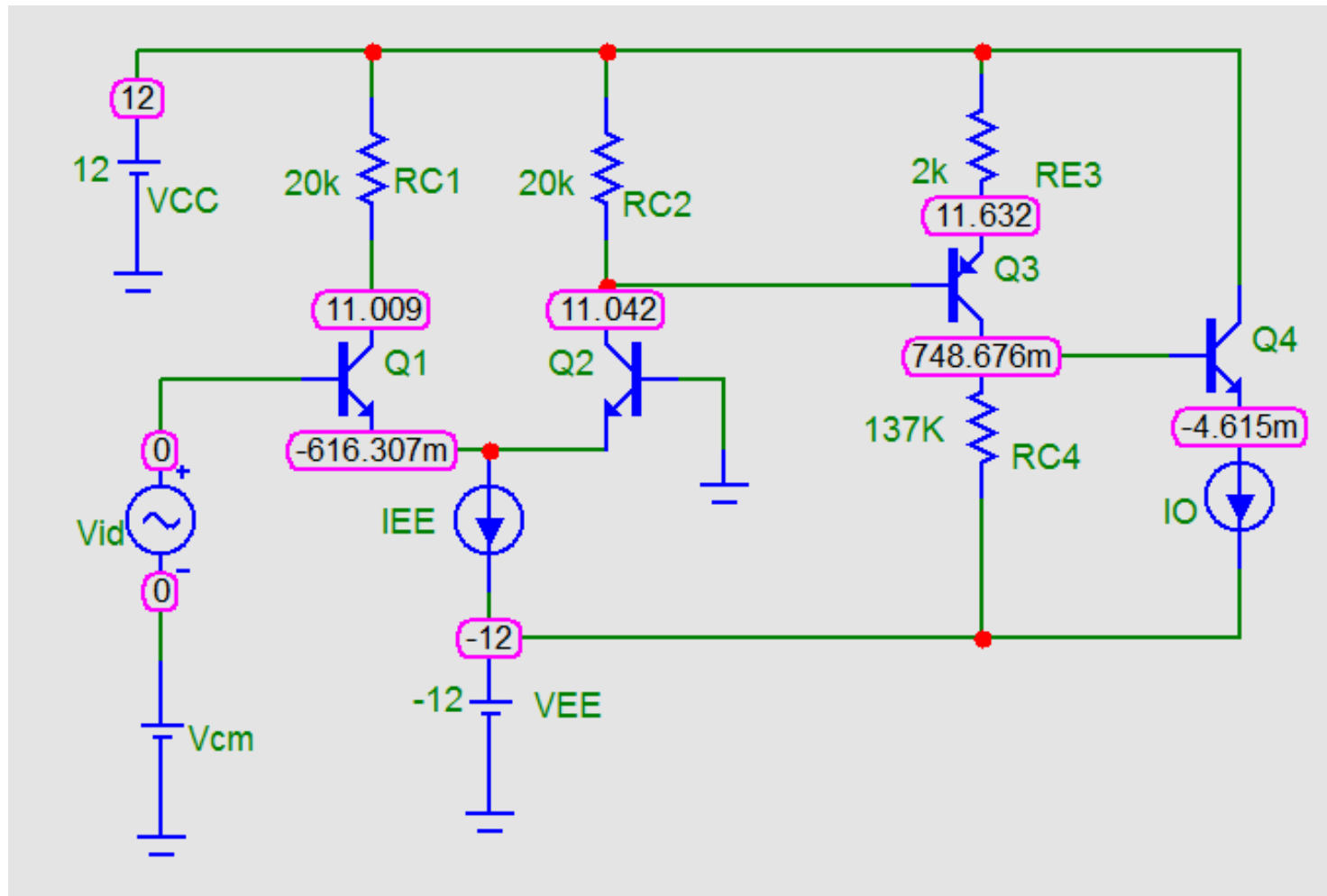
After tuning to obtain ~zero dc output voltage




$$A_V = 972.6$$

$$R_O = 1071\Omega$$

Present design

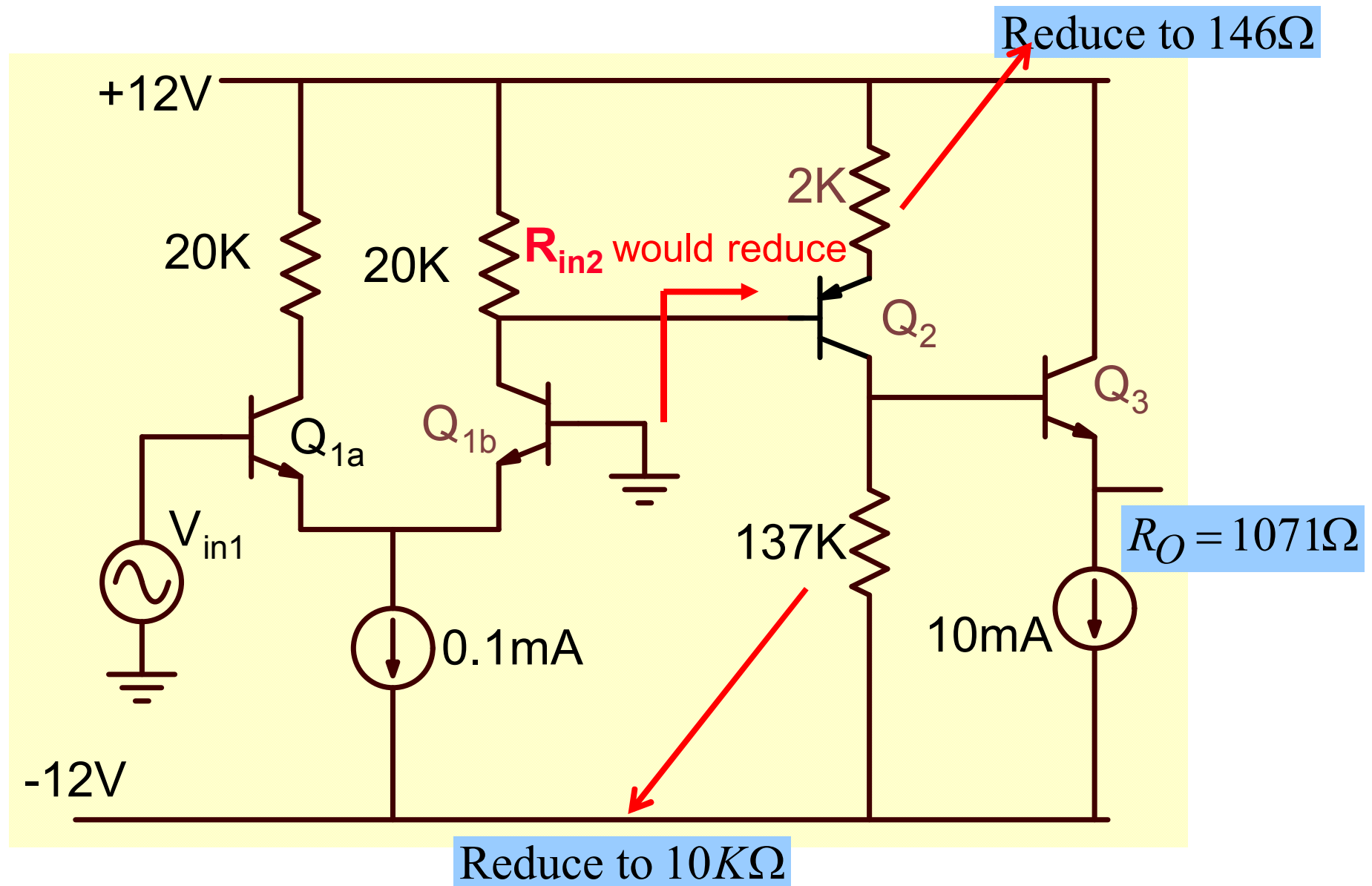

Simulation Results

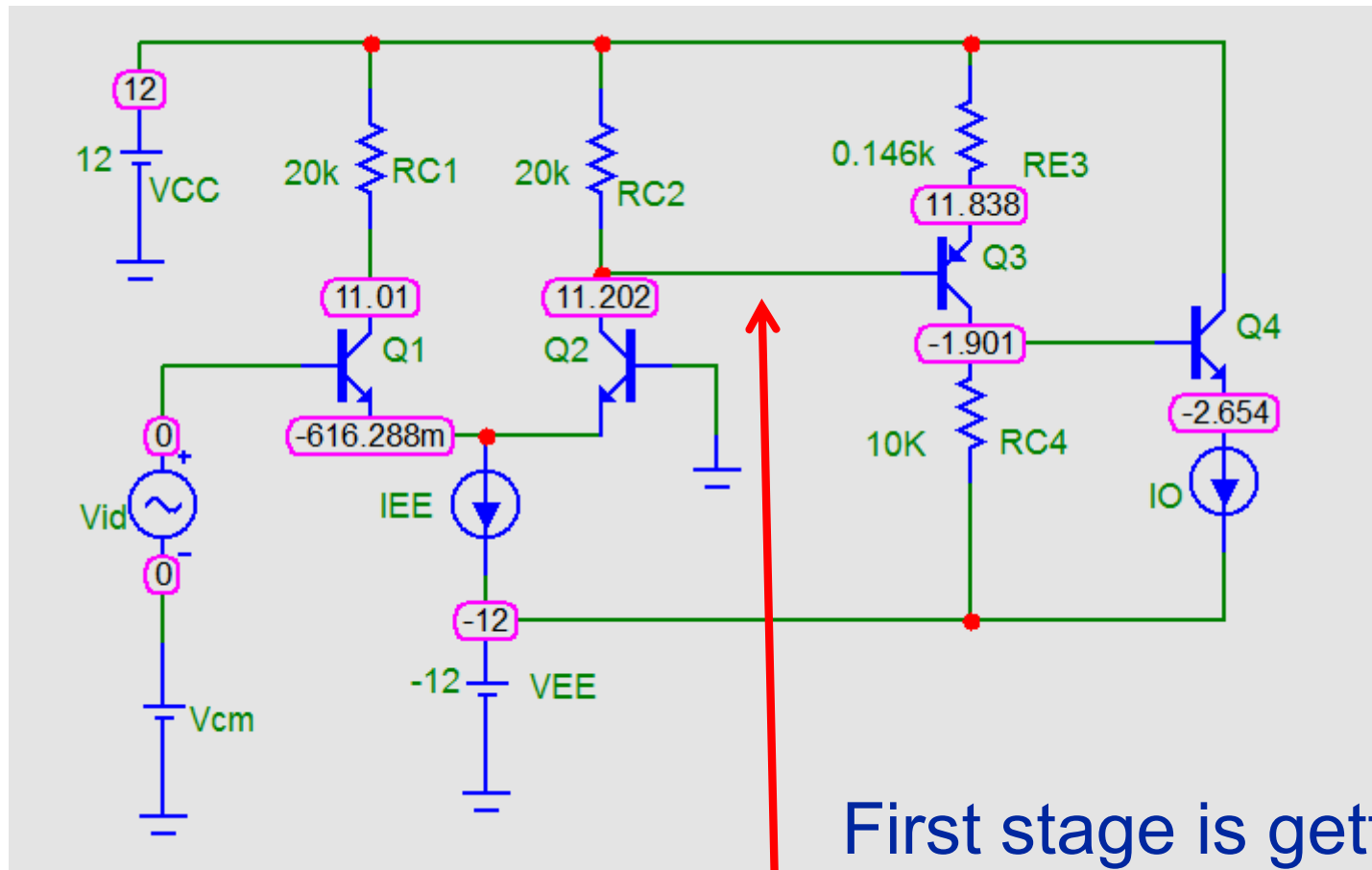


$$A_V = 513$$
$$= 9 \times 57$$


$$R_O = 84\Omega$$

To prevent loading of first stage, add a CC intermediate stage

New Opamp Schematic

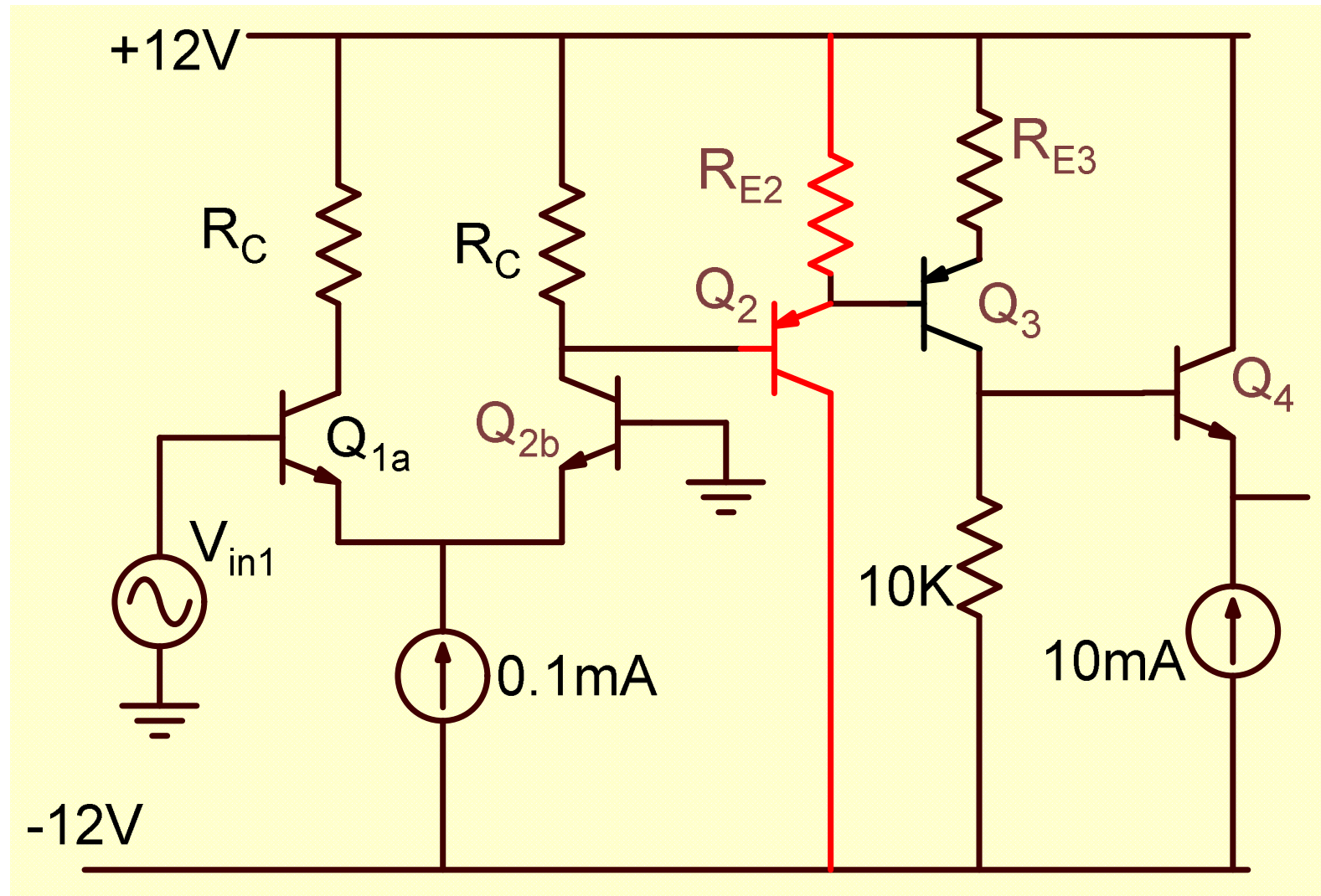

Design

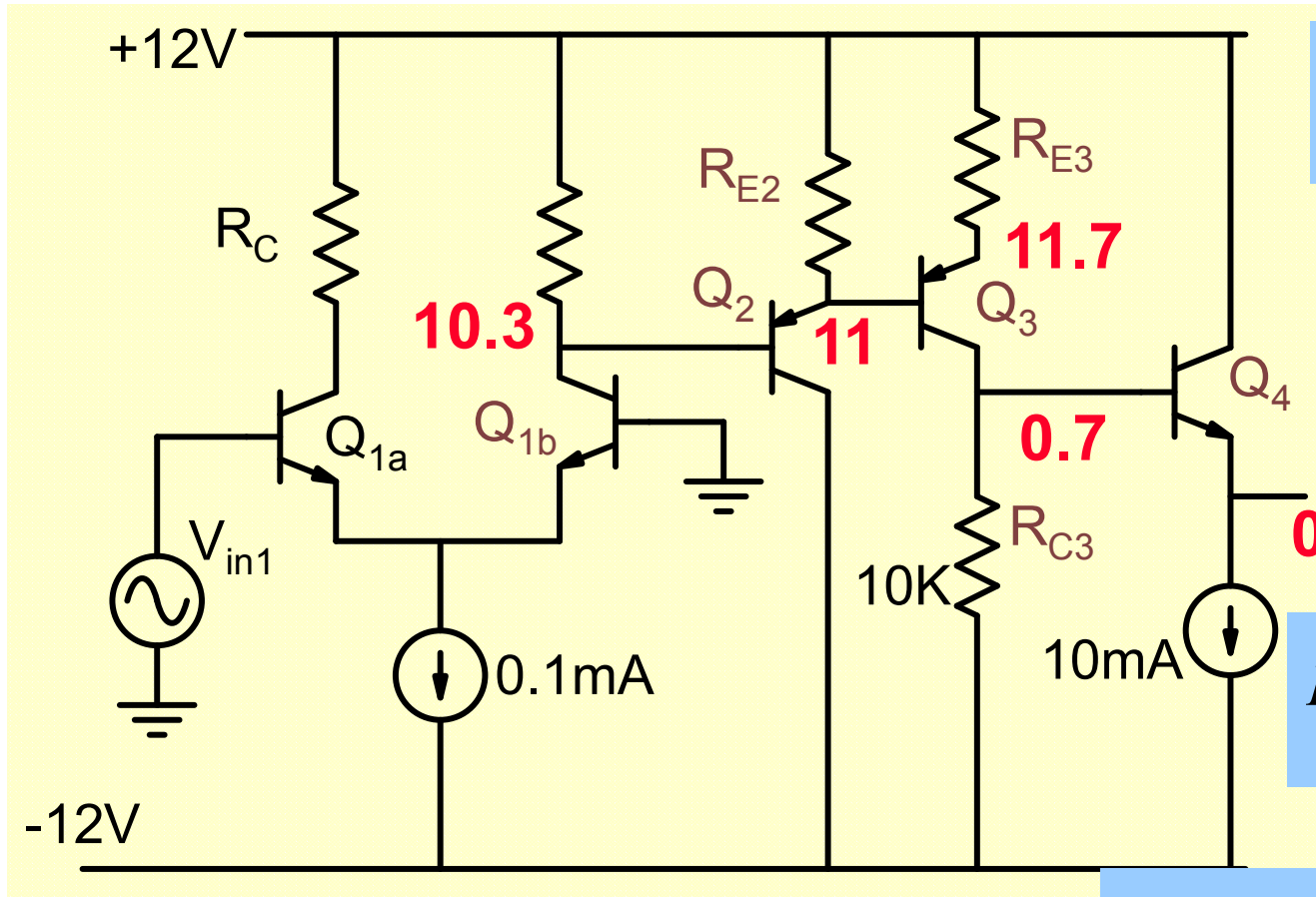

$$A_{V3} = \frac{R_{C3}}{R_{E3}} = \frac{12.7}{12 - V_{E3}}$$

$$\text{Set } V_{E3} = 11.7V$$

$$A_{V3} = 42.3$$

$$R_{E3} = 236\Omega$$


$$R_C = \frac{12 - 10.3}{I_{CQ1}} = 34K\Omega$$

$$A_{V1} = 0.5 \frac{V_{CC} - V_{C1b}}{V_T} = 32.7$$

$$\beta R_{E2} \gg R_C = 34K; R_{E2} \gg 340\Omega$$

$$\text{Let } R_{E2} = 3.4K$$

Simulation Results

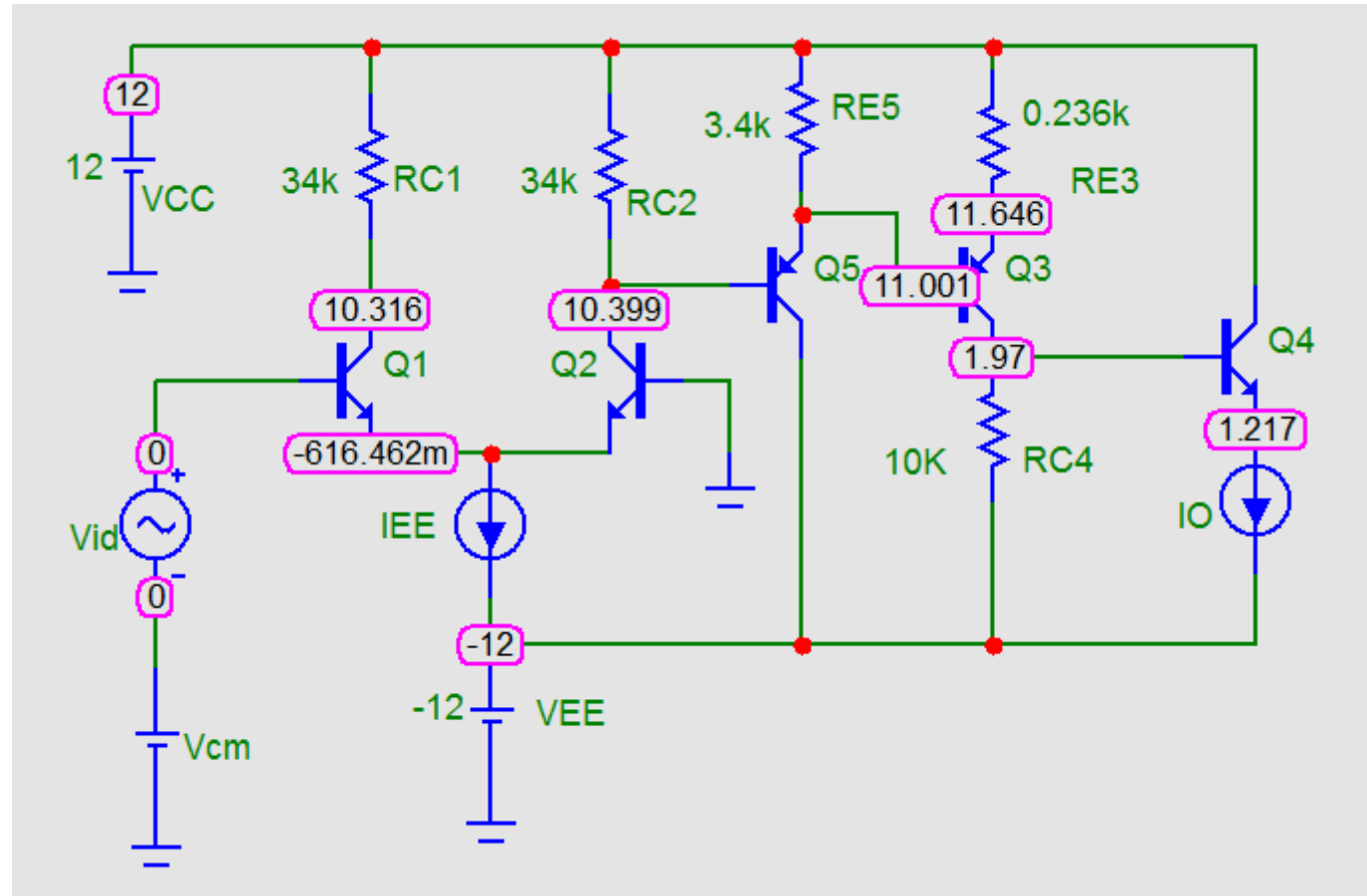


$$A_V = 1099$$

$$R_{in1} = 115K\Omega$$

$$R_O = 90.86K\Omega$$

Some fine tuning is required to bring output closer to zero

After tuning

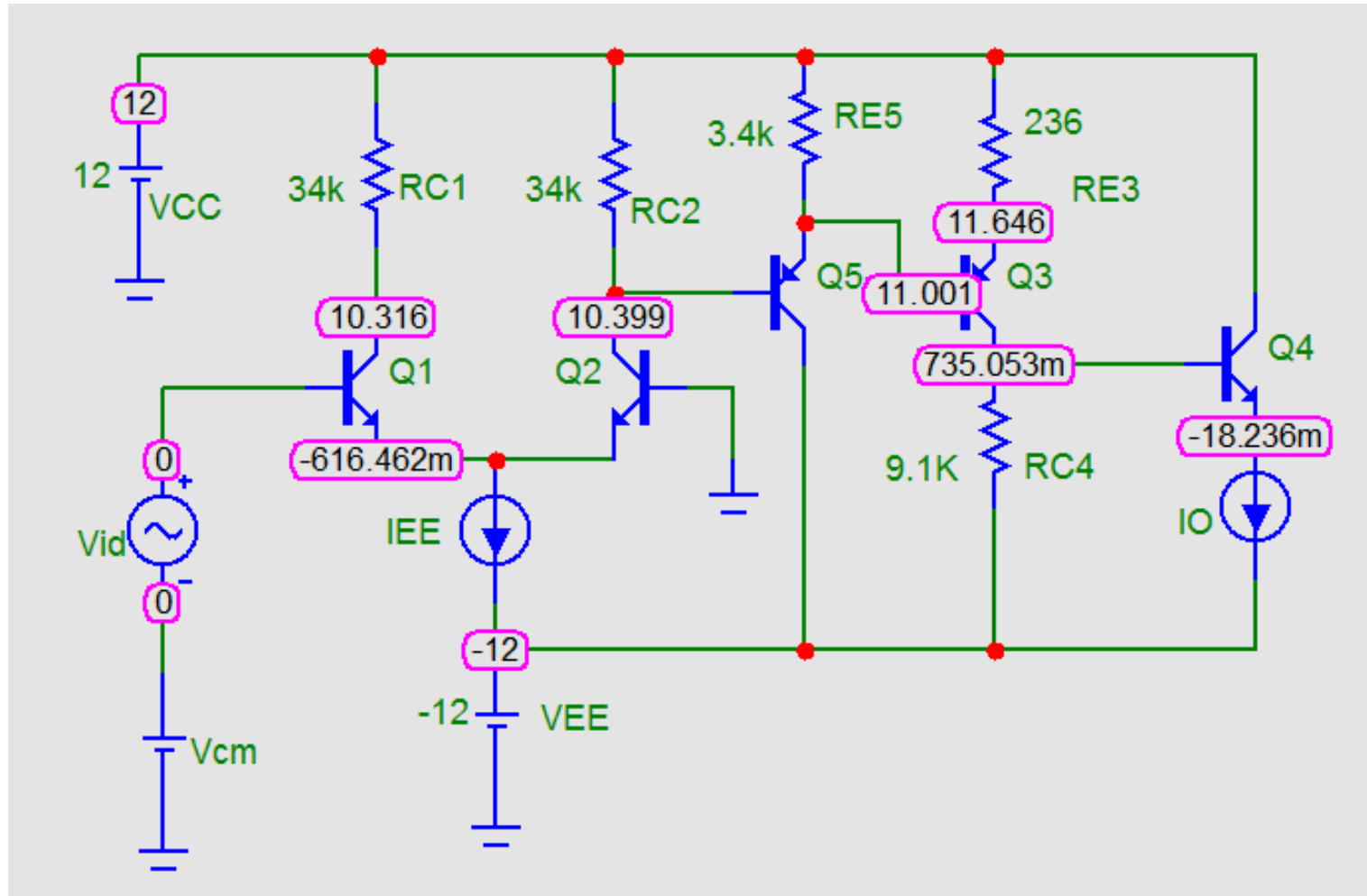



$$A_V = 1002$$

$$R_{in1} = 115K\Omega$$



$$R_O = 82.2K\Omega$$

Final Design

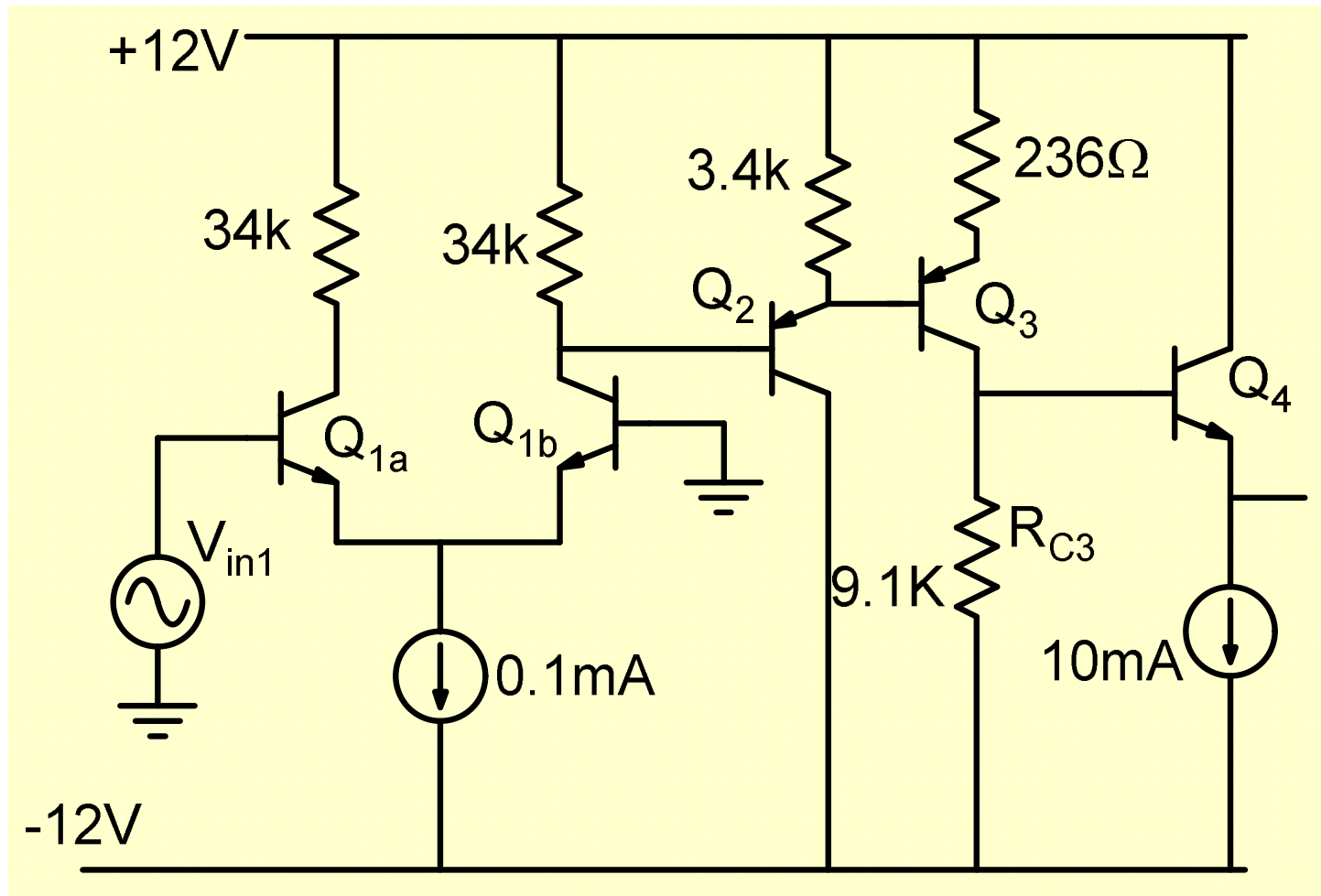


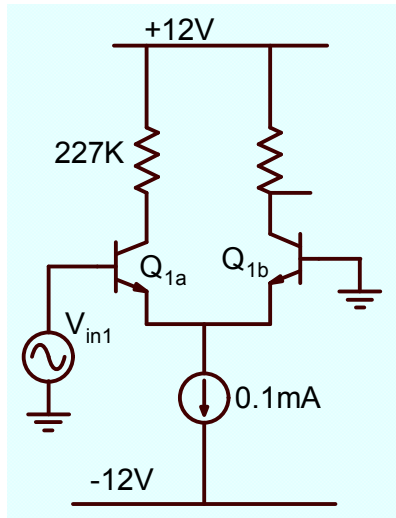

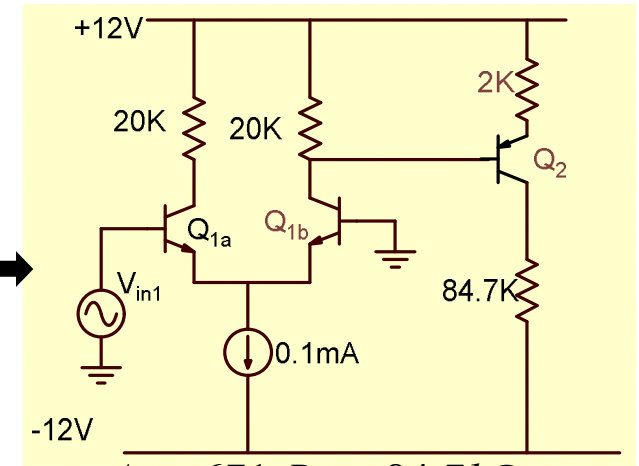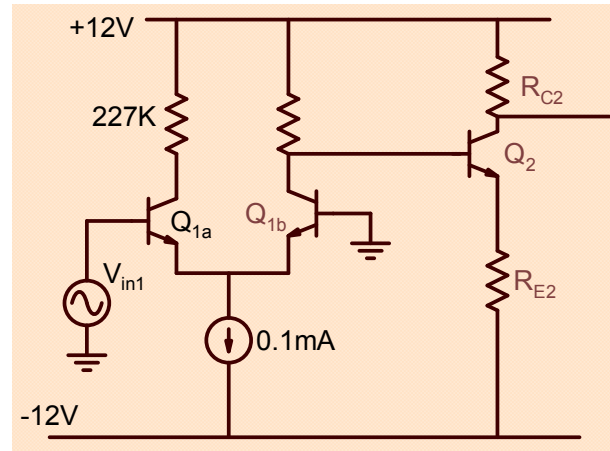
$$A_V = 227; R_{in} = 100k; R_O = 227k\Omega$$




$$A_V = 671; R_O = 84.7k\Omega$$

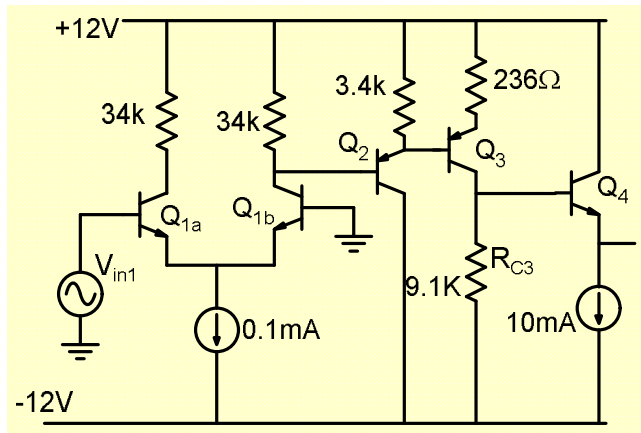
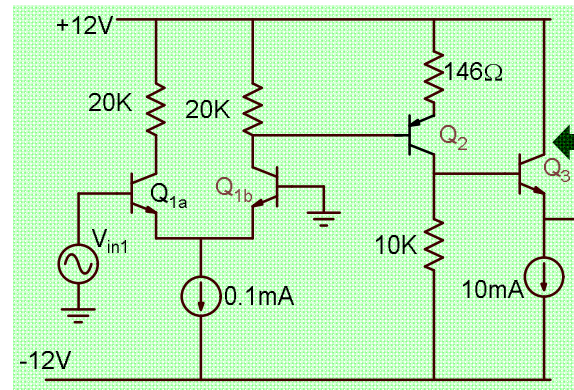
$$A_V = 1002; R_{in} = 115k; R_O = 82\Omega$$



$$A_V = 513; R_O = 84\Omega$$

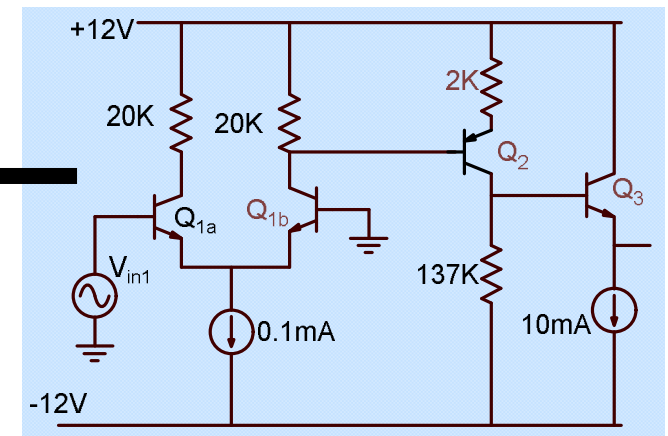

$$A_V = 972; R_O = 1071\Omega$$