EE210: HW-9

Date: 06/03/2019

Unless stated otherwise, the BJT in the problems given below has the following characteristics $I_S=2.03x10^{-15}A;~\beta_F=100;~\beta_R=1;~V_A=\infty;~r_{bb}=200\Omega;~V_T=26mV;~C_{jeo}=1pF;~C_{jeo}=0.5pF;~C_{jso}=3pF;~m=0.5;~V_{bi}=0.85;~\tau_F=1ns$ (For simplicity, include r_{bb} only in high frequency analysis and ignore Cjs)

Q.1 Figure.1 shows a common-base amplifier schematic. Determine voltage gain, input and output resistance and upper cutoff frequency for $R_S = 0$. Determine the voltage gain and upper cutoff frequency again for the case where source has a resistance of 1K.

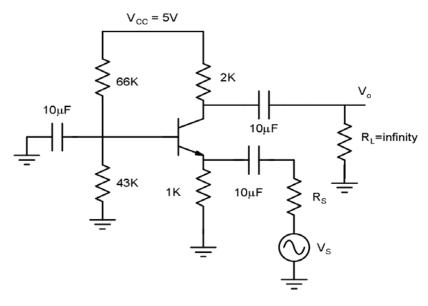


Fig. 1

Q.2 Determine gain, input resistance, output resistance, voltage swing with $HD_2 = 10\%$, upper and lower cutoff frequencies for the Cascode amplifier shown in Fig. 2.

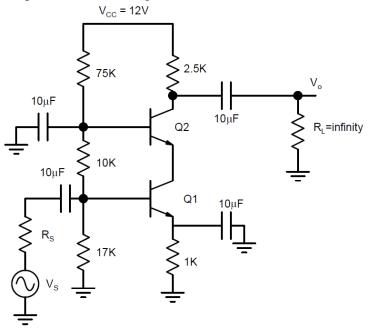


Fig. 2