


# EE210: Microelectronics-I

## Lecture-1 : Introduction

Instructor - Y. S. Chauhan

Slides from B. Mazhari  
Dept. of EE, IIT Kanpur

## EE210 is an Analog Circuits Course

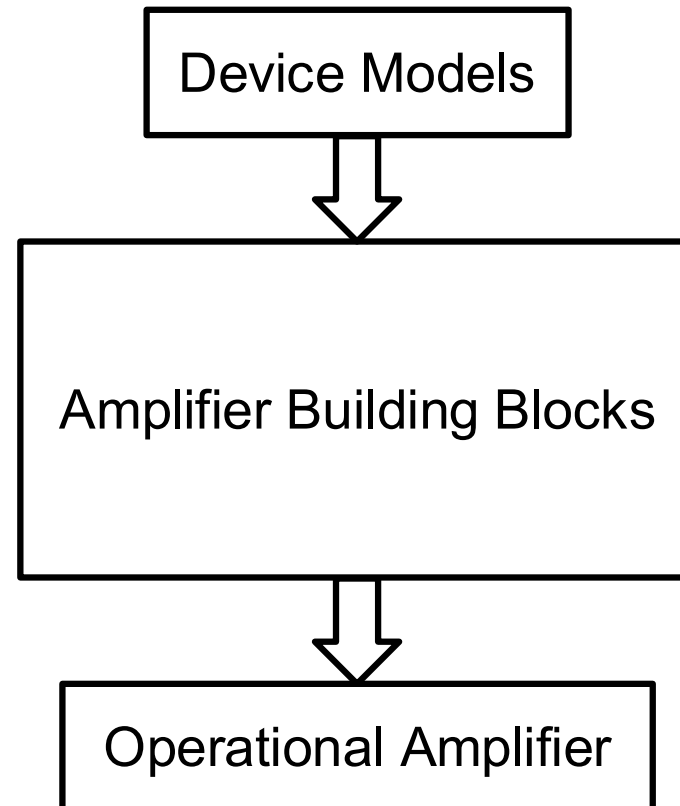

Both BJT and MOS analog circuits will be studied

## Books :


1. Semiconductor Devices and Circuits, A.K. Dutta, Oxford University Press India, 2008.
2. Analysis and Design of Analog Integrated Circuits; P.R. Gray, P.J. Hurst, S.H. Lewis, and R.G. Meyer; John Wiley & Sons, 4th Edition, 2001.
3. Microelectronic Circuits; A.S. Sedra and K.C. Smith; Oxford University Press, 4th Edition, 2000.
4. CMOS Analog Circuit Design, P.E. Allen and D.R. Holberg, Oxford University Press second Edition, 2002.
5. Design of Analog CMOS Integrated Circuits,” B. Razavi, Tata McGraw Hill, 2002

## Journals :




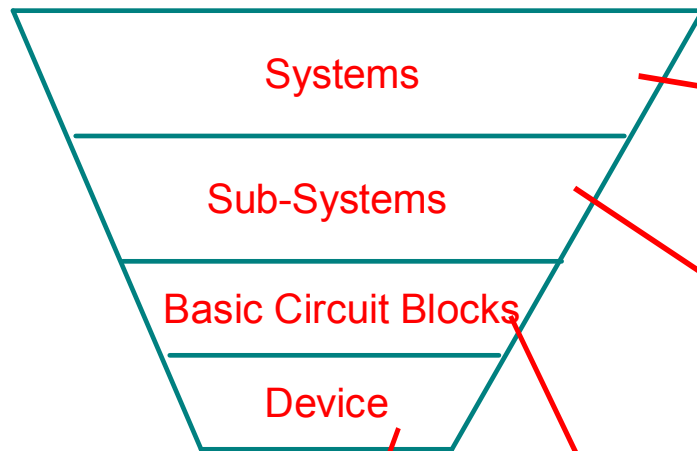
1. IEEE Journal of Solid state circuits
2. IEEE Trans. On Circuits and Systems
3. Analog Integrated Circuits and Signal Processing, springer.

Lecture notes (from previous years) :


<https://www.youtube.com/channel/UCHJ-zINIZnOh3UQMo1lcuZw>



## Blood pressure meter

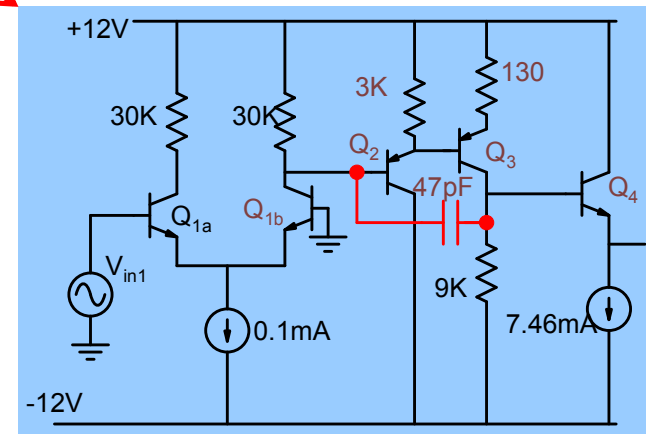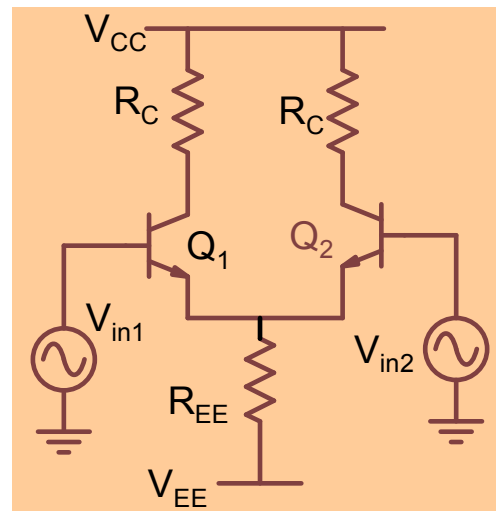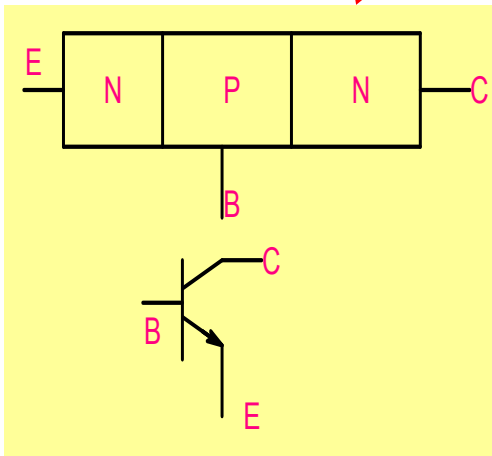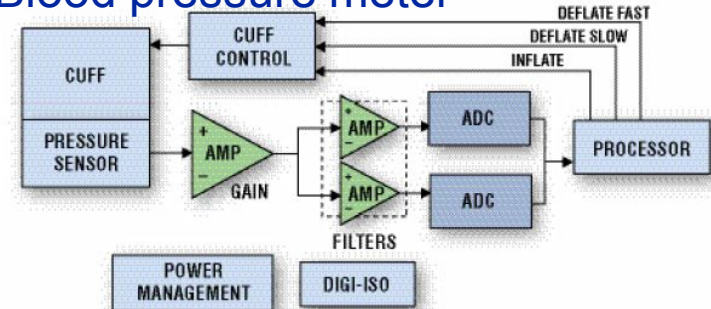

# Microelectronics : Courses

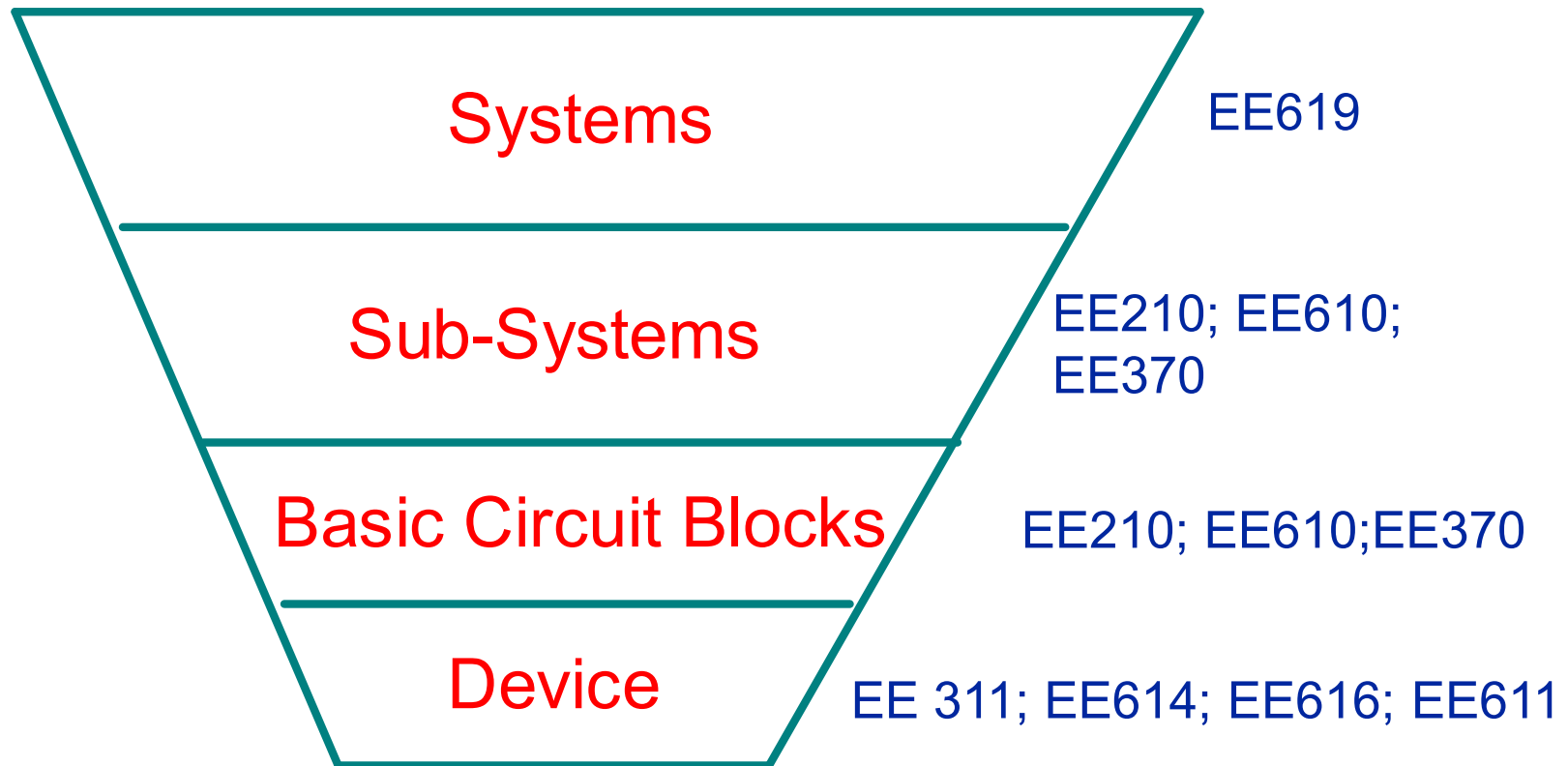


# What is Microelectronics?

It is a field which deals with implementation of 'ideas' on a piece of semiconductor (e.g. Silicon)

Microelectronics is 'Writing in Sand'




# EE 210 is a Course on Amplifiers

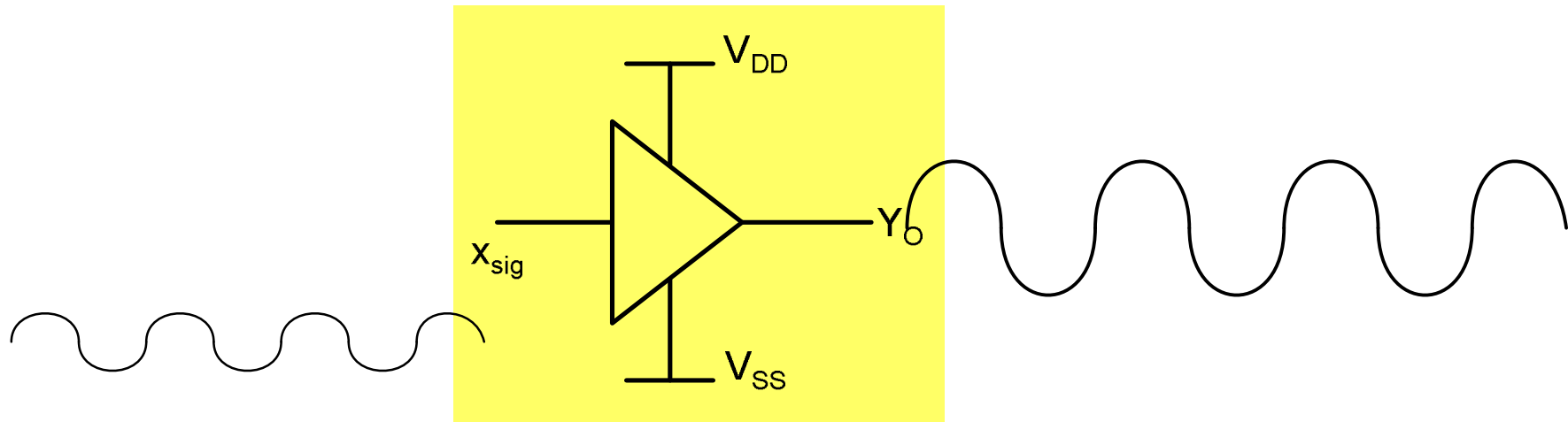

$$\frac{P_o}{P_{sig}} > 1$$


“Amplification is the heartbeat of Electronics”
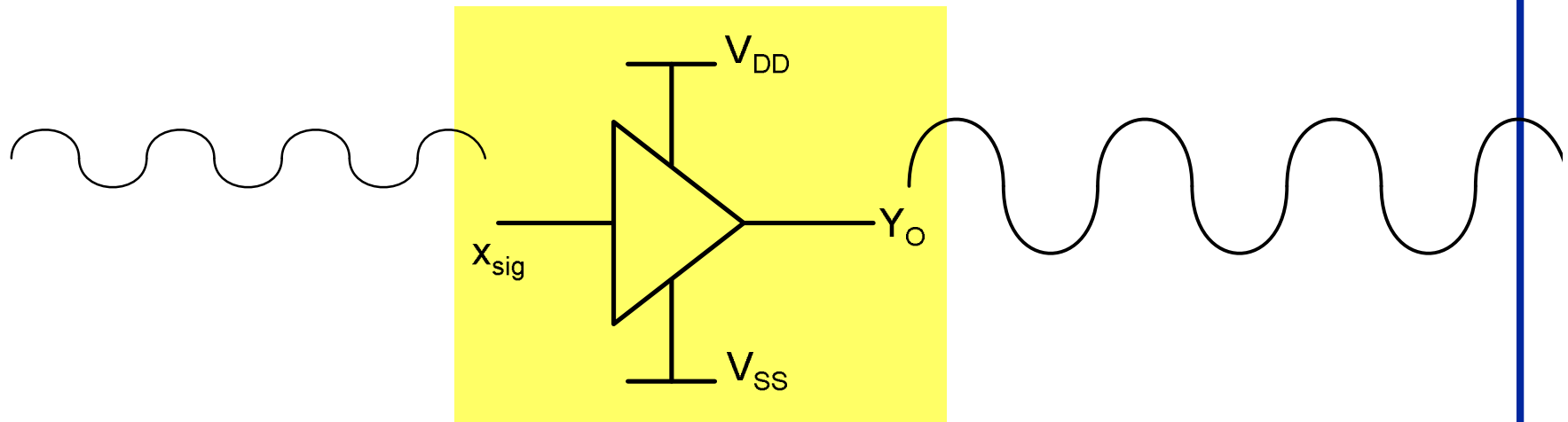
# The foundation of civilization is “Amplification”






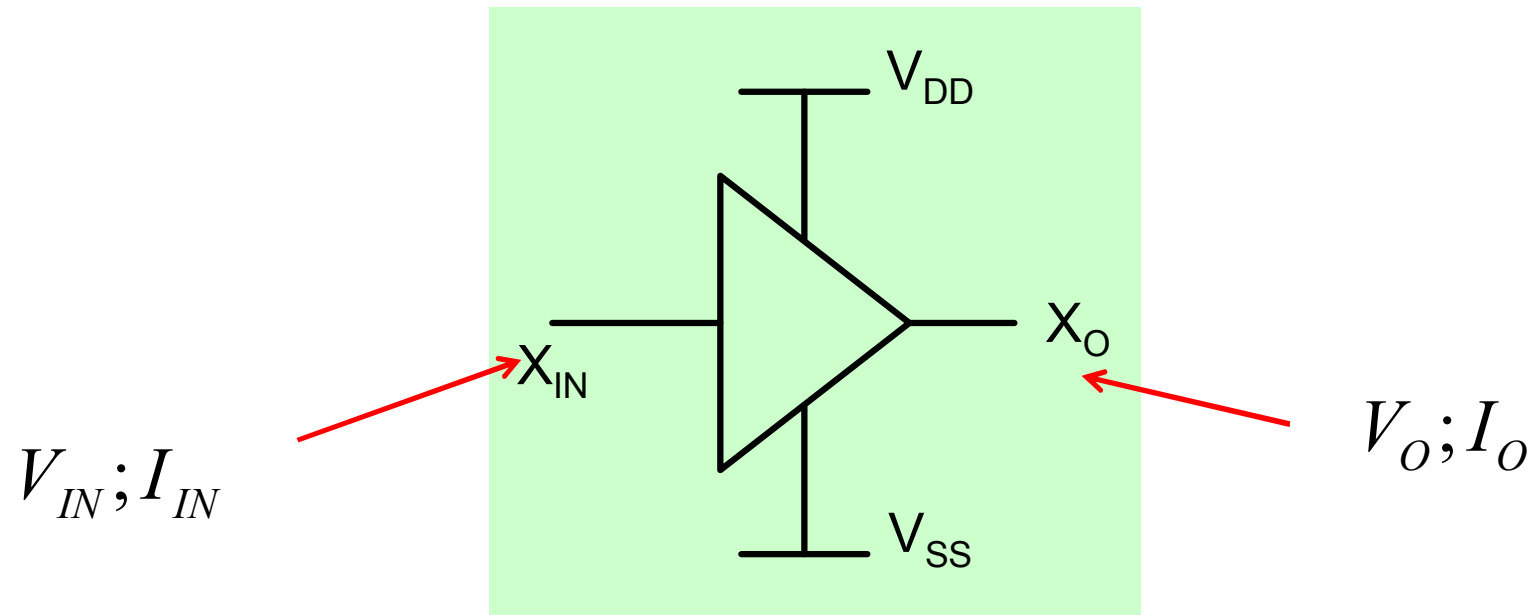Depending on the input and output, there can be four broad classes of amplifiers



INPUT	OUTPUT	Amplifier
V	V	Voltage
V	I	Transconductance
I	I	Current
I	V	Transresistance




# Ideal Voltage Amplifier

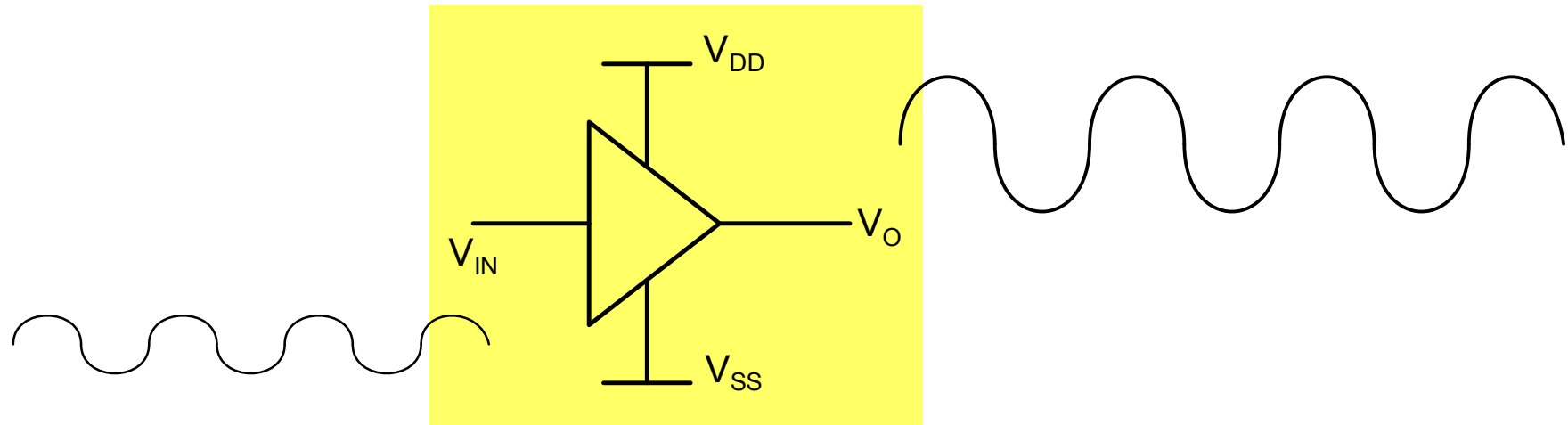

$$V_O = A_v \times V_{IN}$$


**$A_v$  is a constant**

Should  $A_v$  be  $>1$  ?

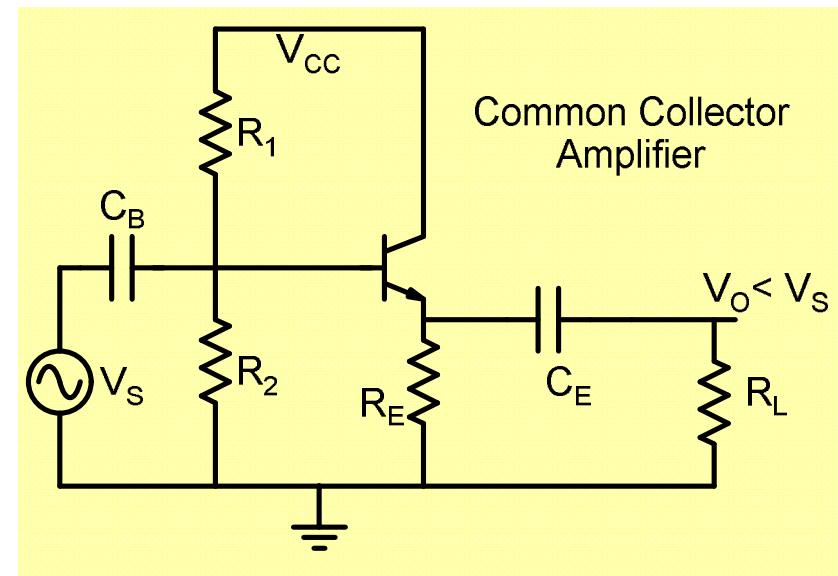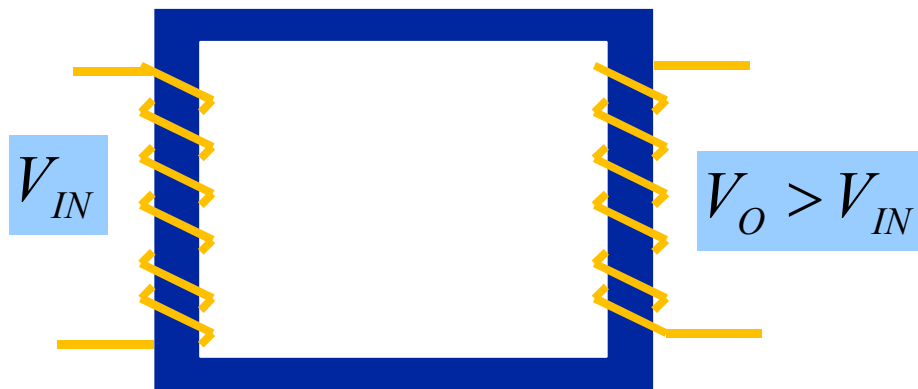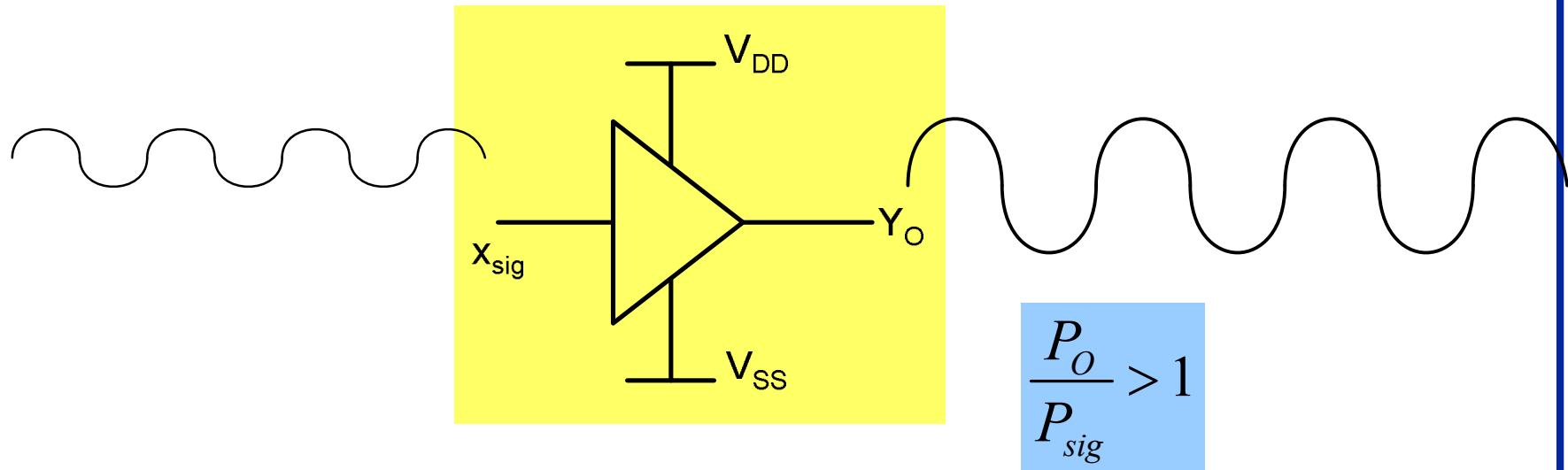
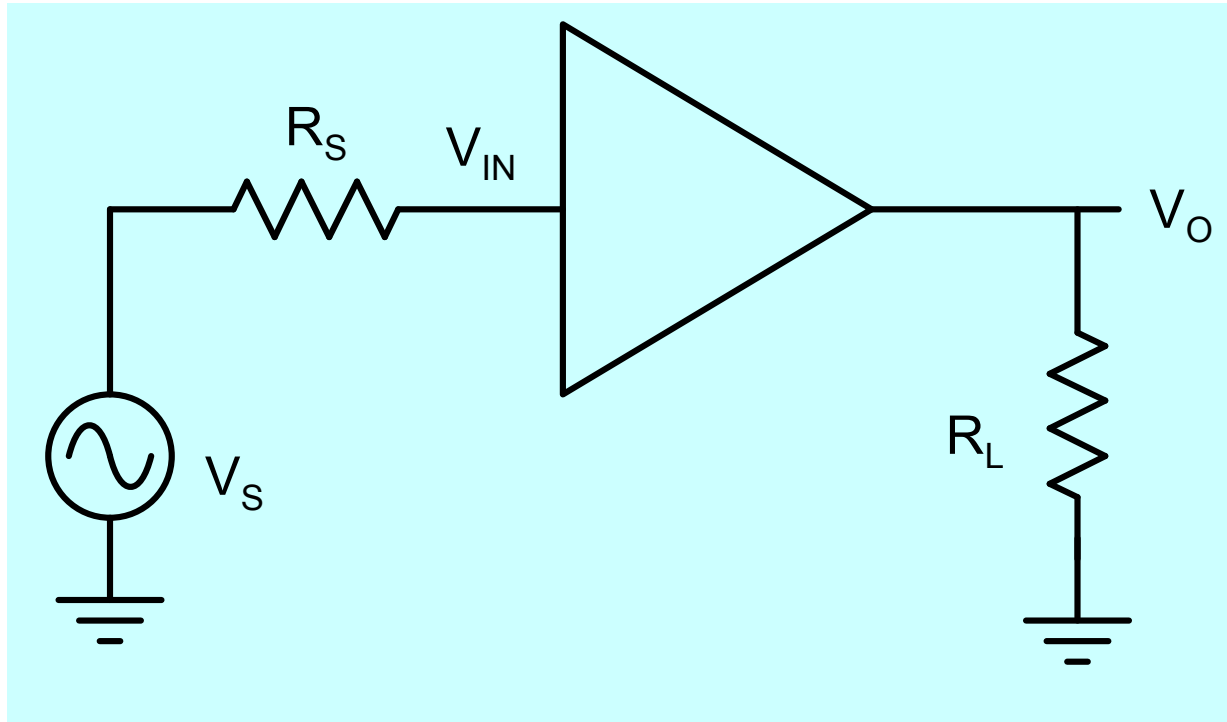
# Practical Amplifier


$$\text{Ideal: } V_O = A_v \times V_{IN}$$




$$V_o = A_v(f, V_{in}, R_L, R_S, T) \times v_{in} + \tilde{e}_N$$
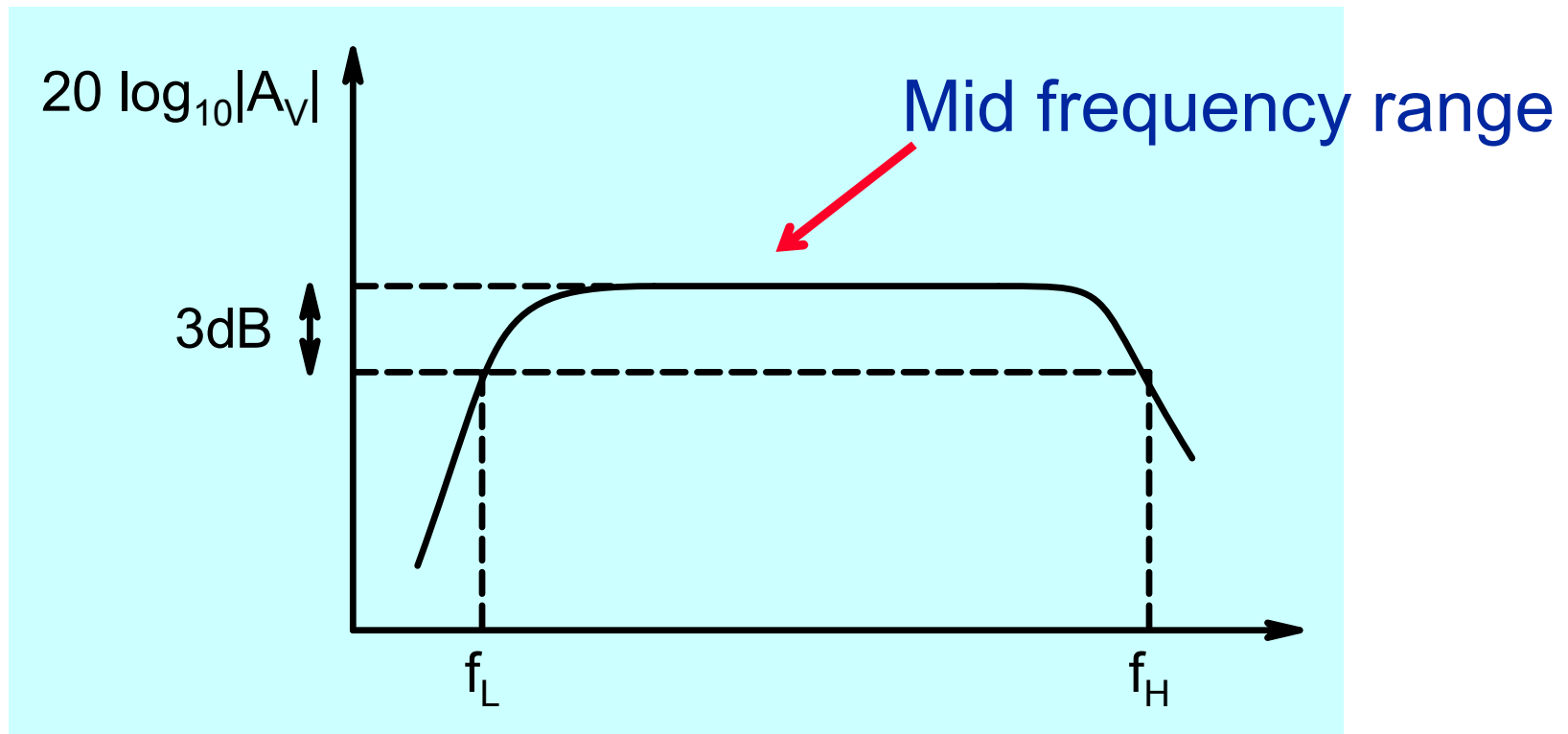
# Frequency Response

$$V_o = A_v(f, V_{in}, R_L, R_S, T) \times v_{in} + \tilde{e}_N$$



# dc Amplifier

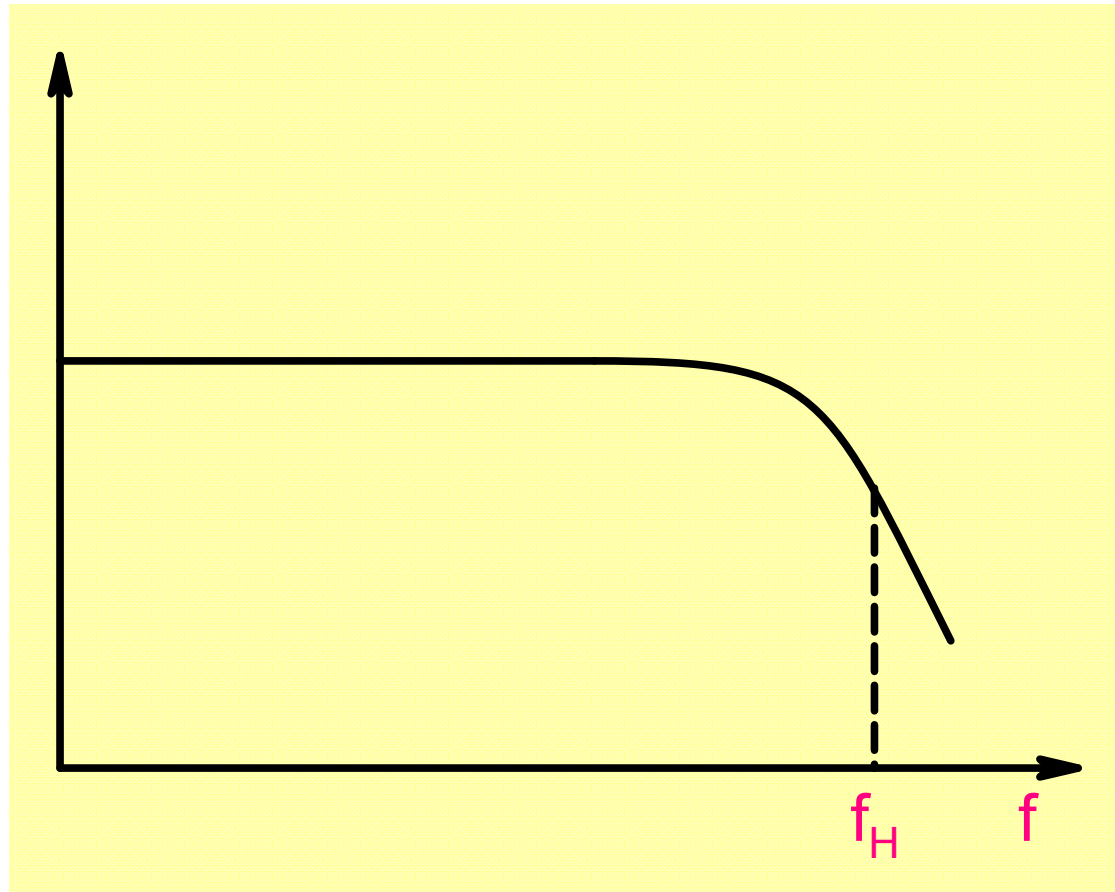

# Unity Gain Frequency

