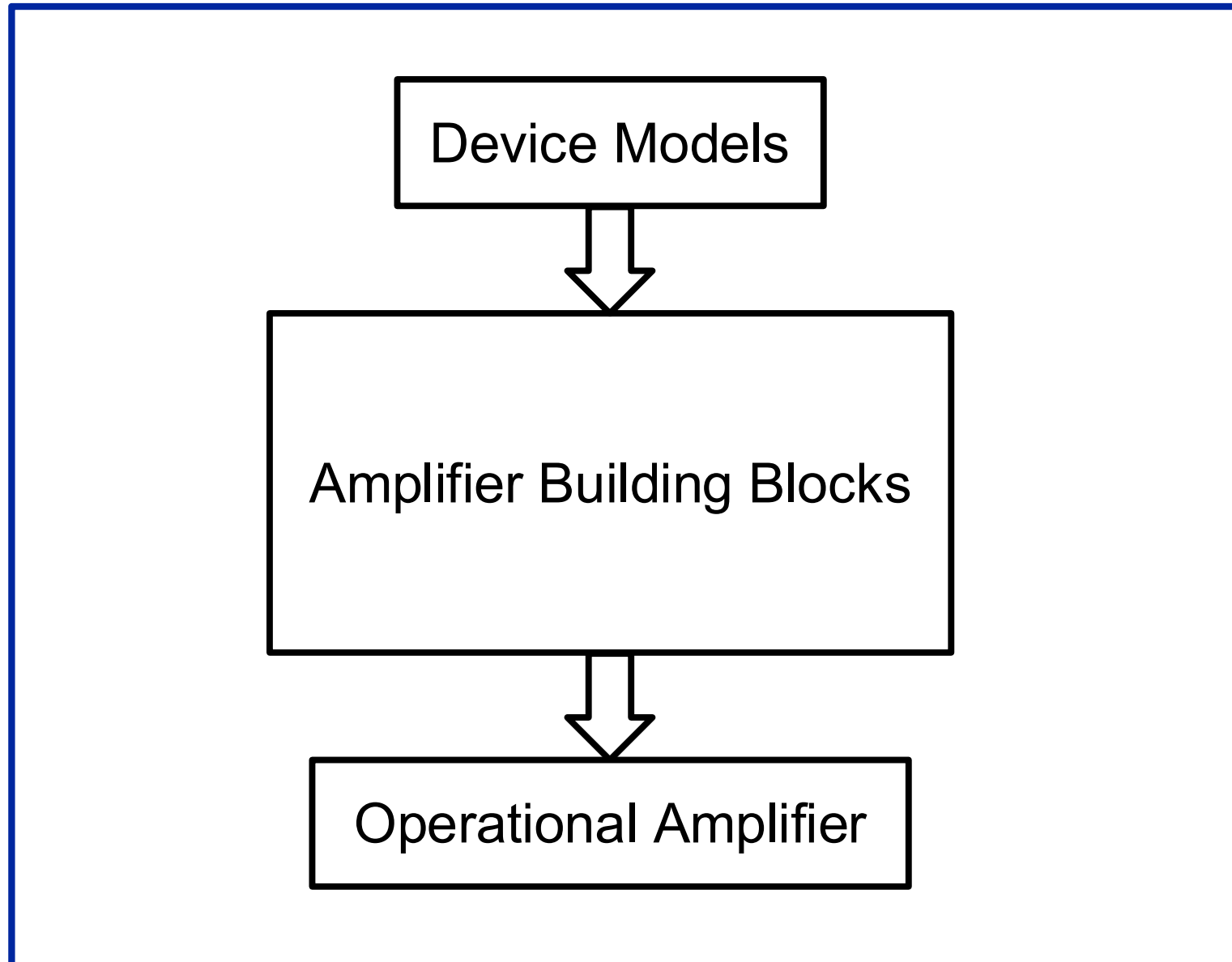


# EE210: Microelectronics-I




## Lecture-35 Review of BJT Circuits-part-1



<https://youtu.be/y6nPaUldzF8>



B. Mazhari  
Dept. of EE, IIT Kanpur




# EE210: Overview

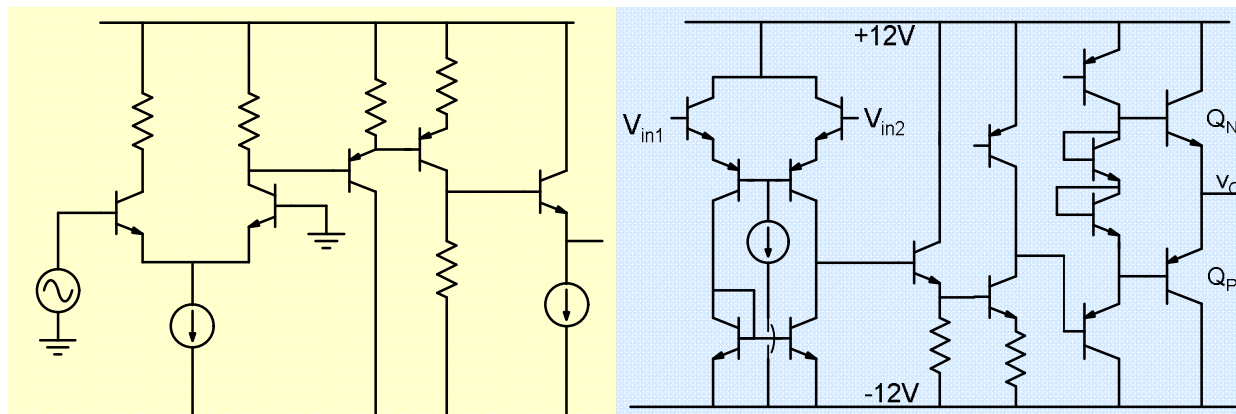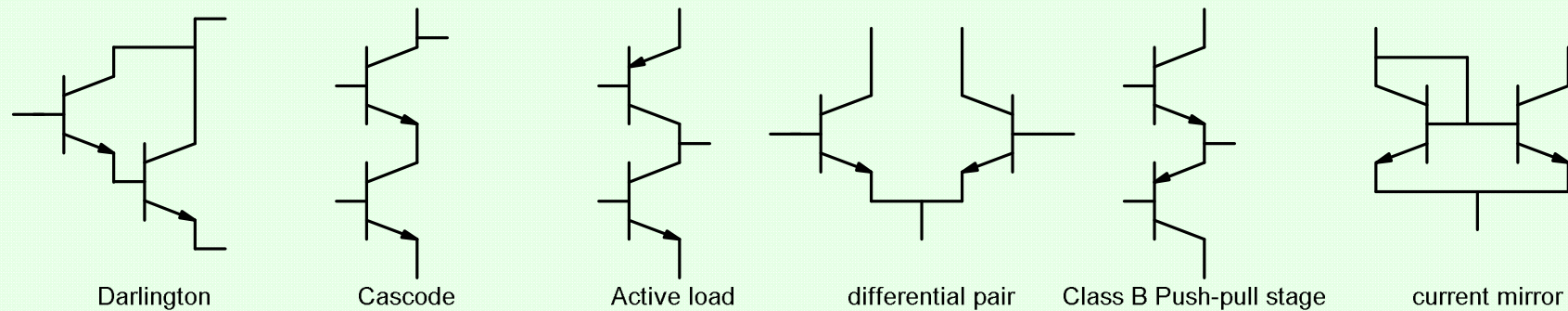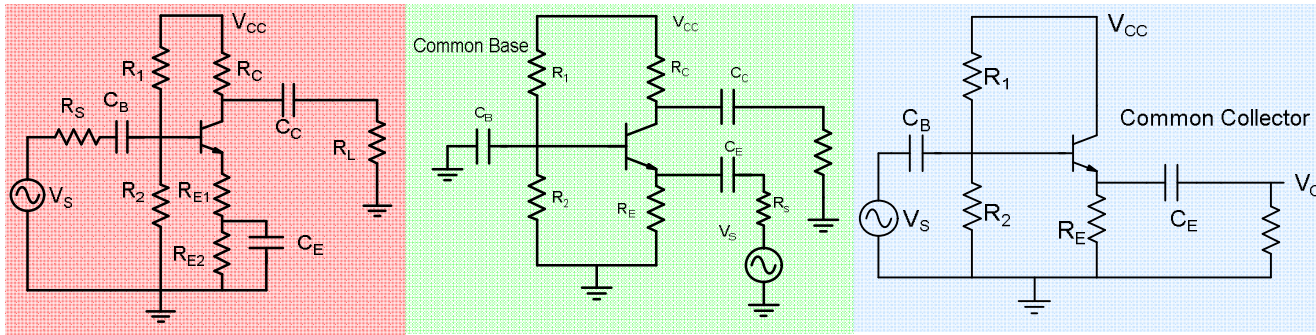

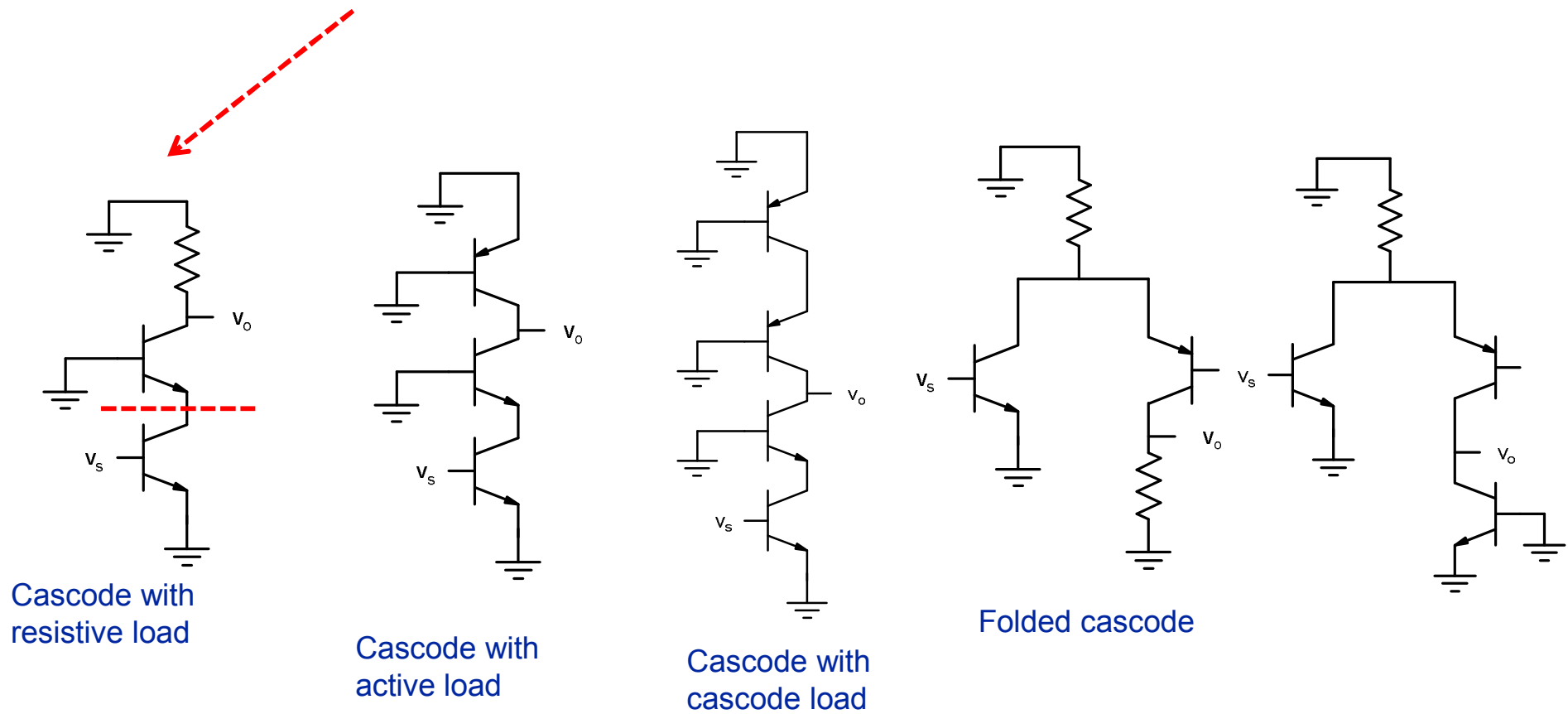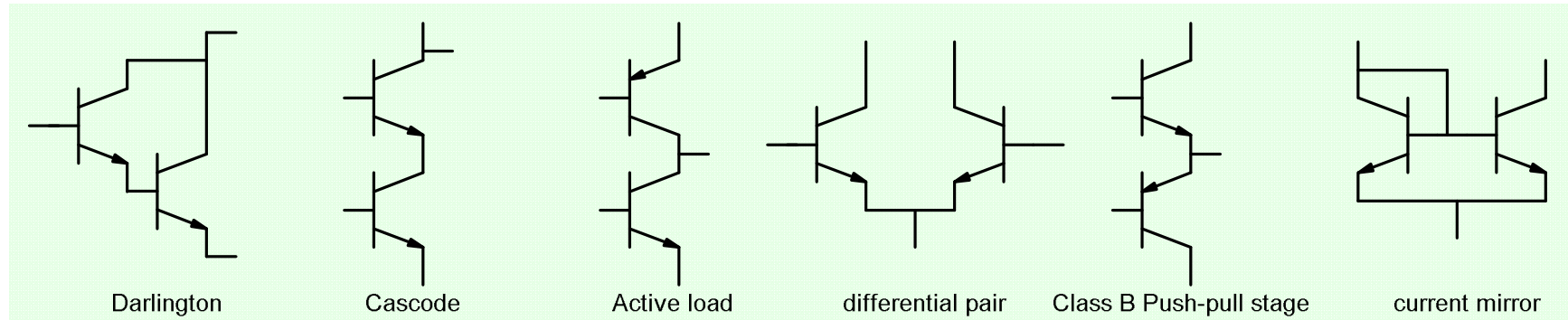


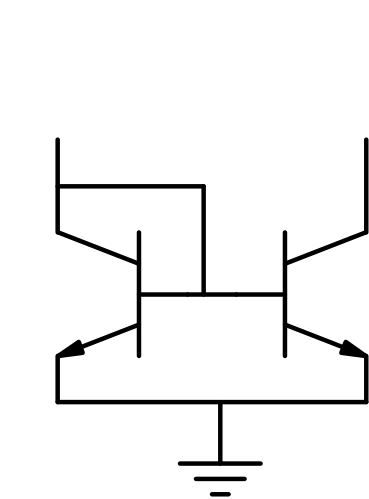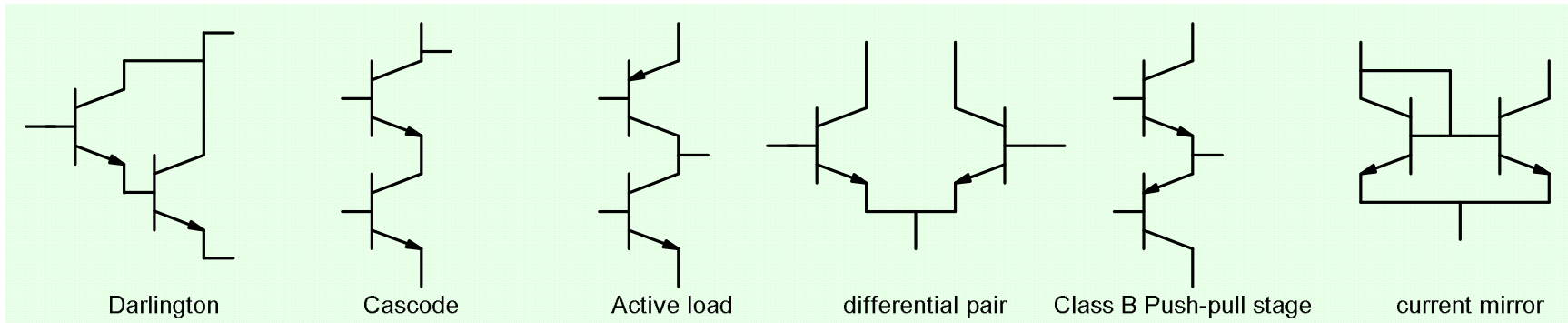


Simple Current Mirror

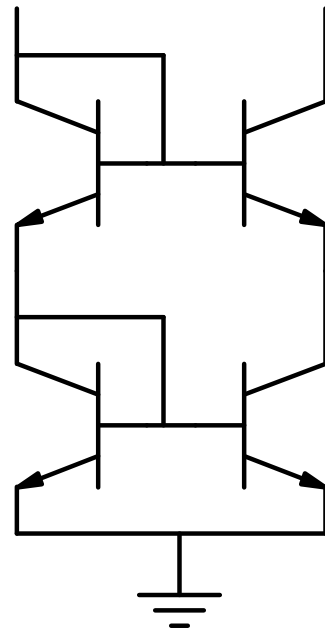

Cascode  
Current Mirror

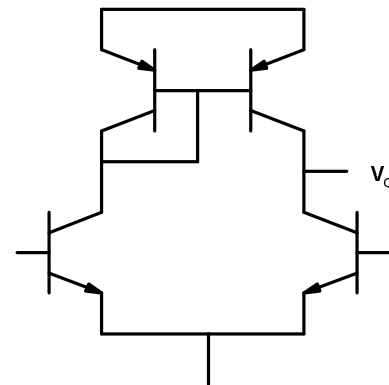


Diff. amp with  
Current Mirror  
load

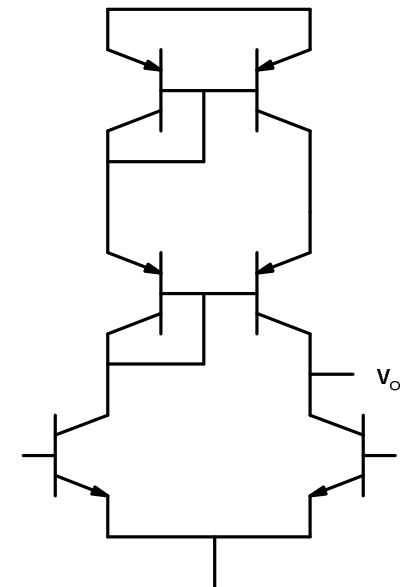


Diff. amp with cascode  
Current Mirror load

# Review
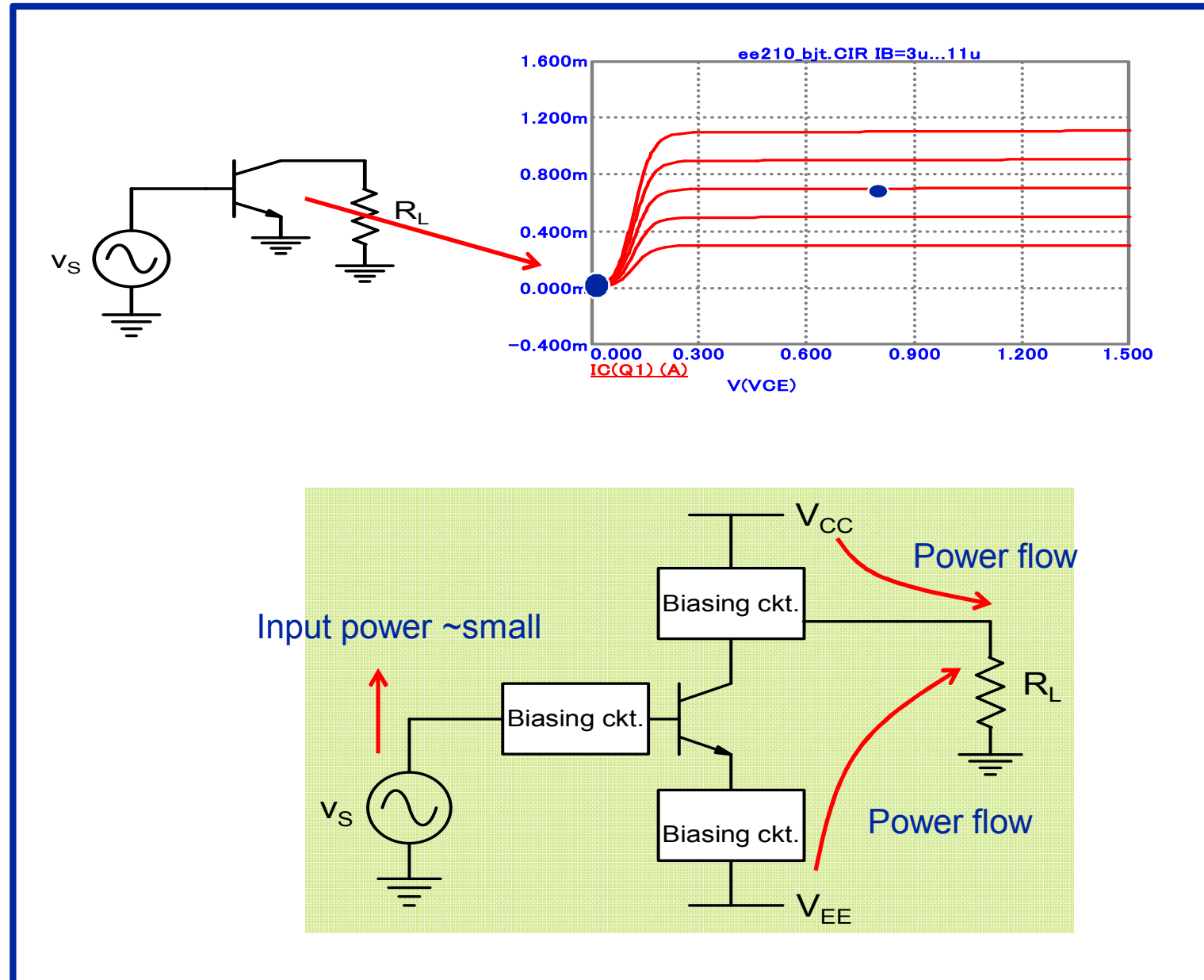
# A Transistor needs to be biased in active region to amplify




# Analysis


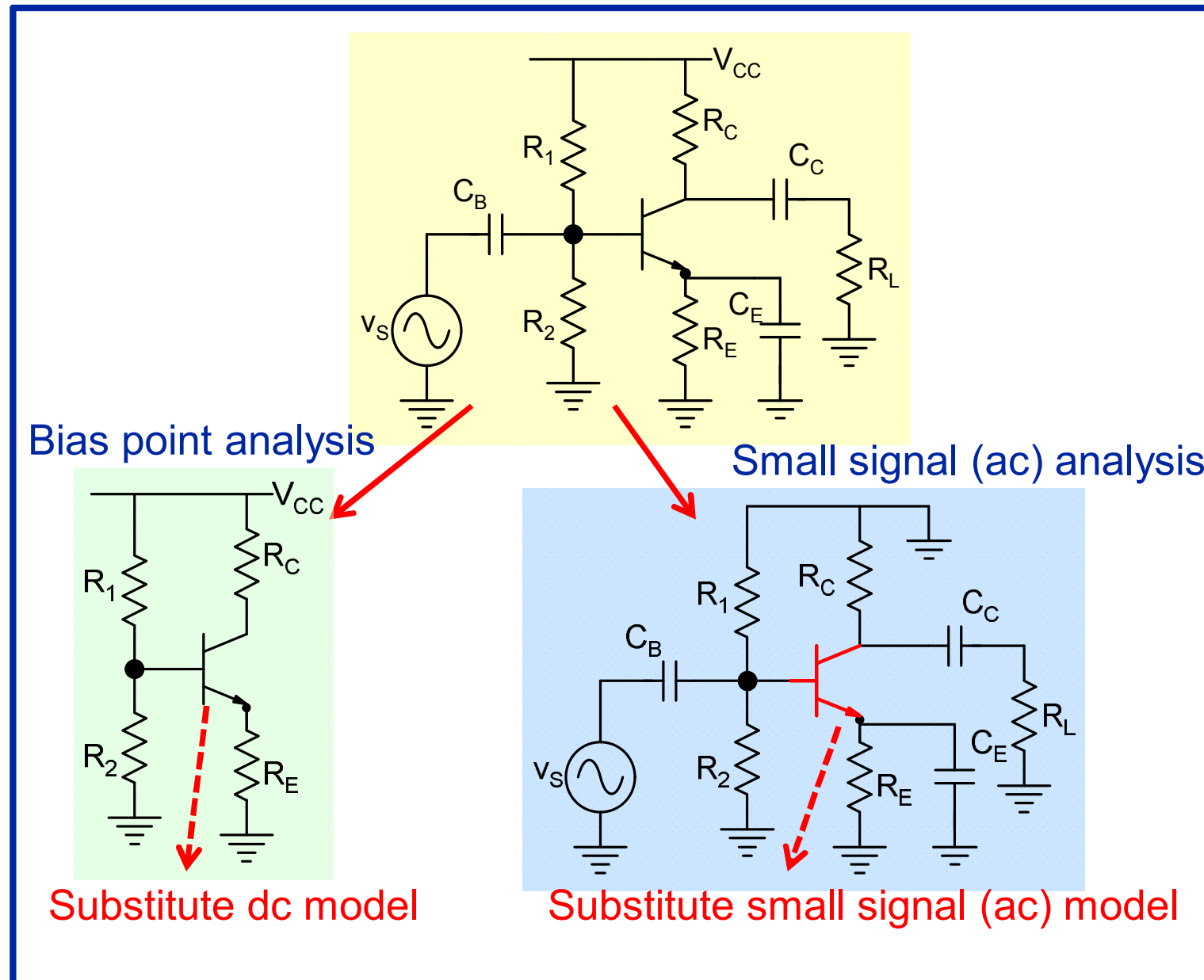




# Role of simple model in design cycle

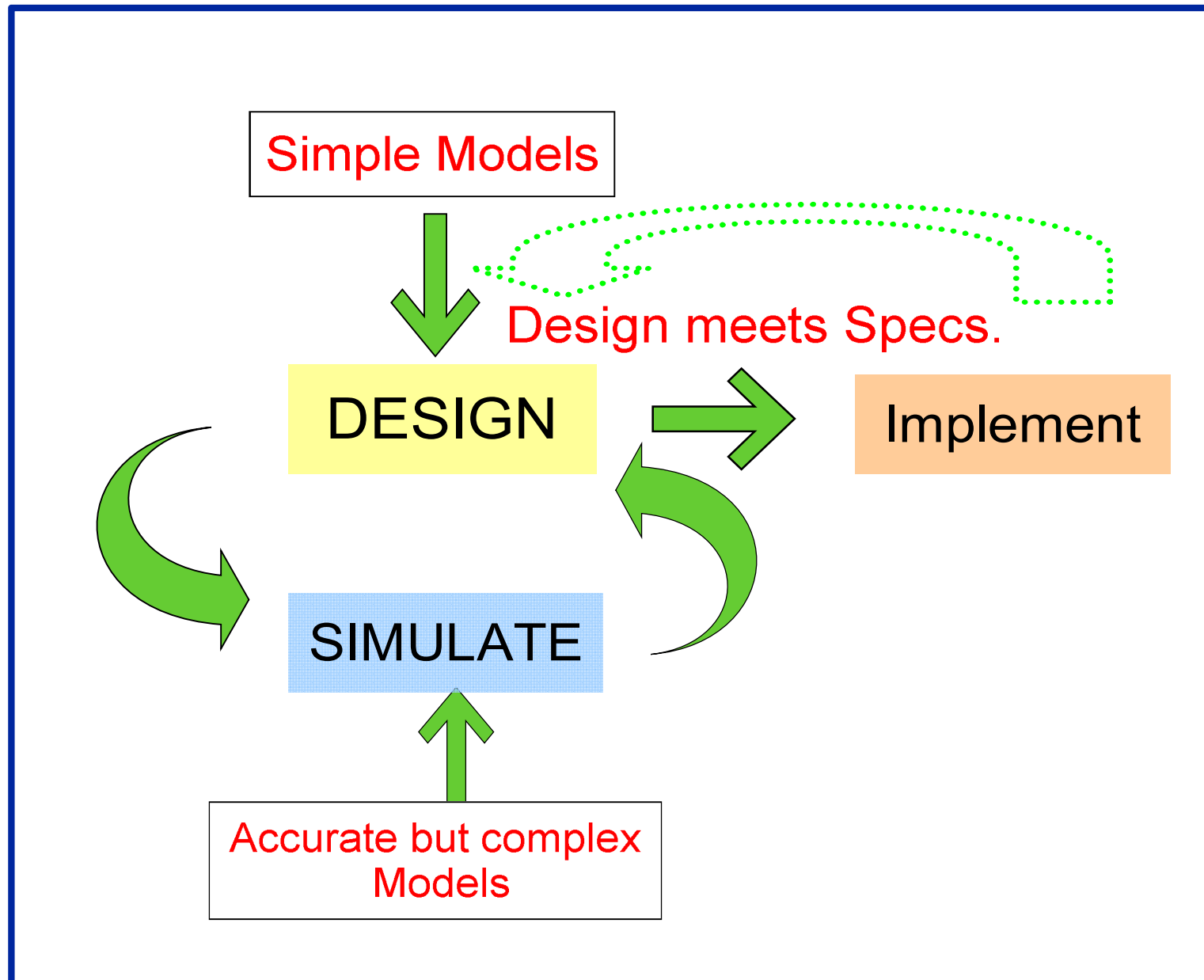
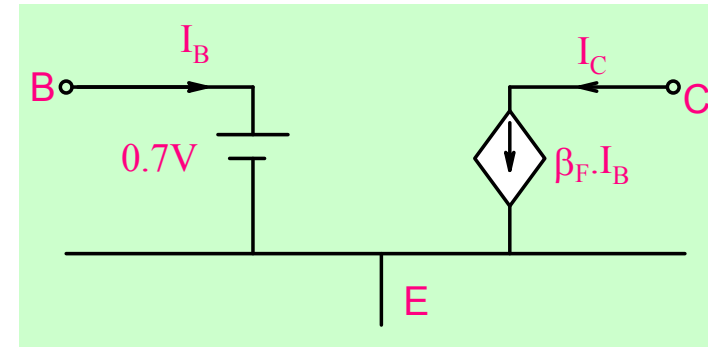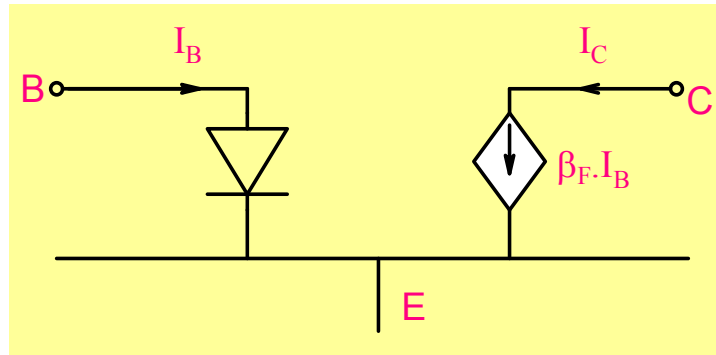
# Model Of An NPN BJT In Forward Active Mode




$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$I_B = \frac{I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)}{\beta_F}$$


$$I_C = \beta_F I_B \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$C_{je} = \frac{C_{jeo}}{\left( 1 - \frac{V_{BE}}{V_{bi}} \right)^m}$$
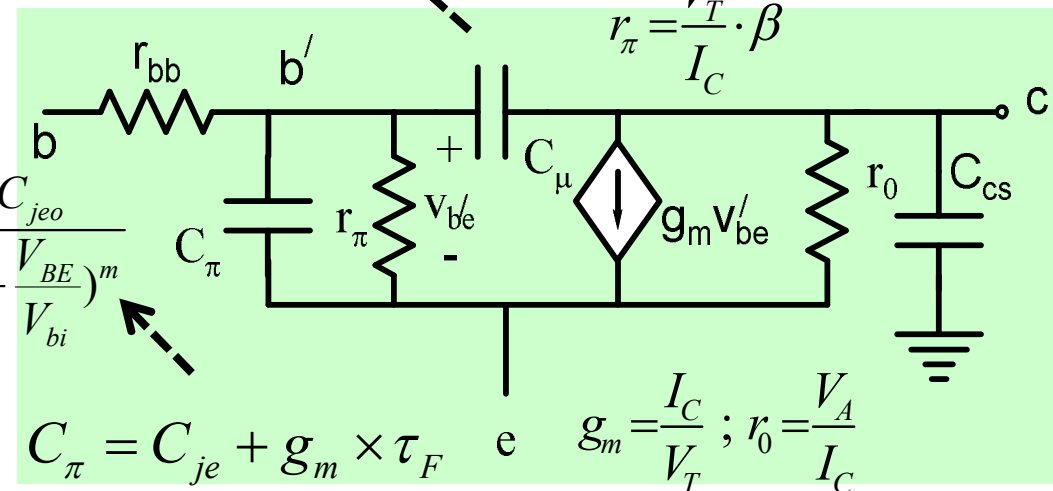
$$C_\mu = C_{jc} = \frac{C_{jco}}{\left( 1 - \frac{V_{BC}}{V_{bi}} \right)^m}$$



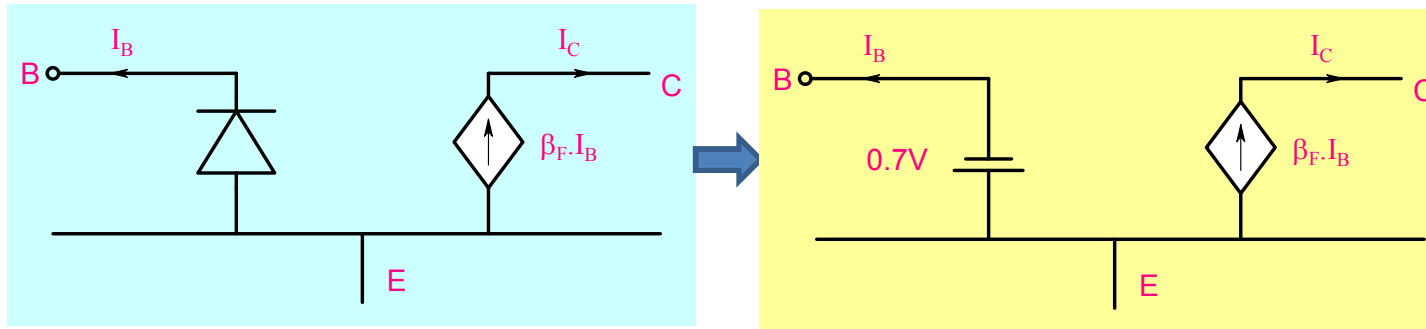
# Model of a PNP BJT In Forward Active Mode




$$I_C = I_S \left( \exp\left(\frac{V_{EB}}{V_T}\right) - 1 \right) \left( 1 + \frac{V_{EC}}{V_A} \right)$$

$$I_B = \frac{I_S \left( \exp\left(\frac{V_{EB}}{V_T}\right) - 1 \right)}{\beta_F}$$

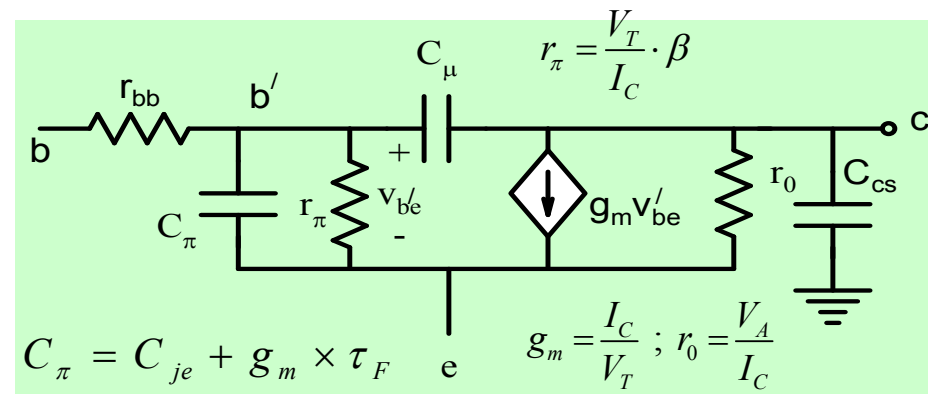
$$I_C = \beta_F I_B \left( 1 + \frac{V_{EC}}{V_A} \right)$$


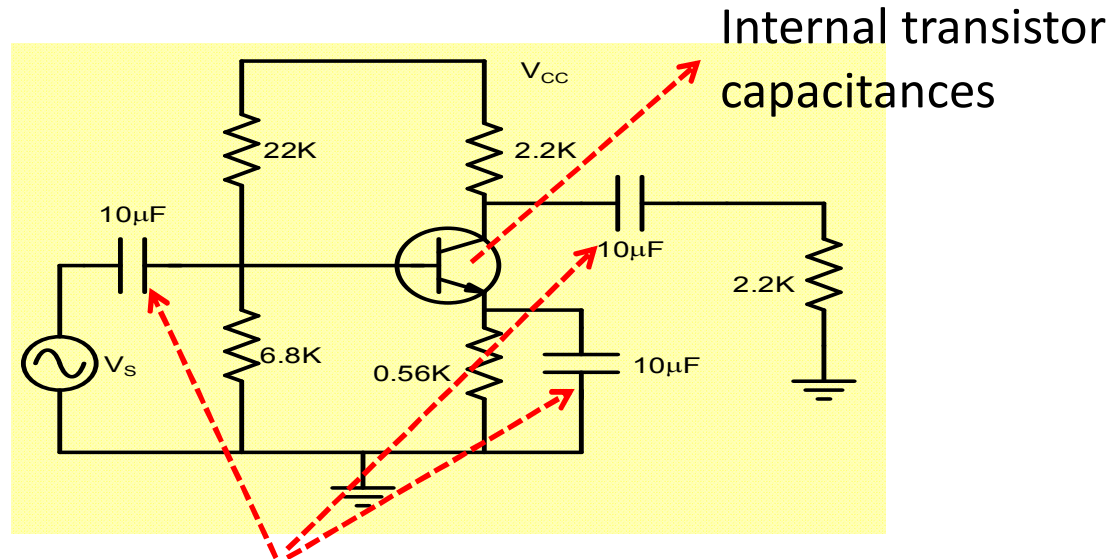
# Characteristics of Amplifiers Are Frequency Dependent






External coupling and bypass capacitors

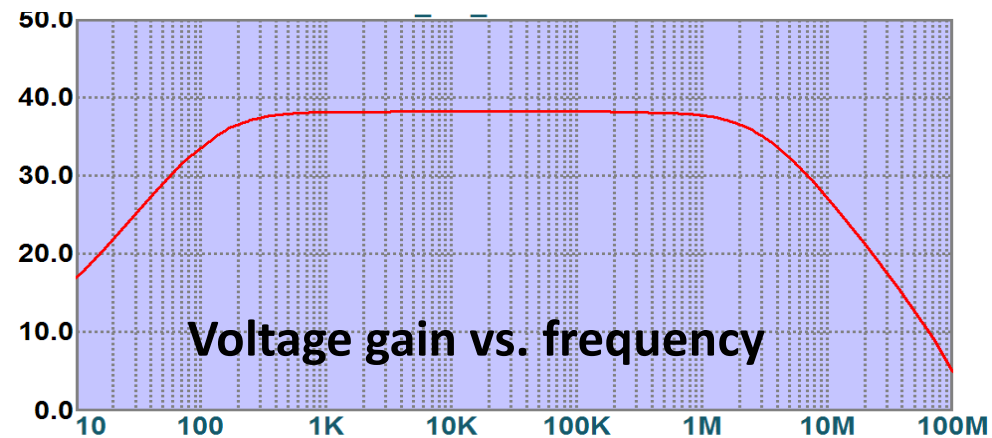


Low frequency behavior  
is caused by external  
capacitances

Mid-frequency region: all  
capacitances can be ignored

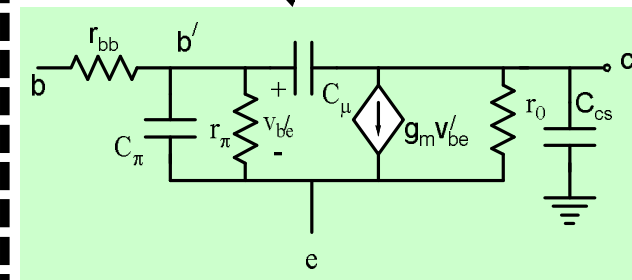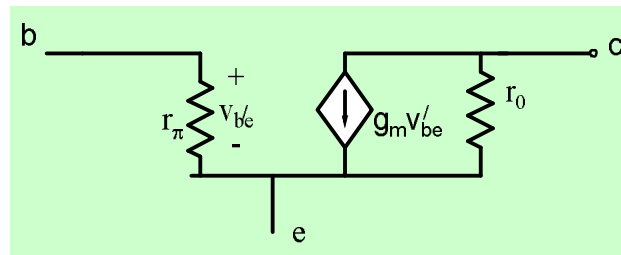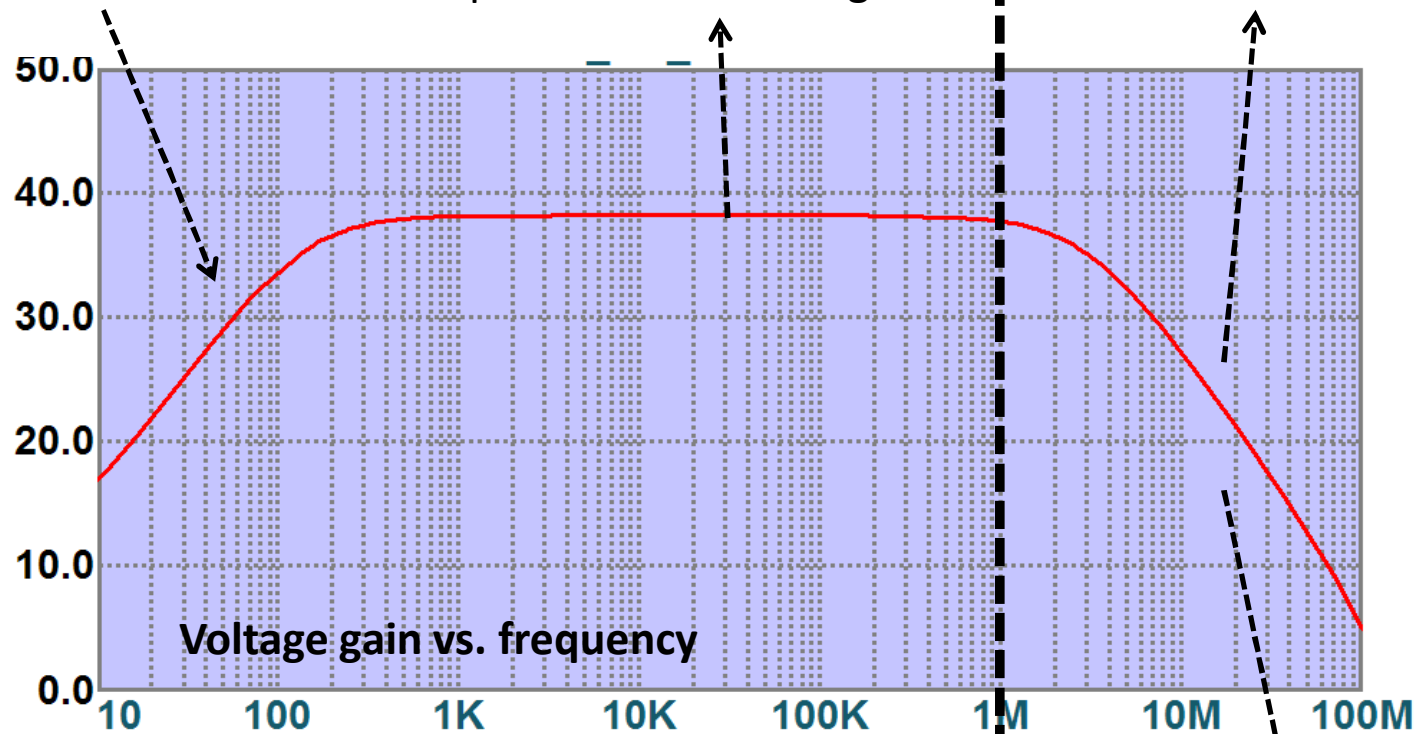High frequency  
behavior is caused by  
internal transistor  
capacitances



# Simple Common Emitter Amplifier

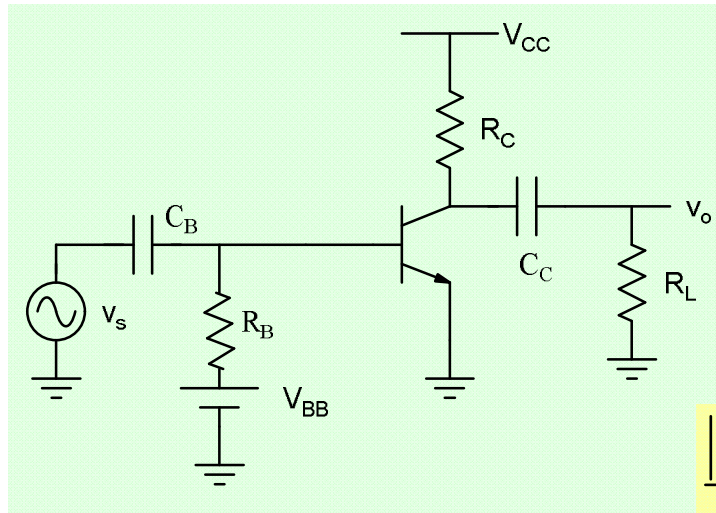




$$A_{VO} = -g_m R_C \Rightarrow |A_{VO}| = \frac{I_{CQ} R_C}{V_T}$$

$$R_{in} = R_B \parallel r_\pi \sim r_\pi = \frac{V_T}{I_{CQ}} \beta$$

$$v_{om} = \text{Min} \left\{ V_{CEQ} - V_{CEsat}; \left( I_{CQ} \times R_C \parallel R_L \right) \times \left( \frac{HD_2}{25} \right) \right\}$$



$$R_O = R_C \parallel r_o \sim R_C$$

$$\frac{|A_{VO}| \times R_{in}}{R_O} \leq \beta$$

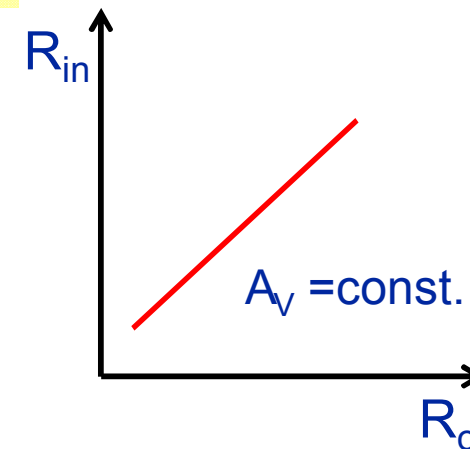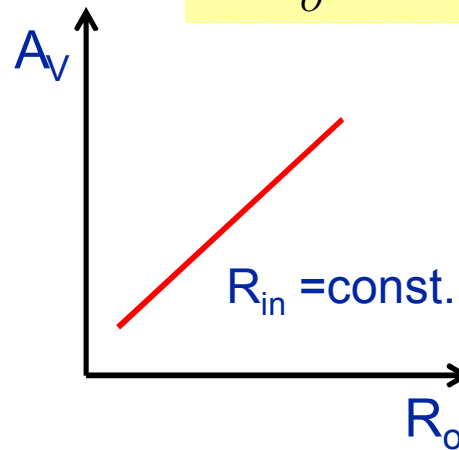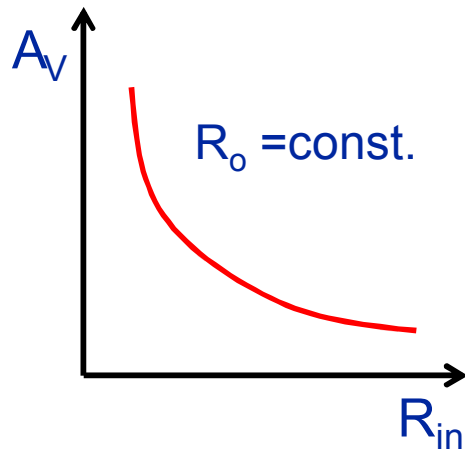

The performance of the BJT voltage amplifier is ultimately limited by  $\beta$ .

# Output Voltage Swing

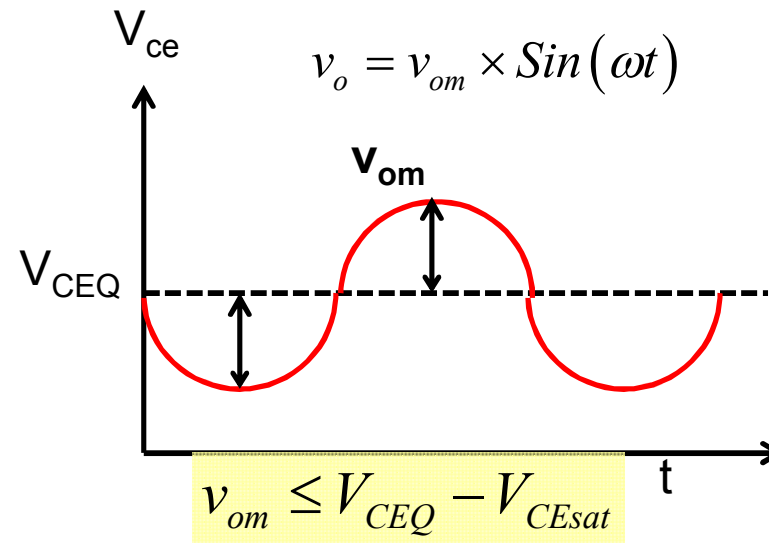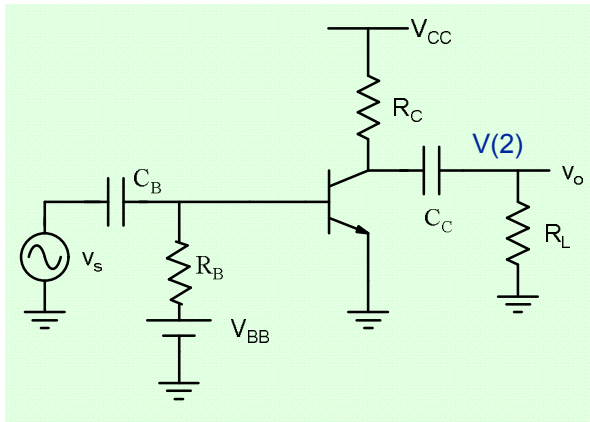


$$\frac{v_{beo}}{V_T} = m$$

$$\frac{i_c}{I_{CQ}} = m \times \sin(\omega t) + \frac{(m \times \sin(\omega t))^2}{2} + \dots$$

$$\frac{i_c}{I_{CQ}} = m \times \sin(\omega t) - \frac{m^2}{4} \cos(2\omega t) + \dots$$


$$HD_2(\%) = \frac{v_{beo}}{V_T} \times 25$$
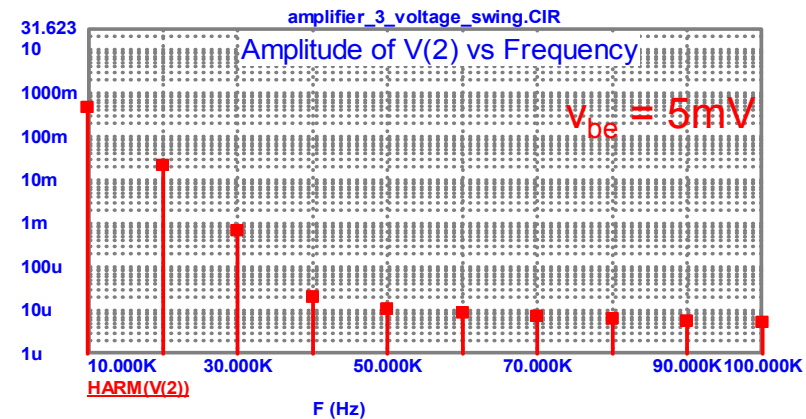
$$V_{om} \leq (I_{CQ} \times R_C \parallel R_L) \times \left( \frac{HD_2}{25} \right)$$




$$v_{om} = \text{Min} \left\{ V_{CEQ} - V_{CEsat}; \left( I_{CQ} \times R_C \parallel R_L \right) \times \left( \frac{HD_2}{25} \right) \right\}$$
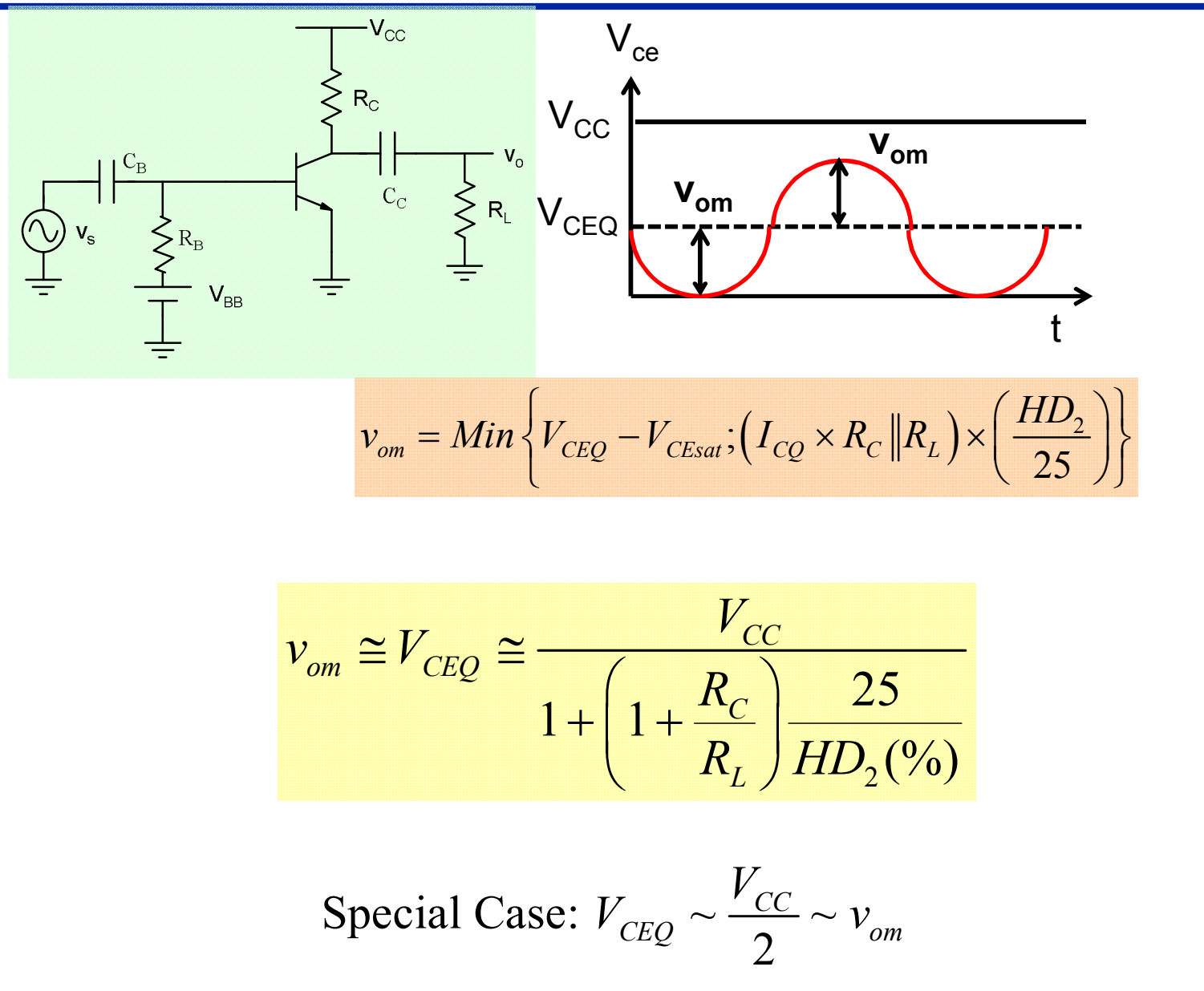
# Design For Maximum Output Voltage Swing





# CE Amplifier With Emitter Resistance

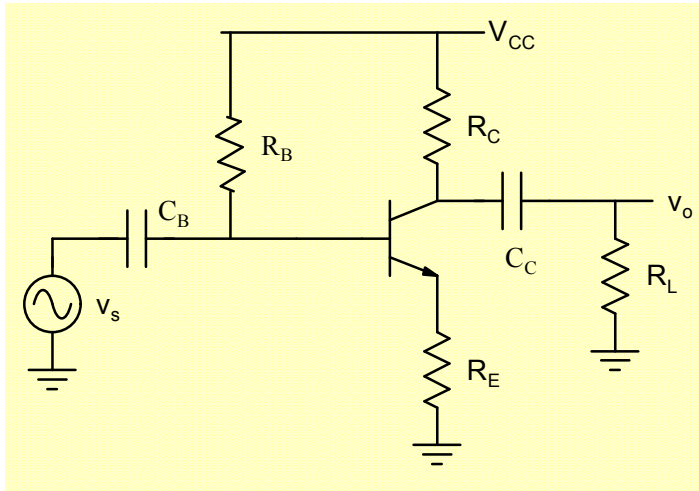

$$A_{VO} \cong -\frac{g_m R_C}{1 + g_m R_E} \quad R_O \sim R_C$$


$$R_{in} = R_B \parallel (r_\pi + (1 + \beta)R_E)$$

$$v_S = v_{be} \times (1 + g_m R_E)$$

Emitter Resistance results in **negative feedback** which improves linearity and reduces distortion

If distortion is sufficiently reduced then  $V_{CEQ} \sim \frac{V_{CC}}{2}$  is a good bias point for maximum output swing

# Stability of Bias Point

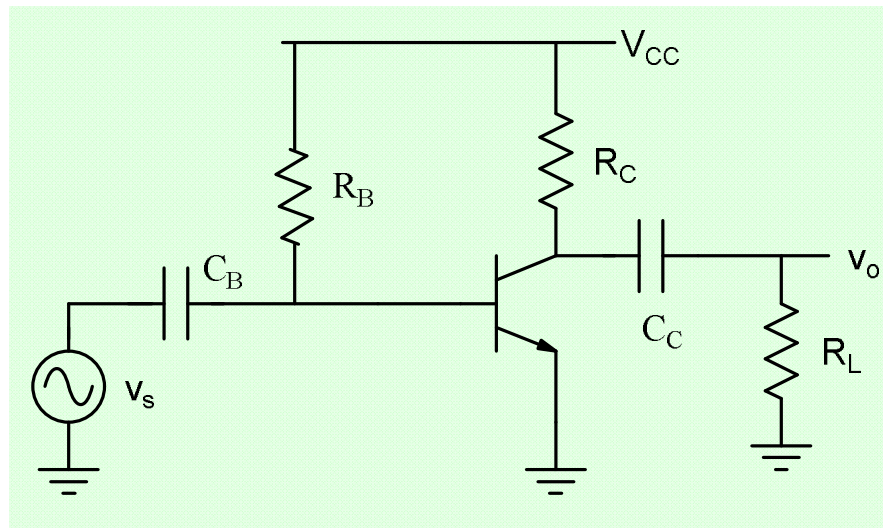

$$S_{\beta} = \frac{\Delta I_{CQ} / I_{CQ}}{\Delta \beta / \beta} = 1$$


Bias Point :  $I_{CQ}, V_{CEQ}$

$$R_{in} \sim r_{\pi} = \frac{V_T}{I_{CQ}} \beta$$

$$|A_{VO}| = \frac{V_{CC} - V_{CEQ}}{V_T}$$

$$v_{om} = \text{Min} \left\{ V_{CEQ} - V_{CEsat}; \left( I_{CQ} \times R_C \parallel R_L \right) \times \left( \frac{HD_2}{25} \right) \right\}$$

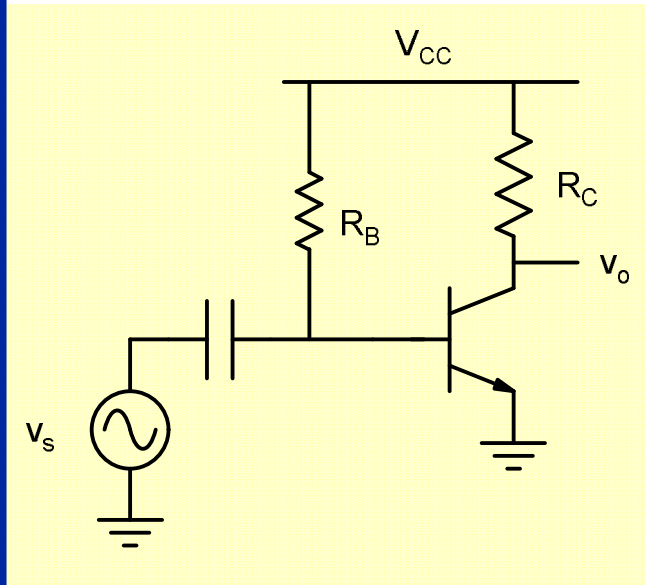
# Stable Biasing with dual Supply Voltage



$$I_{CQ} = \beta \times I_{BQ}$$

$$I_{BQ} = \frac{V_{CC} - 0.7}{R_B}$$
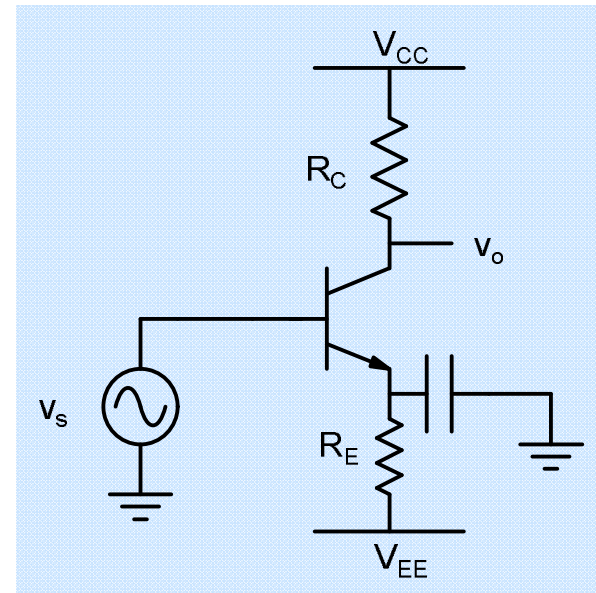
$$S_\beta = \frac{\Delta I_{CQ} / I_{CQ}}{\Delta \beta / \beta} = 1$$




$$I_{CQ} = \left( \frac{\beta}{\beta + 1} \right) I_{EQ}$$

$$I_{EQ} = \frac{-0.7 - V_{EE}}{R_E}$$

$$S_\beta \ll 1$$
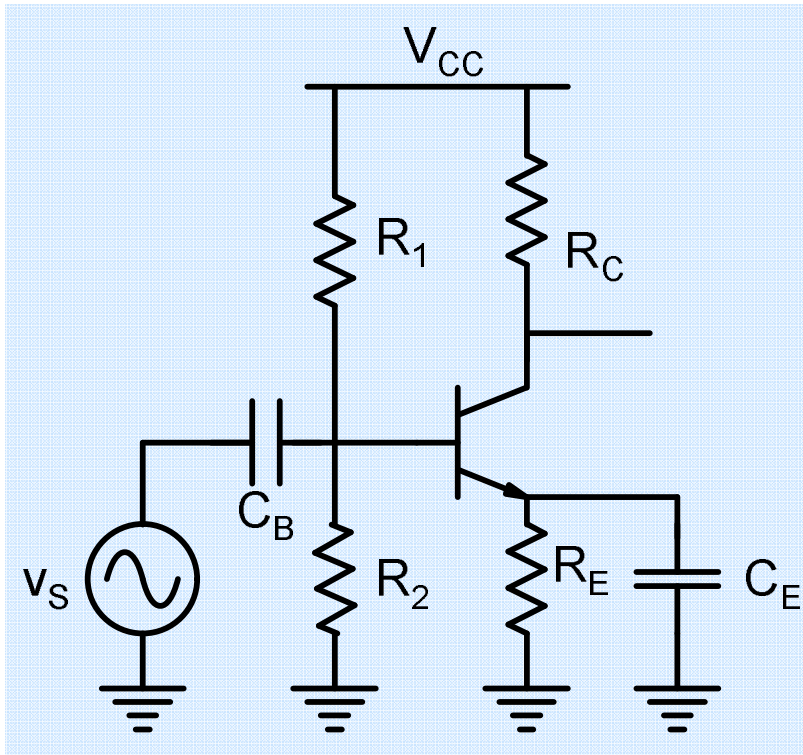
# Stable Biasing with Single Supply Voltage



$$I_C = \frac{V_{BB} - V_{BE}}{\frac{R_B}{\beta} + R_E}$$


$$S = \frac{\Delta I_C / I_C}{\Delta \beta / \beta} = \frac{1}{1 + \frac{R_E \beta}{R_B}}$$

$$R_E \gg \frac{R_B}{\beta}$$


$$y = \frac{I_{C2} - I_{C1}}{I_{C1}} = \frac{(\beta_2 - \beta_1)x}{\beta_1 \times (x + \beta_2)}; x = \frac{R_B}{R_E}$$

$$x = \frac{R_B}{R_E} \leq \frac{y \beta_2 \beta_1}{\beta_2 - \beta_1 \times (1 + y)}$$

# Lower Cutoff Frequency

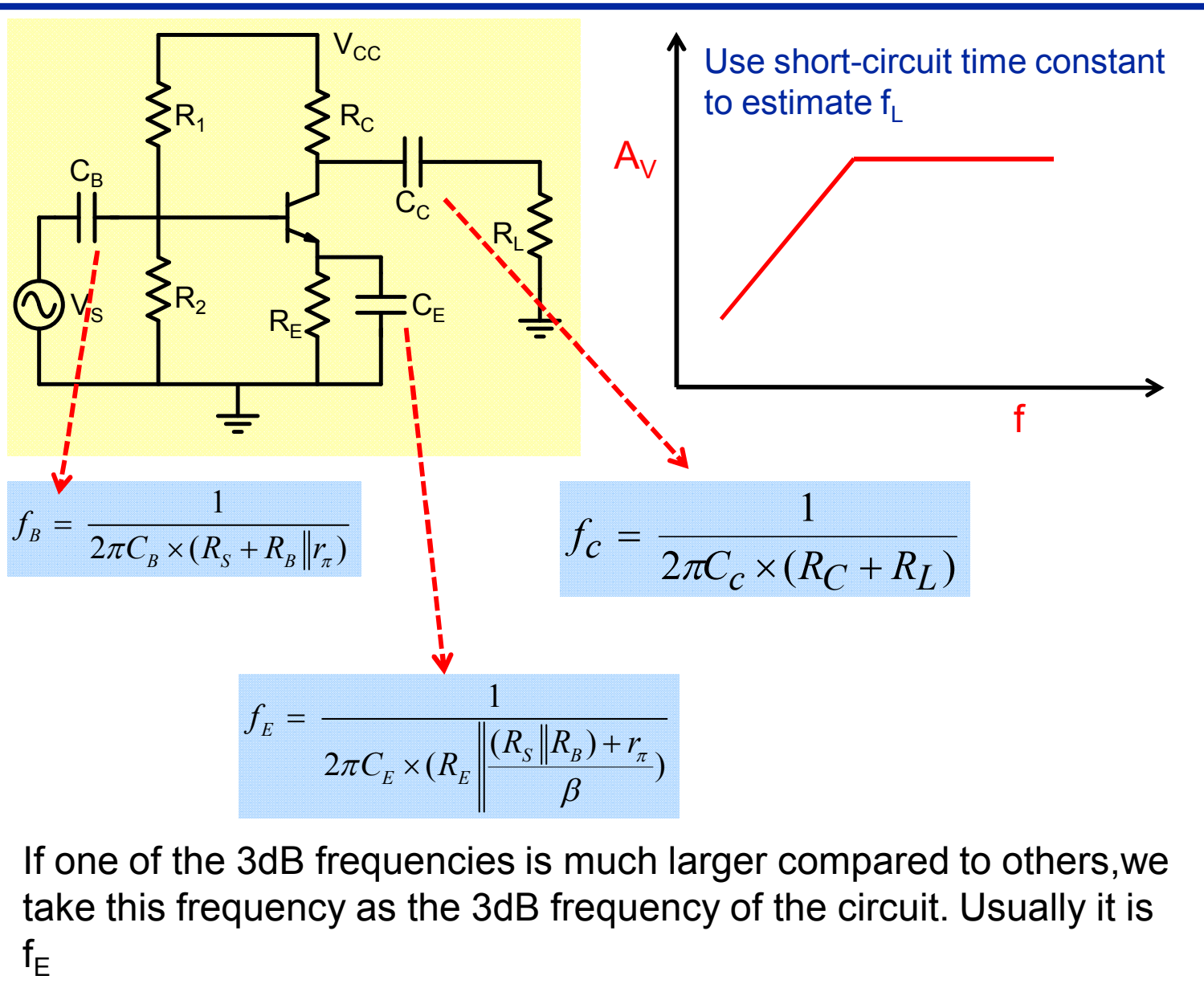


# Upper Cutoff Frequency

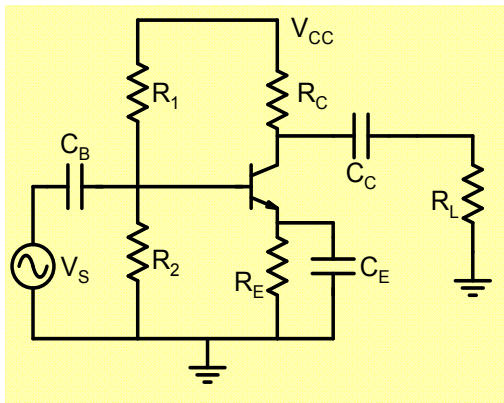


$$R'_S = (R_S \parallel R_B) + r_{bb}$$

$$R'_C = R_C \parallel R_L$$

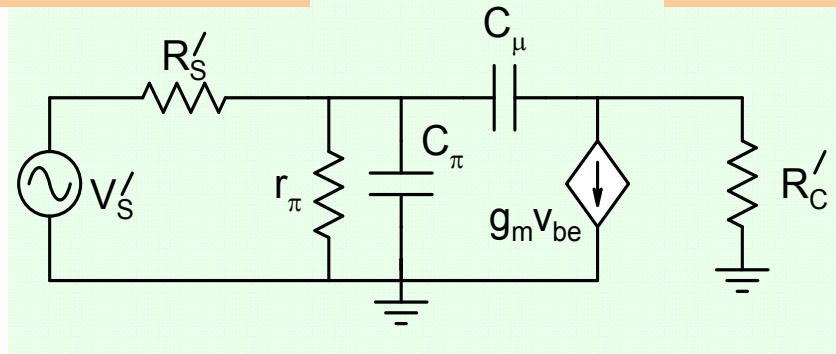

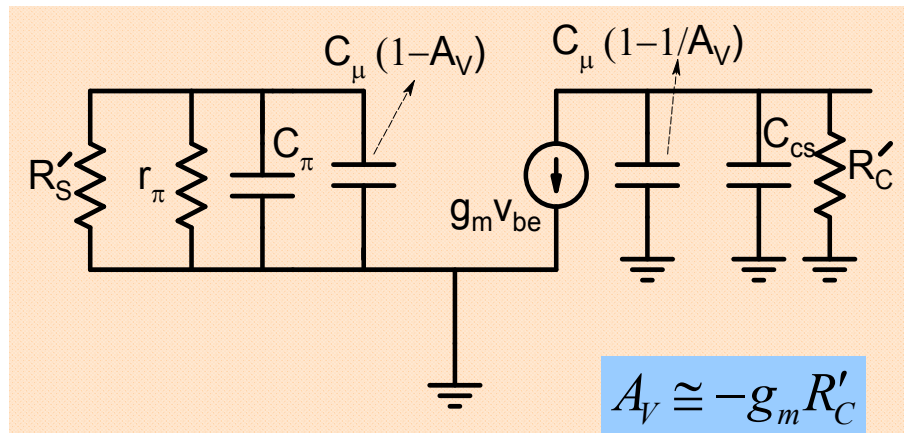
**Method:** Open circuit time constant.  
Apply Miller's theorem to simplify



$$\omega_H \cong \frac{1}{(R'_S \parallel r_\pi) \{C_\pi + C_\mu (1 + g_m R'_C)\} + R'_C C_\mu}$$
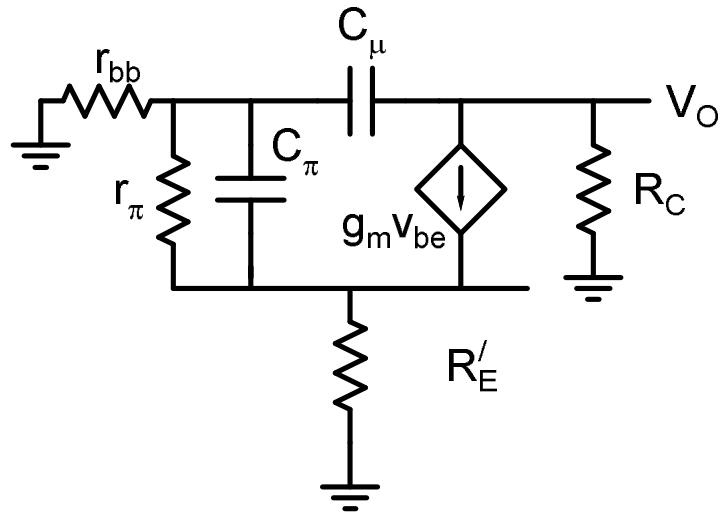
# Upper Cutoff Frequency

Open circuit time constant : General expressions




$$R_{\pi} = \left( 1 + \frac{R'_E}{r_{bb}} \right) \left( r_{\pi} \parallel \frac{r_{bb}}{1 + g_m R'_E} \right)$$

$$R_{\mu} = r_{bb}(1 - x) + R_C \times (1 + x\beta)$$

$$x = \frac{r_{bb}}{r_{bb} + r_{\pi} + \beta R'_E}$$

$$f_H \cong \frac{1}{2\pi \times (R_{\pi} C_{\pi} + R_{\mu} C_{\mu})}$$

# Design Perspective



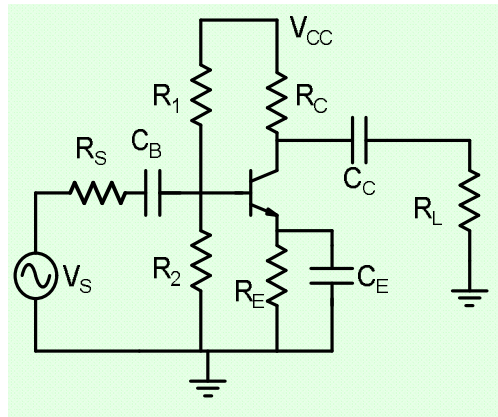


$$A_V = -\frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$R_{in} = r_\pi \parallel R_B$$

$$R_o = R_C$$

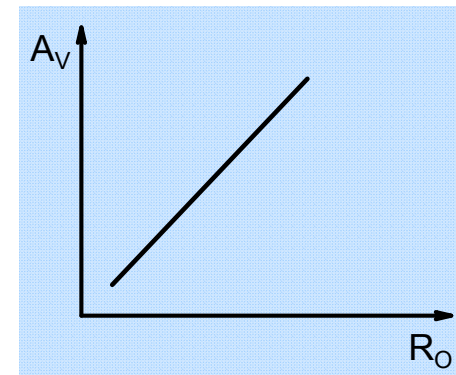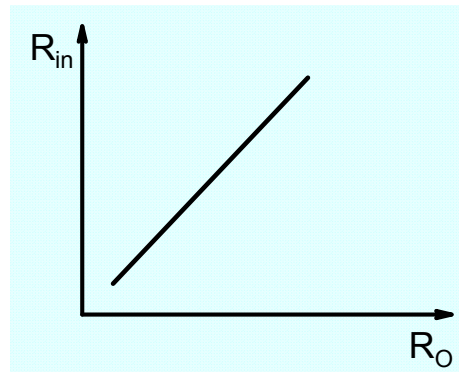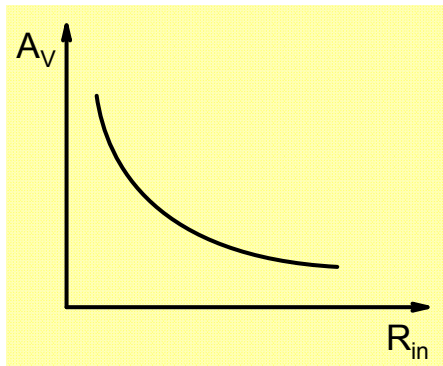Tradeoff between Voltage Gain, Input Resistance and Output Resistance




$$\frac{A_V \times R_{in}}{R_o} = \beta \times \frac{1}{1 + \frac{R_o}{R_L}} \times \frac{1}{1 + \frac{r_\pi}{R_B}}$$

$$\frac{A_V \times R_{in}}{R_o} \leq \beta$$




# Gain-Input resistance Tradeoff

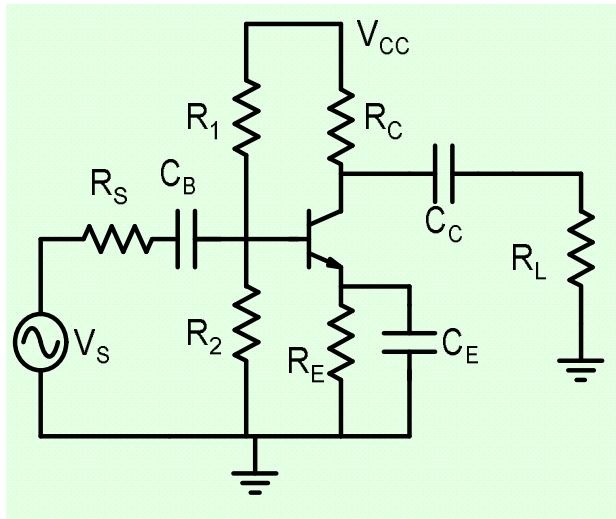

$$A_V = -g_m \times R_C \parallel R_L$$


$$R_{in} = r_\pi \parallel R_B$$

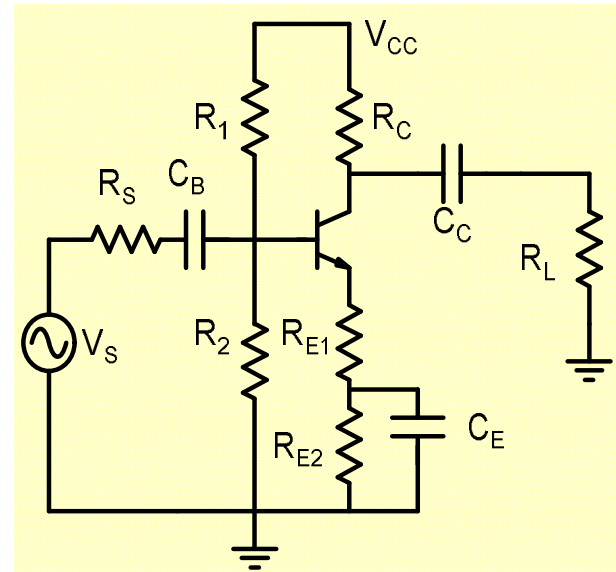

$$A_V = -\frac{g_m}{1 + g_m R_{E1}} \times R_C \parallel R_L$$

$$R_{in} = r_\pi \times (1 + g_m R_{E1}) \parallel R_B$$

# Gain-Swing Tradeoff

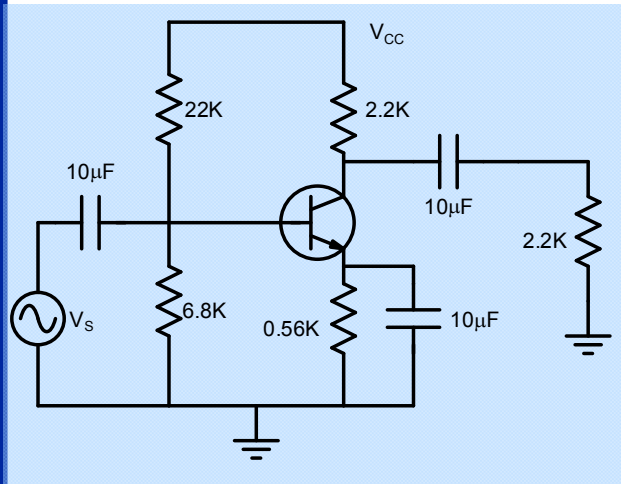

$$A_V = -\frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$V_{om} = \text{Min.} \left\{ (V_{CEQ} - V_{CEsat.}), \frac{H_{D2}}{25} \times I_{CQ} R_C \parallel R_L \right\}$$


$$\beta = 100; V_{CC} = 12V$$

$$I_{CQ} = 3.4mA; V_{CEQ} = 2.57V$$

$$A_V = 110.7; R_{in} = 0.82K; R_o = 2.2K$$

$$v_{om} = 0.39V @ THD = 1.9\%$$

$$f_L = 1.67kHz; f_H = 5.8MHz$$

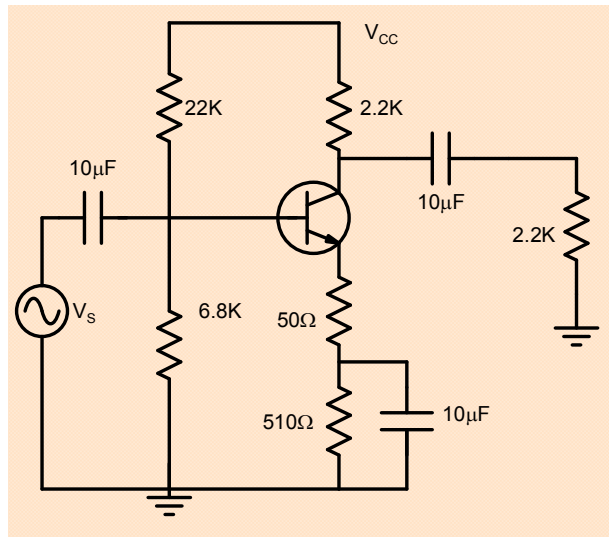

$$\beta = 100$$


$$I_{CQ} = 3.4mA; V_{CEQ} = 2.57V$$

$$A_V = 18.2; R_{in} = 2.76K; R_o = 2.2K$$

$$v_{om} = 2V @ THD = 1.8\%$$

$$f_L = 0.3kHz; f_H = 26.46MHz$$

# Gain-Bandwidth Tradeoff

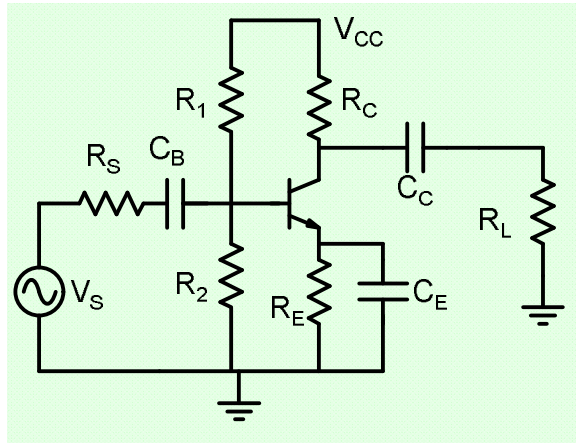

$$\omega_L = \frac{1}{C_E \times (R_E \parallel \frac{(R_S \parallel R_B) + r_\pi}{\beta})} \cong \frac{\beta}{C_E \times r_\pi}$$

$$\omega_L \times R_{in} = \frac{\beta}{C_E}$$


$$\frac{A_V \times R_{in}}{R_O} \leq \beta$$

$$\frac{A_V}{R_O \times \omega_L} \leq C_E$$


Upper Cutoff Frequency

$$\omega_H \cong \frac{1}{(R'_S \parallel r_\pi) \{C_\pi + C_\mu (1 + g_m R'_C)\} + R'_C C_\mu}$$

$$A_V \cong -g_m R'_C$$

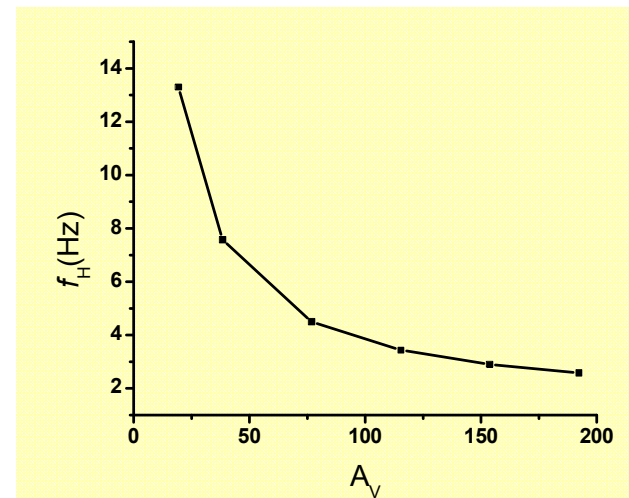

# Design of CE Amplifier

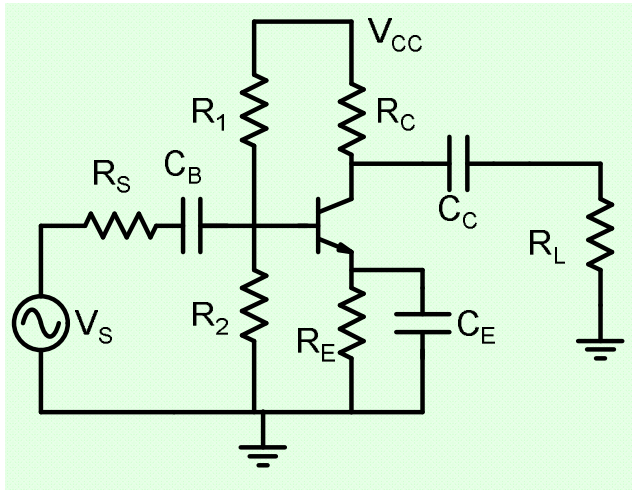

Design variables:

$$R_1, R_2, R_C, R_E$$

$$C_B, C_C, C_E$$

$$V_{CC}$$

Transistor

Design variables:

$$\{\text{Bias point: } I_{CQ}, V_{CEQ}, V_E\}$$

$$R_C$$

$$C_E$$

$$\text{Transistor } \{\beta, \tau_F, C_{jeo}, C_{jco}\}$$

Specifications:

$$A_v \geq 100 \pm 20\% \text{ at } T=300\text{K}$$

$$R_o \leq 2.2k$$

$$R_{in} \geq 0.75k$$

$$v_{om} \geq 0.35V \text{ with THD} \leq 2\%$$

$$f_L \leq 2 \text{ kHz}$$

$$f_H \geq 5\text{MHz}$$

$$R_L = 2.2k; R_S \sim 50\Omega$$

$$\text{Constraints : } V_{CC} \leq 9V; \text{Low cost; Low power}$$

$$I_{CQ} = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE(on)}}{\frac{R_B}{\beta} + R_E}; R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$S = \frac{\Delta I_{CQ} / I_{CQ}}{\Delta \beta / \beta} = \frac{1}{1 + \frac{\beta R_E}{R_B}}; x_b = \frac{R_B}{r_\pi}$$

$$V_{CC} = V_{CEQ} + I_{CQ}(R_C + R_E)$$

$$A_v = -\frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$R_{in} = r_\pi \parallel R_B$$


$$R_o = R_C$$

$$\omega_L = \frac{1}{C_E \times (R_E \parallel \frac{(R_S \parallel R_B) + r_\pi}{\beta})}$$

$$V_{om} = \text{Min.} \left\{ (V_{CEQ} - V_{CEsat.}), \frac{H_{D2}}{25} \times I_{CQ} R_C \parallel R_L \right\}$$

$$\omega_H \cong \frac{1}{((R_S \parallel R_B) + r_{bb}) \parallel r_\pi \{C_\pi + C_\mu(1 + g_m R_C \parallel R_L)\} + C_\mu R_C \parallel R_L}$$

# Design of CE Amplifier

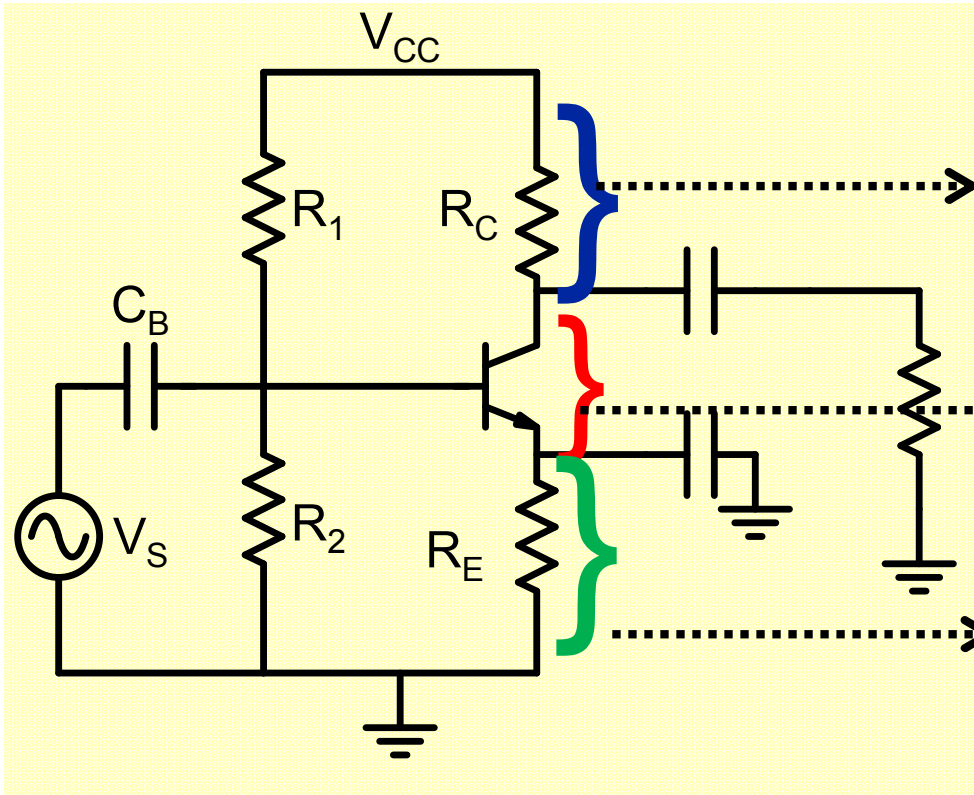

$$I_{CQ} \times R_C \parallel R_L = A_V \times V_T$$

$$I_{CQ} \times R_C \parallel R_L \geq v_{om} \times \frac{25}{HD_2}$$

$$V_{CEQ} \geq v_{om} + 0.2$$

$$V_E = \frac{x_b}{x} \times V_T \times \beta$$

$$x = \frac{R_B}{R_E} \leq \frac{y\beta_2\beta_1}{\beta_2 - \beta_1 \times (1 + y)}; y = \frac{I_{C2} - I_{C1}}{I_{C1}}; x_b = \frac{R_B}{r_\pi}$$

# CE Amplifier : Problems and Solutions

