


# Major Quiz 2 Solution

Date – 11.04.2019

Name: \_\_\_\_\_ Roll No.: \_\_\_\_\_ Section: \_\_\_\_\_

Total Marks: 40

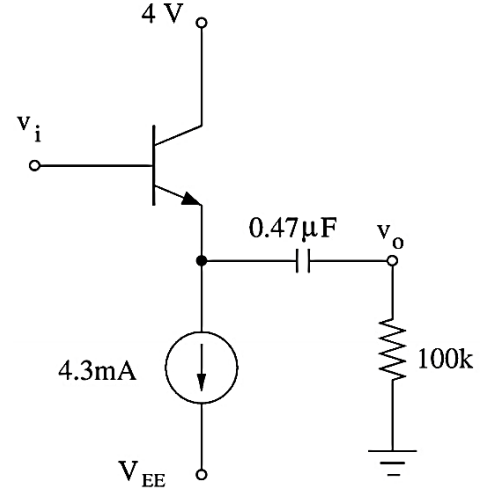**Q1.** Find the bias point ( $I_C$  and  $V_{CE}$ ) and the amplifier parameters ( $R_{in}$ ,  $R_o$ ,  $A_v$  and cut-off frequency  $f_p$ ) of the circuit below. (Si BJT with  $\beta = 200$ ,  $V_A = 150$  V, ignore Early effect in bias calculations). [12]



**Sol.:** Assume BJT is in Active mode.

$$V_{BE} = 0.7 \text{ V}, \quad I_C > 0 \text{ and } V_{CE} > 0.7 \text{ V}$$

$$I_E = 4.3 \text{ mA} \approx I_C$$

$$I_B = \frac{I_C}{\beta} = 21.5 \mu\text{A}$$

$$V_{BE} = 0 - V_E \rightarrow V_E = -0.7 \text{ V}$$

$$V_{CE} = 4 - V_E = 4.7 \text{ V} > 0.7 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = \frac{4.3 \times 10^{-3}}{26 \times 10^{-3}} = 165 \text{ mA/V}$$

$$r_o \approx \frac{V_A}{I_C} = \frac{150}{4.3 \times 10^{-3}} = 34.9 \text{ k}\Omega, \quad r_\pi = \frac{V_T}{I_B} = \frac{\beta}{g_m} = 1212 \Omega$$

**Amplifier Parameters:** This is an emitter follower ( $R_E = \infty$ ).

$$\frac{v_o}{v_i} = \frac{g_m(r_o || R_E || R_L)}{1 + g_m(r_o || R_E || R_L)}$$

$$r_o || R_E || R_L = 34.9 \text{ k} || \infty || 100 \text{ k} = 25.9 \text{ k}$$

$$g_m(r_o || R_E || R_L) = 4269$$

$$A_v = \frac{v_o}{v_i} = \frac{4269}{1 + 4269} \approx 1$$


$$R_i = R_B || [r_\pi + (1 + \beta)(r_o || R_E || R_L)] = 1212 + 201 \times 25.9 \text{ k} = 5.2 \text{ M}\Omega$$

$$R_o \approx R_E || \frac{r_\pi + R_B || R_{sig}}{1 + \beta} \approx \frac{r_\pi}{\beta} = 6.06 \Omega$$

**Cut-off frequency:**

$$f_p = \frac{1}{2\pi[R_L + R_o]C_{c2}} = \frac{1}{2\pi(100 \times 10^3 + 6.06) \times 0.47 \times 10^{-6}} = 3.39 \text{ Hz}$$

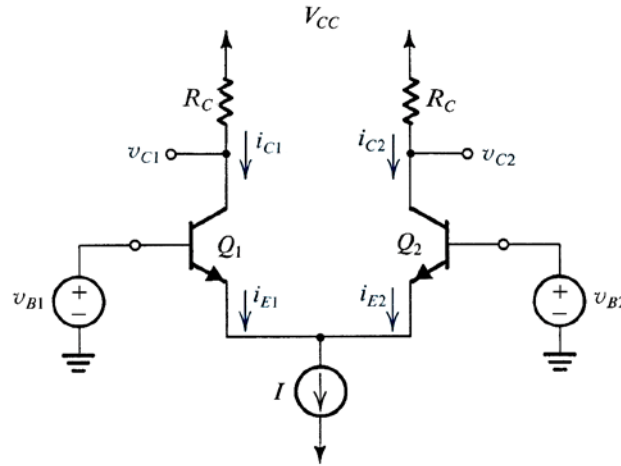**Q3.** Consider the differential amplifier in figure shown below, and let the BJT  $\beta$  be very large:



- What is the largest input common-mode signal that can be applied while the BJTs remain comfortably in the active region with  $V_{CB} = 0$ ? [2]
- If an input difference signal is applied that is large enough to steer the current entirely to one side of the pair, what is the change in voltage at each collector (from the condition for which  $V_{id} = 0$ )? [2]
- If the available power supply  $V_{CC}$  is 5 V, what value of  $I * R_C$  should you choose in order to allow a common-mode input signal of  $\pm 3$  V? [2]
- For the value of  $I * R_C$  found in (c), select values for  $I$  and  $R_C$ . Use the largest possible value for  $I$  subject to the constraint that the base current of each transistor (when  $I$  divides equally) should not exceed  $2\mu A$ . Let  $\beta = 100$ . [4]

**Sol.:**

**a)**

$$V_{CMmax} = V_{C1} = V_{C2} = V_{CC} - \frac{I}{2} * R_C$$

**b)** if the current is steered to  $Q_1$ , then

$$V_{C1} = V_{CC} - IR_C \rightarrow \text{a change of } -\frac{I}{2} R_C$$

$$V_{C2} = V_{CC} \rightarrow \text{a change of } +\frac{I}{2} R_C$$

**c)** For  $V_{CC} = 5V$ ,

$$V_{CMmax} = 3 = 5 - \frac{I}{2} R_C \rightarrow I * R_C = 4V$$

**d)**

$$\frac{I/2}{\beta + 1} \leq 2\mu A \rightarrow I \leq 4(\beta + 1)\mu A$$

$$I = 4 * 101\mu A = 0.404mA$$

Let's select  $I = 0.4mA$ .

$$R_C = \frac{4V}{I} = \frac{4V}{0.4mA} = 10K\Omega$$

**Q3.** In a differential amplifier using a 6-mA emitter bias current source, the two BITs are not matched. Rather, one has one-and-a-half times the emitter junction area of the other. For a differential input signal of zero volts, what do the collector currents become? What difference input is needed to equalize the collector currents? Assume  $\alpha = 1$ . [6]

**Sol.:** The current will divide in the two transistors in proportion of their emitter areas. Thus, with no input,

$$I_{E1} = 1.5 I_{E2}$$

$$I_{E1} + I_{E2} = 6mA$$

$$I_{E2} \cong I_{C2} = 2.4mA$$

$$I_{E1} \cong I_{C1} = 3.6mA$$

To equalize the collector currents, we apply a differential signal  $V_d = V_{B2} - V_{B1}$ .

Now, we know that,

$$i_{E1} = I_{SE1} e^{(V_{B1}-V_E)/V_T}, i_{E2} = I_{SE2} e^{(V_{B2}-V_E)/V_T}$$

Now, we have


$$I_{SE1} = 1.5 I_{SE2}$$

For  $I_{E1} = I_{E2}$ , we have,

$$1 = 1.5 e^{(V_{B1}-V_{B2})/V_T}$$

$$V_{B2} - V_{B1} = 10.1mV$$

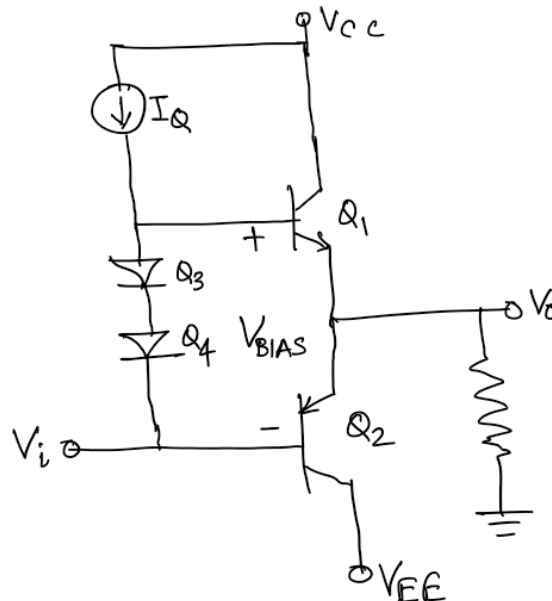**Q4.** Choose the saturation currents of the diode connected transistors  $Q_3$  and  $Q_4$  (both are identical) in the circuit shown below, such that  $V_{BIAS} = 1.1V$  for  $I_Q = 100\mu A$ . Now, if each of the output transistors ( $Q_1$  and  $Q_2$ ) has its area four times that of  $Q_3$  (or  $Q_4$ , same area), determine the standby power dissipation of the circuit. Assume  $V_{CC} = -V_{EE} = 5V$ . [12]



**Sol.:**

Diodes Q<sub>3</sub> and Q<sub>4</sub> are identical, and they are carrying the same bias currents I<sub>Q</sub>. Hence, the voltage drop across each of Q<sub>3</sub> and Q<sub>4</sub> will be same, denoted by V<sub>D</sub>. Then the bias voltage V<sub>BIAS</sub> can be written as,

$$V_{BIAS} = 2V_D = 2V_T \ln\left(\frac{I_Q}{I_S}\right)$$

Where I<sub>S</sub> is the saturation current of Q<sub>3</sub> (and also of Q<sub>4</sub>). Noting that V<sub>BIAS</sub> = 1.1V and I<sub>Q</sub> = 100μA, we get

$$I_S = \frac{I_Q}{e^{\frac{V_{BIAS}}{2V_T}}} = \frac{100 * 10^{-6}}{e^{\frac{1.1}{2*0.026}}} = 6.5 * 10^{-14} A$$

This is the required saturation current of Q<sub>3</sub> (and Q<sub>4</sub>) i.e.

$$I_{S3} = I_{S4} = 6.5 * 10^{-14} A$$

As Q<sub>1</sub> and Q<sub>2</sub> have four times area, we have

$$I_{S1} = I_{S2} = 4I_{S3} = 26 * 10^{-14} A$$

To compute standby power, we need to find standby current as follows.

$$V_{BIAS} = V_{BE3} + V_{BE4} = V_{BE1} + V_{BE2}$$

Under standby condition V<sub>o</sub> = 0, which makes Q<sub>1</sub> and Q<sub>2</sub> carry the same quiescent current (= I<sub>standby</sub>). Neglecting base currents of Q<sub>1</sub> and Q<sub>2</sub>, the current in Q<sub>3</sub> and Q<sub>4</sub> is equal to bias current I<sub>Q</sub>. Thus,

$$\begin{aligned} V_T \ln\left(\frac{I_Q}{I_{S3}}\right) + V_T \ln\left(\frac{I_Q}{I_{S4}}\right) &= V_T \ln\left(\frac{I_{standby}}{I_{S1}}\right) + V_T \ln\left(\frac{I_{standby}}{I_{S2}}\right) \\ V_T \ln\left(\frac{I_Q^2}{I_{S3} * I_{S4}}\right) &= V_T \ln\left(\frac{I_{standby}^2}{I_{S1} * I_{S2}}\right) \end{aligned}$$

Or,

$$I_{standby} = I_Q \sqrt{\frac{I_{S1} * I_{S2}}{I_{S3} * I_{S4}}}$$

Using this equation in our case,

$$\begin{aligned} I_{standby} &= I_Q \frac{I_{S1}}{I_{S3}} = 4I_Q = 400\mu A \\ P_{standby} &= I_{standby} * (V_{CC} - V_{EE}) = 4mW \end{aligned}$$