


EE210: Microelectronics-I

Lecture-36 Review of BJT Circuits-part-2


<https://youtu.be/G-Vh233-ECM>

B. Mazhari
Dept. of EE, IIT Kanpur

CE Amplifier : Problems and Solutions

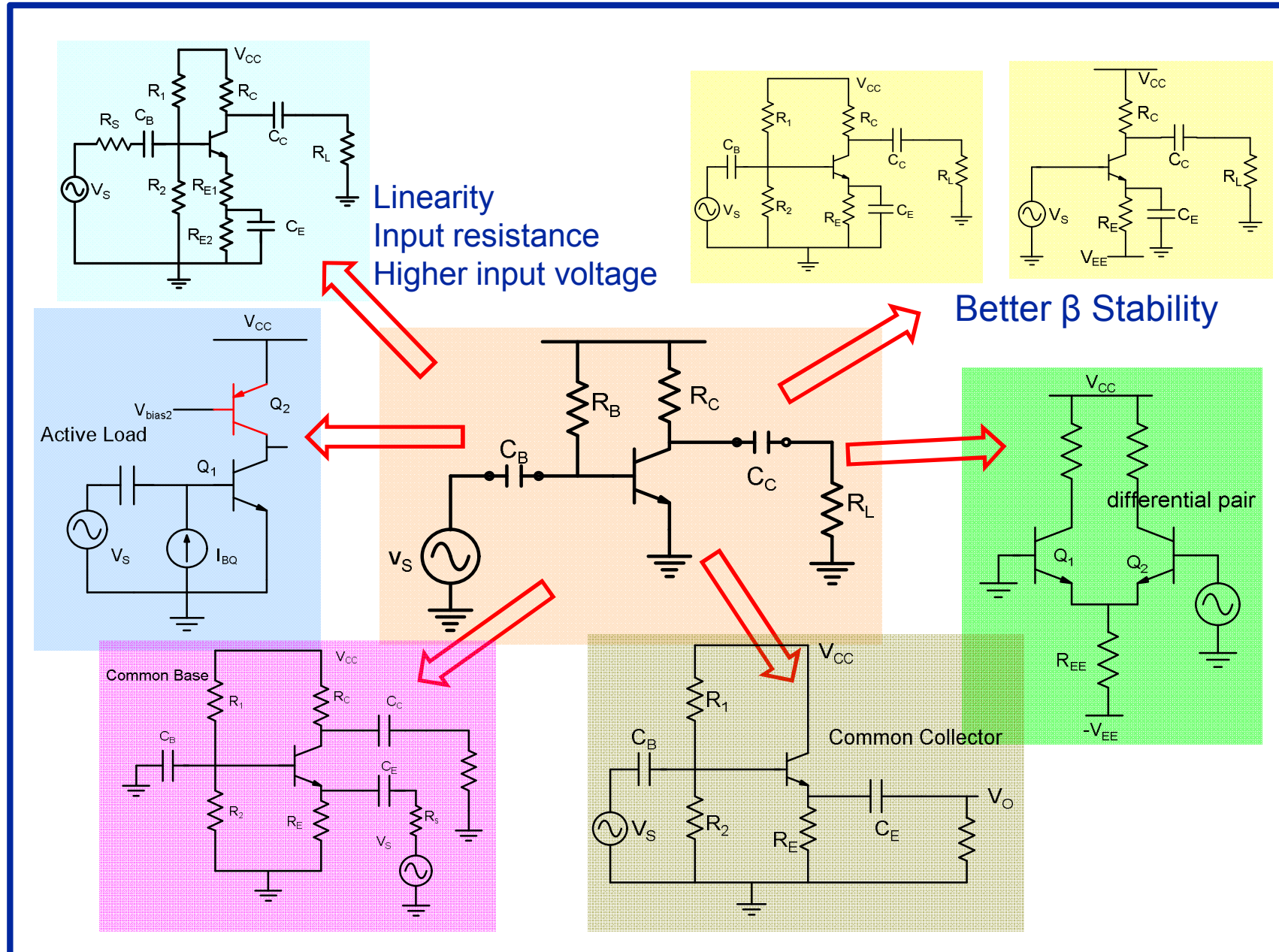

CB Amplifier

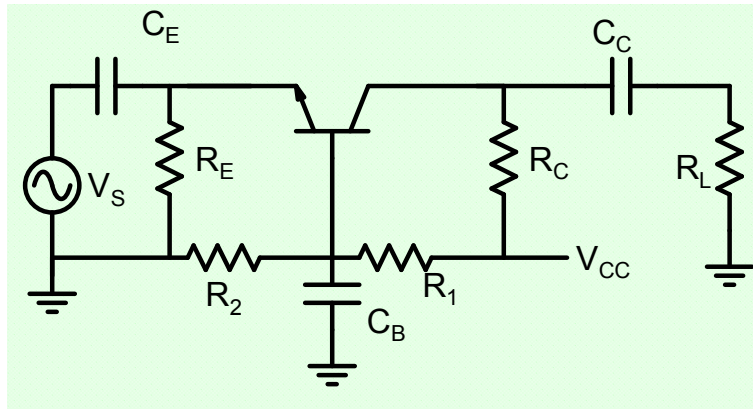


$$A_V = \frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$R_o = R_C$$

$$R_{in} \cong \frac{r_\pi}{\beta} \parallel R_E$$

$$\frac{A_V \times R_{in}}{R_O} \leq 1$$

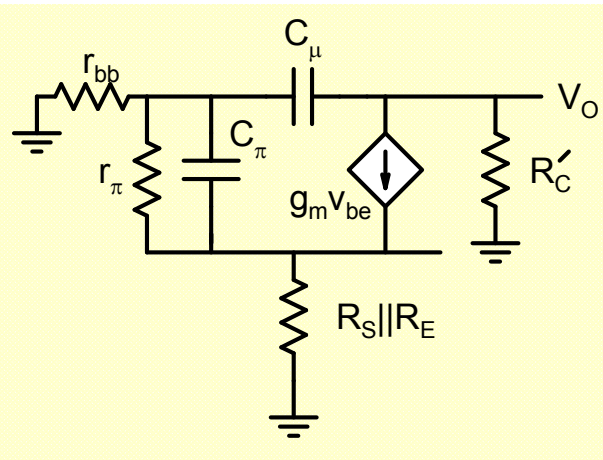



$$\frac{A_V(CE)}{A_V(CB)} \times \frac{R_{in}(CE)}{R_{in}(CB)} \times \frac{R_O(CB)}{R_O(CE)} \sim \beta$$

For large effective emitter resistance high bandwidth is obtained:

$$\omega_H \cong \frac{1}{(r_{bb} + R'_C)C_\mu + \frac{C_\pi}{g_m}}$$


Cascode Amplifier

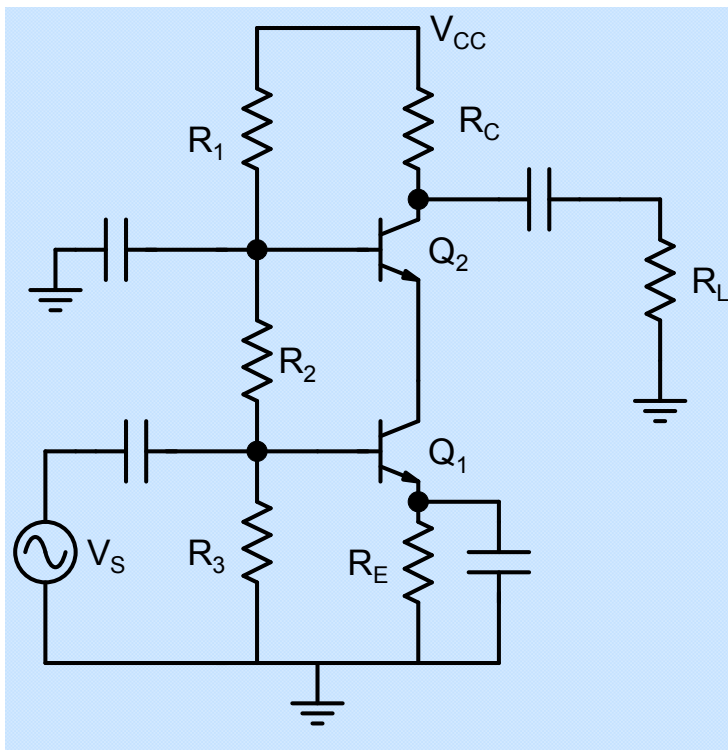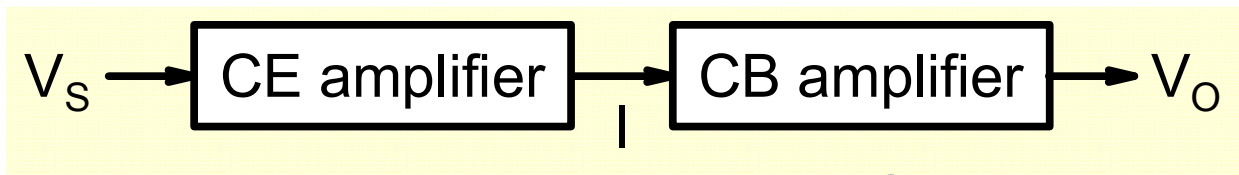Central idea: A CB amplifier has good frequency response when driven by current source and a CE configuration is a good voltage to current converter



1. Same voltage gain, input and output resistance as a CE amplifier
2. Improved upper cutoff frequency
3. Reduced sensitivity of upper cutoff frequency to increase in voltage gain

CC Amplifier-1

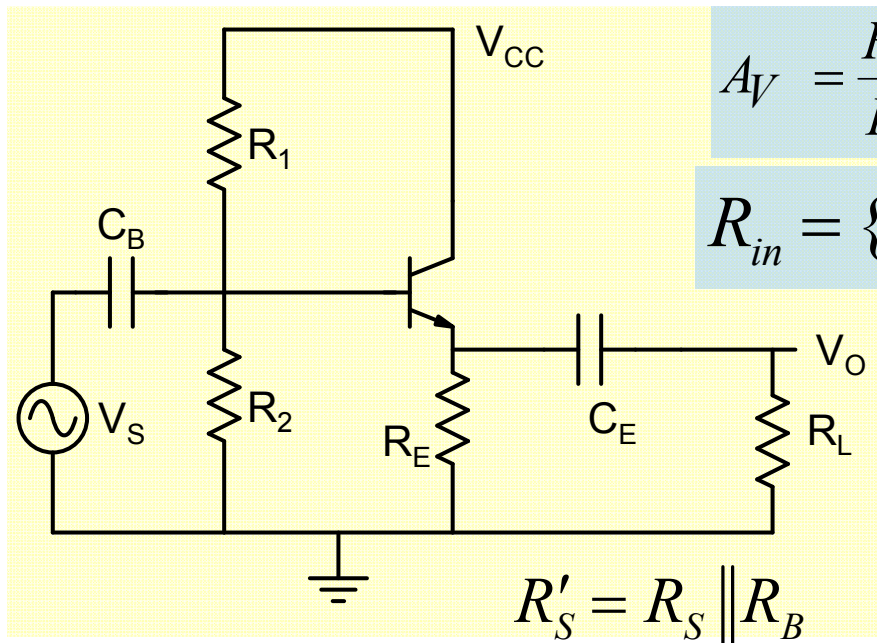

$$A_V = \frac{R'_S}{R_S} \times \frac{(\beta + 1) \times R'_E}{R'_S + r_\pi + (\beta + 1) \times R'_E}$$

$$R_{in} = \{r_\pi + (\beta + 1) \times R'_E\} \parallel R_B$$


$$R_O = \frac{(r_\pi + R'_S)}{\beta + 1} \parallel R_E$$

$$\frac{R_{in}}{R_O} \gg \beta$$

A common collector amplifier can deliver much lower output resistance and higher input resistance as compared to CE amplifier. Further it has higher swing and low distortion

$$v_O \leq I_{CQ} R_E \parallel R_L; V_O \leq V_{CC} - V_{BE} - I_{CQ} R_E$$

CC Amplifier-2

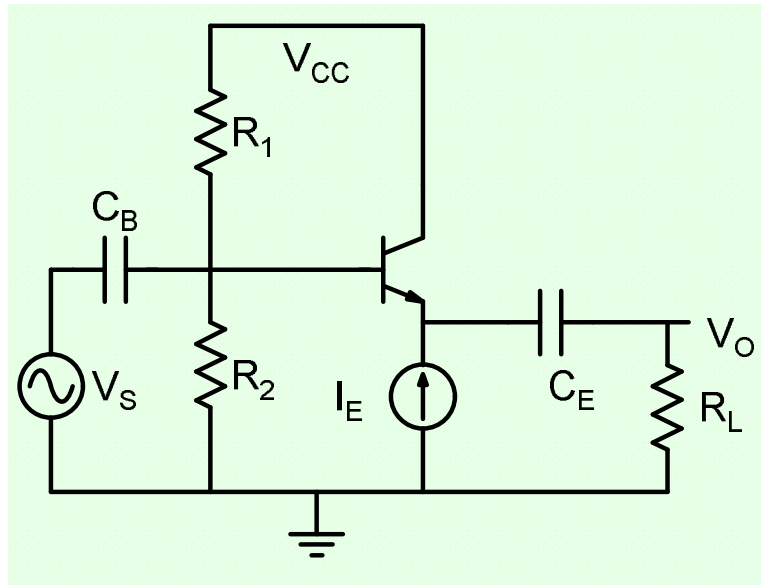


$$v_O \leq I_{EQ} R_L$$

$V_E - v_O > 0$ so as to maintain
Tr. implementing current source
in active region

$$H(s) \cong \frac{1 + \frac{C_\pi}{g_m} s}{1 + (R'_S C_\mu + \frac{C_\pi}{g_m}) s + \frac{R'_S}{g_m} C_\pi C_\mu s^2}$$

Due to pole-zero cancellation effect , bandwidth is often decided by non-dominant pole resulting in a very high bandwidth amplifier


Class AB Output stage

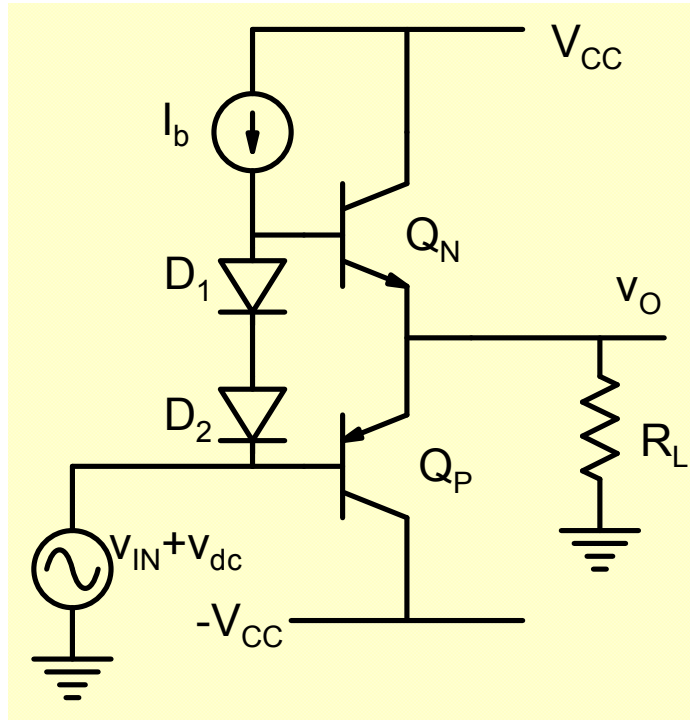

$$\eta < \frac{\pi}{4} \times \frac{v_{op}}{V_{CC}} \times 100$$

An efficient amplifier should take power from the supply only when power is to be delivered to the load !


Active Load

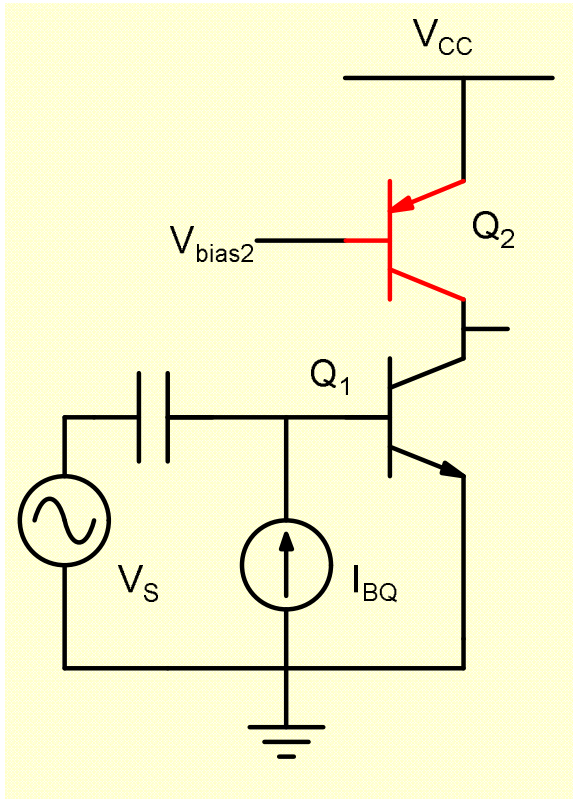

$$|A_V| = \frac{1}{V_T} \times \frac{V_{AN} \times V_{AP}}{V_{AN} + V_{AP}}$$

Active load allows us to obtain higher voltage gain without requiring very high supply voltage

Differential Amplifier-1

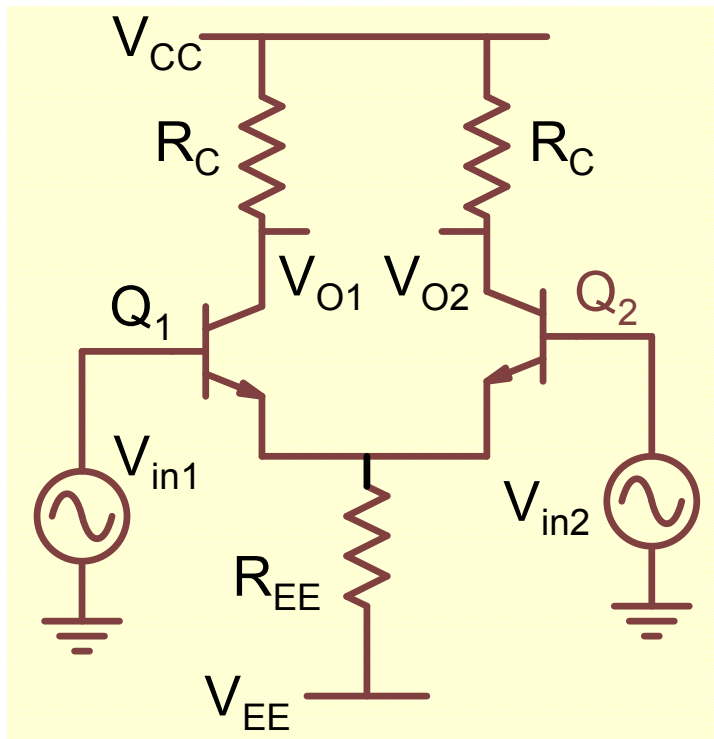

- An amplifier does not use any coupling or bypass capacitors thereby allowing monolithic implementation

- An amplifier that amplifies differential input signal and rejects common mode signals

$$A_{dm} = -0.5g_m R_C$$


$$R_o = R_C$$

$$R_{id} = 2r_\pi$$

$$A_{cm} = -\frac{g_m}{1 + 2g_m R_{EE}} R_C$$

$$R_{ic} = r_\pi + (1 + \beta) \times 2R_{EE}$$

Differential Amplifier-2


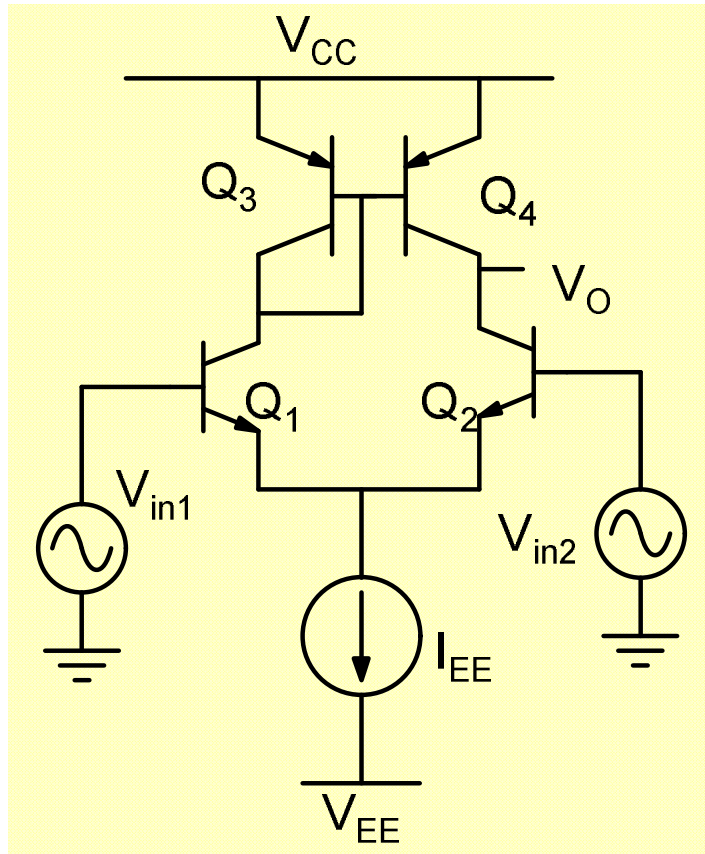


- This amplifier with current mirror load and current source biasing allows stable biasing, high differential mode gain and very low common mode gain


$$A_{dm} = \frac{v_o}{v_{id}} = 0.5g_m \times r_{o2} \parallel r_{o4}$$

The two inputs contribute in an opposite manner to the output voltage resulting in low common mode gain


Basic building blocks

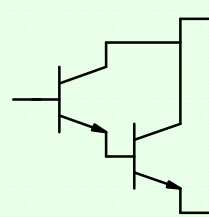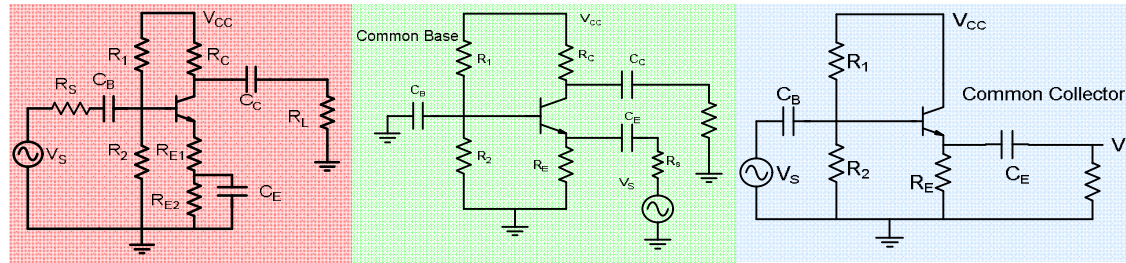


Darlington

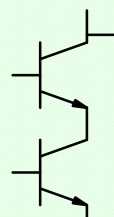


Cascode

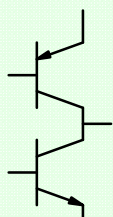


Active load

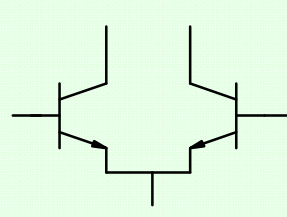

differential pair

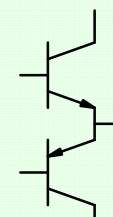


Class B Push-pull stage

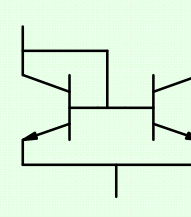

current mirror


Many new circuits can be created by connecting and combining these basic building blocks

Operational Amplifier-1

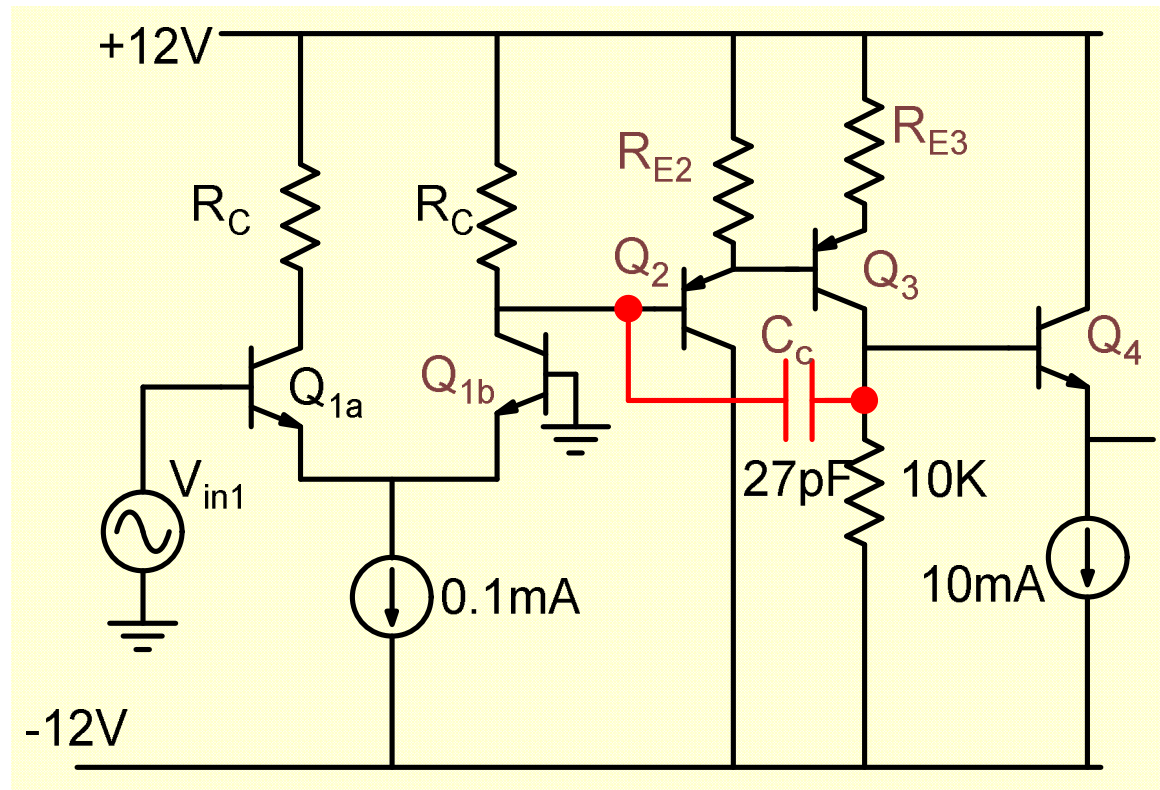





Note the use of complementary transistors and compensation capacitor

Operational Amplifier-2

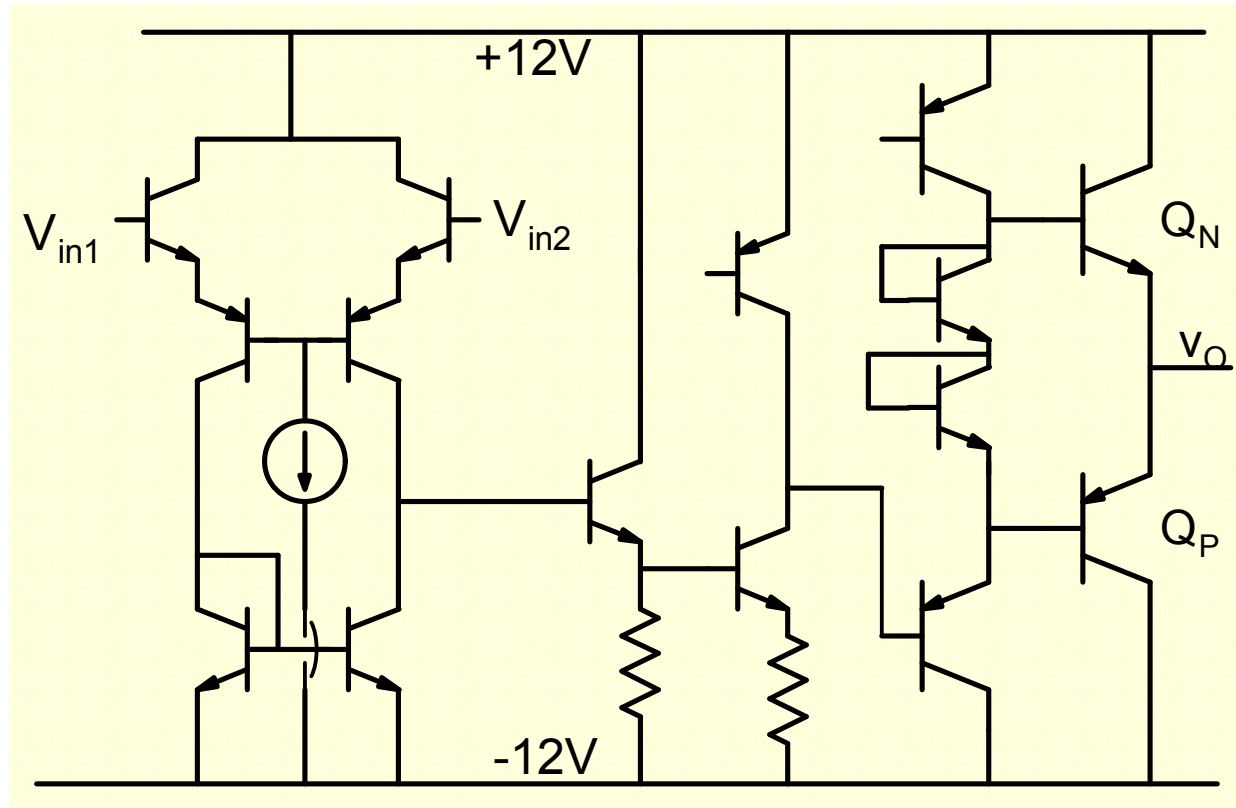


Note the use of active loads, class AB push-pull stage and NPN-PNP pair at the input

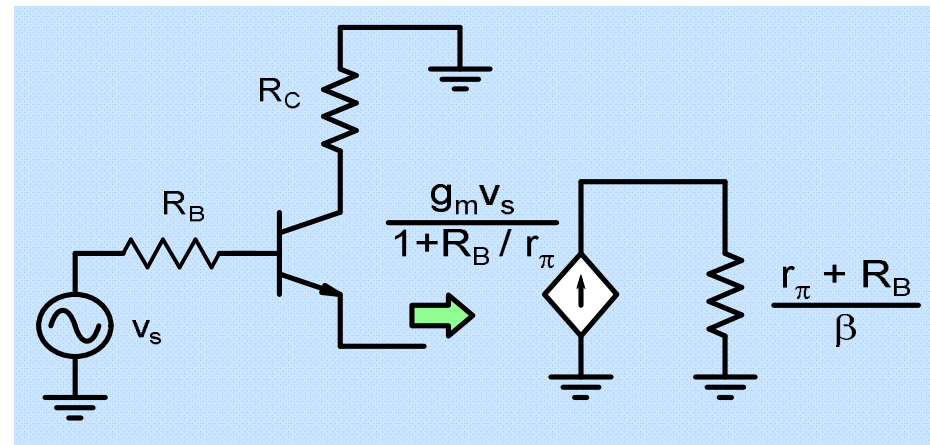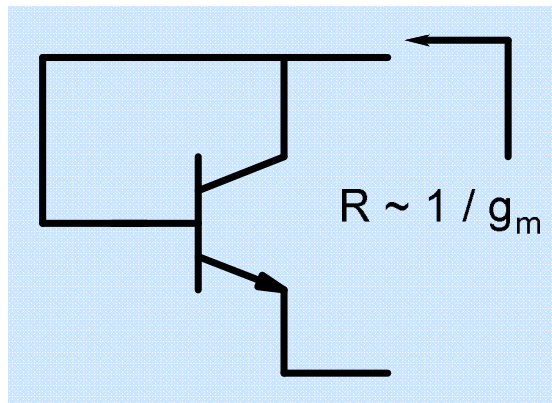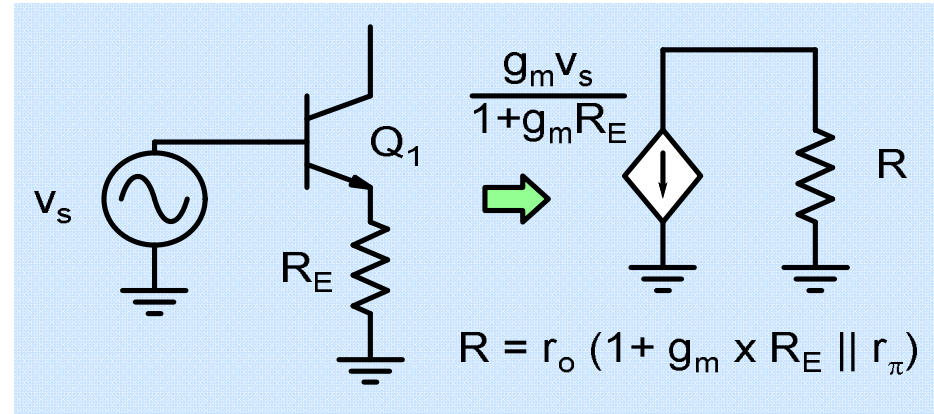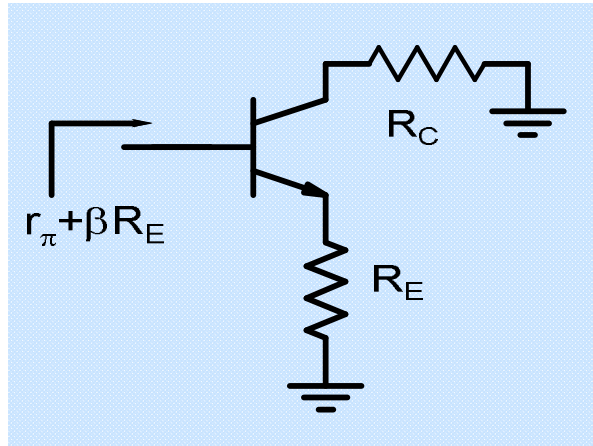Analysis Using “Divide & Reuse” Methodology-1



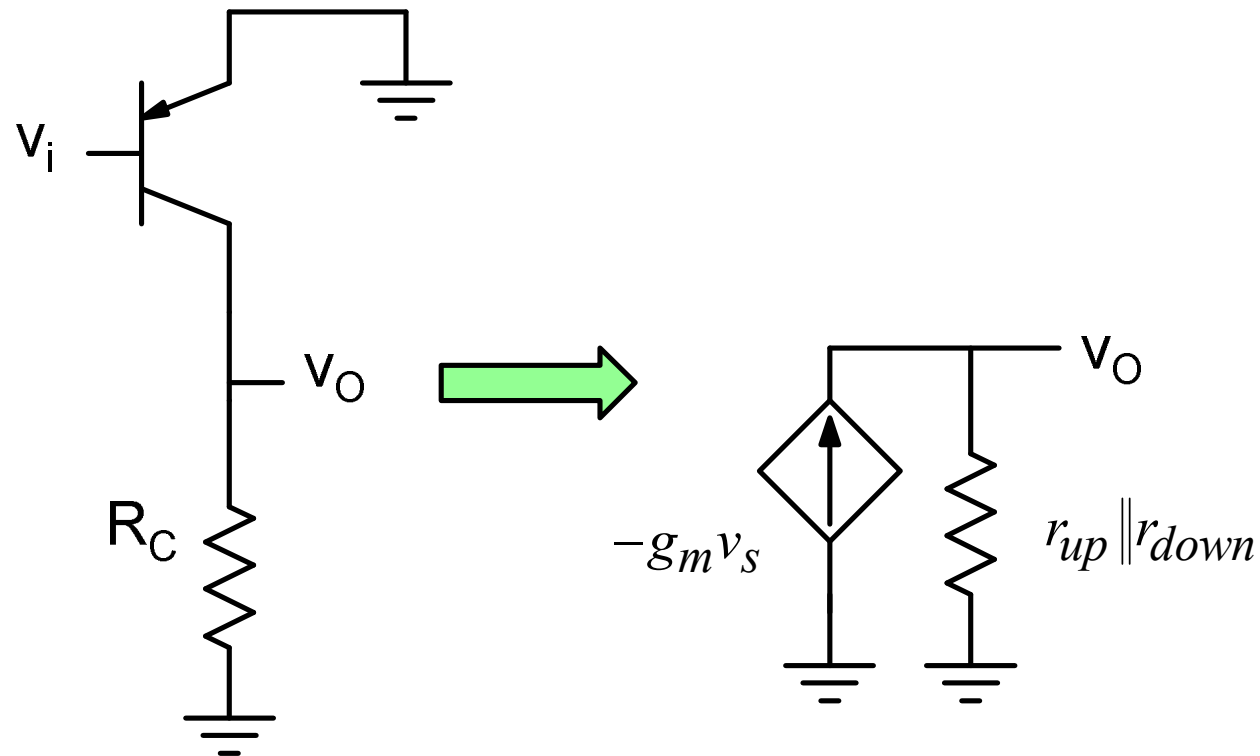Analysis Using “Divide & Reuse” Methodology-2



Build Norton's equivalent at the node of interest by using pre-derived and pre-verified results

MOS Amplifiers