



## EE210: HW-5

Date: 05.02.2019

Unless stated otherwise, the BJT in the problems given below has the following characteristics



$$I_S = 2.03 \times 10^{-15} \text{ A}; \beta_F = 100; \beta_R = 1; V_A = 100; r_{bb} = 200\Omega; V_T = 26 \text{ mV}; C_{je0} = 1 \text{ pF}; \\ C_{jc0} = 0.5 \text{ pF}; C_{js0} = 3 \text{ pF}; m = 0.5; V_{bi} = 0.85; \tau_F = 1 \text{ ns}$$

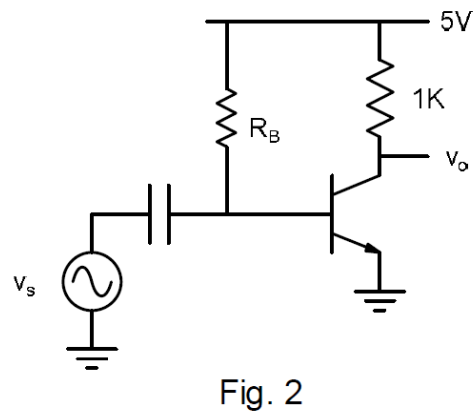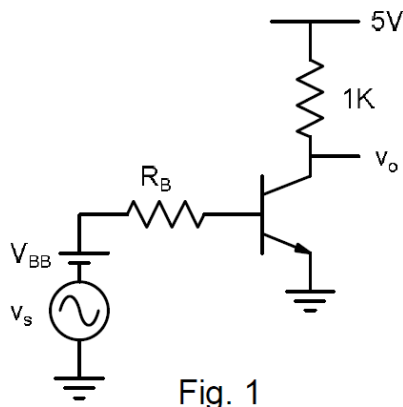**Q.1** Design the amplifier shown in Fig.1 such that open circuit voltage gain is 100. What happens to the bias point if  $V_{BB}$  increases by 10%?



**Q.2** Design the amplifier shown in Fig. 2 such that open circuit voltage gain is also 100. What happens to the bias point if  $V_{CC}$  increases by 10%? What would be the impact on the amplifier's characteristics if  $\beta$  were to become 200?

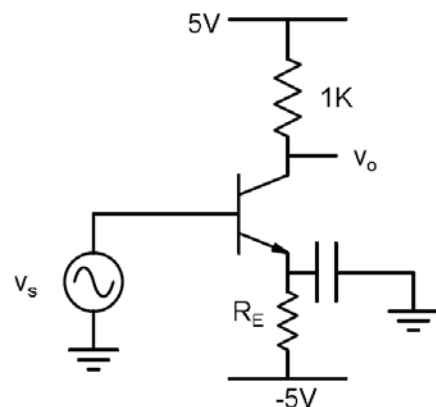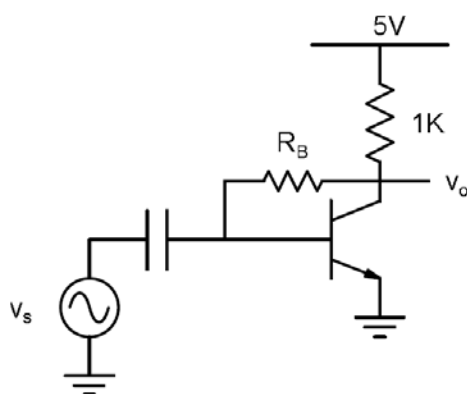**Q.3** Two alternative bias schemes are shown below. Design these amplifiers also for an open circuit voltage gain of 100 and check their sensitivity to  $\beta$ . Also try to evaluate your design using circuit simulation.



**Q.4 (a)** Design the amplifier shown below in Fig. 5 such that:  $A_{v0} = -100$ ;  $R_{in} = 1k\Omega$ .

**(b)** Determine the voltage gain and maximum voltage swing with 10%  $HD_2$  distortion for  $R_L = 2k\Omega$ . Assume a saturation voltage of  $\sim 0.2V$ .

**(c)** Determine the value of an extra un-bypassed emitter resistance that may be required to reduce open circuit voltage gain by half. Determine the new value of  $R_{in}$ . Simulate the circuit to determine the swing for harmonic distortion of 10%.

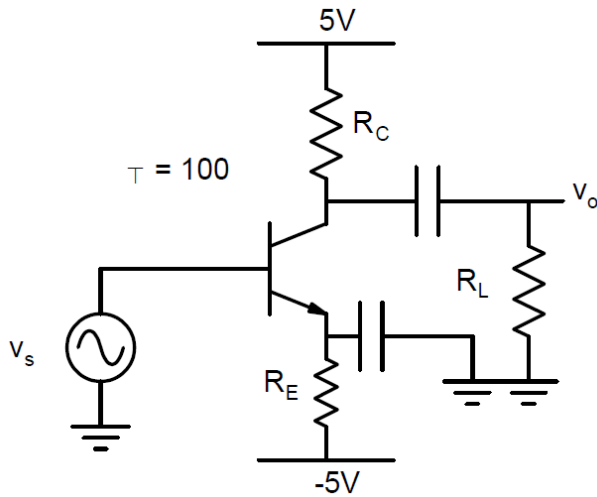


Fig. 5

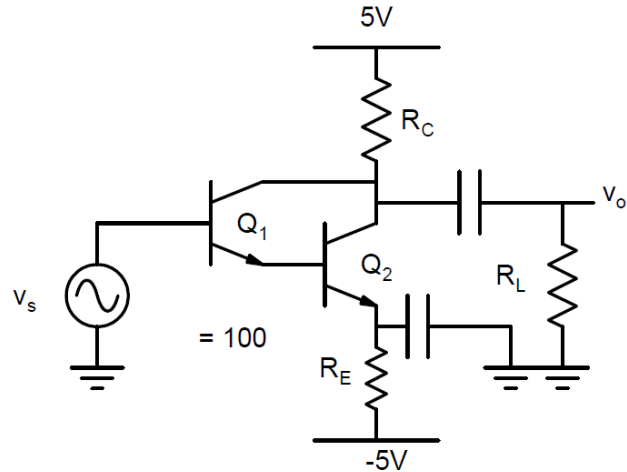


Fig.6

**Q.5** Suppose the amplifier shown in Fig. 6 is designed with same bias point ( $I_{CQ}$  and  $V_{CEQ}$ ) calculated earlier in Q.4. What would be the open circuit voltage gain and input resistance for this amplifier? Will the output swing be similar?