




# EE210: Microelectronics-I

## Lecture-18 : BJT Amplifier-part-7 Frequency Response

Instructor - Y. S. Chauhan


Slides from: B. Mazhari  
Dept. of EE, IIT Kanpur
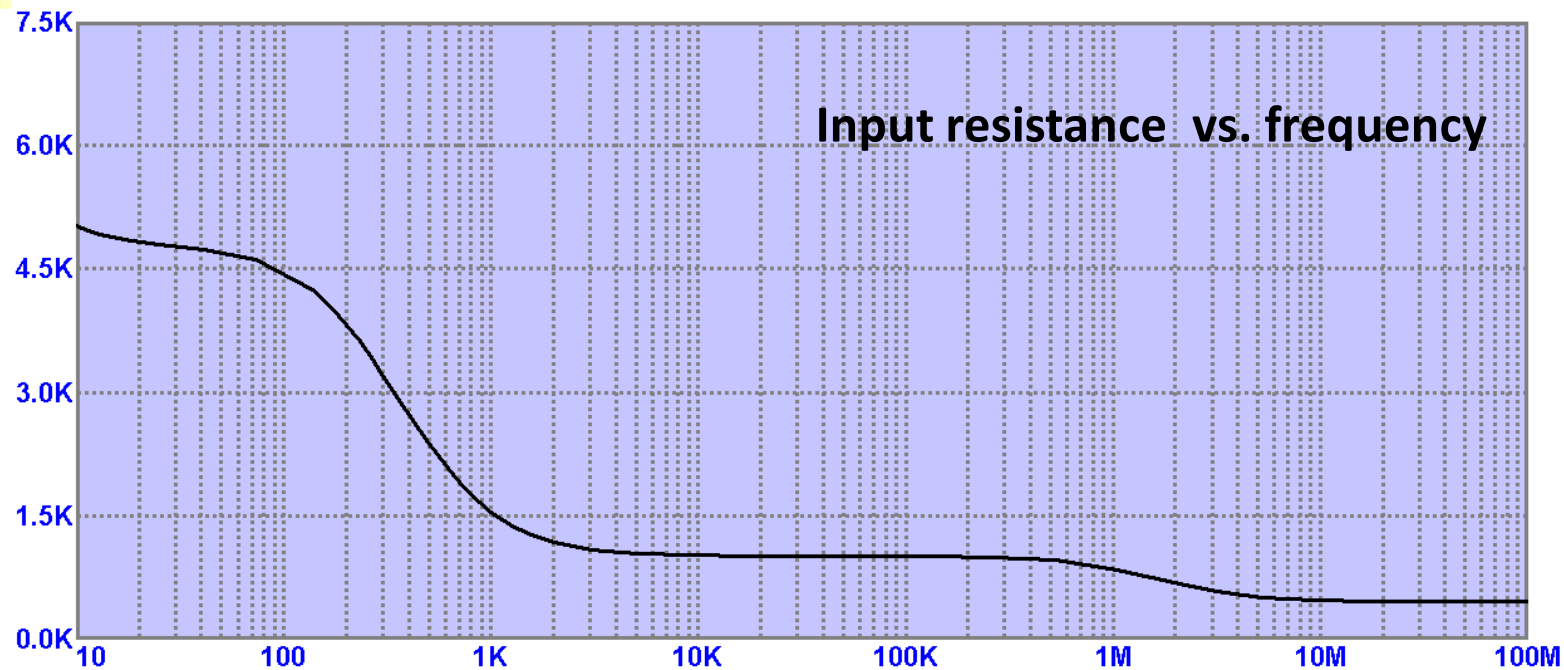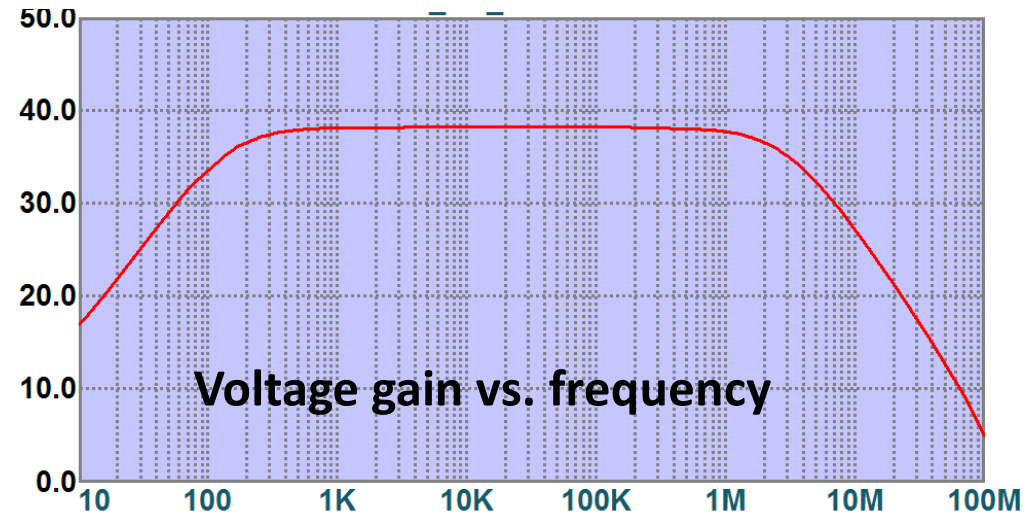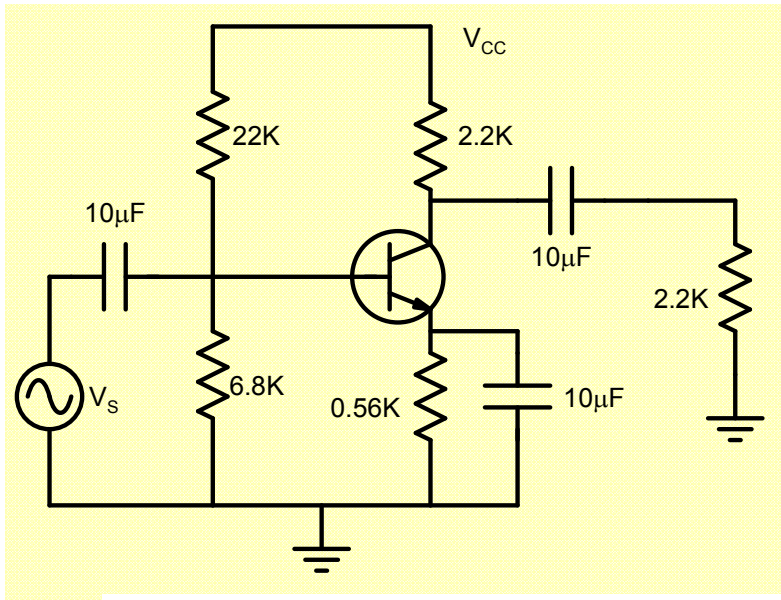
# Characteristics of Amplifiers are frequency dependent




Frequency dependent behavior occurs because of resistances and capacitances

Internal transistor capacitances

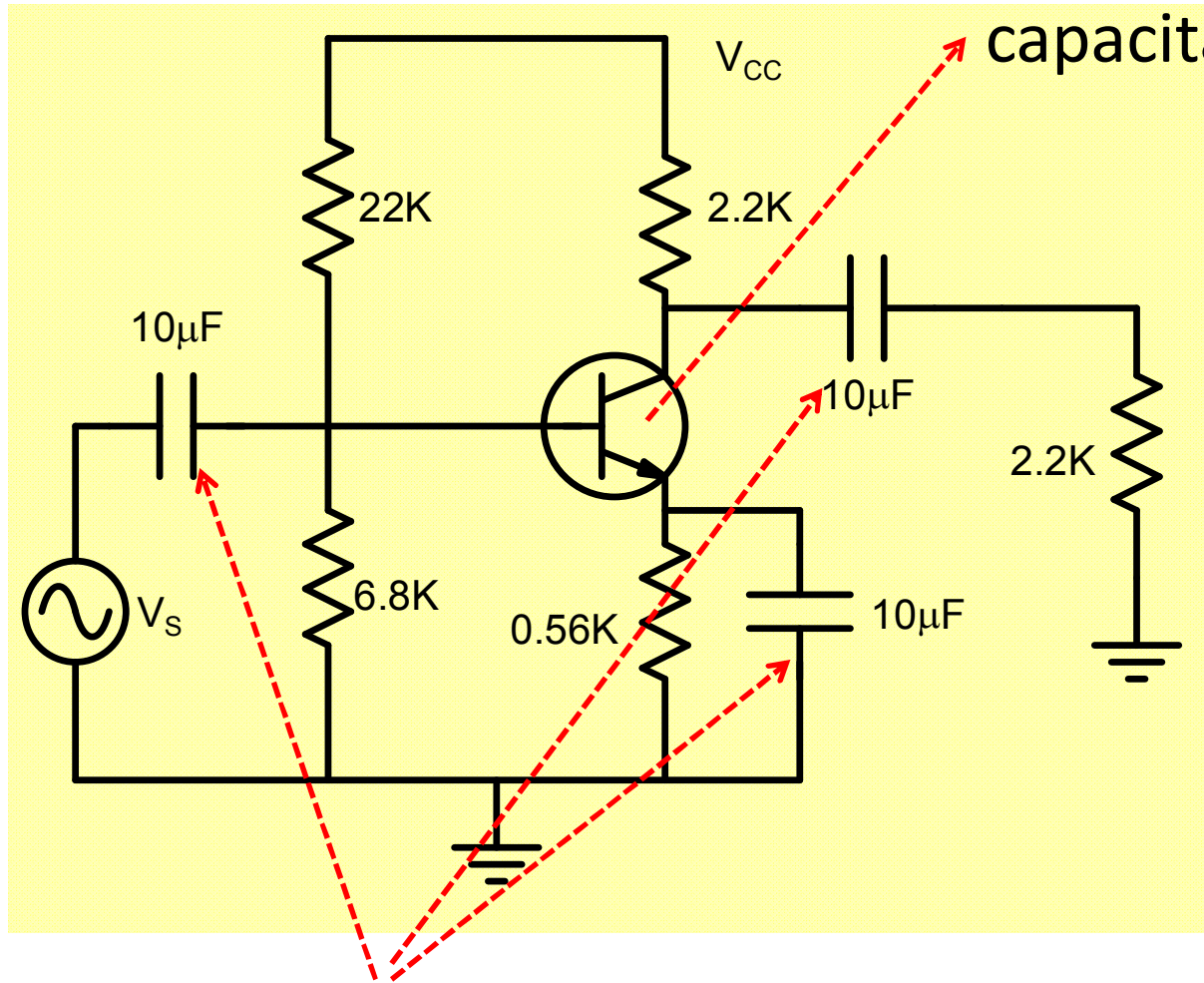

External coupling and bypass capacitors

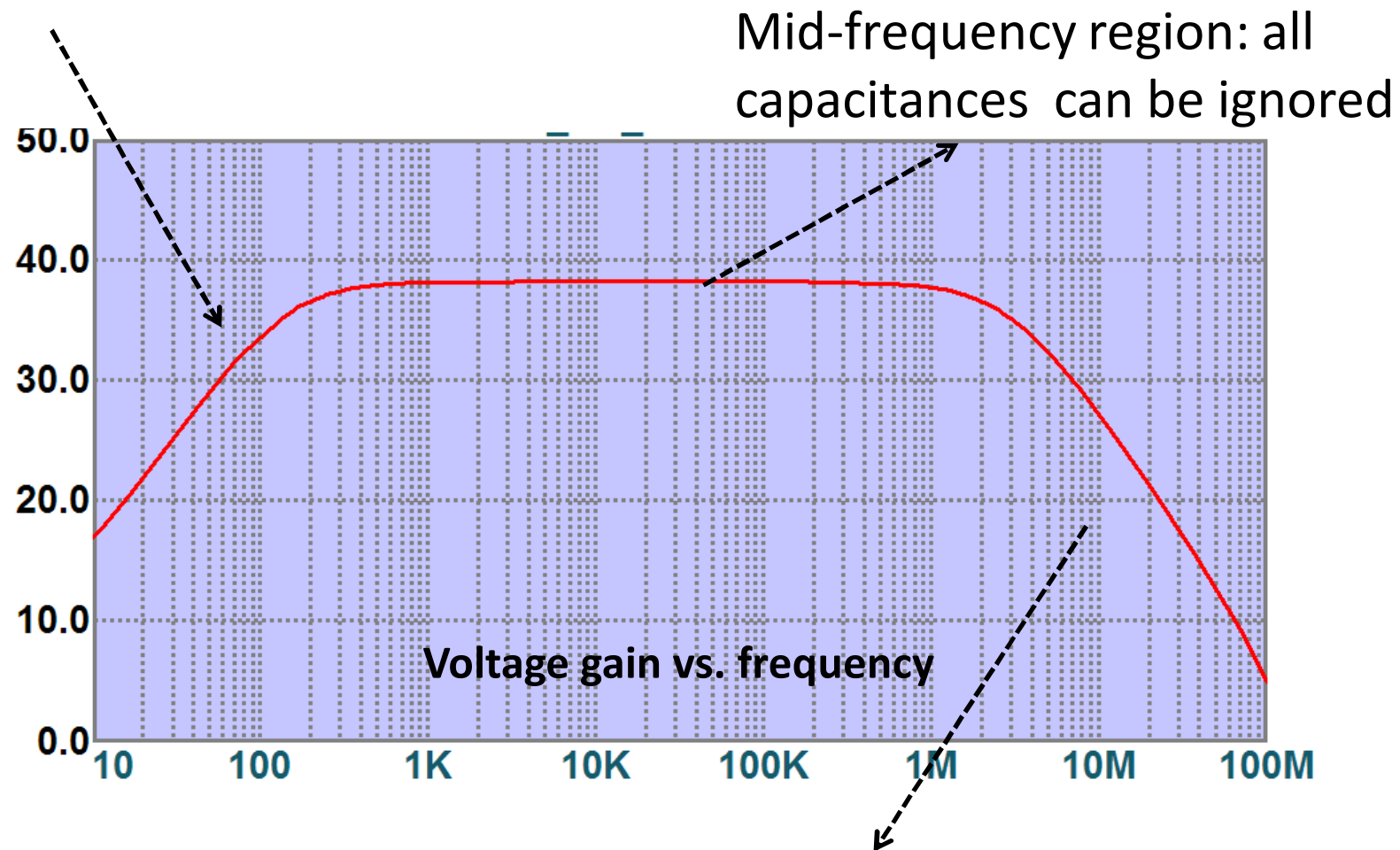
Low frequency behavior is caused by external capacitances



High frequency behavior is caused by internal transistor capacitances

## Background : Analysis of RC Circuits

Simple Low pass RC filter circuit

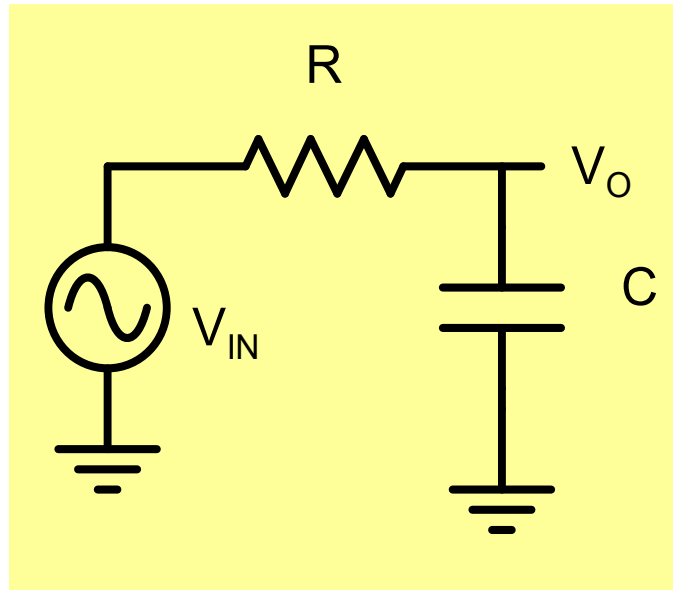

Time domain

Frequency domain

Frequency domain:

$$H(s) = \frac{v_o(s)}{v_{in}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{sCR + 1}$$


Substitute  $s = j\omega$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$


$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$
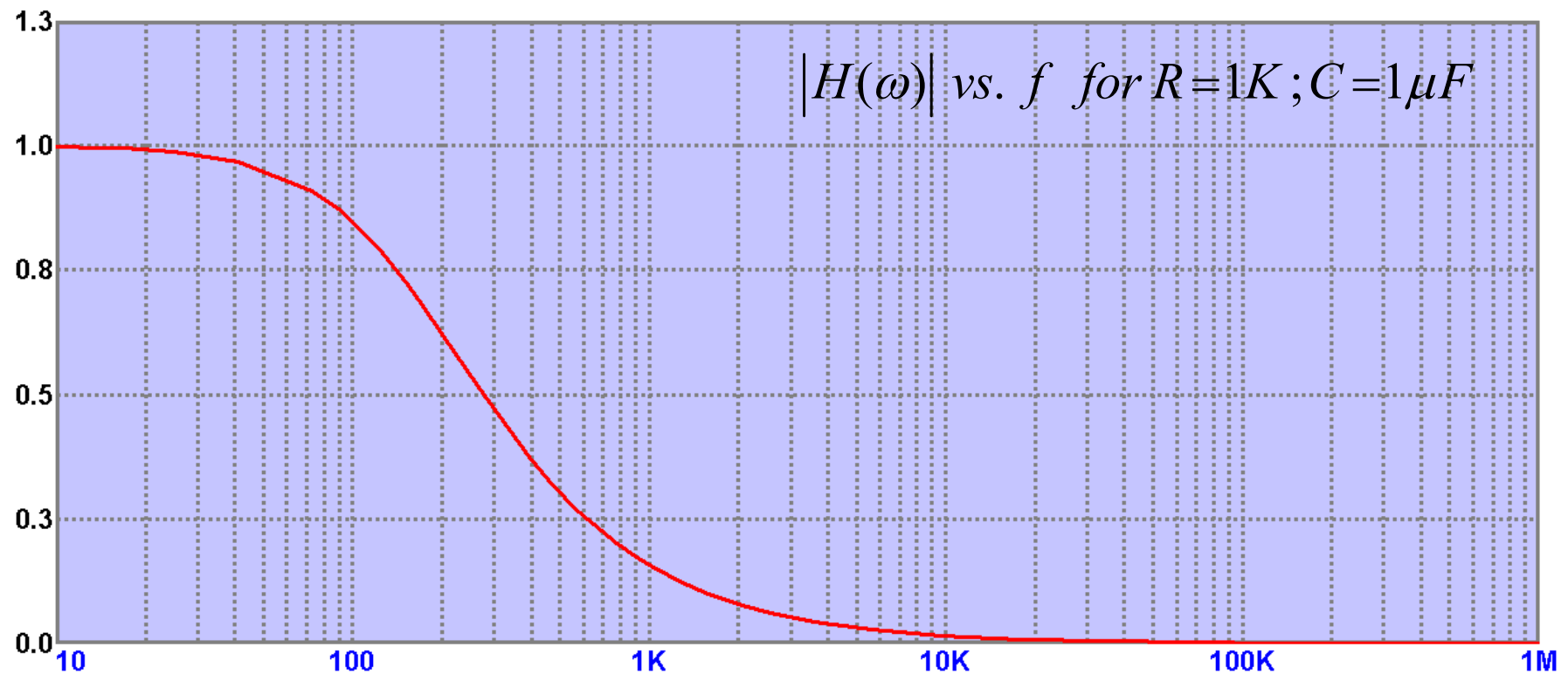
$$\text{Phase}(H) = -\tan^{-1}(\omega RC)$$



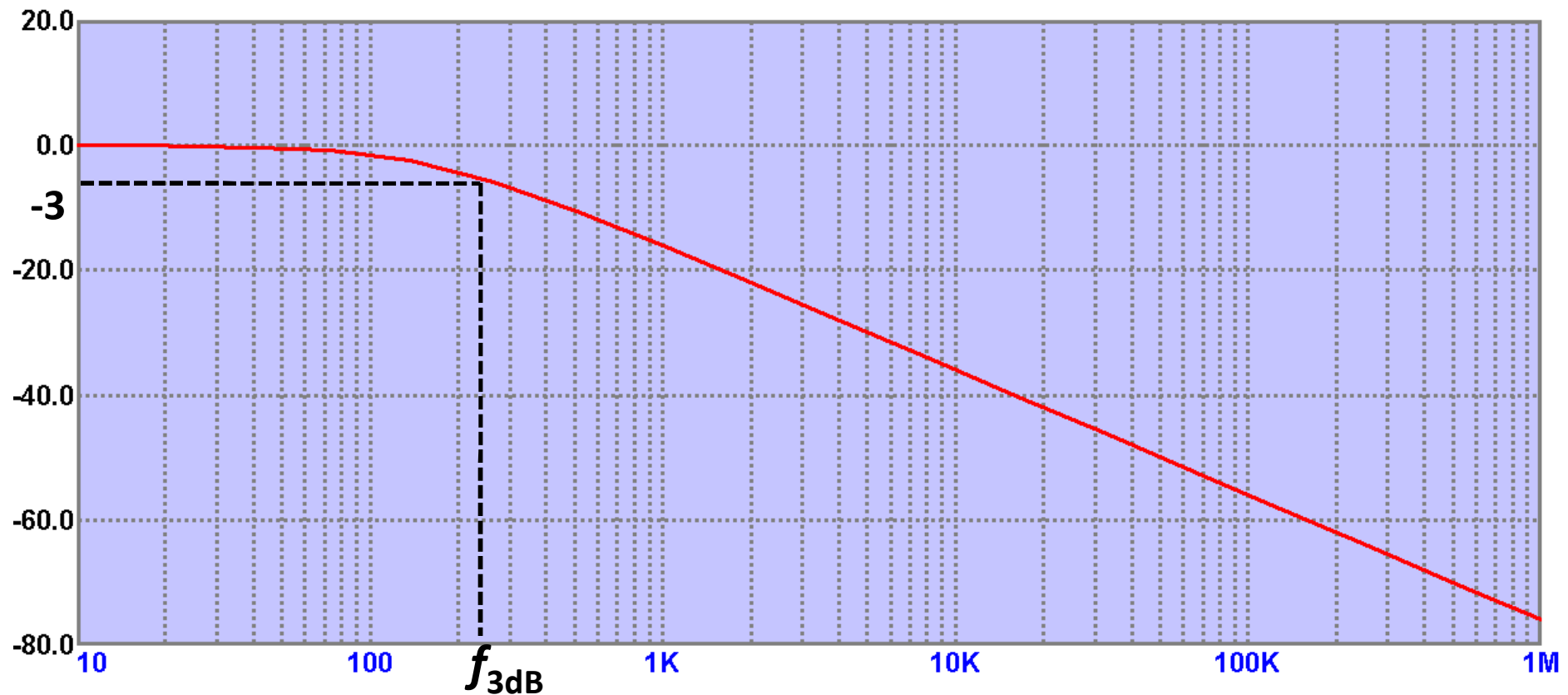Magnitude plot is often plotted in dB vs. frequency



$$20\text{Log}_{10}(|H(\omega)|) = -10\text{Log}_{10}(1 + \omega^2 R^2 C^2)$$

3dB frequency:

$$\omega_{3dB} RC = 1 \Rightarrow |H| = -3\text{dB}$$

$$f_{3dB} = \frac{1}{2\pi RC}$$

3dB frequency gives complete information about the behavior of RC circuit

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$H(\omega) = \frac{1}{1 + j\left(\frac{f}{f_{3dB}}\right)}$$


$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}}$$

$$\text{Phase}(H) = -\tan^{-1}\left(\frac{f}{f_{3dB}}\right)$$




# Time Domain (or Transient) Analysis


## Step Response

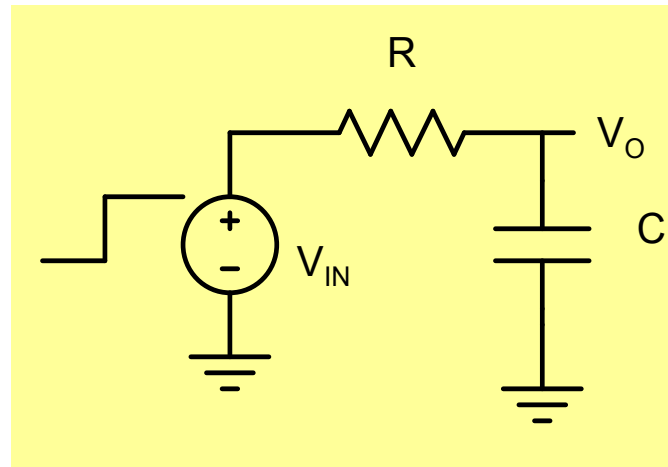
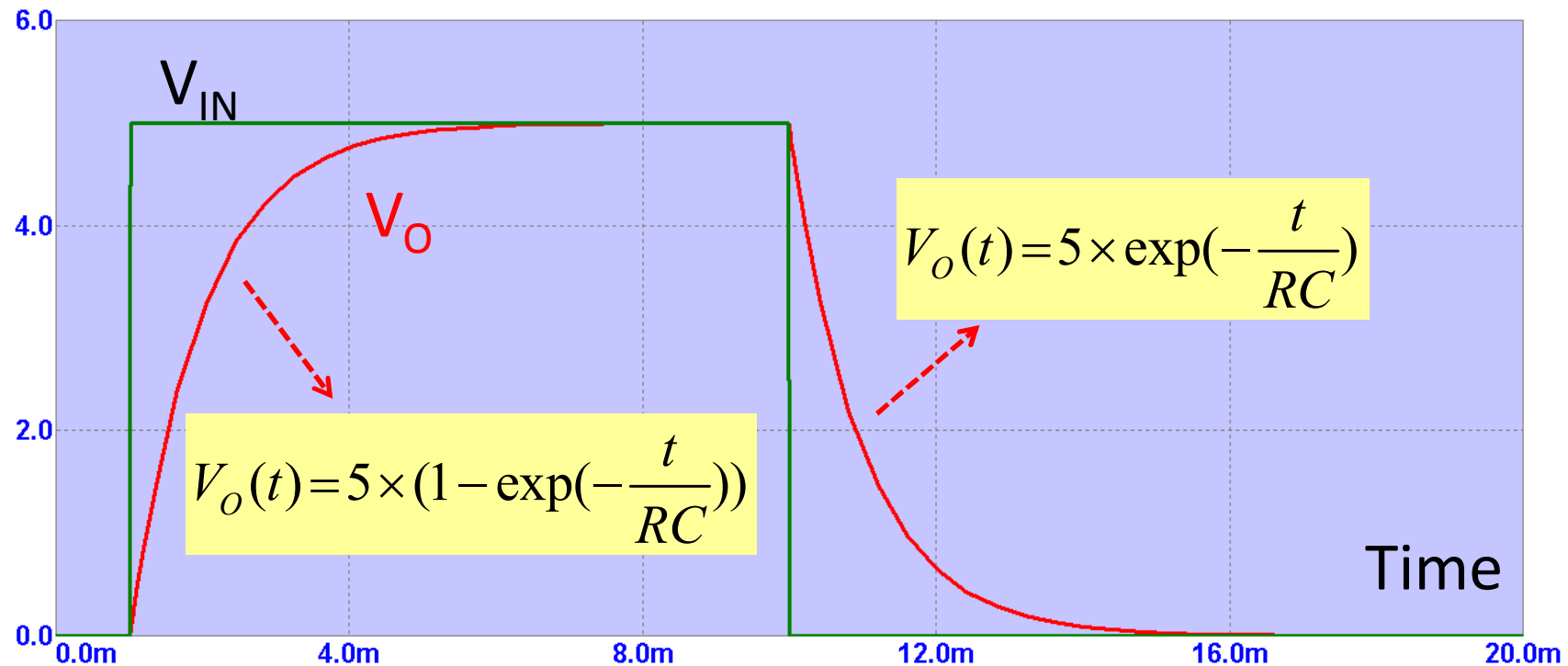
$$\tau_R = \tau_F = 2.2RC = \frac{0.35}{f_{3dB}}$$




# Simple High pass RC filter circuit

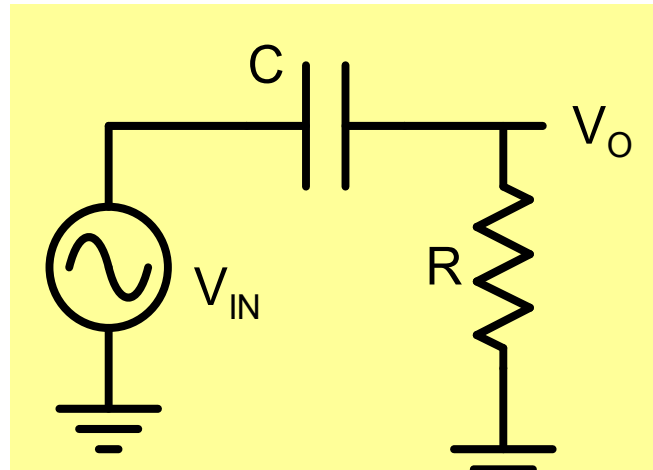

$$H(s) = \frac{v_o(s)}{v_{in}(s)} = \frac{R}{R + 1/sC} = \frac{sCR}{sCR + 1}$$


$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

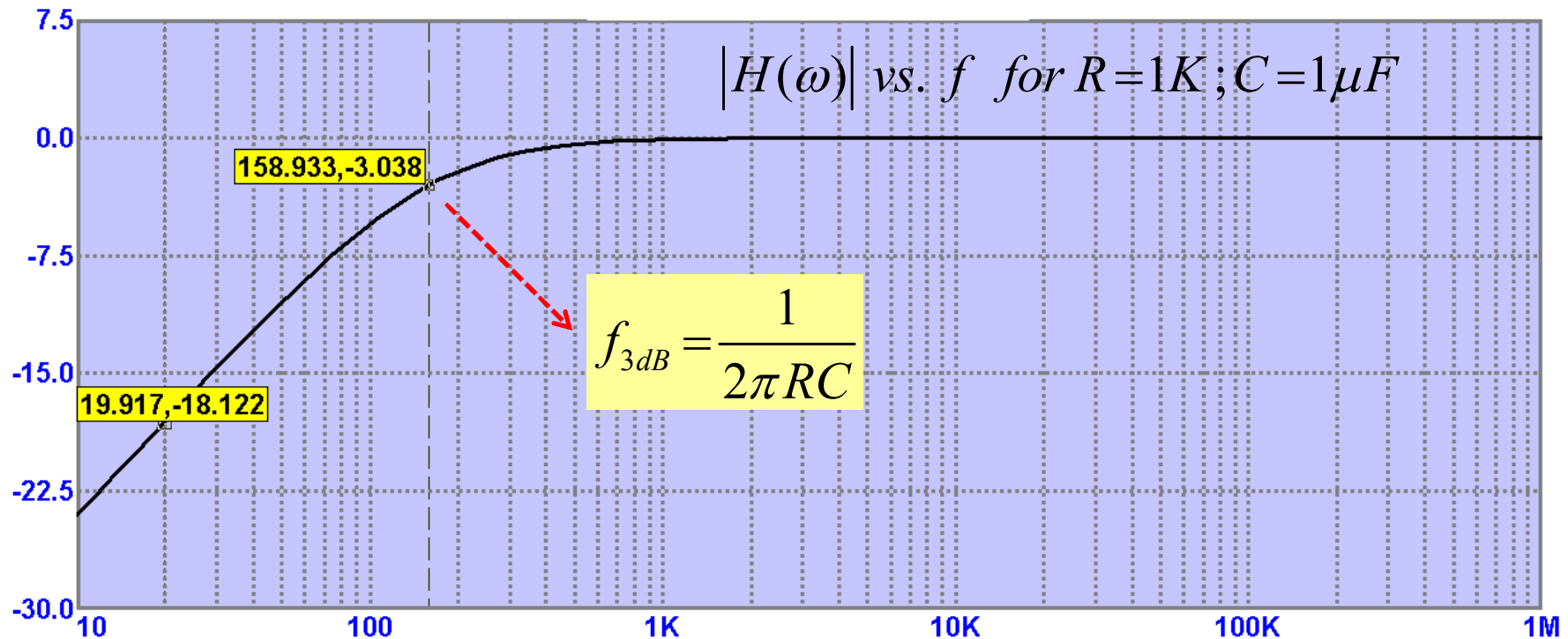


# Simple High pass RC filter circuit: Transient Response


## Step Response

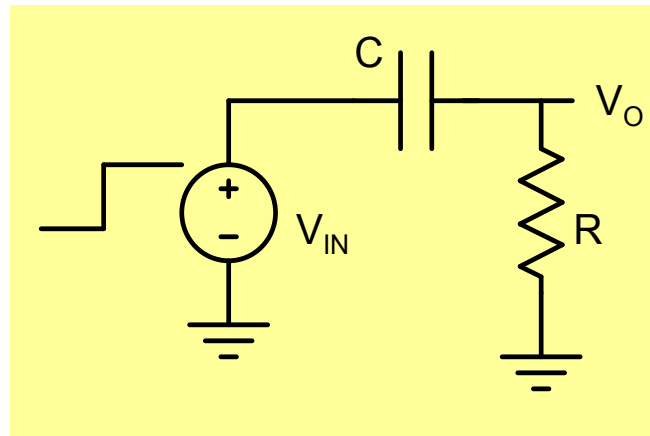
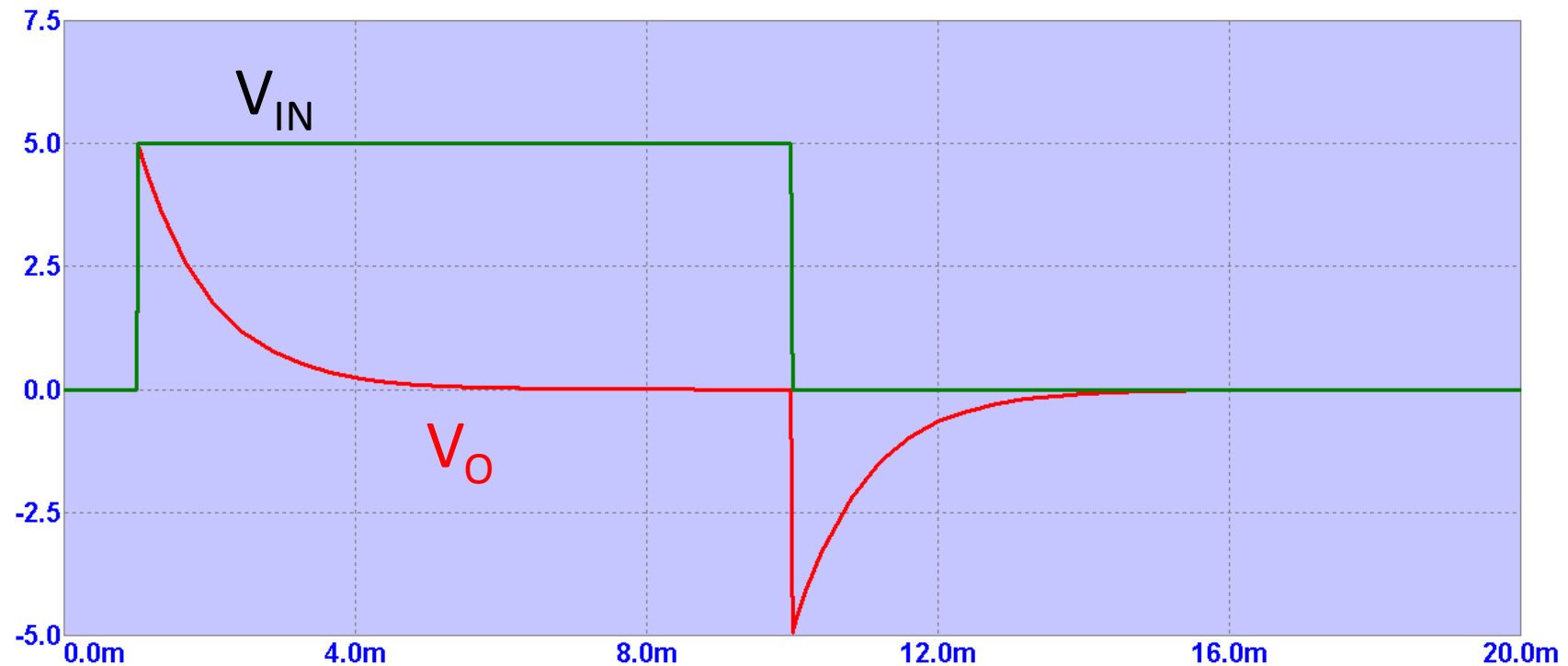
$$\tau_R = \tau_F = 2.2RC = \frac{0.35}{f_{3dB}}$$



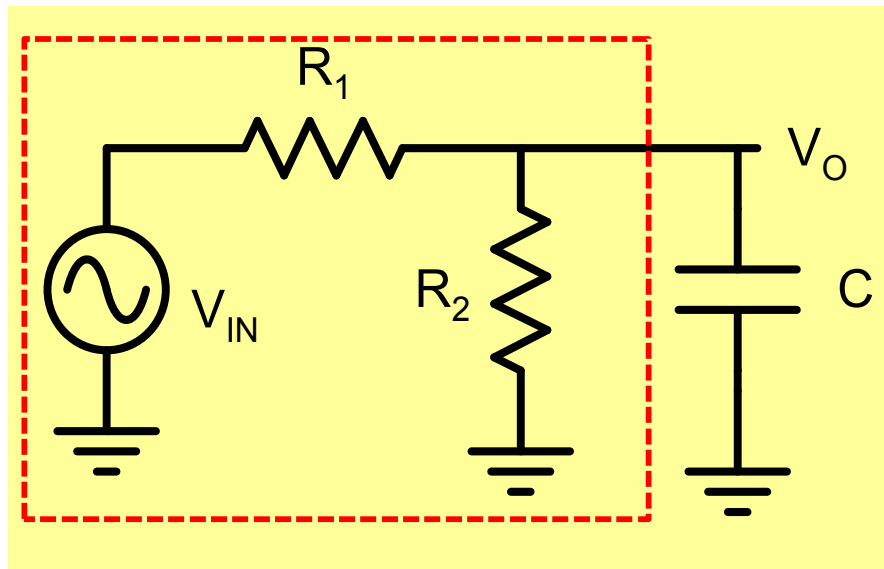
## Circuits with one capacitor but many Resistors




$$f_{3dB} = ?$$

Apply Thevenin's theorem:

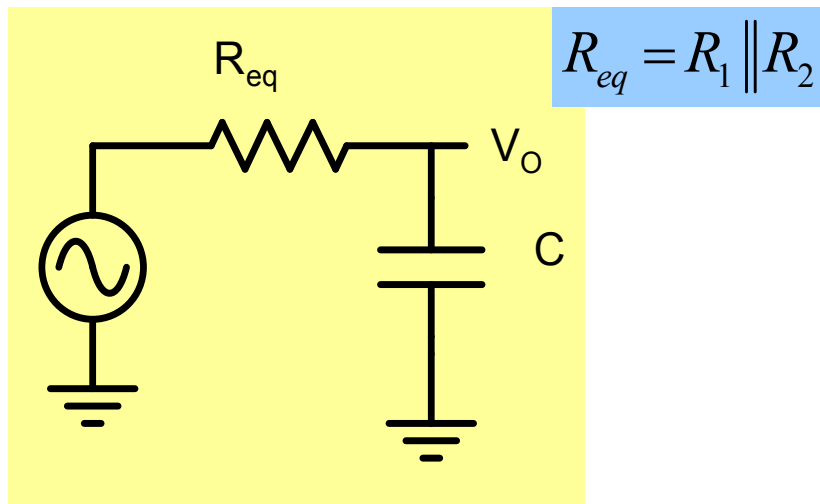

$$f_{3dB} = \frac{1}{2\pi R_{eq} C}$$


# Generalization

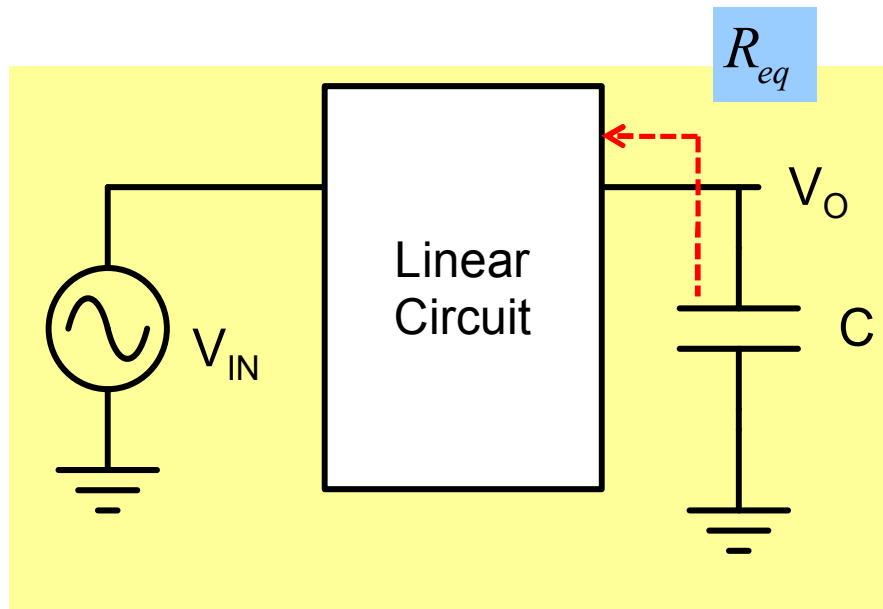

$$f_{3dB} = \frac{1}{2\pi R_{eq} C}$$

How do we know if the capacitor causes high or low pass behavior?

# Lower Cutoff Frequency

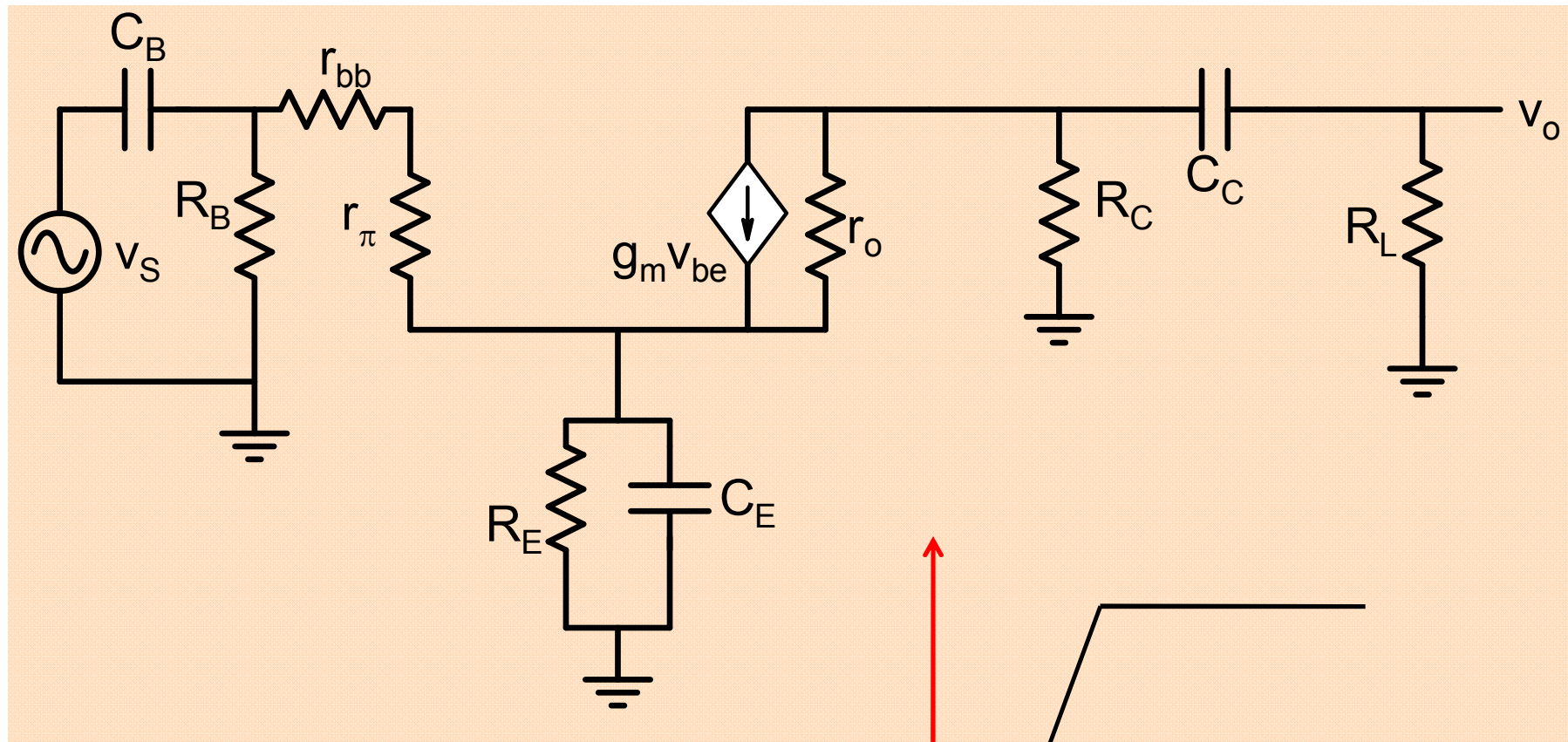

$$H(j\omega) = \frac{v_o}{v_s}$$

# Transfer Function

$(-Hgm\_q1 \ Cc \ CB \ RB \ RC \ RL) \ s^2$

$(-Hgm\_q1 \ Cc \ CE \ CB \ RB \ RC \ RE \ RL) \ s^3$

---

$(+ \ Gbe\_q1 \ RE + Gbe\_q1 \ RB + Hgm\_q1 \ RE + 1)$

$(+ \ Gbe\_q1 \ CB \ RE \ RS + Gbe\_q1 \ CB \ RB \ RS + Gbe\_q1 \ CB \ RB \ RE +$   
 $Hgm\_q1 \ CB \ RE \ RS + Hgm\_q1 \ CB \ RB \ RE + CB \ RS + CB \ RB + Gbe\_q1 \ CE \ RB \ RE +$   
 $CE \ RE + Gbe\_q1 \ Cc \ RE \ RL + Gbe\_q1 \ Cc \ RC \ RE + Gbe\_q1 \ Cc \ RB \ RL +$   
 $Gbe\_q1 \ Cc \ RB \ RC + Hgm\_q1 \ Cc \ RE \ RL + Hgm\_q1 \ Cc \ RC \ RE + Cc \ RL + Cc \ RC) \ s$

$(+ \ Gbe\_q1 \ CE \ CB \ RB \ RE \ RS + CE \ CB \ RE \ RS + CE \ CB \ RB \ RE +$   
 $Gbe\_q1 \ Cc \ CB \ RE \ RL \ RS + Gbe\_q1 \ Cc \ CB \ RC \ RE \ RS +$   
 $Gbe\_q1 \ Cc \ CB \ RB \ RL \ RS + Gbe\_q1 \ Cc \ CB \ RB \ RE \ RL +$   
 $Gbe\_q1 \ Cc \ CB \ RB \ RC \ RS + Gbe\_q1 \ Cc \ CB \ RB \ RC \ RE +$   
 $Hgm\_q1 \ Cc \ CB \ RE \ RL \ RS + Hgm\_q1 \ Cc \ CB \ RC \ RE \ RS +$   
 $Hgm\_q1 \ Cc \ CB \ RB \ RE \ RL + Hgm\_q1 \ Cc \ CB \ RB \ RC \ RE +$   
 $Cc \ CB \ RL \ RS + Cc \ CB \ RC \ RS + Cc \ CB \ RB \ RL + Cc \ CB \ RB \ RC +$   
 $Gbe\_q1 \ Cc \ CE \ RB \ RE \ RL + Gbe\_q1 \ Cc \ CE \ RB \ RC \ RE + Cc \ CE \ RE \ RL + Cc \ CE \ RC \ RE) \ s^2$

$(+ \ Gbe\_q1 \ Cc \ CE \ CB \ RB \ RE \ RL \ RS + Gbe\_q1 \ Cc \ CE \ CB \ RB \ RC \ RE \ RS +$   
 $Cc \ CE \ CB \ RE \ RL \ RS + Cc \ CE \ CB \ RC \ RE \ RS + Cc \ CE \ CB \ RB \ RE \ RL + Cc \ CE \ CB \ RB \ RC \ RE) \ s^3$

# Simplified Transfer Function

$$\frac{(-H_{gm\_q1} C_c C_B R_C R_L) s^2}{(-H_{gm\_q1} C_c C_E C_B R_C R_E R_L) s^3}$$


---


$$(+G_{be\_q1})$$

$$(+G_{be\_q1} C_B R_E + H_{gm\_q1} C_B R_E + C_B + G_{be\_q1} C_E R_E + G_{be\_q1} C_c R_L + G_{be\_q1} C_c R_C) s$$

$$(+C_E C_B R_E + G_{be\_q1} C_c C_B R_E R_L + G_{be\_q1} C_c C_B R_C R_E + H_{gm\_q1} C_c C_B R_E R_L + H_{gm\_q1} C_c C_B R_C R_E + C_c C_B R_L + C_c C_B R_C + G_{be\_q1} C_c C_E R_E R_L + G_{be\_q1} C_c C_E R_C R_E) s^2$$


$$(+C_c C_E C_B R_E R_L + C_c C_E C_B R_C R_E) s^3$$

$R_B, R_S$  neglected


Determine impact of each capacitor independently



# Lower Cutoff Frequency

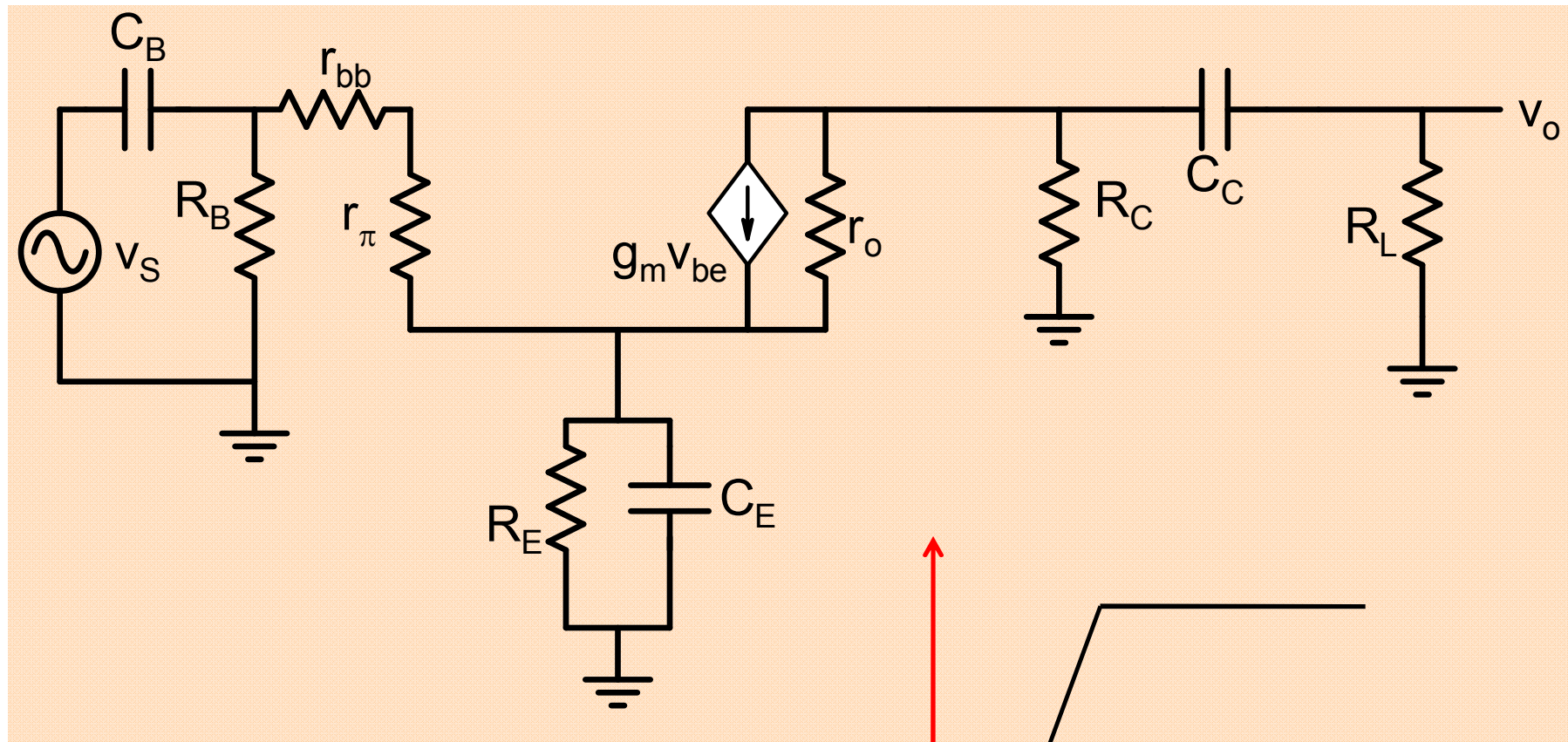

$$H(j\omega) = \frac{v_o}{v_s}$$

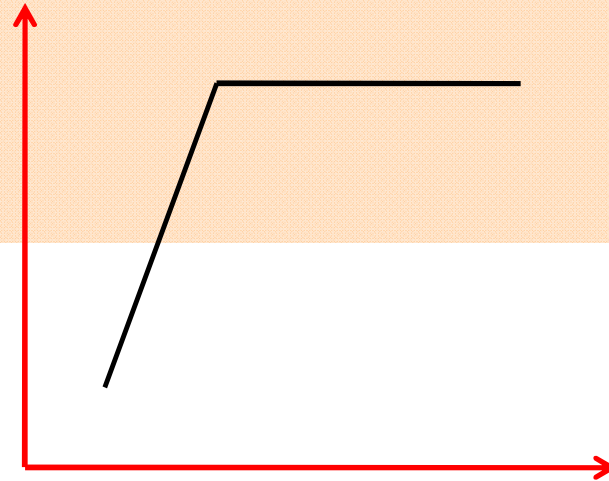

## Simplified Procedure

## Short-circuit time constant approach


- We consider one capacitor ( $C_j$ ) at a time assuming that it plays a dominant role and short-circuit the remaining.
- We then determine time constant  $R_{eqj}C_j$  and 3dB frequency  $f_j$  due to this capacitor.
- Like this we determine for each of the capacitors.
- If one of the 3dB frequencies is larger by a factor of 4 or so compared to others, we take this frequency as the 3dB frequency of the circuit
- otherwise

$$f_L \cong \frac{1}{2\pi} \sum \frac{1}{R_{eqj}C_j} = \sum f_j$$

$$f_L \leq \sqrt{\sum f_{pi}^2 - 2 \sum f_{zi}^2}$$
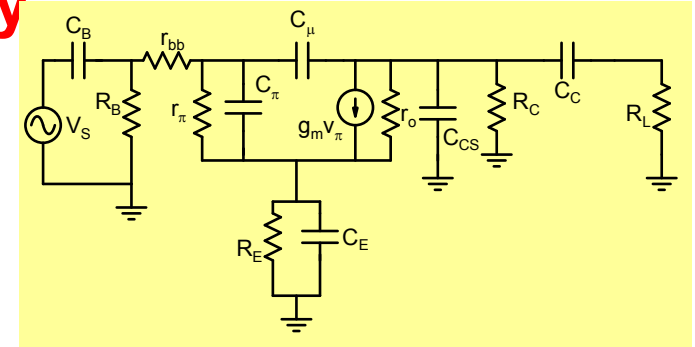
# Determination of upper cutoff frequency

First classify the capacitors into 2 classes



$(C_B, C_C, C_E, C_\pi, C_\mu, C_{CS})$


HP

LP

$(C_B, C_C, C_E)$

$(C_\pi, C_\mu, C_{CS})$

Short circuit these capacitors

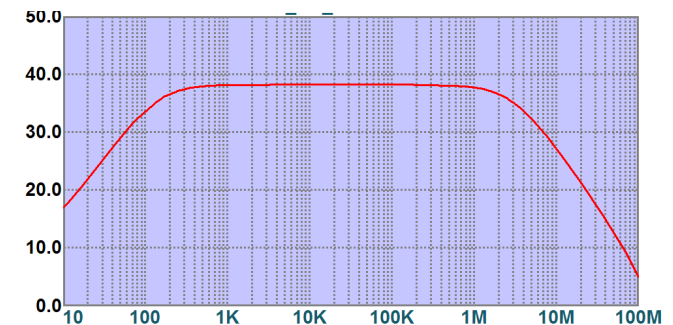

We still have three capacitors while we know only how to estimate 3 dB frequency when only one capacitor is present. So we use a simplified method to obtain an approximate value.



## Simplified Procedure

## Open-circuit time constant approach

- We consider one capacitor ( $C_j$ ) at a time assuming that it plays a dominant role and **open-circuit** the remaining.
- We then determine time constant  $R_{eqj}C_j$  and 3dB frequency  $f_j$  due to this capacitor.
- Like this we determine for each of the capacitors.
- If one of the 3dB frequencies is **smaller** by a factor of 4 or so compared to others, we take this frequency as the 3dB frequency of the circuit
- otherwise



$$f_H \cong \frac{1}{2\pi \sum R_{eqj} C_j}$$

## Example

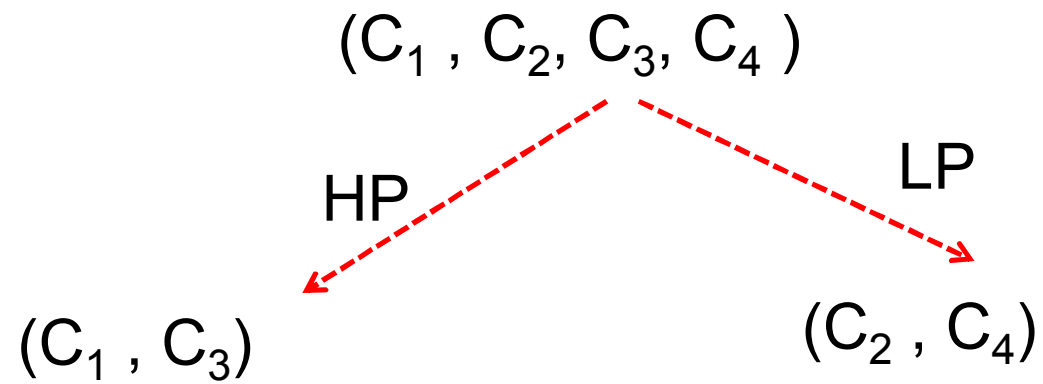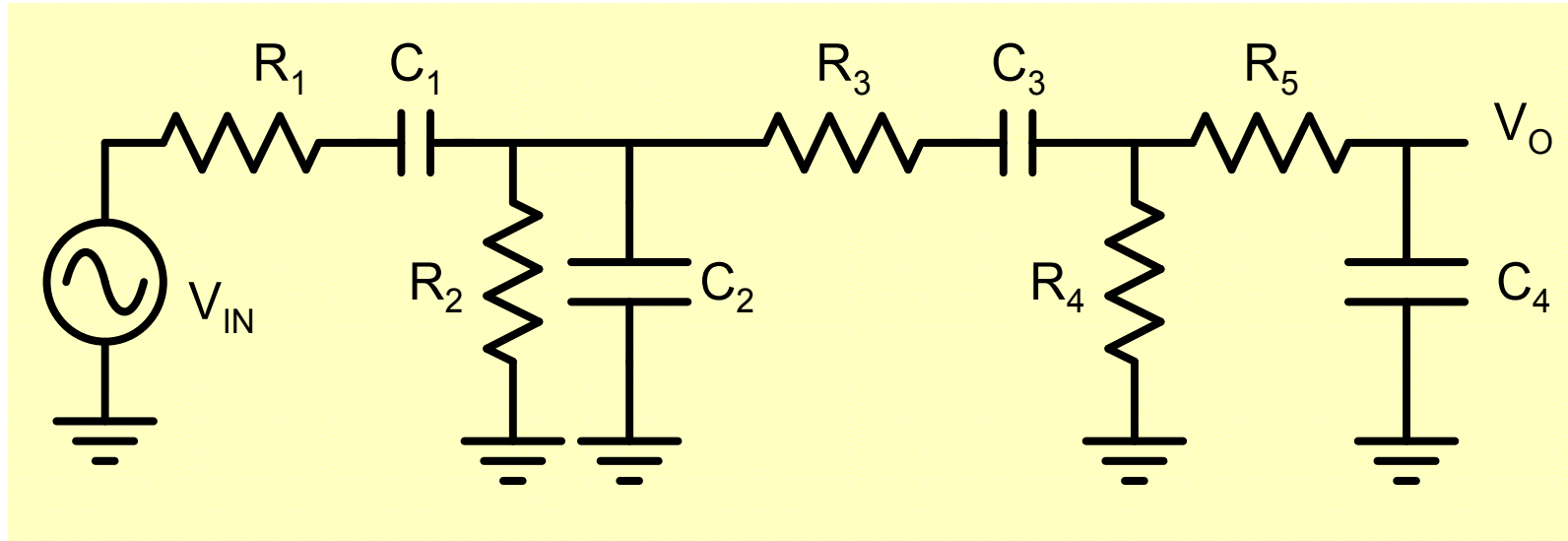

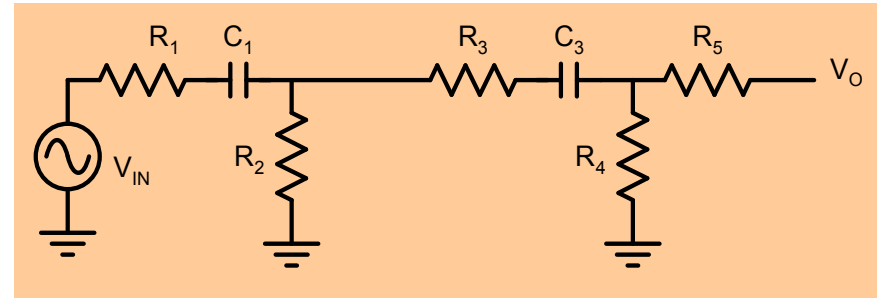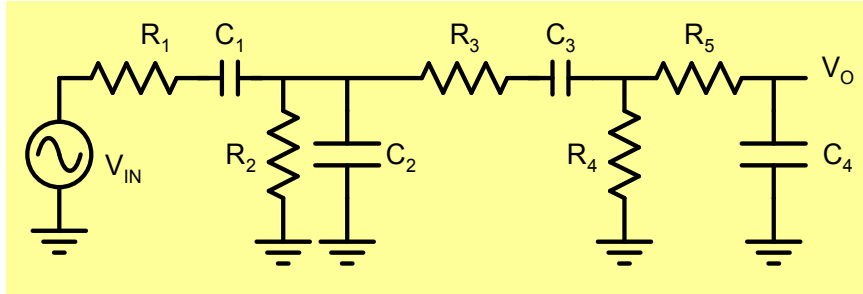
# Determination of lower cutoff frequency

Open circuit capacitors  $C_2$  and  $C_4$



Consider  $C_1$  first .

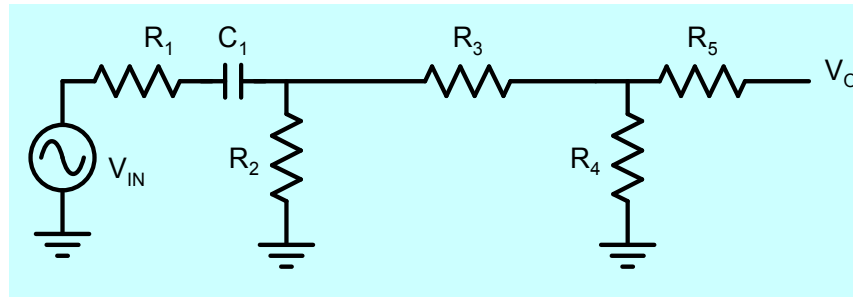


$$R_{eq1} = R_1 + R_2 \parallel (R_3 + R_4)$$

$$\tau_1 = C_1 R_{eq1}$$

$$f_1 = \frac{1}{2\pi C_1 R_{eq1}}$$

Consider  $C_3$  next.

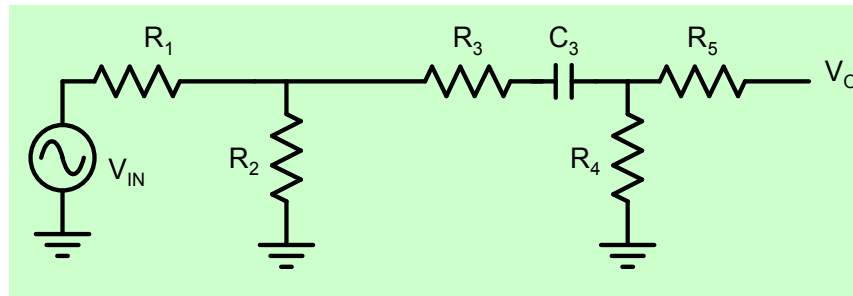

$$R_{eq3} = R_4 + (R_2 \parallel R_1) + R_3$$

$$\tau_3 = C_3 R_{eq3}$$

$$f_3 = \frac{1}{2\pi C_3 R_{eq3}}$$

Suppose all resistors are 1K and  $C_1 = 1\mu F$  ,  $C_3 = 10\mu F$   $C_2 = 1pF$  ,  $C_4 = 0.5pF$

$$R_{eq1} = R_1 + R_2 \parallel (R_3 + R_4) = 1.67K$$

$$\tau_1 = C_1 R_{eq1} = 1.67ms$$


$$f_1 = \frac{1}{2\pi C_1 R_{eq1}} = 95.3Hz$$

$$R_{eq3} = R_4 + (R_2 \parallel R_1) + R_3 = 2.5K$$

$$\tau_3 = C_3 R_{eq3} = 25ms$$



$$f_3 = \frac{1}{2\pi C_3 R_{eq3}} = 6.36Hz$$

$$f_L \cong f_1 = 95.3Hz$$

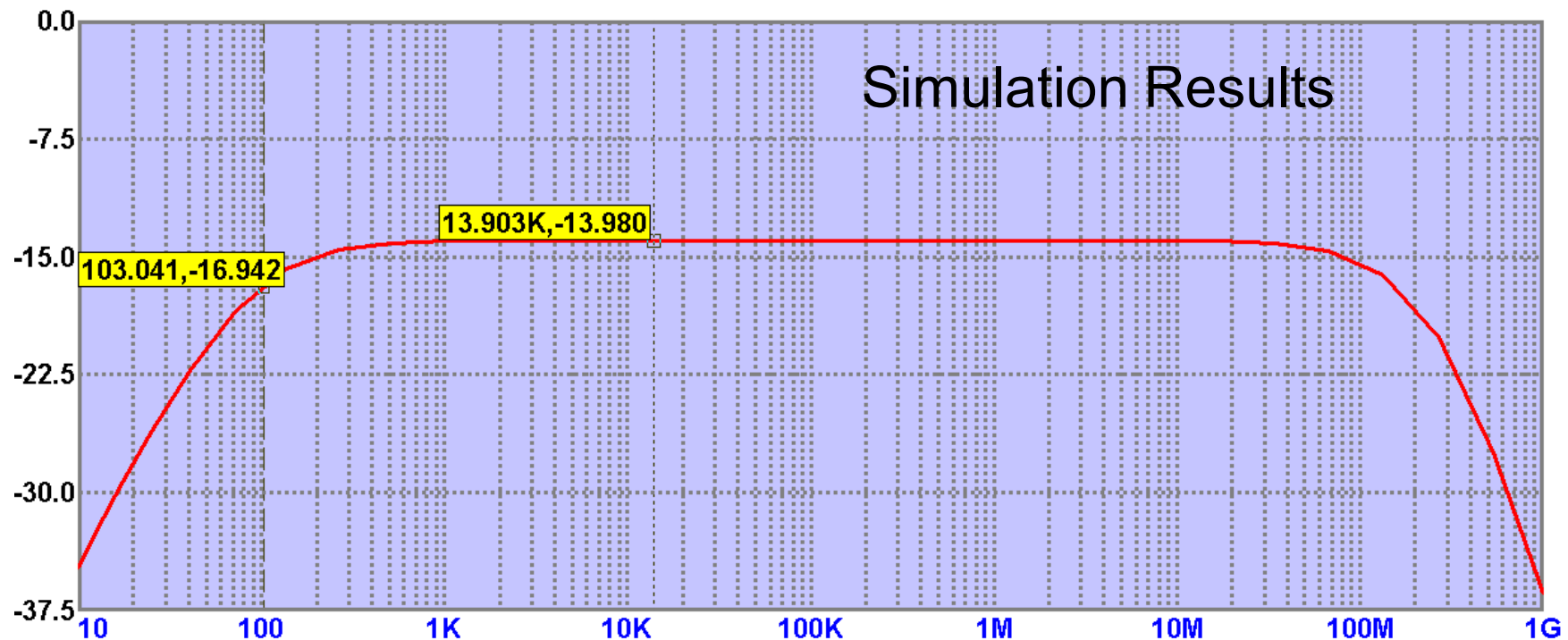

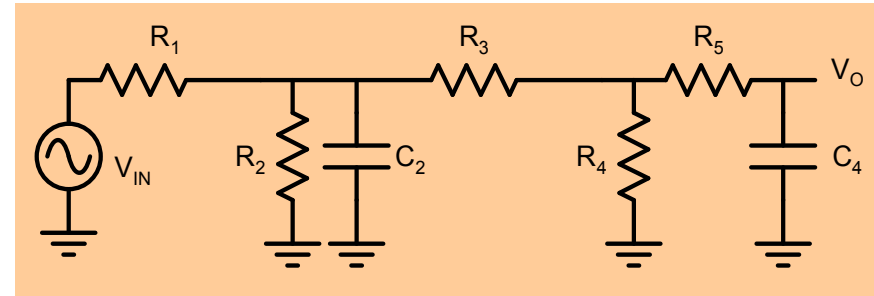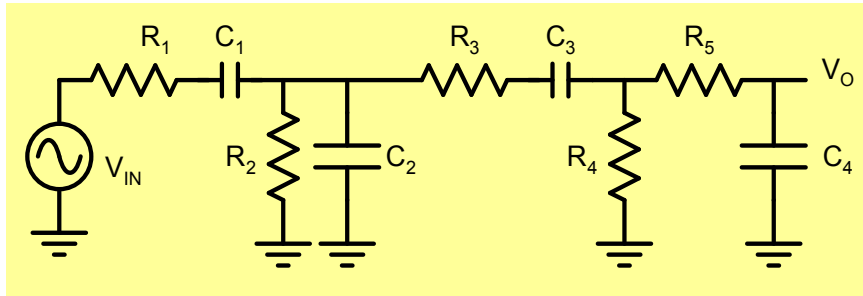
# Determination of upper cutoff frequency

Short circuit capacitors  $C_1$  and  $C_3$



Consider  $C_2$  first .

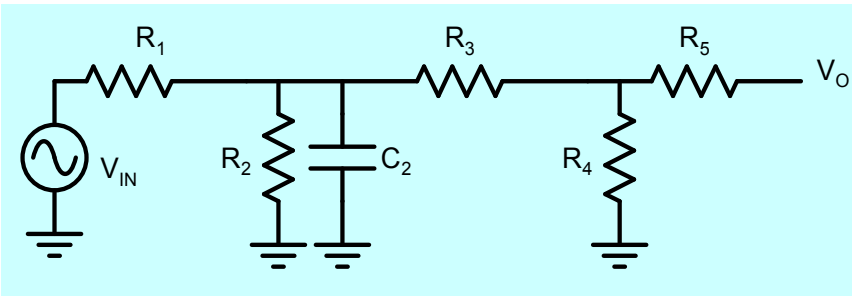


$$R_{eq2} = R_1 \parallel R_2 \parallel (R_3 + R_4)$$

$$\tau_2 = C_2 R_{eq2}$$

$$f_2 = \frac{1}{2\pi C_2 R_{eq2}}$$

Consider  $C_4$  next .

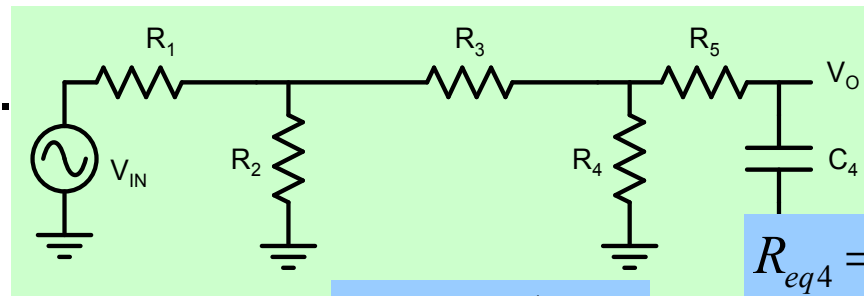

$$R_{eq4} = [\{(R_1 \parallel R_2) + R_3\} \parallel R_4] + R_5$$

$$f_4 = \frac{1}{2\pi C_4 R_{eq4}}$$

$$\tau_4 = C_4 R_{eq4}$$



$$R_{eq2} = R_1 \parallel R_2 \parallel (R_3 + R_4) = 0.4K$$

$$\tau_2 = C_2 R_{eq2} = 0.4ns$$

$$f_2 = \frac{1}{2\pi C_2 R_{eq2}} = 0.39GHz$$


$$R_{eq4} = [\{(R_1 \parallel R_2) + R_3\} \parallel R_4] + R_5 = 1.6K$$

$$\tau_4 = C_4 R_{eq4} = 0.8ns$$

$$f_4 = \frac{1}{2\pi C_4 R_{eq4}} = 0.2GHz$$

Since no frequency is dominant

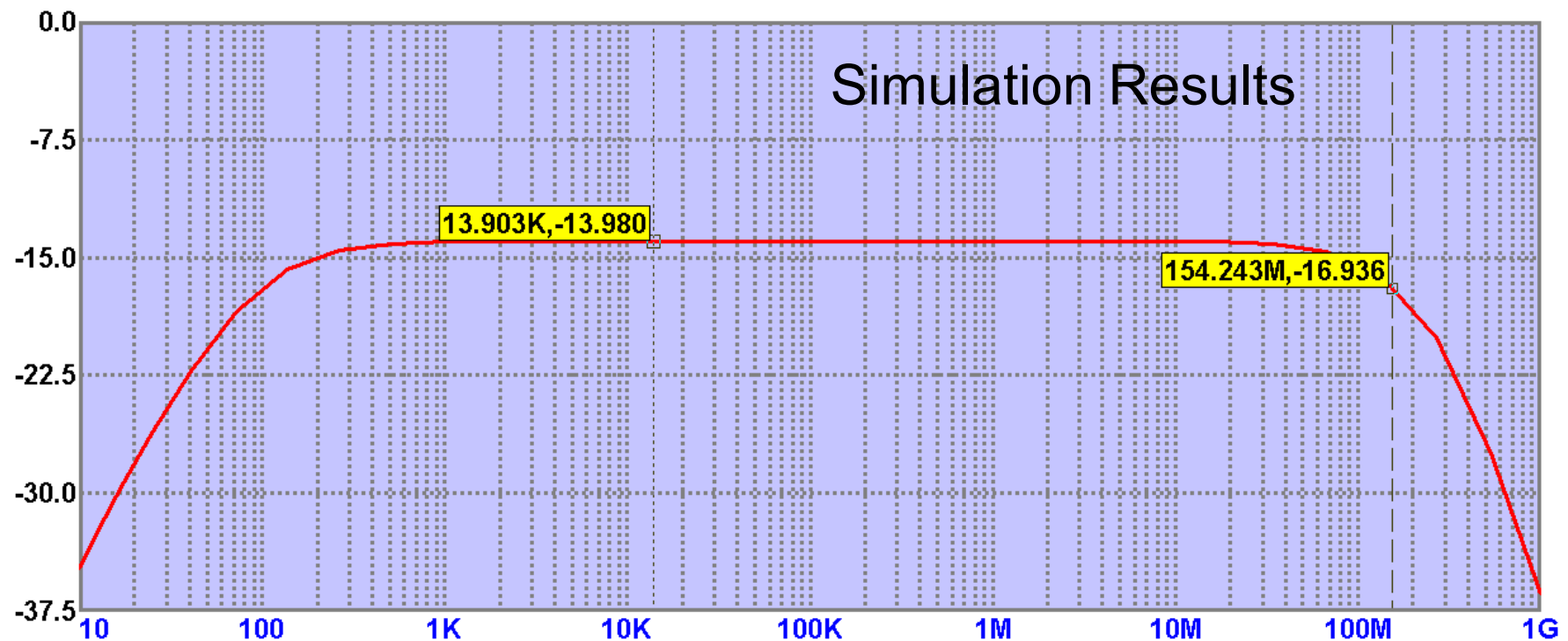
$$f_H \cong \frac{1}{2\pi \sum R_{eqj} C_j} = 0.13GHz$$




**Lower Cutoff Frequency**

In the estimation of 3dB frequency, we have to determine equivalent resistance seen by a capacitance. The results given below can be very useful for determination of these equivalent resistances


$$r_{\pi} + (1 + \beta)R_E$$

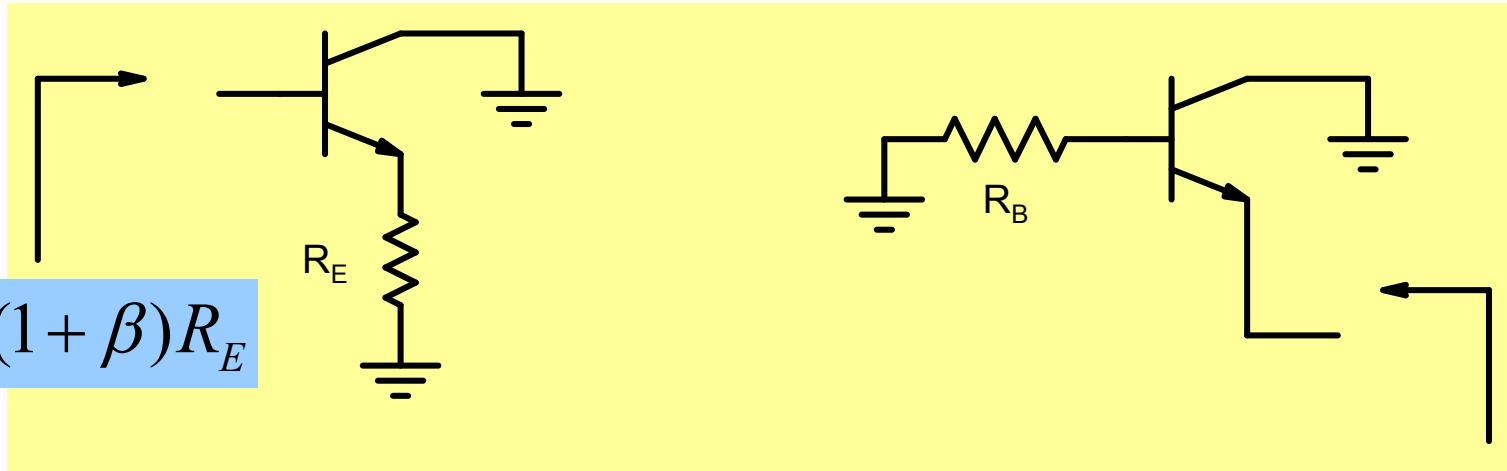



$$\frac{r_{\pi} + R_B}{1 + \beta}$$

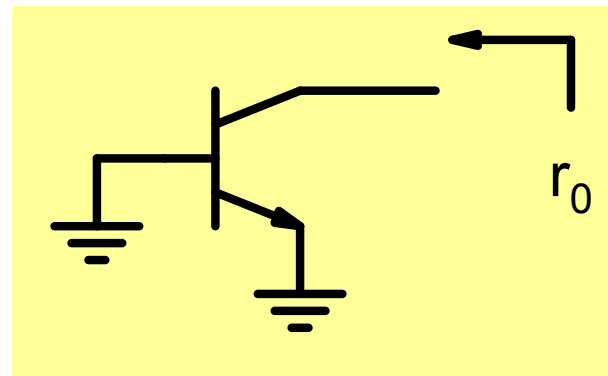


$$r_o$$

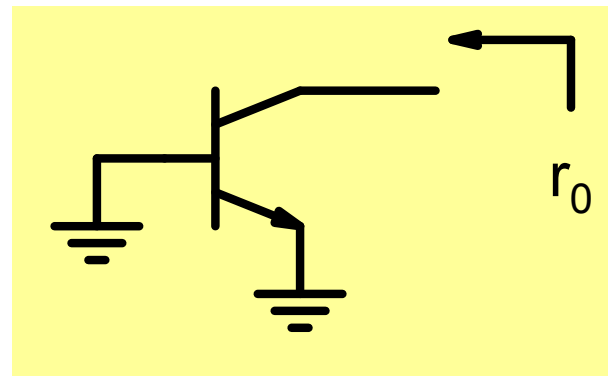

## CE Amplifier

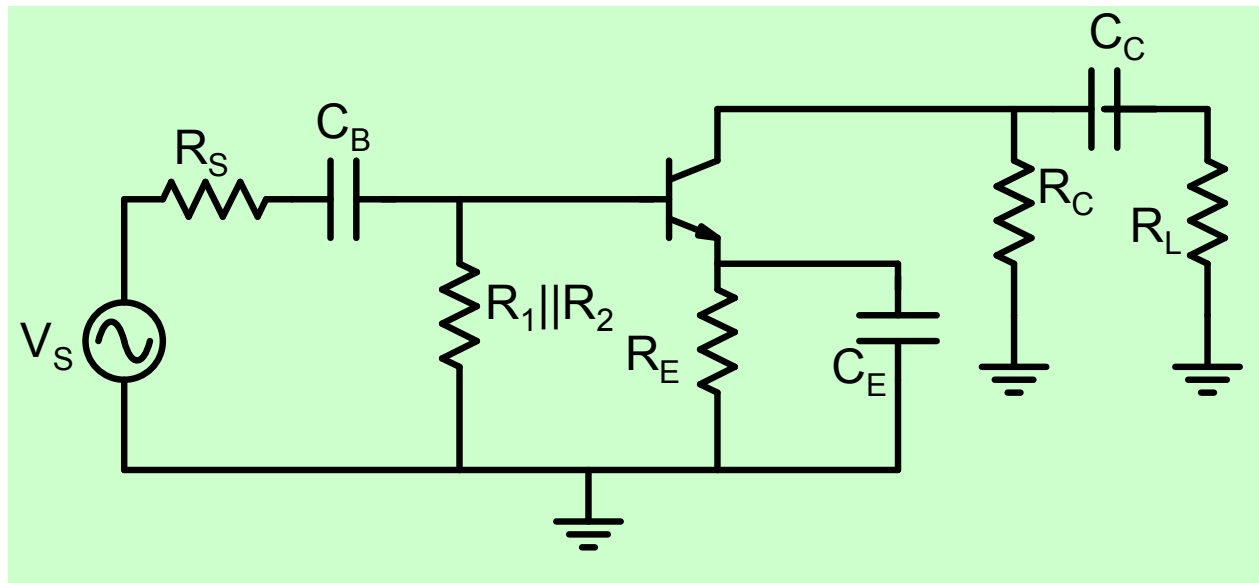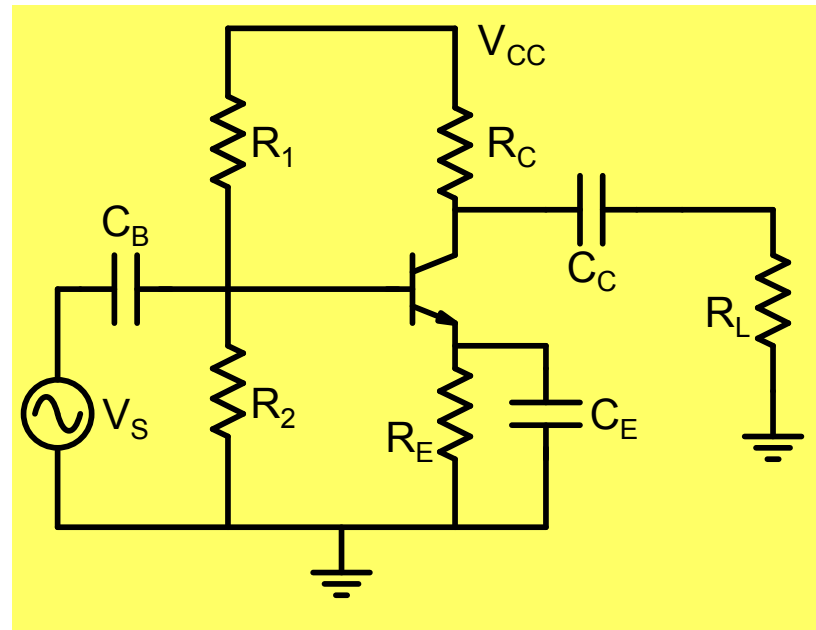


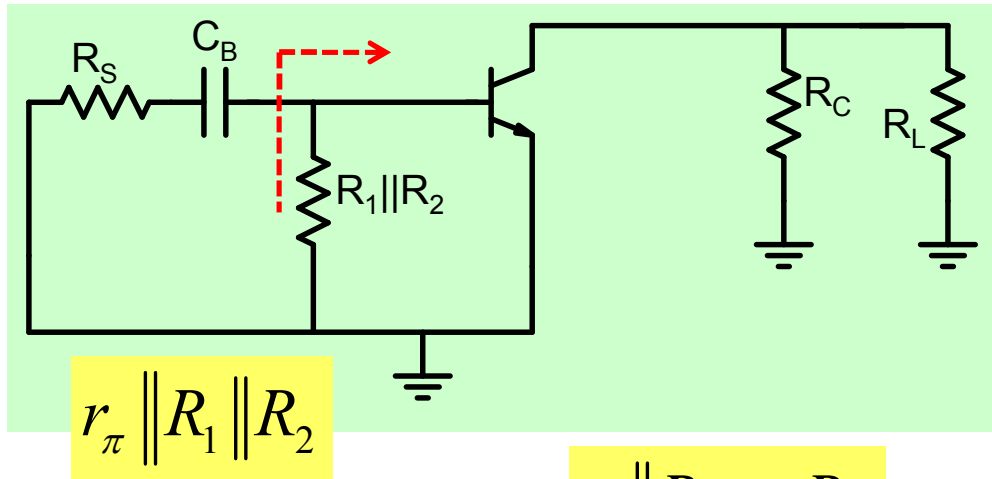Let us calculate 3dB frequency due to each capacitor alone





$$R_{eqB} = R_S + (r_{\pi} \parallel R_1 \parallel R_2)$$
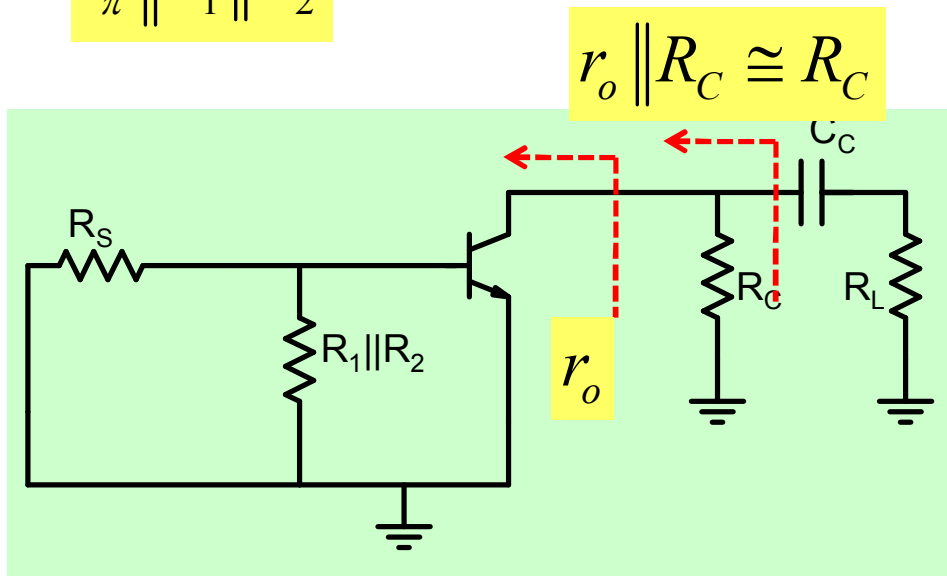
$$f_B = \frac{1}{2\pi C_B \{R_S + (r_{\pi} \parallel R_1 \parallel R_2)\}}$$



$$R_{eqC} = R_C + R_L$$
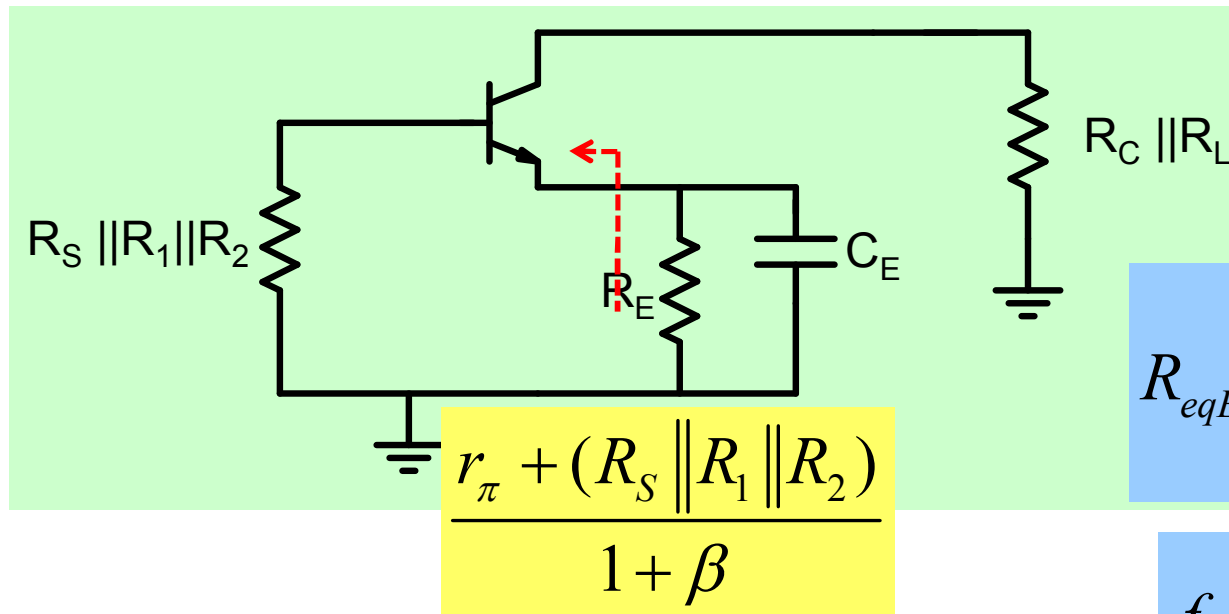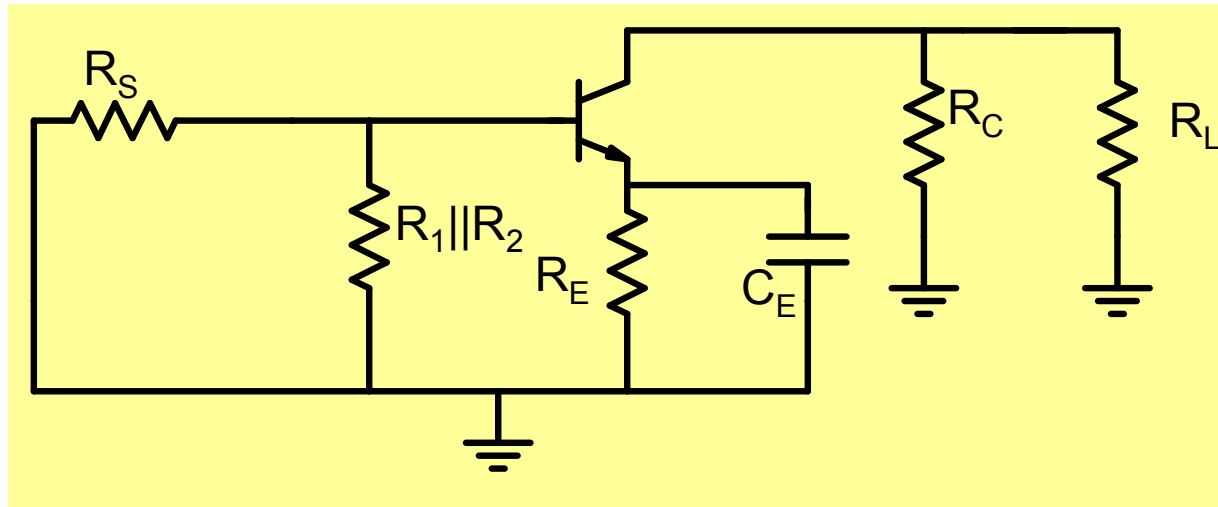
$$f_C = \frac{1}{2\pi C_C \{R_C + R_L\}}$$




$$\frac{r_{\pi} + (R_S \parallel R_1 \parallel R_2)}{1 + \beta}$$

$$R_{eqE} = R_E \parallel \frac{r_{\pi} + (R_S \parallel R_1 \parallel R_2)}{1 + \beta}$$

$$f_E = \frac{1}{2\pi C_E R_{eqE}}$$

## Example

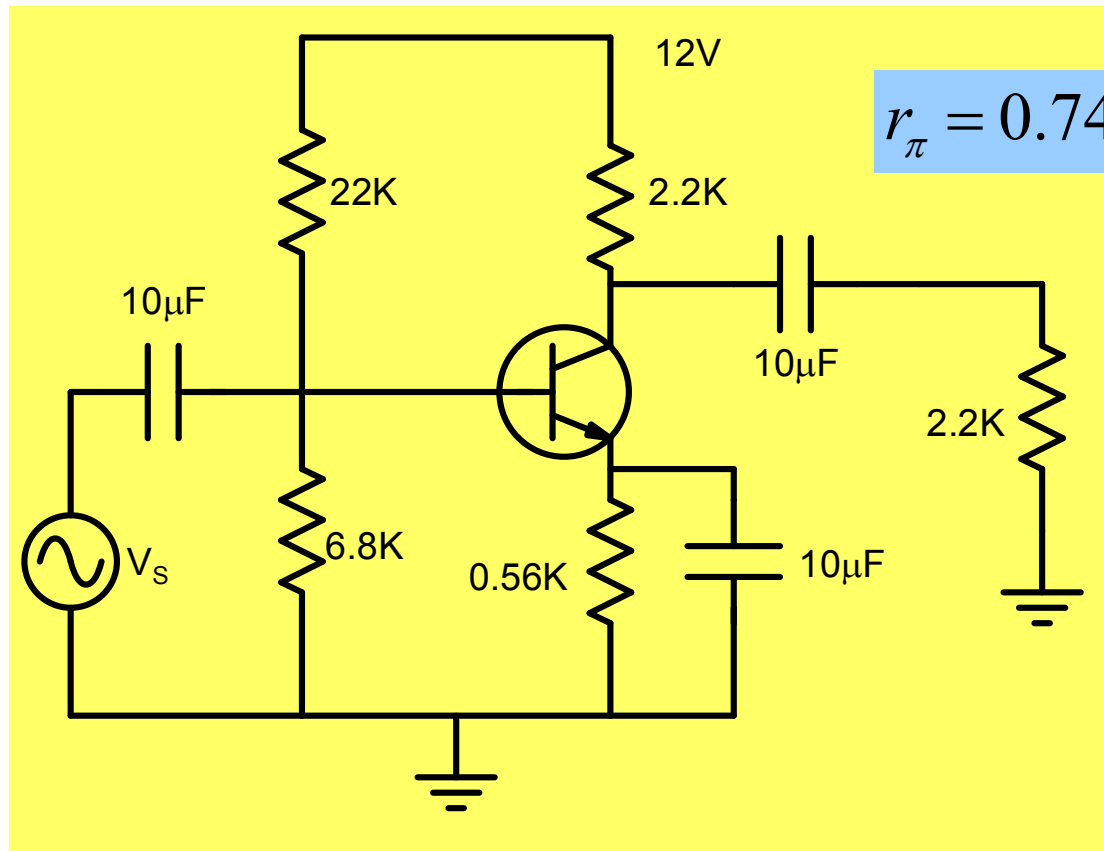

$$I_{CQ} = 3.48mA$$

$$r_{\pi} = 0.74K ; g_m = 0.13 \square ; A_V = -147.5$$


$$f_B = 24.4Hz$$

$$f_C = 3.6Hz$$

$$f_E = 2.18KHz$$

$$f_L \cong 2.18KHz$$

# Simulation Results

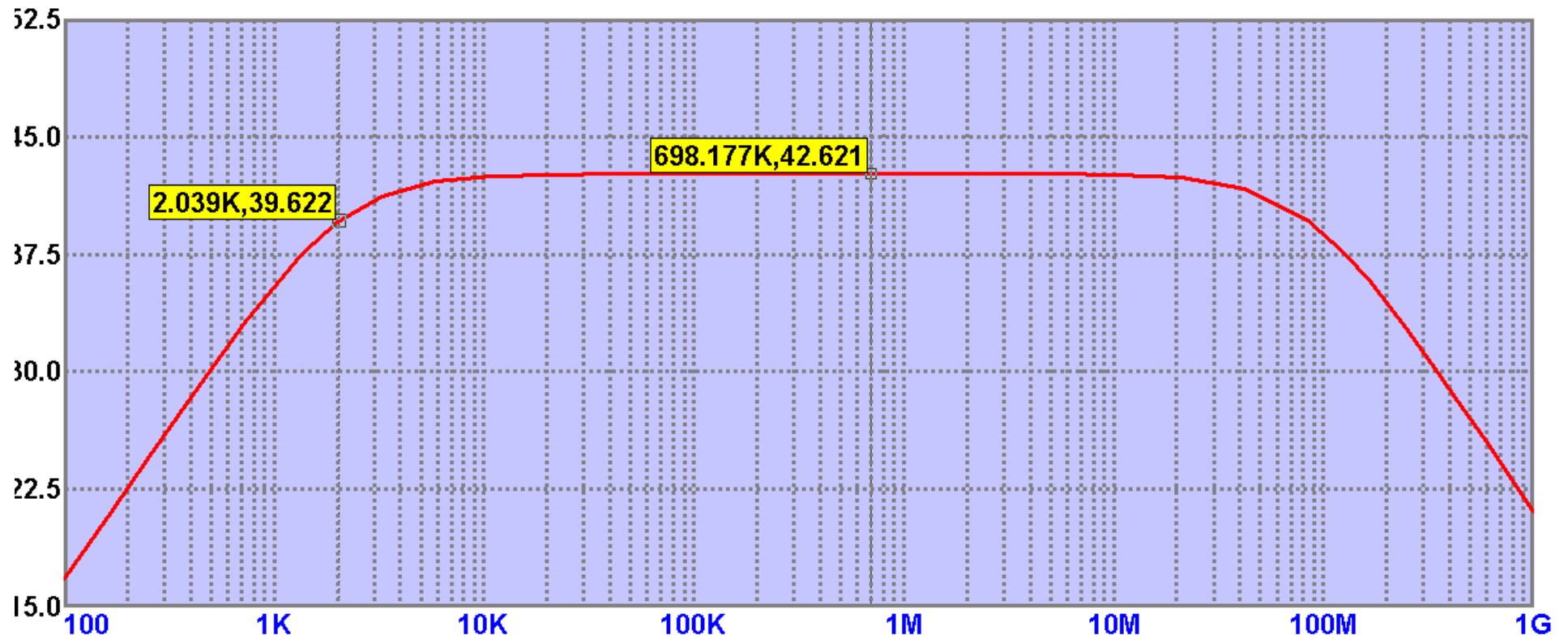



Typically  $f_E \gg f_B$  and  $f_c$

Consider a case where  $R_S \sim 0$ , no load and all capacitors are of equal magnitude

$$f_B = \frac{1}{2\pi C_B \times (R_S + R_B \parallel r_\pi)}$$

$$f_B \cong \frac{1}{2\pi C_B \times r_\pi}$$

$$f_c = \frac{1}{2\pi C_c \times (R_C + R_L)}$$

$$f_c \leq \frac{1}{2\pi C_c \times R_C}$$

$$f_E = \frac{1}{2\pi C_E \times (R_E \parallel \frac{(R_S \parallel R_B) + r_\pi}{\beta})}$$

$$f_E \cong \frac{\beta}{2\pi C_E \times r_\pi}$$

Note that :

$$I_{CQ} R_E \gg V_T \Rightarrow R_E \gg \frac{r_\pi}{\beta}$$

$$f_B \cong \frac{1}{2\pi C \times r_\pi}$$

$$f_c \leq \frac{1}{2\pi C \times R_C}$$

$$f_E \cong \frac{\beta}{2\pi C \times r_\pi}$$

$$f_E = \beta \times f_B$$

$$\frac{f_E}{f_c} \geq \frac{I_{CQ} R_C}{V_T} = A_V \gg 1$$

This shows that typically, emitter bypass capacitor determines lower cutoff frequency !


**EE 210**

**BJT Amplifier Analysis**

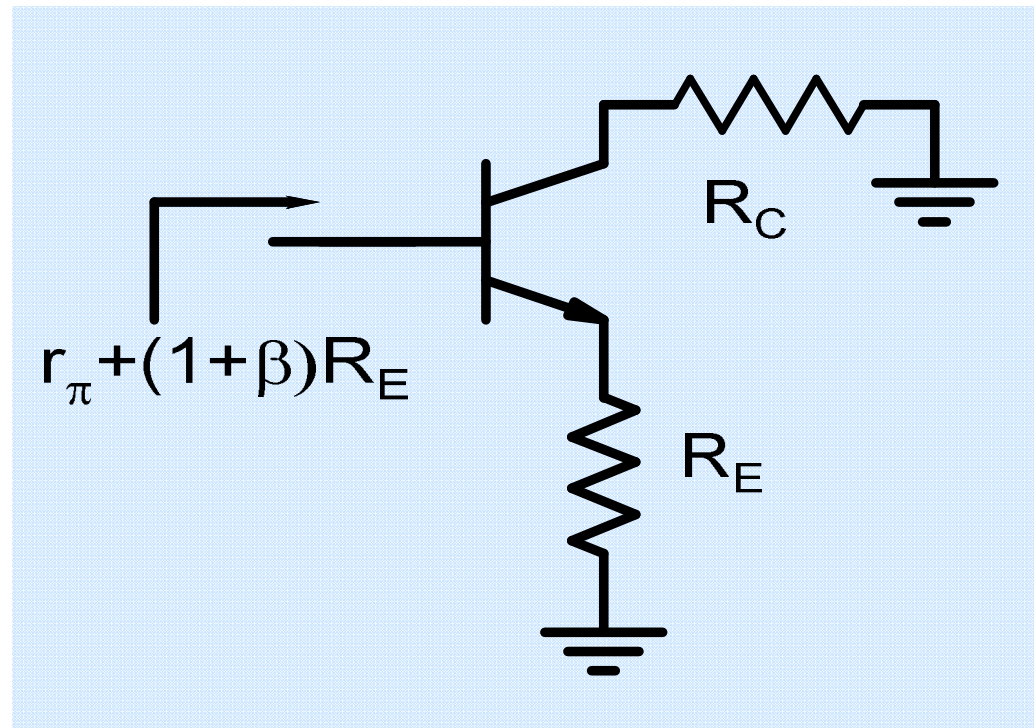
B. Mazhari  
Dept. of EE, IIT Kanpur

<https://youtu.be/HGqLEM8gaRM>

□ One useful result in small signal analysis of BJT amplifiers is that “looking from the base” the emitter resistance gets multiplied by the current gain  $\beta$  of the transistor.




## Simple Derivation

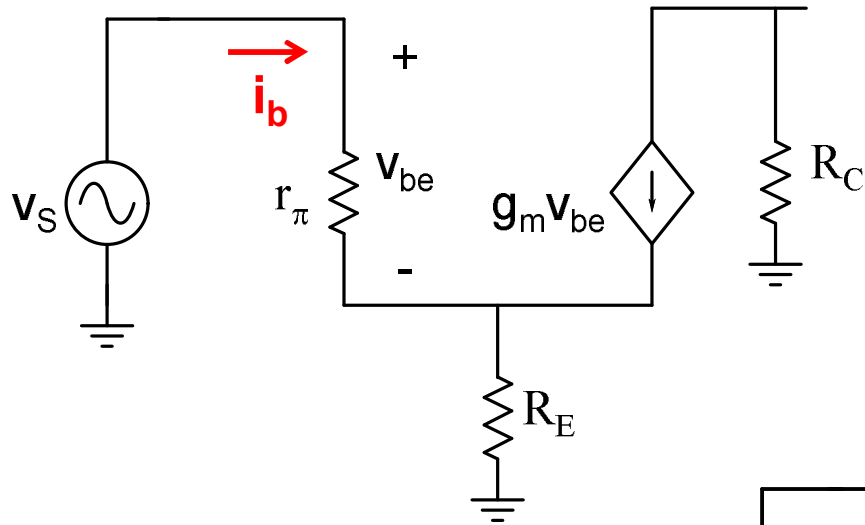



Circuit to Equation


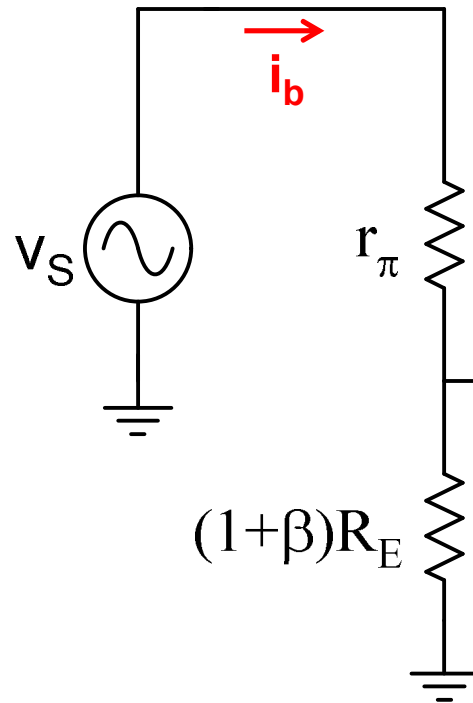
$$\begin{aligned} v_s &= i_b r_\pi + (i_b + g_m \times (i_b r_\pi)) R_E \\ &= i_b \times r_\pi + i_b \times (1 + \beta) R_E \end{aligned}$$





Equation to Circuit
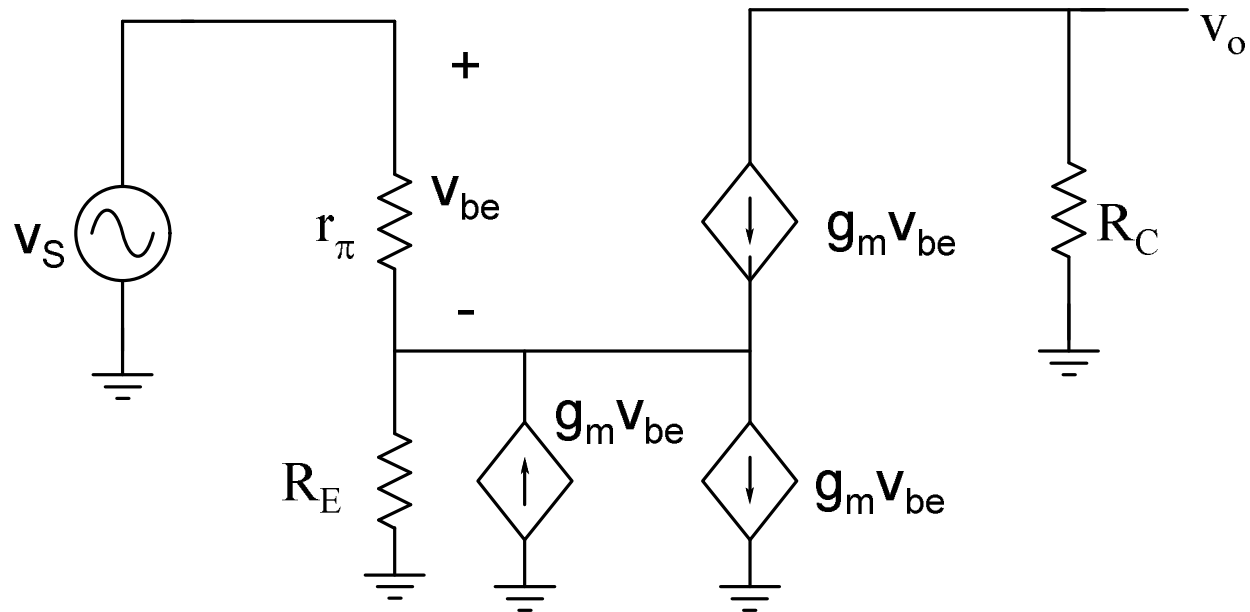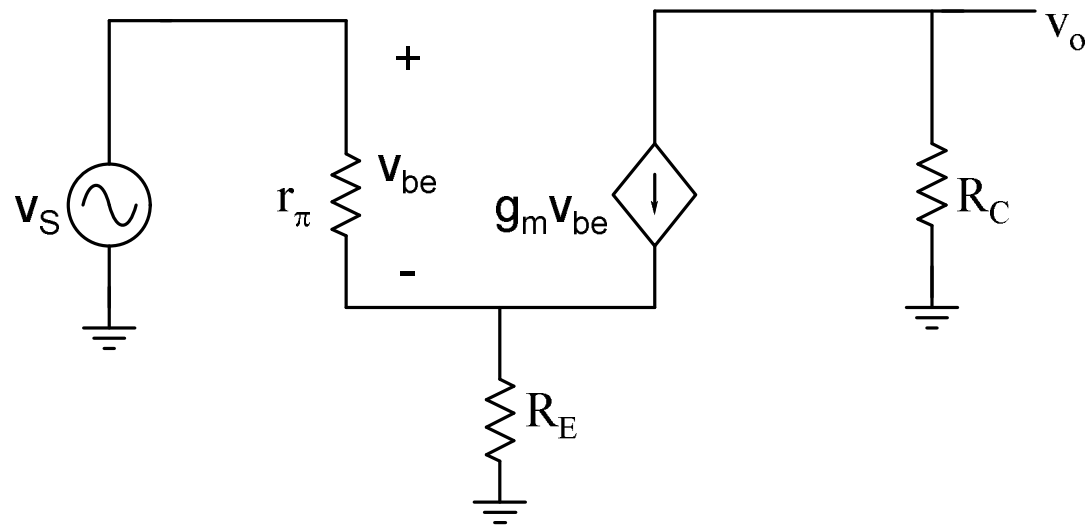
## Alternative derivation based on circuit transformation




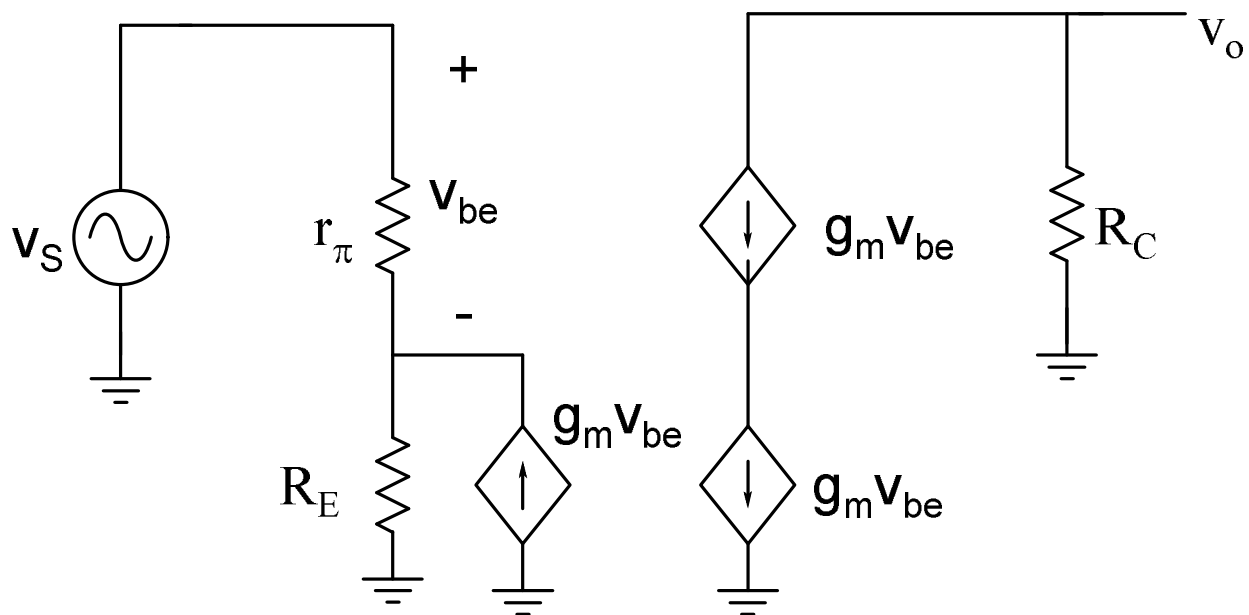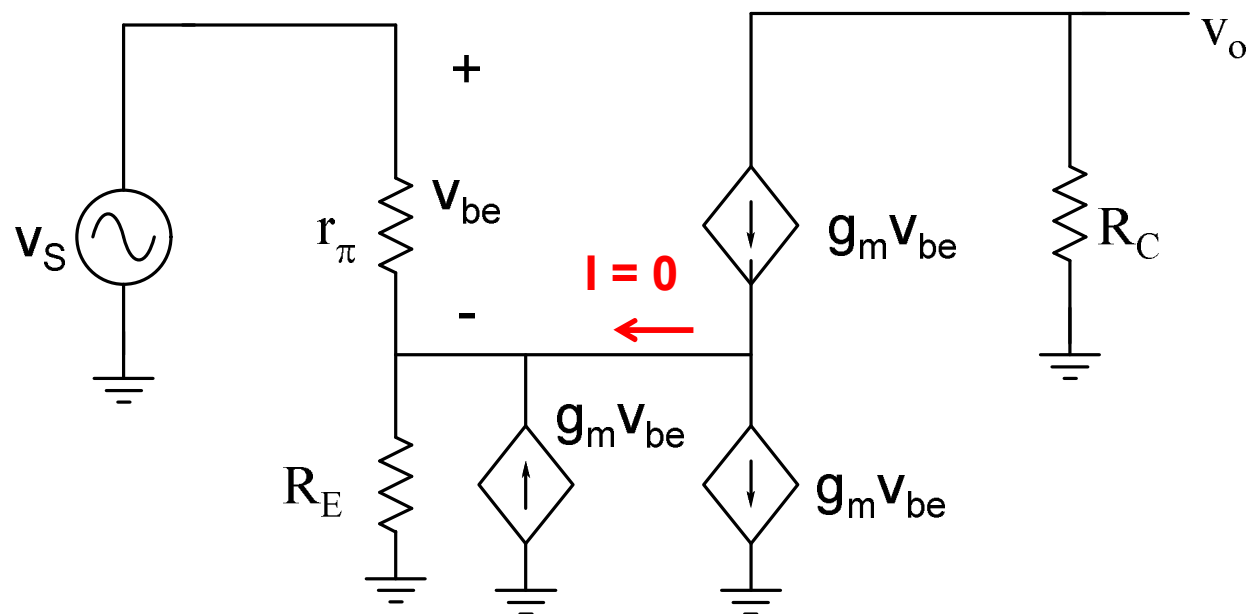

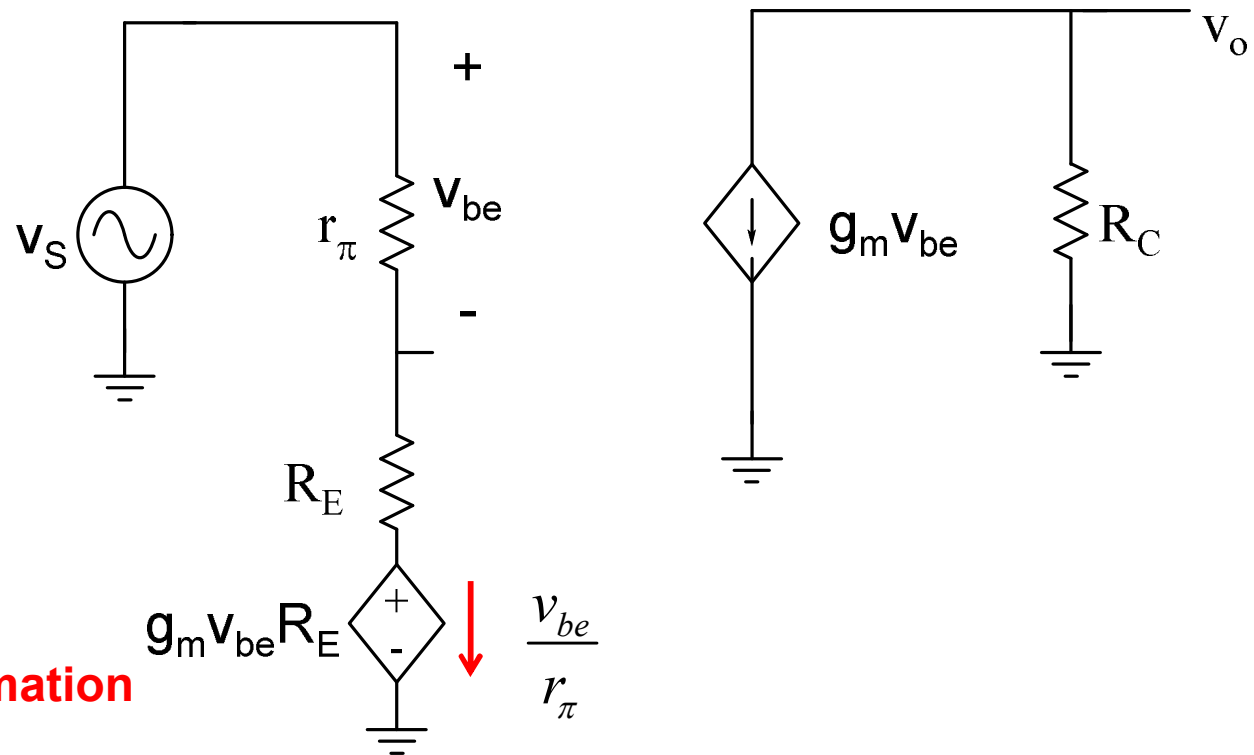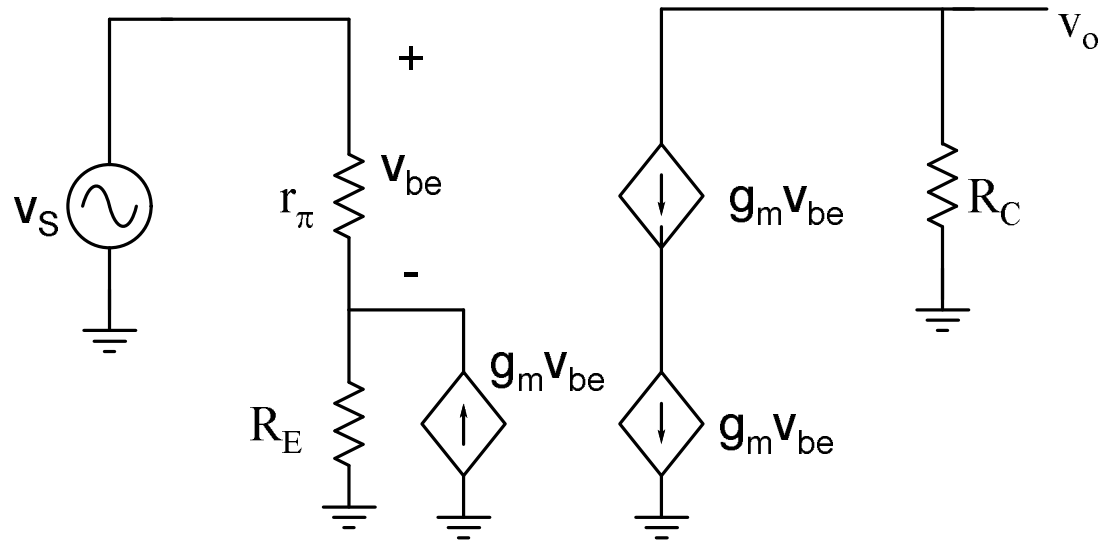



**Source transformation**





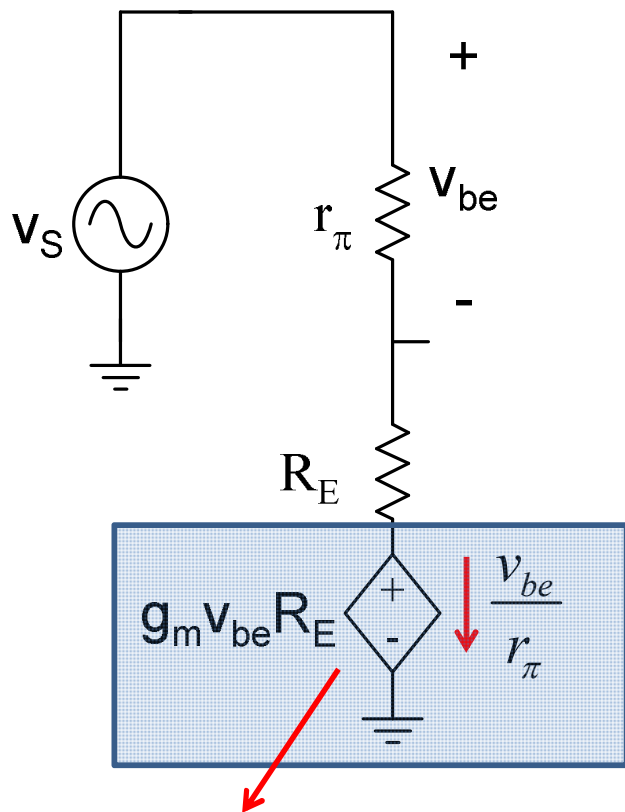


$$R = \frac{g_m v_{be} R_E}{\frac{v_{be}}{r_\pi}}$$

$$= g_m r_\pi R_E = \beta R_E$$

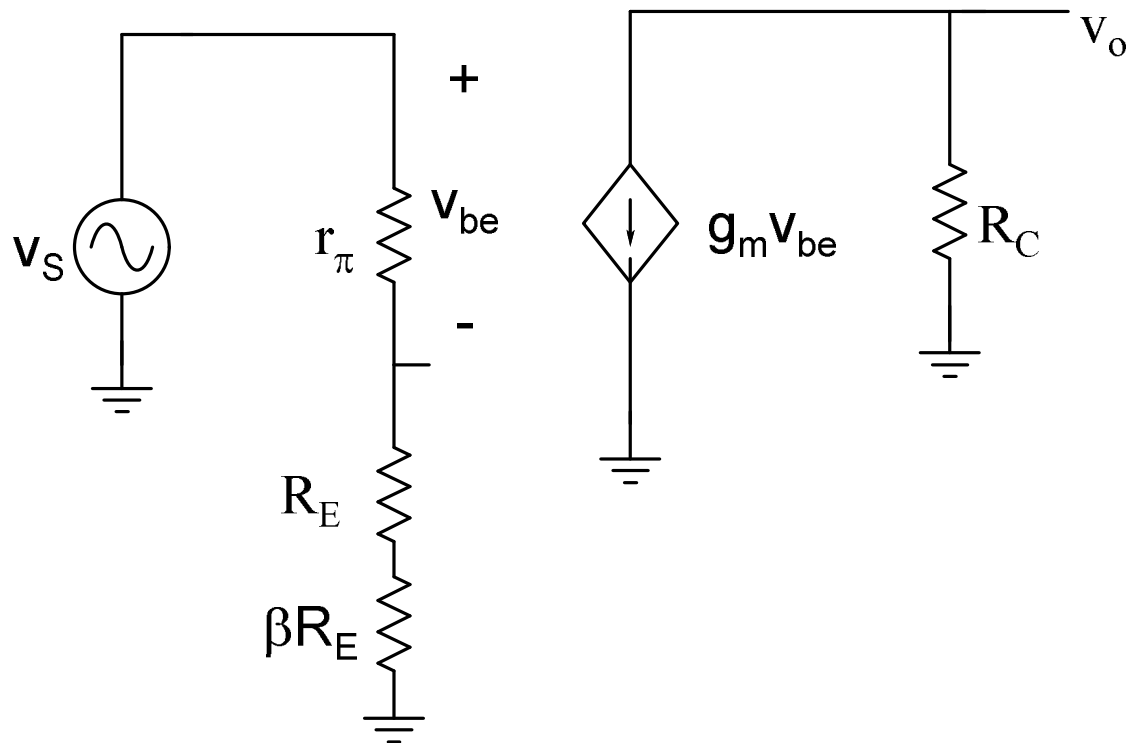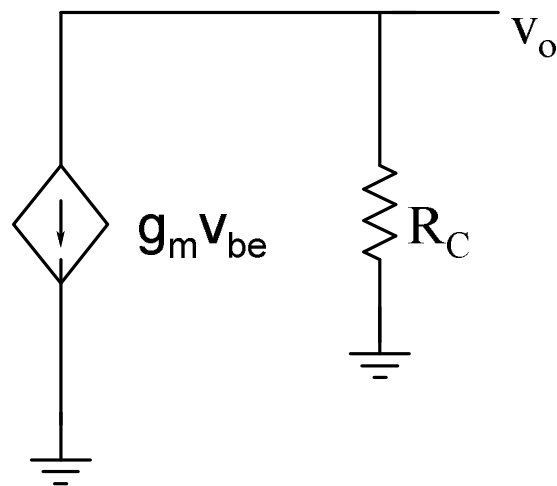

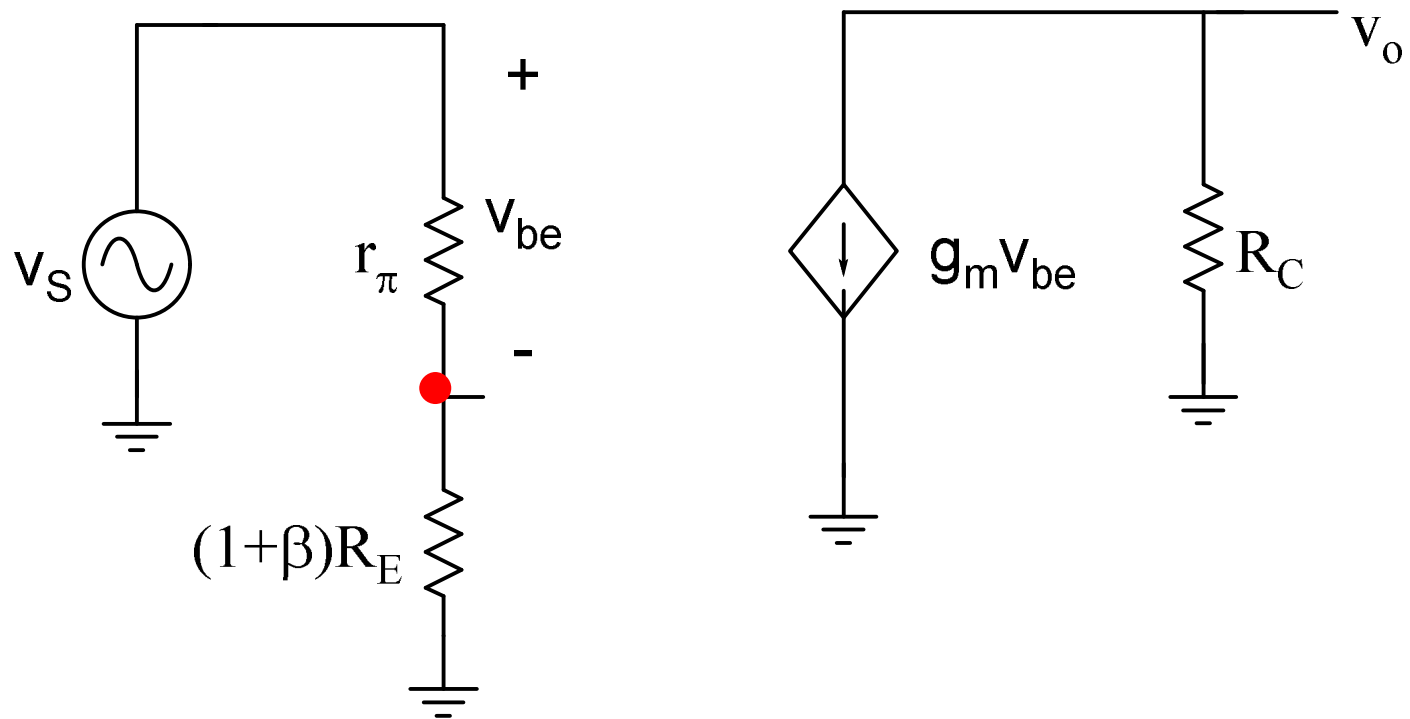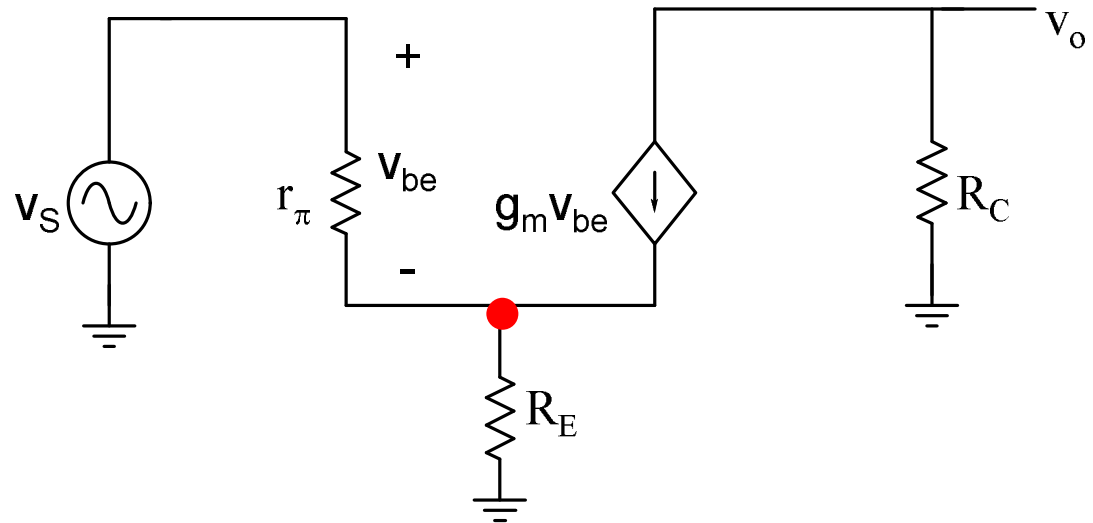

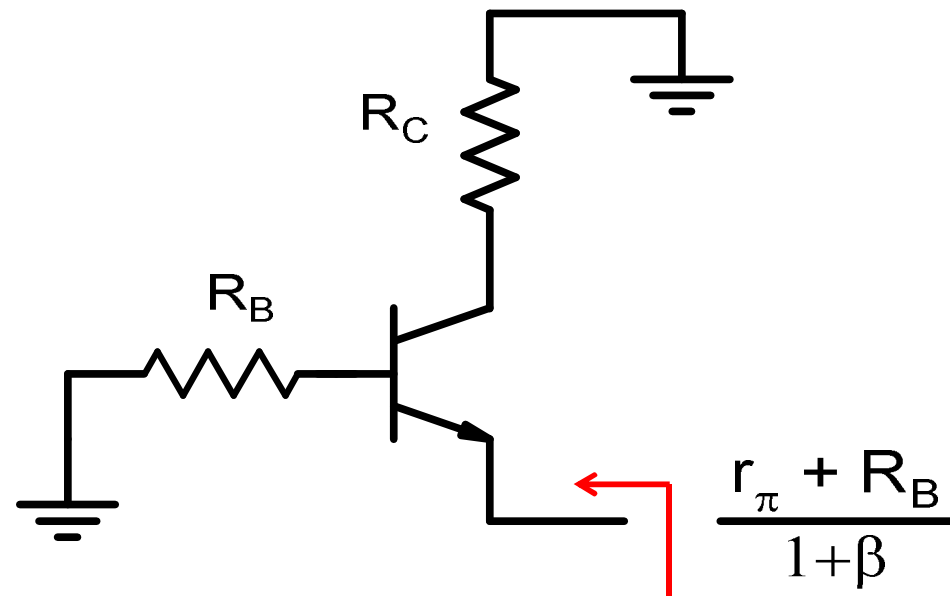□ Another useful result in small signal analysis of BJT amplifiers is that “looking from the emitter” any resistance in the base gets divided by the current gain  $\beta$  of the transistor.



## Derivation based on circuit transformation

