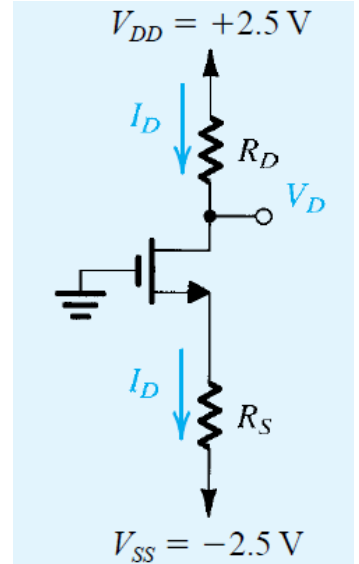


EE210: HW-14


Date: 11/04/2019

Q.1 What are different regions of operation of the Enhancement mode NMOS Transistor?


Q.2 Design the circuit of Fig. shown below, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $L = 1 \mu\text{m}$, and $W = 32 \mu\text{m}$. Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$).



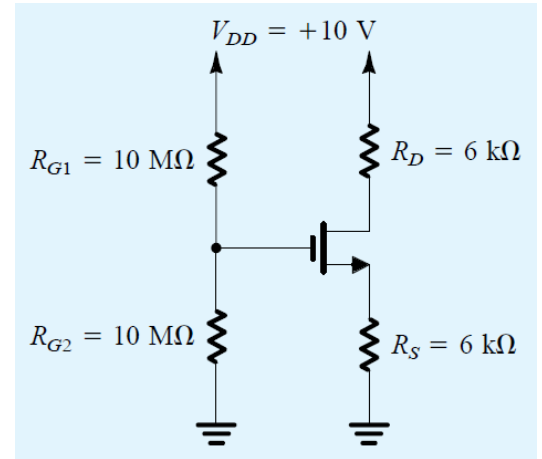Q.3 Analyze the circuit shown in Fig. below to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1 \text{ V}$ and $k_n' (W/L) = 1 \text{ mA/V}^2$ and Neglect the channel-length modulation effect.



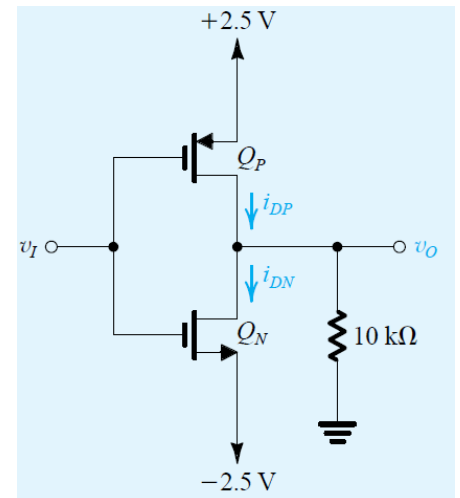
Q.4 The NMOS and PMOS transistors in the circuit shown below are matched, with $k_n' (W_n/L_n) = k_p' (W_p/L_p) = 1 \text{ mA/V}^2$ and, $V_{tn} = -V_{tp} = 1 \text{ V}$. Assuming $\lambda = 0$ for both devices, find the drain currents i_{DN} and i_{DP} , as well as the voltage v_O , for $v_I = 0 \text{ V}$, $+2.5 \text{ V}$, -2.5 V .



Q.5 For the Common Drain circuit shown in Fig. below, assume that the MOSFET M has $W/L = 10$ and $\lambda = 0$. Other parameters are: $k_n' = 40 \mu\text{A}/\text{V}^2$, $\gamma = 0.4 \text{ V}^{1/2}$, $2\phi_F = 0.6\text{V}$, and $V_{TN0} = 0.7\text{V}$. Find the dc output voltage V_0 , and the ac small-signal midband voltage gain v_0/v_i under the following conditions:

(i) Ignoring body effect and with $R \rightarrow \infty$.

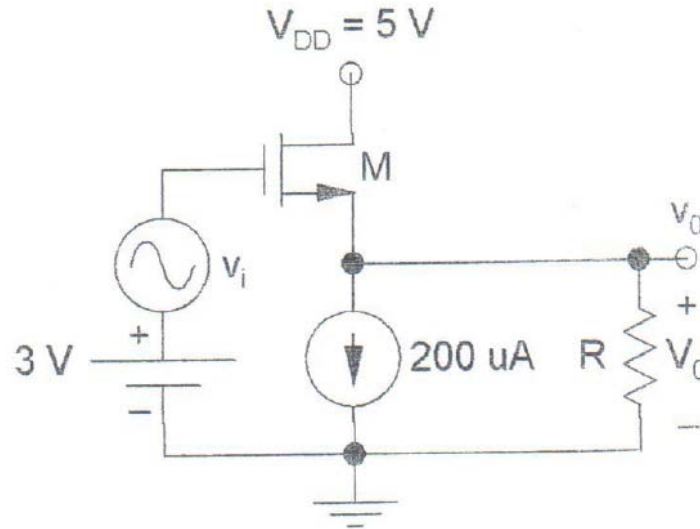(ii) Including body effect and with $R \rightarrow \infty$.



Q.6 Repeat Q.5 under the following conditions:

(i) Ignoring body effect and with $R \rightarrow 100\text{k}\Omega$.

(ii) Including body effect and with $R \rightarrow 10\text{k}\Omega$.