

EE210: Microelectronics-I


Lecture-22 :CE Amplifier-10

Problems



Instructor - Y. S. Chauhan

Slides - B. Mazhari
Dept. of EE, IIT Kanpur





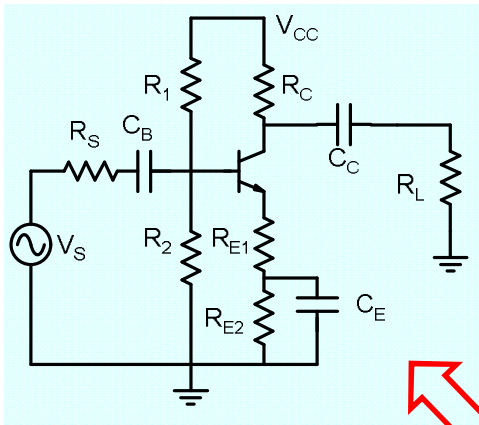
**Today's Problems are a result
of yesterday's Solutions !**




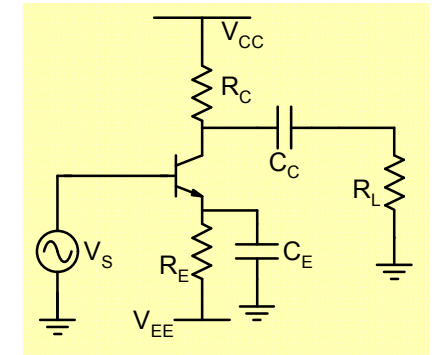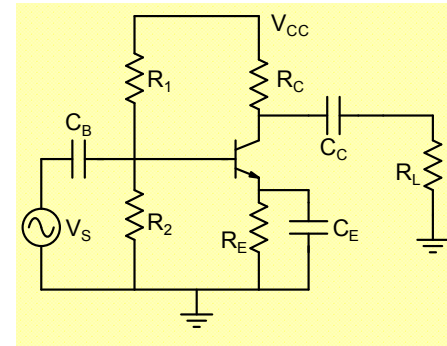Linearity
Input resistance
Higher input voltage





Better β Stability

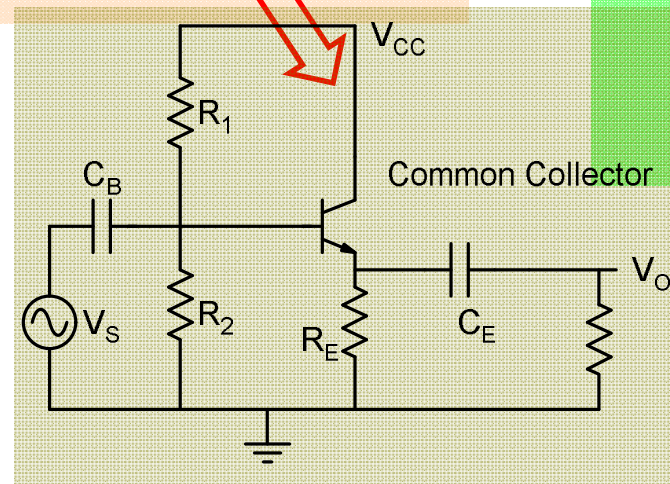
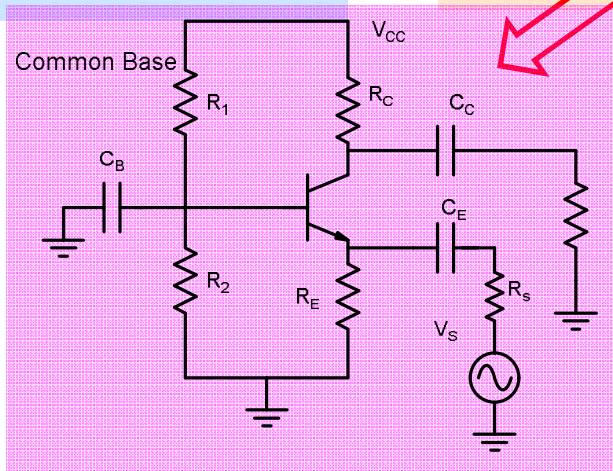
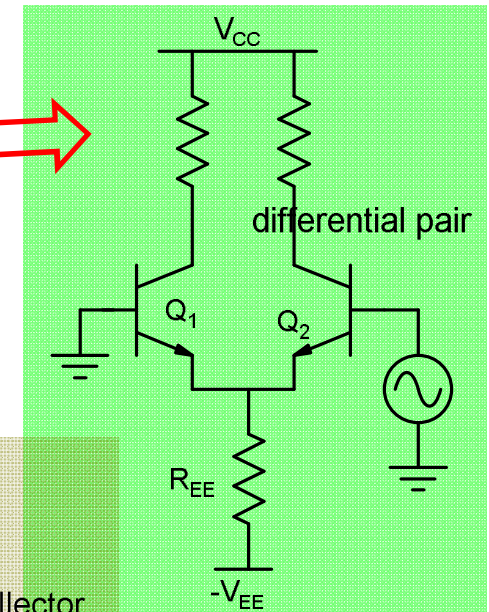
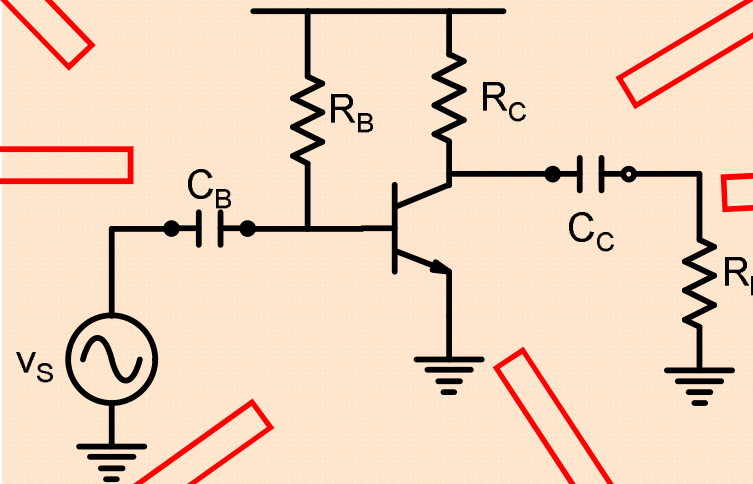
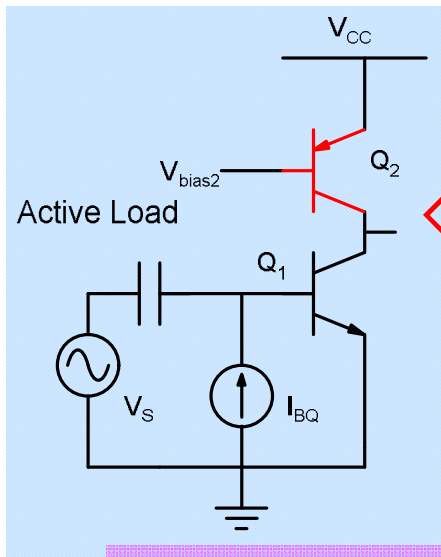


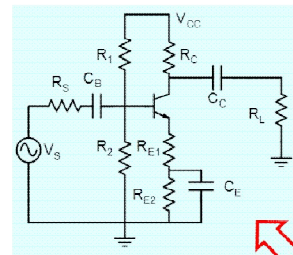

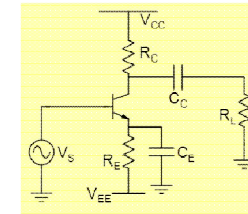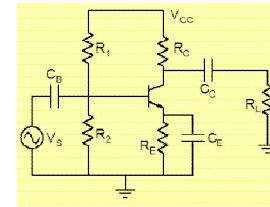
Linearity
Input resistance
Higher input voltage



Better β Stability

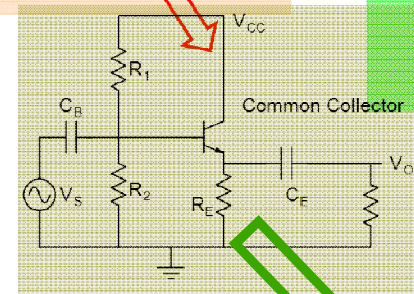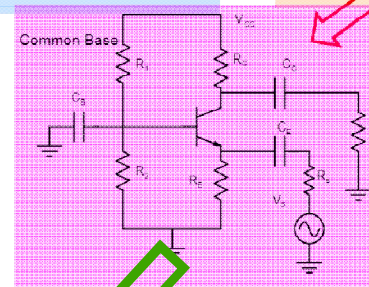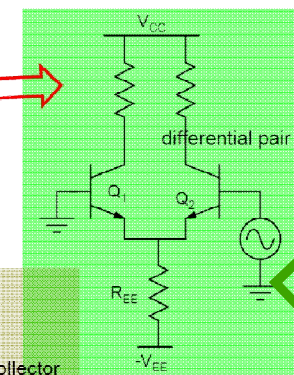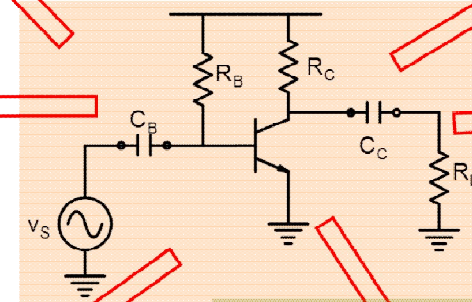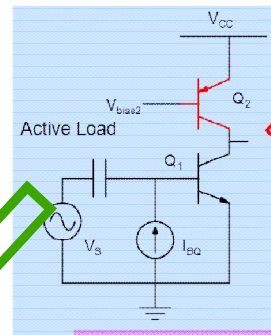

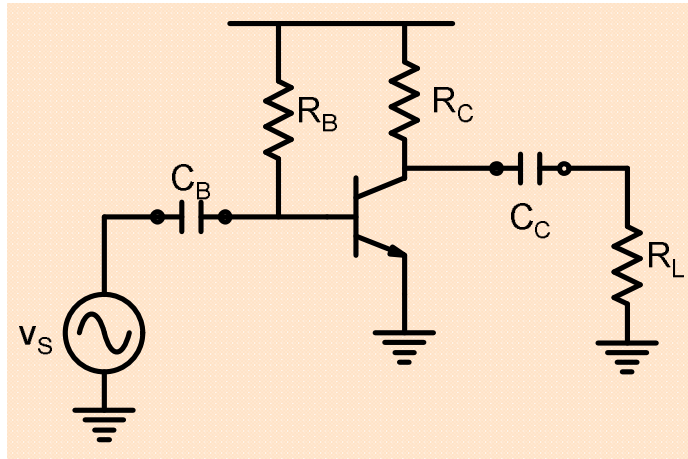Problem-1: How can we obtain higher voltage gain without requiring very high supply voltage?





$$A_V = -\frac{I_{CQ}}{V_T} \times R_C \parallel R_L$$

$$A_V < \frac{I_{CQ} R_C}{V_T}$$

For $A_V = 10^3$, $V_{CC} > 26 \text{ V}$


For $V_{CC} = 1.5 \text{ V}$, $A_V < 50$

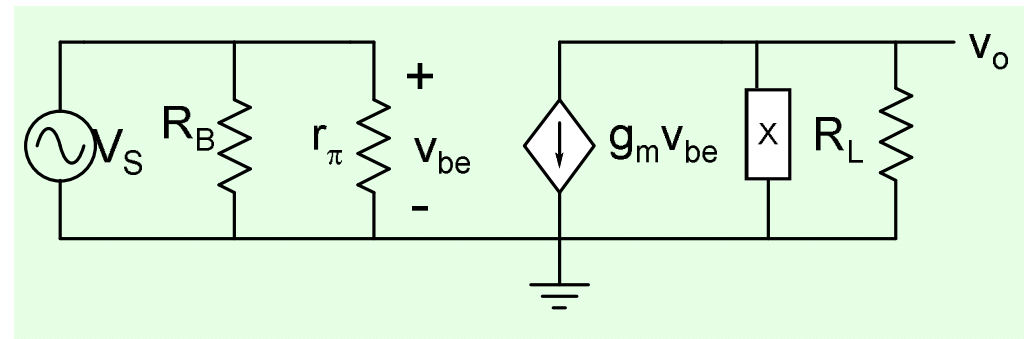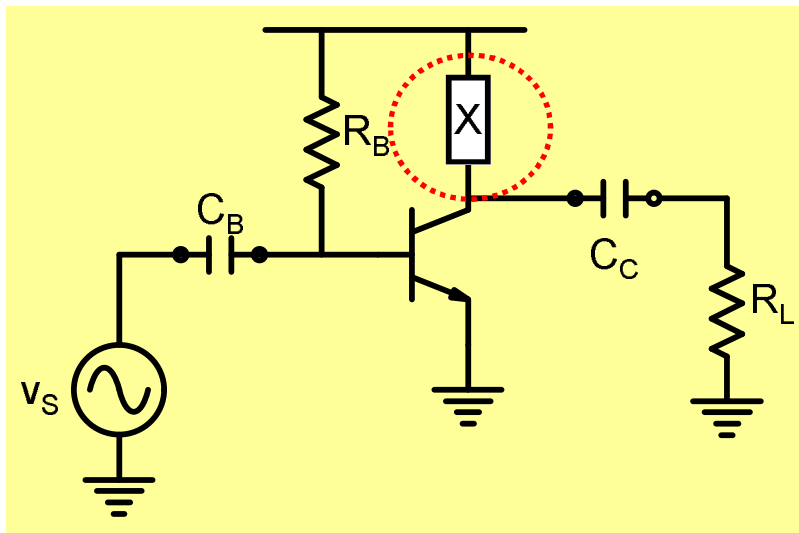



$$A_V < g_m \times r_X$$



We want an element that has **high small signal resistance** but **small dc voltage drop** across it.




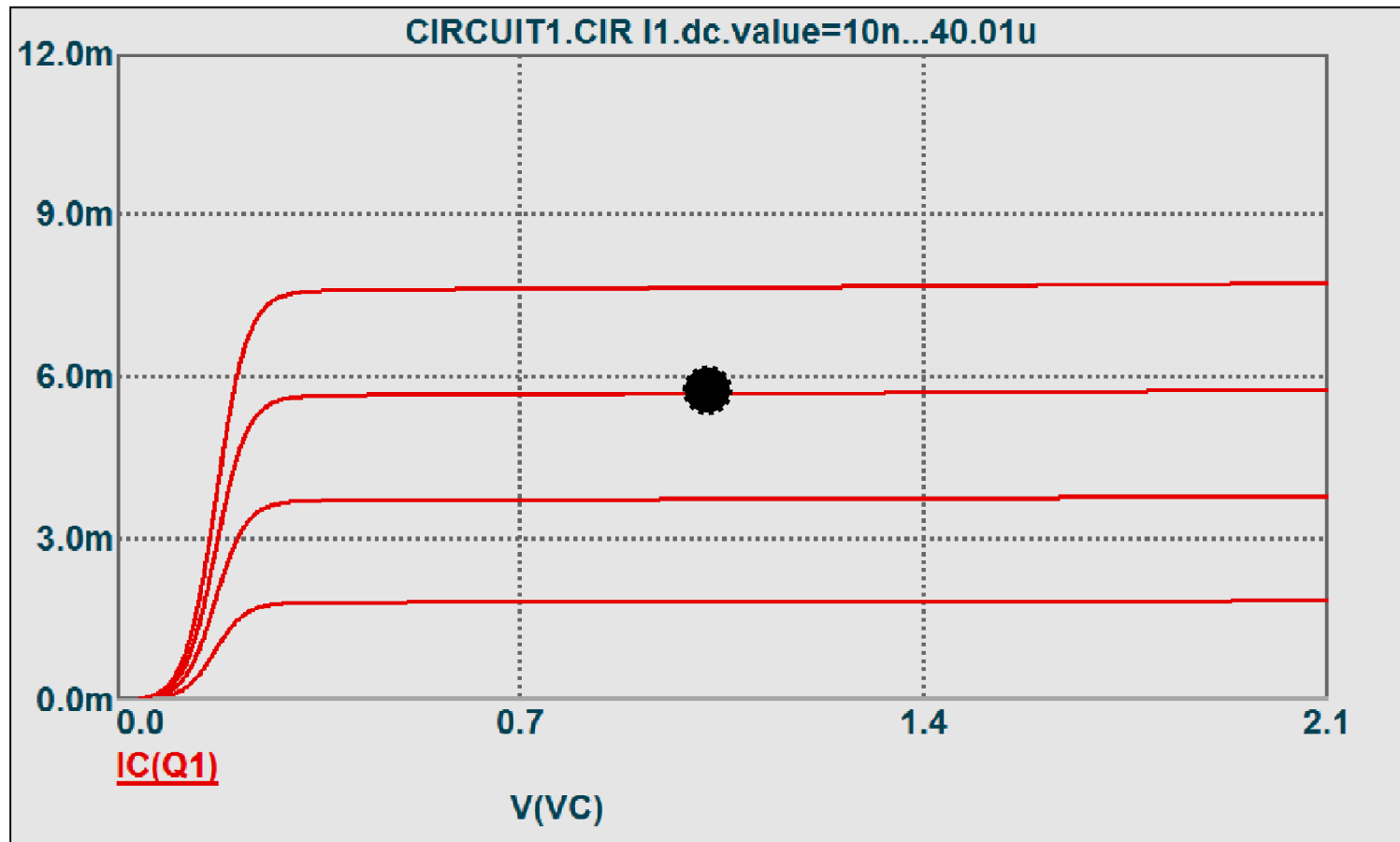
A Transistor has this desired property and can serve as an excellent 'load' element






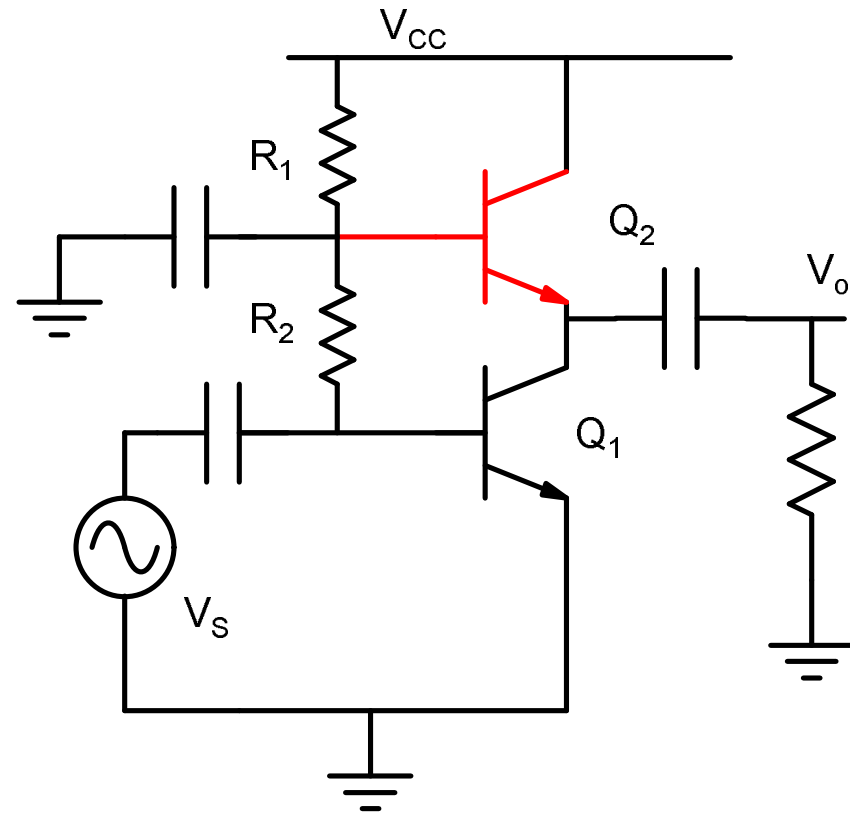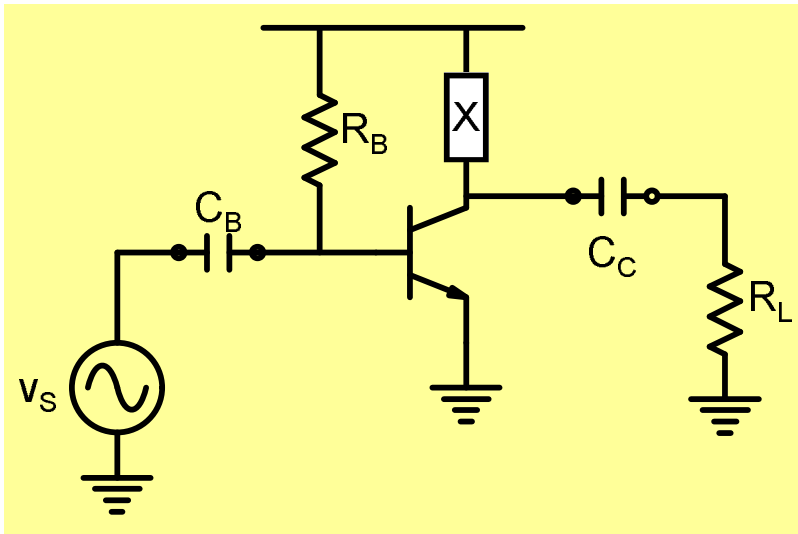Many high voltage gain amplifiers have active load !



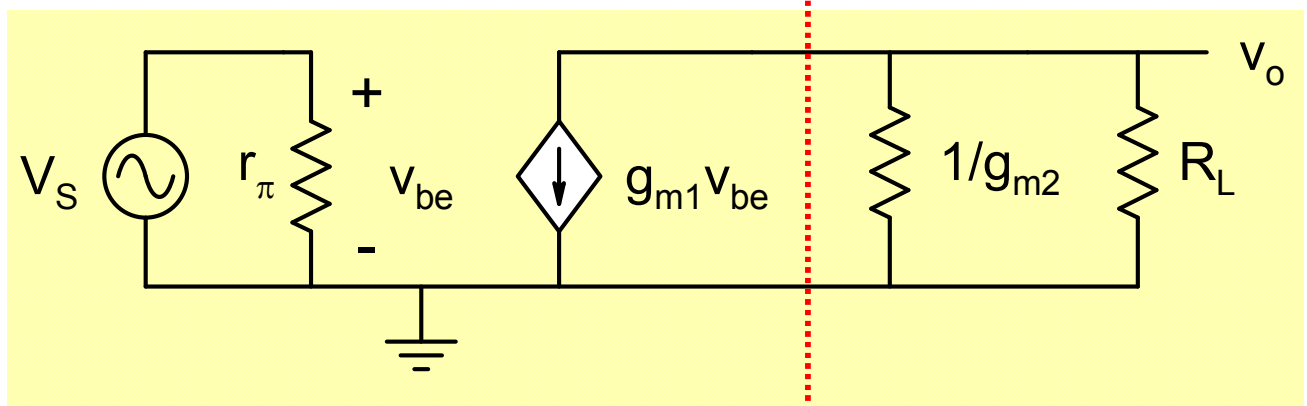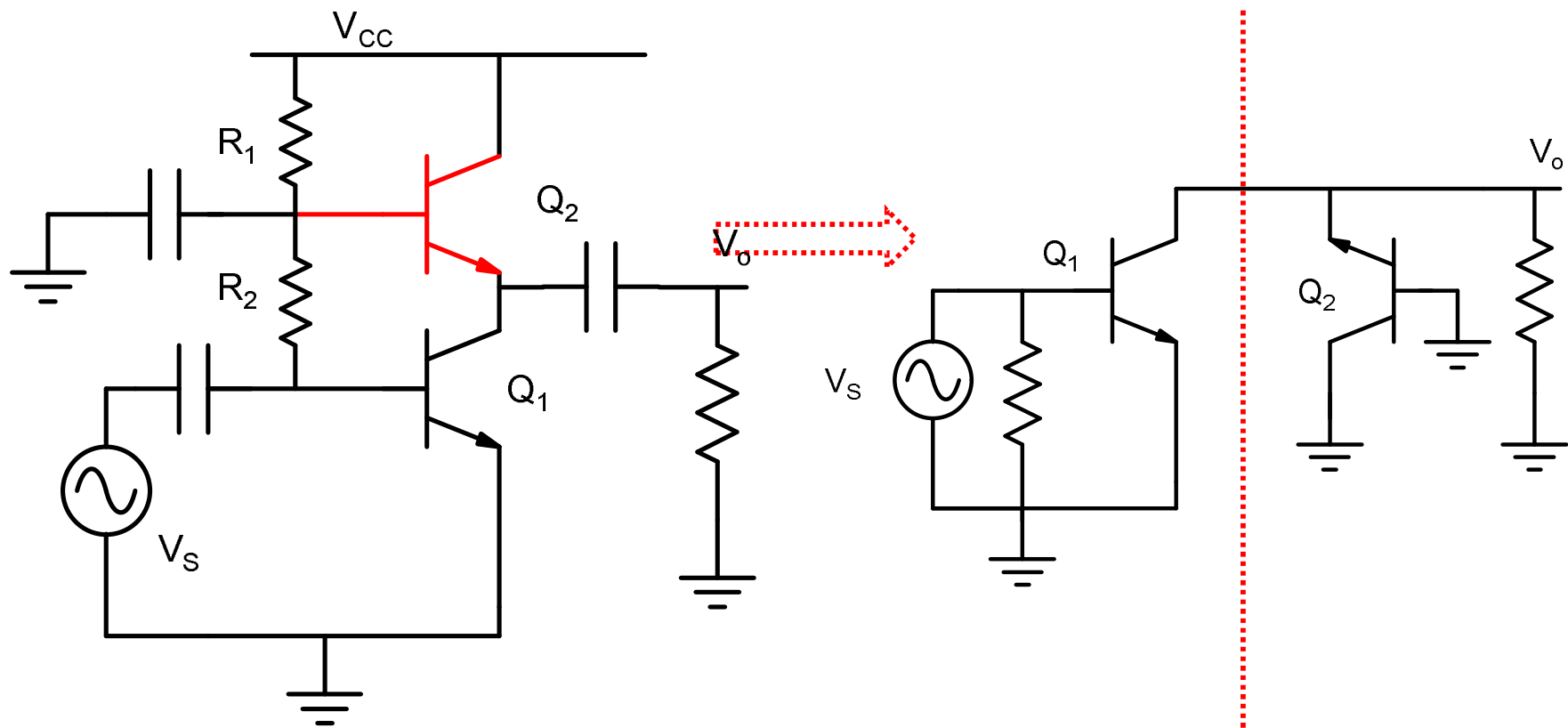

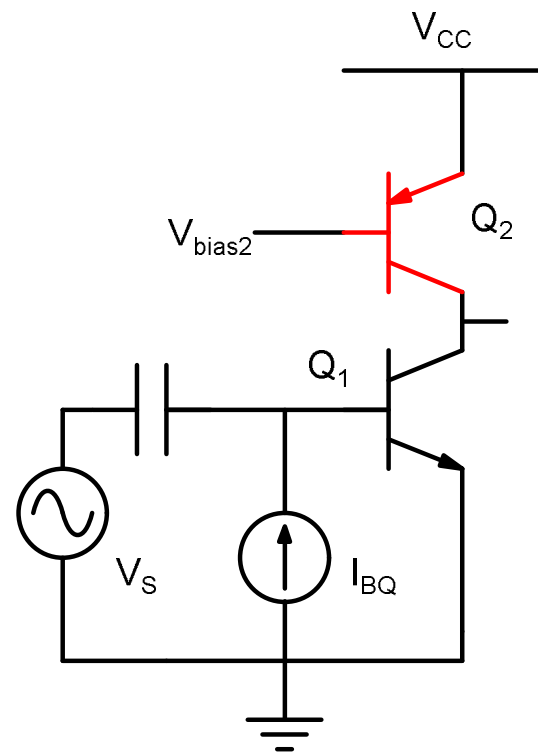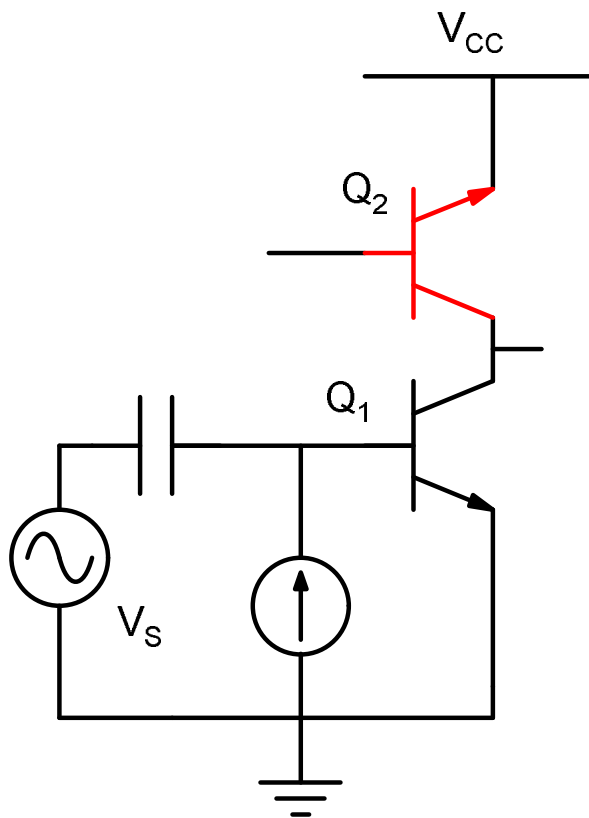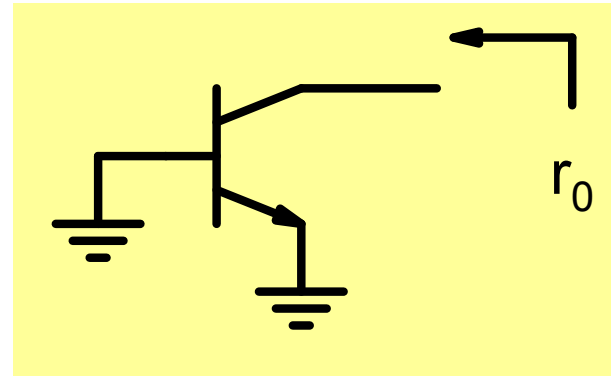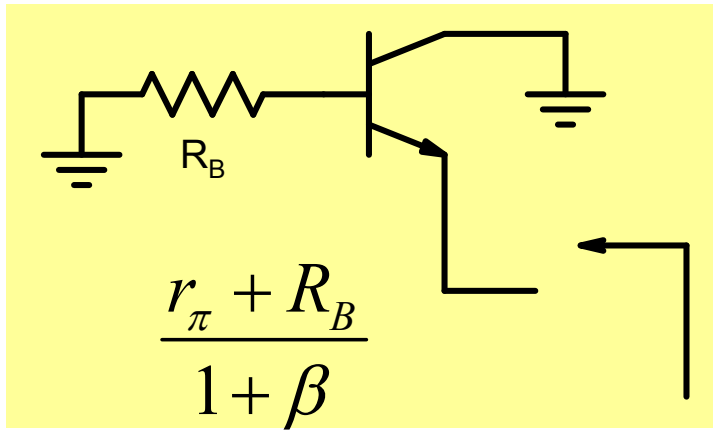


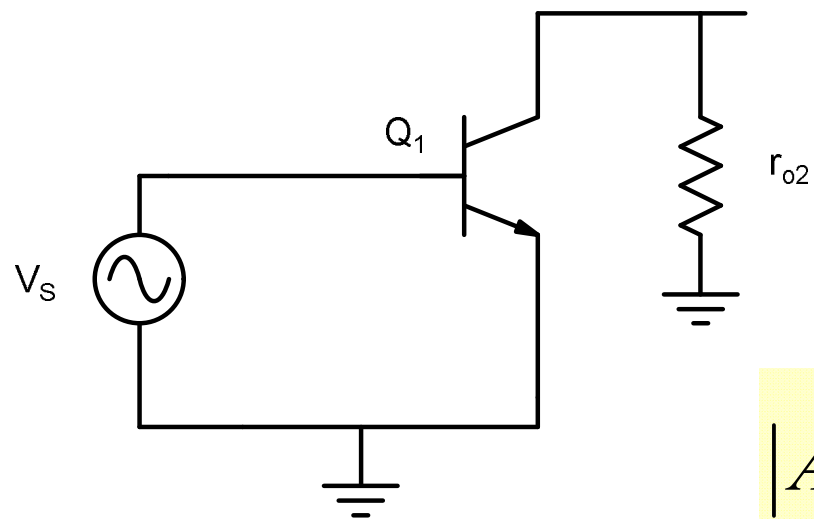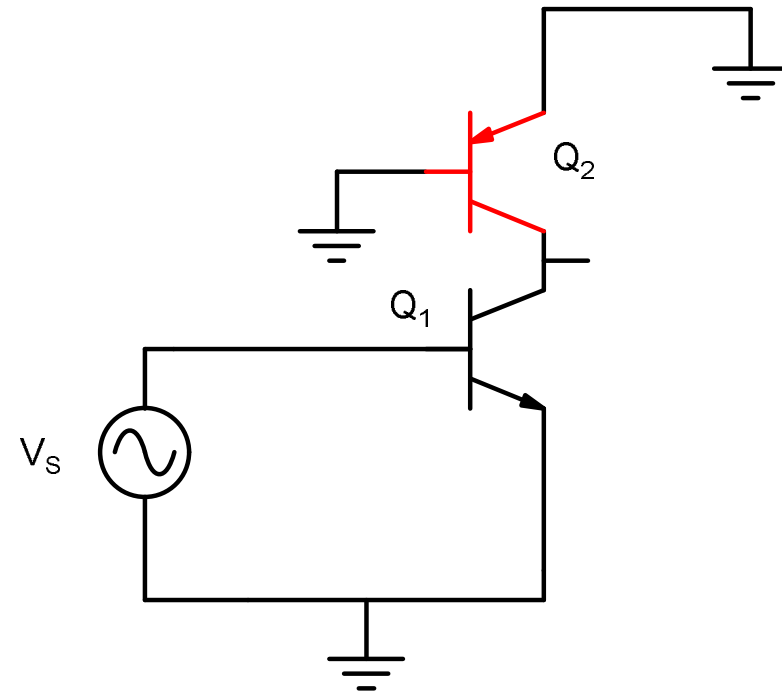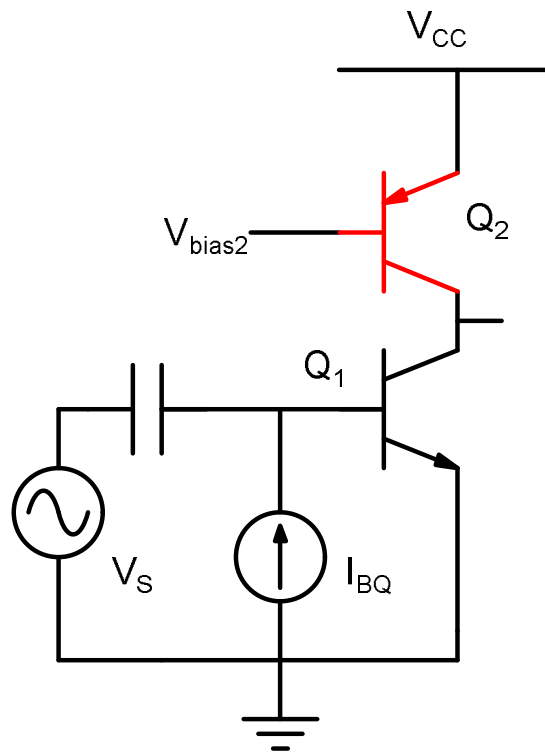

$$|A_V| = g_m \times r_{o1} \parallel r_{o2}$$

$$r_{o1} = \frac{V_{AN}}{I_{CQ}}; r_{o2} = \frac{V_{AP}}{I_{CQ}}$$

$$|A_V| = \frac{1}{V_T} \times \frac{V_{AN} \times V_{AP}}{V_{AN} + V_{AP}}$$

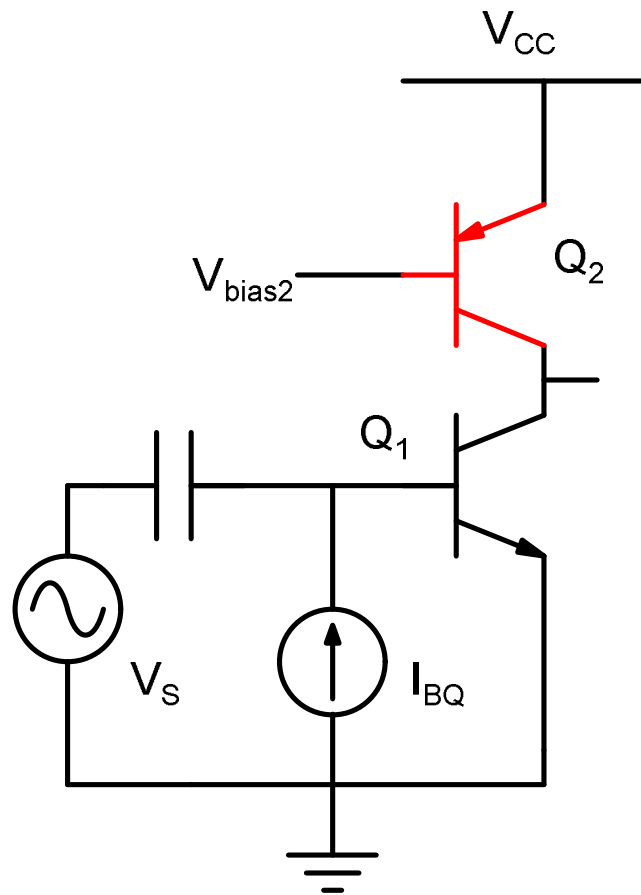


$$|A_V| = \frac{1}{V_T} \times \frac{V_{AN} \times V_{AP}}{V_{AN} + V_{AP}}$$

For $V_{AN} = V_{AP} = 100$, $A_V = 1.9 \times 10^3$
independent of supply voltage

Alternative Solution

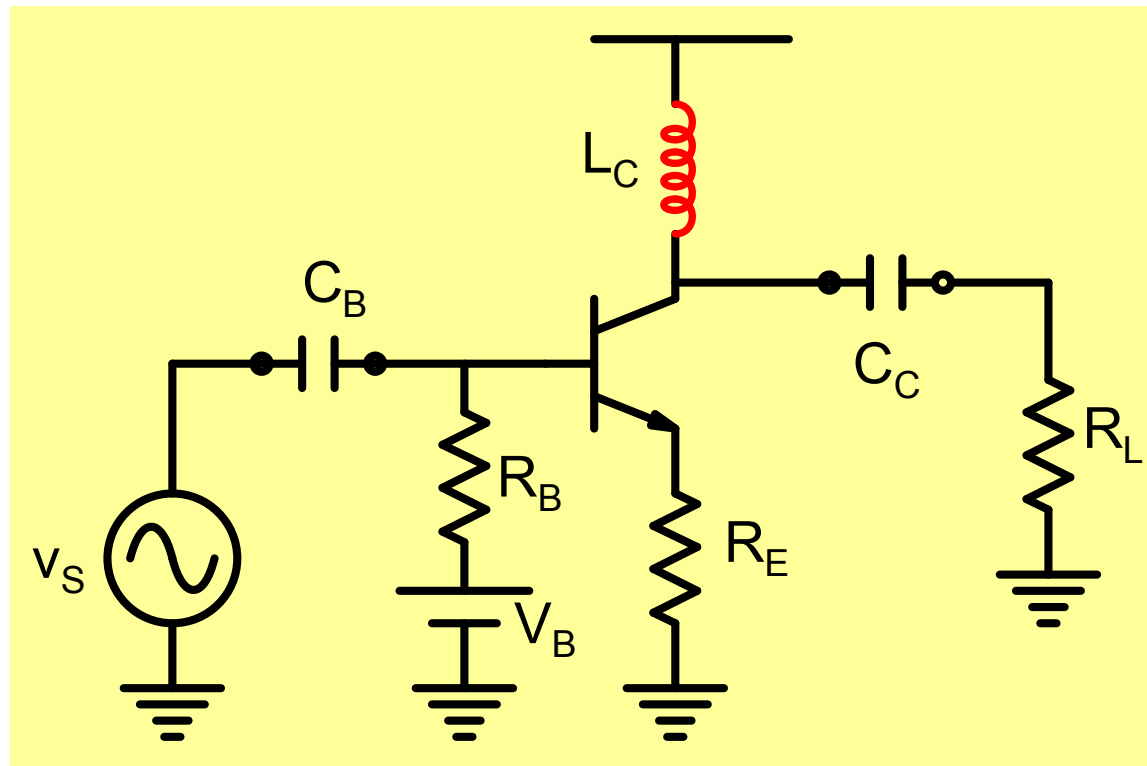
An Inductor has zero dc drop but can have high ac impedance !



$$\omega L \gg R_L$$


$$f = 1K; R_L = 1K \Rightarrow L > 1.6H!!$$

AM radio receiver circuit

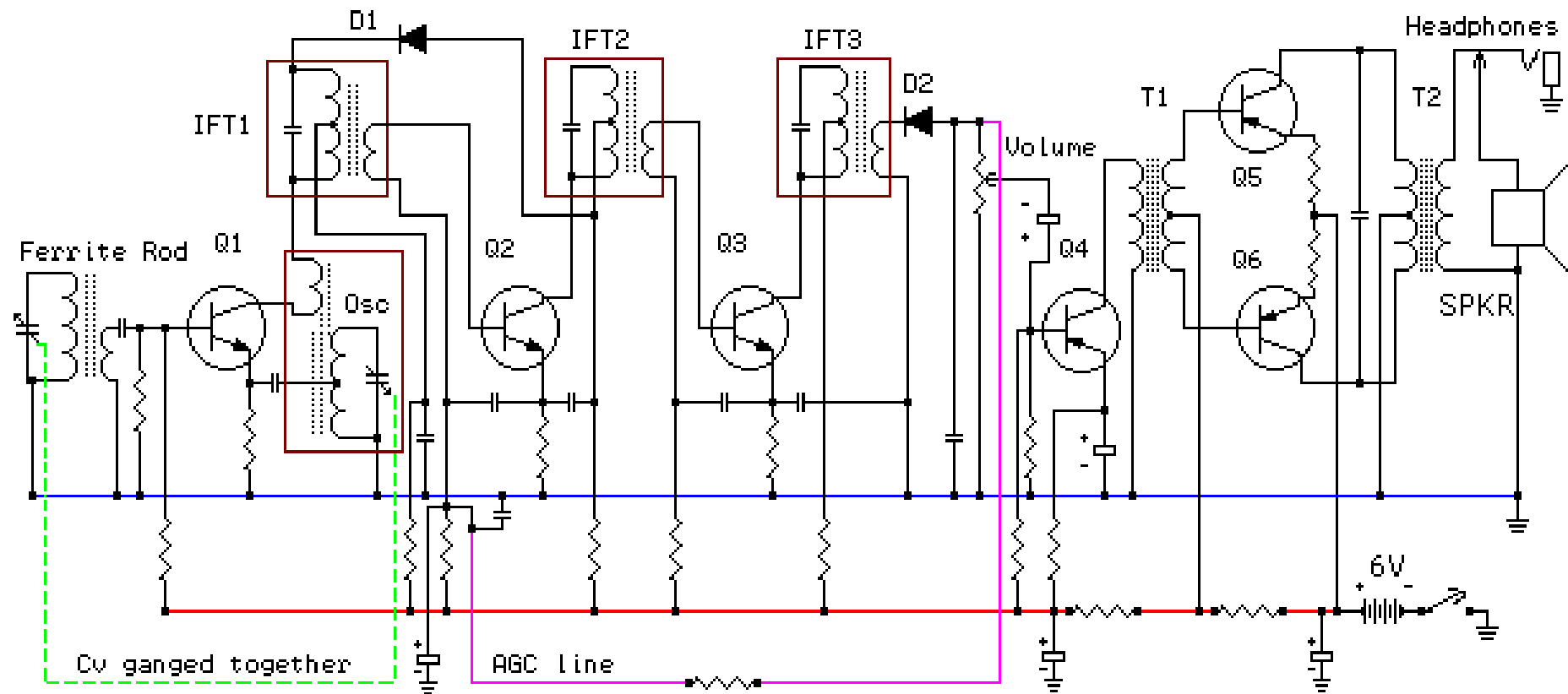


Note the use of lots of transformers

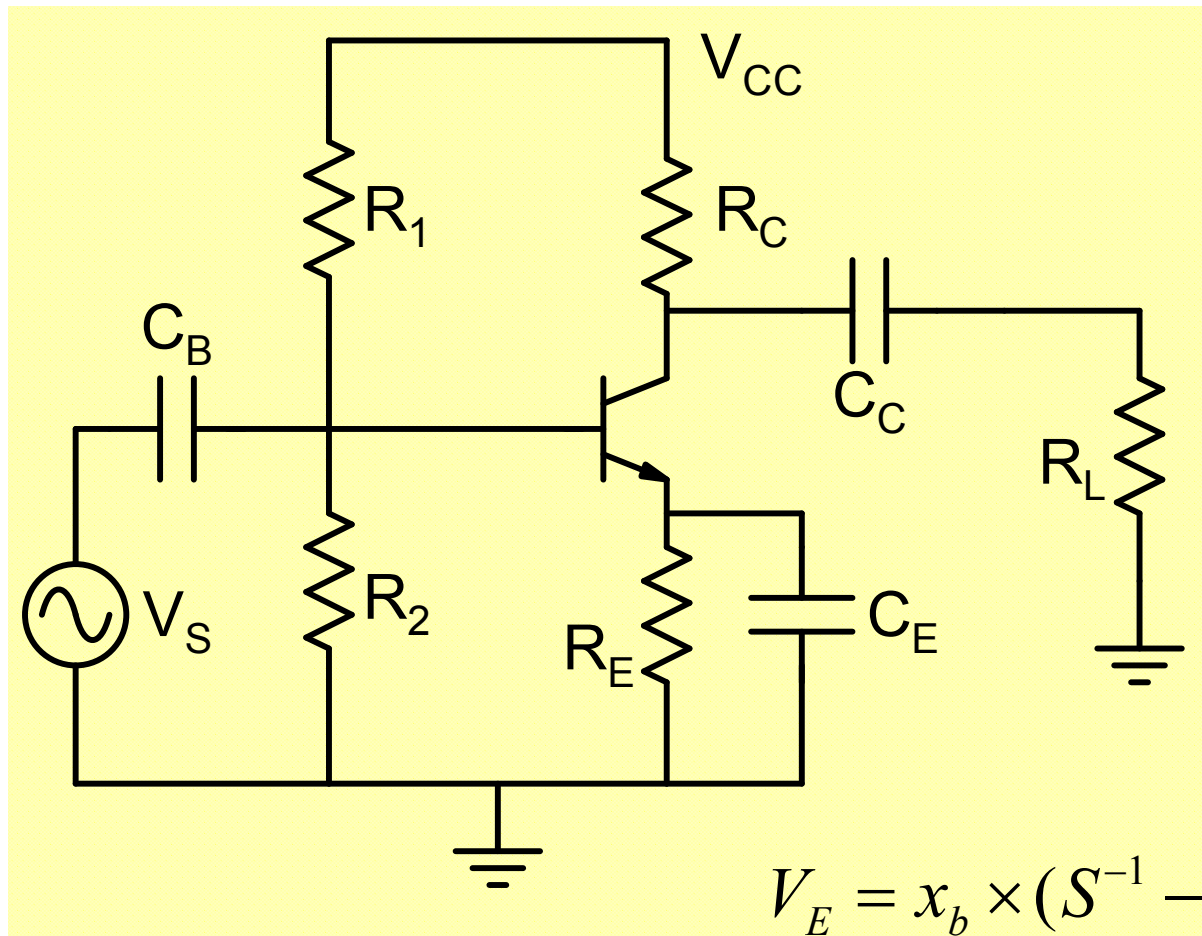Problem-2: Is there a way of eliminating R_B ?





$$R_{in} = r_{\pi} \parallel R_B$$
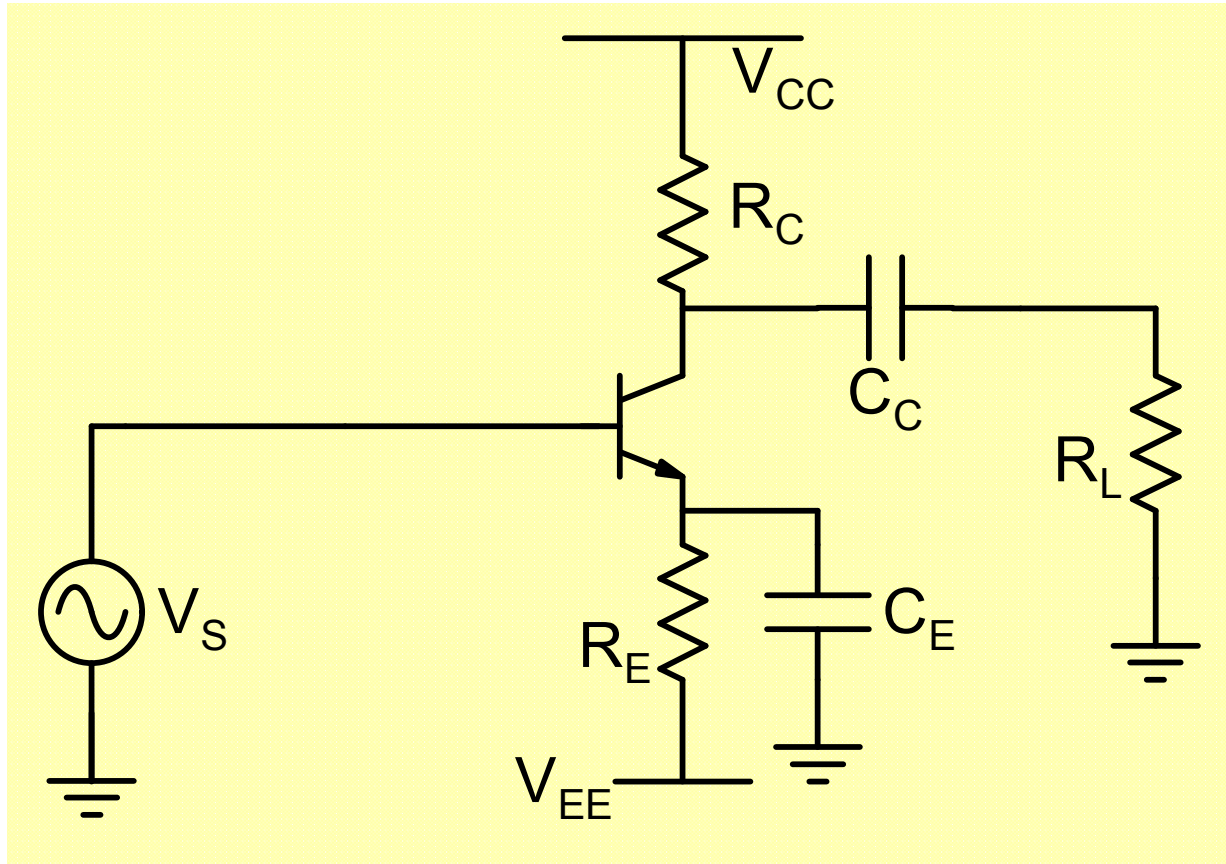
$$S = \frac{\Delta I_{CQ} / I_{CQ}}{\Delta \beta / \beta} = \frac{1}{1 + \frac{\beta R_E}{R_B}}; \quad x_b = \frac{R_B}{r_{\pi}}$$




But requires a separate negative power supply !

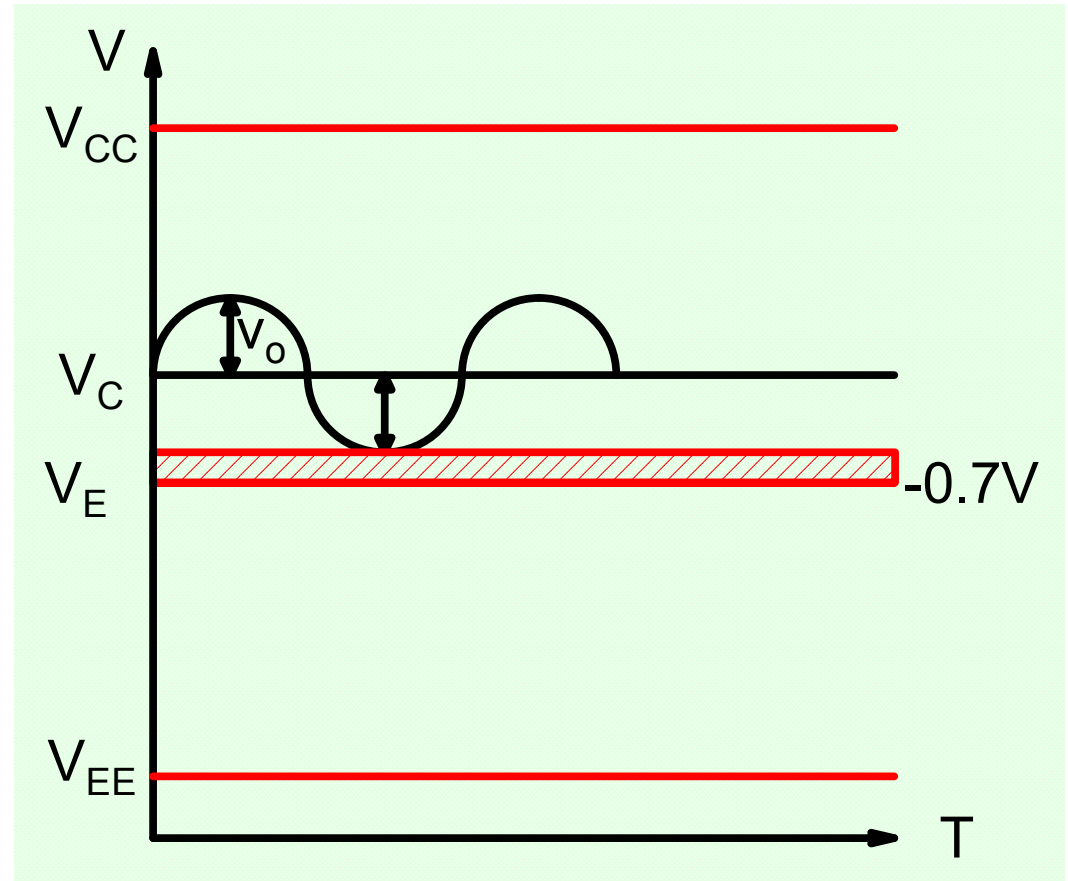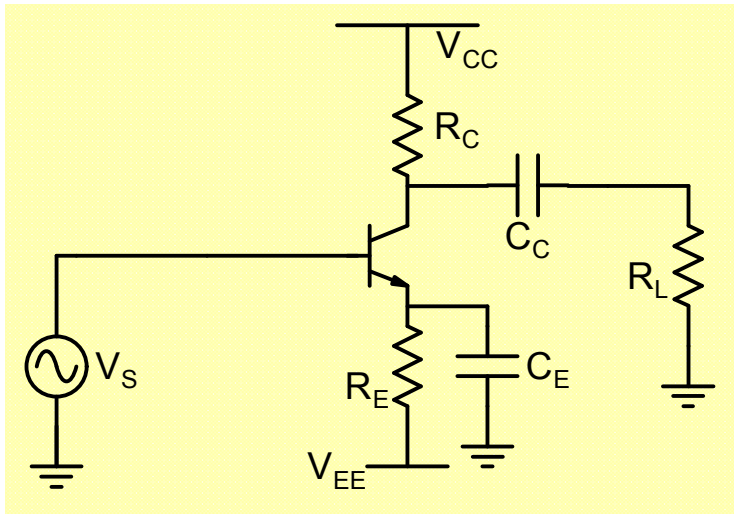
Voltage swing in the negative direction is far from negative supply rail



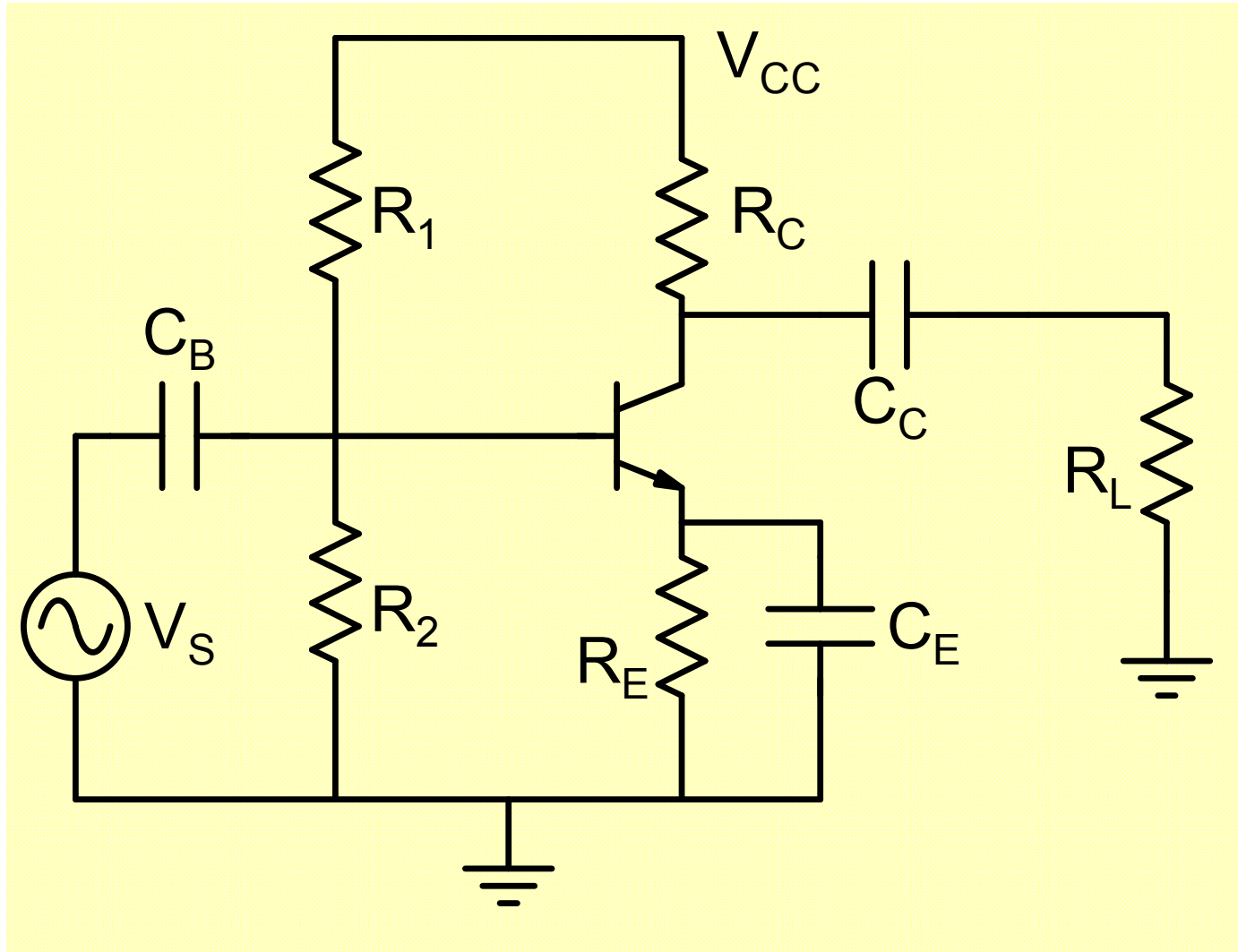Problem-3 : Is there a way of biasing without use of coupling capacitors?



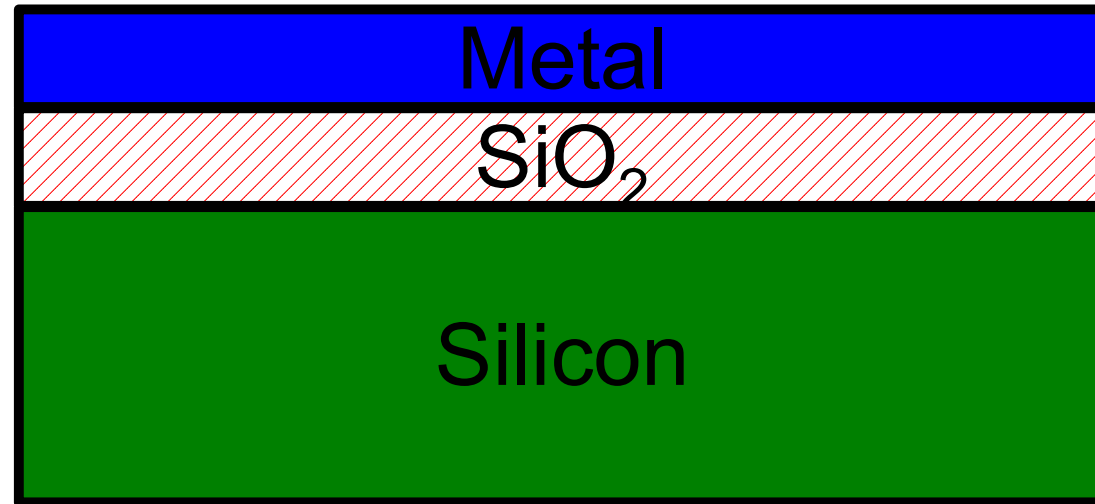Making large capacitors (μF) on chip is impossible !




$$C = \frac{\epsilon_{ox}}{t_{ox}} \times Area$$


$$\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-14} \text{ F / cm} ; t_{ox} = 20 \text{ nm}$$

$$Area = 57 \text{ cm}^2 !! \text{ for } 10 \mu\text{F capacitor}$$

One can only make capacitors of the order of a few picofarads on chip

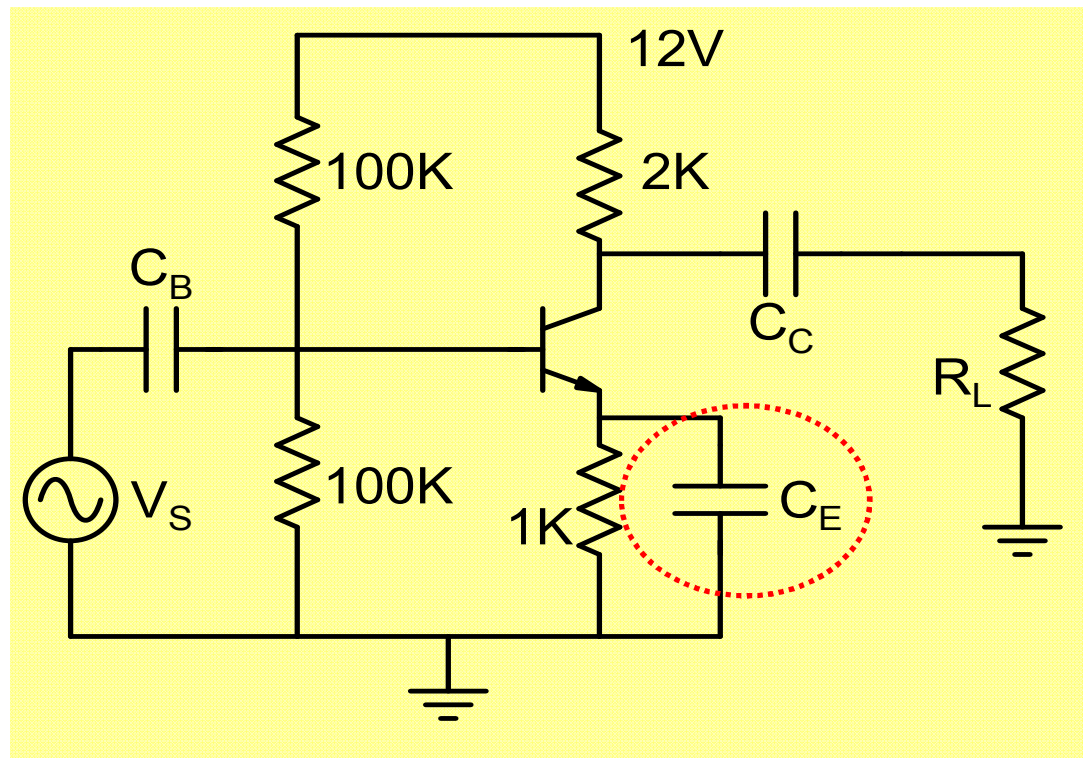
This would lead to an unacceptably large lower cutoff frequency




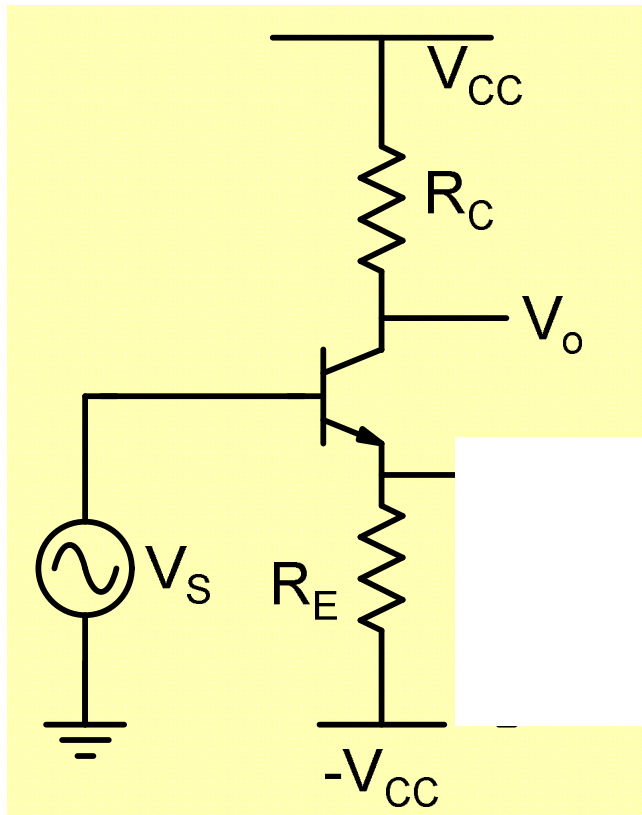


$$|A_V| = \frac{g_m R_C}{1 + g_m R_E} \sim \frac{R_C}{R_E}$$
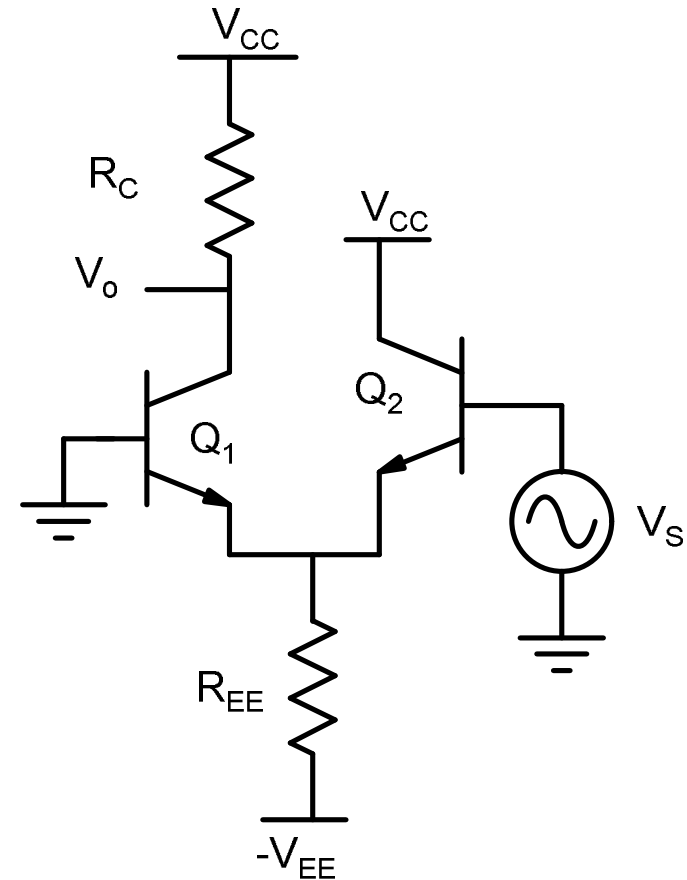
$$\sim \frac{I_{CQ} R_C}{I_{CQ} R_E} \sim 1$$




$$|A_V| = 0.5 g_m R_C$$

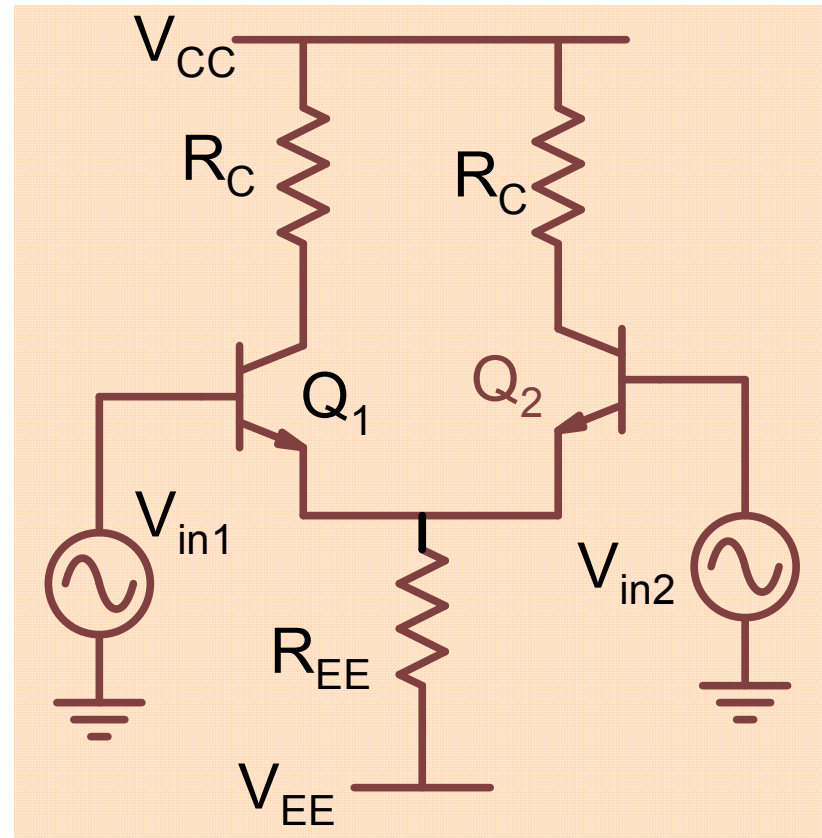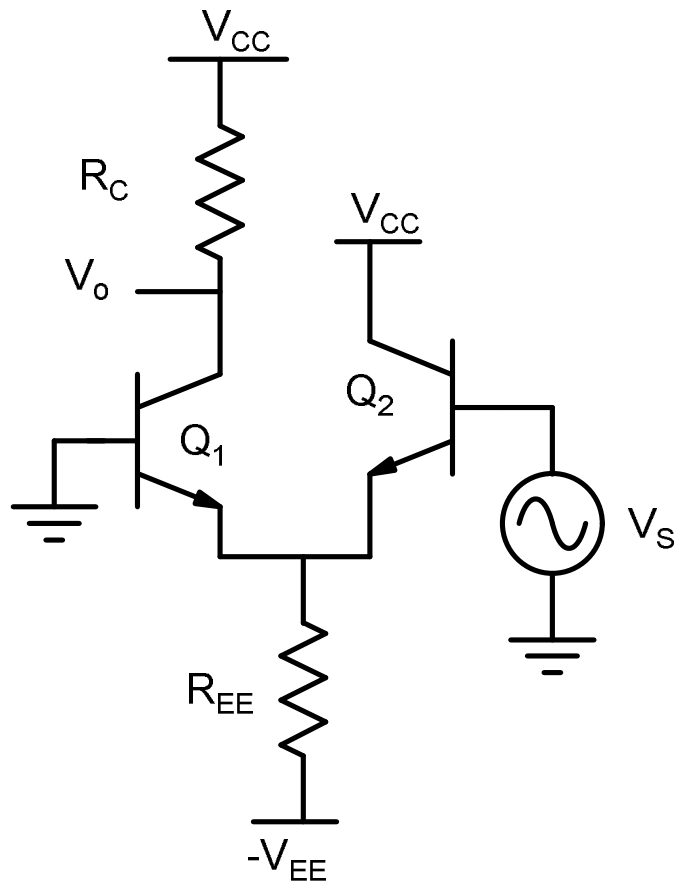


Differential amplifier

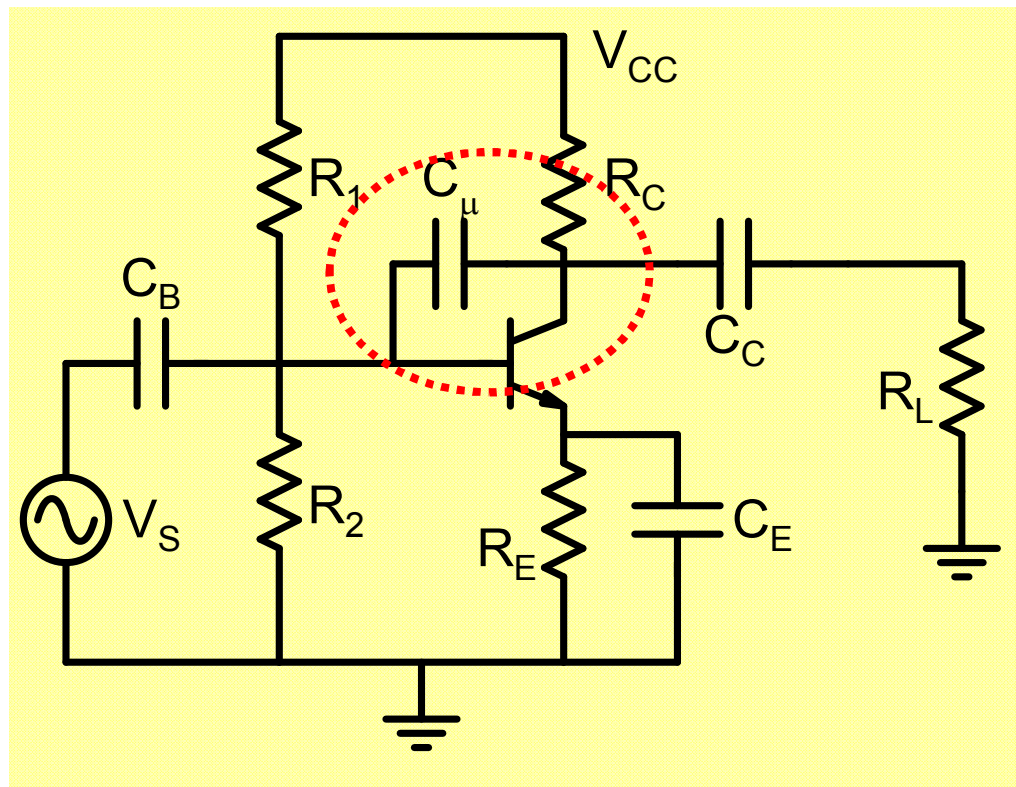Problem-4: Can one get rid of Miller's capacitance which reduces bandwidth at high gain

$$\omega_H \cong \frac{1}{(R'_S \parallel r_\pi) \{C_\pi + C_\mu(1 + g_m R'_C)\} + R'_C C_\mu}$$




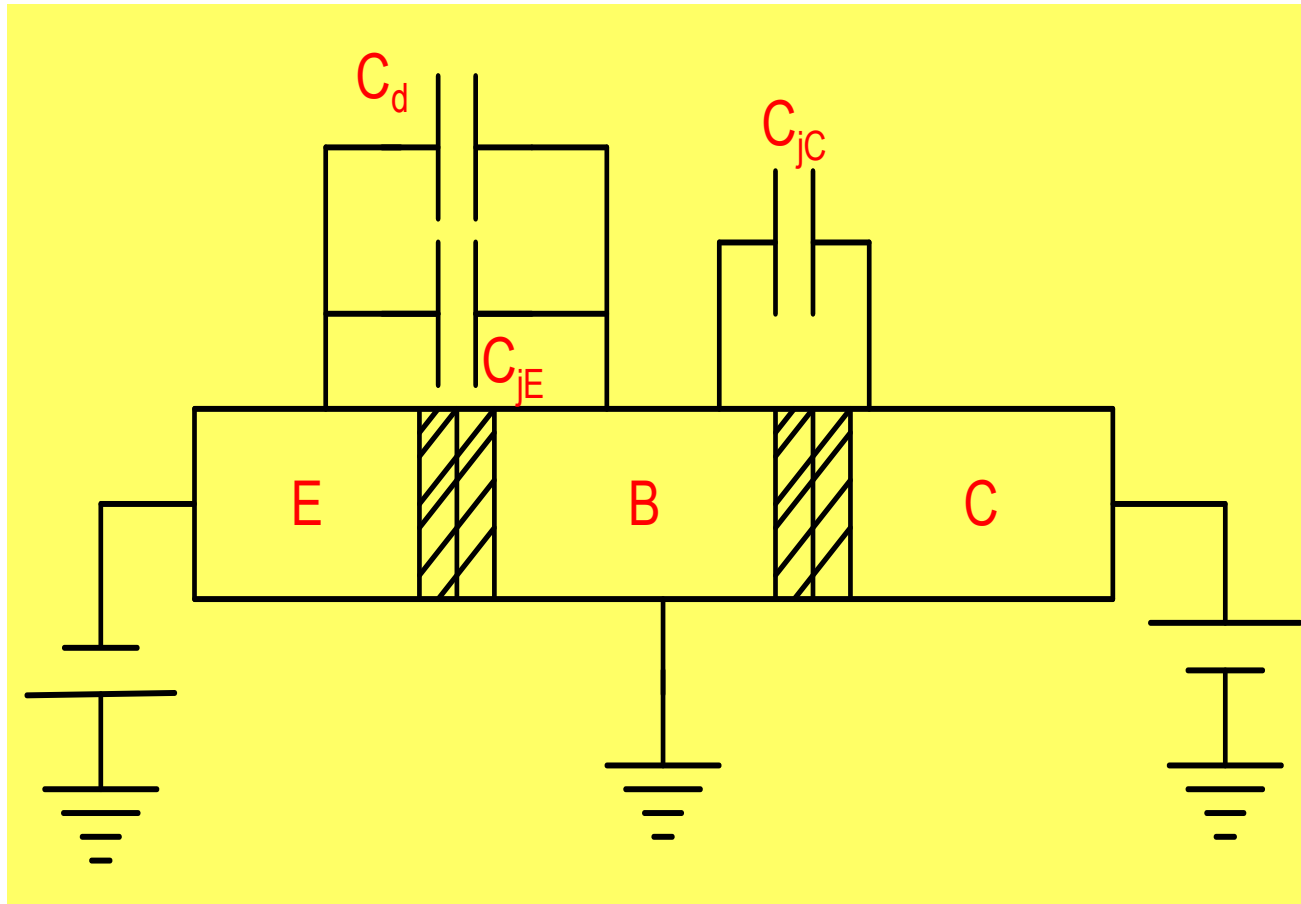Look for an amplifier circuit in which there is no capacitance between input and output ports




Note that there is no capacitance between emitter and collector

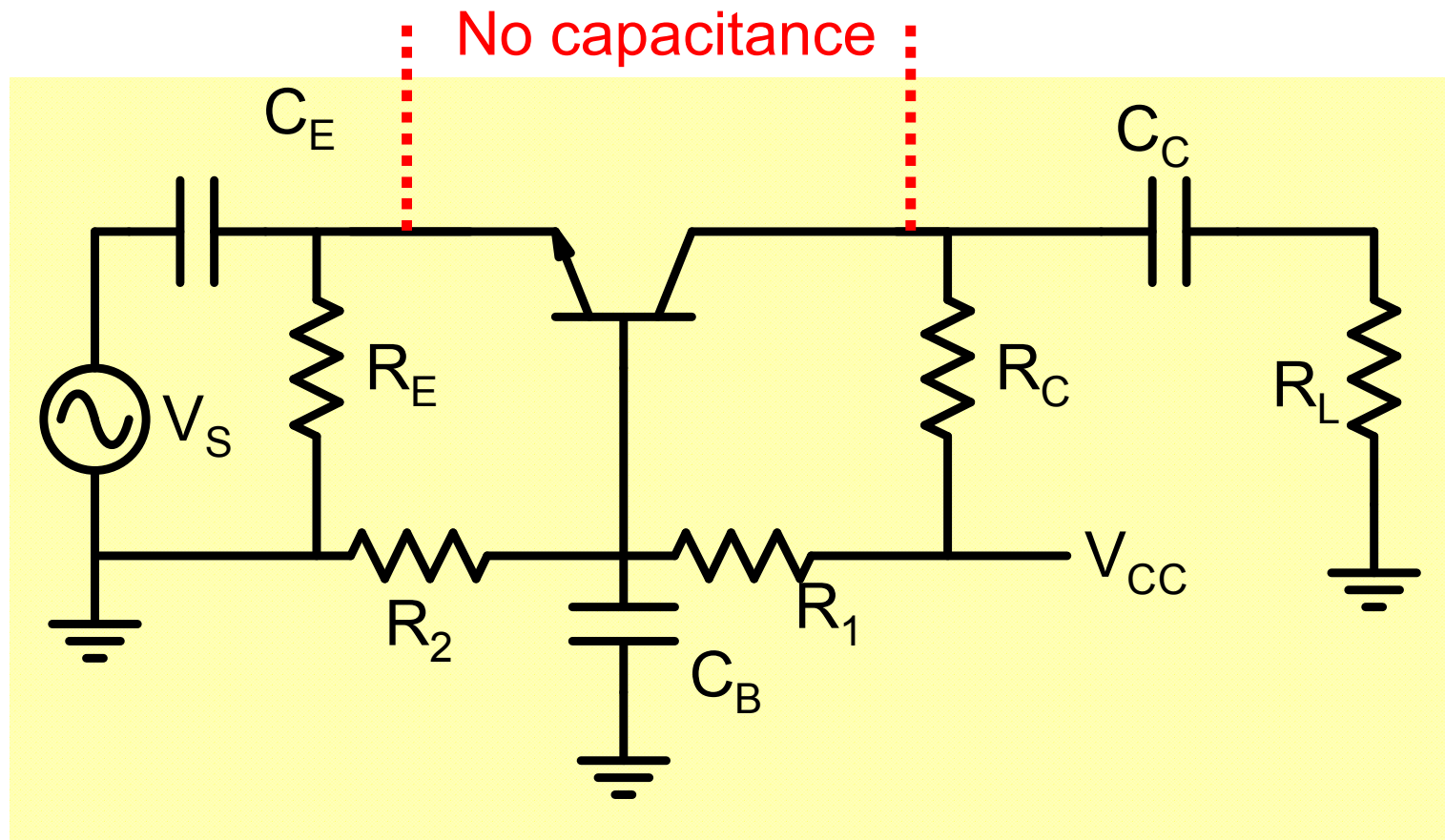Natural solution is a Common Base (CB) Amplifier



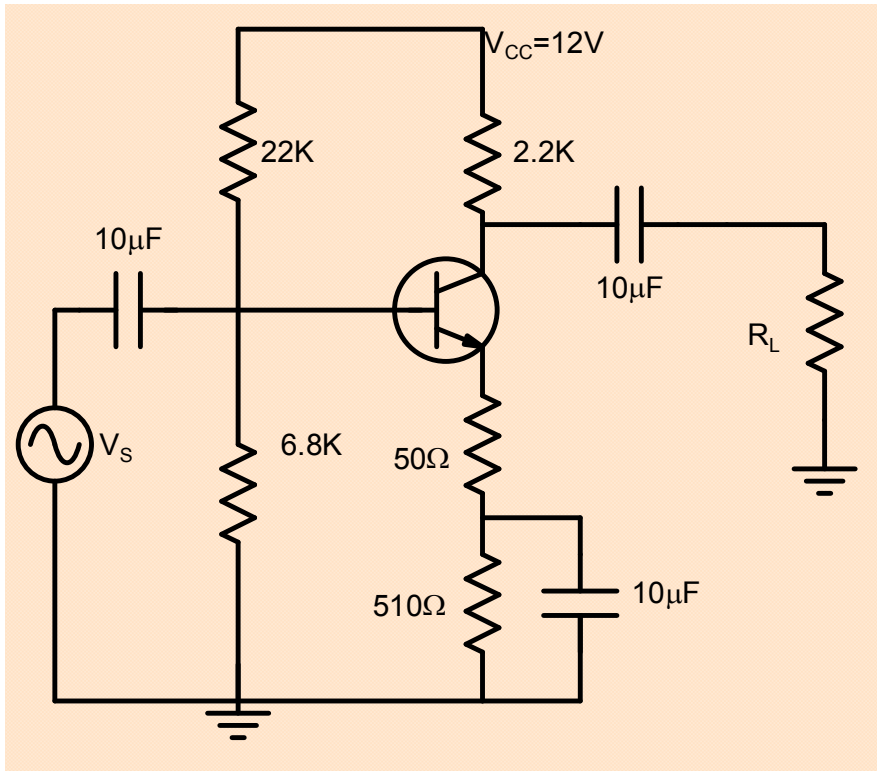Problem-5: Driving low impedance loads is a problem !



$$A_V = I_{CQ} R_C \parallel R_L$$

$$R_L = 2.2k; I_{CQ} = 3.4mA; P_{sup ply} = 46mW$$

$$A_V = 18.2; R_{in} = 2.76K; R_O = 2.2K$$

$$v_{om} = 2V @ THD = 1.8\%;$$

$$P_{Lmax} = \frac{v_{om}^2}{2R_L} = 0.9mW$$

$$\eta = \frac{P_L}{P_{sup ply}} \times 100 \sim 2\%$$


$$f_L = 0.3kHz$$

$$R_L = 22\Omega$$

$$A_V = 0.36; R_{in} = 2.76K; R_O = 2.2K$$

$$v_{om} \sim 40mV @ THD = 1.8\%$$

$$f_L = 0.3kHz$$

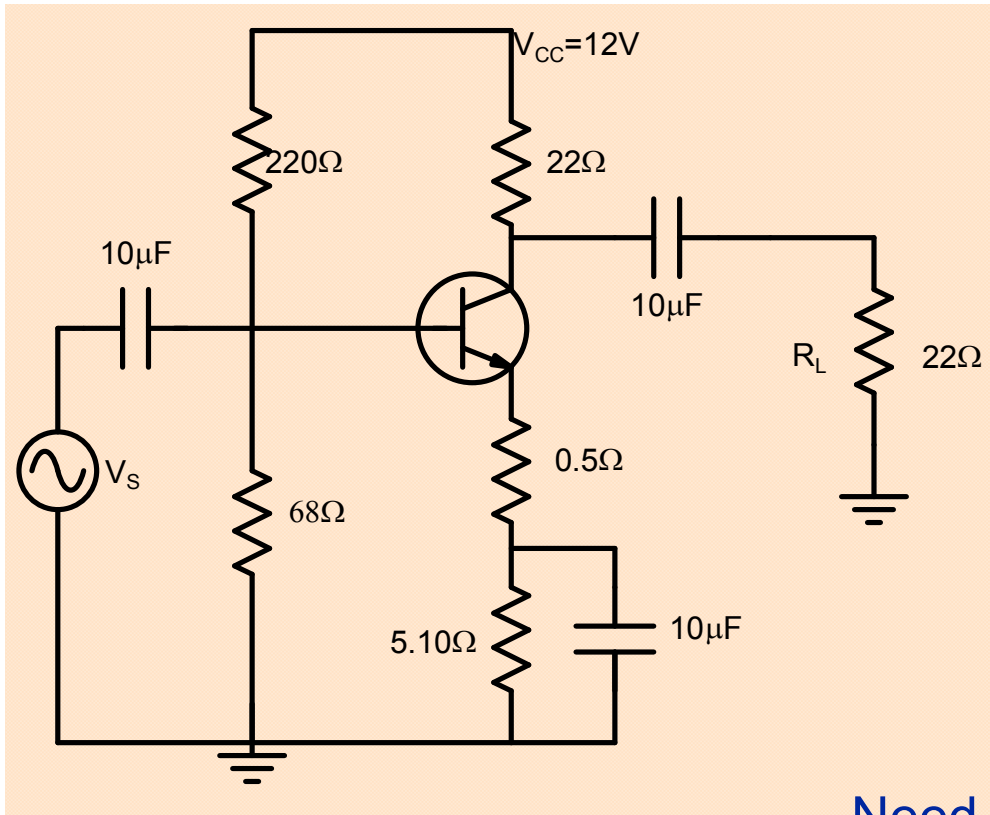

$$R_L = 22\Omega; I_{CQ} = 247mA; P_{\text{supply}} = 3.47W$$


$$A_V = 4.2; R_{in} = 43\Omega; R_O = 22\Omega$$

$$v_{om} \sim 2.6V @ THD = 1.8\%$$

$$P_{L\text{max}} = \frac{v_{om}^2}{2R_L} = 0.15W$$

$$f_L = 8.3kHz$$

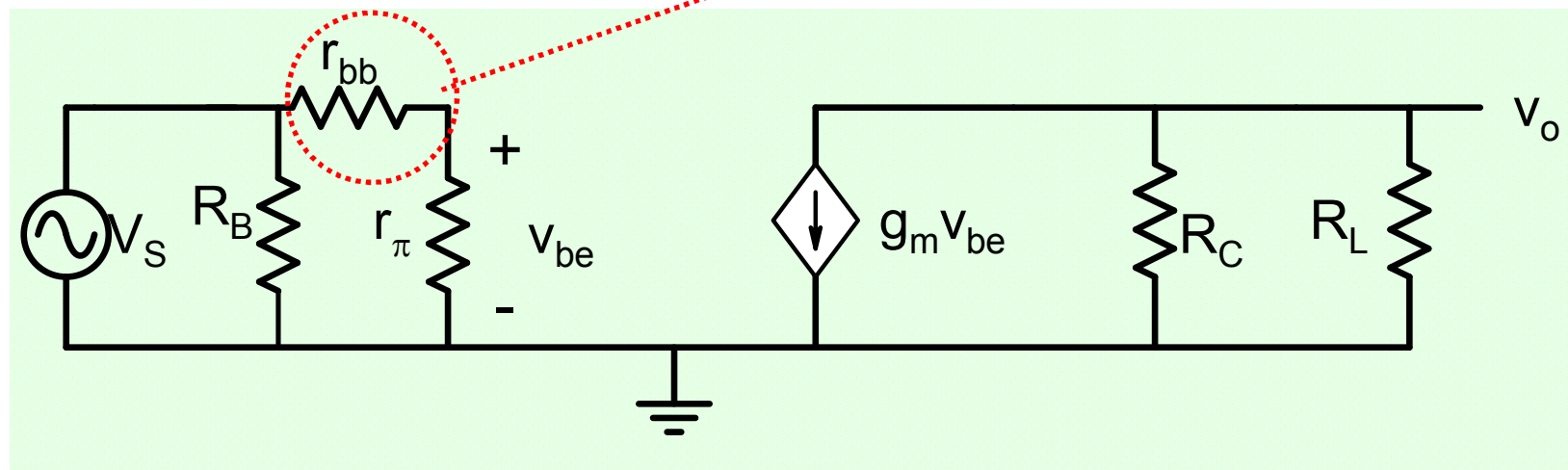
Need a transistor with lower base resistance




CE amplifier has great difficulty driving low load resistances

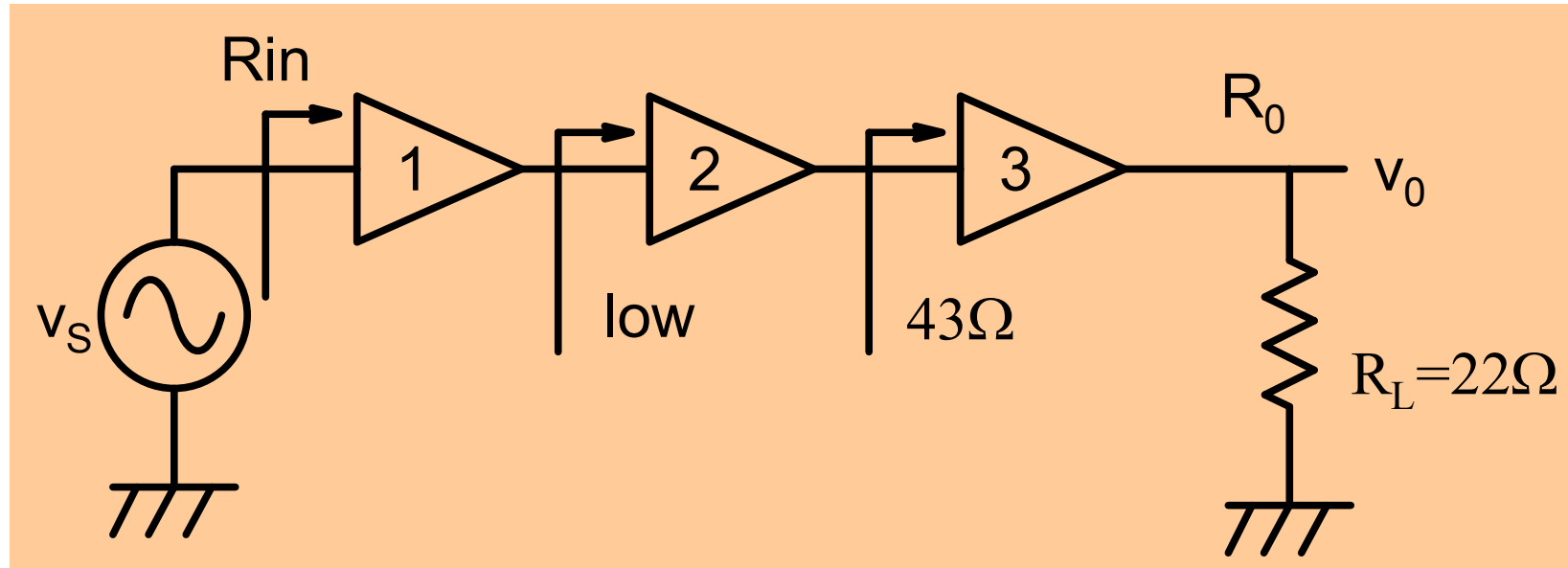
1. High current requirement
2. Very inefficient

The stages driving the output stage suffer also





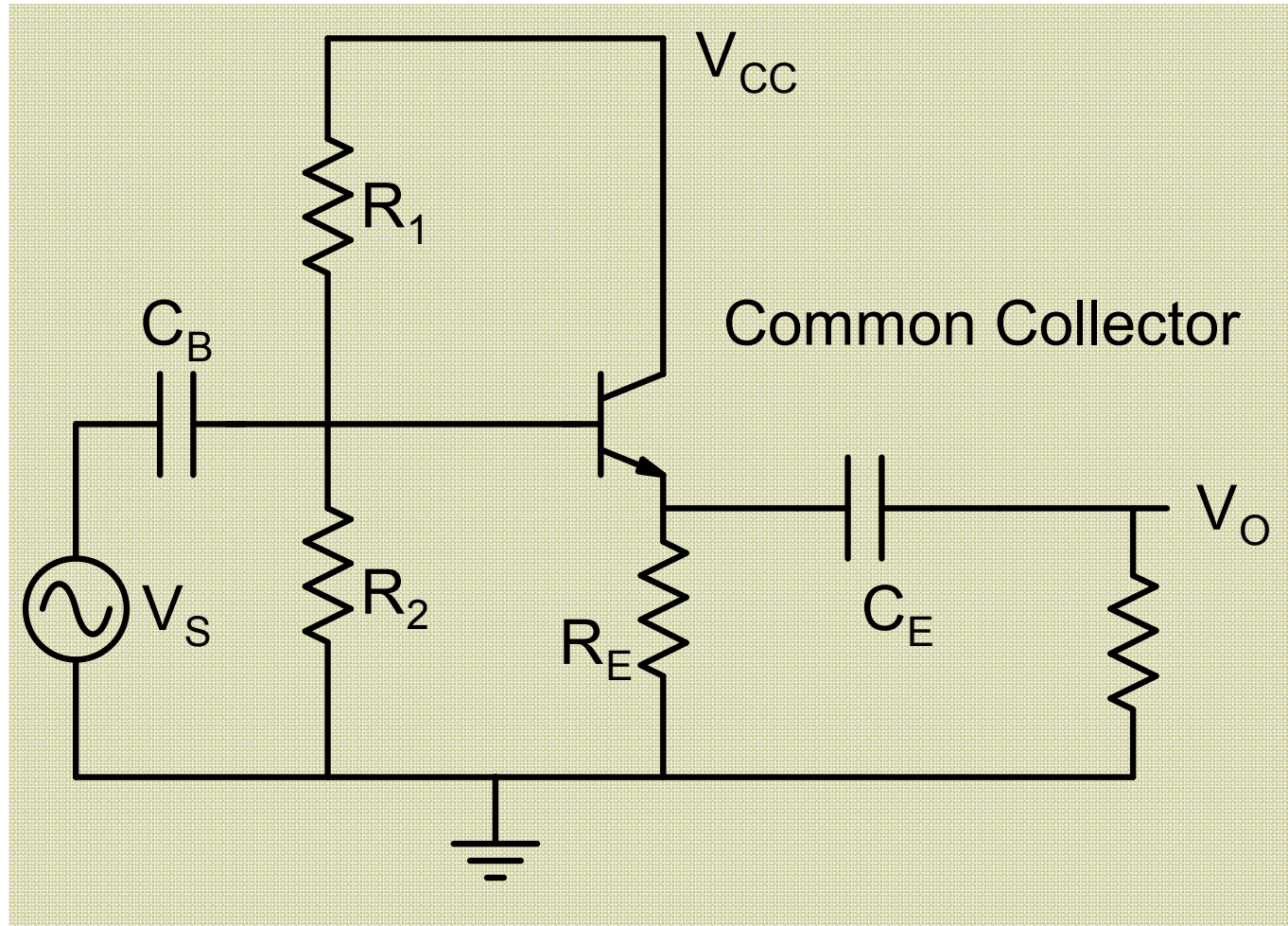Challenge: How can we drive low impedance loads without requiring excessive bias current leading to high power dissipation - and despite large current, obtain high input resistance



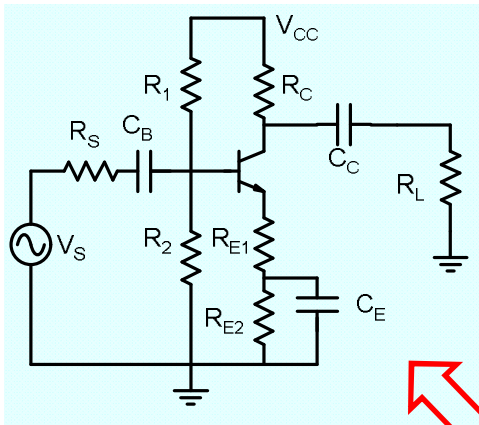

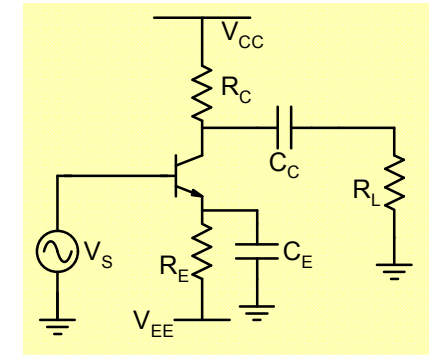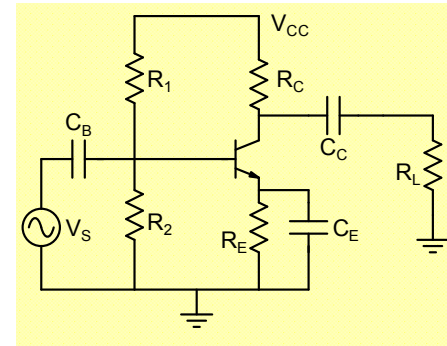Linearity
Input resistance
Higher input voltage



Better β Stability

