


EE210: Microelectronics-I

Lecture-7 : PN Junction Diode-3

Instructor: Y. S. Chauhan

Slides from: B. Mazhari
Dept. of EE, IIT Kanpur

Diode Model: Forward Bias

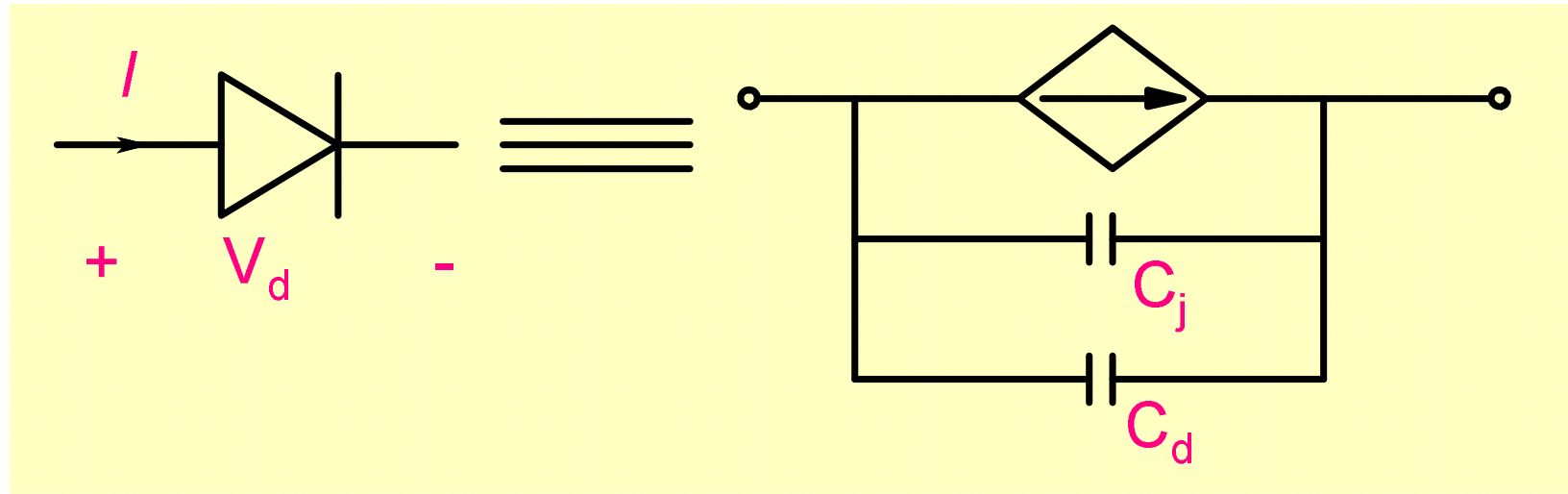

$$I = I_s \times \left(\exp\left(\frac{V_d}{n V_T}\right) - 1 \right)$$

$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_d}{V_{bi}}\right)^m}$$

$$C_d = \frac{I_F}{V_T} \cdot \tau$$

No. of parameters: 3+3+1

Temperature dependence of diode characteristics

$$I_D = I_S \times \left\{ \exp\left(\frac{V_d}{V_T}\right) - 1 \right\}$$

$$V_T = \frac{kT}{q}$$

$$I_S \propto n_i^2 \propto e^{-\frac{E_g}{kT}}$$

Reverse saturation current increases with temperature. For forward bias, even though V_T increases, current still increases because of greater influence of I_S


For a diode in forward bias at a fixed current I_O : $V_D = V_T \times \ln(I_O/I_S + 1)$

For Silicon diodes, V_D decreases at the rate of $\sim -2\text{mV}/^\circ\text{C}$

If the diode voltage is 0.7 at 27°C , then at 100°C it would be only :

$$0.7 - 2 \times 10^{-3} \times (100 - 27) = 0.554\text{V}$$

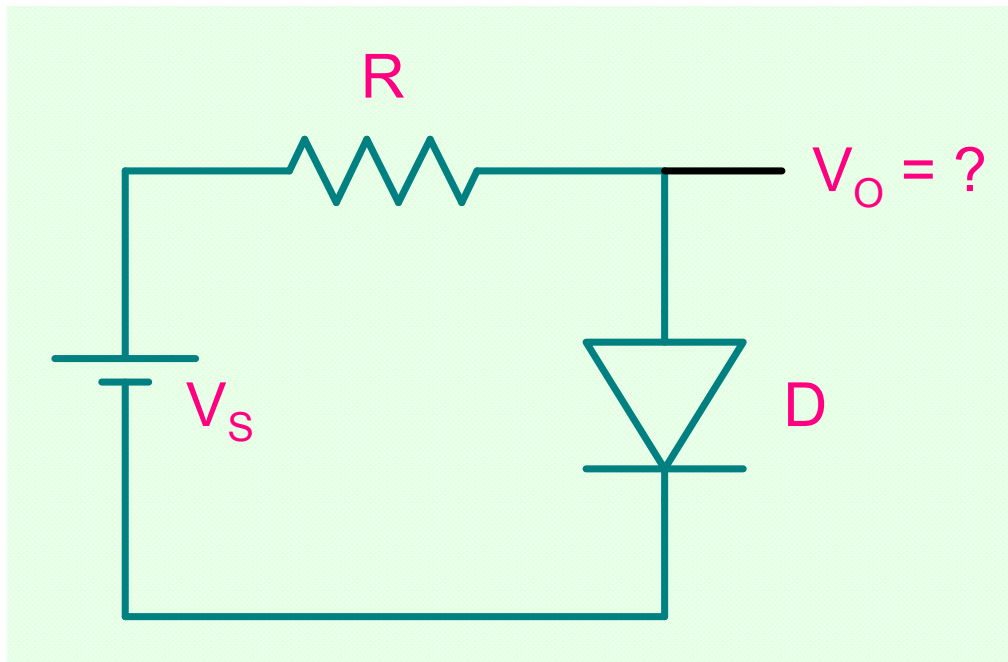Analysis using non-linear diode model is not easy



$$V_S = I \times R + V_O \quad (1)$$

$$I = I_S \times \left(\exp\left(\frac{V_O}{nV_T}\right) - 1 \right) \quad (2)$$

$$\Rightarrow V_O = nV_T \times \ln\left(\frac{I}{I_S} + 1\right) \quad (3)$$

$$\Rightarrow V_S = I \times R + nV_T \times \ln\left(\frac{I}{I_S} + 1\right) \quad (4)$$

Iterative Method:

$$V_S = I \times R + V_O \quad (1)$$

$$I = I_S \times \left\{ \exp\left(\frac{V_O}{n V_T}\right) - 1 \right\} \quad (2)$$

Assume

$$V_O = 0.6\text{V}$$

Calculate


$$I = \frac{V_S - V_O}{R}$$


Re-calculate

$$V_O = n V_T \times \ln(I/I_S + 1)$$

Convergence:

$$\frac{\Delta I}{I} \leq \varepsilon$$

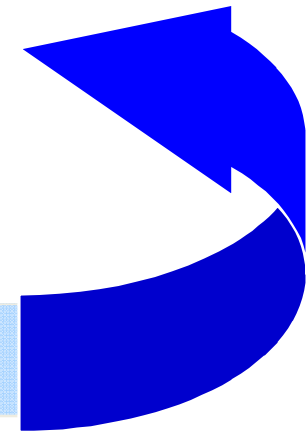

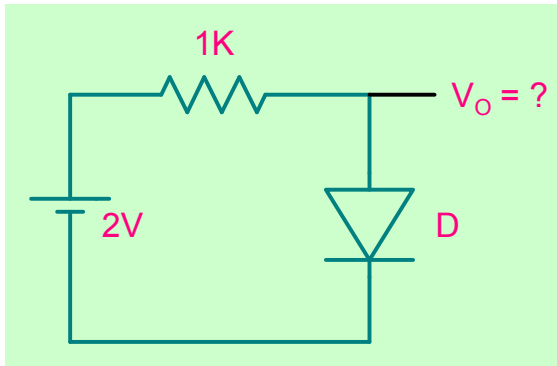

$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$

$$I_S = 2 \times 10^{-15} \text{ A}$$

$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$

Assume V_O

$$V_O = 0.5$$

$$V_O = 0.711$$

$$V_O = 0.707$$

$$I = \frac{V_S - V_O}{R}$$

$$I = 1.5 \times 10^{-3}$$

$$I = 1.289 \times 10^{-3}$$

$$I = 1.293 \times 10^{-3}$$


$$V_O = nV_T \times \ln(I/I_S + 1)$$

$$V_O = 0.711$$

$$V_O = 0.707$$

$$V_O = 0.707$$

CONVERGENCE

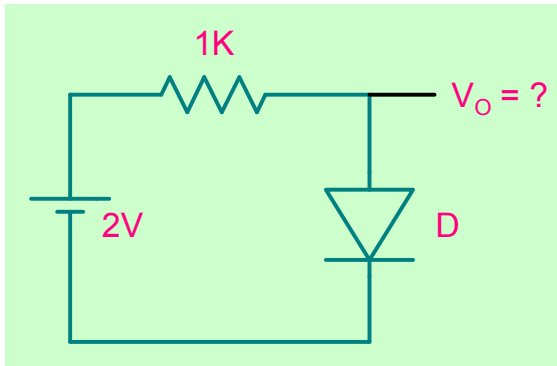

$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$

$$I_S = 2 \times 10^{-15} \text{ A}$$

$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$

Assume V_O

$$V_O = 1.0$$

$$V_O = 0.7$$

$$V_O = 0.707$$

$$I = \frac{V_S - V_O}{R}$$

$$I = 1.0 \times 10^{-3}$$

$$I = 1.3 \times 10^{-3}$$

$$I = 1.293 \times 10^{-3}$$

$$V_O = nV_T \times \ln(I/I_S + 1)$$



$$V_O = 0.7$$

$$V_O = 0.707$$

$$V_O = 0.707$$

CONVERGENCE to the same Result


Graphical Method: Method of Load Line

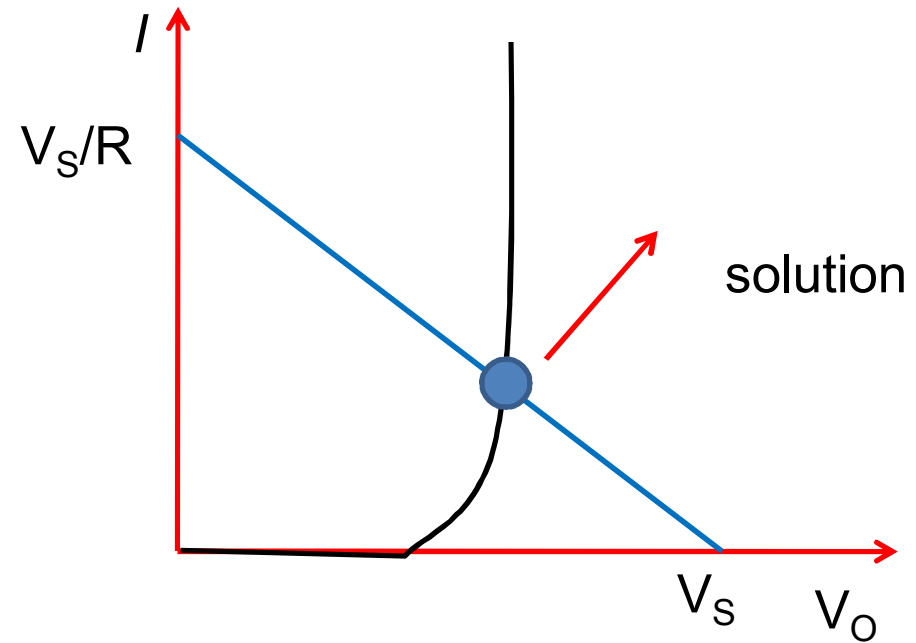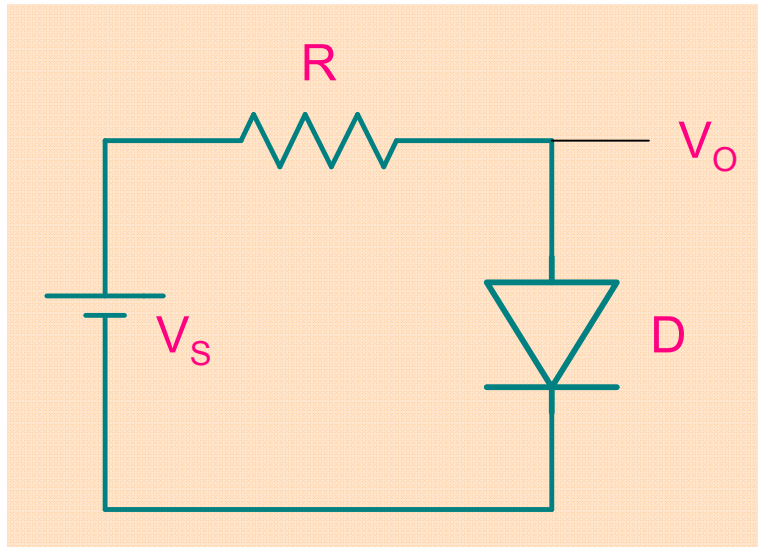

$$V_s = I \times R + V_o$$

$$I = I_s \times \left\{ \exp\left(\frac{V_o}{n V_T}\right) - 1 \right\}$$

$$I = \frac{V_s - V_o}{R}$$

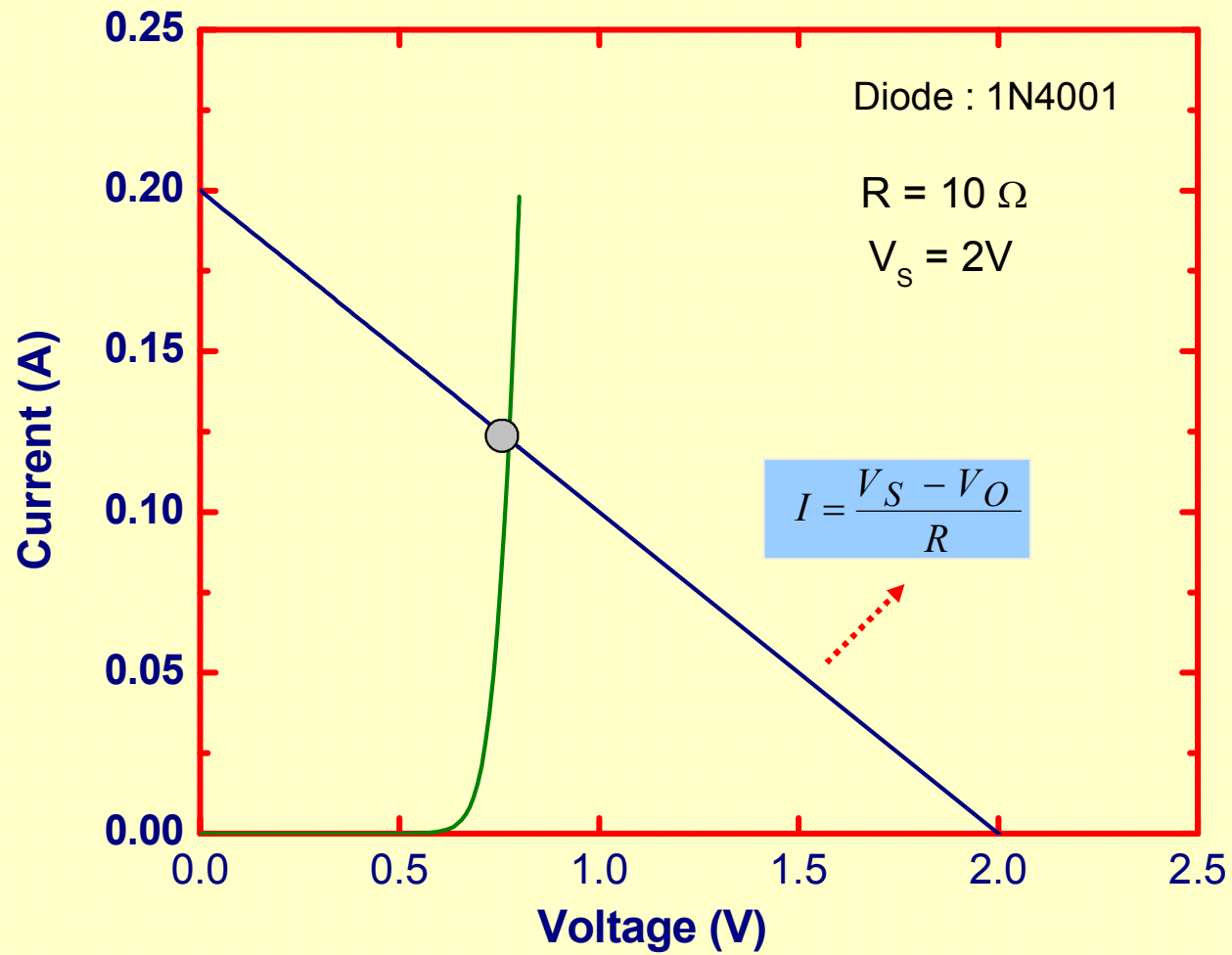



$$V_O = 0.77V; I = 0.12A$$

For “hand analysis” of circuits, we need simpler models!

- Analysis using a **non-linear** diode model is relatively difficult and time consuming.
- It also does not give a symbolic expression that can provide insight and help in the design of the circuit.

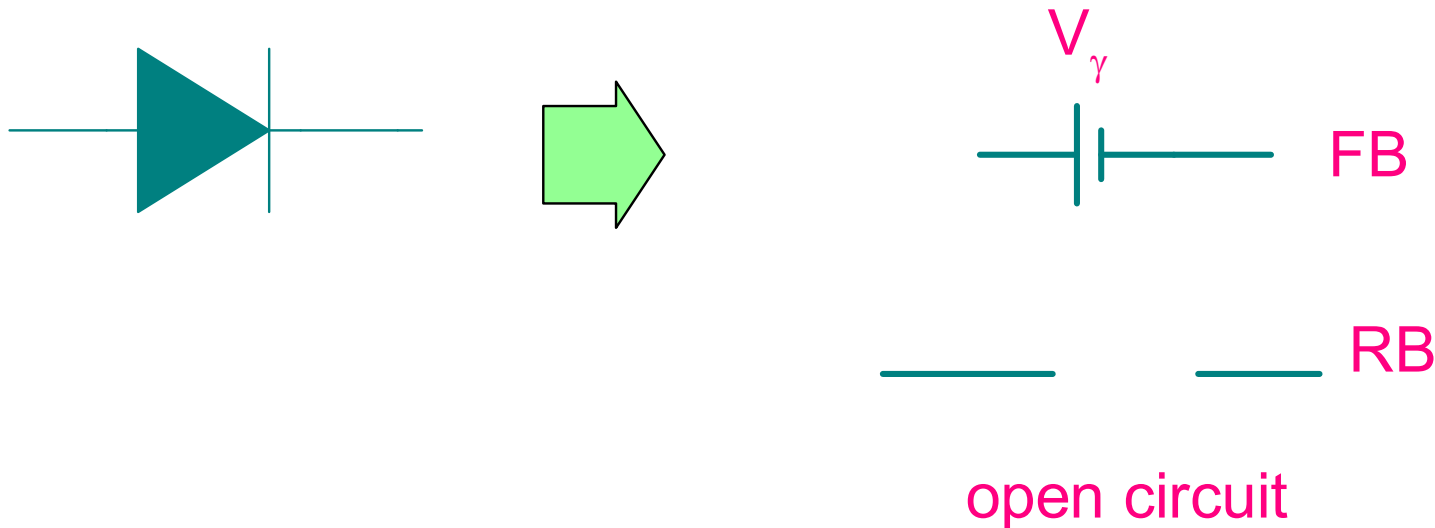Need **SIMPLER** and **LINEAR** Device Models




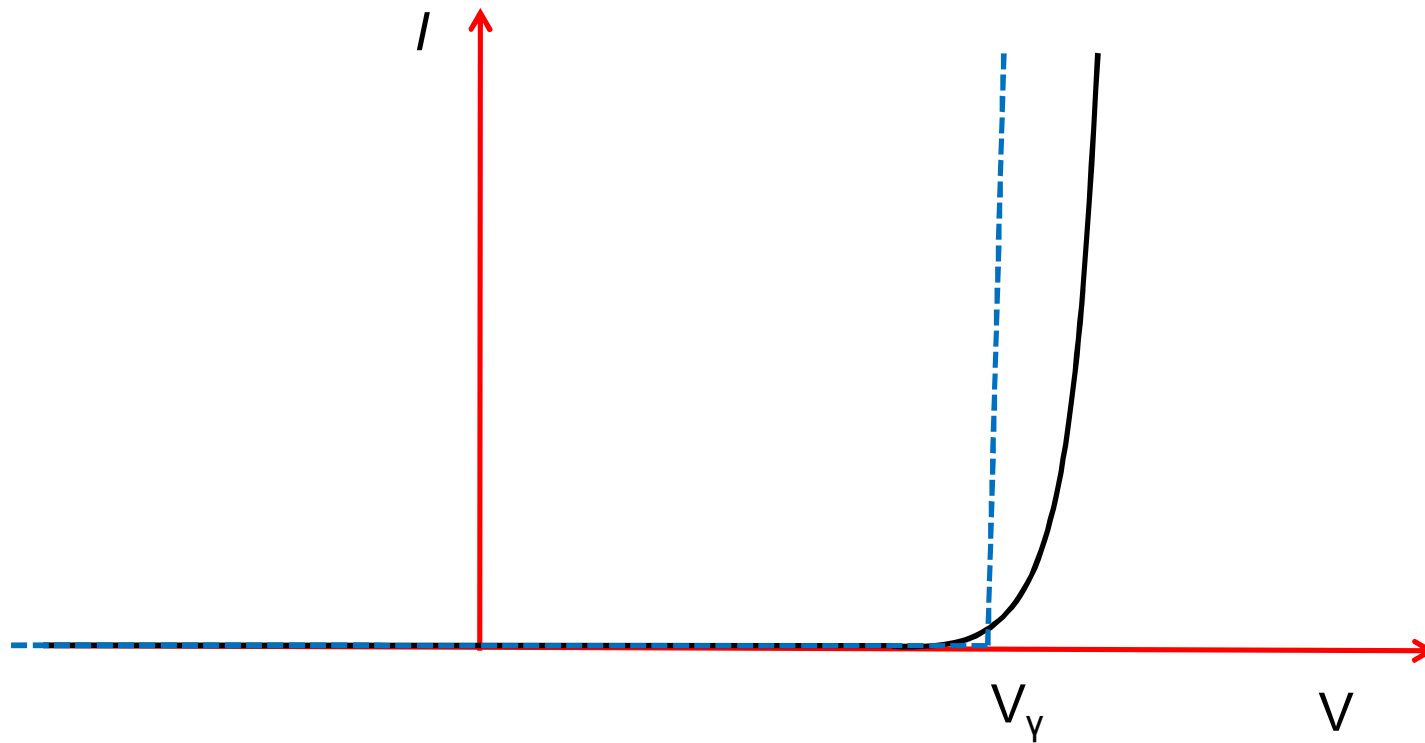

Cut-in Voltage: V_γ

$\sim 0.6-0.7V$

Second Edition

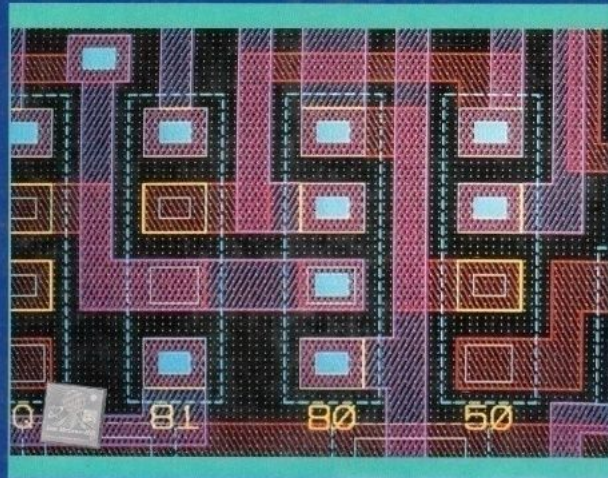MICROELECTRONICSJacob Millman
Arvin GrabelTATA MCGRAW-HILL EDITION
FOR SALE IN INDIA ONLY

currents; for specified carrier densities, an increase in the area results in an increase in the current capacity of the junction.

Examination of Eq. (2-3) indicates that for forward bias, and for V_D several times V_T which makes $e^{V_D/\eta V_T} \gg 1$, I_D varies exponentially with applied voltage. For this case, Eq. (2-3) can be approximated by

$$I_D = I_S e^{V_D/\eta V_T} \quad \text{A} \quad (2-5)$$

This result is expected as a decrease in the potential barrier permits carriers to diffuse more readily across the junction. Similarly, I_D is negative with magnitude I_S for reverse bias when V_D has a magnitude which is several times V_T . Both the negative sign, indicating current from n to p , and the constant current value for reverse bias are consistent with the discussion in Sec. 2-2.


Often, because forward and reverse currents differ by several orders of magnitude, two different current scales are used to display the junction characteristic as in Fig. 2-4b. The dashed portion of the reverse-biased characteristic (note the broken scale) indicates that at a voltage $-V_Z$ the junction exhibits an abrupt departure from Eq. (2-3). At this voltage a large reverse current may exist and the junction is in its *breakdown* region. This phenomenon is discussed in Sec. 2-11.

The forward characteristic of the 1N4153, a fast-switching silicon diode, is depicted in Fig. 2-5. A noteworthy feature of this characteristic is the existence of a *cut-in*, *offset*, or *turn-on* voltage V_γ below which the current is small (less than 1 percent of rated current). From Fig. 2-5, V_γ is approximately 0.6 V; beyond V_γ , the current increases rapidly. The significance of the offset voltage is that the diode characteristic can be approximated as having negligible current for applied voltages less than V_γ .



The parameter η can be determined from the exponential nature of the volt-ampere characteristic. From Eq. (2-5), we have

$$\log I_D = \log I_S + \frac{0.43 V_D}{\eta V_T} \quad (2-6)$$

FIGURE 2-5
The forward volt-ampere characteristic of an 1N4153 silicon diode at 25°C.

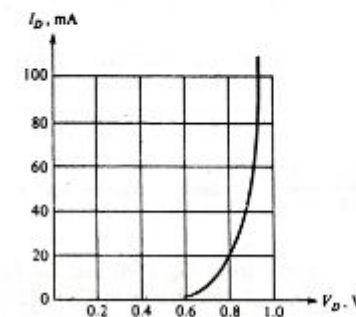

The forward characteristic of the 1N4153, a fast-switching silicon diode, is depicted in Fig. 2-5. A noteworthy feature of this characteristic is the existence of a *cut-in, offset, or turn-on voltage* V_γ below which the current is small (less than 1 percent of rated current). From Fig. 2-5, V_γ is approximately 0.6 V; beyond V_γ , the current increases rapidly. The significance of the offset voltage

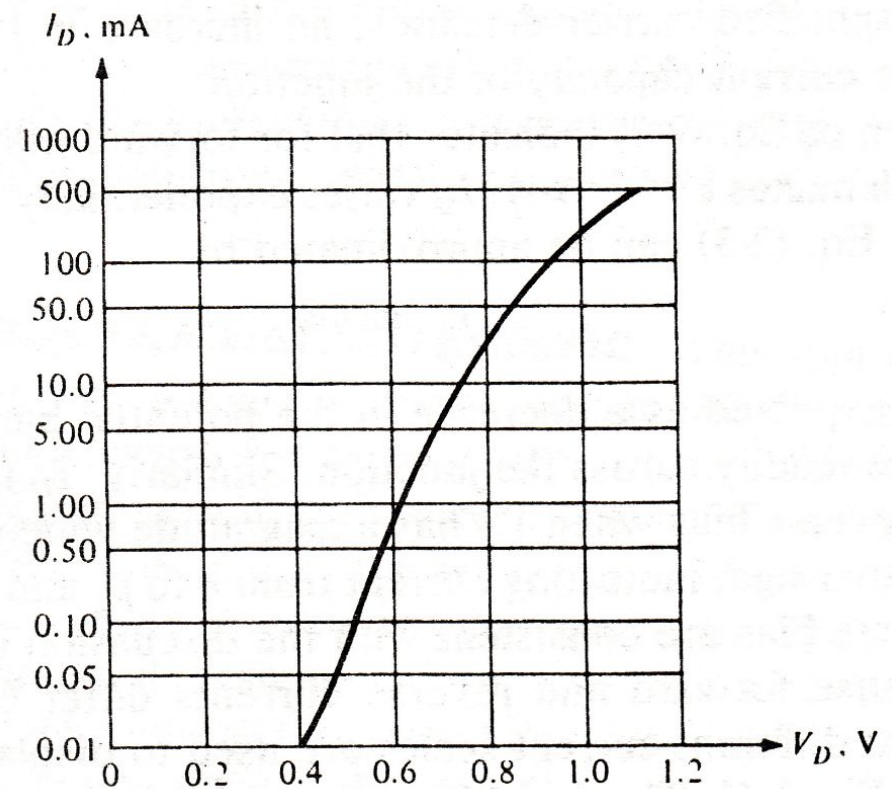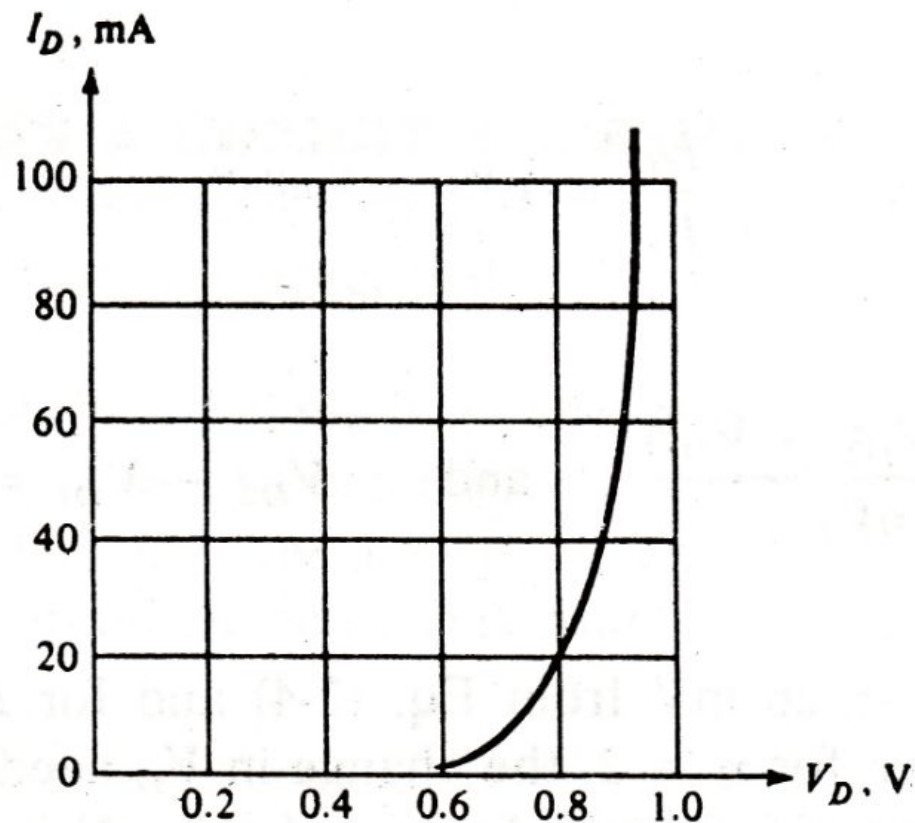




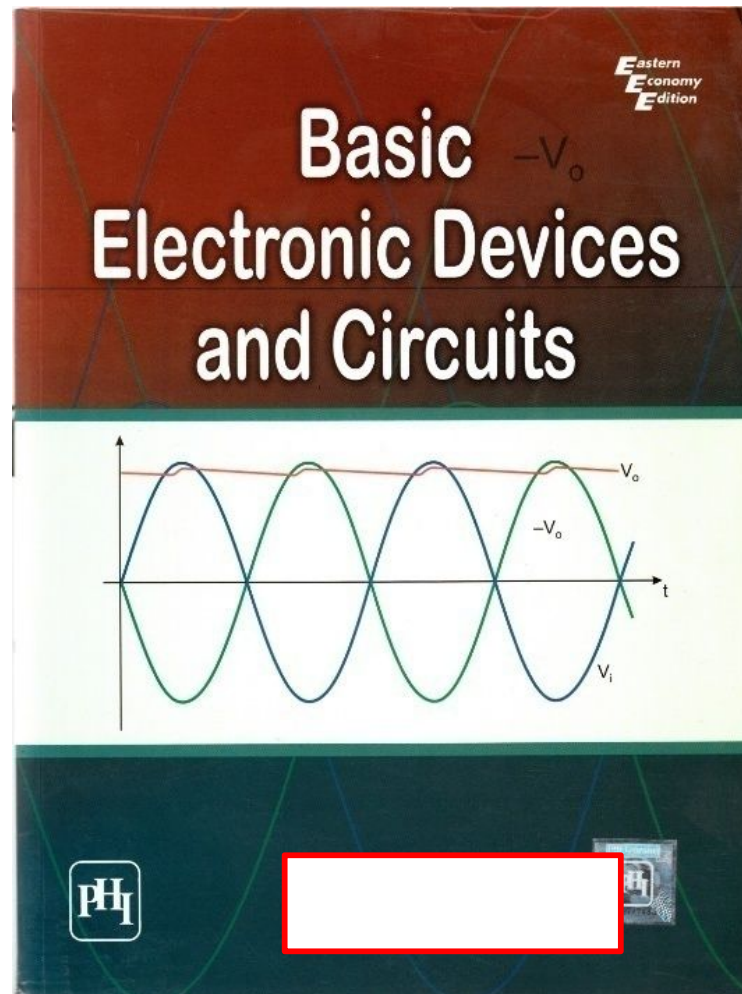
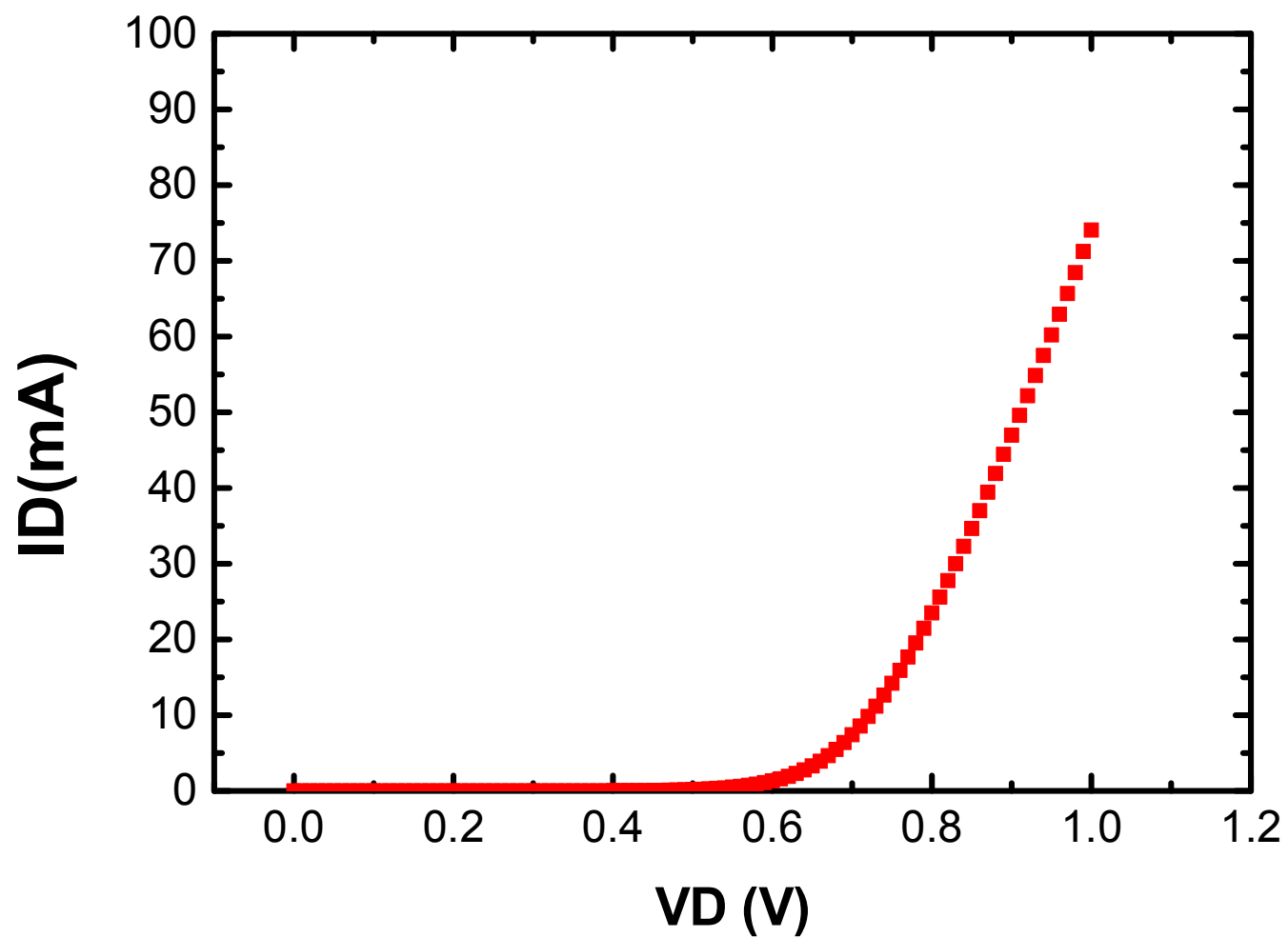



Figure 6.2(a) shows the I - V curve under forward bias as obtained from the Shockley equation. Note that the current is negligibly small up to about 0.6 V and rises sharply beyond that. Under reverse bias, the Shockley equation predicts $I \approx -I_s$ which is negligibly small. However, as we have seen in Chapter 3, a real diode will

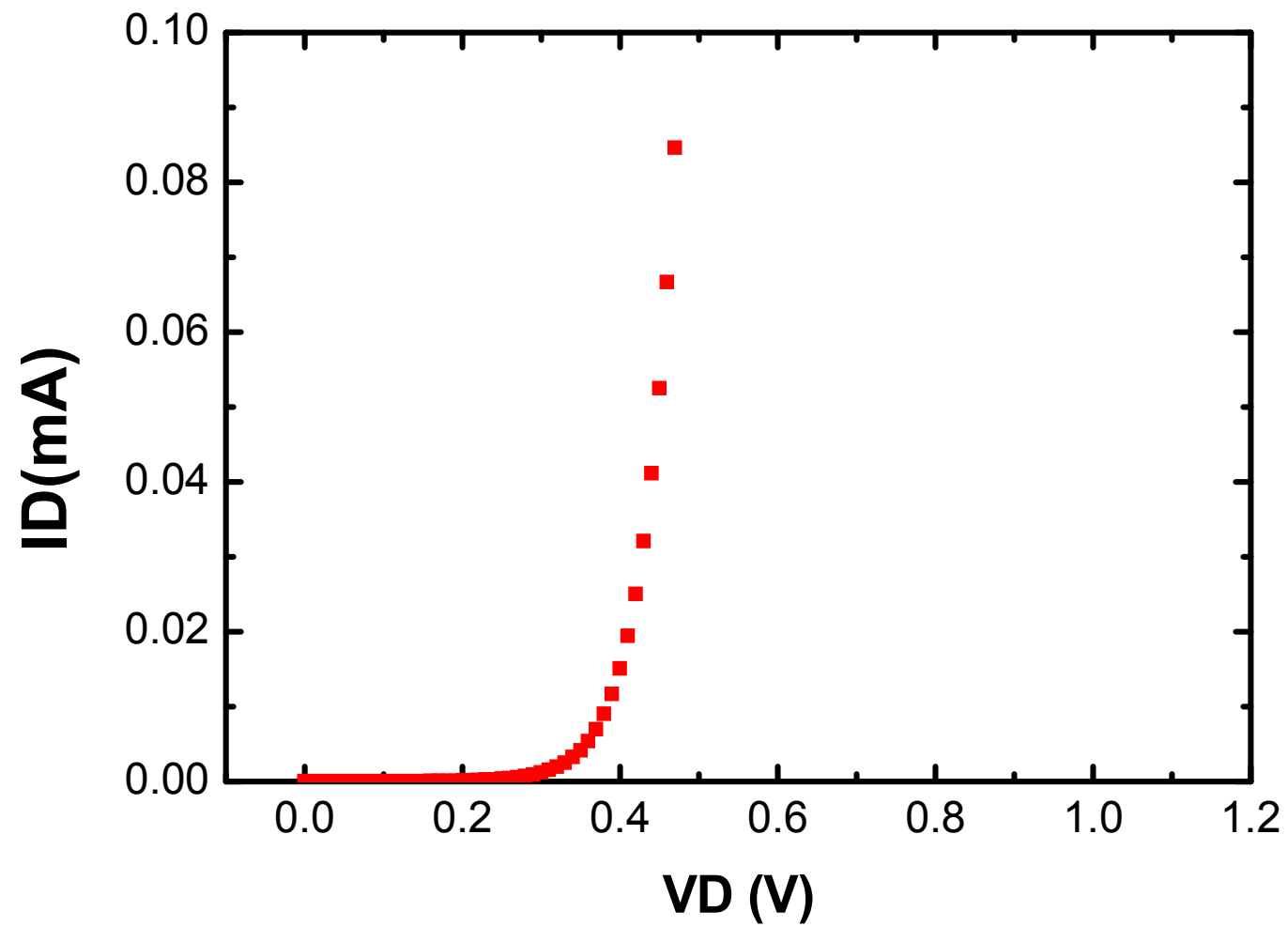

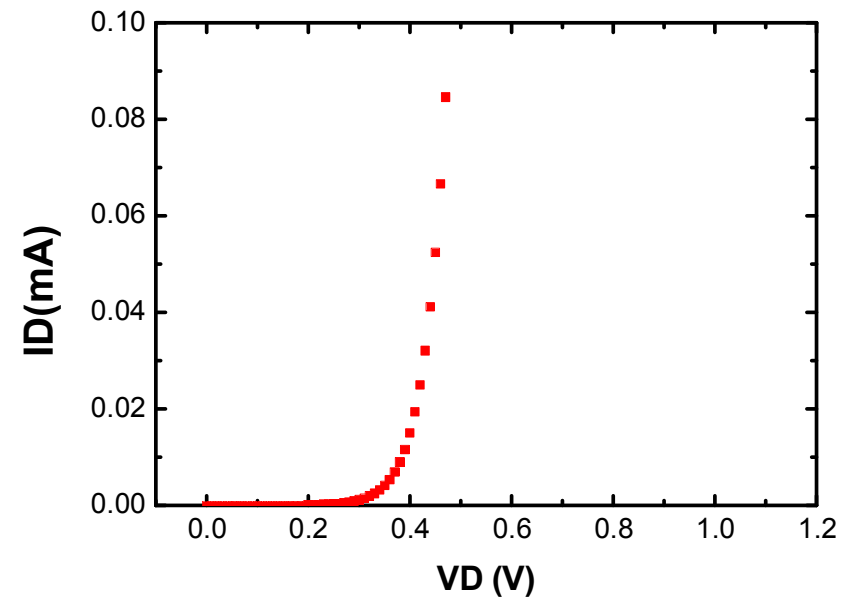


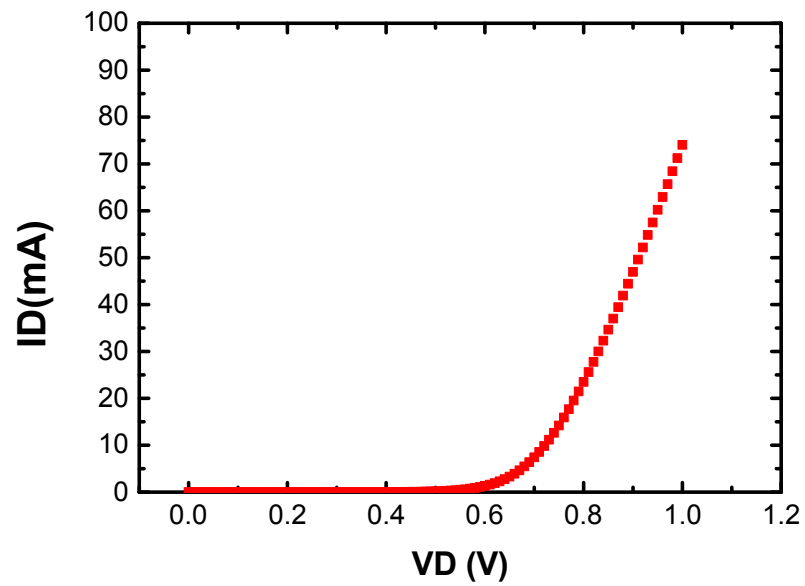

Both are identical diodes : 1N4007

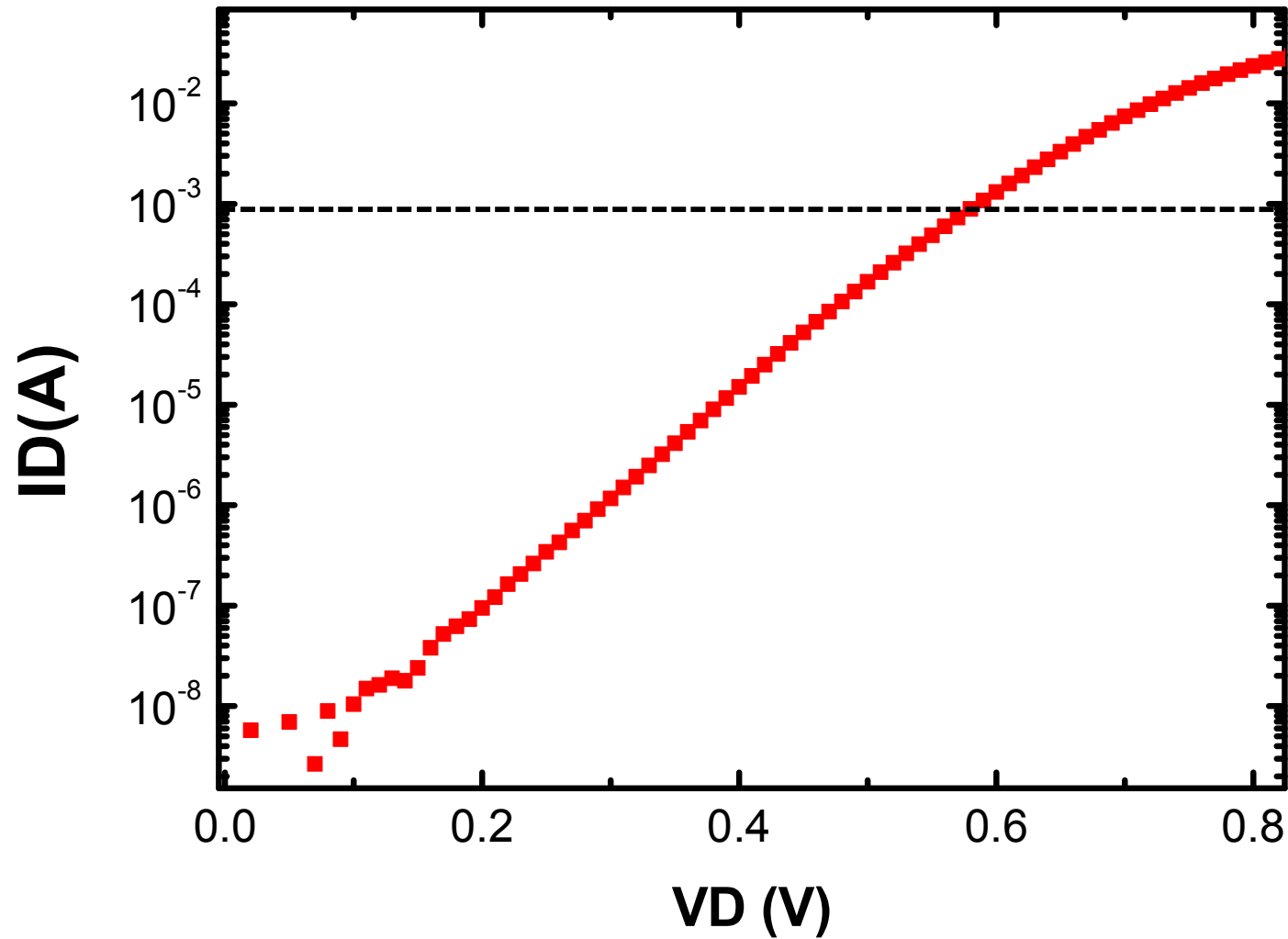

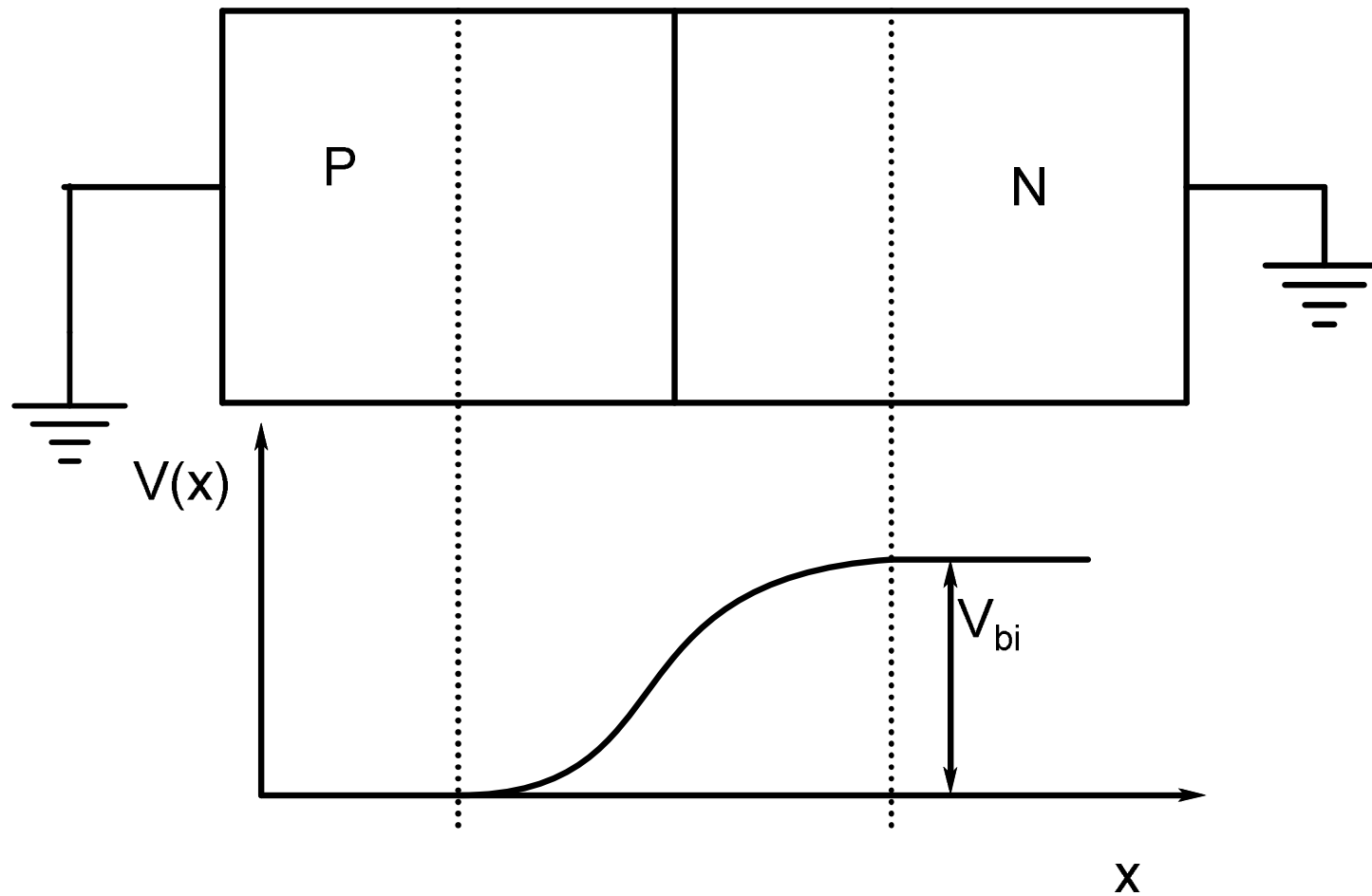
V_y the cut-in or turn-on voltage depends on nature of diode and range of current considered



Misconception: $V_{\gamma} \sim V_{bi}$

“Learning is not just accumulation of knowledge
but the detection and correction of errors”


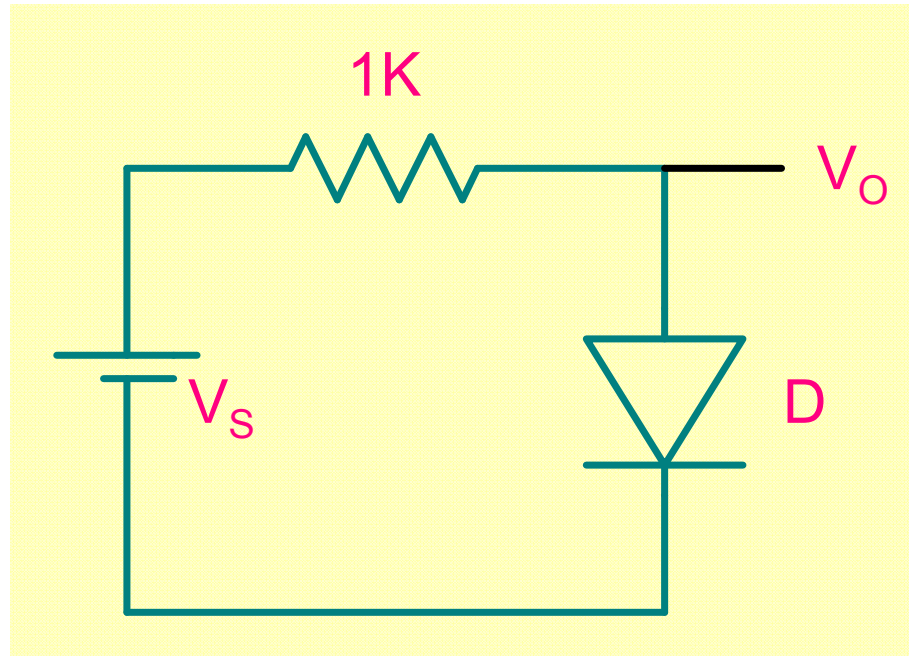
Constant diode voltage approximation becomes worse as applied voltage approaches the diode drop !



$$I = \frac{V - V_D}{R}$$
$$\Delta I = -\frac{\Delta V_D}{R}$$
$$\frac{\Delta I}{I} = -\left(\frac{\Delta V_D}{V - V_D}\right)$$

As V_s approaches $V_D \rightarrow \left(\frac{\Delta I}{I}\right)$ increases

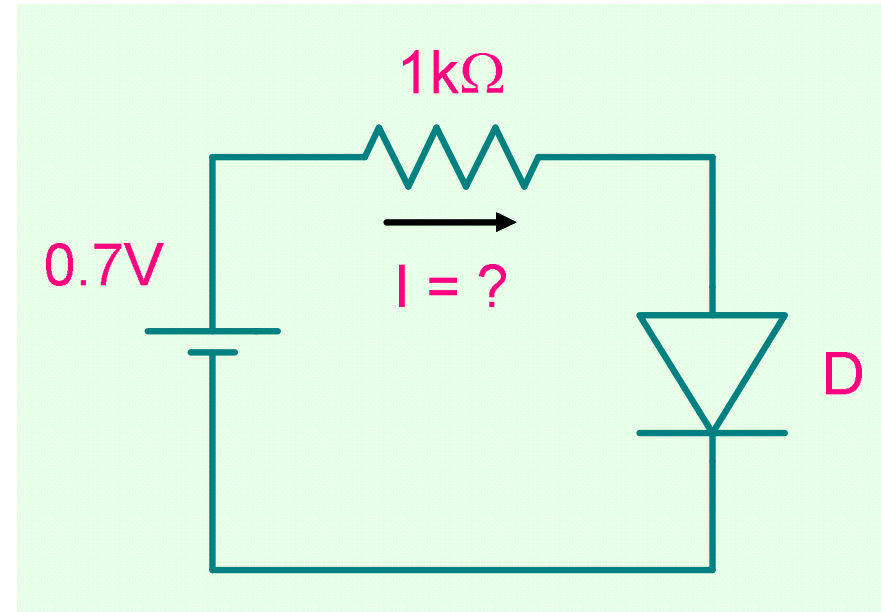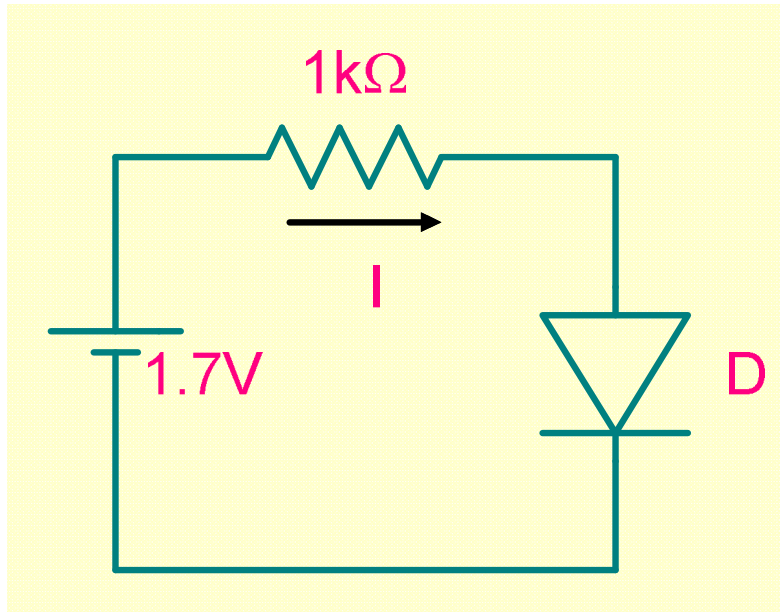Error was ~9% with 1.7 V but 63% with 0.8V supply






$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$





$$I_S = 2 \times 10^{-15} \text{ A}$$

$$V_T = kT / q \cong 26 \text{ mV} \text{ at } T = 300\text{K}$$

A better Diode Model

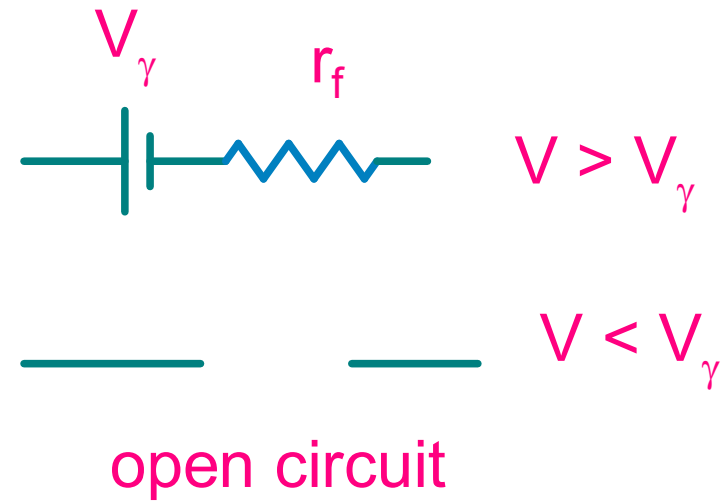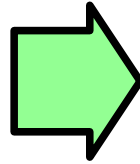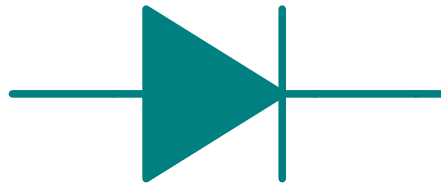


Piece-Wise Linear approximation

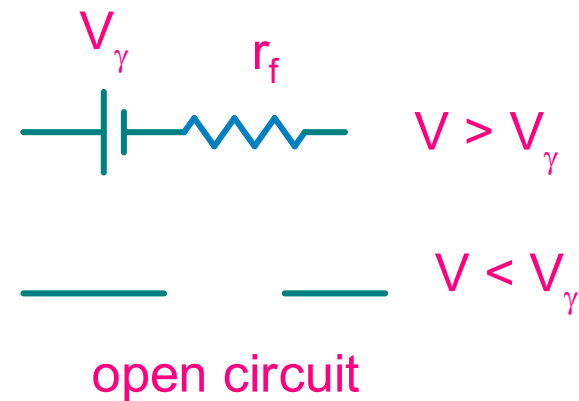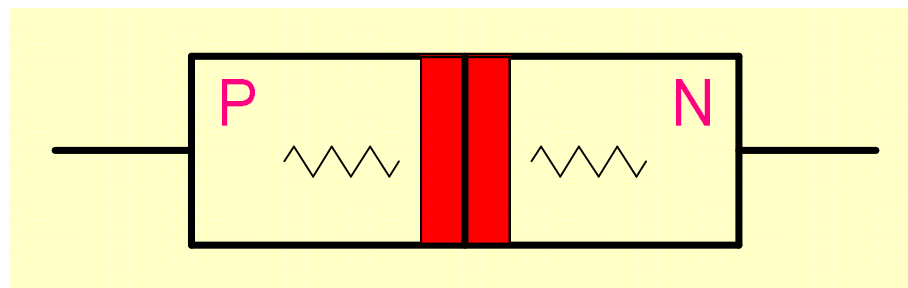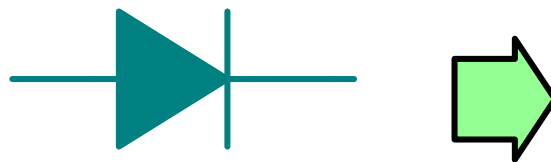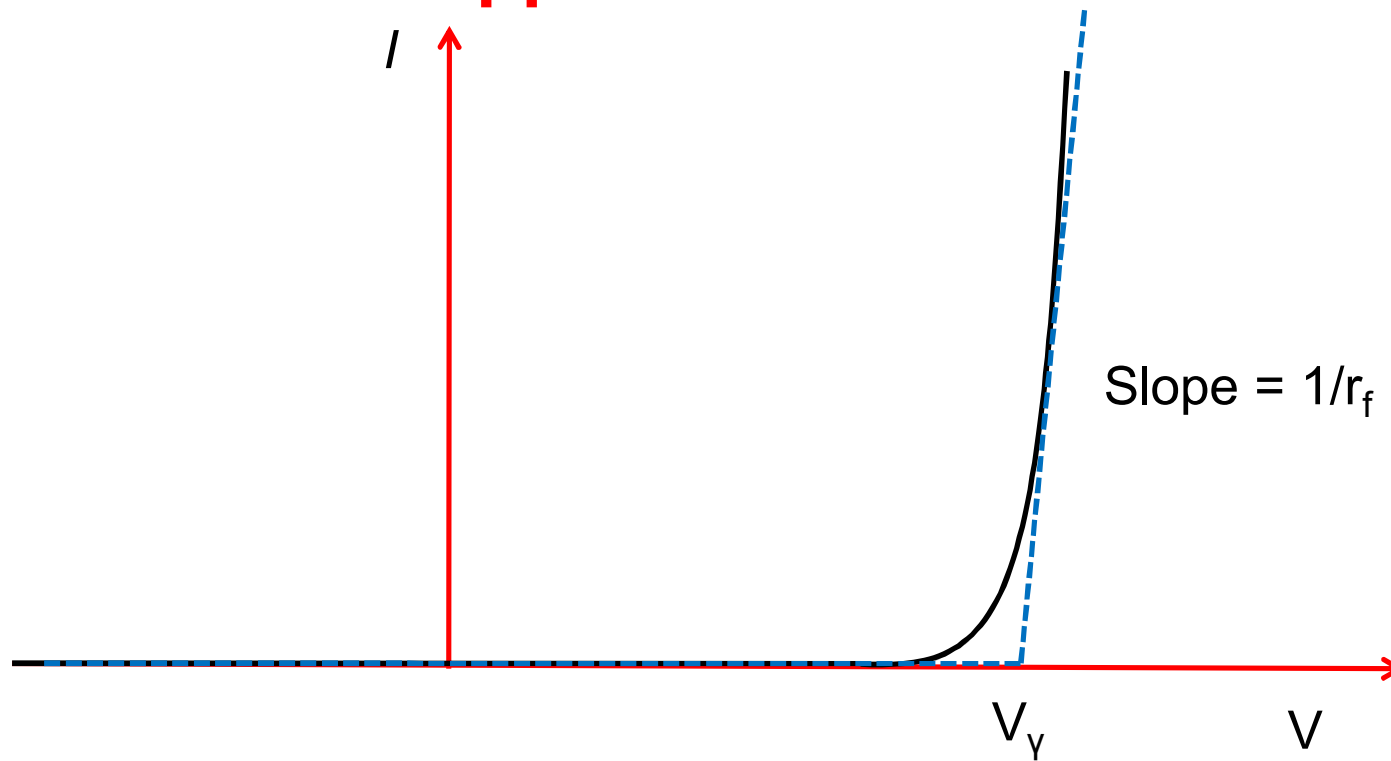


$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$


$$I_S = 2 \times 10^{-15} \text{ A}$$
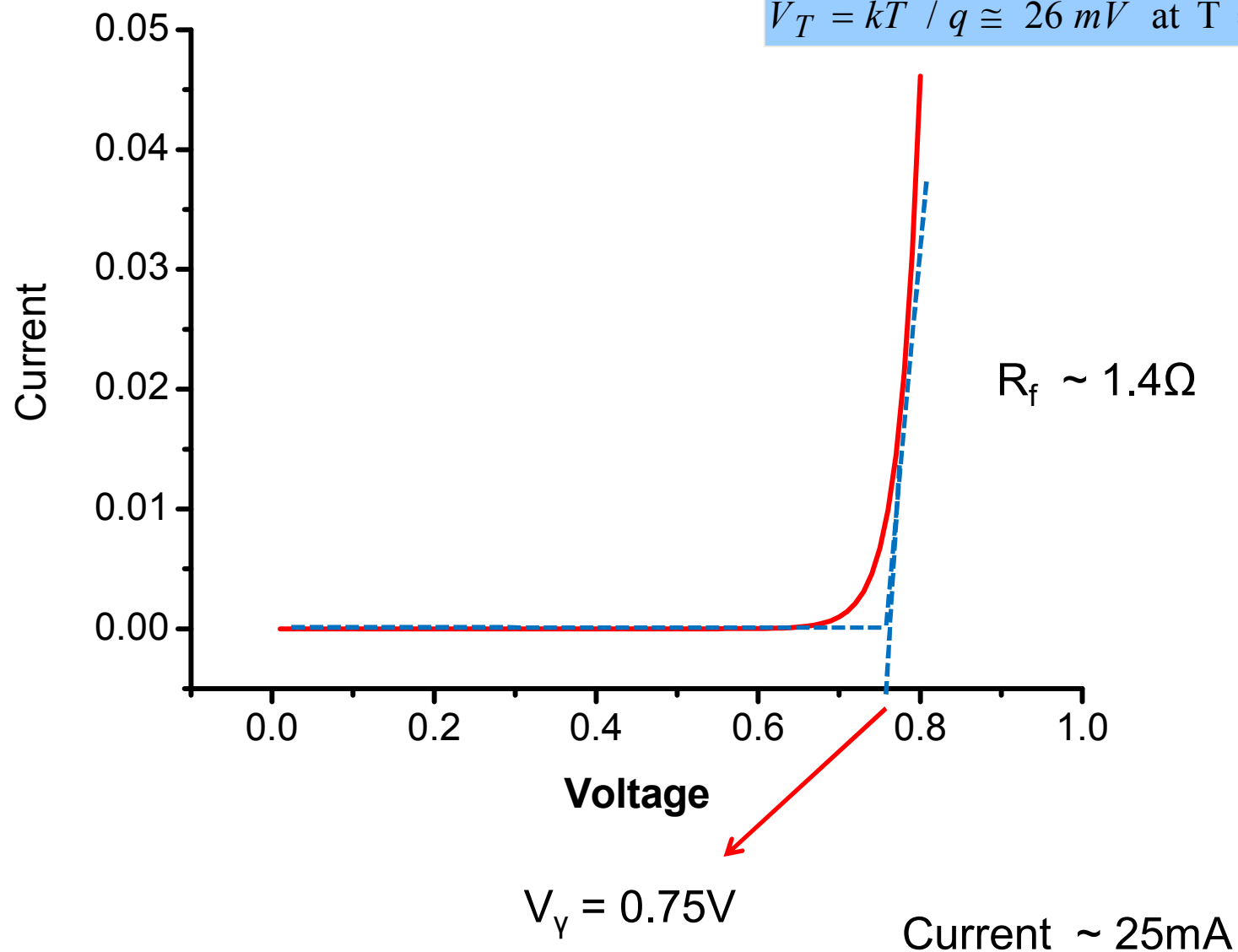
$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$




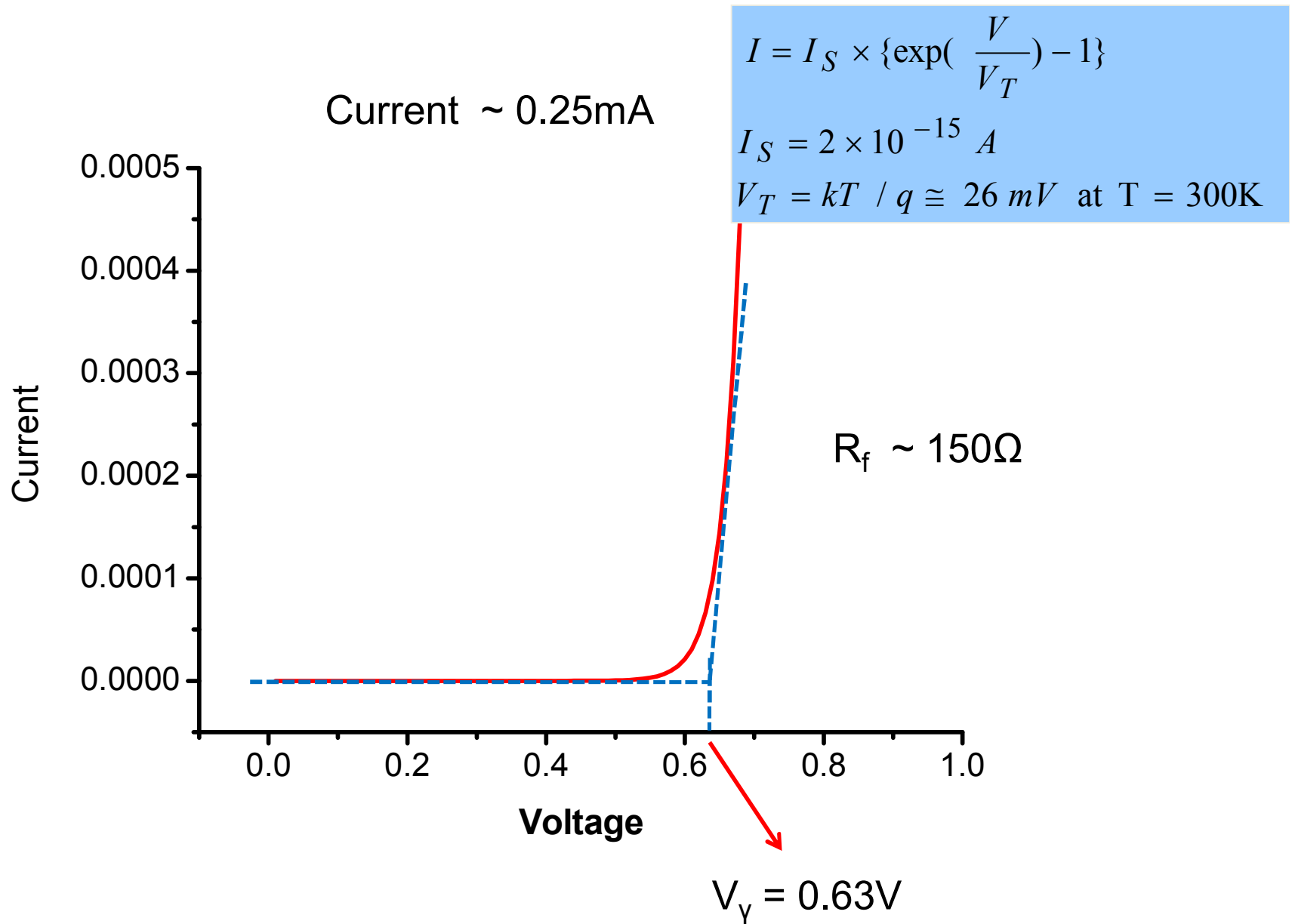

Even Simpler Diode Models

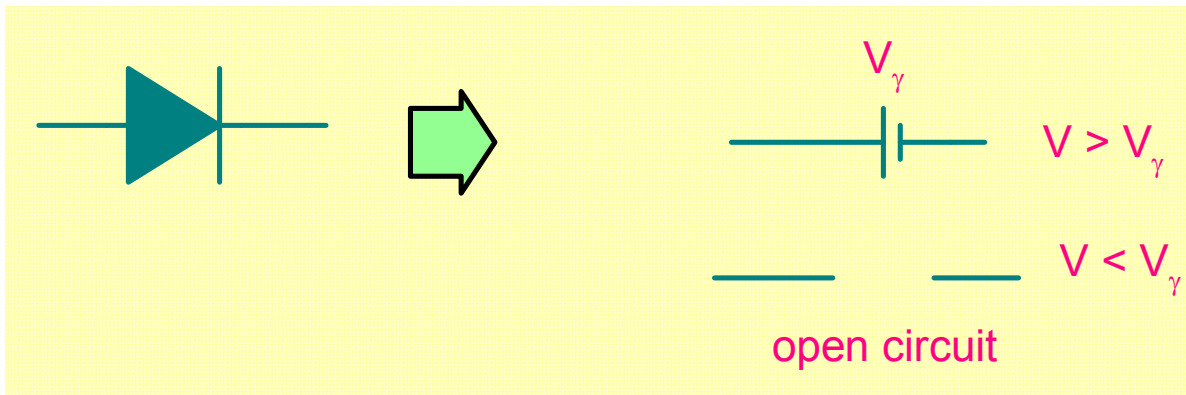


Ideal diode model

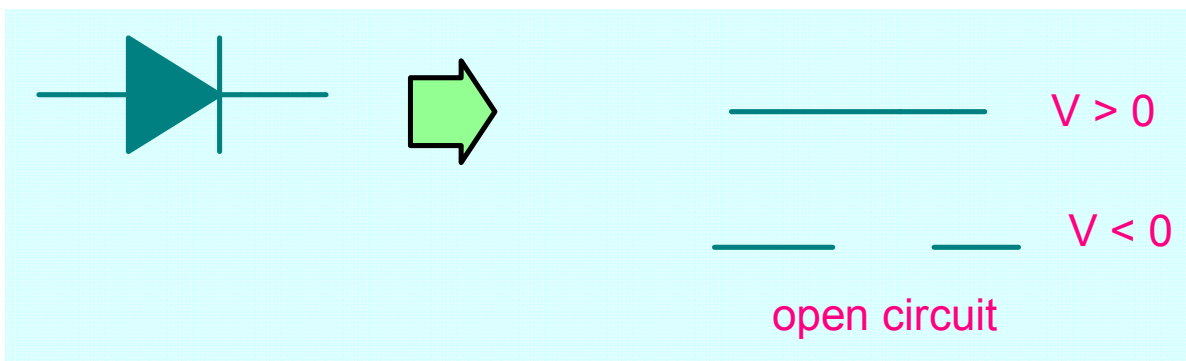

Diode Models


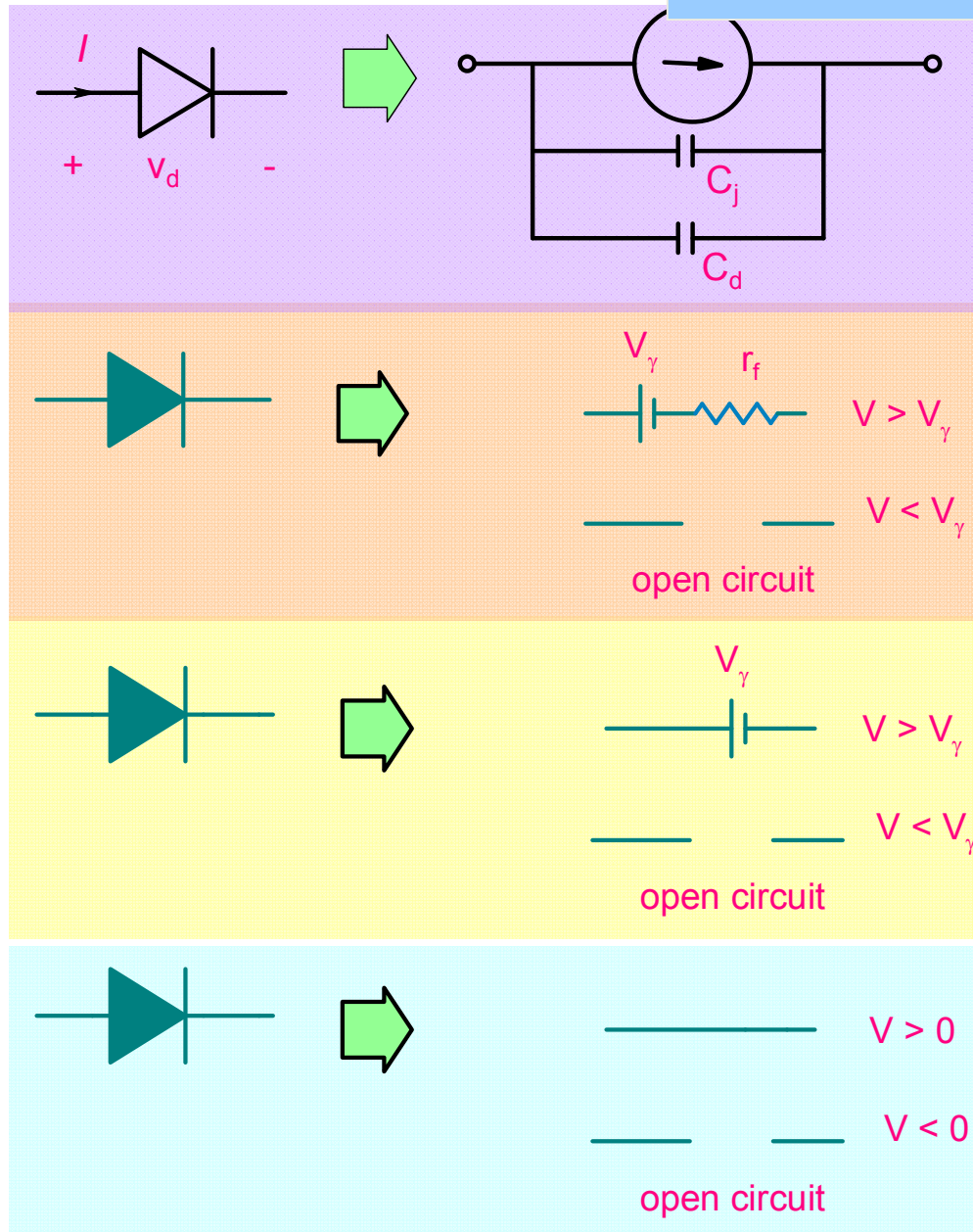
$$I = I_S \times \left\{ \exp\left(\frac{V_d}{V_T}\right) - 1 \right\}$$




Simplicity

Accuracy

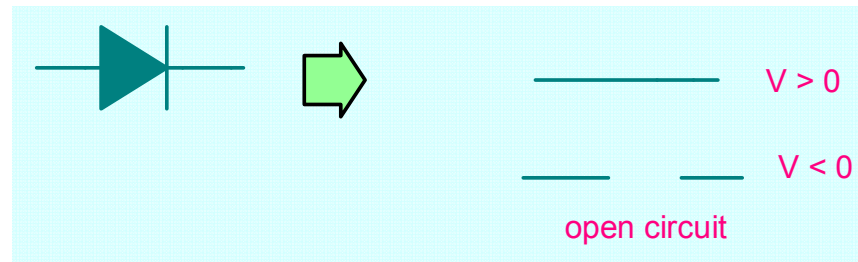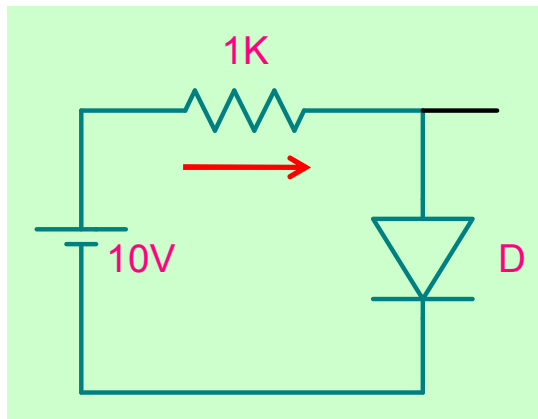
Use the simplest model that will yield results with desired accuracy



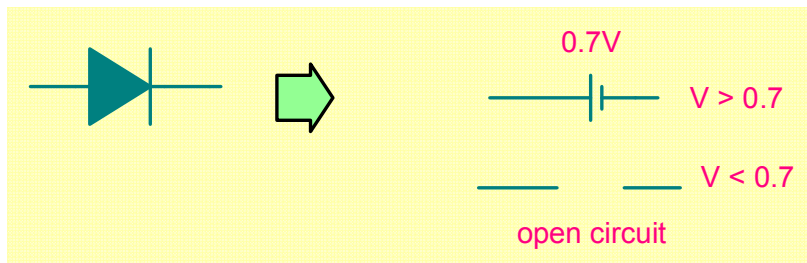
$$I = 10 / 10^3 = 10 \text{ mA} \quad 8.2\%$$


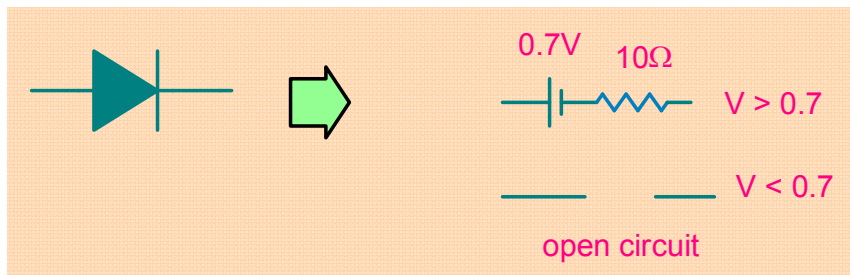
$$I = (10 - 0.7) / 10^3 = 9.3 \text{ mA} \quad 0.65\%$$




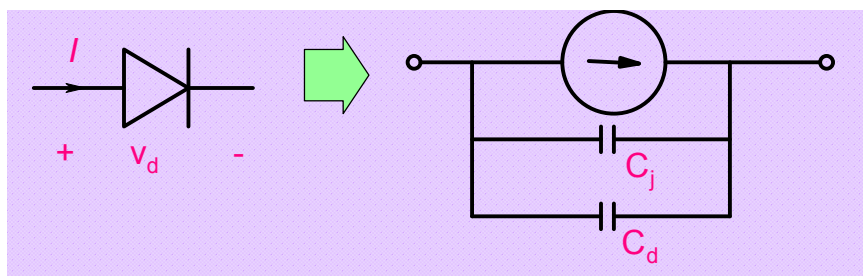
$$I = (10 - 0.7) / (10^3 + 10) = 9.208 \text{ mA} \quad -0.34\%$$




$$I = 9.24 \text{ mA}$$

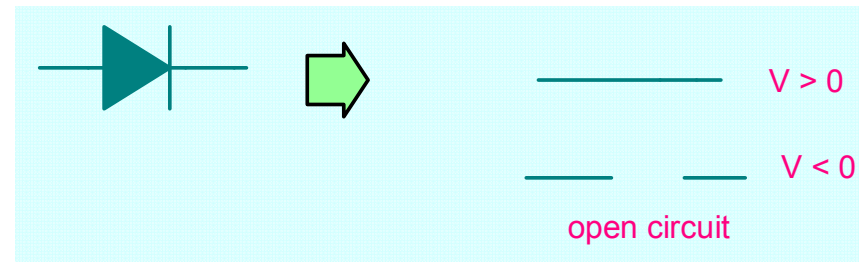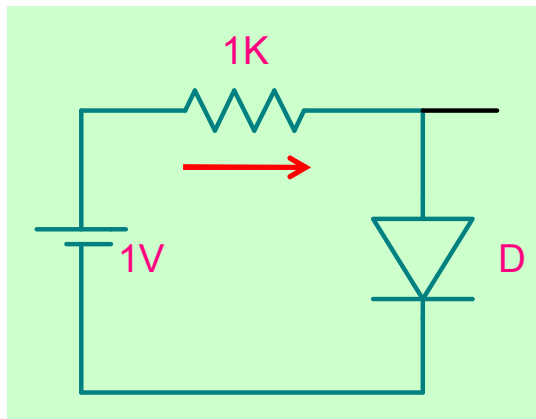
Use the simplest model that will yield results with desired accuracy



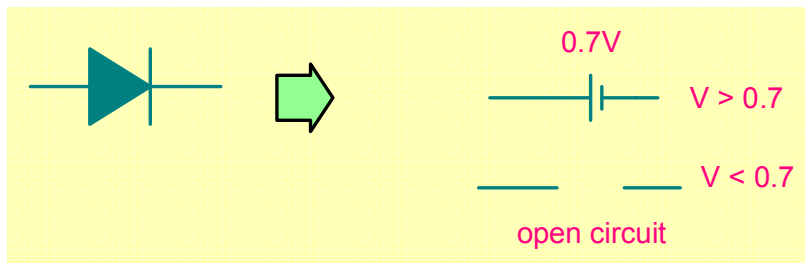
$$I = 1 / 10^3 = 1 \text{ m A} \quad \sim 200\%$$


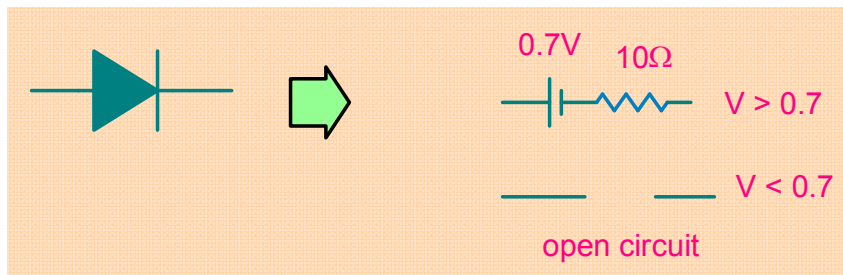
$$I = (1 - 0.7) / 10^3 = 0.3 \text{ m A} \quad -8.8\%$$


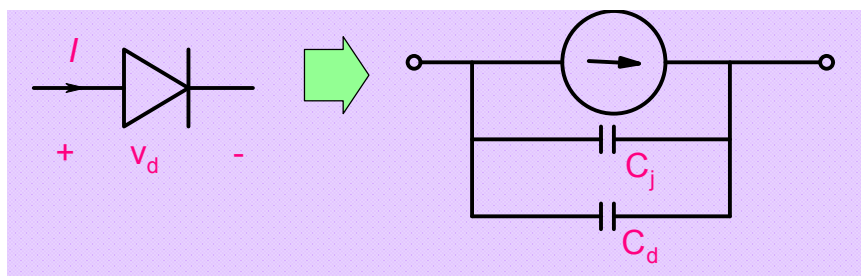
$$I = (1 - 0.7) / (10^3 + 10) = 0.297 \text{ m A} \quad -9.7\%$$



$$I = 0.329 \text{ m A}$$

Diode: Small Signal Model (dc or low frequency)

Forward Bias

$$I_d = I_s e^{\frac{V_d}{nV_T}}$$

$$I_{DQ} + i_d = I_s e^{\frac{V_{DQ} + v_d}{nV_T}}$$

$$i_d = I_{DQ} \left(e^{\frac{v_d}{nV_T}} - 1 \right)$$

$$i_d = I_{DQ} \left(\frac{v_d}{nV_T} + \frac{v_d^2}{2(nV_T)^2} + \dots \right)$$

Small signal approx : $\frac{v_d}{nV_T} \ll 1$

$$i_d = I_{DQ} \left(\frac{v_d}{nV_T} + \frac{v_d^2}{2(nV_T)^2} + \dots \right)$$

$$i_d \cong \left(\frac{I_{DQ}}{nV_T} \right) v_d$$

$$i_d = \frac{v_d}{r_d} ; r_d = \frac{nV_T}{I_{DQ}}$$

