



# EE210: Microelectronics-I

## Lecture-9 : Bipolar Junction Transistor-2


Instructor: Y. S. Chauhan

Slides from: B. Mazhari  
Dept. of EE, IIT Kanpur

# BJT : equivalent circuit

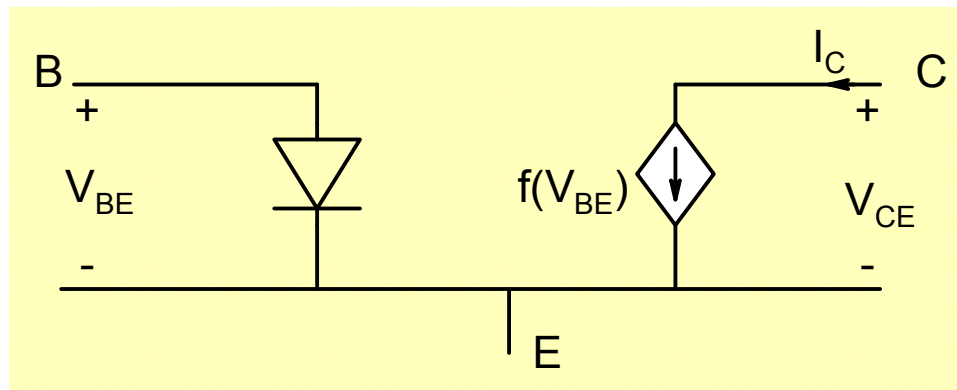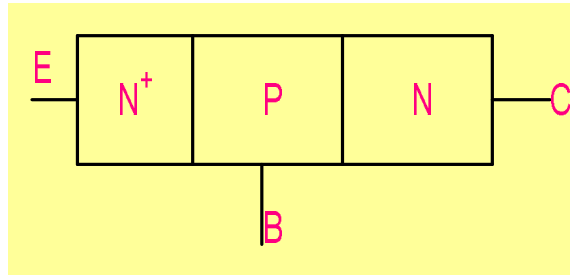


$$\beta = \frac{I_C}{I_B}$$



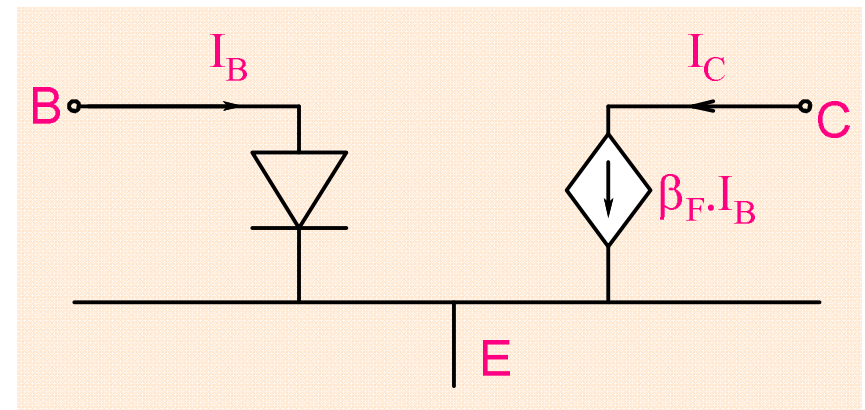


$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta}$$



# Forward Active Mode

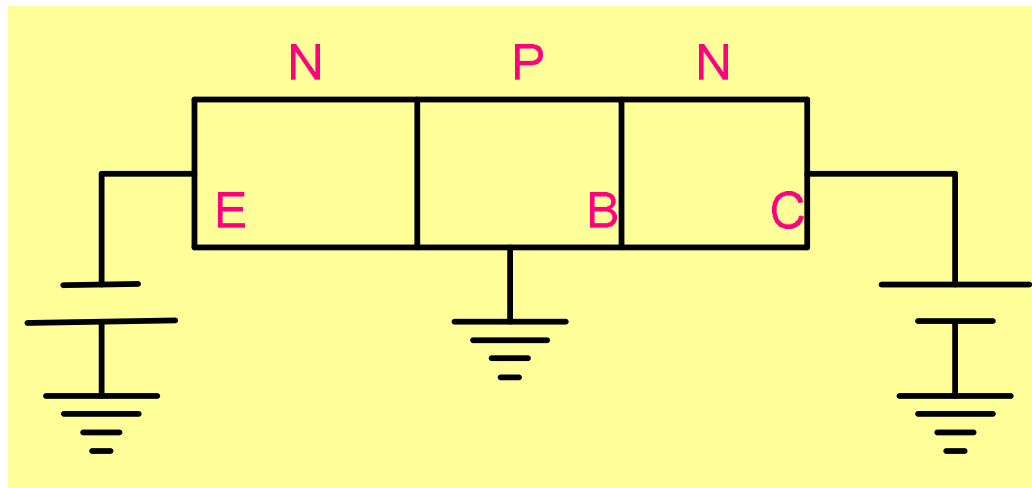

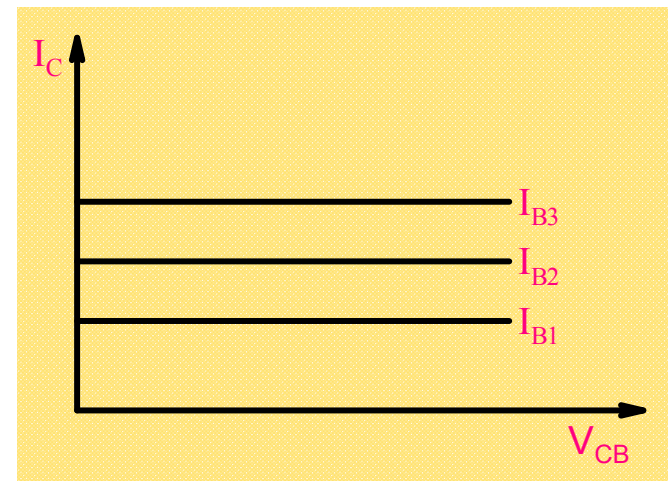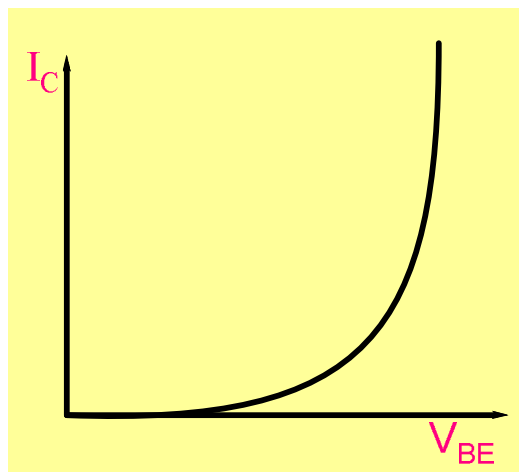
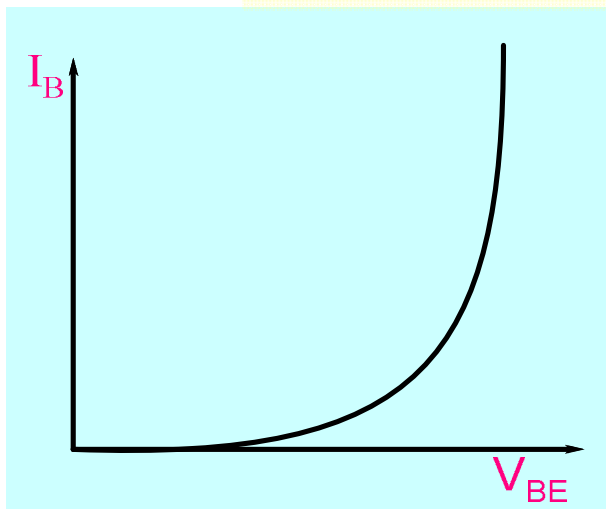
$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) ; \quad I_B = \frac{I_C}{\beta}$$



# Modes of operation

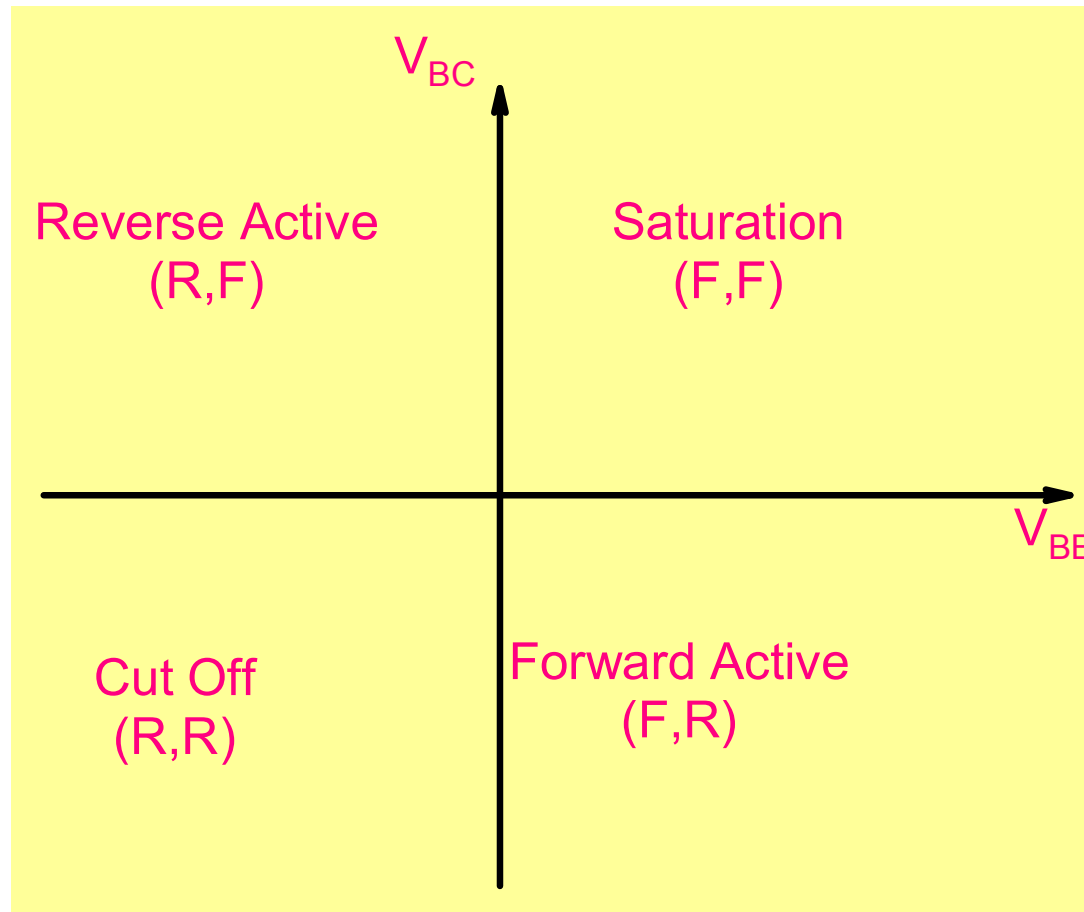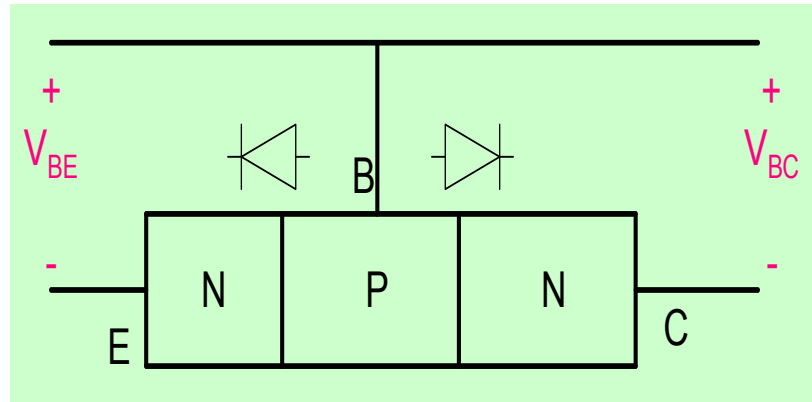




# Saturation

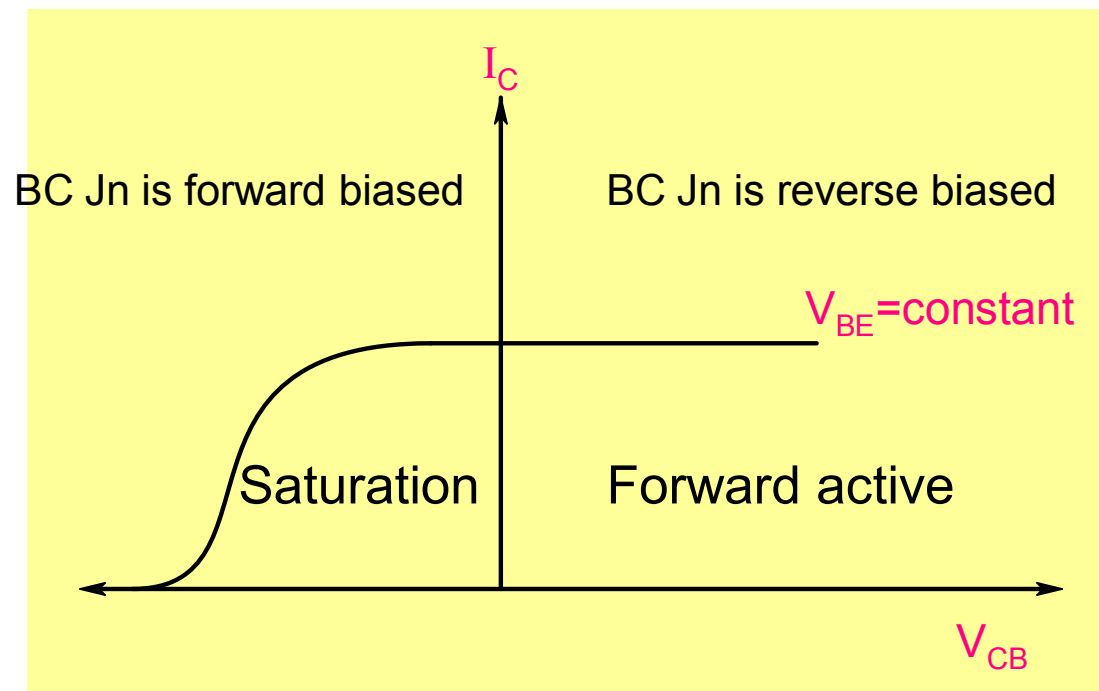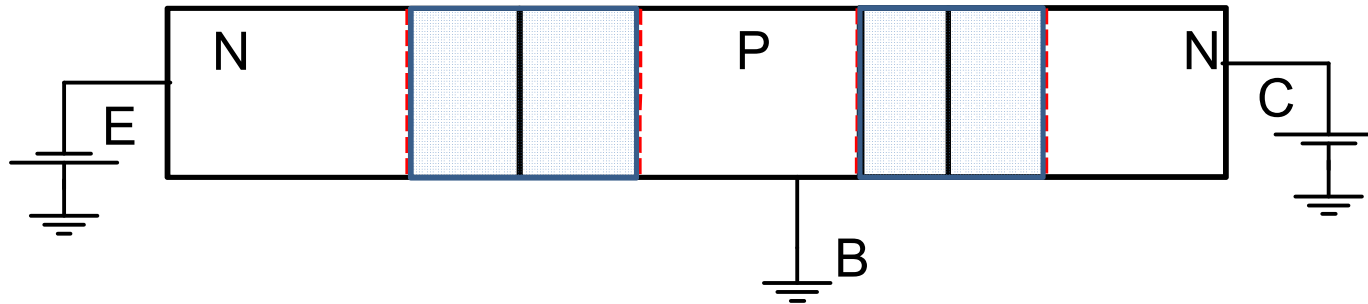



Why does  $I_C$  drop in saturation?

$$I_C = 1mA ; I_B = 0.01mA$$


$$\frac{I_C}{I_B} = 100 = \beta$$

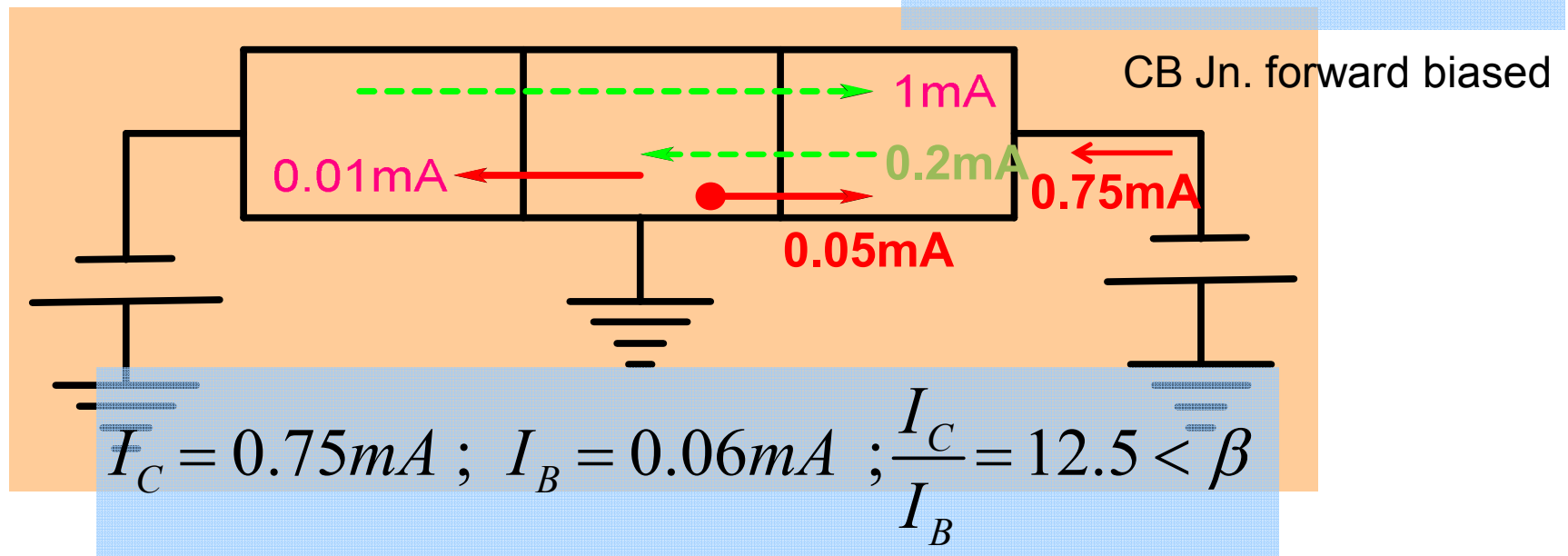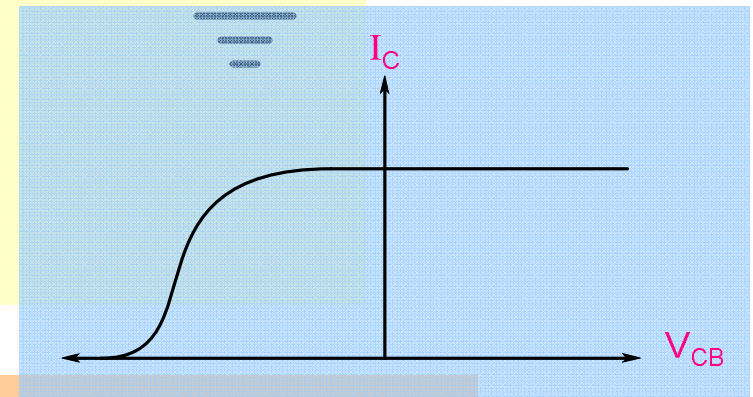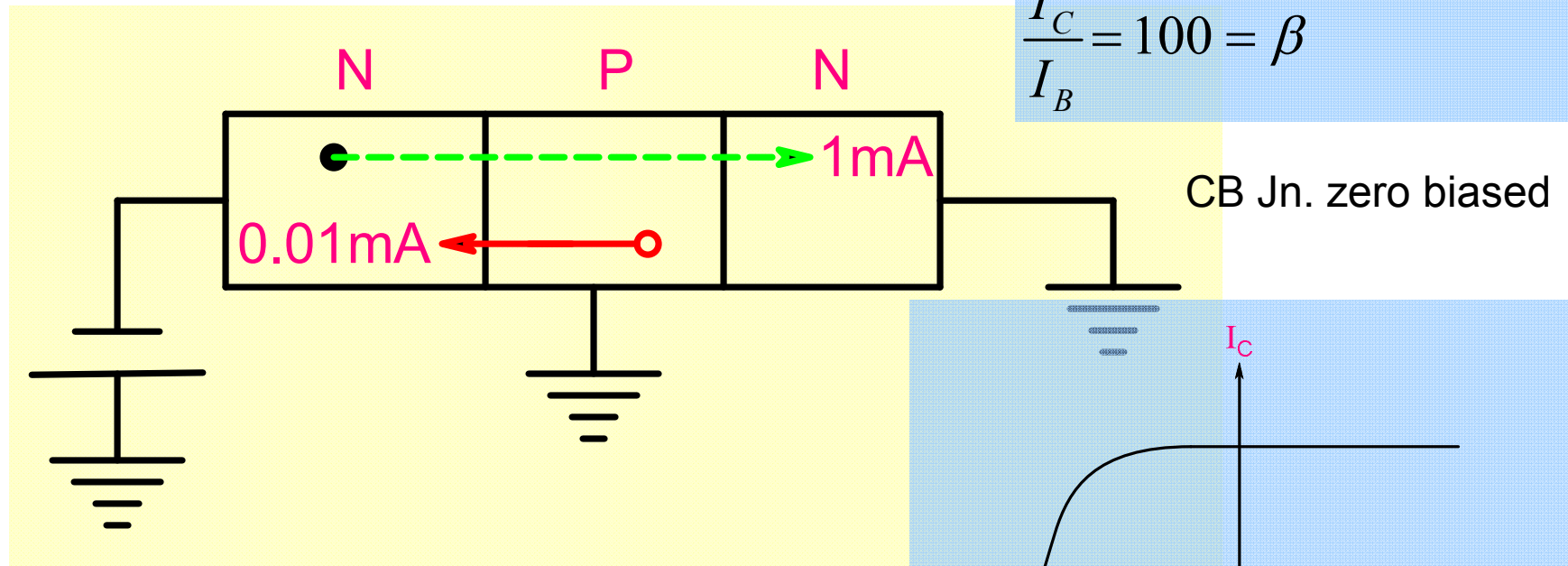
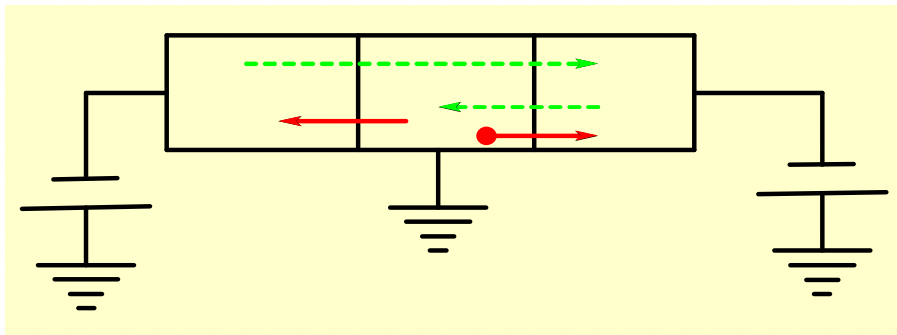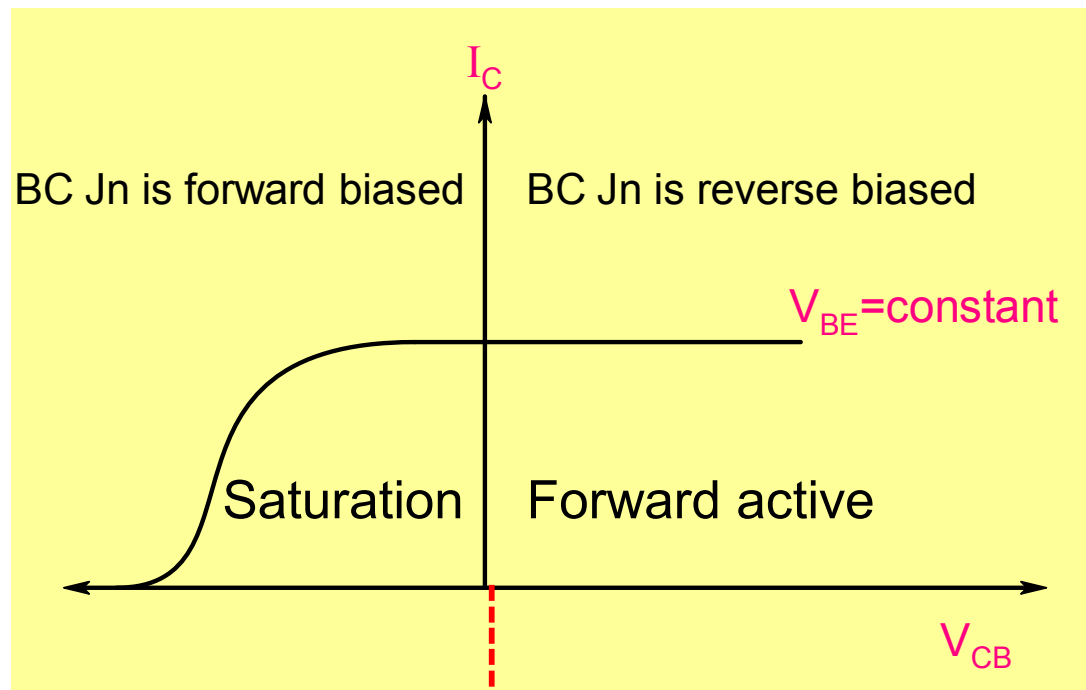
$$I_C = 0.75mA ; I_B = 0.06mA ; \frac{I_C}{I_B} = 12.5 < \beta$$




$$\frac{I_C}{\beta \times I_B} < 1$$

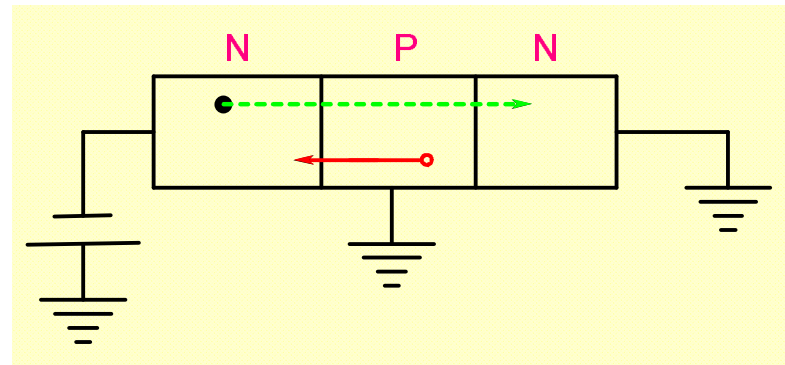




$$\frac{I_C}{\beta \times I_B} = 1$$

# Forward Active Mode

# Common-Base


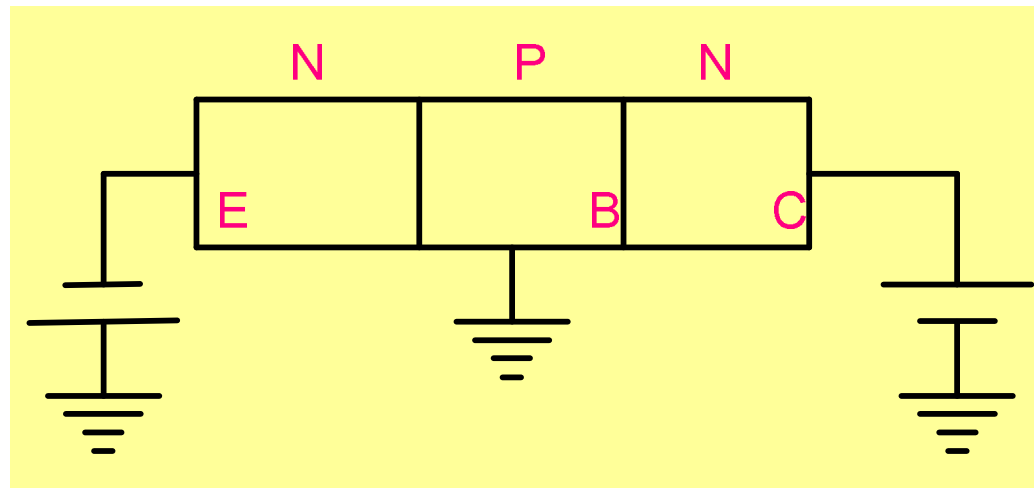

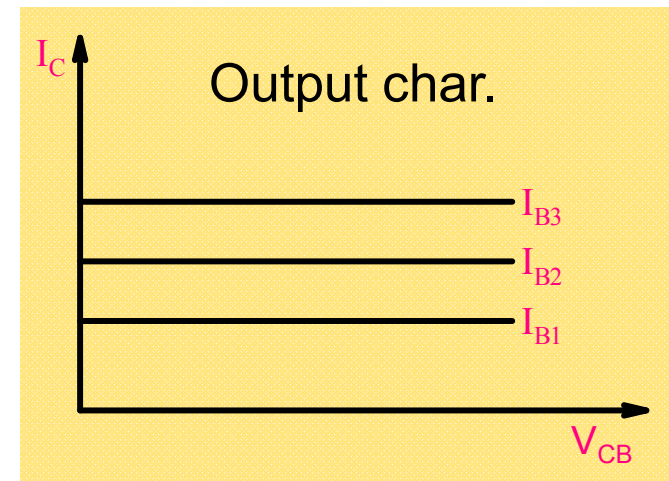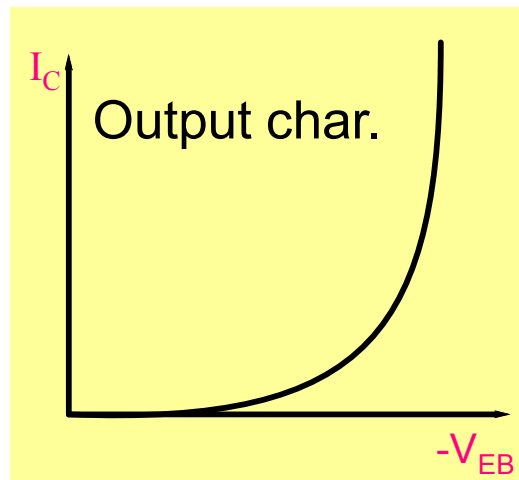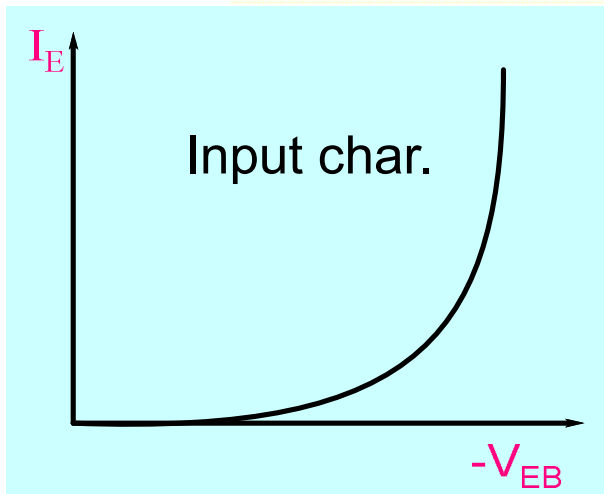
$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) ; \quad I_B = \frac{I_C}{\beta_F}$$







# Common-Emitter

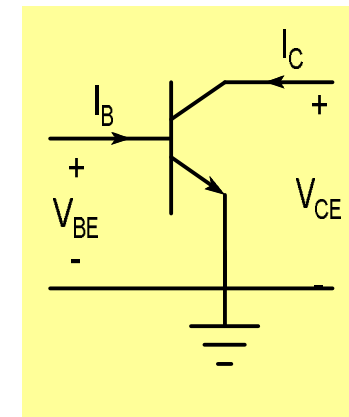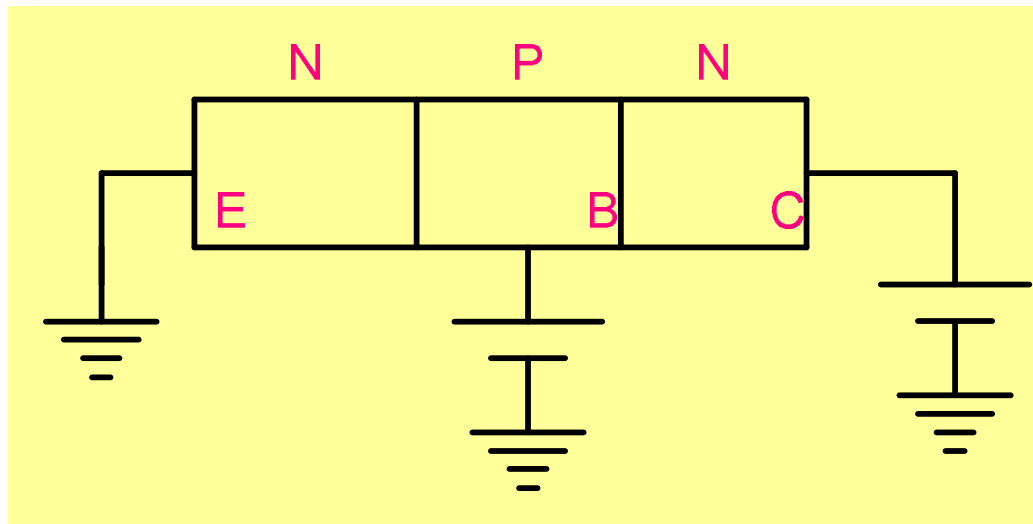


Input char.

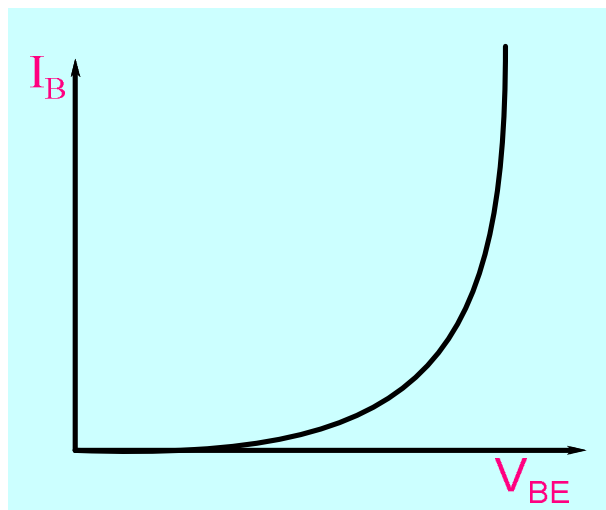


Output char.

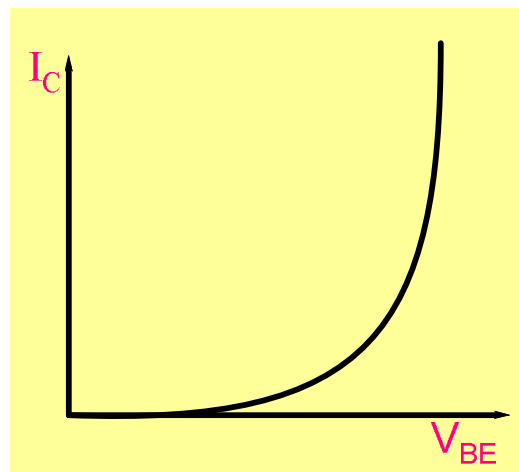

Output char.

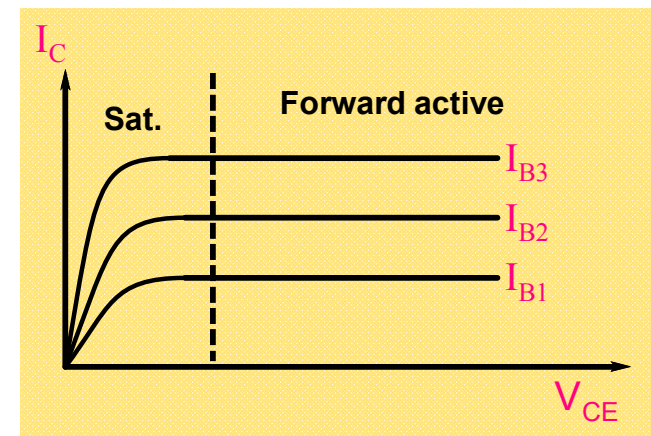

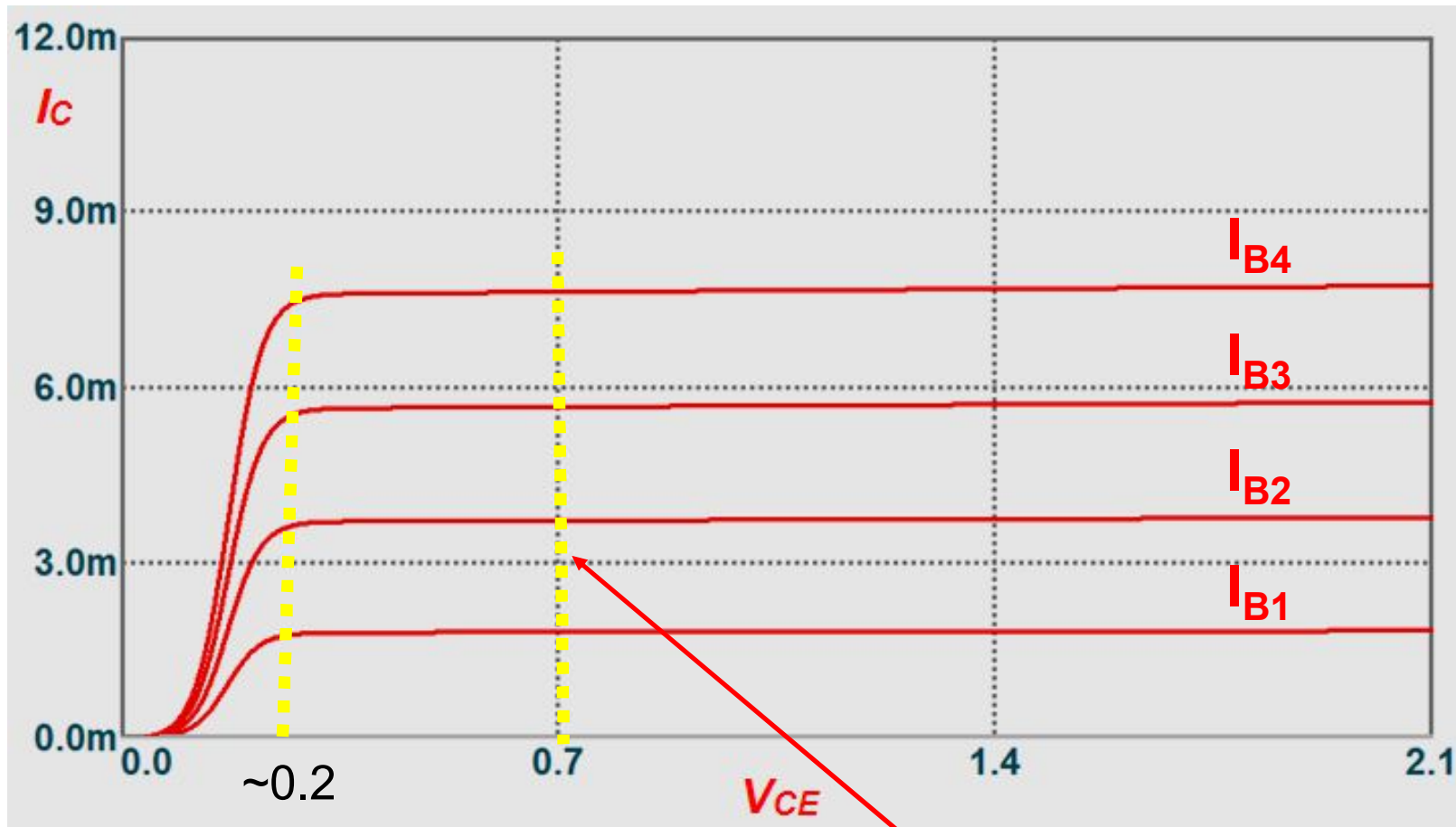

$$V_{CE} = V_{CB} + V_{BE}$$



$$= V_{BE} - V_{BC}$$

$$V_{BC} = 0.7 - V_{CE}$$



CbB jn. Starts to get forward biased

Note that in saturation:  $\frac{I_C}{\beta I_B} < 1$





**CB**

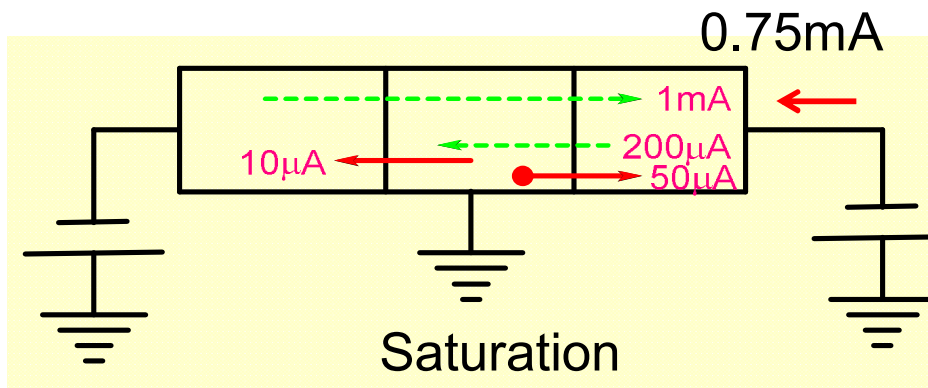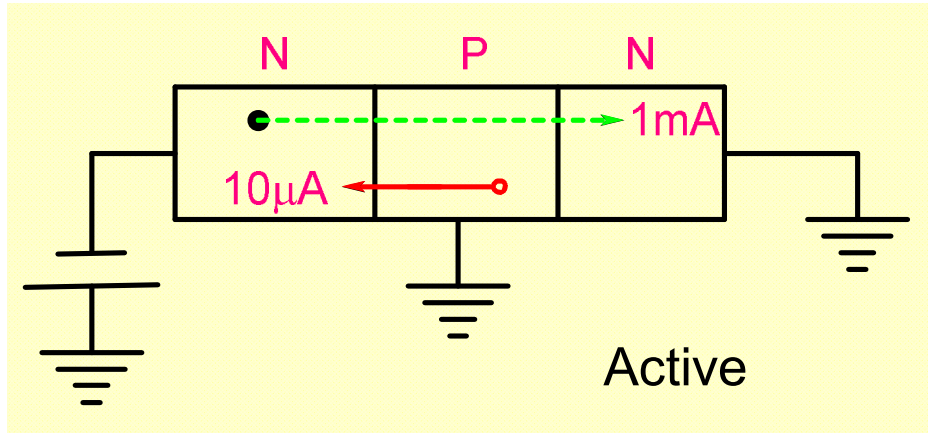

**CE**



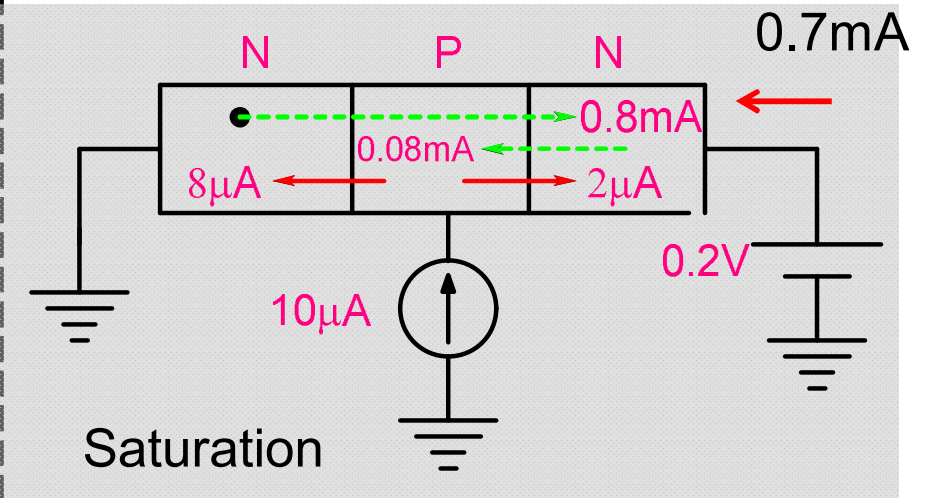
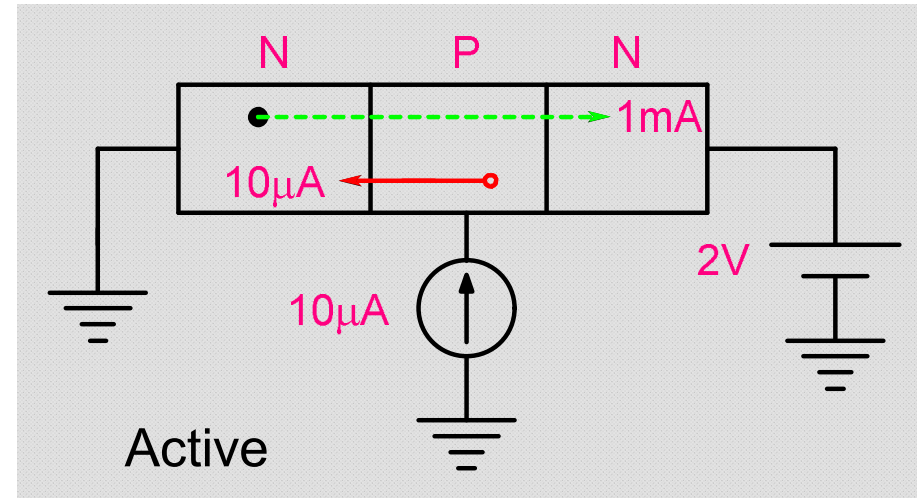


# Model of a BJT in Saturation mode

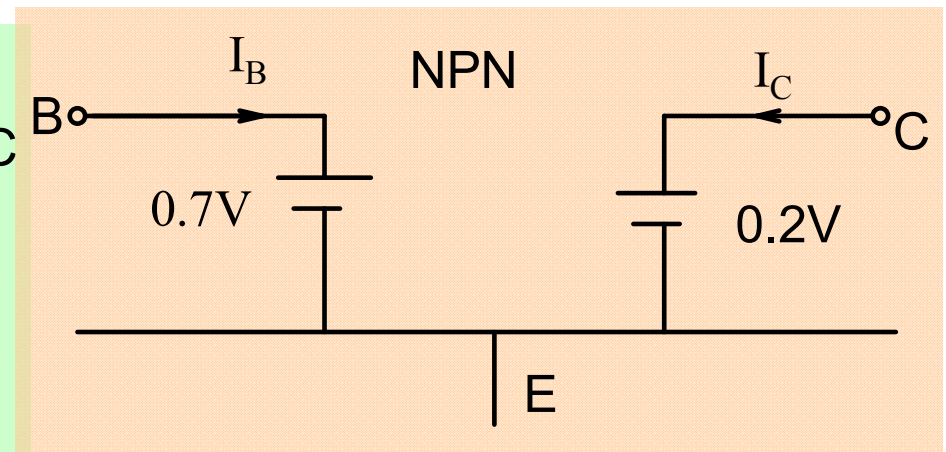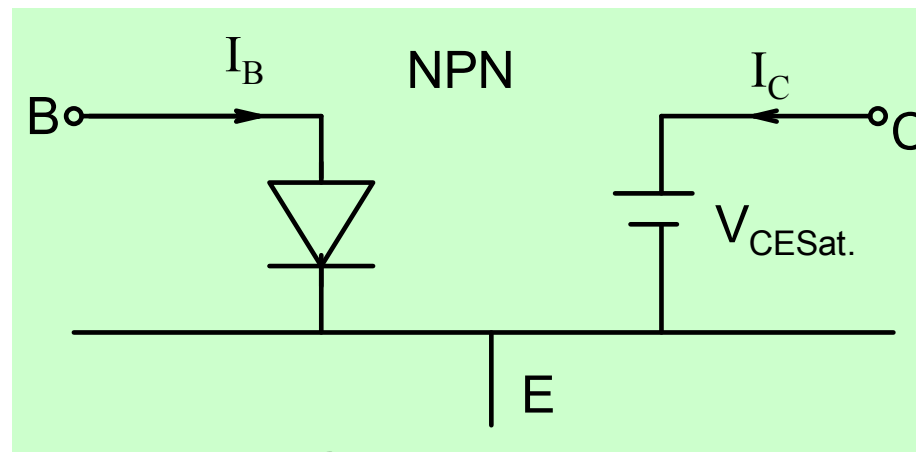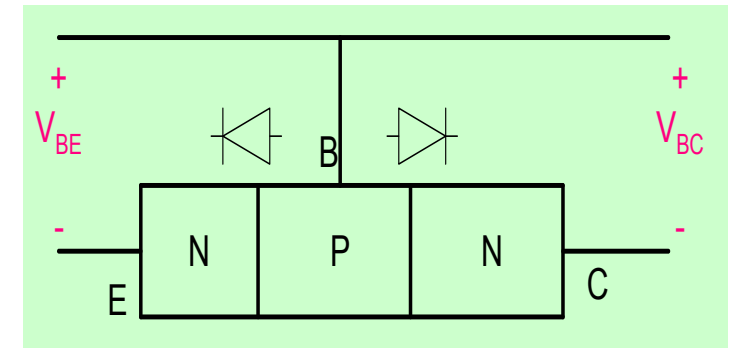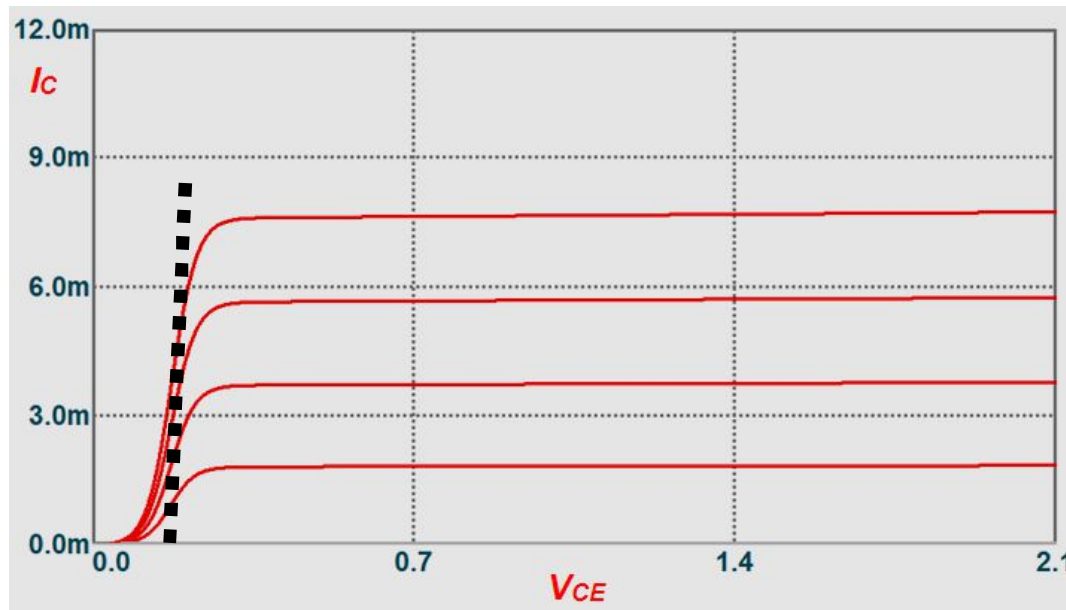


$$I_C \neq \beta I_B \quad V_{CESat.} \cong 0.2V$$

## Simplified Model

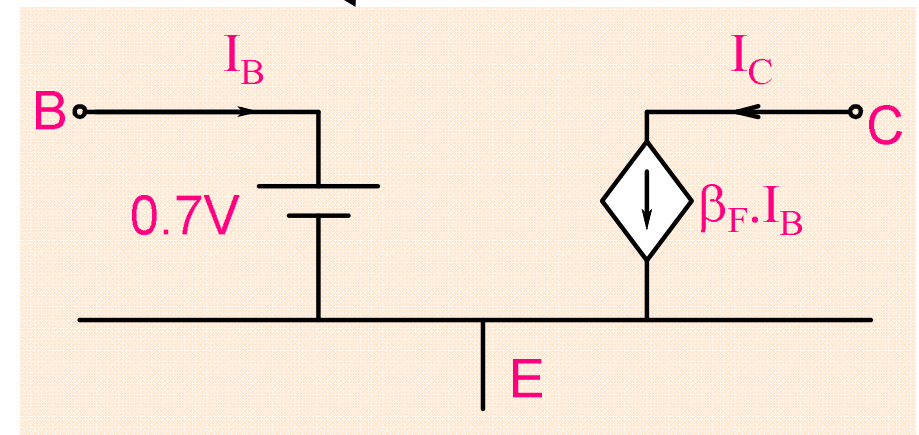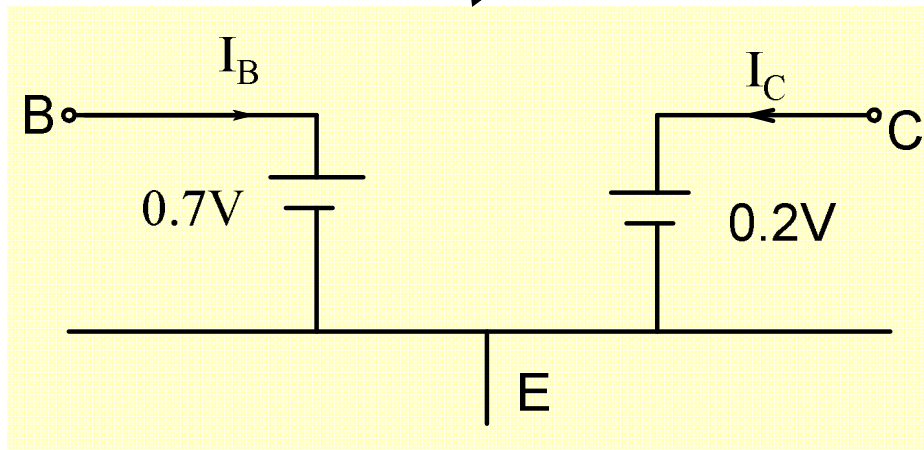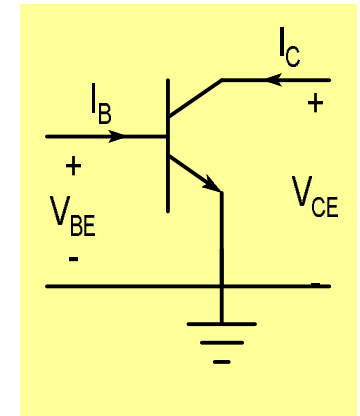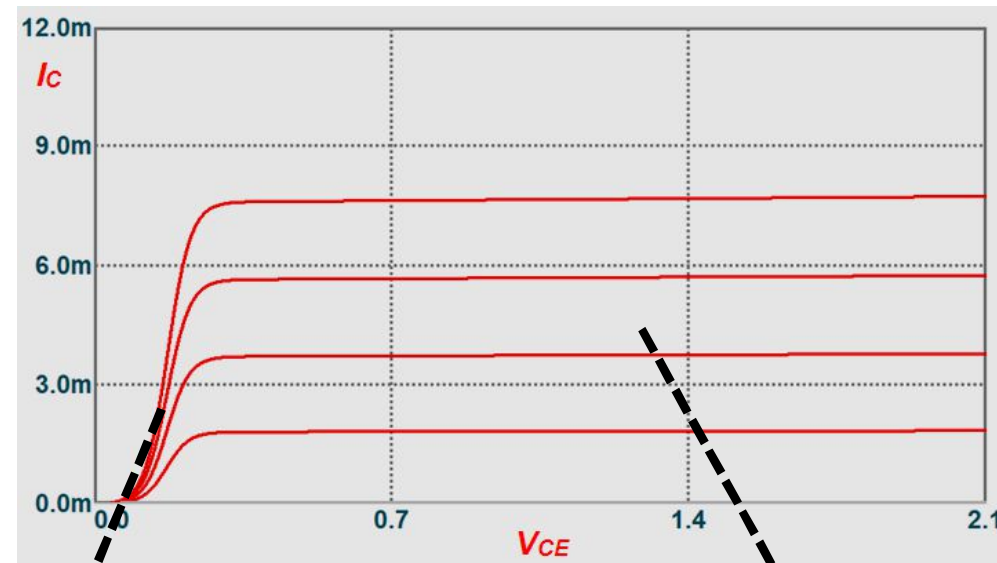


# **Generalized Transistor Model**

## Forward Active Mode

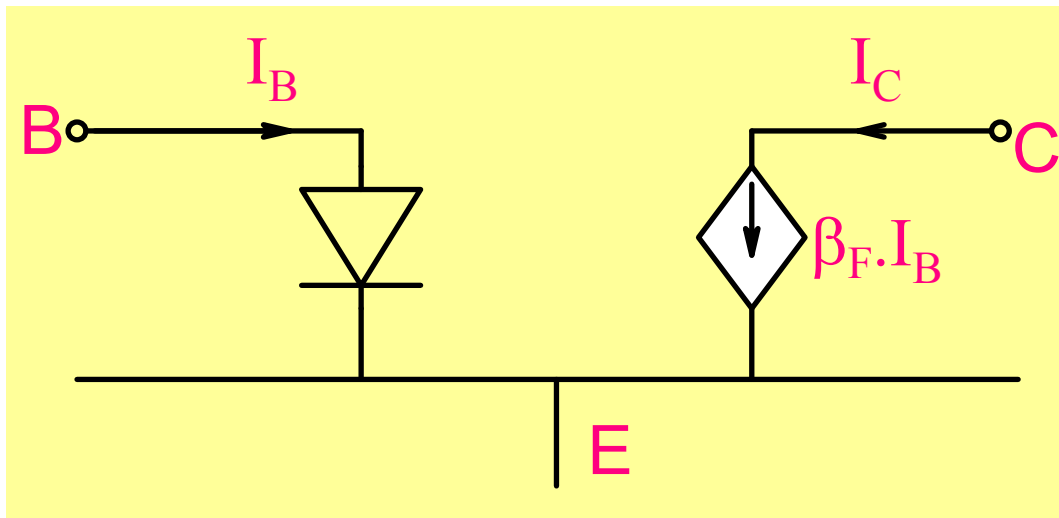
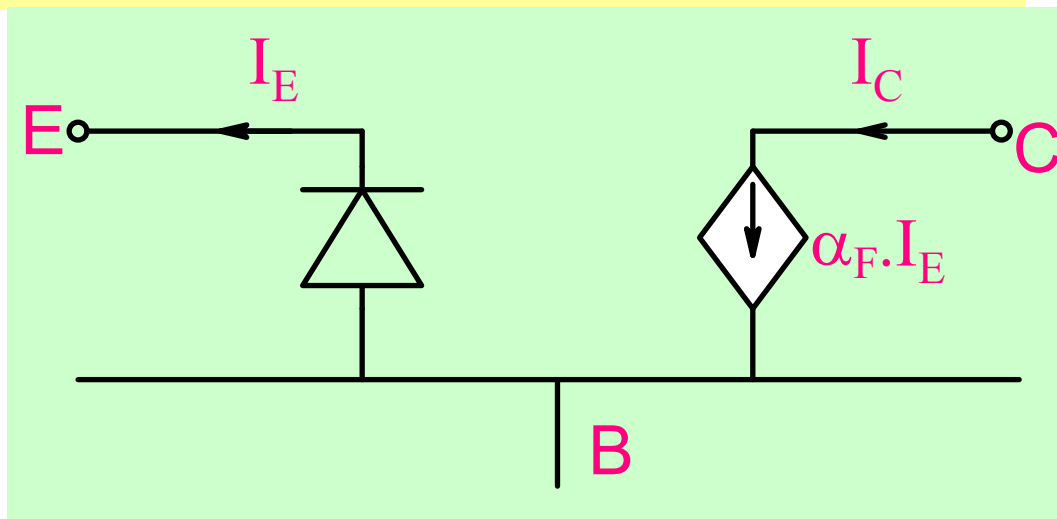
$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta_F}$$



$$I_C = \beta_F \times I_B$$



$$I_E = I_C + I_B$$

$$I_C = \alpha_F \times I_E$$

$$\alpha_F = \frac{\beta_F}{1 + \beta_F}$$

$\beta_F$  : Common Emitter Current Gain



$\alpha_F$  : Common Base Current Gain

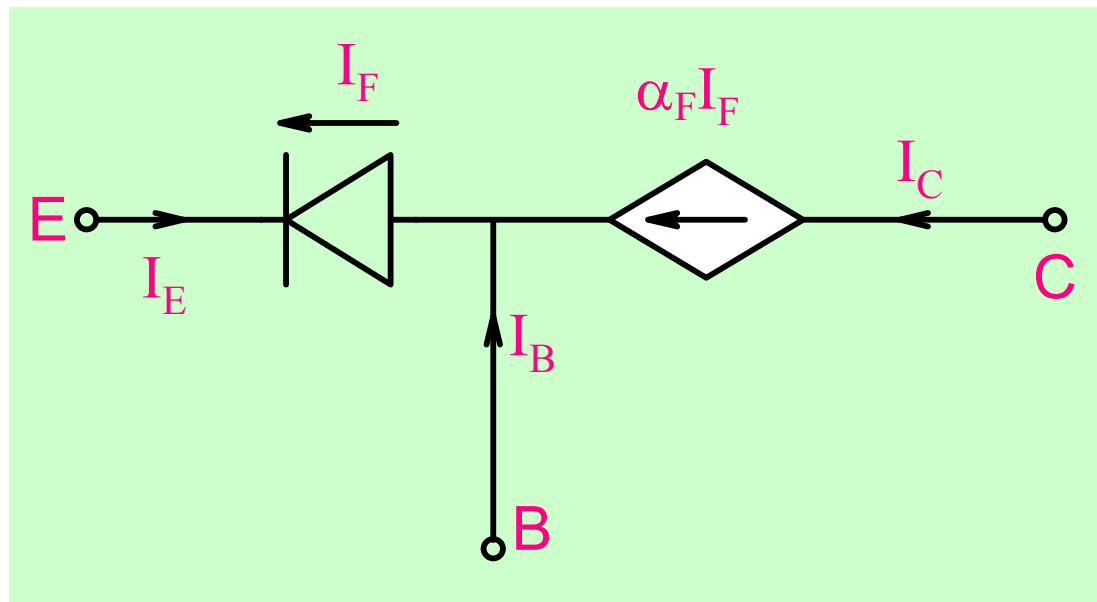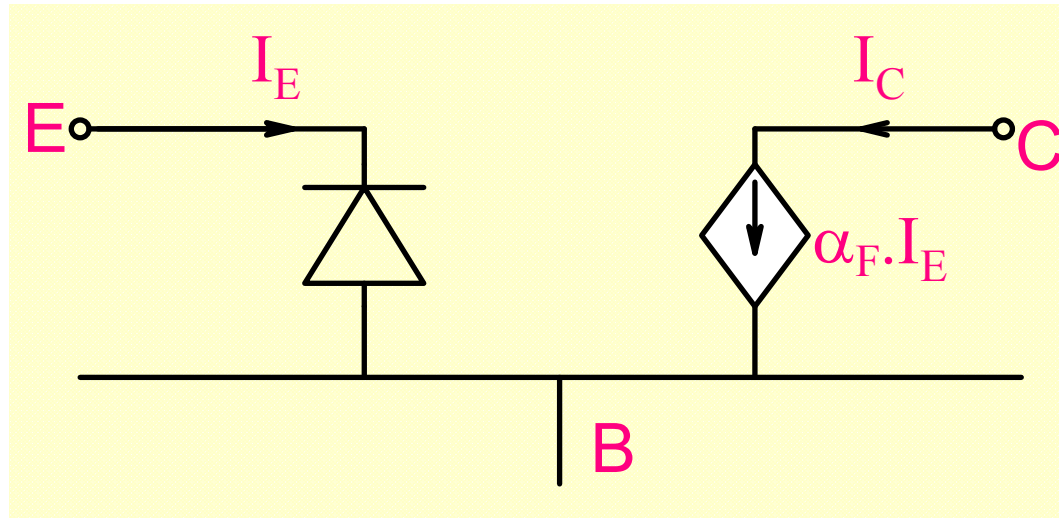

Forward Active Mode





# Forward Active Mode




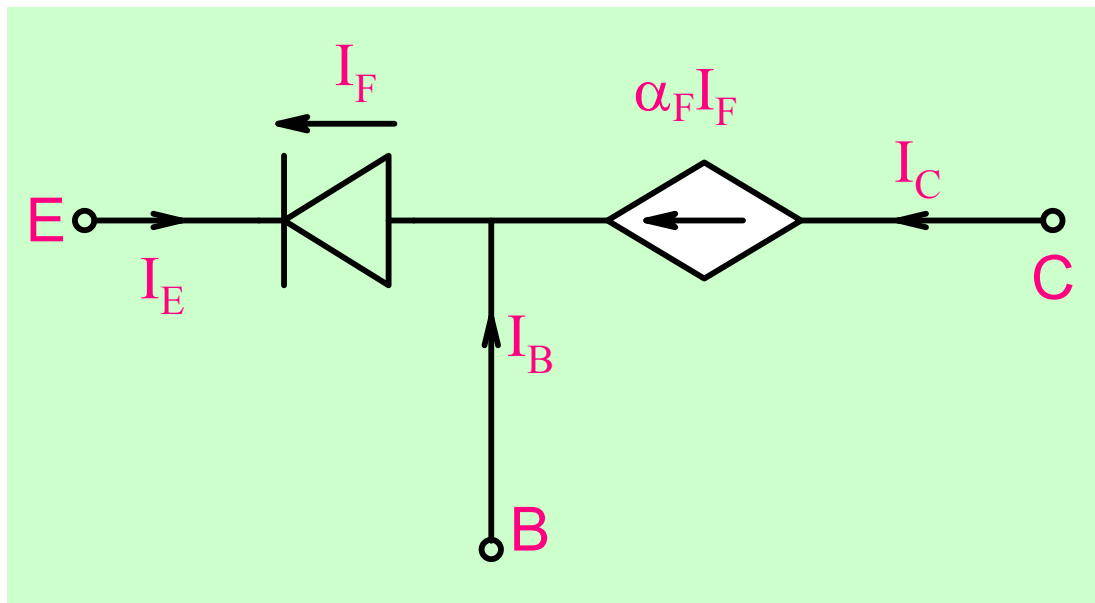
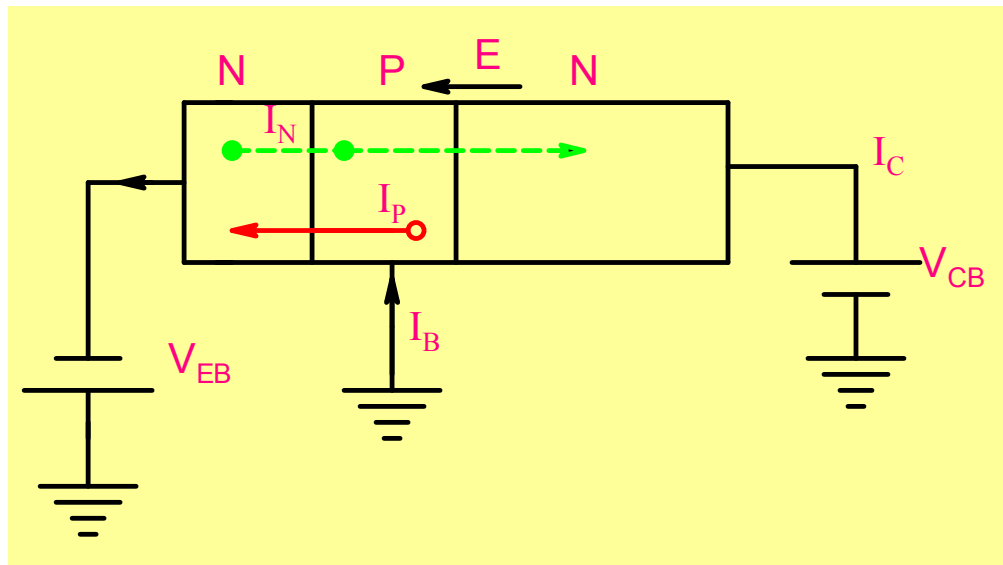


$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

## Reverse Active Mode

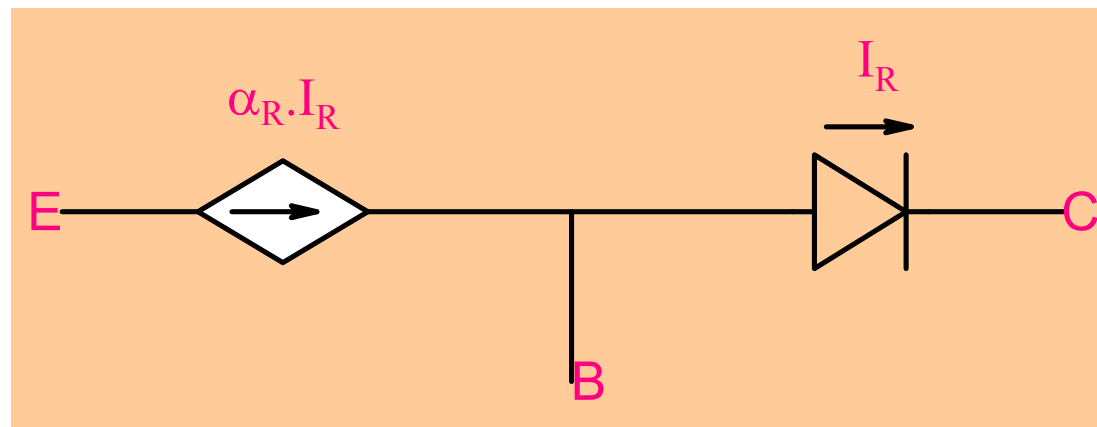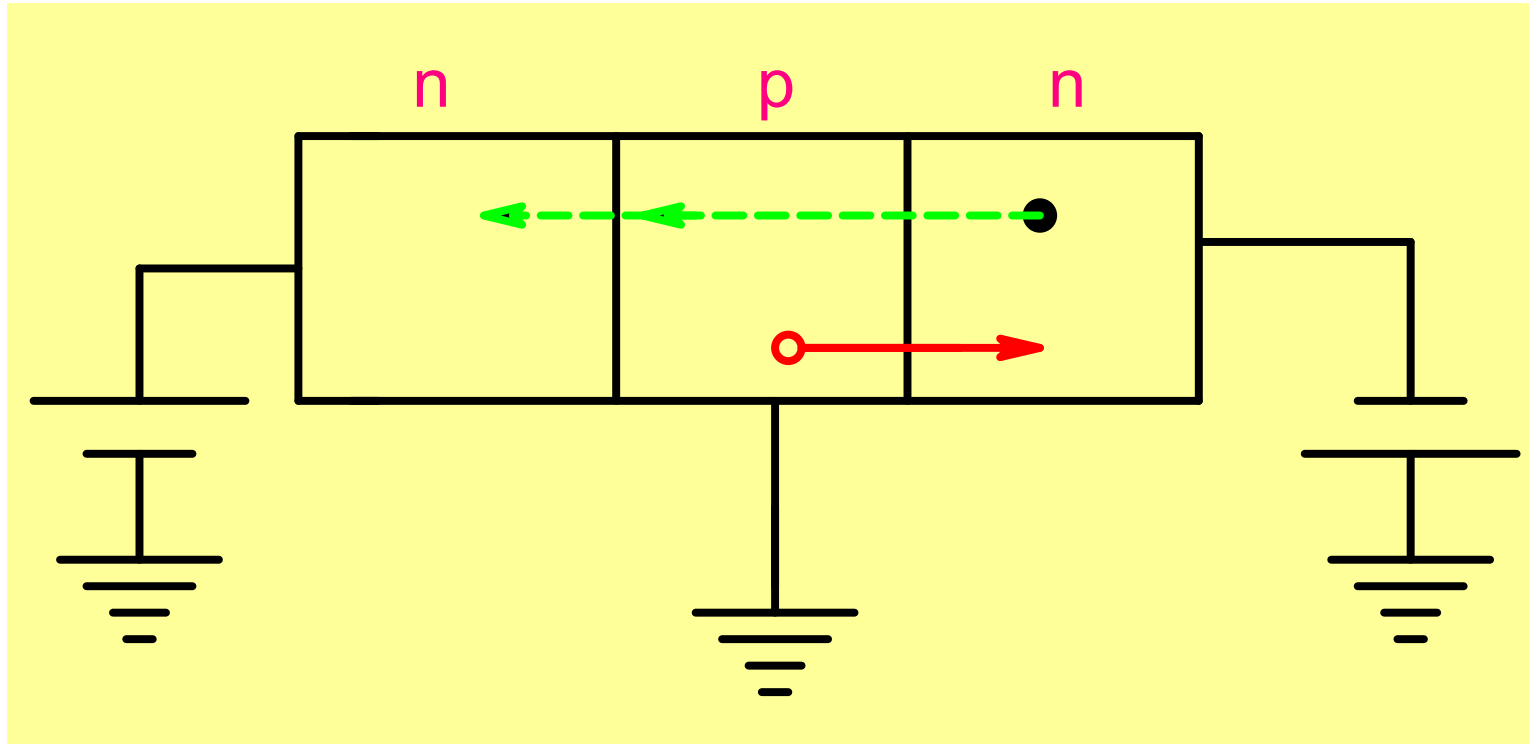
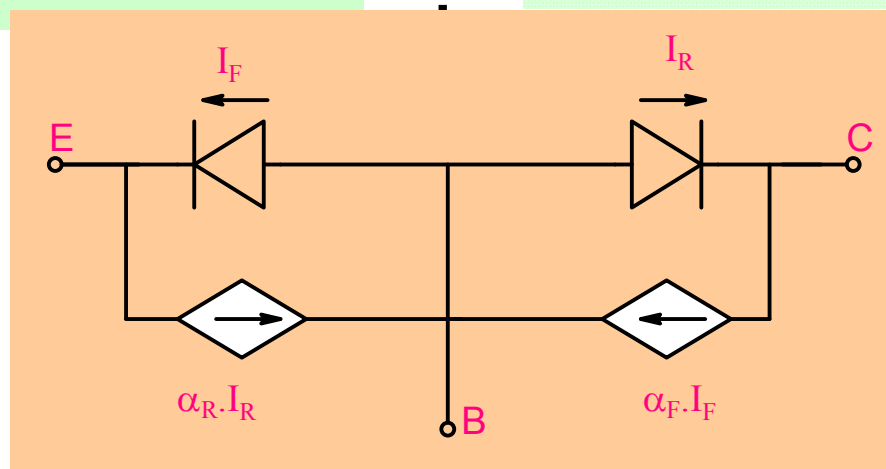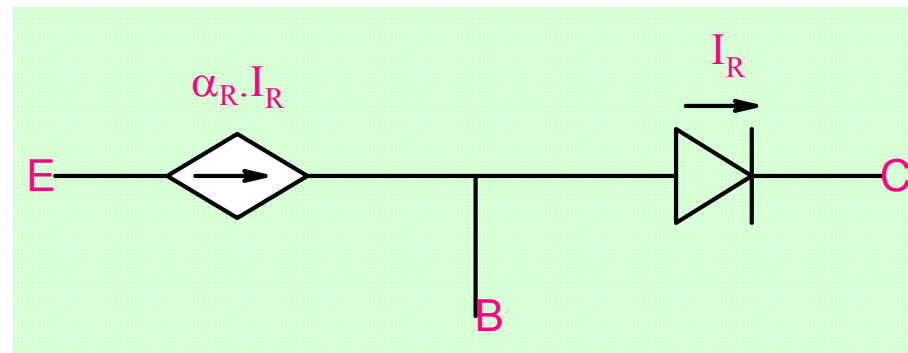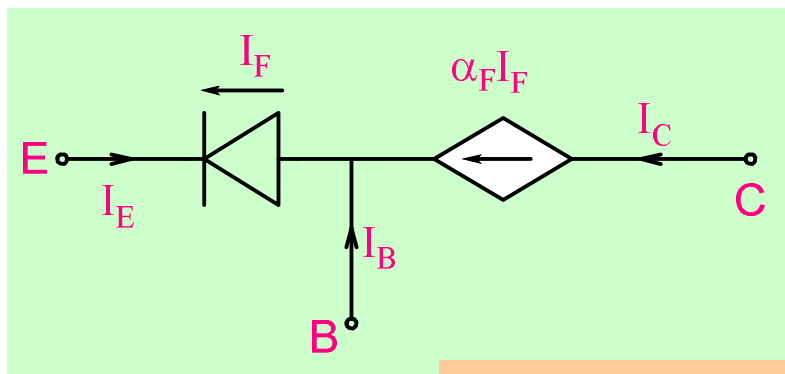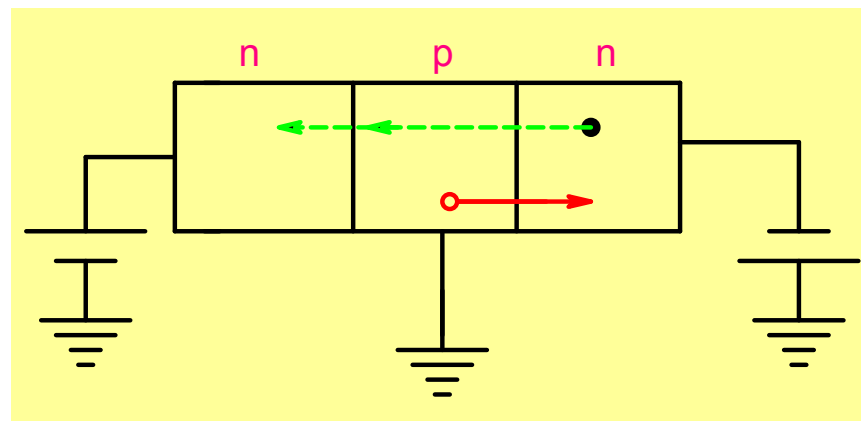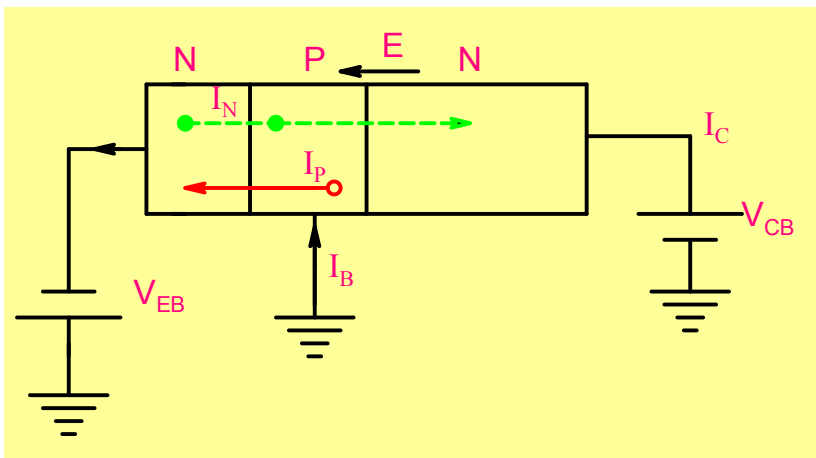
$$\beta_R = \frac{\alpha_R}{1 - \alpha_R}$$



# Ebers Moll Model

